

Lecture 26

EE 320

May 7, 2014

Review past exams, H.W.s, & Quizzes

Review Op-Amps

Topologies

imperfections

offset voltage

finite gain

$$A_{olDC} = 100$$

$$V_{OS} = 10 \mu V$$

$$V_{out} = ?$$

$$V_{out} = A_{olDC} (V_+ - V_-)$$

↓
= 1V



$$V_{out} = \frac{1K}{1K + 10K} = V_+$$

11

$f_{un} = G_{AV} \cdot Bw = \text{unity-gain frequency}$

$20 \log 10^3$



$A_{OL} = 1,000$

$10^6 = 10^3 \cdot f_{3dB,CL}$

$f_{un} = 1 \text{ MHz}$

$f_{3dB,CL} = 10^5$
 $= 100 \text{ kHz}$

Sketch the frequency resp. of the op-amp

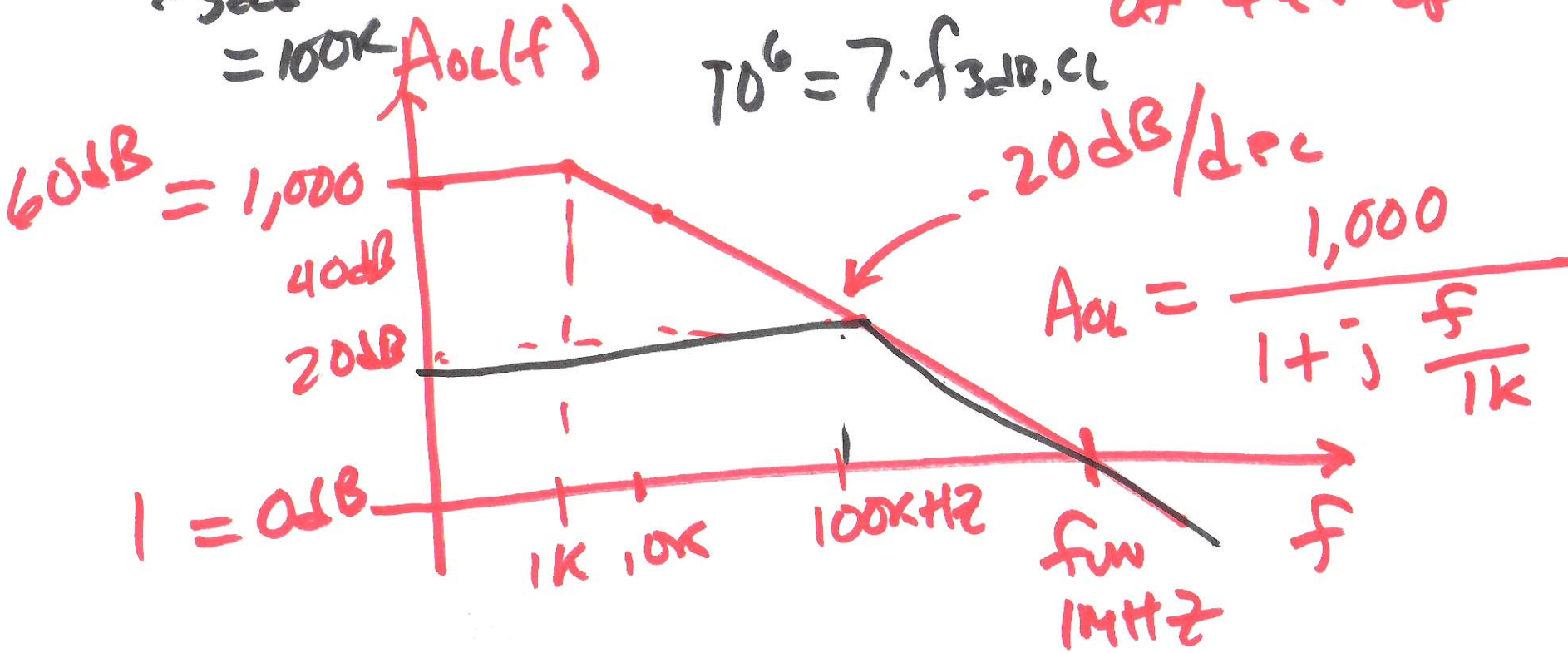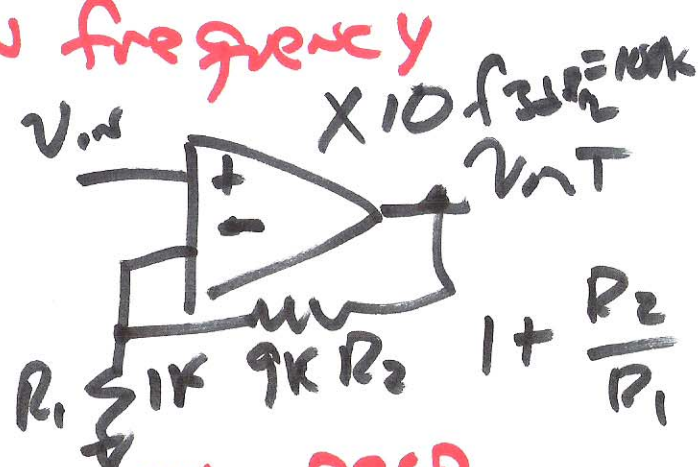


2)

RC - CKTS

SPICE netlists!

Mag & phase

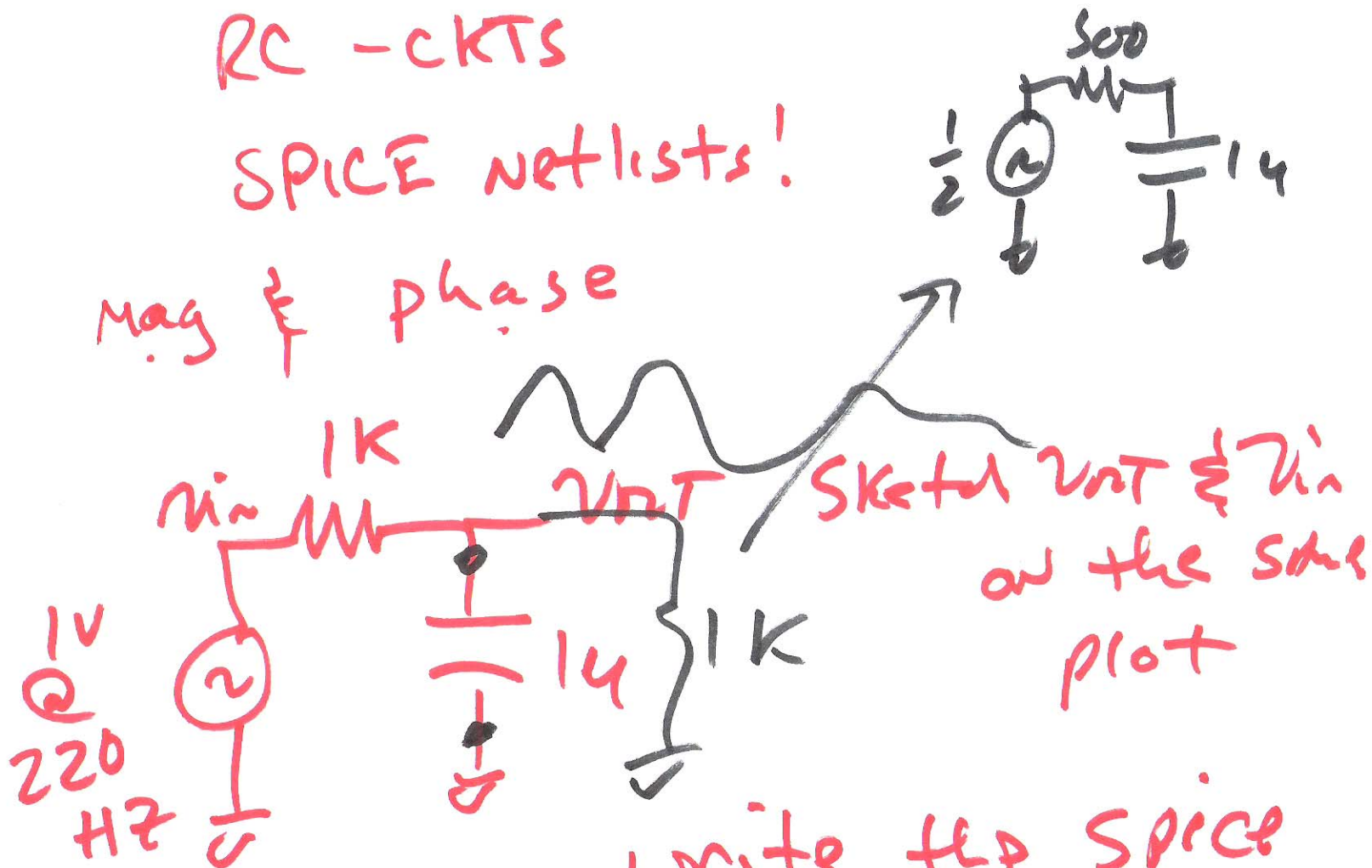

write the SPICE NETLIST

Comment line

`kn v1 0 DC0 S.W 0 1 220`

`R1 kn vnt 1k`

`C1 vnt 0 1u`

`.TRAN 10ns`
`.end`




3)

Semiconductors


N-type





Resistor problem
PN-junctions (diode)

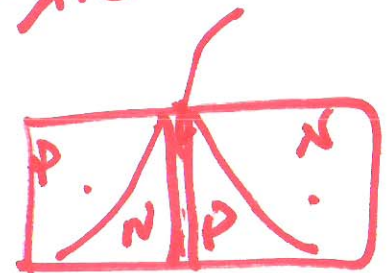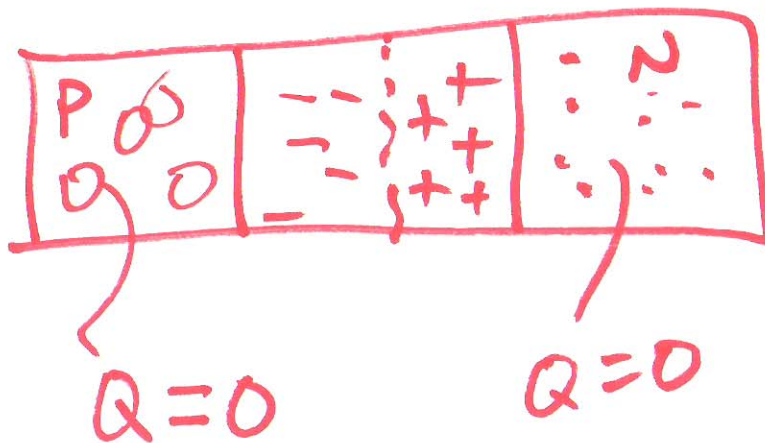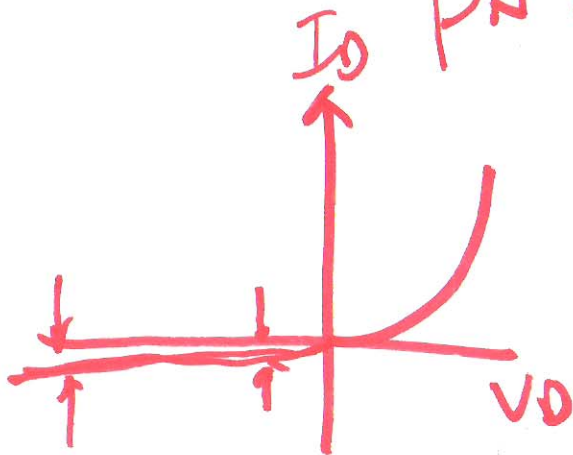


4)

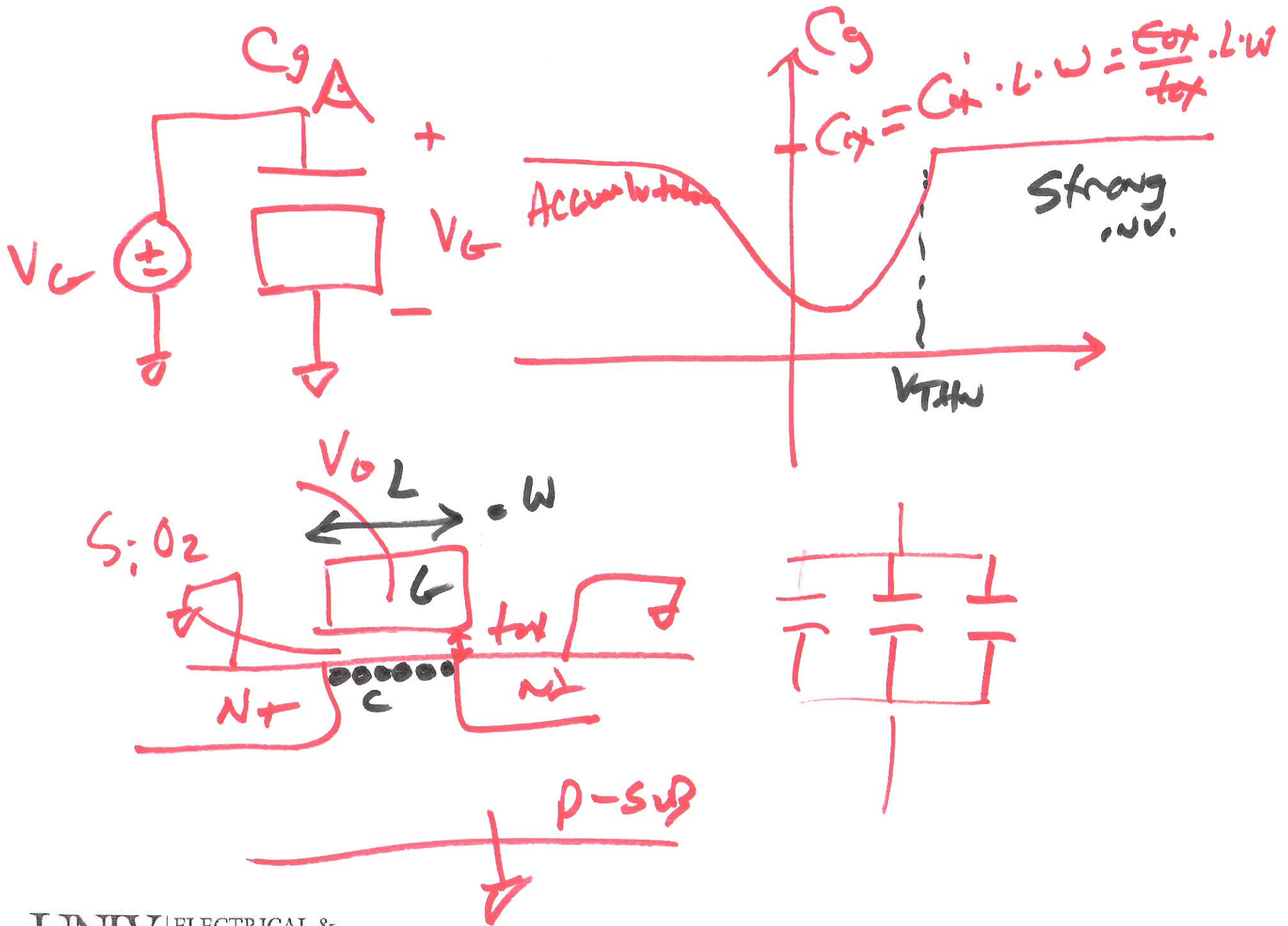

5)

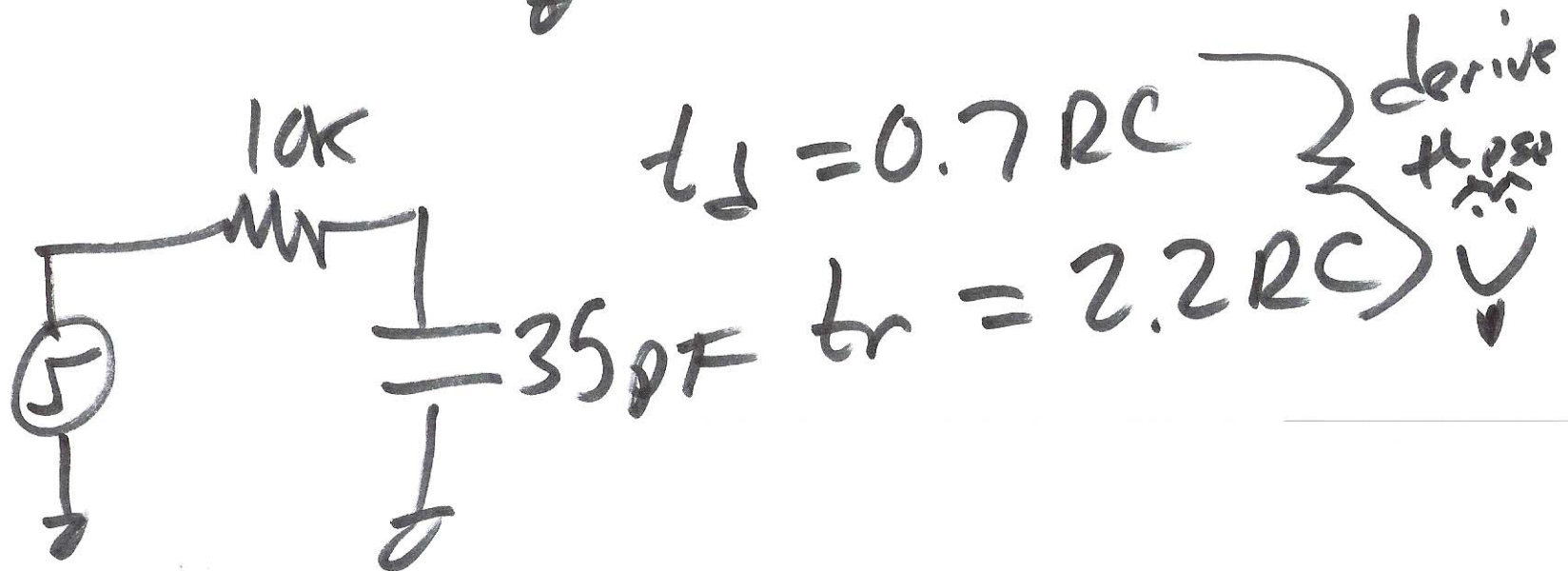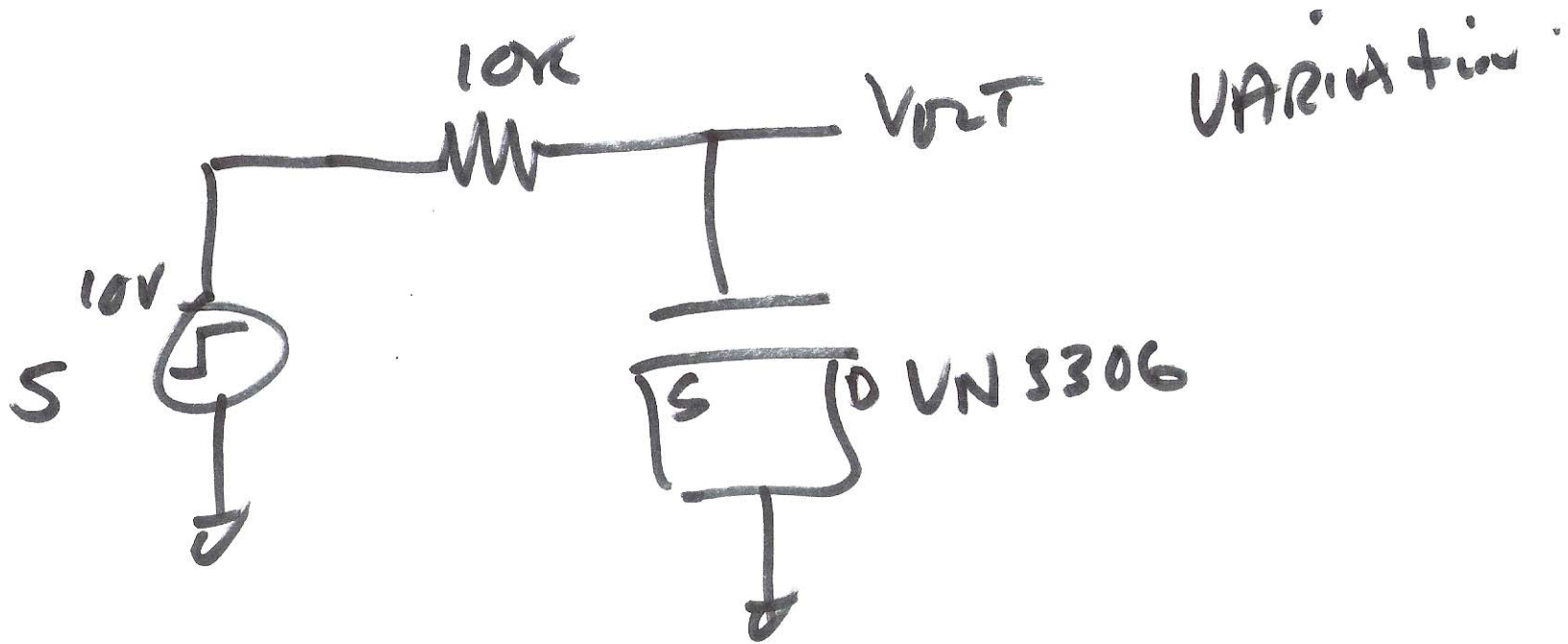



6)


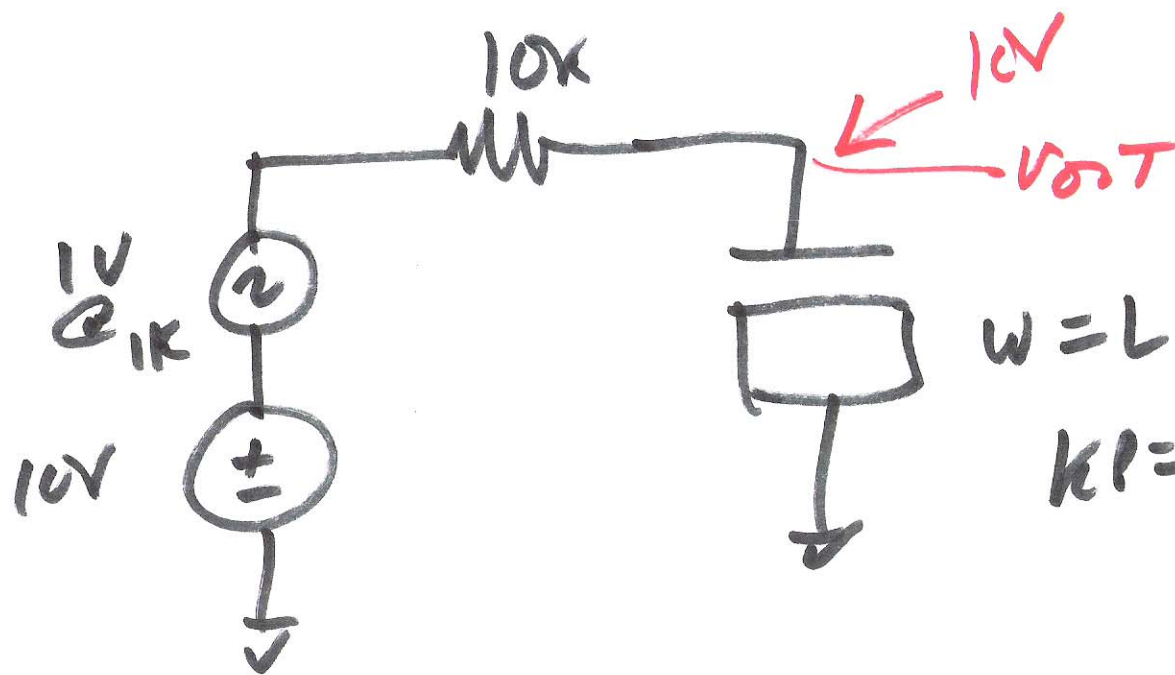


$W = L = 100 \mu\text{m}$

$k_p = 120 \mu\text{A/V}$


$C_{ox} = 2.5 \text{ fF}/\mu\text{m}^2$

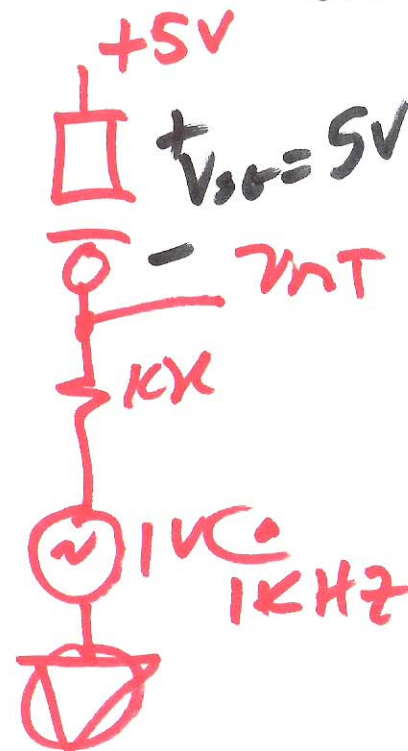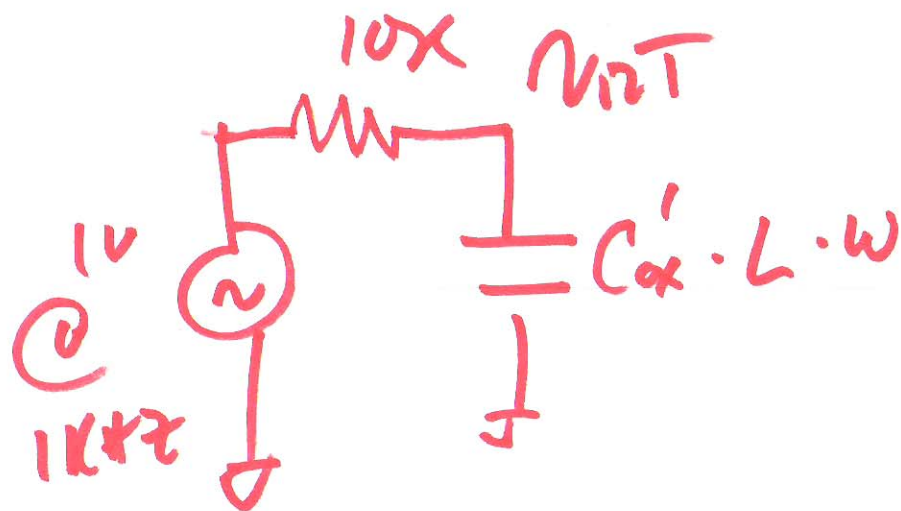

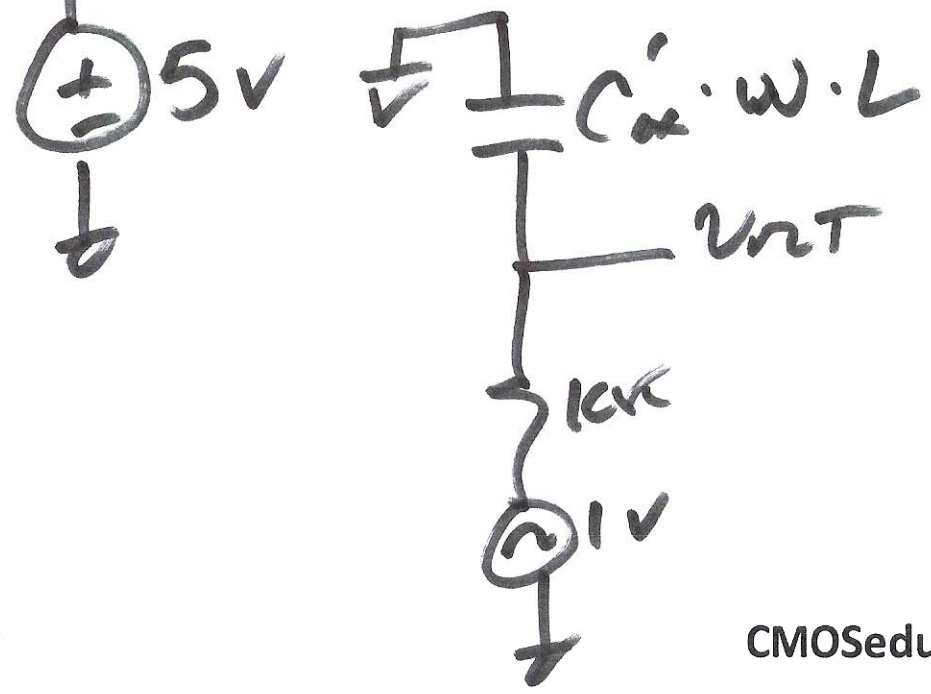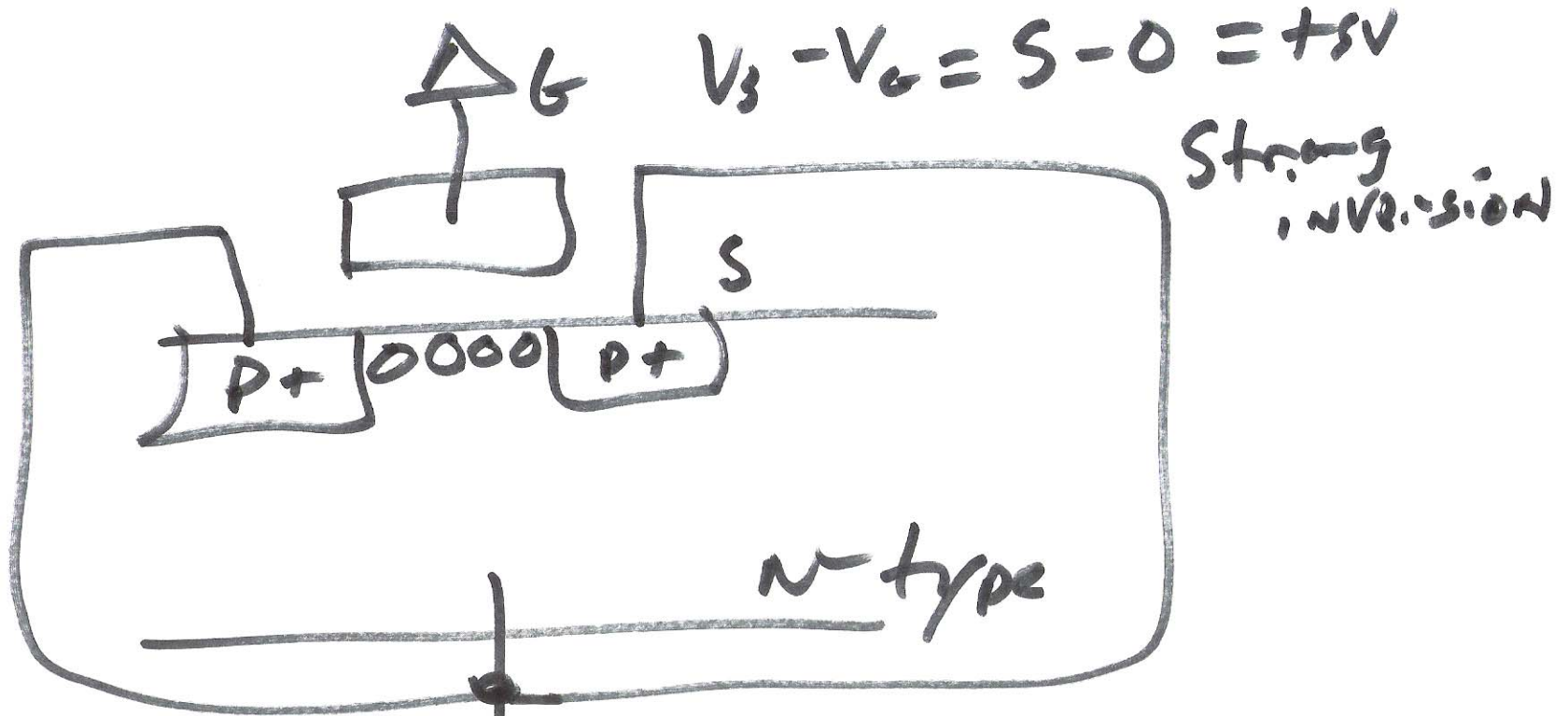


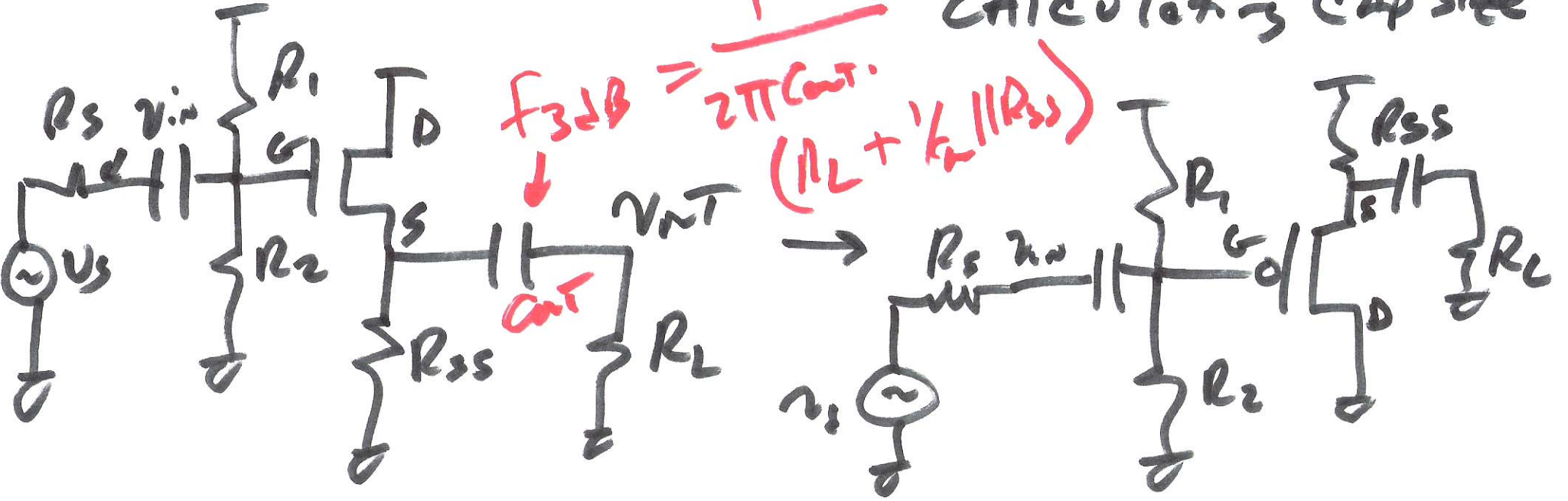8)

GAINS, INPUT RES., OUTPUT RES., CALCULATING CAP SIZE





Derive g

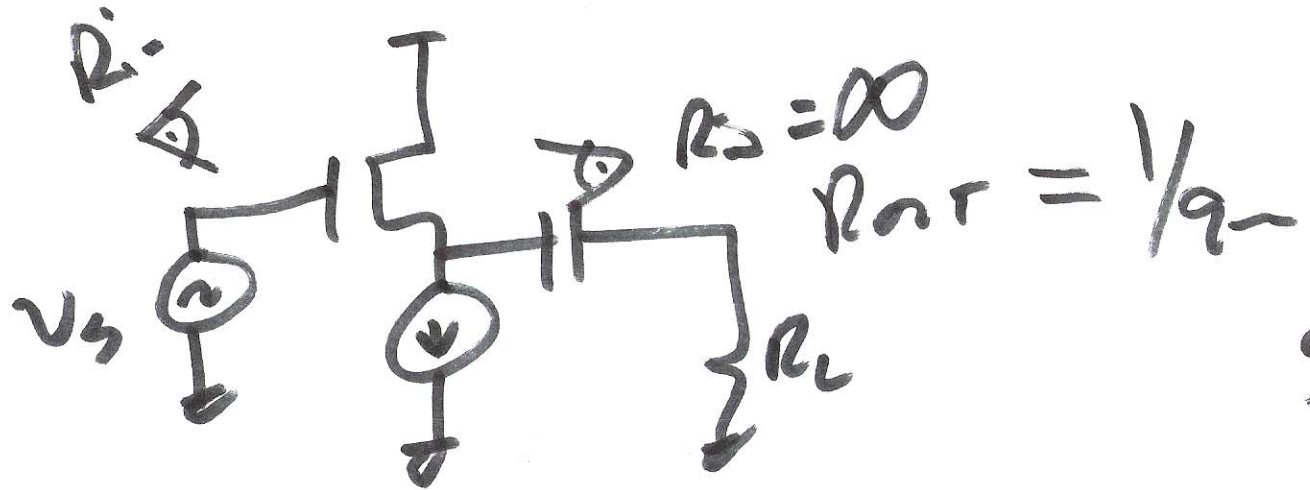

S.F.

9)

C.S.

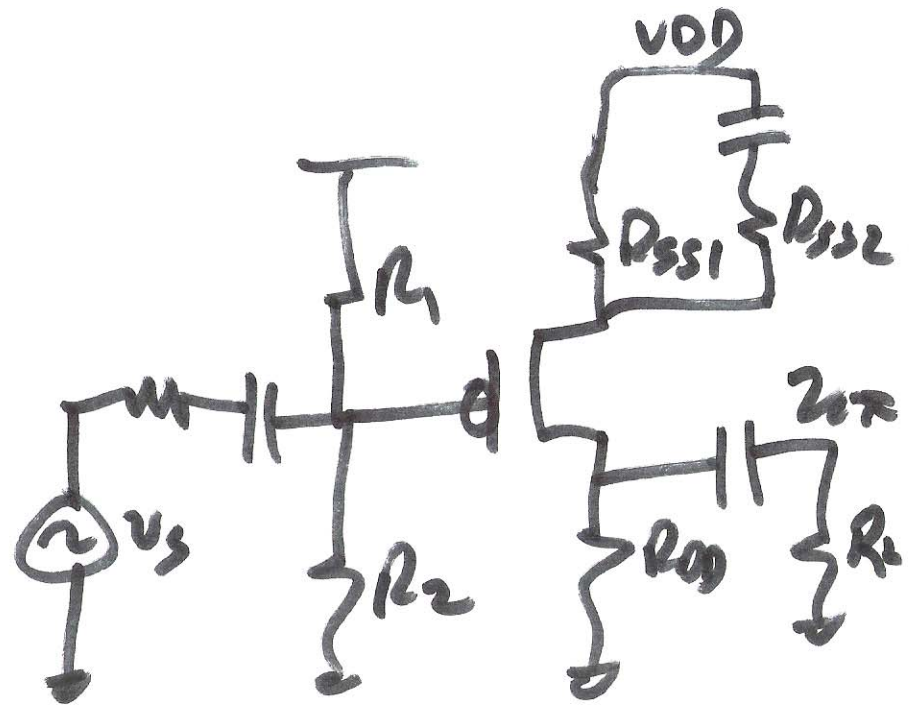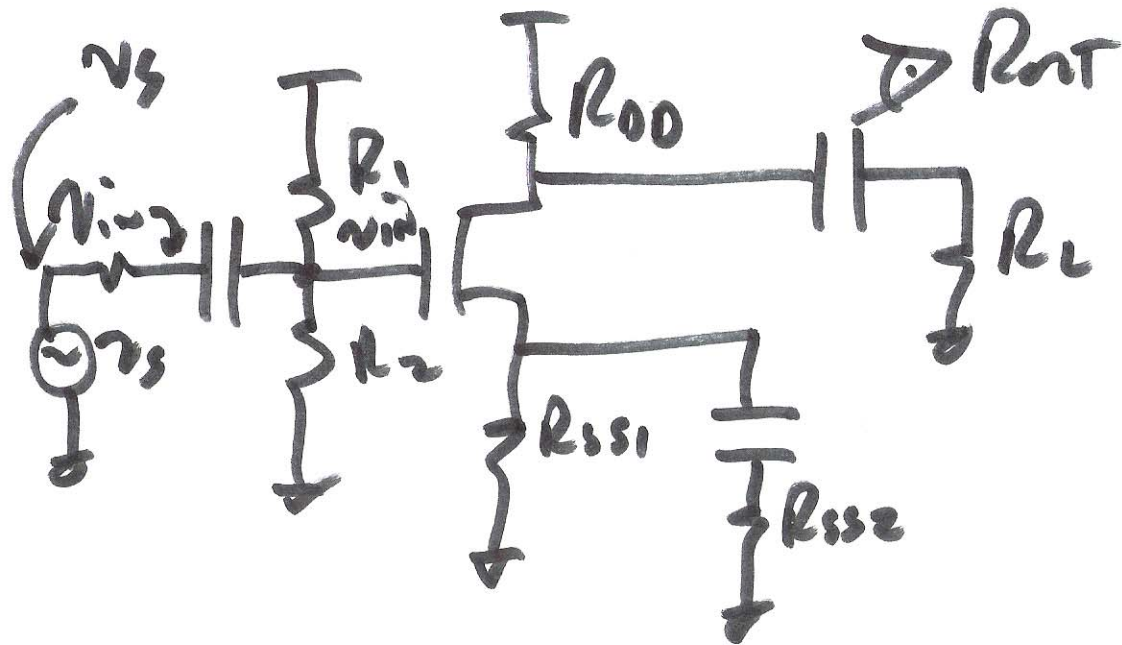

$$R_{in} = R_1 \parallel R_2$$

$$A_v = \frac{v_{out}}{v_{in}} =$$


$$R_{out} = R_{DD}$$

$$\frac{R_{DD} \parallel R_L}{\frac{1}{g_m} + R_{SS1} \parallel R_{SS2}}$$

$$\frac{v_{in}}{v_s} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s}$$

I can derive this!

C.G

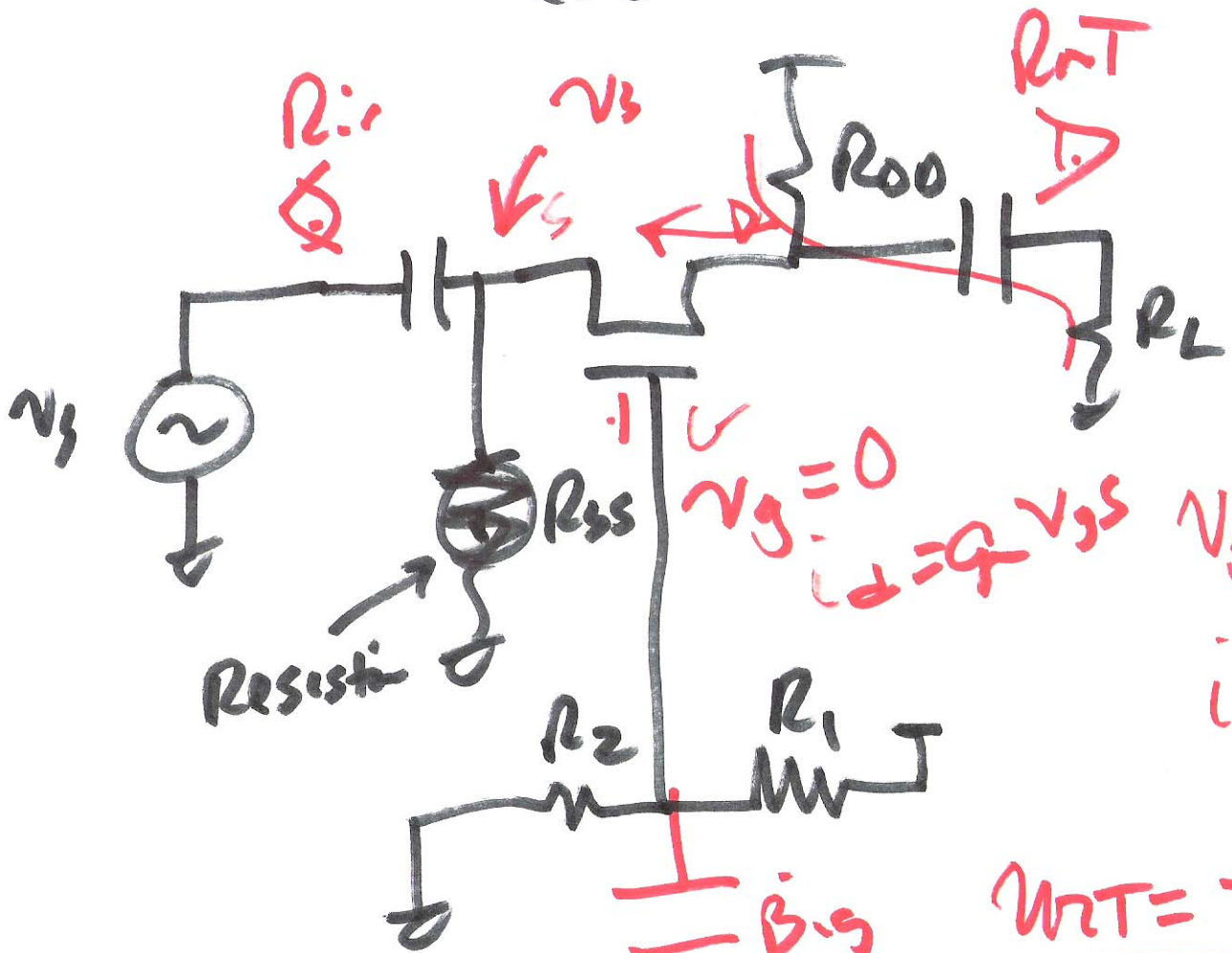

$$R_{in} = R_{ss} \parallel \frac{1}{g_m}$$

$$R_{out} = R_{oD}$$

$$v_g = 0$$

$$i_d = g_m v_{gs}$$

$$v_{gs} = -v_s$$


$$i_d = -g_m v_s$$

$$v_{oT} = -i_d \cdot R_{oD} \parallel R_L$$

$$\frac{v_{oT}}{v_s} = g_m R_{oD} \parallel R_L$$


$$\frac{R_{oD} \parallel R_L}{\frac{1}{g_m}} =$$

11)

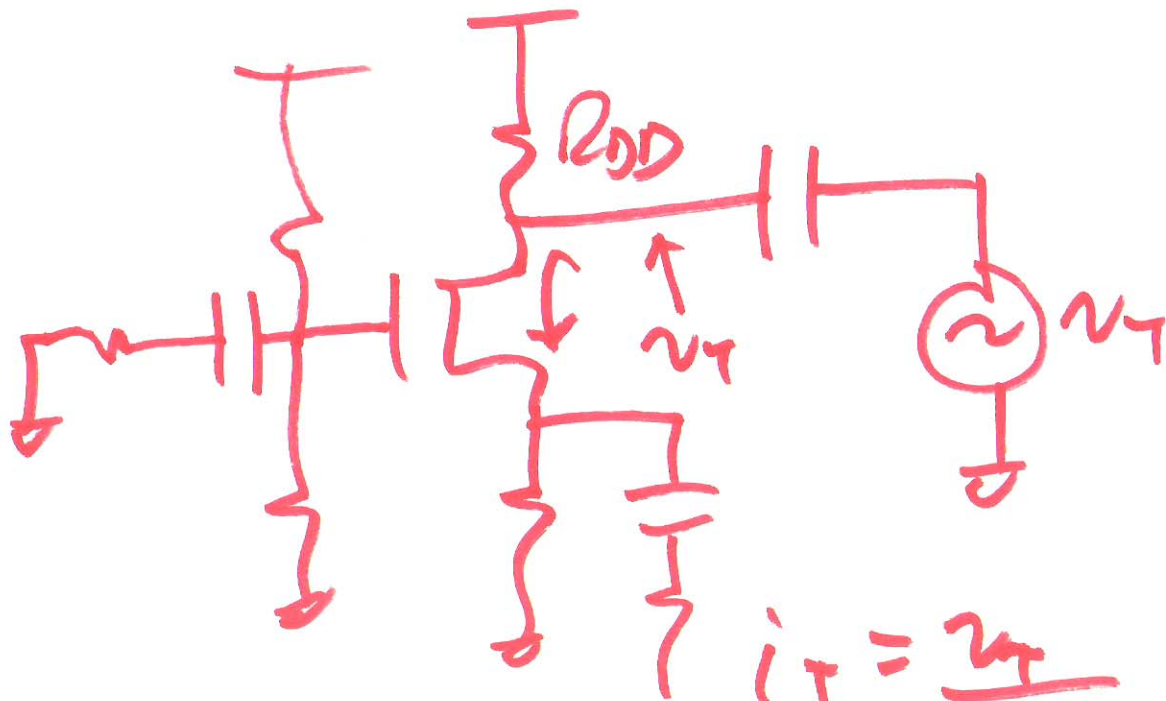


$$i_T = \frac{v_{in}}{R_{OD}}$$
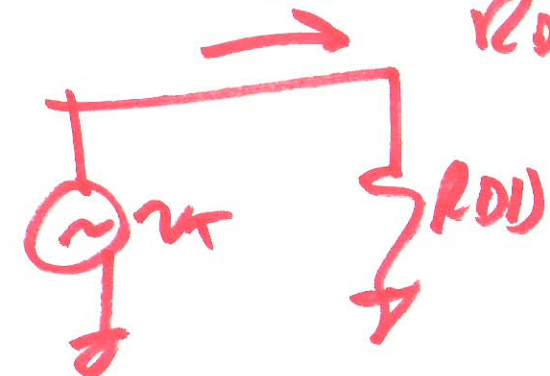
$$\frac{v_{in}}{i_T} = R_{OD} = R_{out}$$



12)

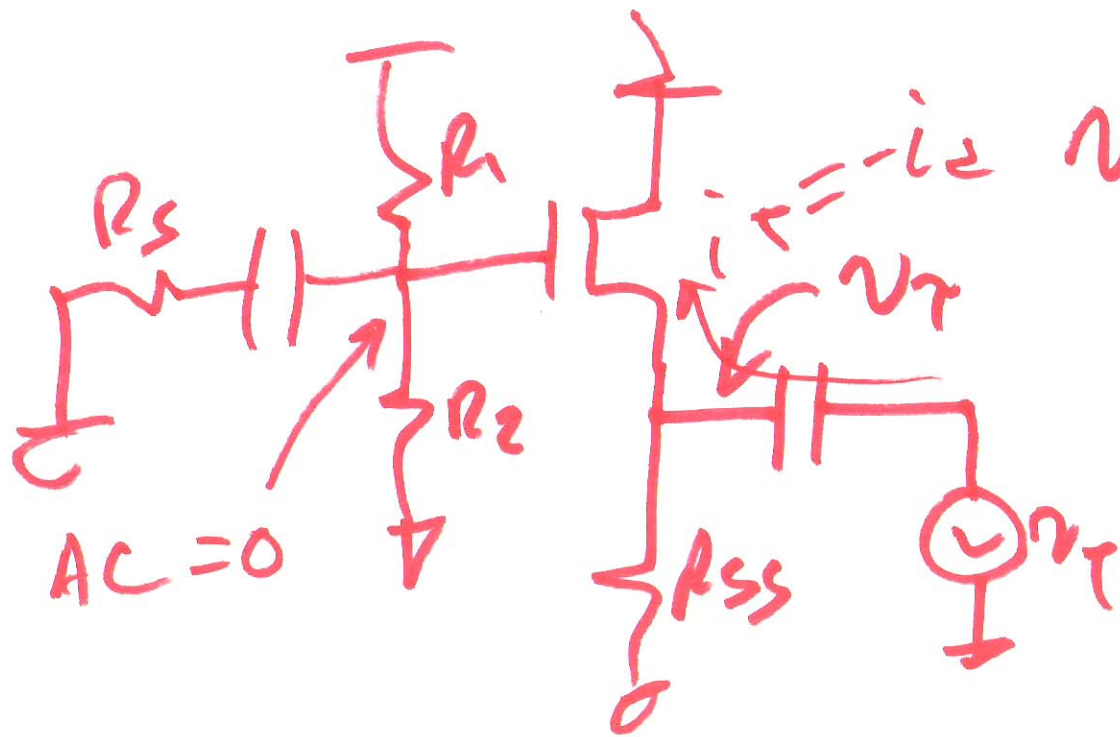

$$i_T = -i_D = g_m v_{GS} = g_m (-v_T)$$

$$\frac{v_T}{i_T} = \frac{1}{g_m}$$

$$R_{out} = R_{SS} \parallel \frac{1}{g_m}$$