

# Lecture 2 1/27/14


EE 320

OP-AMPS

NON-INVERTING at POS. I/P

$V_P$

$V_{in}$

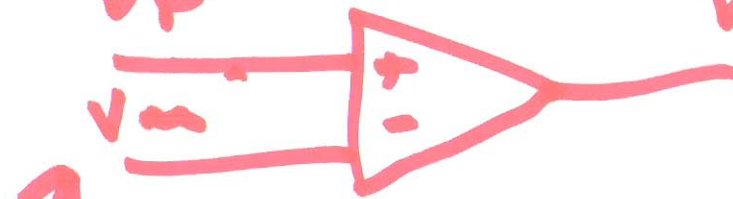


$$V_{OUT} = A_{OL} (V_P - V_{-})$$


$$A_{OL} \rightarrow \infty$$

$$V_P = V_{in}$$


INVERTING INPUT

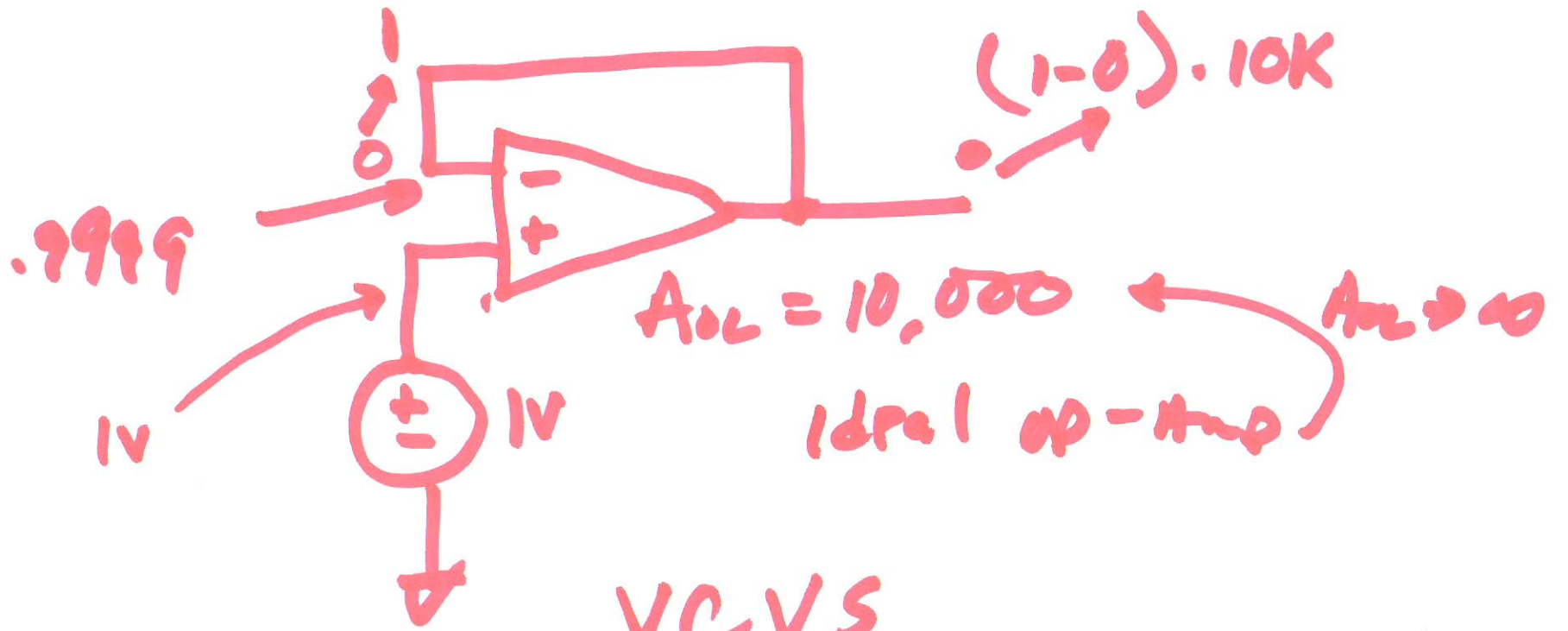

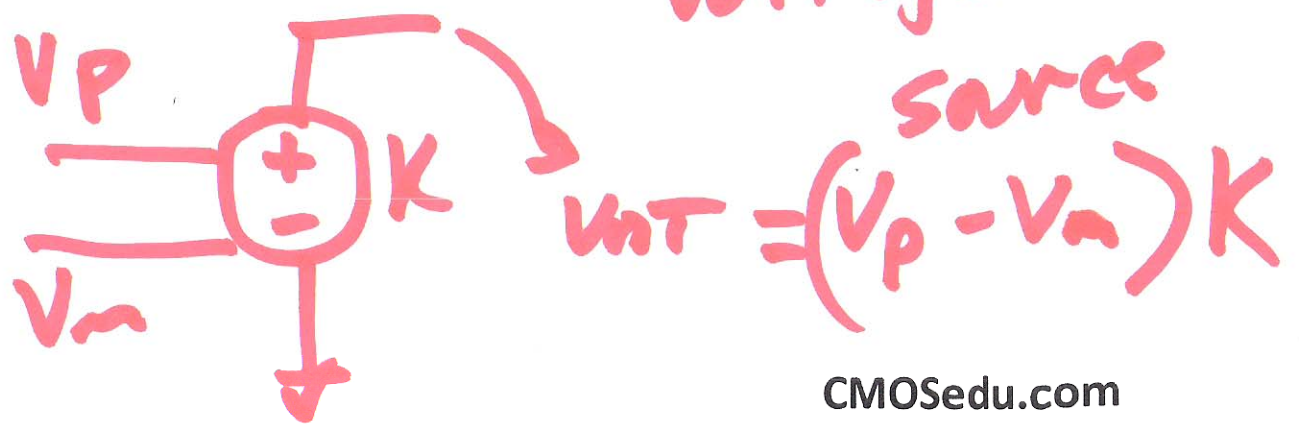VCVS  
 Voltage Controlled  
 Voltage Source



2)

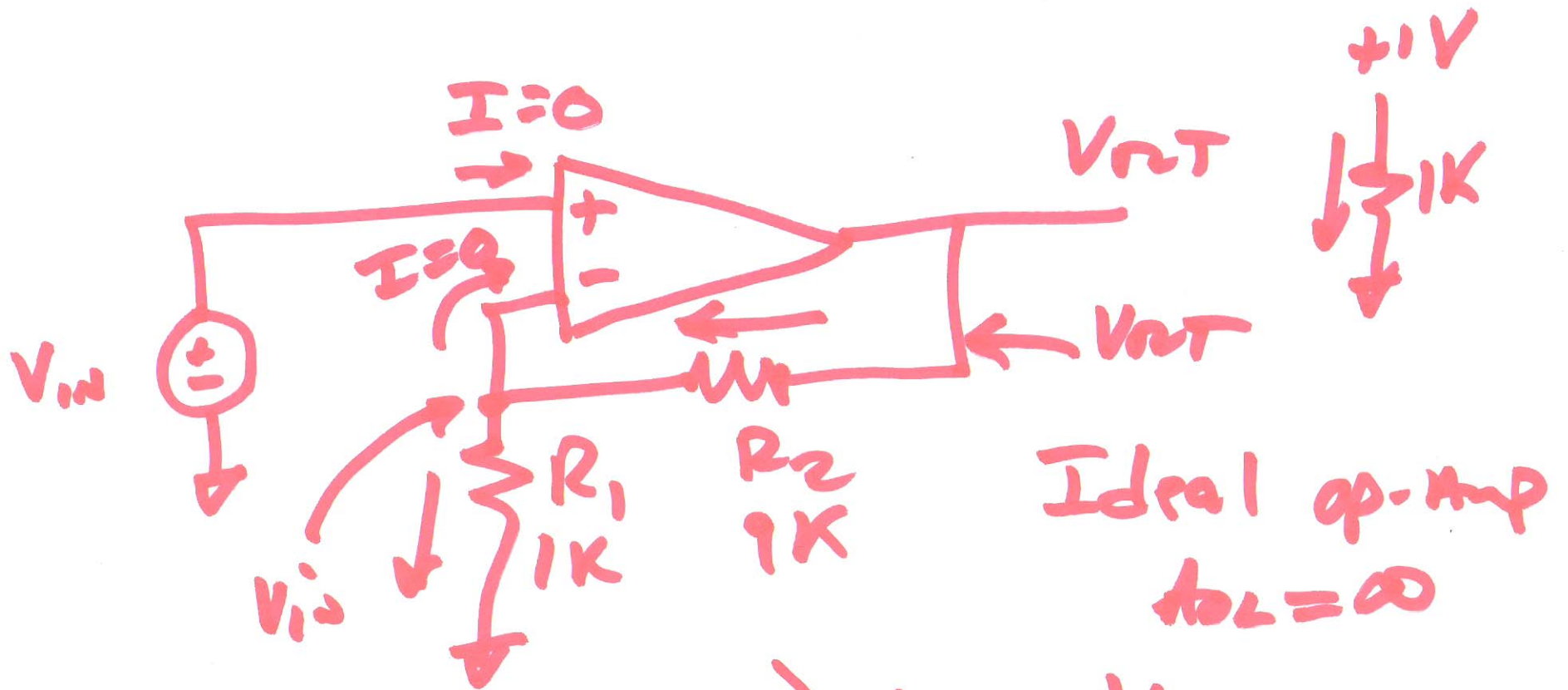

$$\frac{V_{in}}{R_1} = \frac{V_{OUT} - V_{in}}{R_2}$$

$$V_{in} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{OUT}}{R_2}$$


1)  $V_p = V_m$

2) KCL @ minus input

$$\frac{V_{OUT}}{R_2} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$$

3)


# NON-INVERTING OP AMP

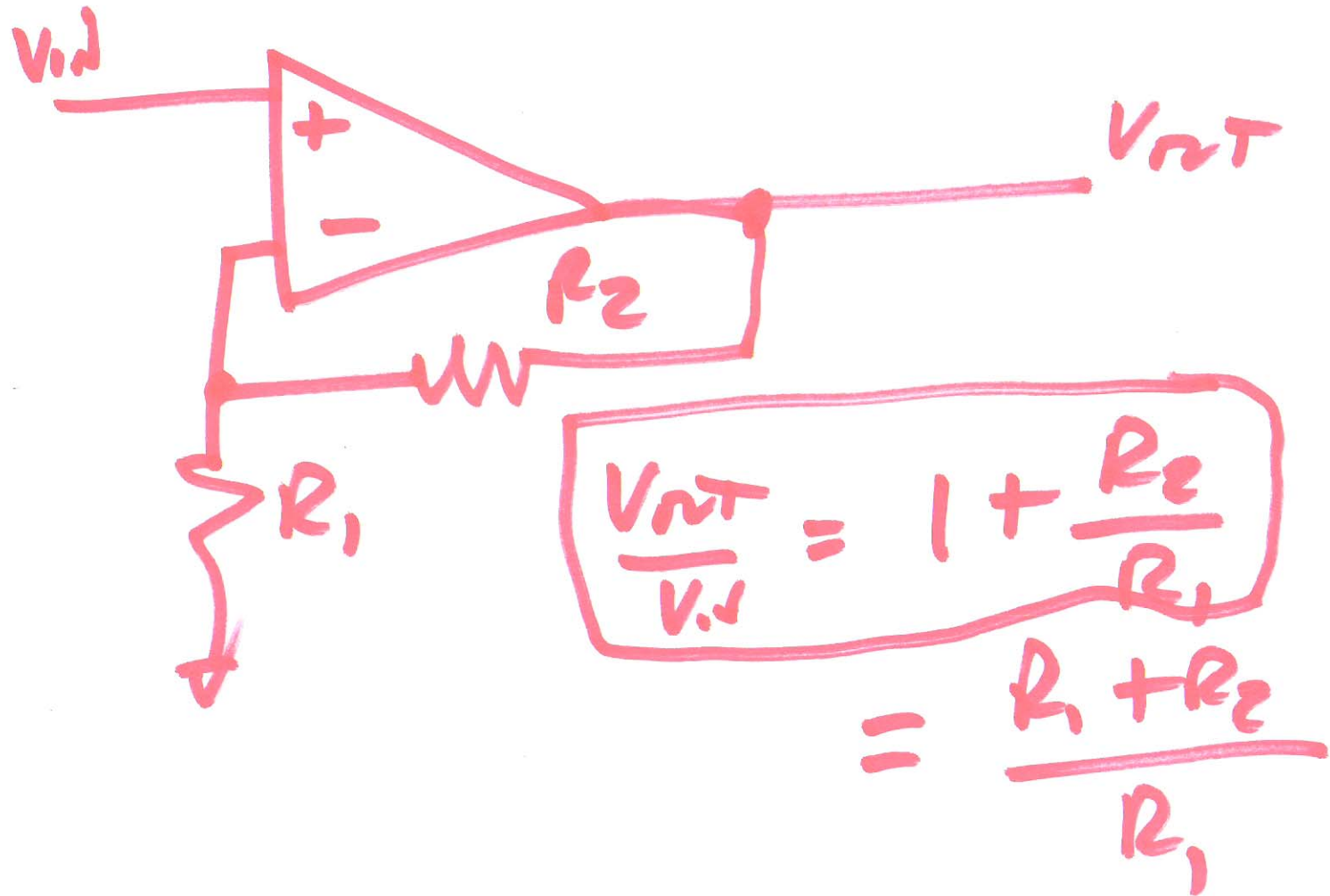



# INVERTING op-Amp

topology

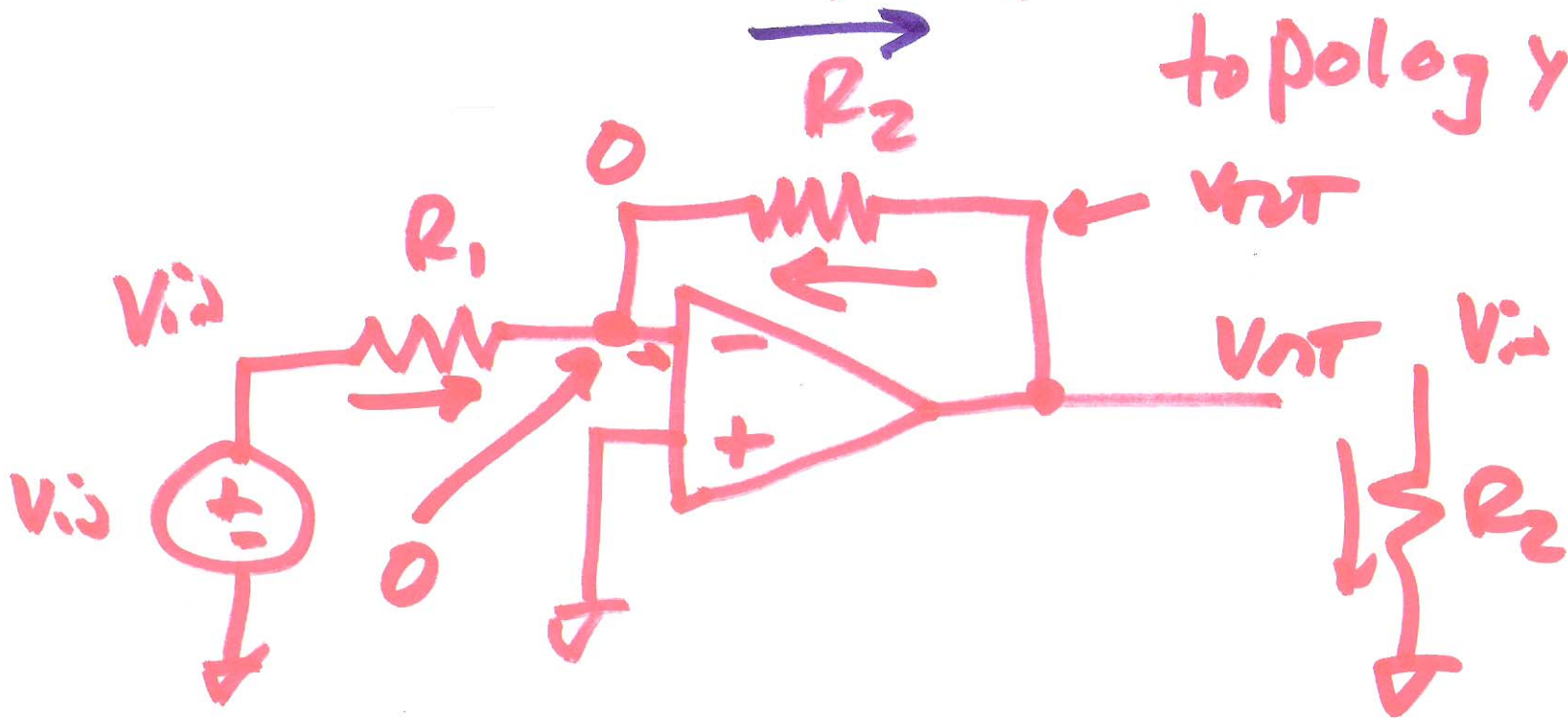

$$\frac{V_{in}}{R_1} + \frac{V_{out} - 0}{R_2} = 0$$


$$\frac{V_{in}}{R_1} = \frac{0 - V_{out}}{R_2}$$


$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$




$$1 + \frac{10K}{1K} = 11$$

$$-\frac{10K}{1K} = -10$$

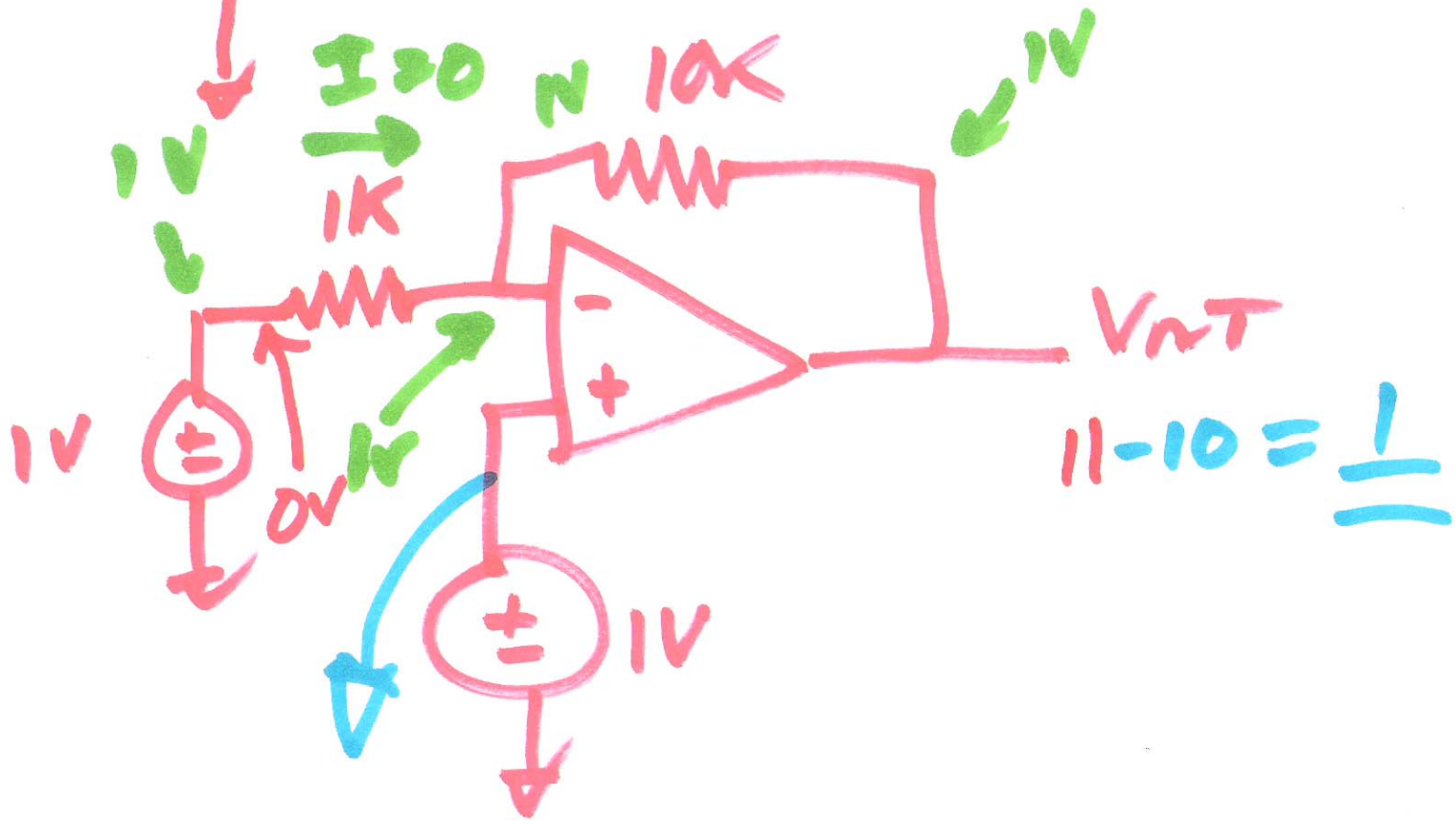

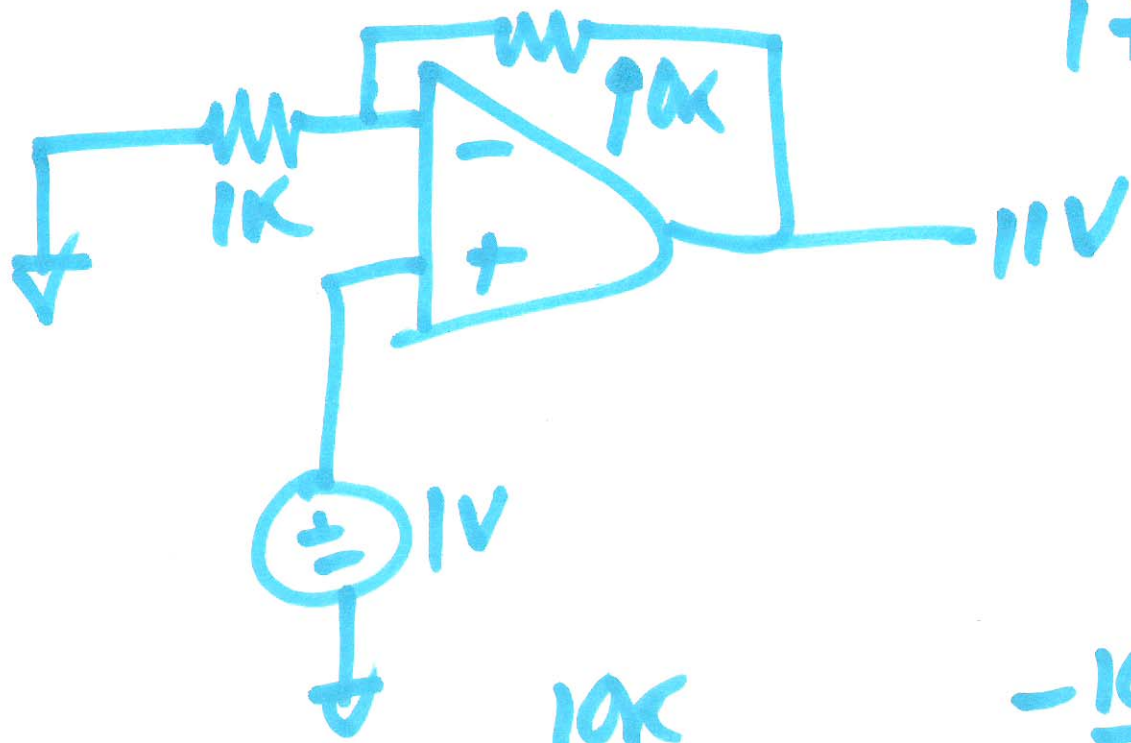


$$1 + \frac{10K}{1K} = 11$$

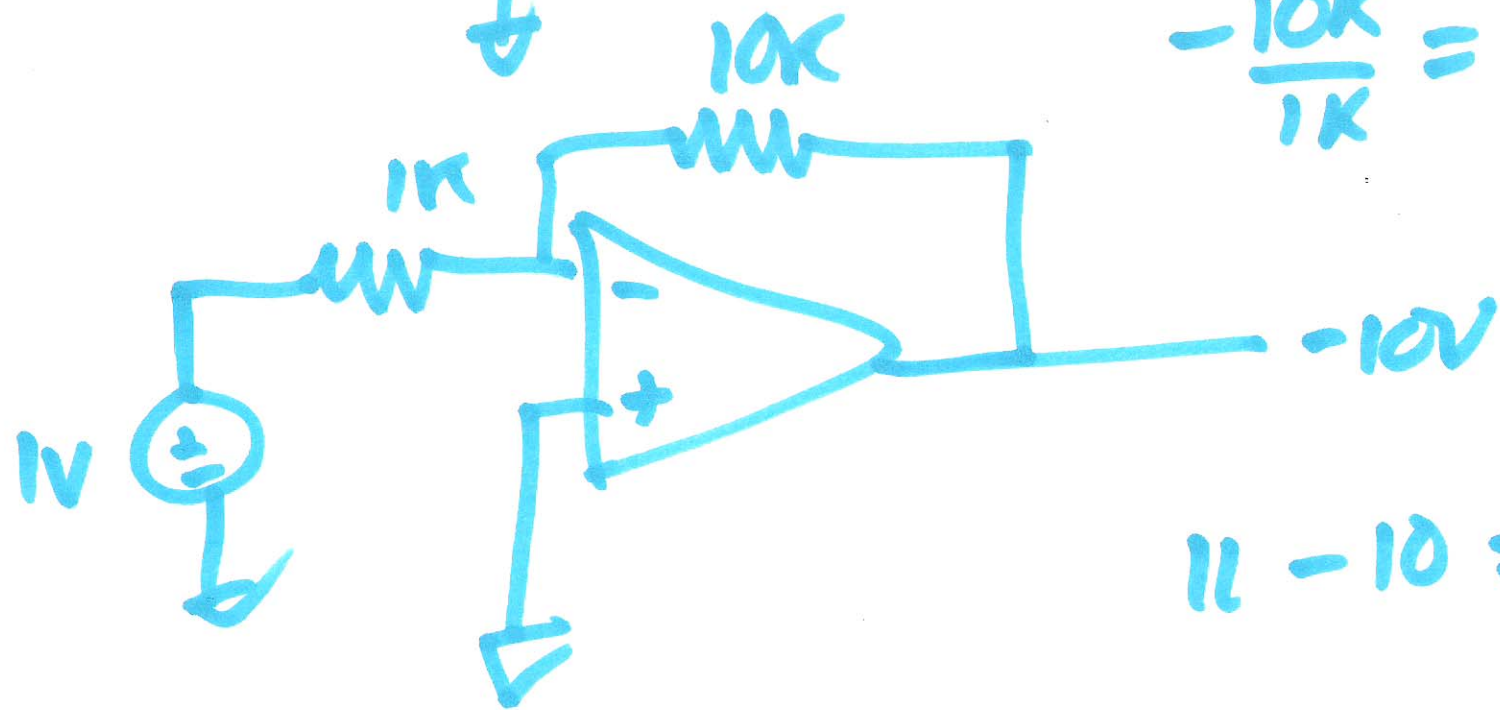

$$-\frac{10K}{1K} = -10$$

$$11 - 10 = \underline{\underline{1V}}$$




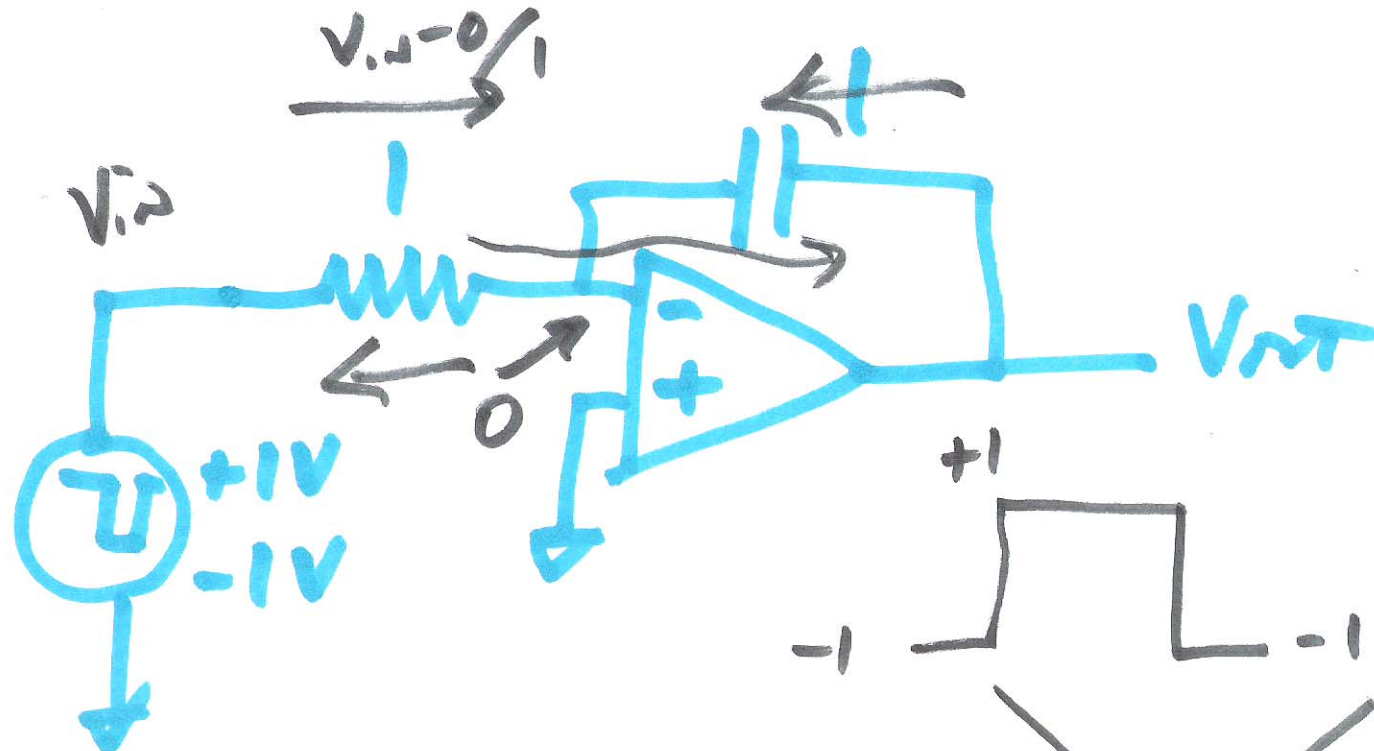

high at 1V for 1s  
 low at -1V for 1s

8)



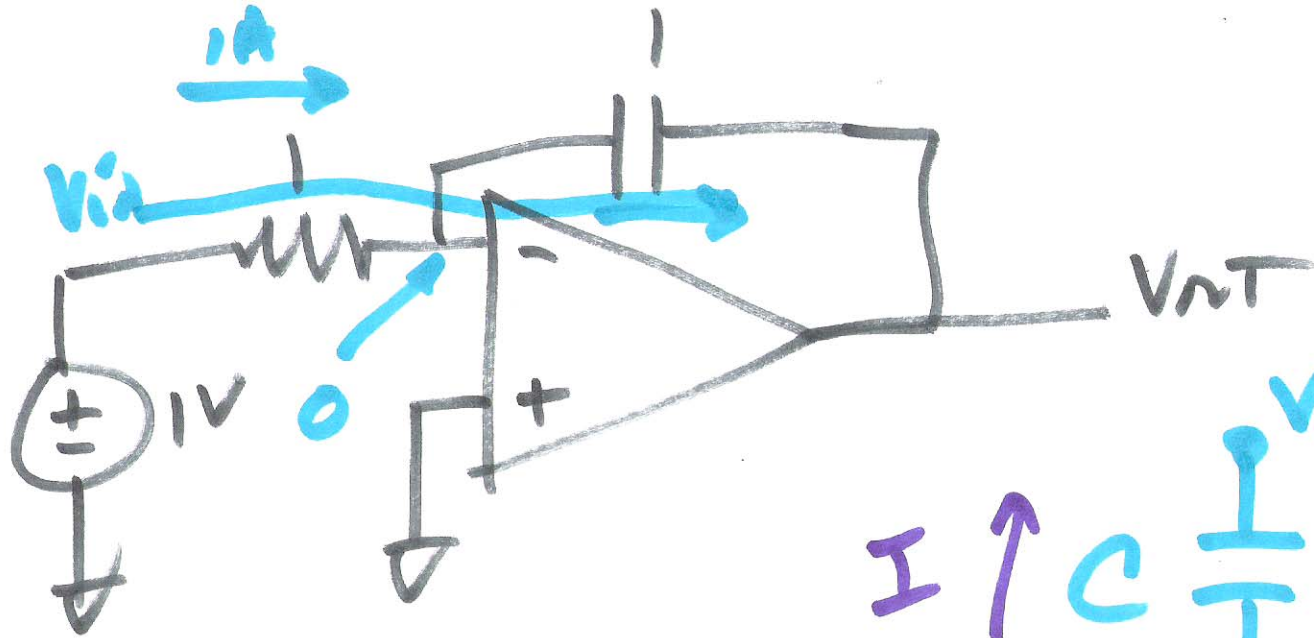


$$I \uparrow \quad C \quad \begin{matrix} \uparrow V_c \\ \downarrow I \end{matrix}$$

$$V_c = -\frac{1}{C} \int I dt$$

$$= -\frac{1}{C} I \cdot t$$


$$= -\frac{1V}{5} t$$

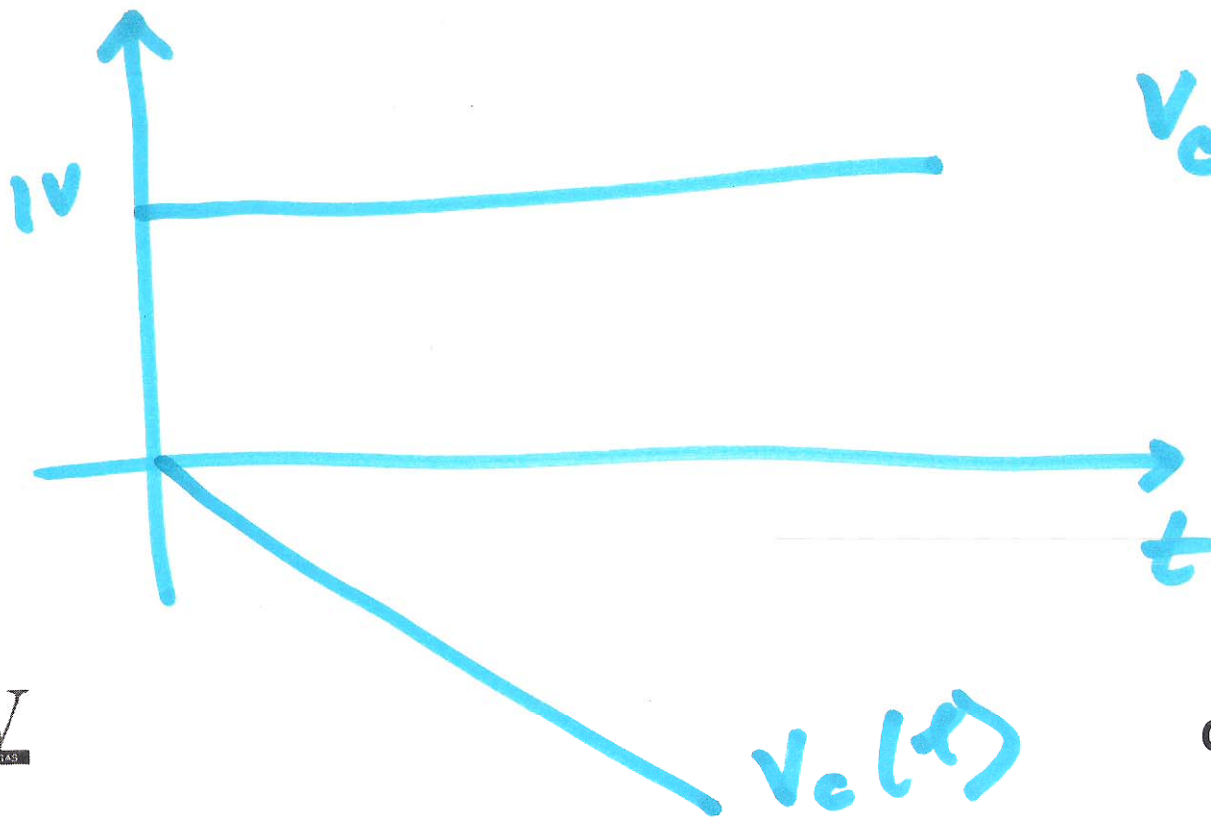

EX. QUIZ question

Assume


ideal  
op-amp,  $1/2$ - $3$

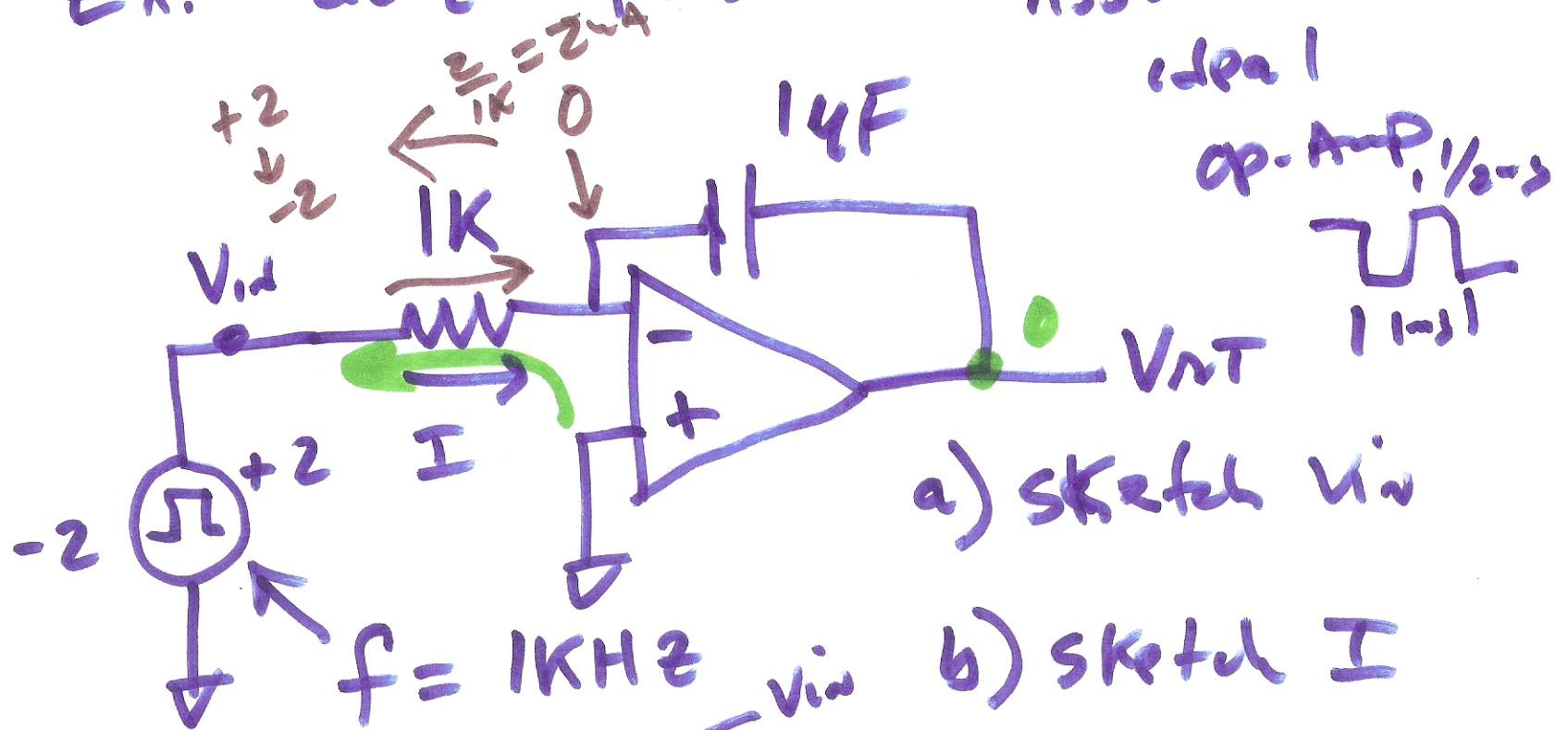

a) sketch  $v_{in}$

b) sketch  $I$

c) sketch  $V_{out}$

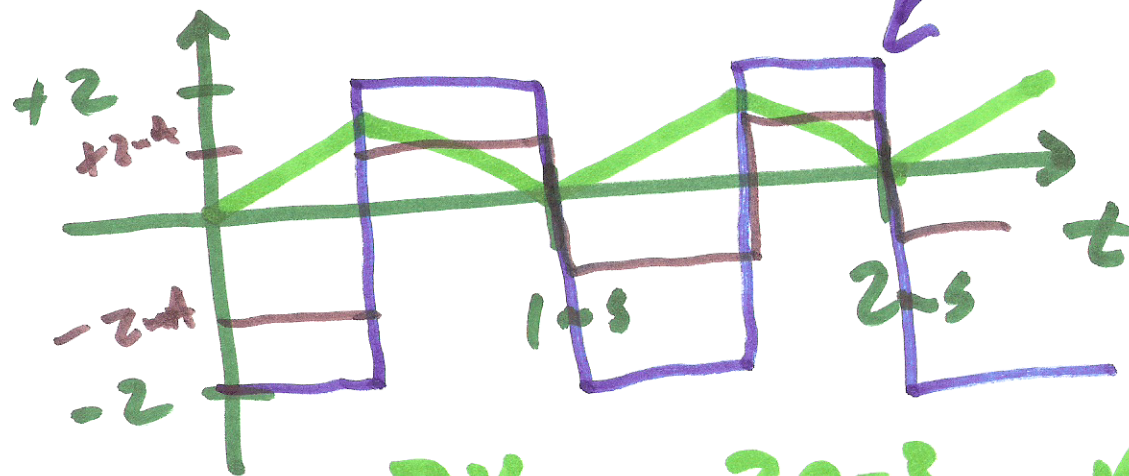

$$\frac{2V}{ms} = \frac{2e-3}{1e-6}$$

$$V_{out} = \frac{1}{C} \int I \cdot dt$$

$$V_{out} = \frac{2e-3}{14F} \cdot t$$