

EE 320

Lecture 4

2/3/14


→ TBE B310 H.W.
GRADER

By 4:00
on 2/5

IN my mailbox



1.25)

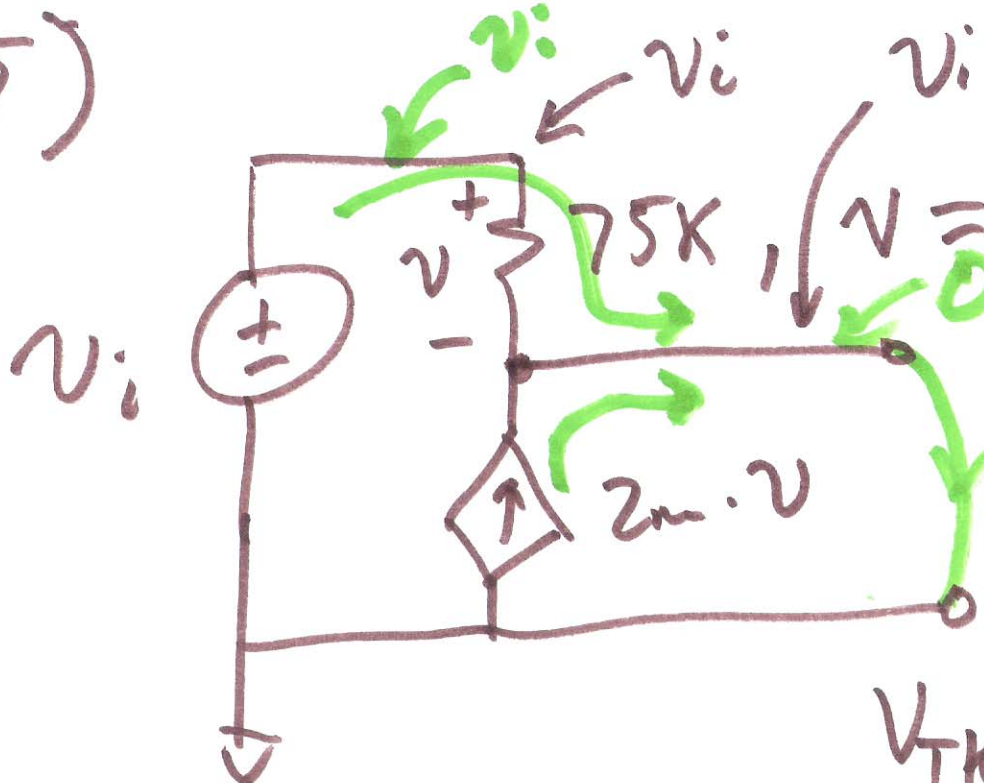

$$v = -(2\text{mA} \cdot v) \cdot 75\text{k}$$

$$v = 0$$

$$i_{sc} = 2\text{mA} \cdot v + \frac{v}{75\text{k}}$$


$$i_{sc} = v_i \left(2\text{mA} + \frac{1}{75\text{k}} \right)$$

$$V_{TH} = v_i = V_{oc}$$

$$R_{TH} = \frac{V_{oc}}{i_{sc}} = \frac{1}{2\text{mA} + \frac{1}{75\text{k}}}$$

$$v = -iR$$

$$v = iR$$

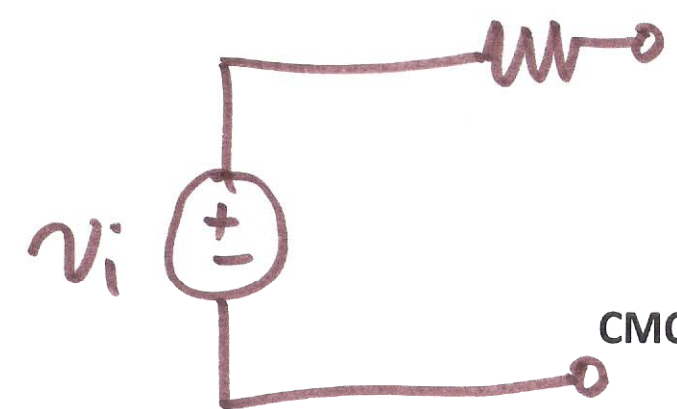

2)

$$A_{OL} = 500$$

$$V_{CC}^+ = 5V$$

$$V_{CC}^- = 0$$


Sketch

V_{OUT}


vs.

$$V_P - V_{in}$$

$$500 \quad -1\mu V$$

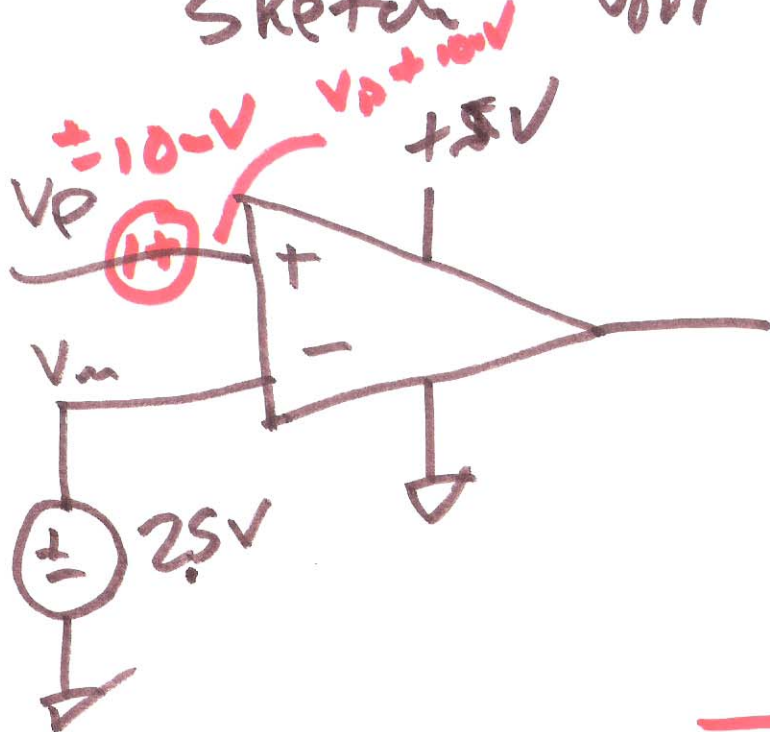

$$V_{OUT} = A_{OL} (V_P - V_{in})$$

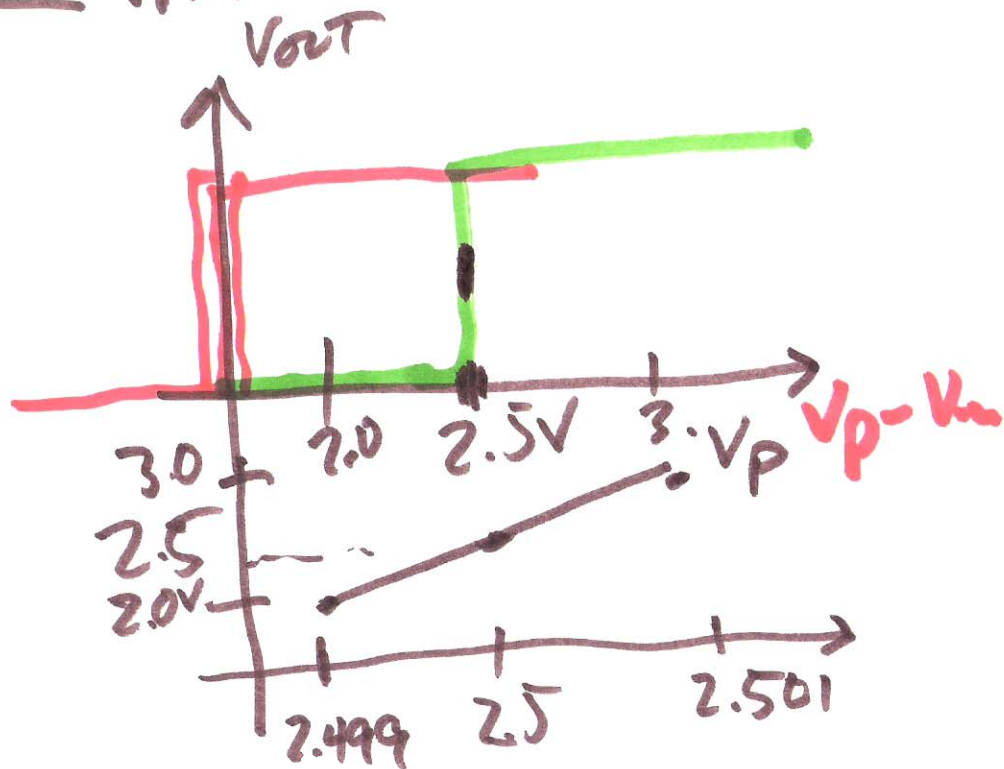


3)

find V_{out} if

$$A_{OL} = 1,000$$

$$V_{OS} = \pm 10 \text{ mV}$$

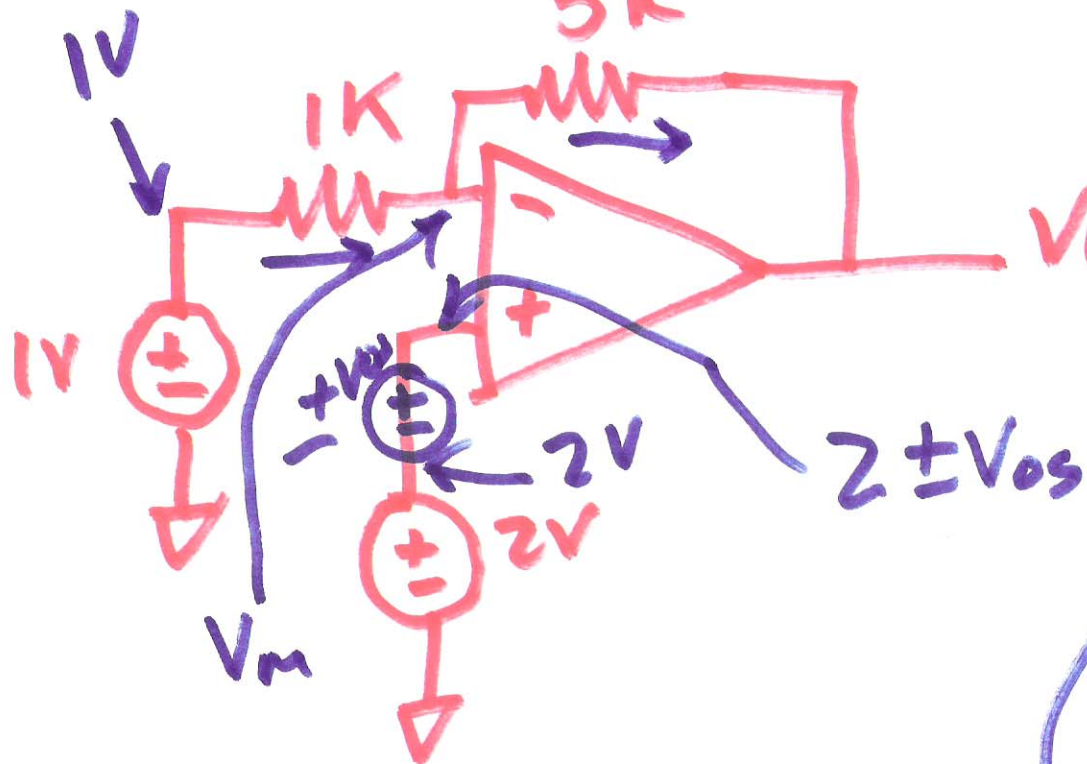

$$V_{out} = 10^3 (2 \pm V_{OS} - V_m)$$

$$\frac{1 - V_m}{1K} = \frac{V_m - V_{out}}{5K}$$

$$5 - 5V_m = V_m - V_{out}$$

$$5 + V_{out} = 6V_m$$

$$V_m = \frac{5}{6} + \frac{V_{out}}{6}$$

$$V_{out} = 2,000 \pm 1,000 V_{OS}$$

$$- \frac{5000}{6} + \frac{1,000 V_{out}}{6}$$

$$V_{out} \left(\frac{6}{6} + \frac{1,000}{6} \right) = \frac{12,000}{6} - \frac{5,000}{6} \pm 1,000 V_{OS}$$

$$= \frac{12,000}{6} - \frac{5,000}{6} \pm 1,000 V_{OS}$$

$$V_{NT} 1006 = 7,000 \pm 6000 \text{ Vos}$$

$$V_{NT} = \frac{7 \pm 6 \text{ Vos}}{1.006}$$

$$V_{os} = +10 \mu\text{V}, V_{NT} = \frac{7 + 60 \mu\text{V}}{1.006} = 7.0179 \text{ V}$$

$$\begin{array}{l}
 +20\text{dB} \\
 -20\text{dB} \\
 +6\text{dB} \\
 -6\text{dB} \\
 14\text{dB}
 \end{array}
 \begin{array}{l}
 \times 10 \text{ Vos} = -10 \mu\text{V} \\
 \div 10 \\
 \times 2 \\
 \div 2 \\
 \times 5
 \end{array}
 \begin{array}{l}
 1.2 \text{ KHz} \\
 \div 2 \\
 \times 2
 \end{array}
 \begin{array}{l}
 \div 10 \\
 \times 10 \\
 \text{OCT}
 \end{array}
 \begin{array}{l}
 V_{NT} = \frac{7 - 60 \mu\text{V}}{1.006} \\
 = 6.9403 \\
 8986
 \end{array}$$

5)

$$78 = \frac{t_d}{T} \cdot 360$$


$$T = \frac{1}{800} = 1.25 \text{ms}$$

$$t_d = \frac{78}{360} \cdot 1.25 \text{ms}$$

$$\underline{\underline{.27 \text{ms}}}$$

4)


$10^3 = A_{OL_{DC}}$
 \downarrow
 60dB

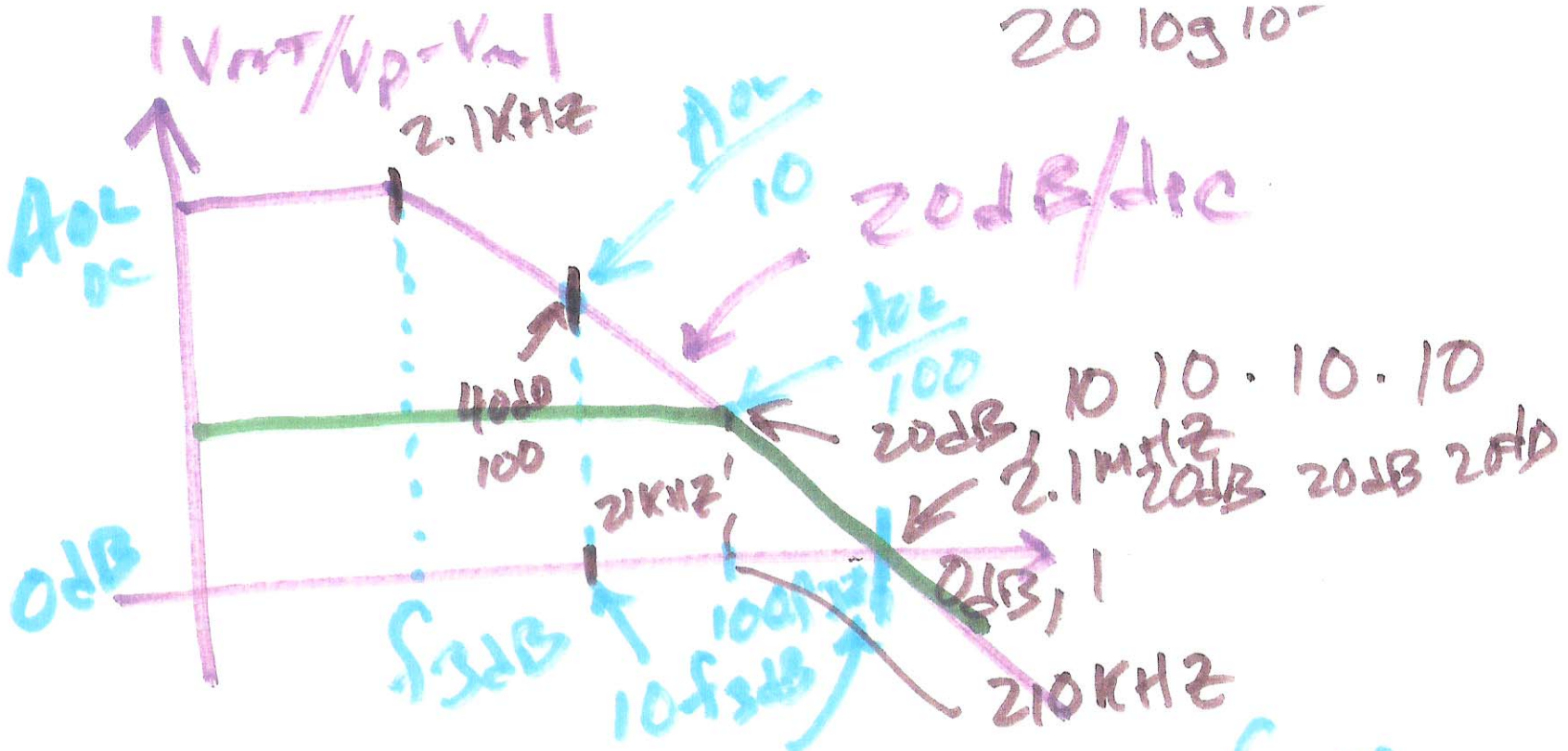

$A_{OL}(f) = \frac{A_{OL_{DC}}}{1 + j \frac{f}{f_{3dB}}}$

Unity-gain freq.
 Gain · BW product
 $210K \cdot 10 = 2.1MHz$

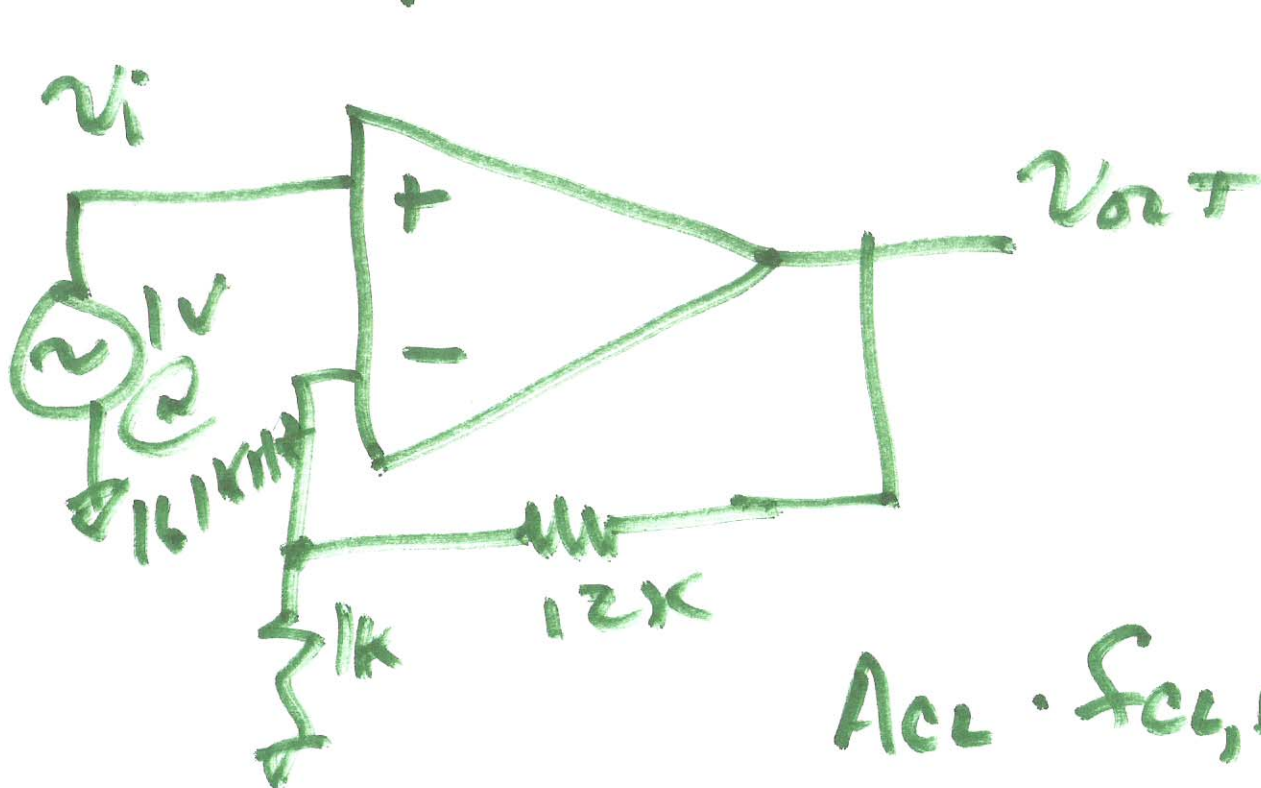OP-AMP with $f_{\text{un}} = 2.1 \text{ MHz}$
 NON-INVERTING \leftarrow unity-gain
 gain \cdot BW



BW = ?

$$A_{\text{CL}} = 1 + \frac{12\text{k}}{1\text{k}} = 13$$

$$A_{\text{CL}} \cdot f_{\text{CL, BW}} = 2.1 \text{ MHz}$$

$$161 \text{ kHz} = f_{\text{CL, BW}} = \frac{2.1 \text{ MHz}}{13}$$

8)