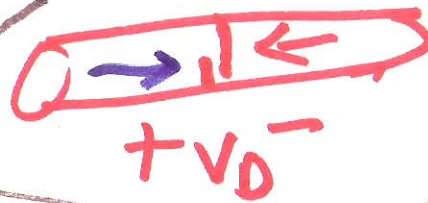


EE 320 Electronics


2/17/14

Lecture 8

for forward bias
 $V_D = N V_T \ln \frac{I_D}{I_S}$



ideal diode turns on when $V_D = 0$

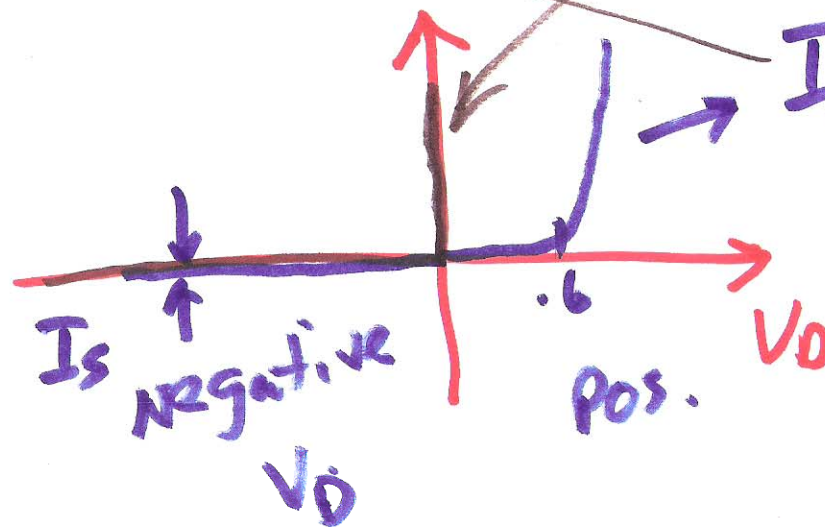


$$I_D = I_S (e^{V_D / N V_T} - 1)$$

$N \rightarrow$ emission coeff.

$$V_T = \frac{kT}{q} = 25 \text{ mV @ room Temp}$$

Logarithmic ∞ -Amp

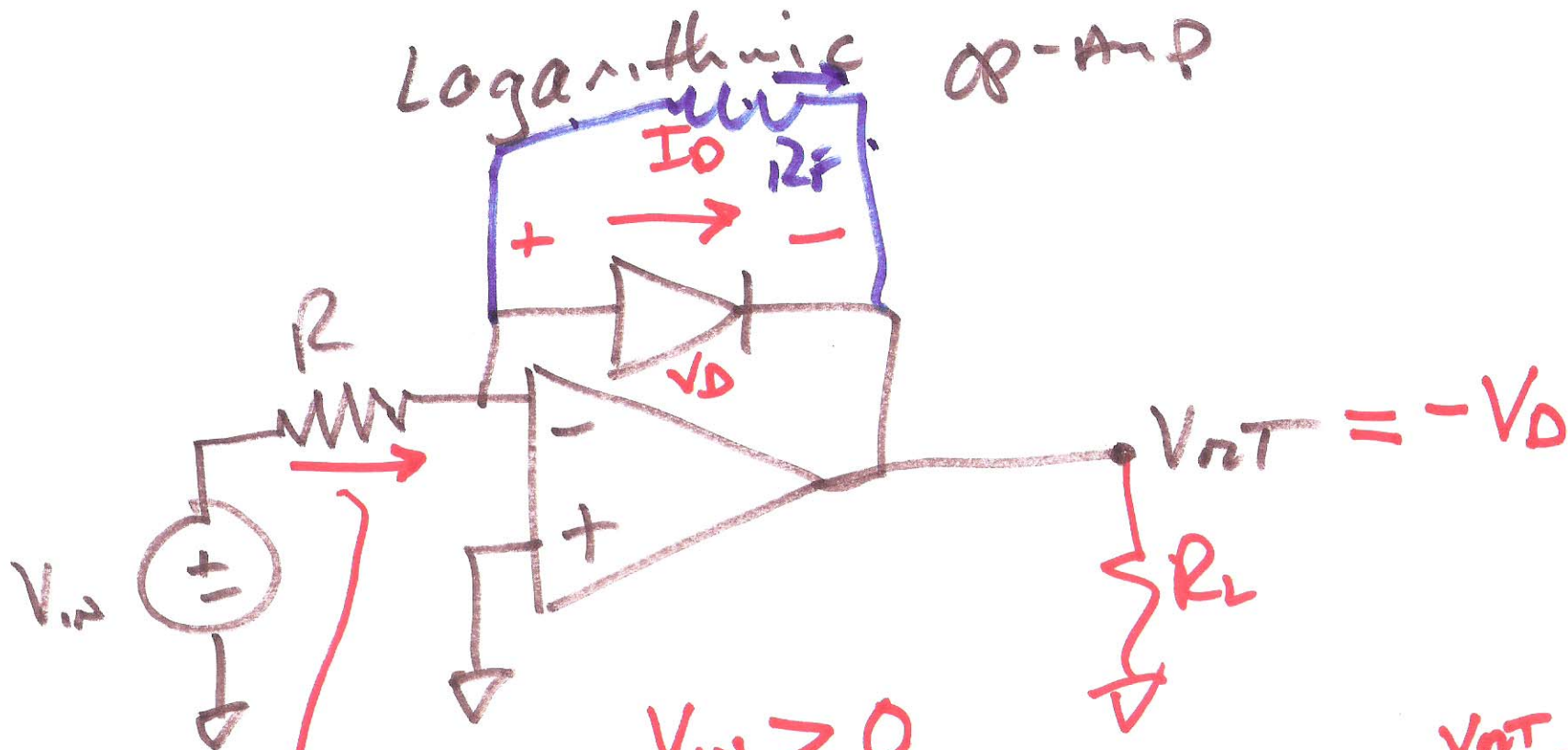

$$V_{in} > 0$$

$$\frac{V_D}{NVT} = I_S e^{-\frac{V_D}{NVT}}$$

$$\frac{0 - V_{out}}{R_f} + I_0 = \frac{V_{in}}{R}$$

$$= I_0 \approx I_S e^{-\frac{V_{out}}{NVT}}$$


$$e^{-\frac{V_{out}}{NVT}} = \frac{V_{in}}{R \cdot I_S}$$

$$-\frac{V_{out}}{NVT} = \ln \frac{V_{in}}{R \cdot I_S}$$

$$V_{out} = -NVT \ln \frac{V_{in}}{R \cdot I_S}$$


$$C = \frac{\epsilon \cdot A}{t}$$


$$CV = Q$$

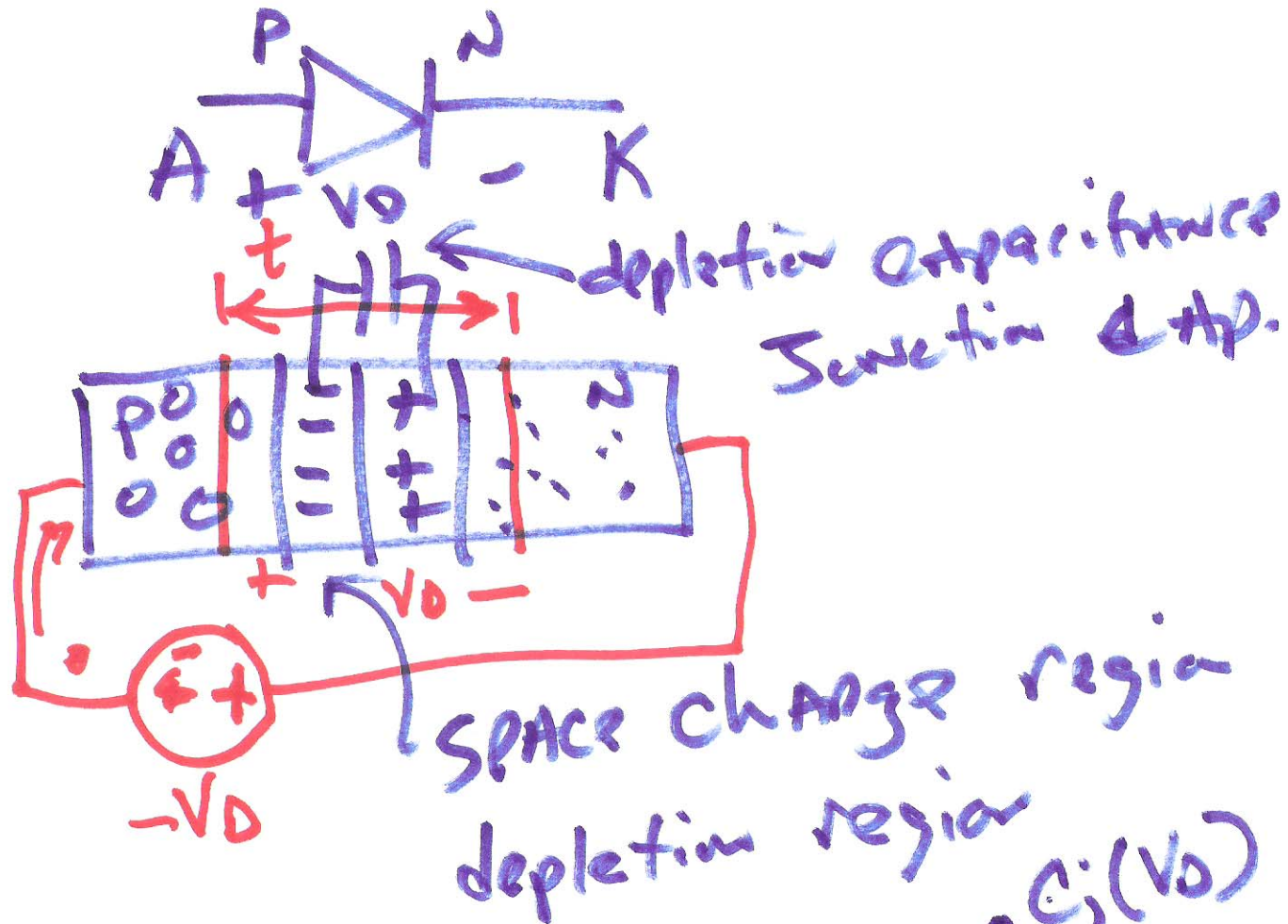


$$C_j(V_0)$$

$$= \frac{C_{j0}}{\left(1 + \frac{|V_0|}{V_{bi}}\right)^m}$$


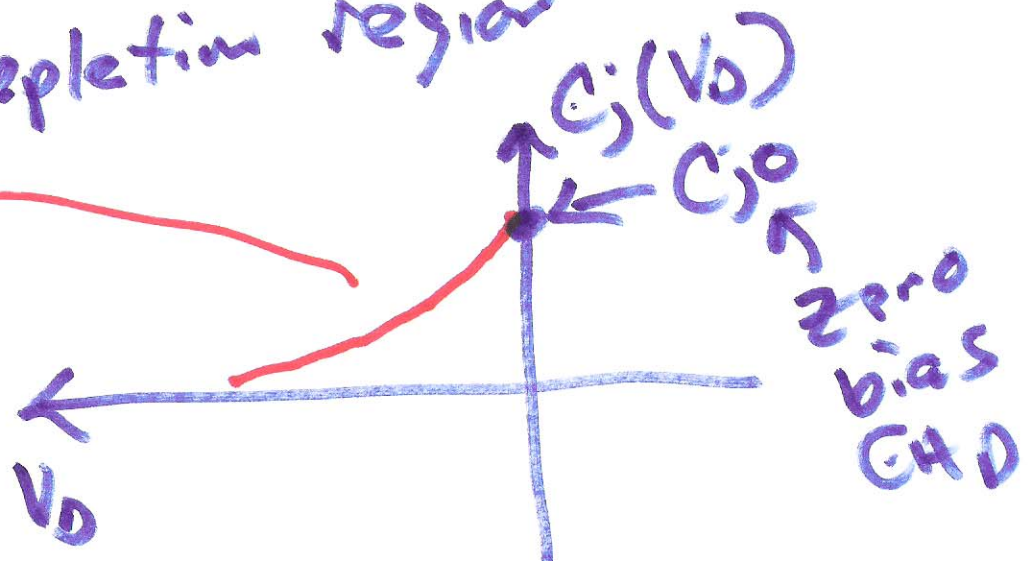


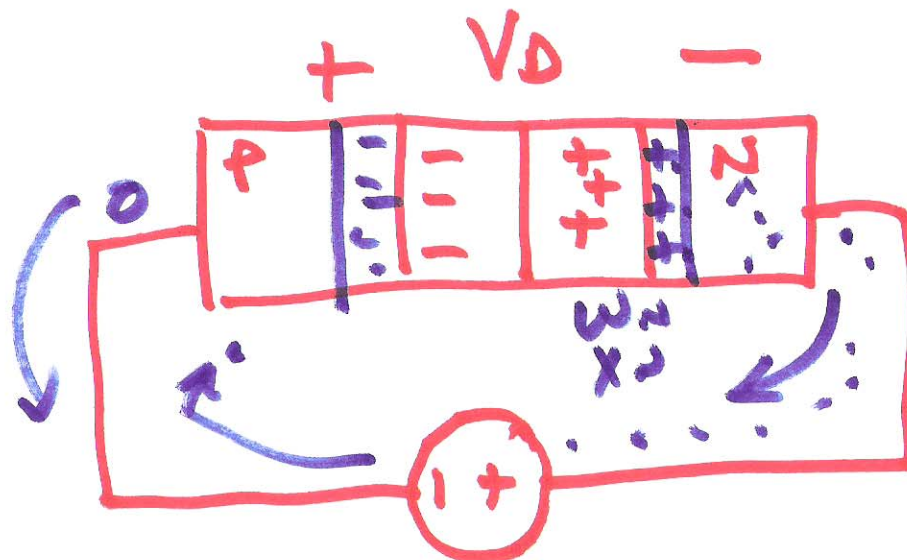

$$V_X + V_D = 0$$

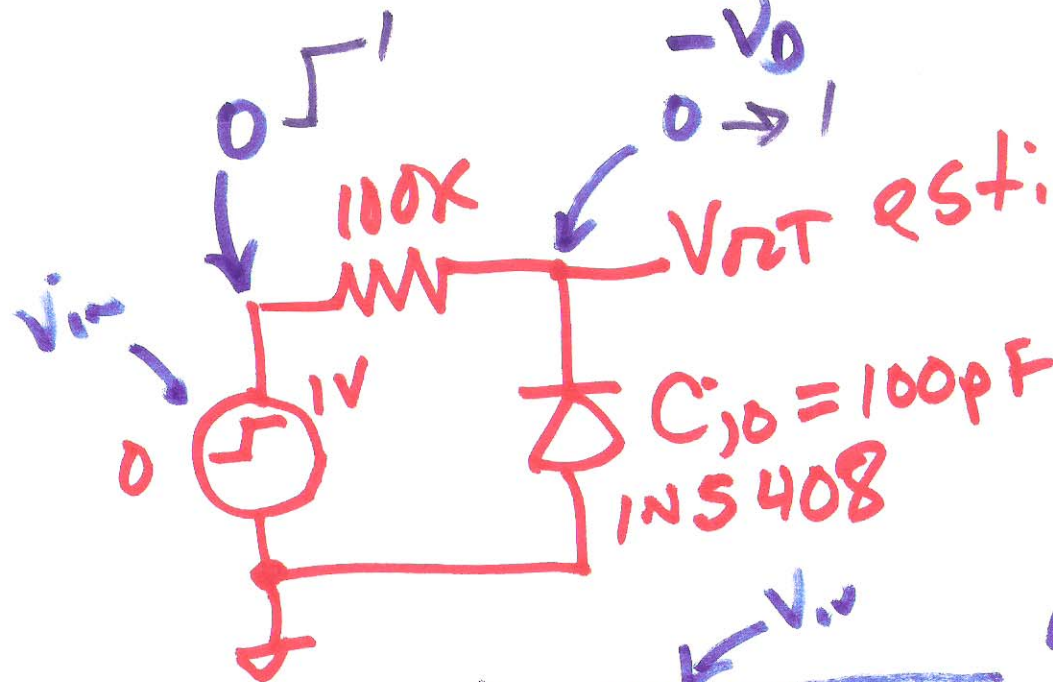


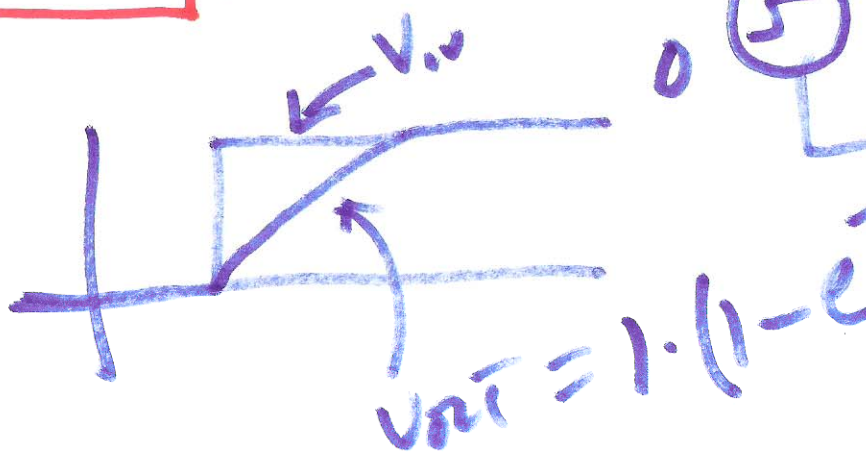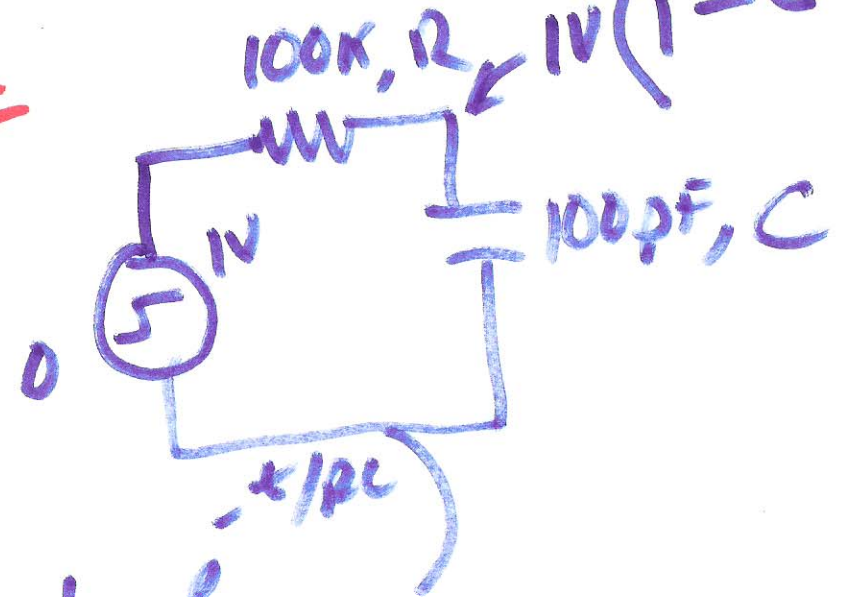V_{out} estimate $V_X = -V_D$ $\frac{t}{RC}$




Load lines and Q-point

→ Quiescent


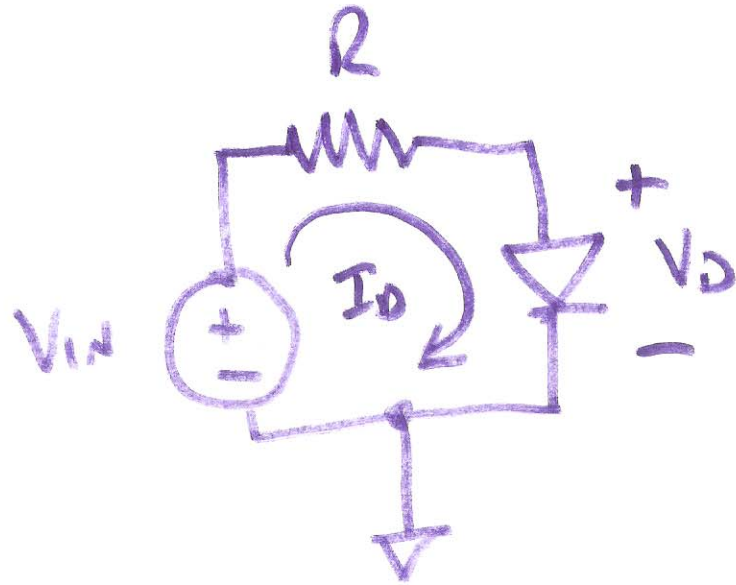


$$I_D = \frac{V_{IN} - V_D}{R}$$
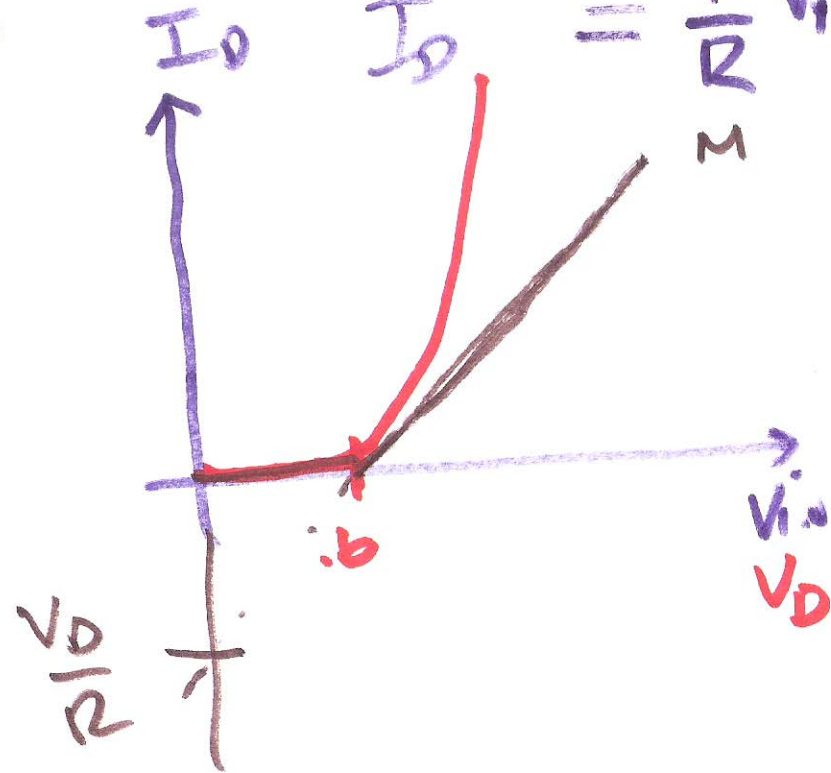
$$I_D = \frac{1}{R} V_{IN} - \frac{V_D}{R}$$






3.69)

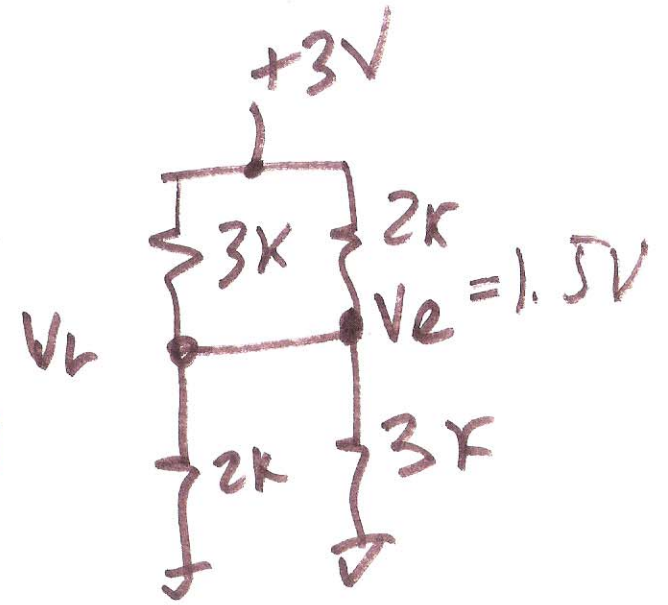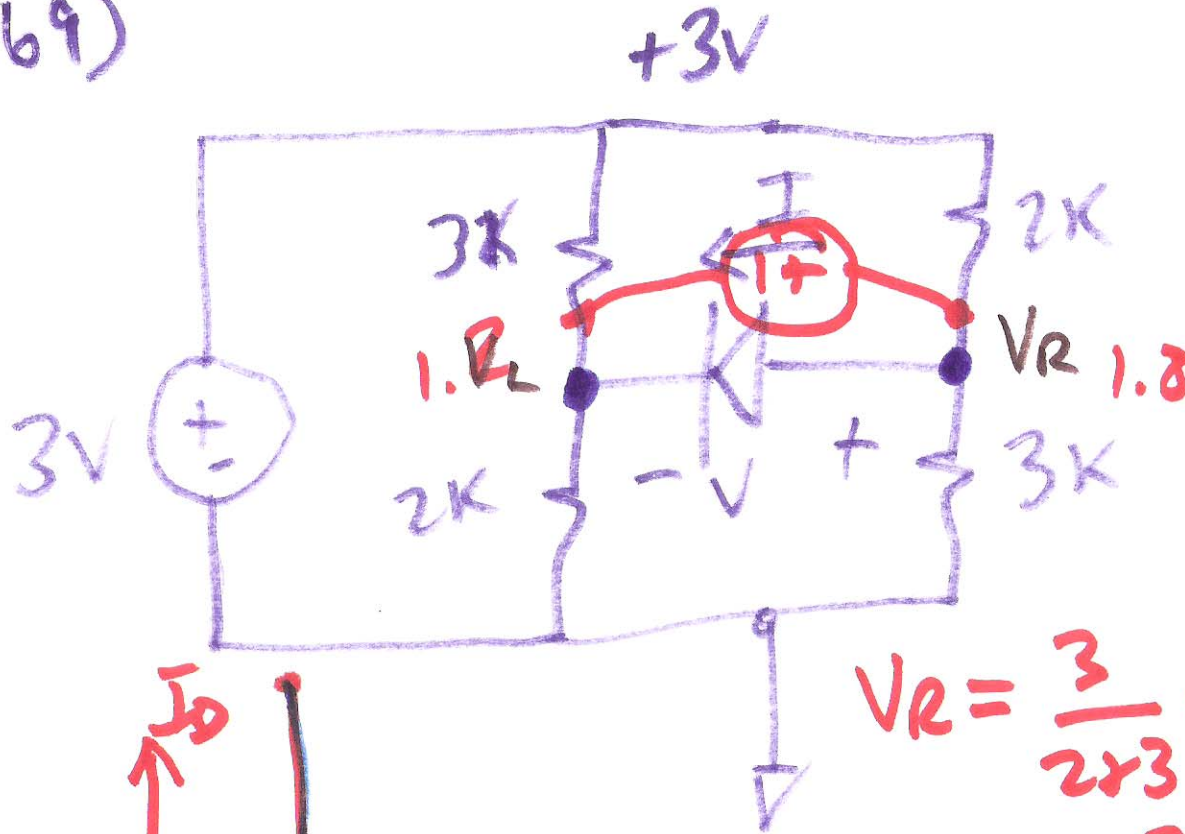




$$V_R = \frac{3}{2+3} \cdot 3 = \frac{9}{5} = 1.8$$
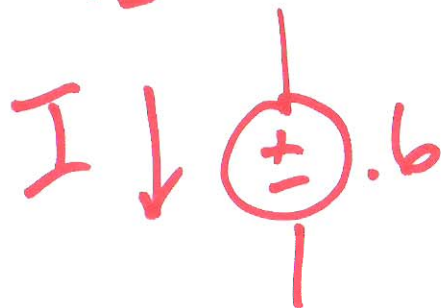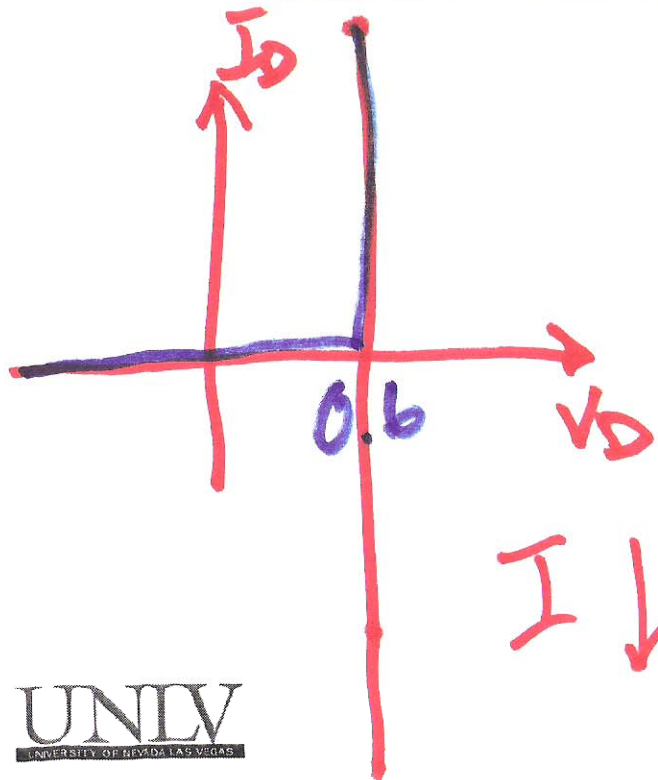
$$V_L = \frac{2}{2+3} \cdot 3 = \frac{6}{5} = 1.2$$




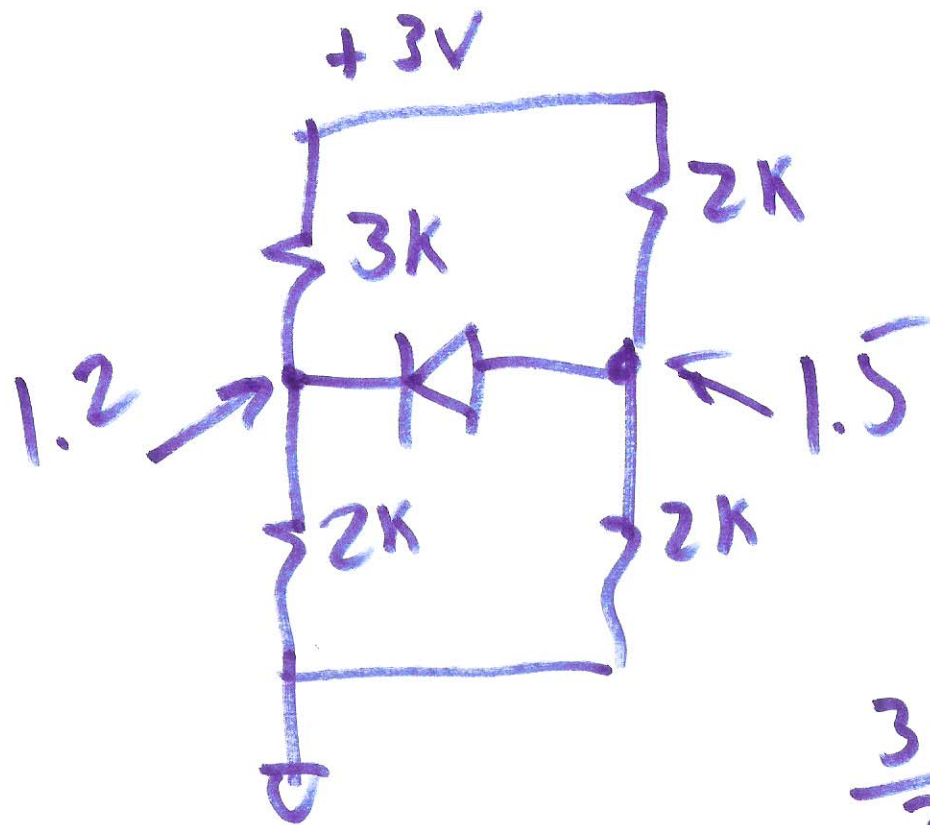

(b)

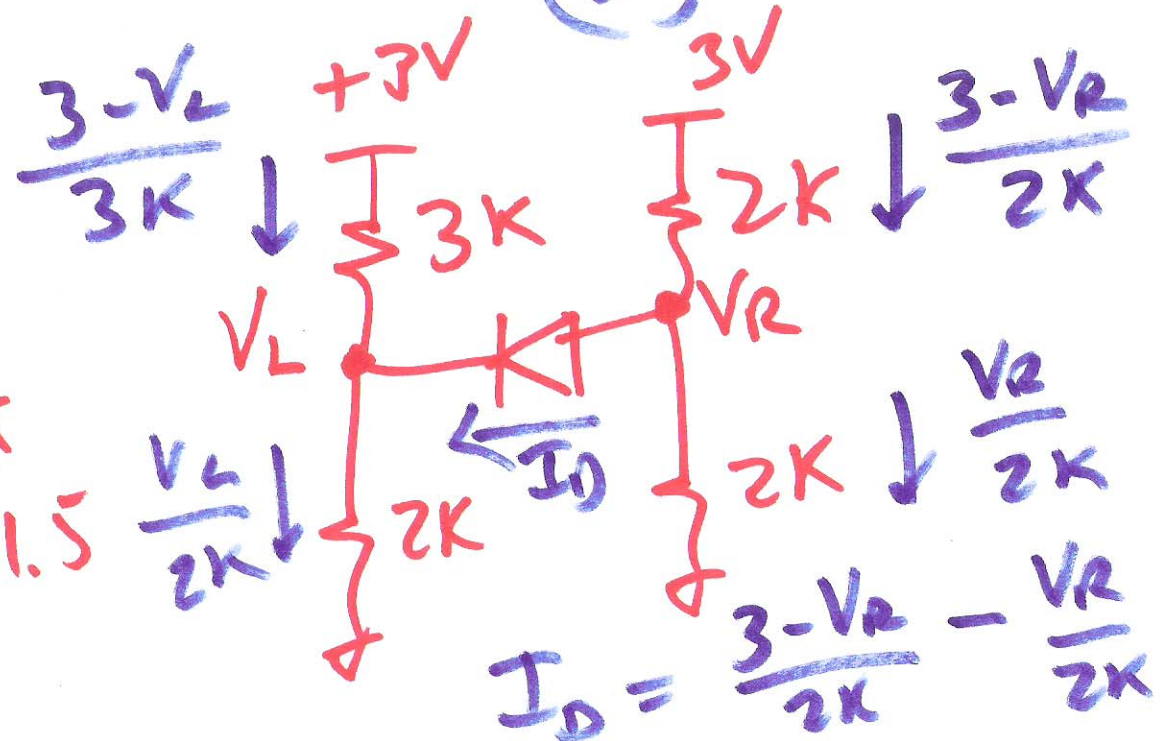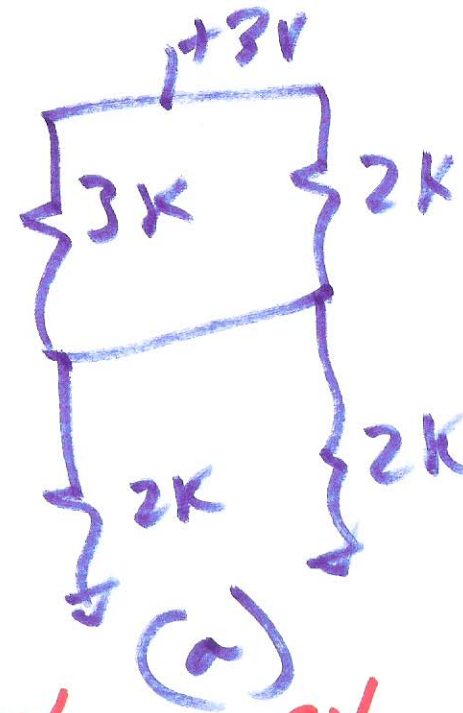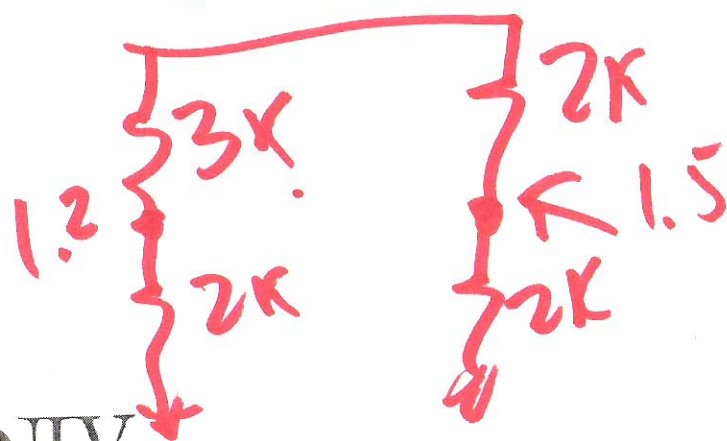
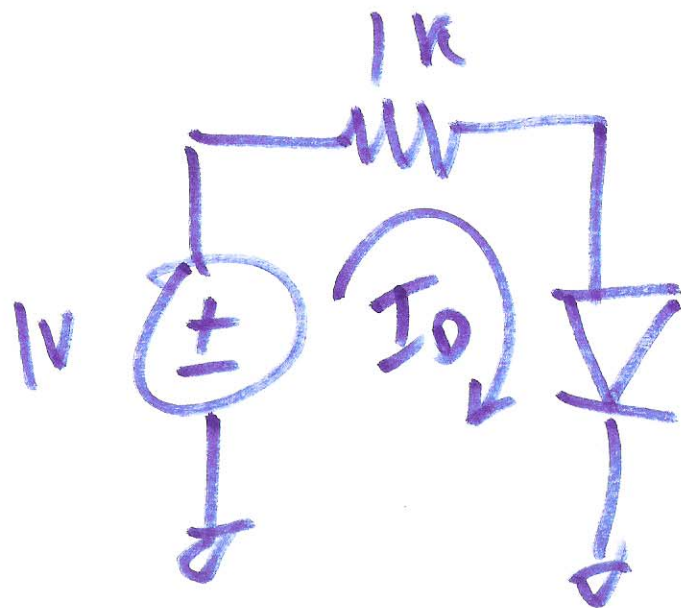
$$I_D = \frac{3 - V_R}{2k} - \frac{V_R}{2k}$$



$$I_s = 10^{-15} \text{ A}, N=1, \text{ room temp}$$

$$\text{find } V_D = ?$$

$$\frac{1 - V_D}{1k} = I_D \approx I_s e^{\frac{V_D}{0.025}}$$

L	R	V_D
0.4	0.826	0.6
0.3	1.44	0.7
0.35	1.15	0.65

