
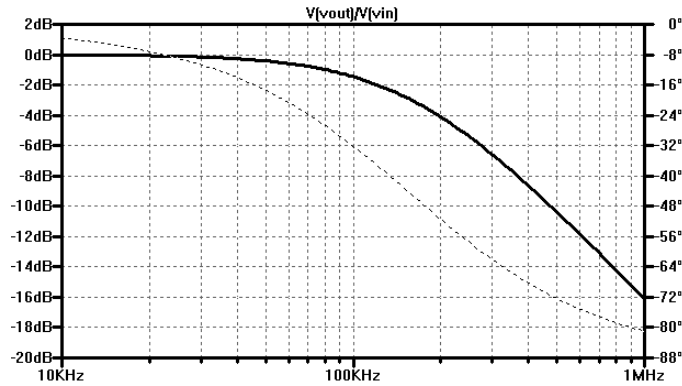


H.W. # 2 - Spring 2015 EE 320 Engineering Electronics I

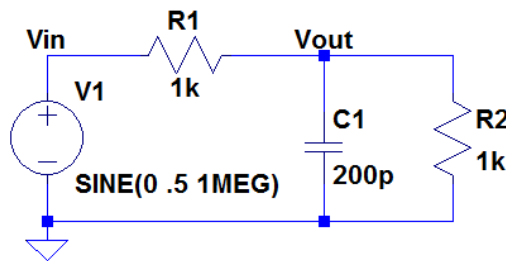
- Sketch the input and output of a circuit on the same plot against time if the circuit has the following frequency response. The input signal has an amplitude of 200 mV and is at a frequency of 200 kHz. (5 points)



- Calculate, and sketch with the input, the output of the following circuit. Use simulations to verify your answer (It's OK from this point on to use LTspice's schematic editor). (5 points)



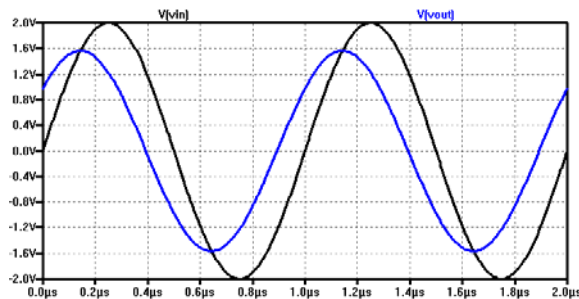- What is the phase-shift between the following sinusoids? (2 points)



- What is the frequency one decade below 1.2 kHz? What is the frequency one octave above 1.2 kHz? What is the magnitude of a transfer function rolling off at -20 dB/decade one decade below where the magnitude is 0 dB? (3 points, 1 point each)

5. Assuming an ideal op-amp (infinite open-loop gain) show how to calculate the output of the following circuit. Verify your answer with simulations. (5 points)

