
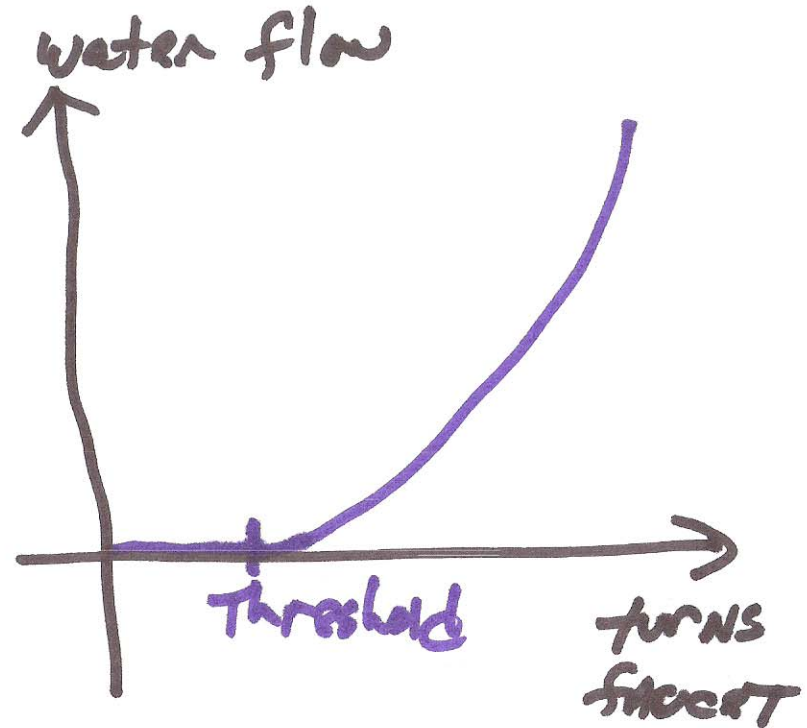


EE 320


Electronics

MARch 18, 2015

Lecture 17


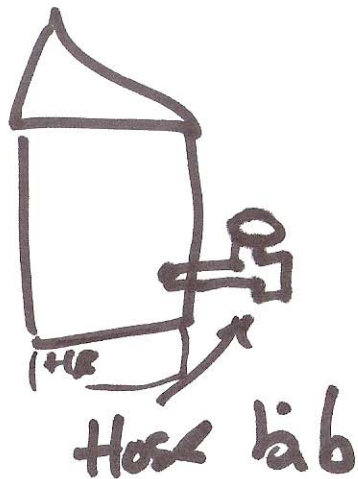


MOSFET
oxide
capacitance
transistor

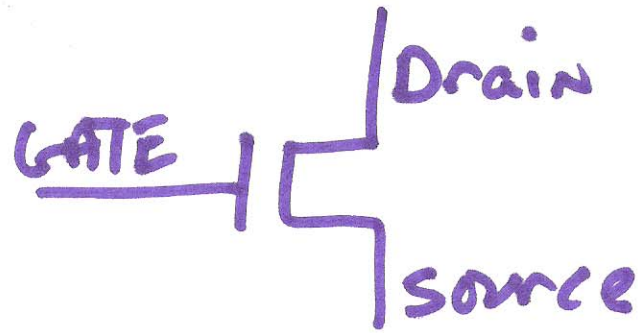

$$V_{GS} = V_G - V_S = V_G$$

$$V_{DS} = V_D - V_S = V_D$$

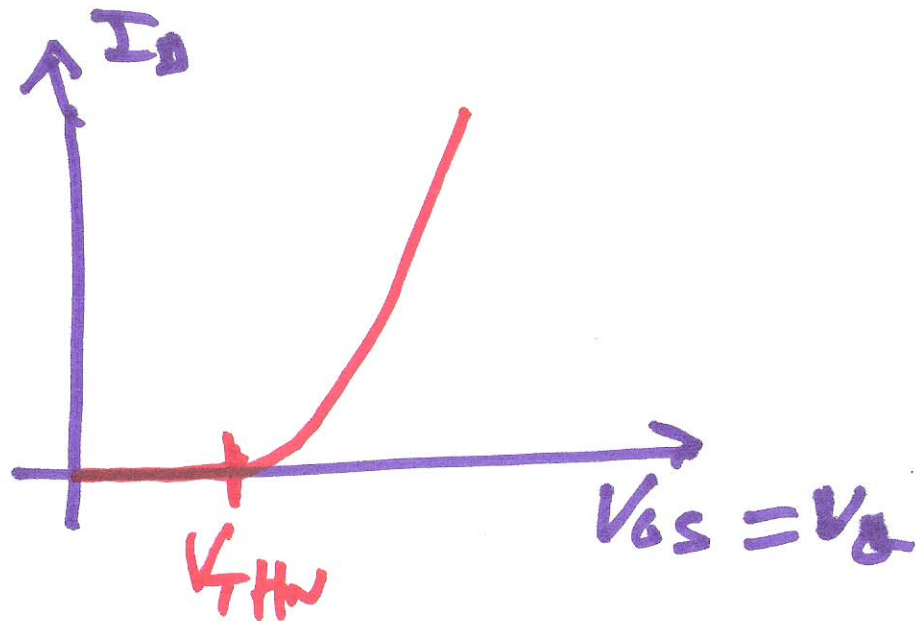
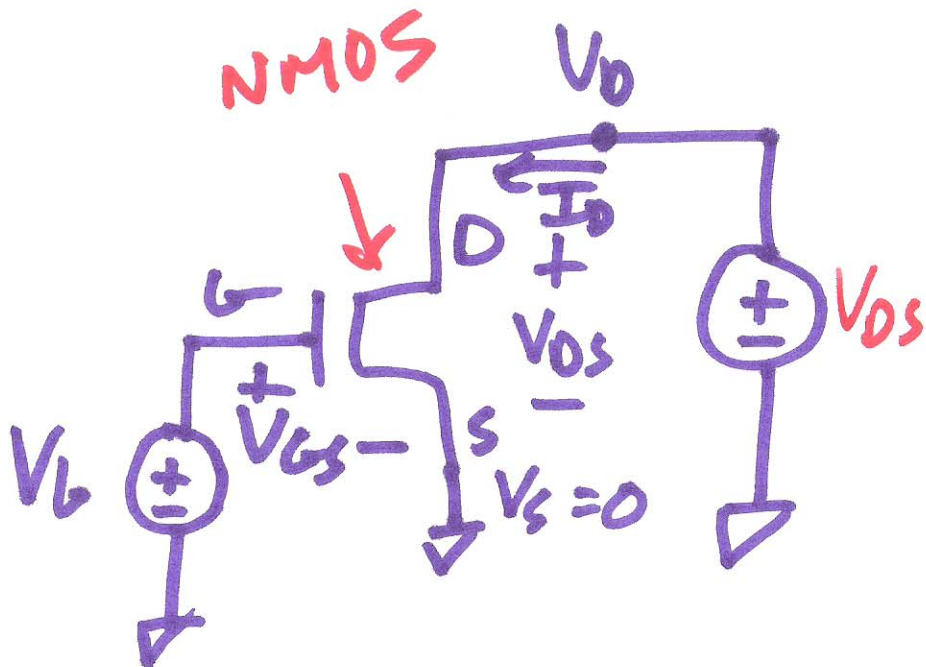


2)





1-turn
2-turns
3-turns

$2^{15} = 32K$

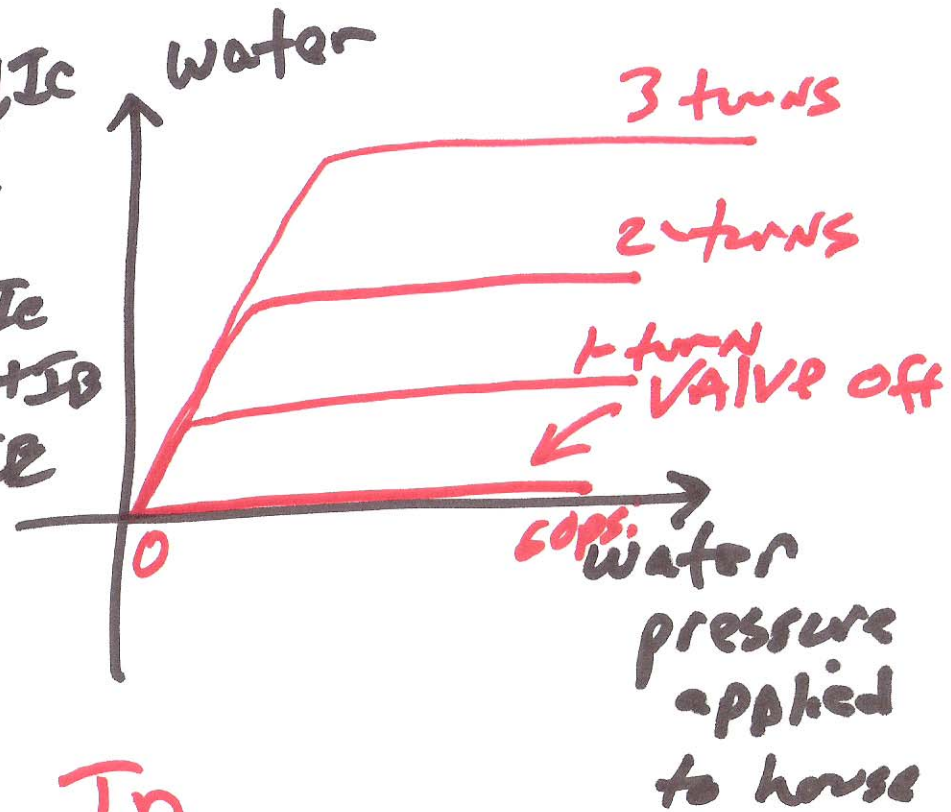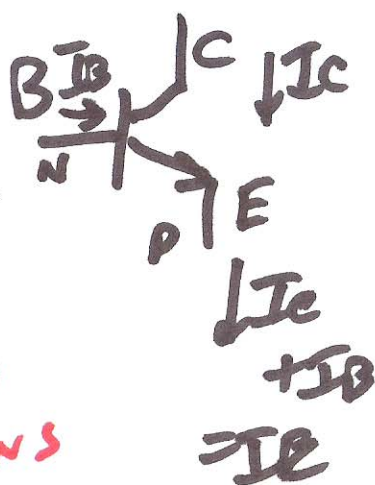

$V_{THN} = 1V$

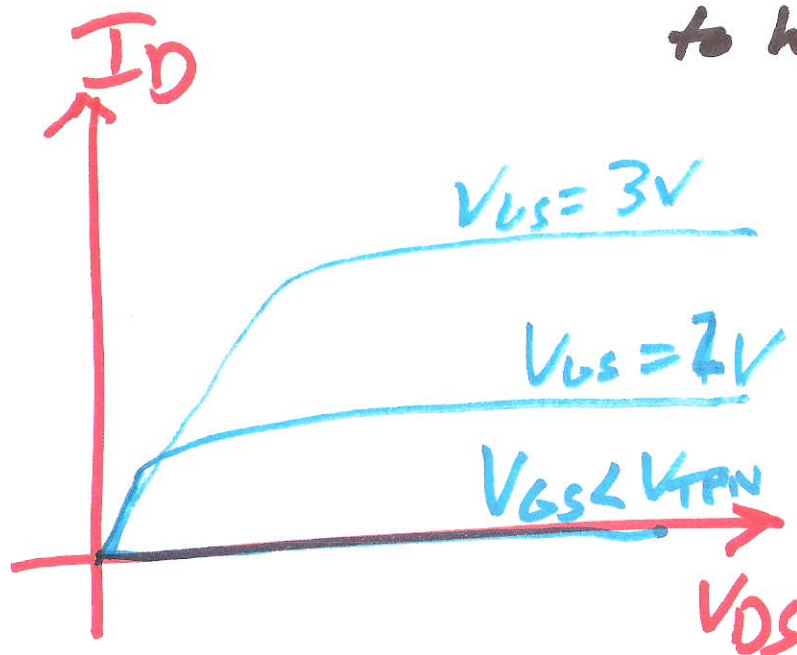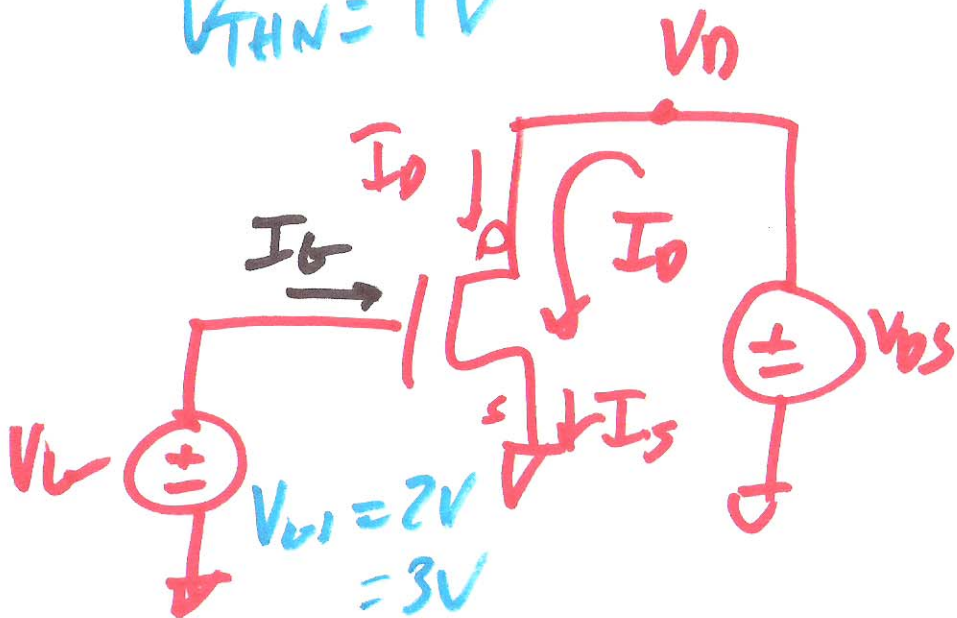


$V_{GS} < V_{THN}$


3)

$$I_D = \frac{K_P}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2$$

$V_{GS} \geq V_{THN}$

K_P = transconductance parameter

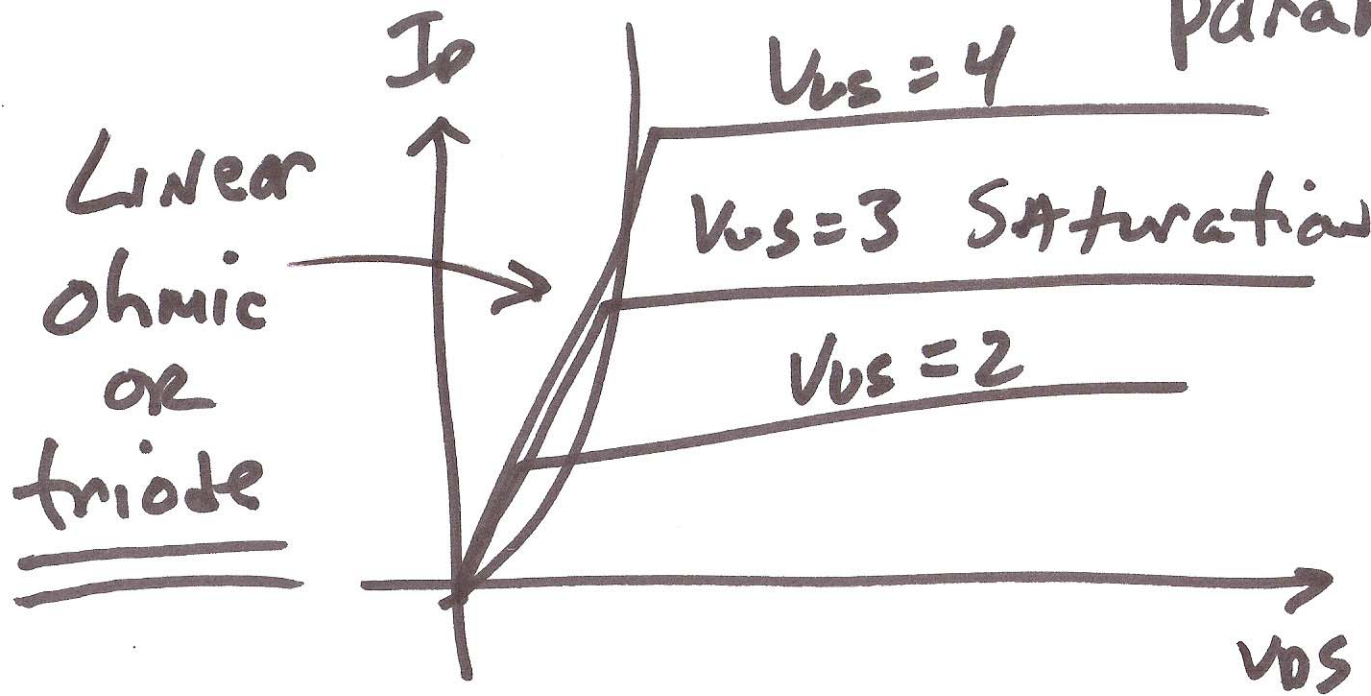

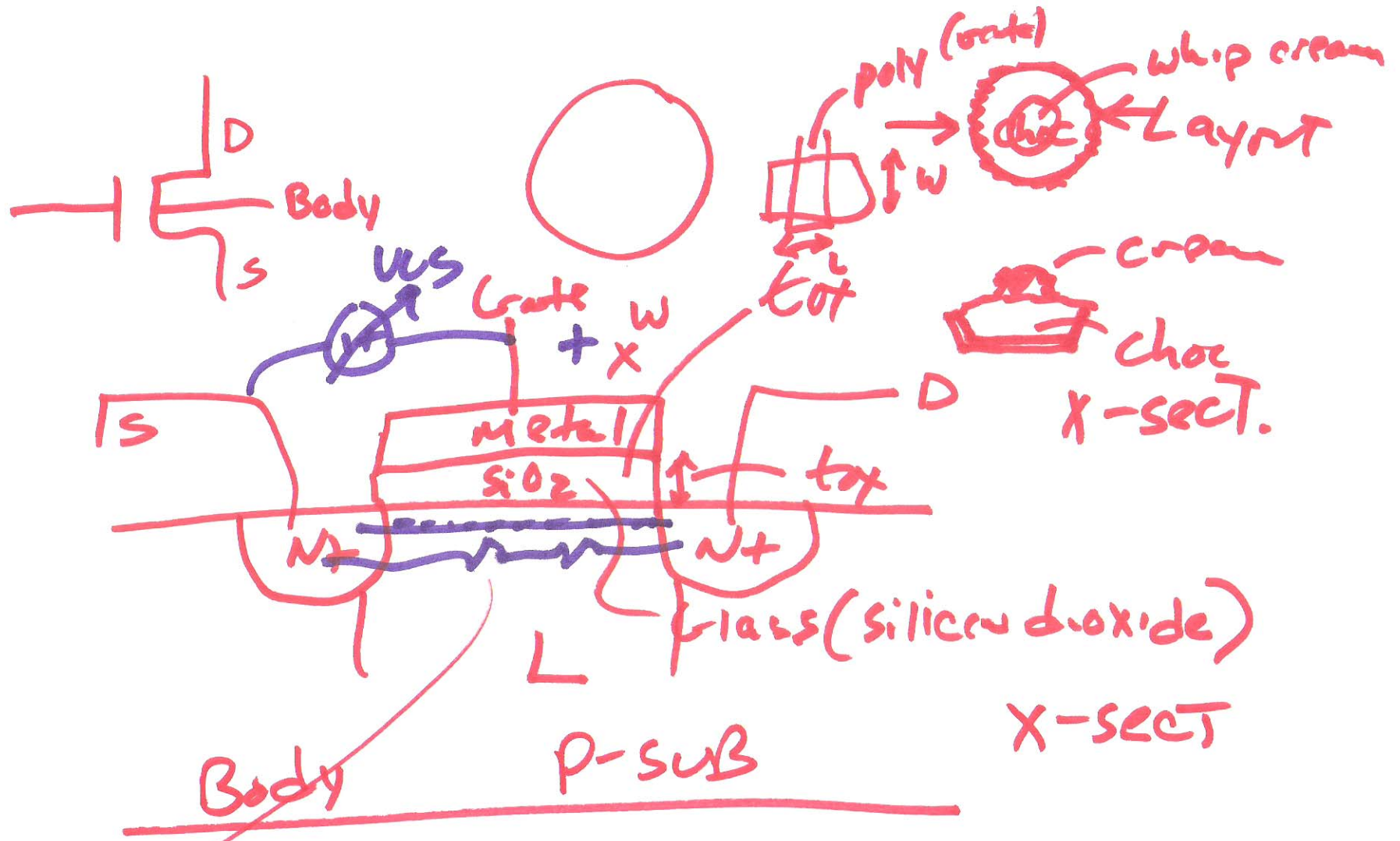

channel is
N-type

NMOS
↑

5)

$$K_{P_N} = K_P = K'_N = \mu_n \cdot C_{ox} = \mu_n \cdot \frac{\epsilon_{ox}}{t_{ox}}$$

\nearrow mos \nearrow spice
 transconductance

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$= \frac{K'_N}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad \left. \begin{matrix} K'_P = K_P = K'_P = \mu_p \cdot C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \cdot \mu_p \end{matrix} \right\} \begin{matrix} \text{2 parameters} \\ \text{pmos spice} \end{matrix}$$

$$I_D = \frac{\beta_N}{2} (V_{GS} - V_{TH})^2 \quad \left. \begin{matrix} \beta_N = K_N = K_{P_N} \cdot \frac{W}{L} = K'_N \cdot \frac{W}{L} \end{matrix} \right\} \begin{matrix} \text{2 parameters} \\ \text{pmos spice} \end{matrix}$$

$$= \frac{K_N}{2} (V_{GS} - V_{TH})^2 \quad \left. \begin{matrix} \beta_P = K_P = K_{P_P} \cdot \frac{W}{L} \cdot K'_P \cdot \frac{W}{L} \end{matrix} \right\}$$

6)

$$W = 10 \mu \quad K_{P_n} = K_{n} = 100 \mu A/V^2$$

$$L = 1 \mu$$

$$V_{THN} = 1V$$



$$I_D = \frac{100 \mu}{2} \cdot \frac{10}{1} (2-1)^2$$


$$= \underline{\underline{500 \mu A}}$$

$$V_{GS} = 2V$$



$V_{GS} > V_{THN}$
yes

$$V_{DS} = 5V$$

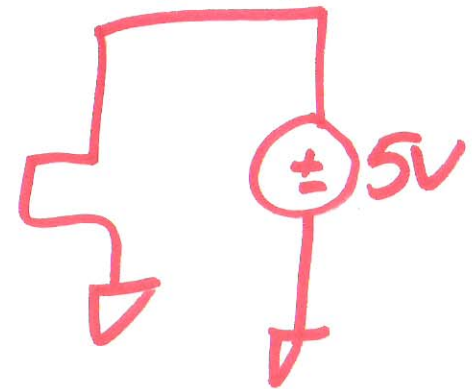

verify in sat.


$$V_{DS} \geq V_{GS} - V_{THN}$$

$$V_D - V_S \geq V_G - V_S - V_{THN}$$

$$V_D \geq V_G - V_{THN}$$

yes,
IN SAT! CMOSedu.com

7)

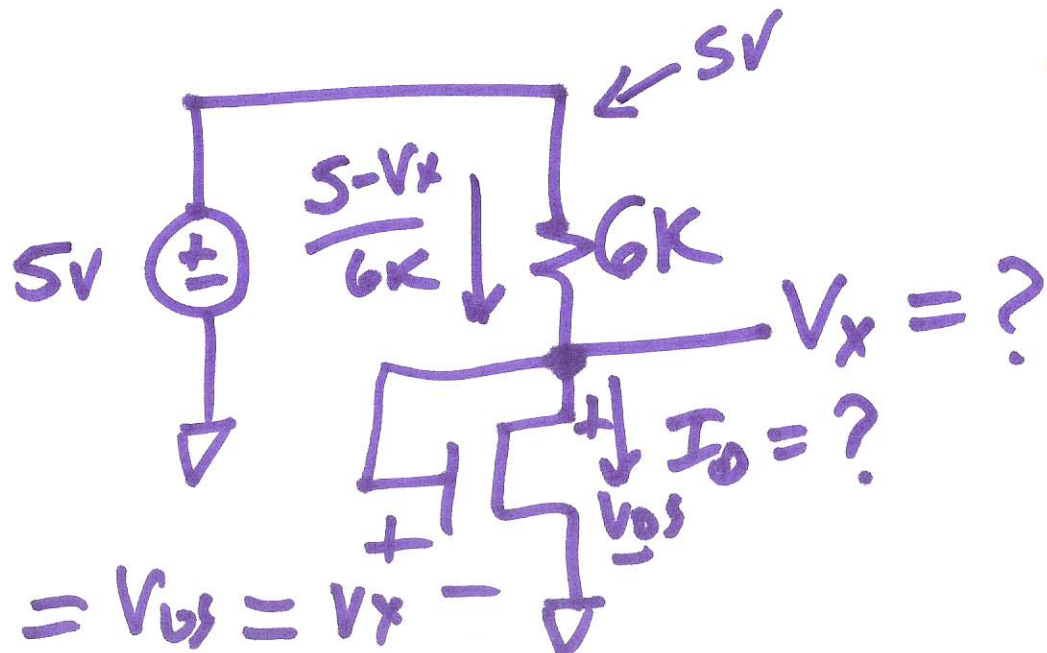

$$2V = V_{GS} = V_X - 0$$

diode connected

for $V_{DS} \geq V_{GS} - V_{THN}$

$$V_{DS} = V_{GS}$$

$$0 \geq -V_{THN}$$

yes,
in sat.

$$\frac{5 - V_X}{6k} = \frac{K_P \cdot W}{2} \cdot \frac{L}{2} (V_X - V_{THN})^2$$

V_X	L	R