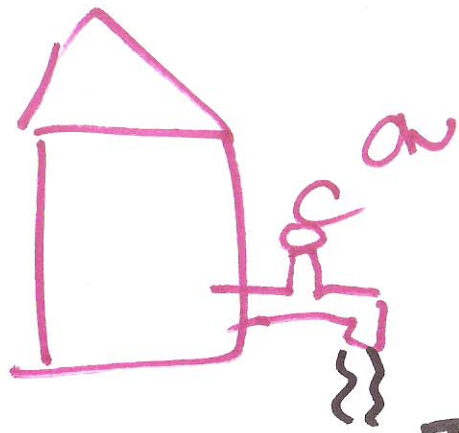



EE 320 Electronics I

MARCH 23, 2015


Lecture 18





triode
dynamic
linear

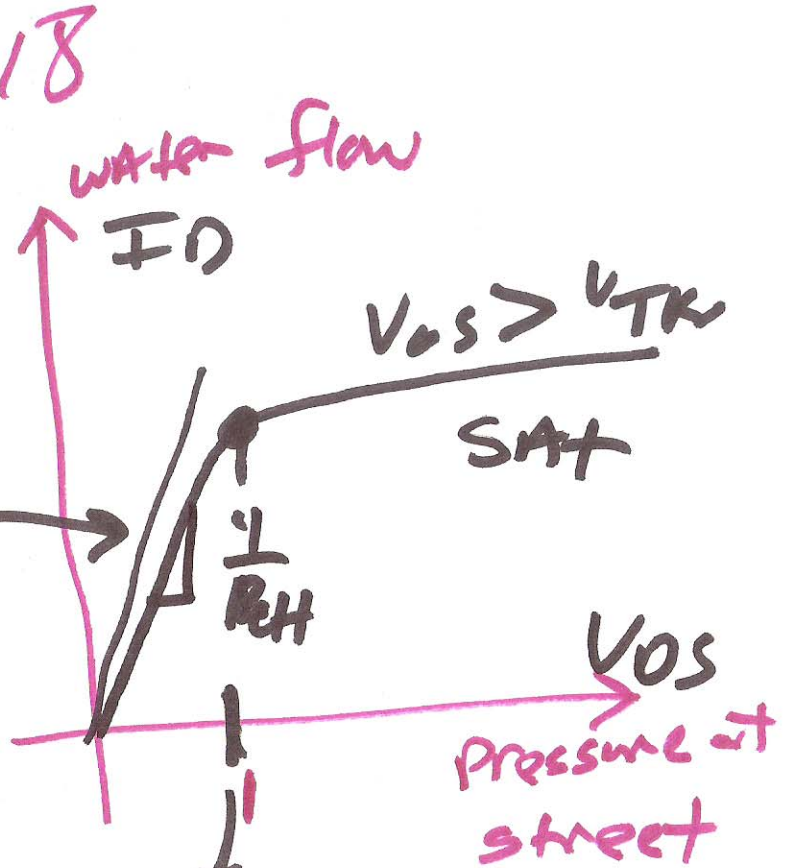
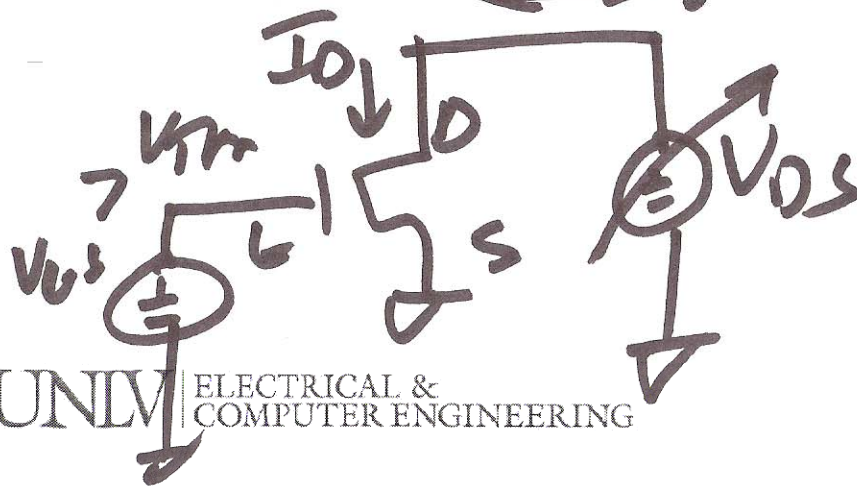
$$V_{GS} - V_{TK} = V_{DS, SAT} = V_{OV, N}$$



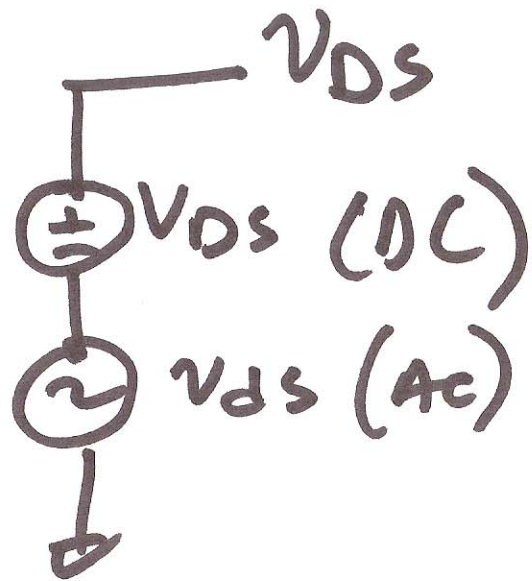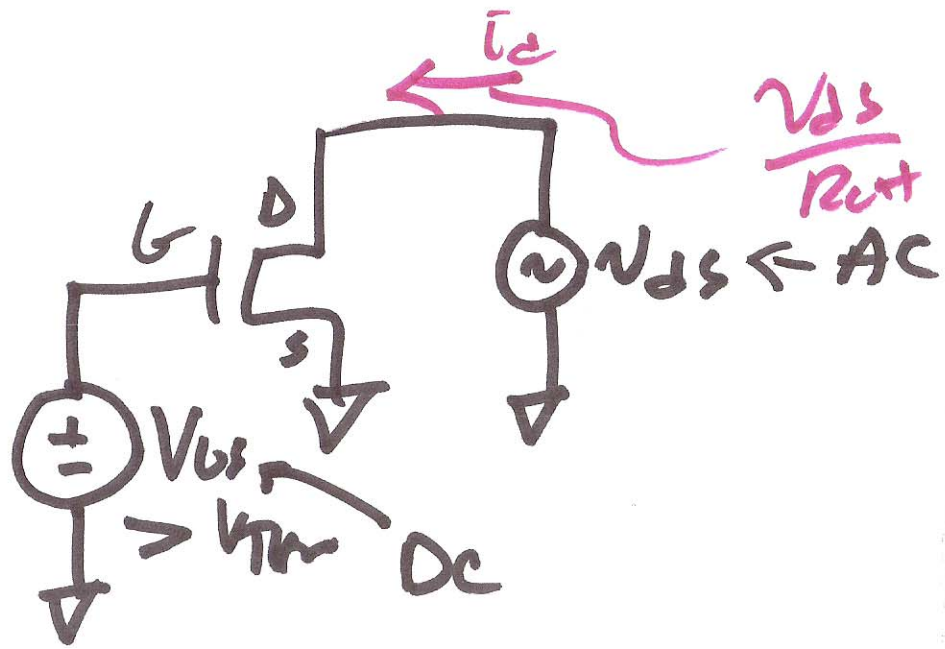

for SAT $K_N \approx K'_N \cdot \frac{W}{L}$

$$I_D = \frac{K_N}{2} (V_{GS} - V_{TH})^2$$

$$V_{GS} > V_{TH}$$



$$V_{DS} \geq V_{GS} - V_{TH} \quad (SAT)$$

for triode

$$I_D = K_N \left((V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$V_{GS} > V_{TH}$$

$$V_{DS} \leq V_{GS} - V_{TH}$$

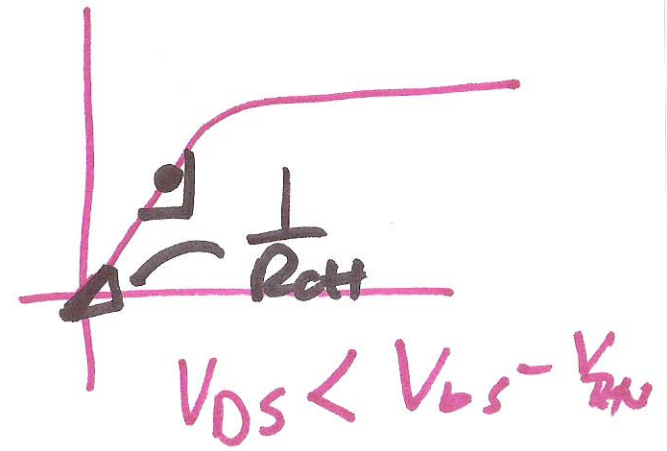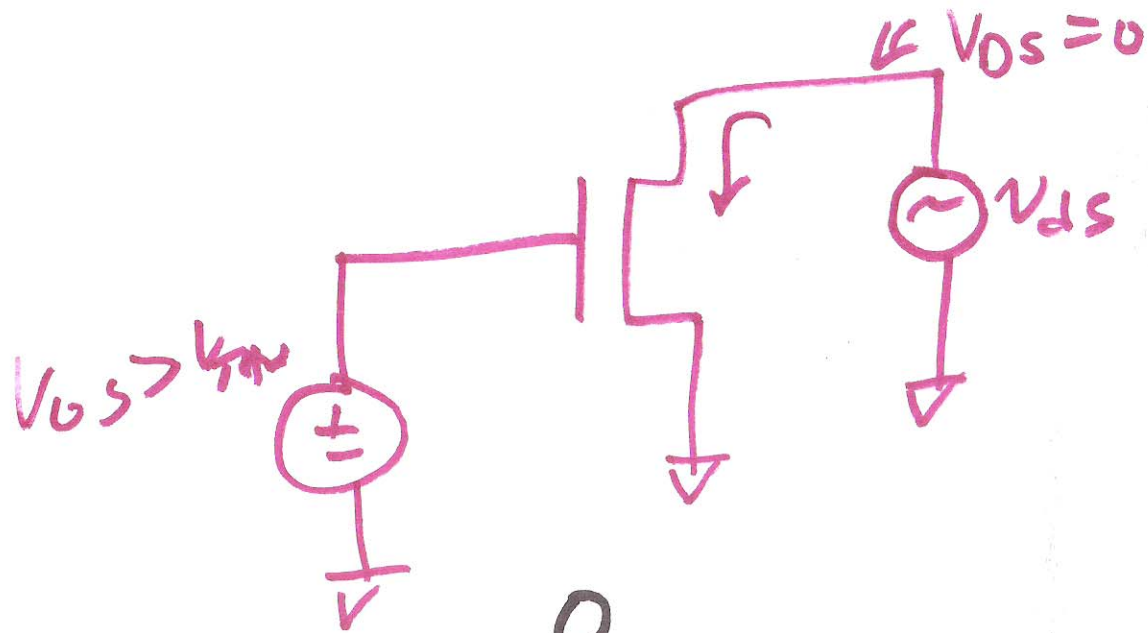


$$I_D + i_d = K_n \left((V_{bs} - V_{thn}) \frac{(V_{bs} + v_{ds})}{2} - \frac{v_{ds}^2}{2} \right)$$

$$\frac{1}{R_{ott}} = \left. \frac{\partial i_d}{\partial v_{ds}} \right|_{\substack{I_D = \text{const} \\ V_{bs} = \text{const}}} = \frac{\partial}{\partial v_{ds}} \left(K_n \left((V_{bs} - V_{thn}) v_{ds} - \frac{v_{ds}^2}{2} \right) \right)$$



$$= K_n (V_{bs} - V_{thn} - v_{ds})$$

$$\rightarrow R_{CH} = \frac{1}{\mu_n C_{ox} (W/L) (V_{GS} - V_{THN} - V_{DS})} \approx \frac{1}{\mu_n C_{ox} (W/L) (V_{GS} - V_{THN})}$$

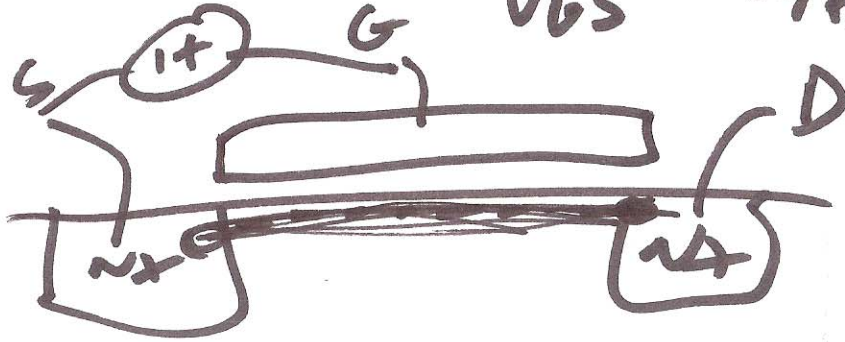$V_{GS} - V_{THN} \gg V_{DS}$
 $\approx V_{GS, SAT}$
 Small-signal approx.



4)

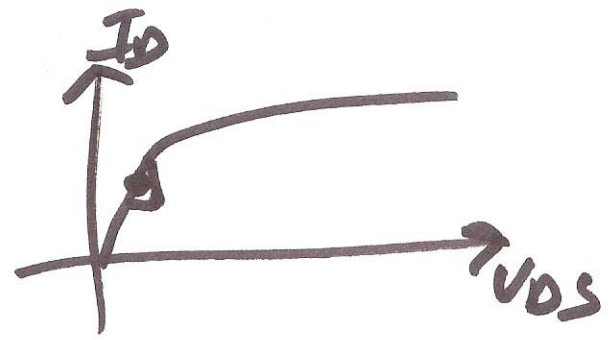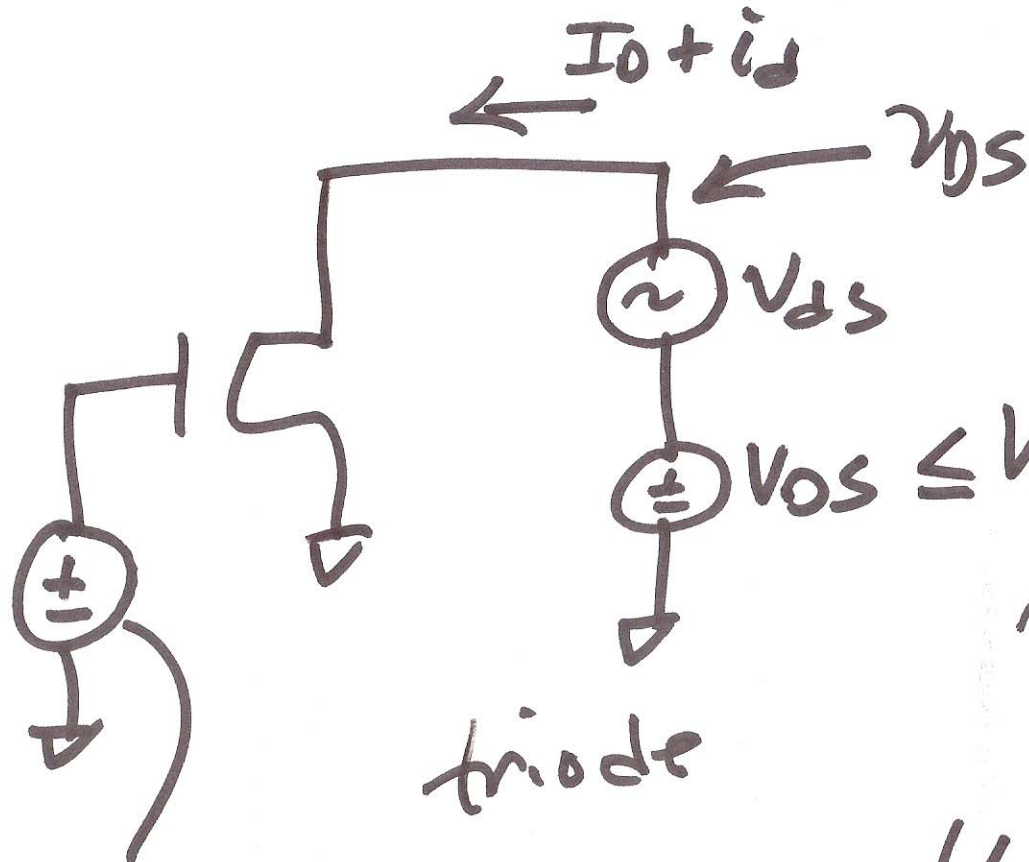

$$V_{OS} \leq V_{GS} - V_{THN}$$

$$v_{OS} = v_{ds} + V_{OS}$$

triode

$$V_{GS} > V_{THN} \quad I_0 + i_d = K_N \left((V_{GS} - V_{THN}) v_{OS} - \frac{v_{OS}^2}{2} \right)$$

$$i_d = DC + AC$$

$$\frac{1}{R_{en}} = \frac{\delta i_d}{\delta v_{OS}} \Bigg|_{\substack{I_D = \text{const} \\ V_{GS} = \text{const}}} = K_N (V_{GS} - V_{THN}) - v_{OS}$$

5)

$$R_{CH} = \frac{1}{K_N \left((V_{GS} - V_{THN}) - \underbrace{(V_{DS} + V_{DS})}_{V_{DS}} \right)}$$


$$V_{DS} \gg V_{DS}$$


$$R_{CH} = \frac{1}{K_N \left((V_{GS} - V_{THN}) - V_{DS} \right)}$$

$$\text{if } V_{GS} - V_{THN} \gg V_{DS}$$


$$R_{CH} \approx \frac{1}{K_N (V_{GS} - V_{THN})}$$


Automatic Gain Control

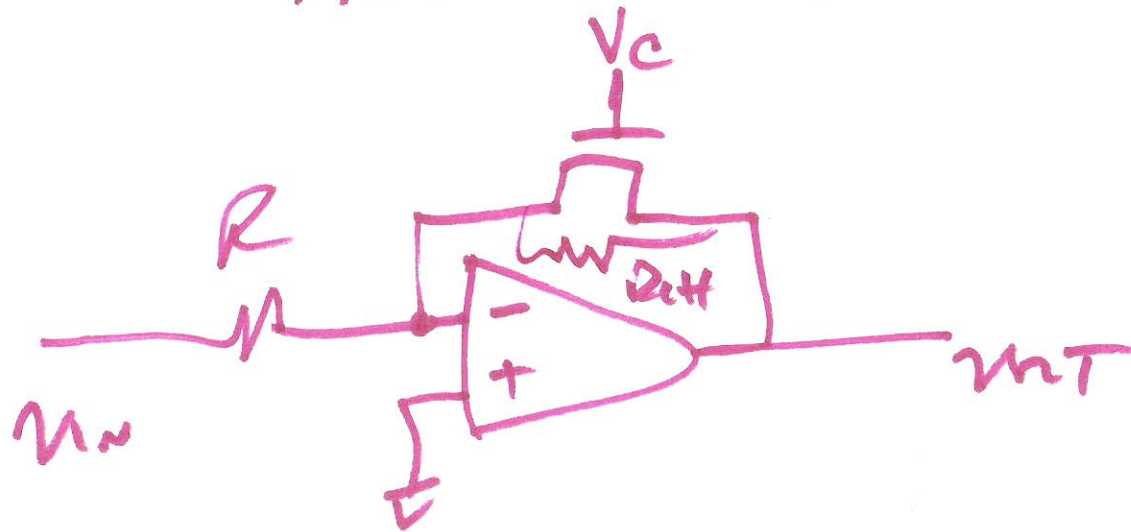

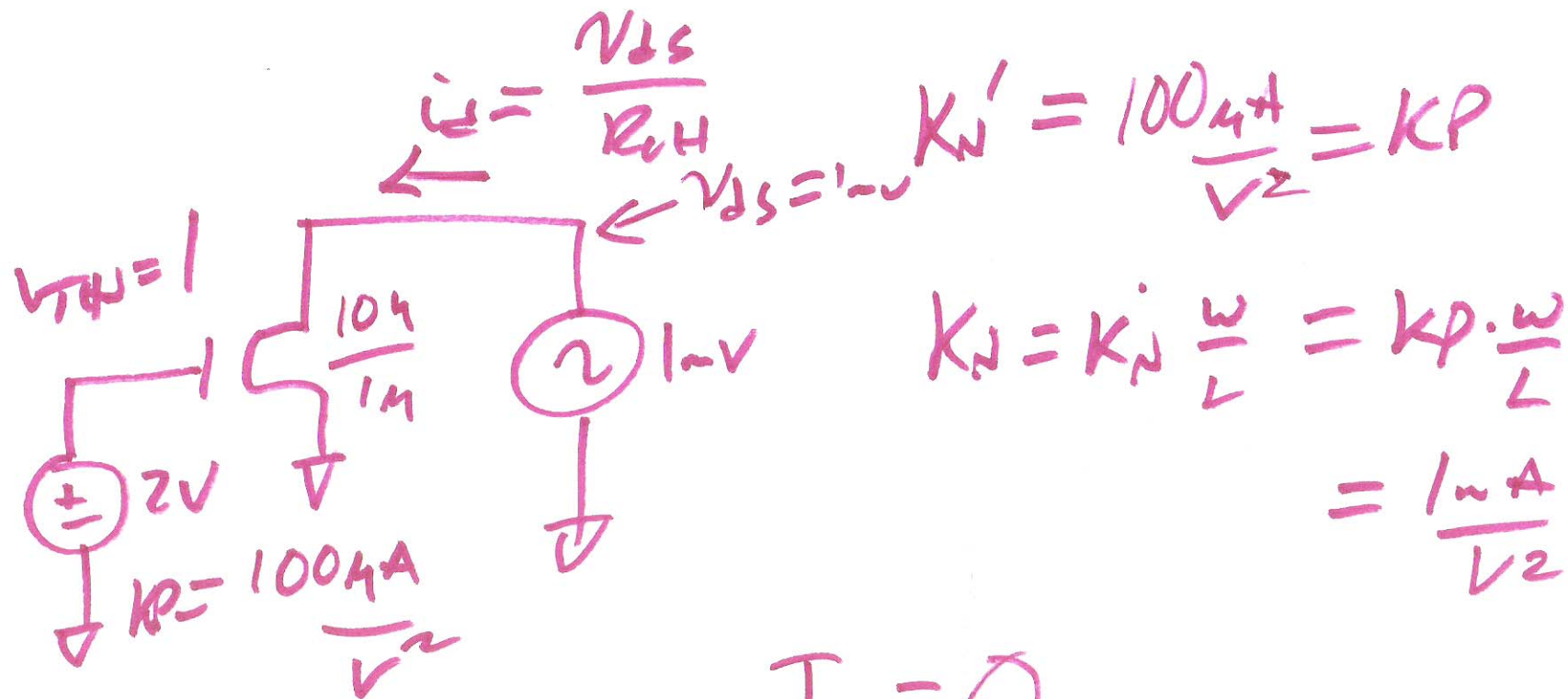

$I_D = 0$

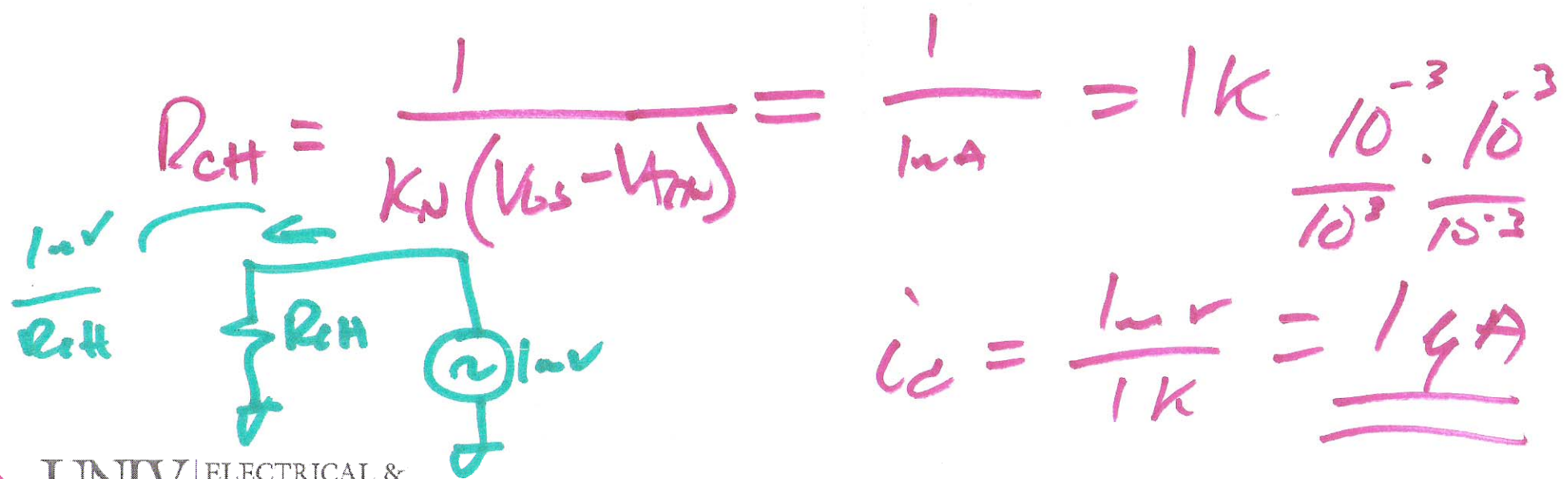

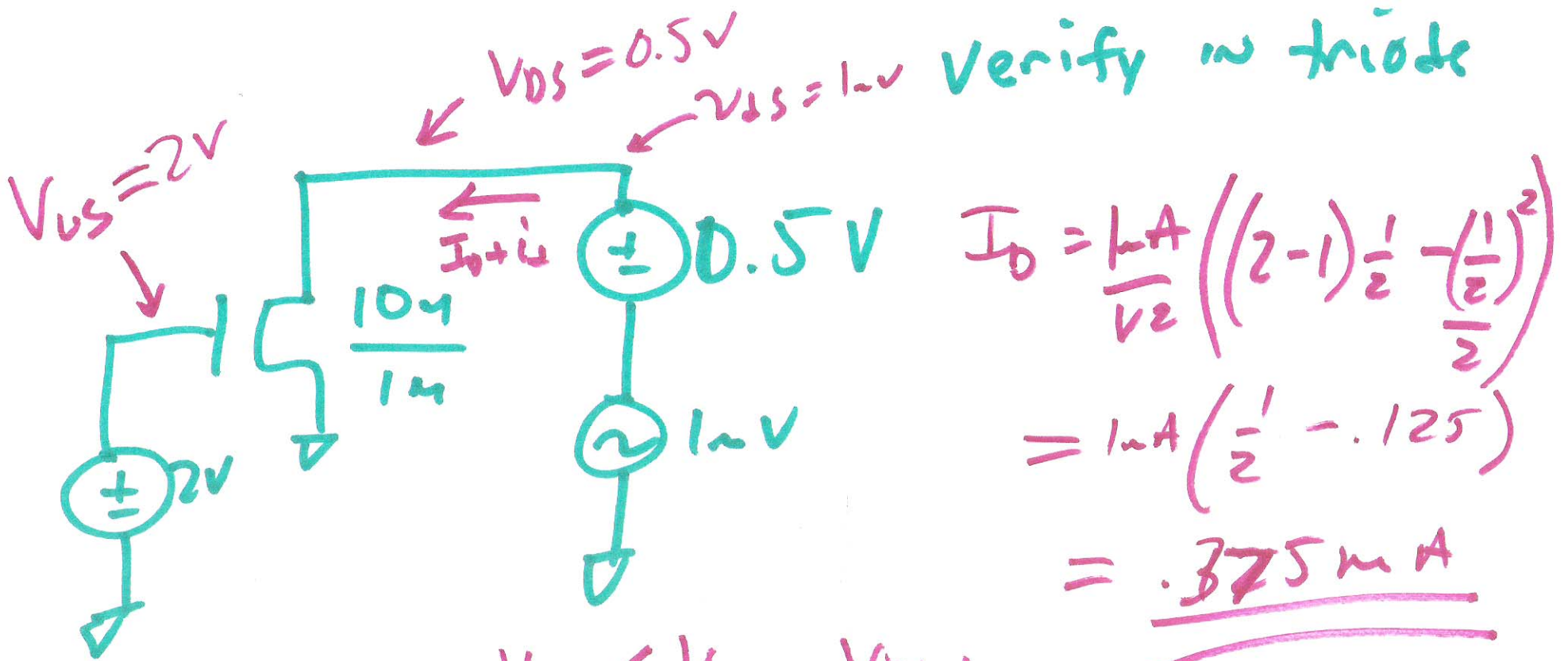

$$I_D = \frac{1 \mu A}{\sqrt{2}} \left((2-1) \frac{1}{2} - \left(\frac{1}{2} \right)^2 \right)$$

$$= 1 \mu A \left(\frac{1}{2} - .125 \right)$$

$$= \underline{\underline{.375 \mu A}}$$

$$V_{DS} \leq V_{GS} - V_{thn}$$

$$\frac{1}{2} \stackrel{?}{\leq} 2 - 1$$



Yes

$$R_{eff} = \frac{1}{\frac{1 \mu A}{\sqrt{2}} \left((2-1) - \frac{1}{2} \right)}$$

$$I_D = \frac{1 \mu V}{2K} = \frac{1}{2} \mu A$$


9)

NMOS

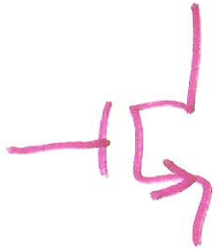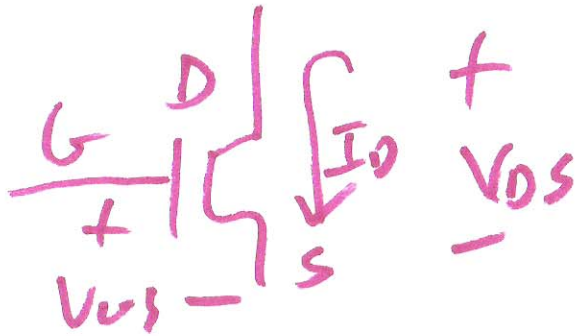

PMOS

$$V_{T0} = -1$$

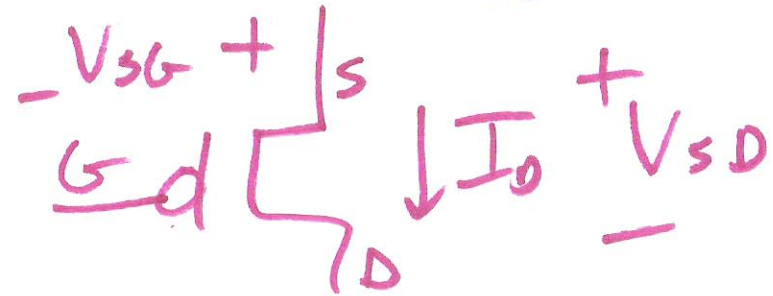


$$I_D = \frac{K_P}{2} (V_{SG} - V_{THP})^2$$

$$V_{SG} > V_{THP} \text{ SAT}$$

$$V_{SD} \geq V_{SG} - V_{THP}$$

CMOSedu.com

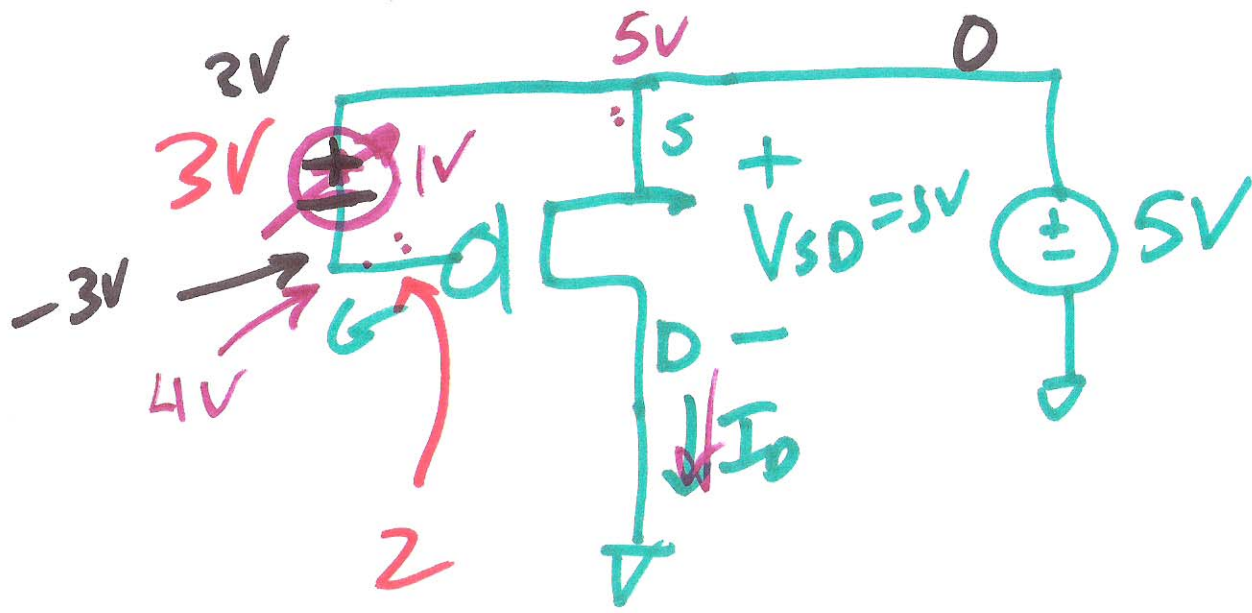

$$\begin{aligned}
 V_{SG} &= V_S - V_G \\
 &= 1 \\
 &= 5 - 4
 \end{aligned}$$

$$I_D = \frac{k_p}{2} (V_{SG} - V_{TH})^2$$

