



EE 320

Engineering


Electronics I

March 25, 2015

Lecture 19

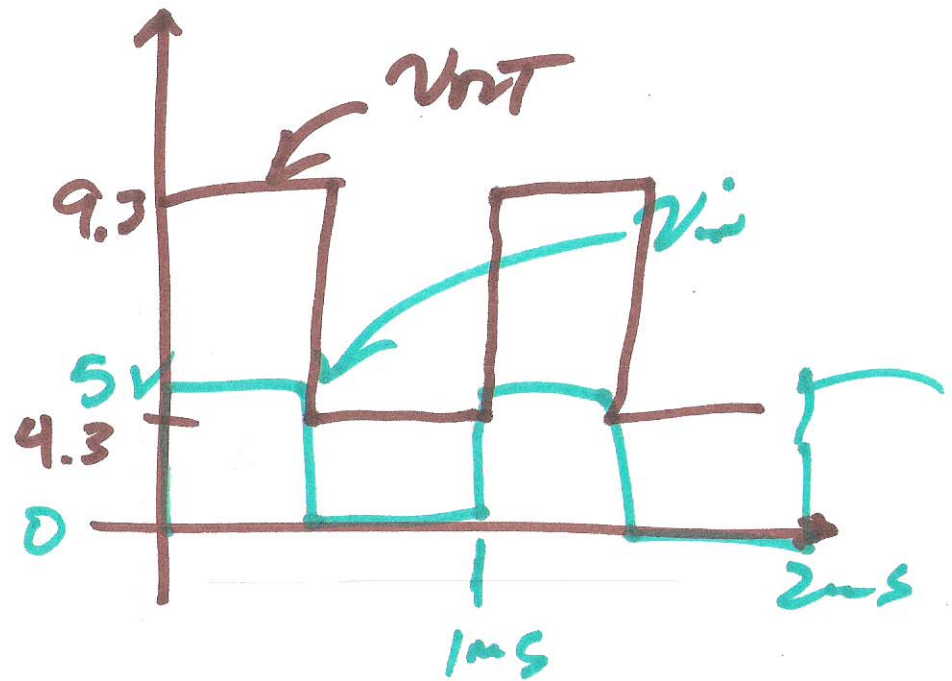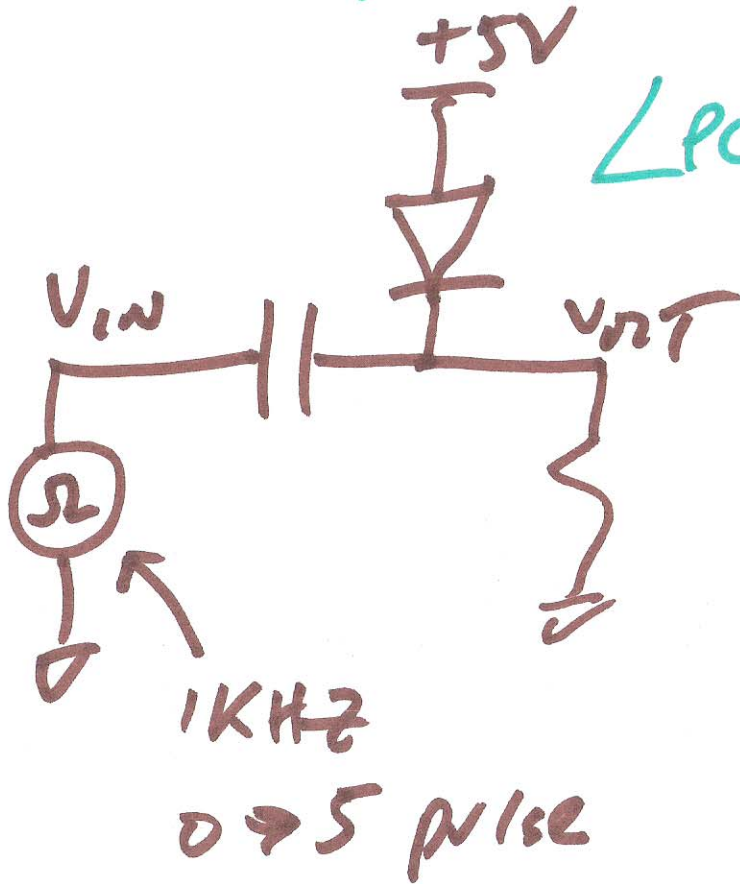
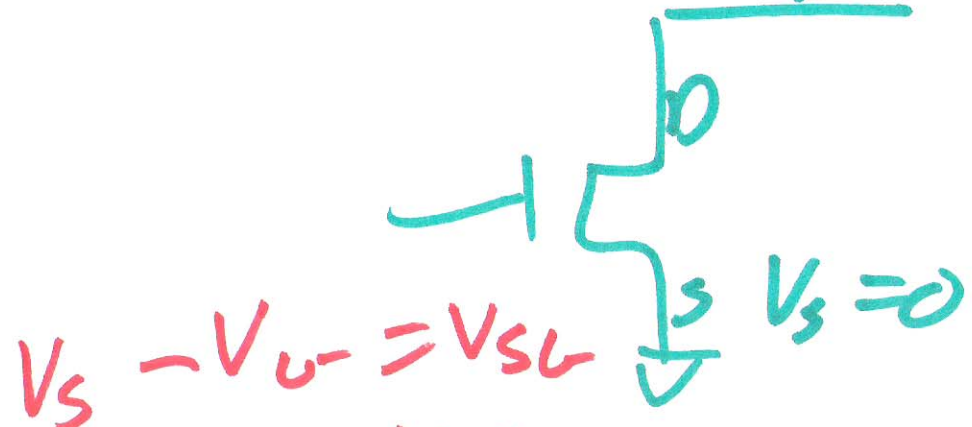
$$V_D = V_{DS} = V_D - V_S \rightarrow 0$$




$$V_S - V_{D-} = V_{SD}$$

$$V_G - V_S = V_{GS} \text{ triode}$$

PMOS


$$V_{THP} = N_{eq}$$

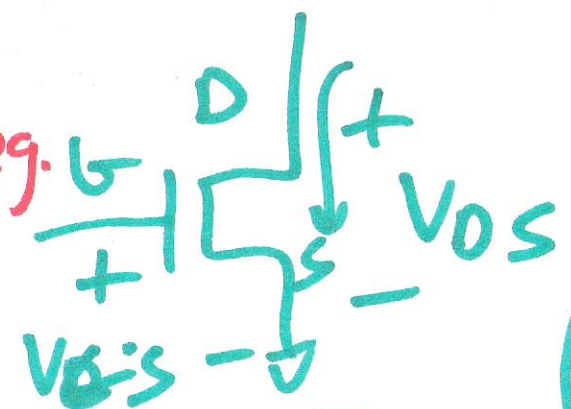

SAT:


$$V_{GS} > V_{THP}$$

$$V_{DS} \geq V_{GS} - V_{THP}$$

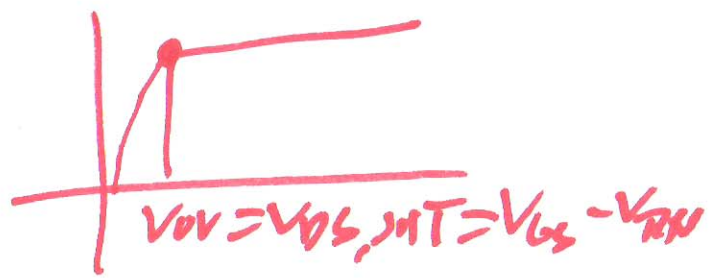

triode

V_{DD}

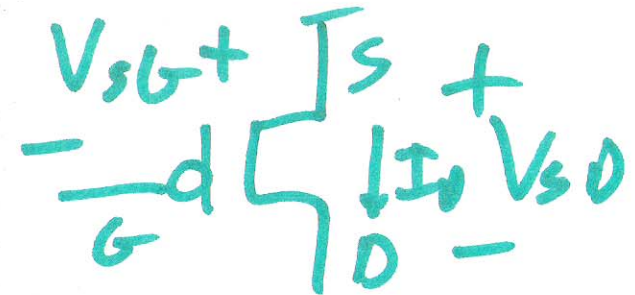

$$\text{SAT: } V_{SD} > V_{THP}$$


$$V_{SD} \geq V_{SG} - V_{THP}$$

$$V_{OV} = V_{GS,SAT}$$

CMOSedu.com

2)

SAT

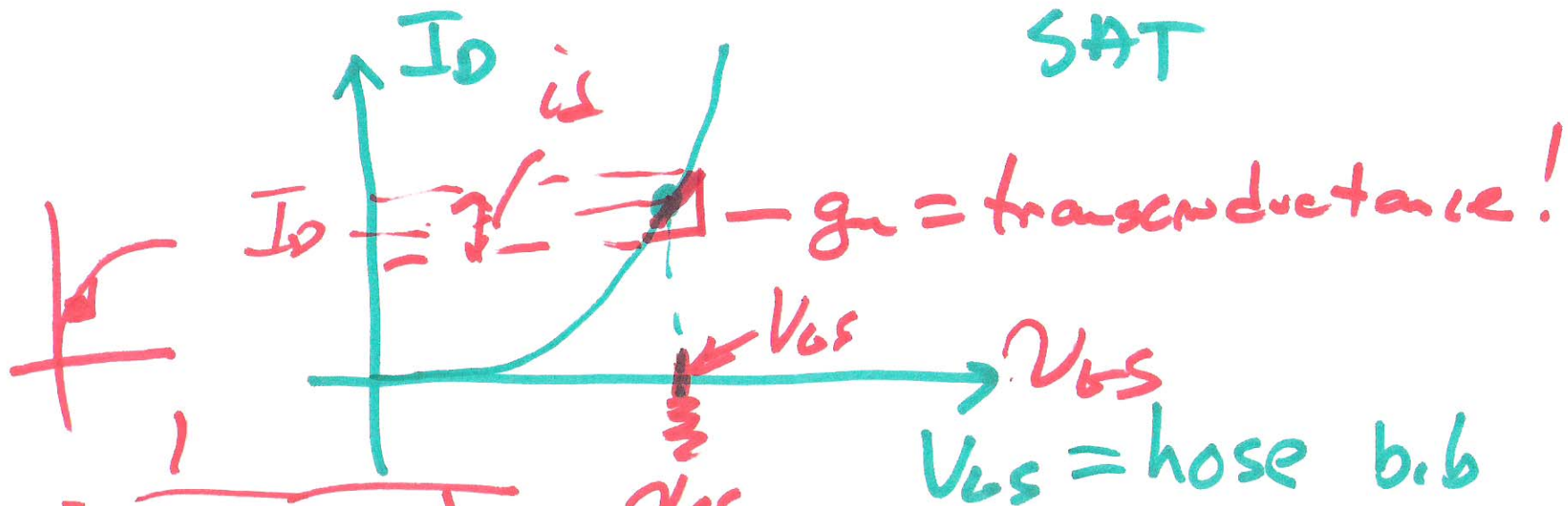


$R_{eff} = \frac{1}{K_n (V_{GS} - V_{THW})}$

↑ triode

$g_m = \frac{C_d}{V_{GS}}$

$V_{DS} \geq \frac{V_{GS} - V_{THW}}{2}$

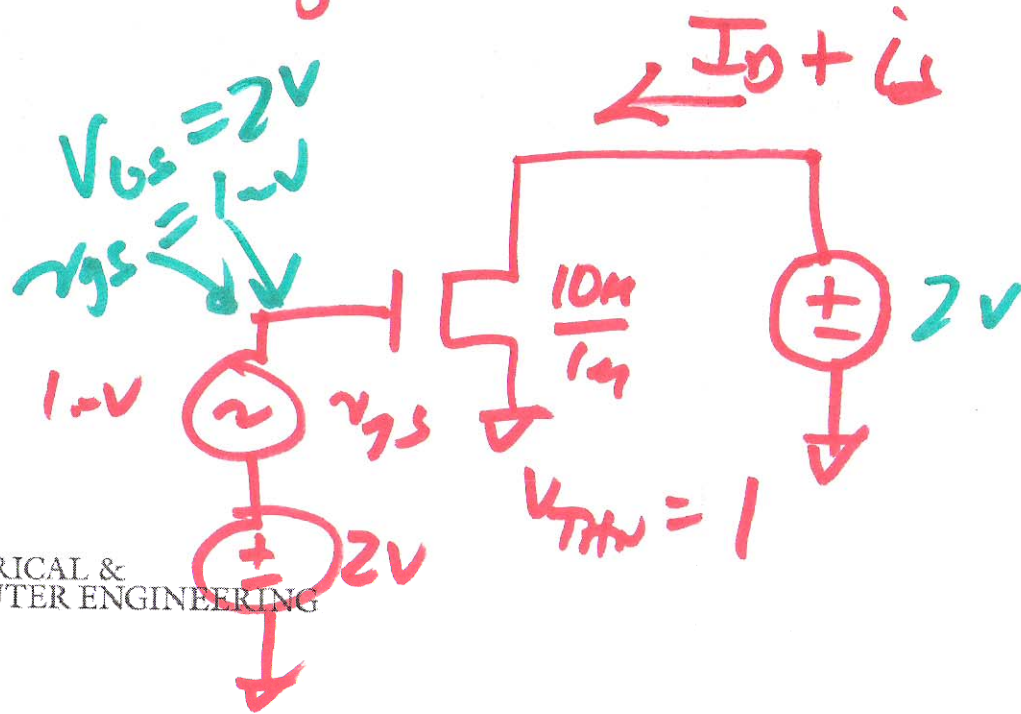

3)

$$i_D = i_d + I_D = \frac{K_N}{2} \left(\underbrace{v_{gs} + V_{GS}}_{v_{GS}} - V_{THN} \right)^2$$


$$g_m = \frac{\delta i_D}{\delta v_{GS}} \left| \begin{array}{l} I_D = \text{CONST} \\ V_{GS} = \text{CONST} \end{array} \right. = K_N \left(v_{GS} - V_{THN} \right)$$

\downarrow
 $v_{GS} + V_{GS}$

$$g_m \approx K_N (V_{GS} - V_{THN})$$

Small-signal Approx

$$v_{GS} \Rightarrow v_{gs}$$

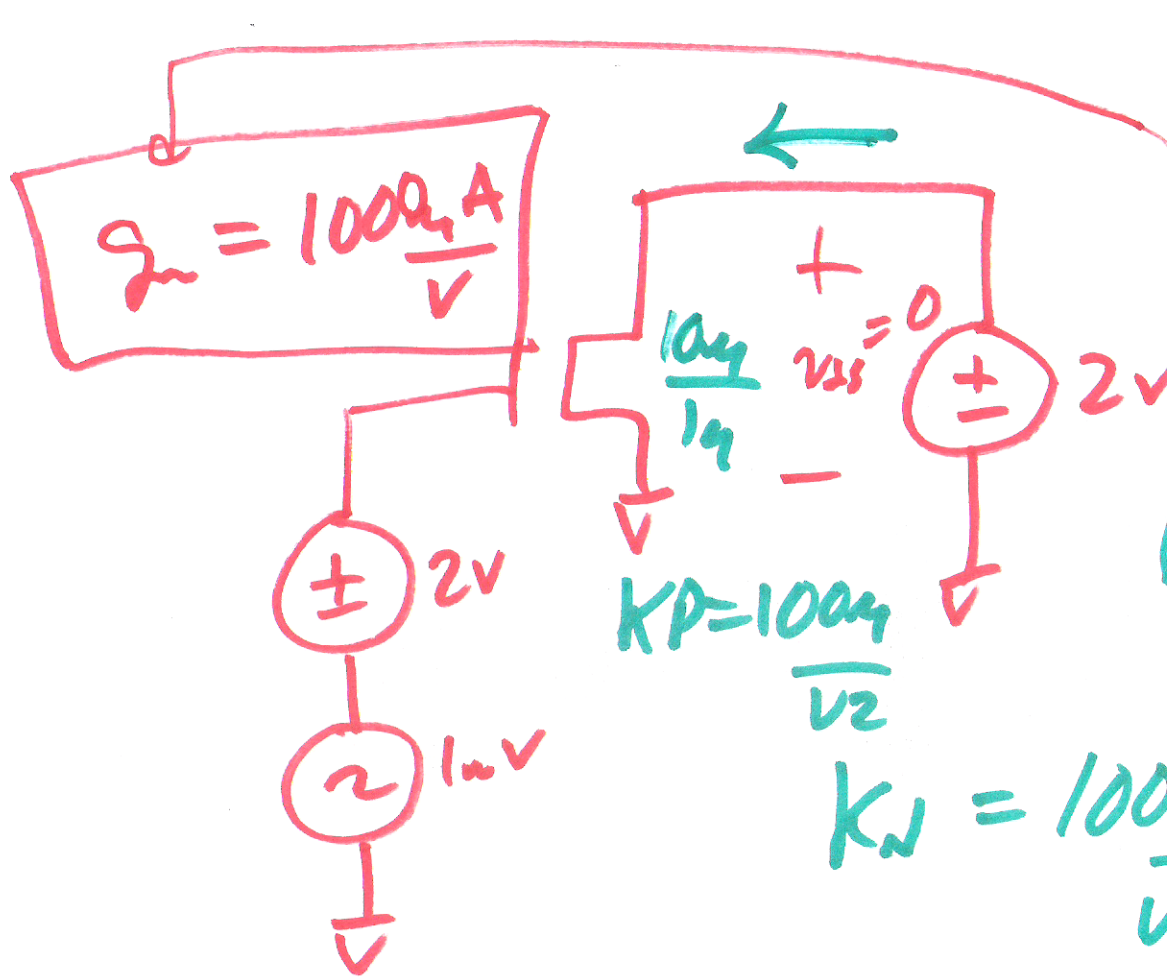

$$g_m = K_n (V_{GS} - V_{THN})^2$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{THN})^2$$

$$V_{GS} - V_{THN} = \sqrt{\frac{2I_D}{K_n}}$$


$$K_n = 100 \mu A \cdot \frac{10}{\sqrt{2}} = \frac{1 \mu A}{\sqrt{2}}$$

$$I_D = \frac{1 \mu A / \sqrt{2}}{2} (2 - 1)^2 = 500 \mu A$$

$$g_m = K_n \sqrt{\frac{2I_D}{K_n}} = g_m = \sqrt{2I_D \cdot K_n}$$

5)


AC CKT



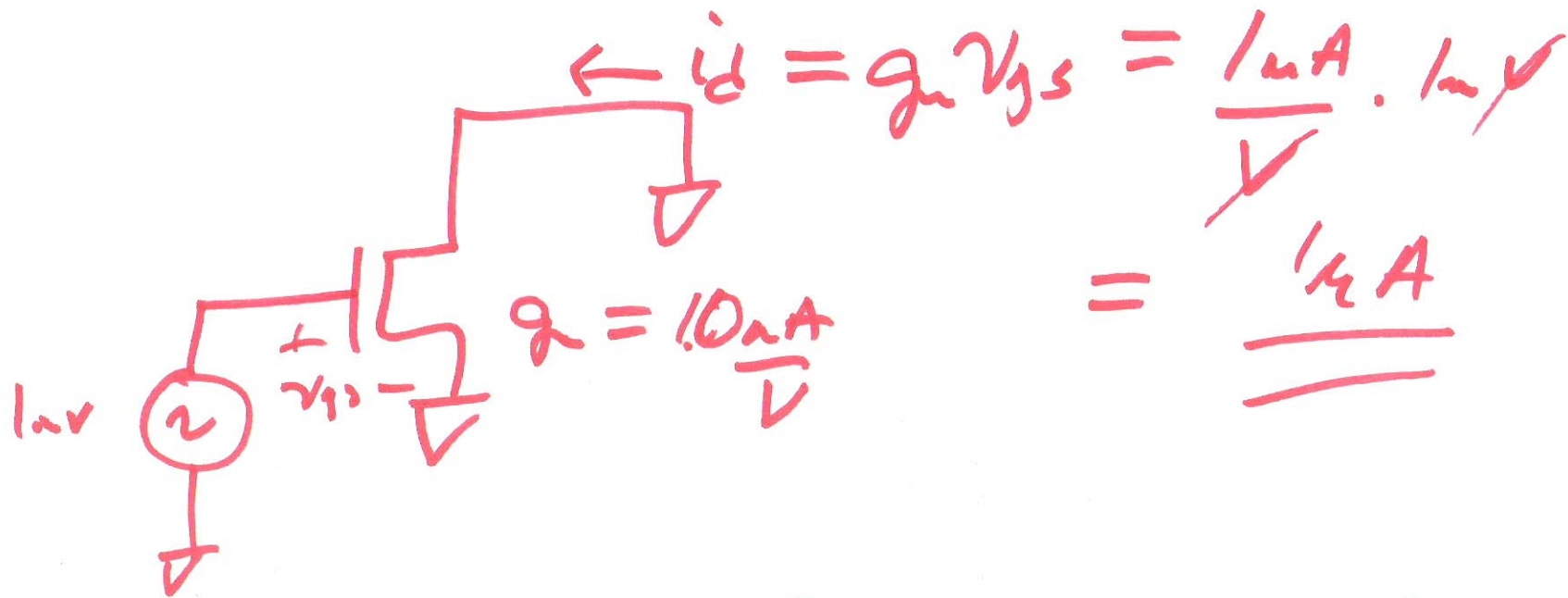


$$20 \log 10^{-3} = -60 \log 10$$


$$= -60 dB = \underline{\underline{1mV}}$$
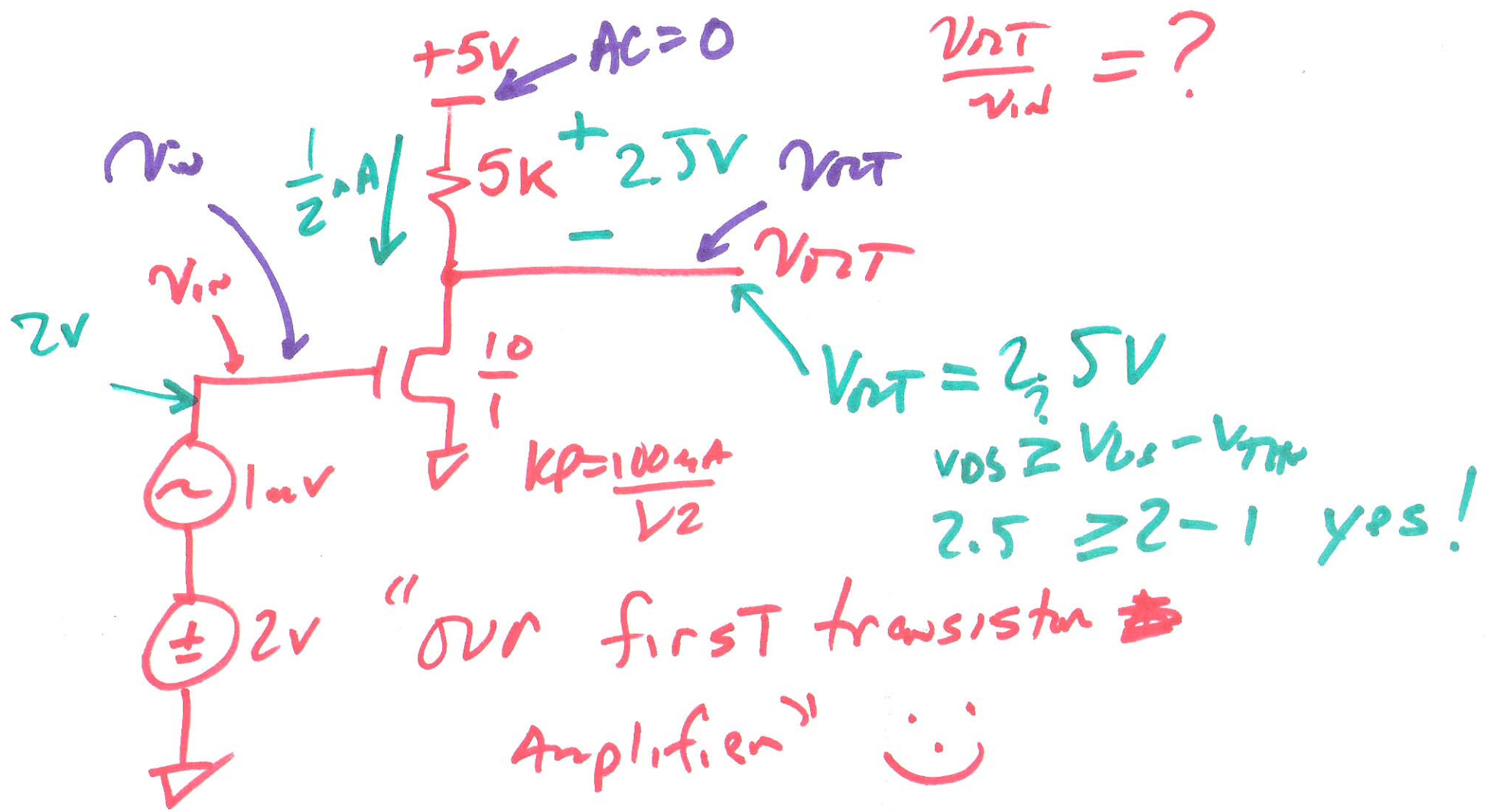
$$-20 \log 10^6 = -120 dB = \underline{\underline{1\mu A}}$$



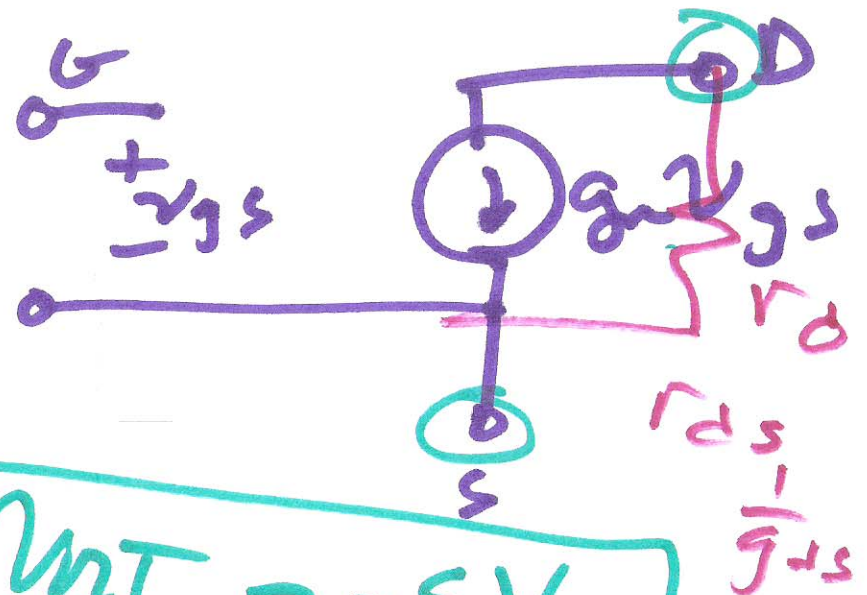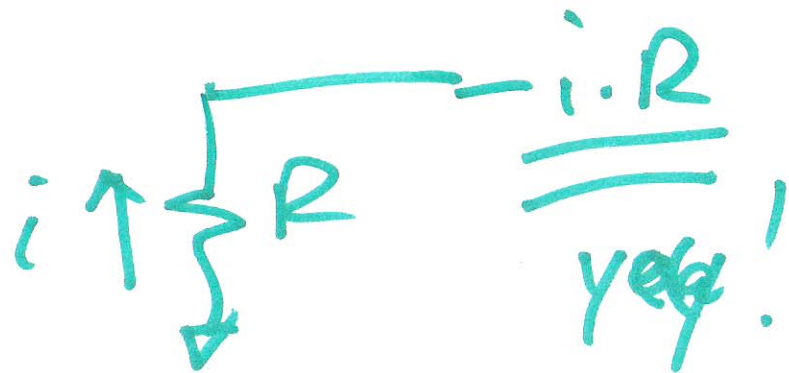
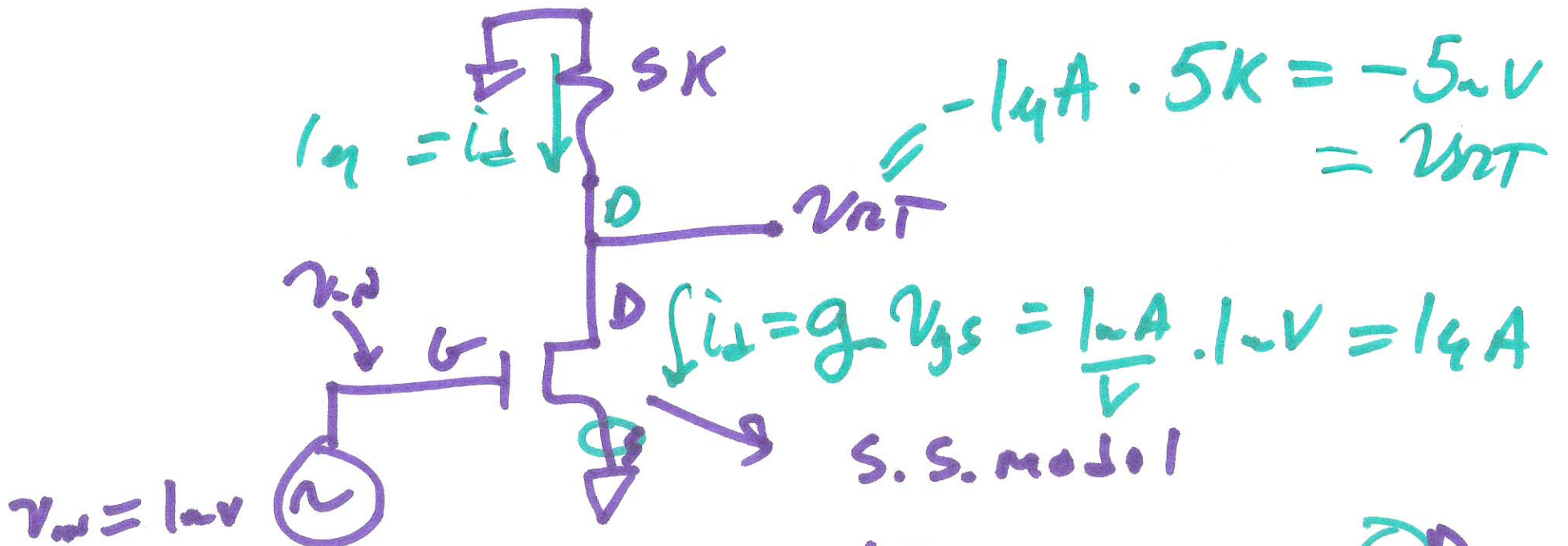


$$\frac{v_{out}}{v_{in}} = -5V$$

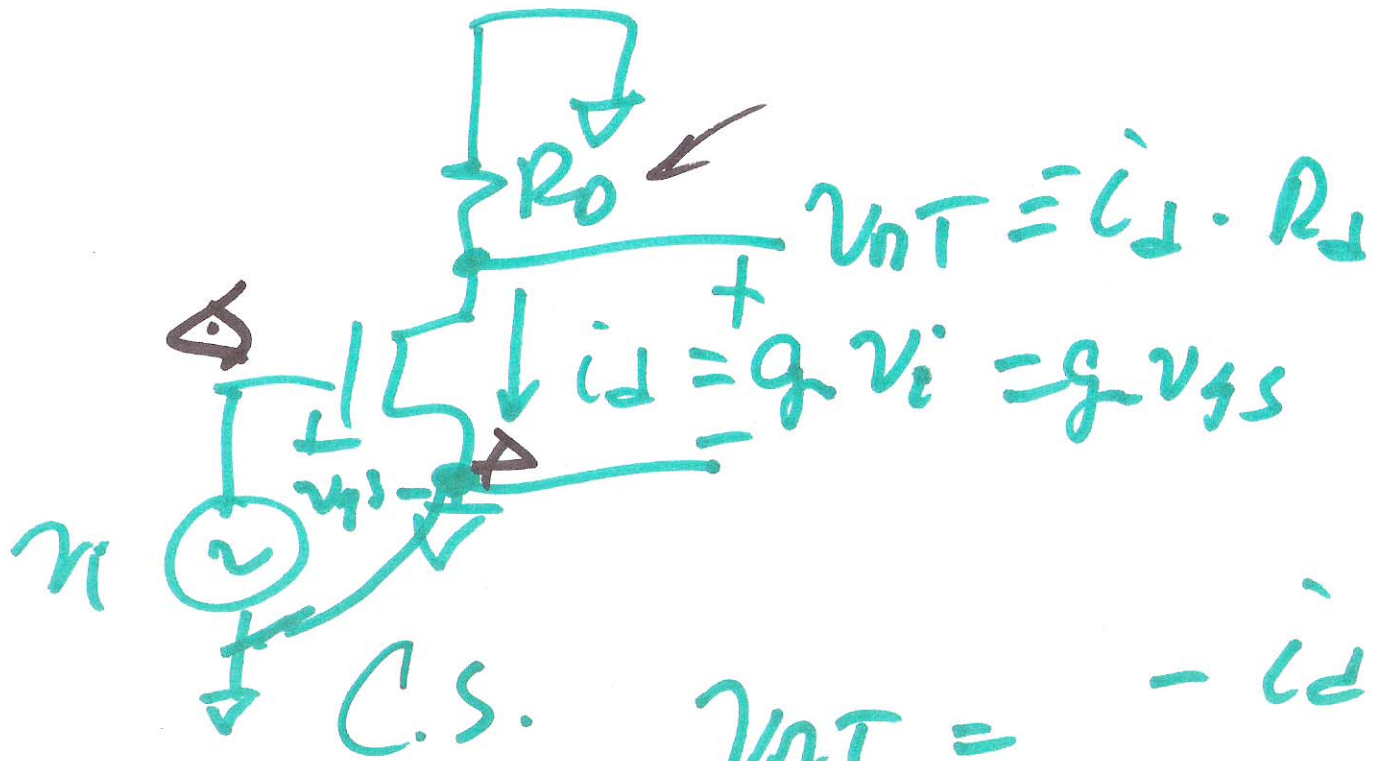


COMMON
 SOURCE $v_{gs} = v_i$
 Amplifier
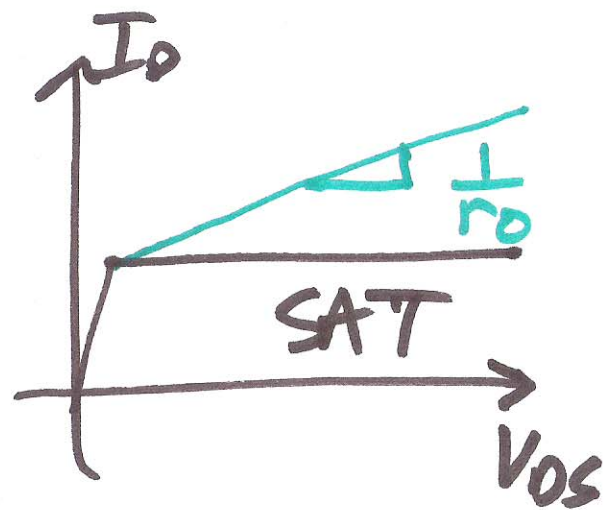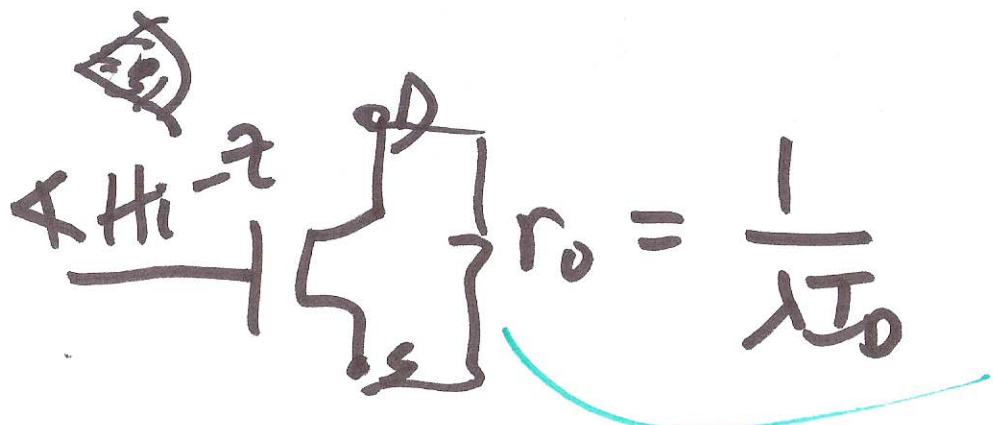
$$\frac{v_{OUT}}{v_i} = \frac{-i_d \cdot R_D}{i_d / g_m} = -\frac{R_D}{1/g_m} = -g_m R_D$$





IN SAT

$$r_o = \frac{1}{\lambda I_D}$$

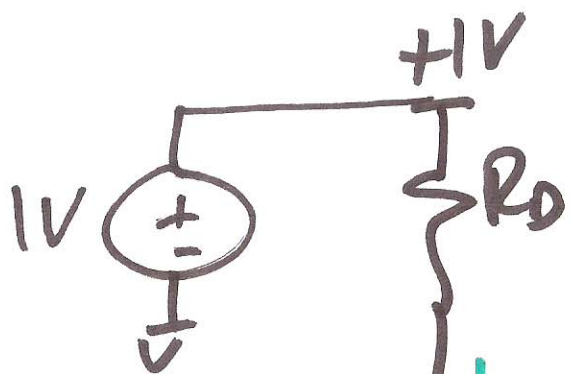

$V_{THN} = 2V$
 0.8
 Assume SAT

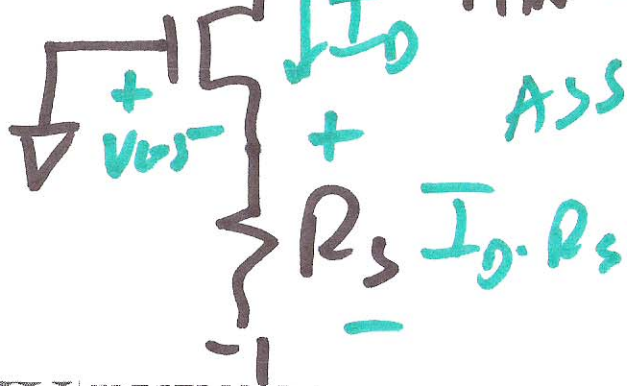

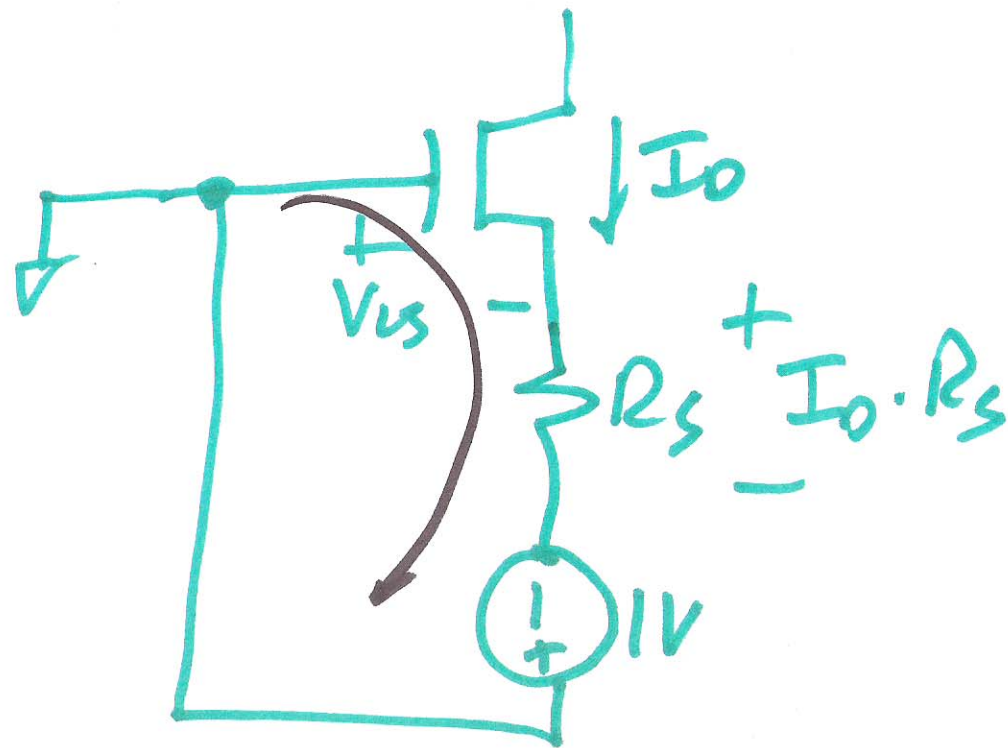

$$V_{GS} + I_D \cdot R_S - 1 = 0$$

ASSUME SAT

$$I_D = \frac{K_N}{2} (V_{GS} - V_{THN})^2$$