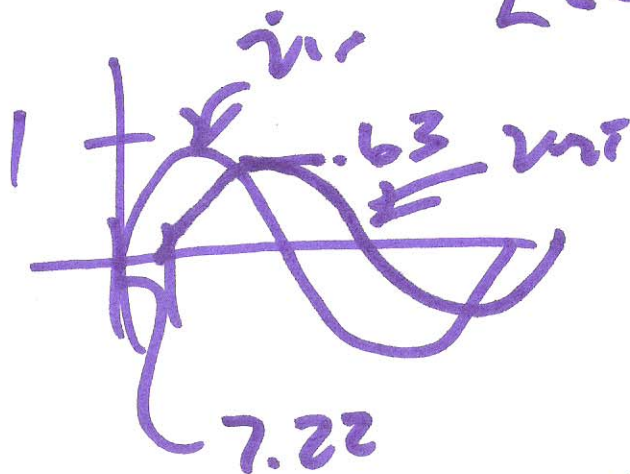


Lecture 21

April 13, 2015

EE 320



7.22

$$20 \log \frac{V_{VT}}{V_N} = -4 \text{ dB} = .63$$

$$\frac{V_{VT}}{V_N} = 10^{-4/20} = .63$$


$$V_N = 1$$

$$V_{VT} = .63$$

$$\frac{t_d}{T} \cdot 360 = \theta$$

$$t_d = \frac{52}{360} \cdot 50 \text{ ns}$$
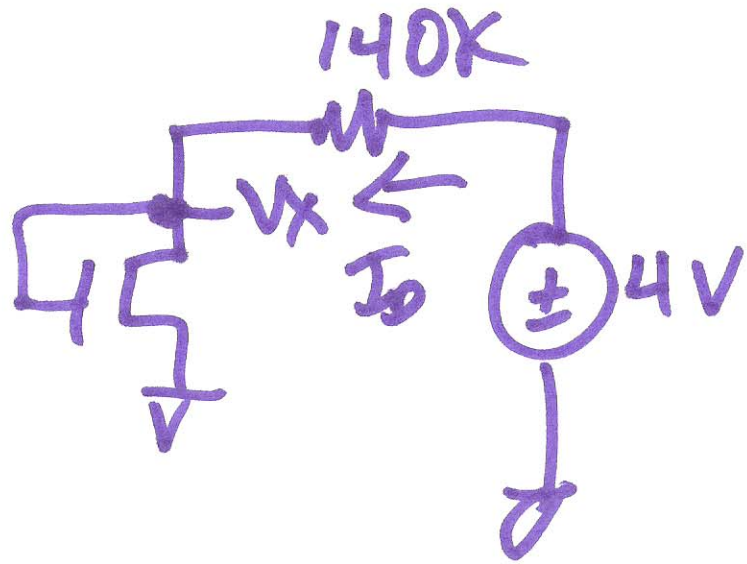
$$t_d = \underline{\underline{7.22 \text{ ns}}}$$





$$\frac{4 - V_x}{140K} = \frac{K_P \mu}{2L} (V_x - V_{TH})^2$$

$$I_D = 20 \mu A$$

$$V_x = 1.2V$$

nmos

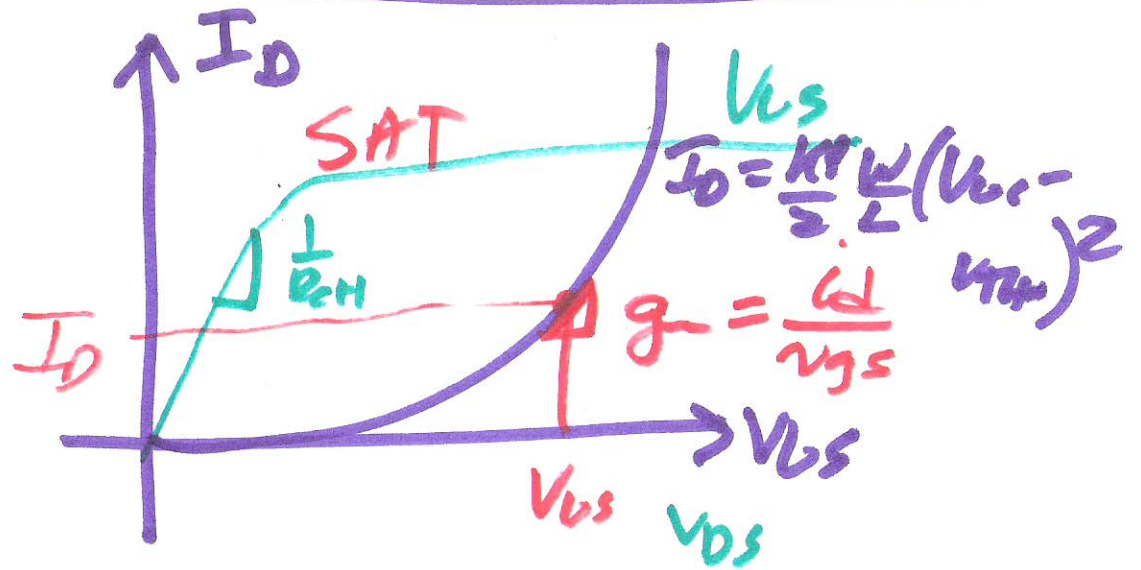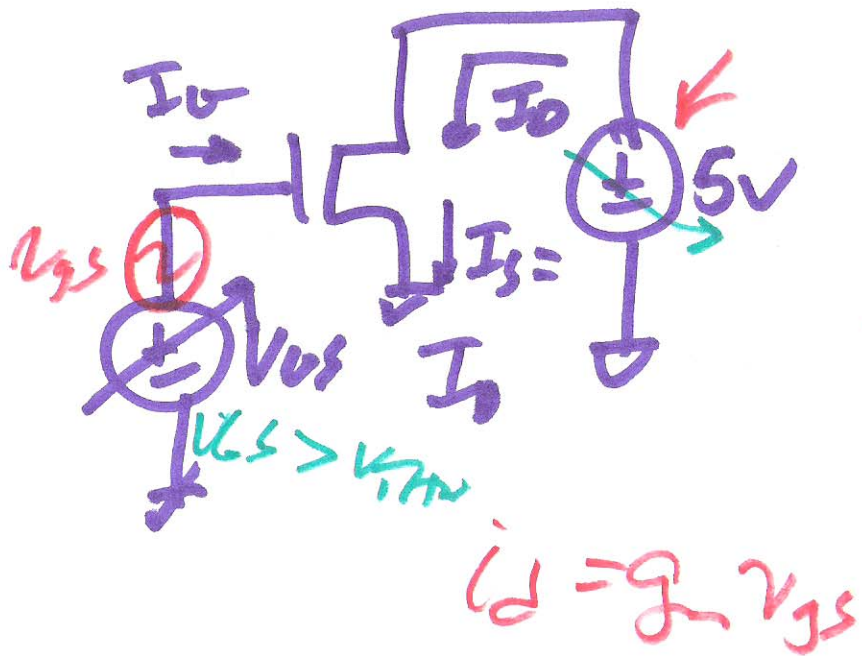

2)

$$g_m = \left. \frac{\delta i_D}{\delta v_{GS}} \right|_{\substack{I_D = \text{CONST} \\ v_{DS} = \text{CONST}}} = \frac{\delta}{\delta v_{GS}} \frac{k_p \mu}{2L} \left(\frac{v_{GS} + v_{GS} - V_{THN}}{v_{GS}} \right)^2$$


$$\frac{\delta(x-k)}{\delta x} = 1 \quad \rightarrow \quad = k_p \cdot \frac{\mu}{L} (v_{GS} - V_{THN}) \cdot \frac{\delta}{\delta v_{GS}}$$

$$i_D = I_D + i_d$$

$$v_{GS} = v_{GS} + v_{GS}$$

$$v_{GS} \gg v_{GS}$$


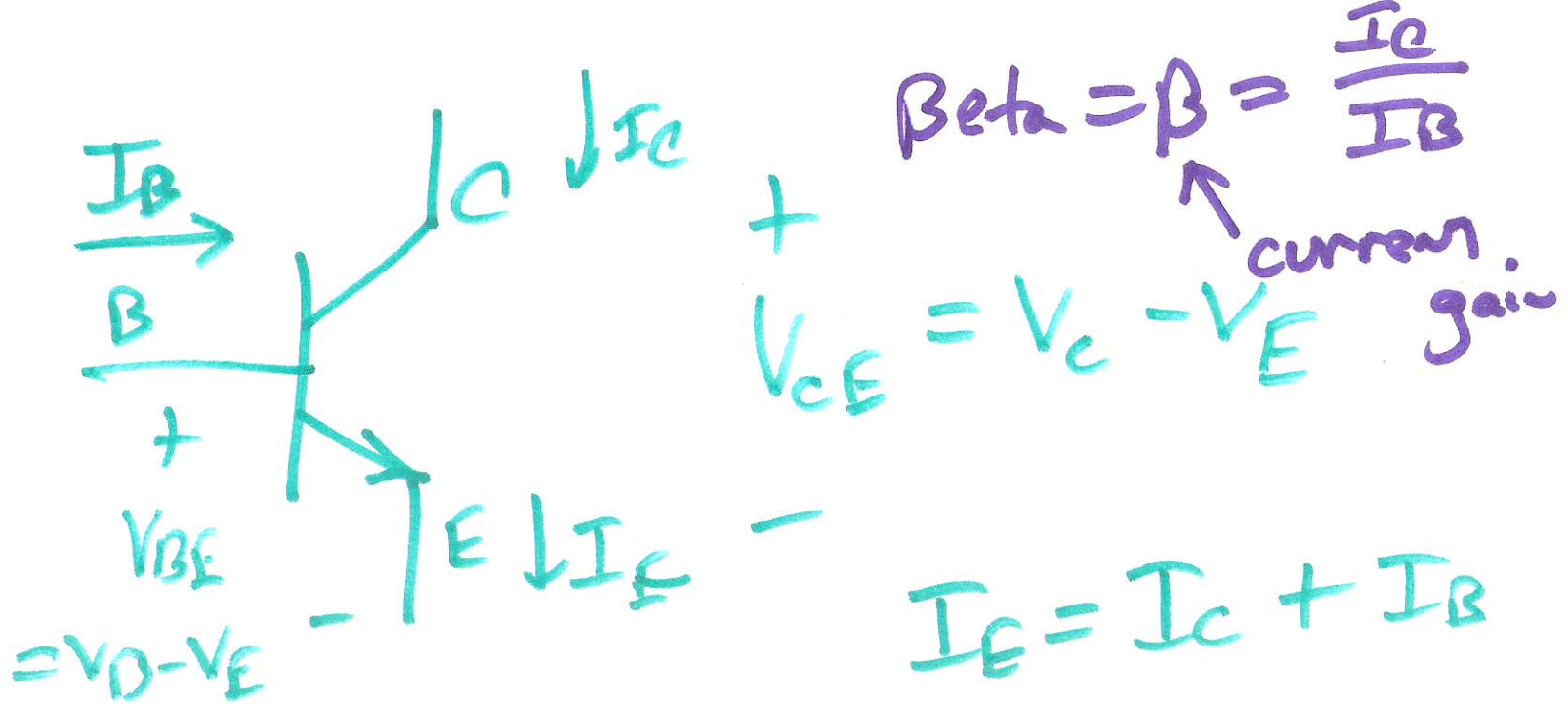
$$g_m = k_p \cdot \frac{\mu}{L} (v_{GS} - V_{THN})$$





$\beta = \frac{I_C}{I_B}$
 current gain

$I_E = I_C + I_B$

Bipolar Junction Transistors (BJTs)

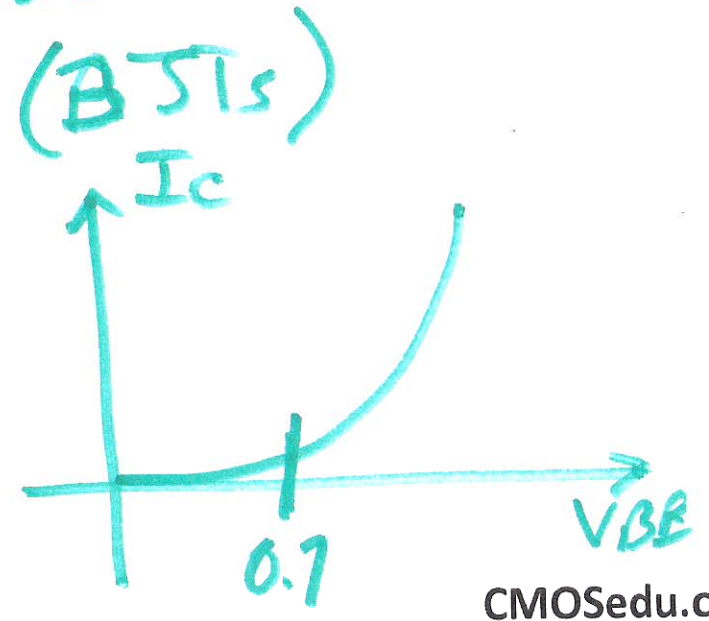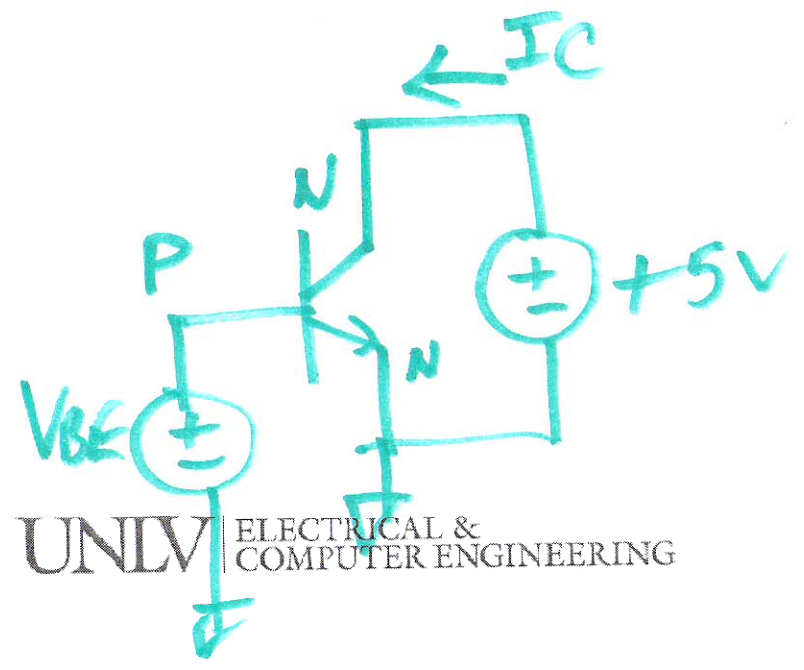

4)

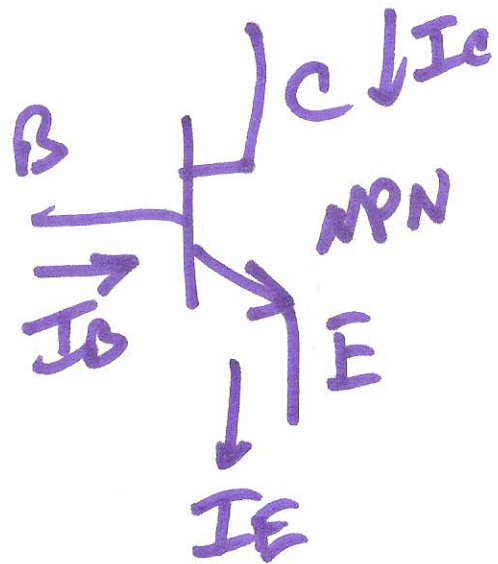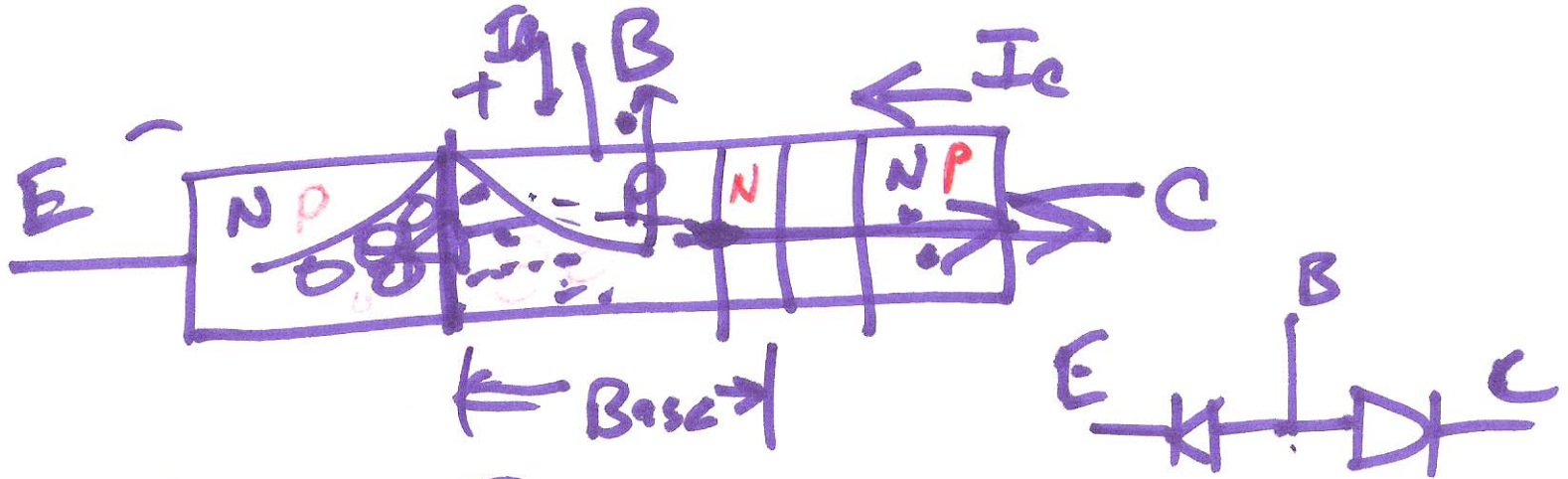


$$\frac{I_C}{I_E} = \alpha$$

fraction of I_C is of I_B

$$\beta = \frac{\alpha}{1-\alpha}$$


$$I_C + I_B = I_E$$

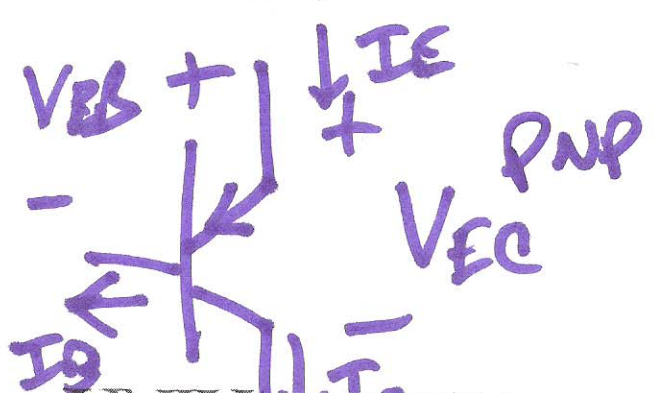


$$I_E = \alpha I_C$$

$$I_B \cdot \beta = I_C$$

$$I_B (\beta + 1) = I_E$$

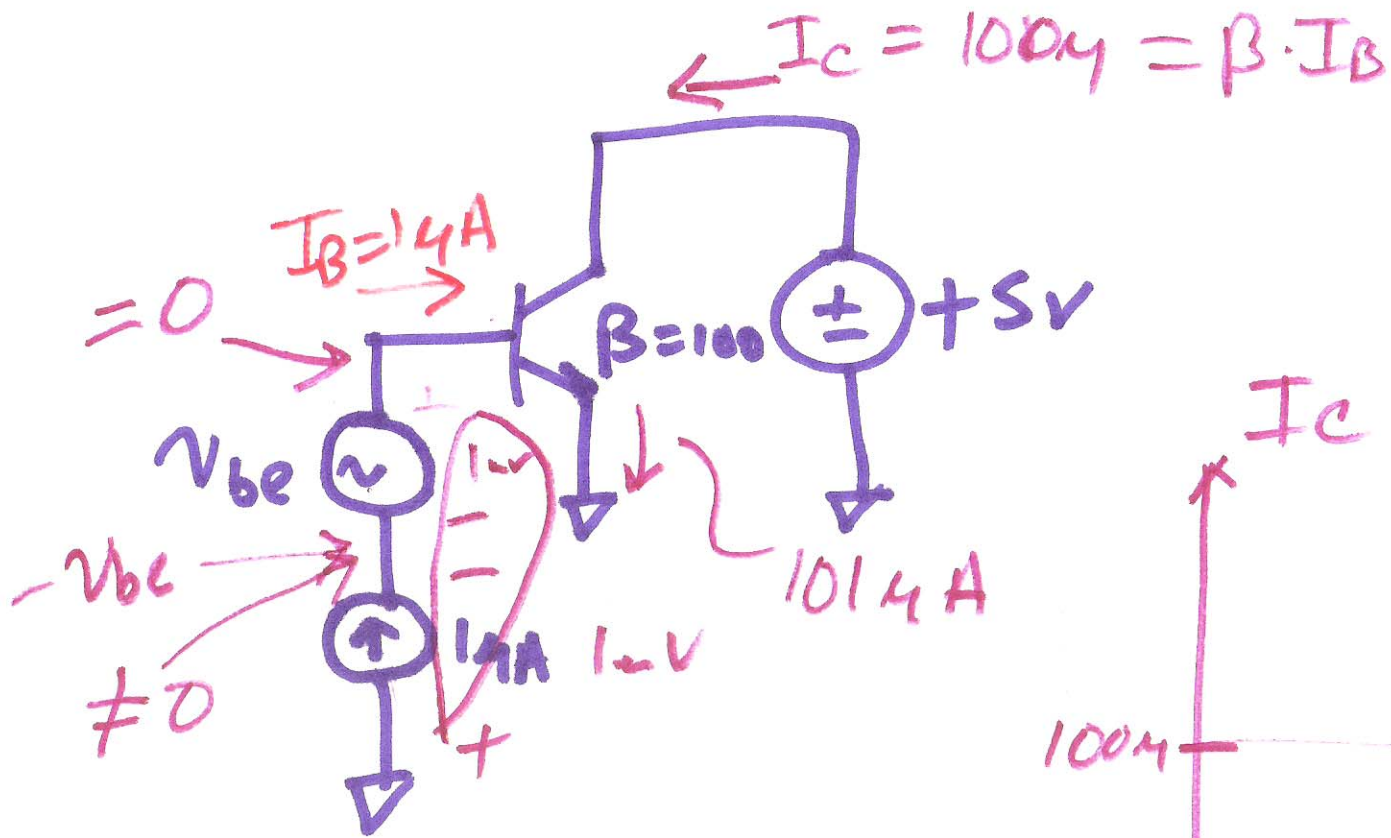


MISTAKE
 NO AC CURRENT
 LTH flow

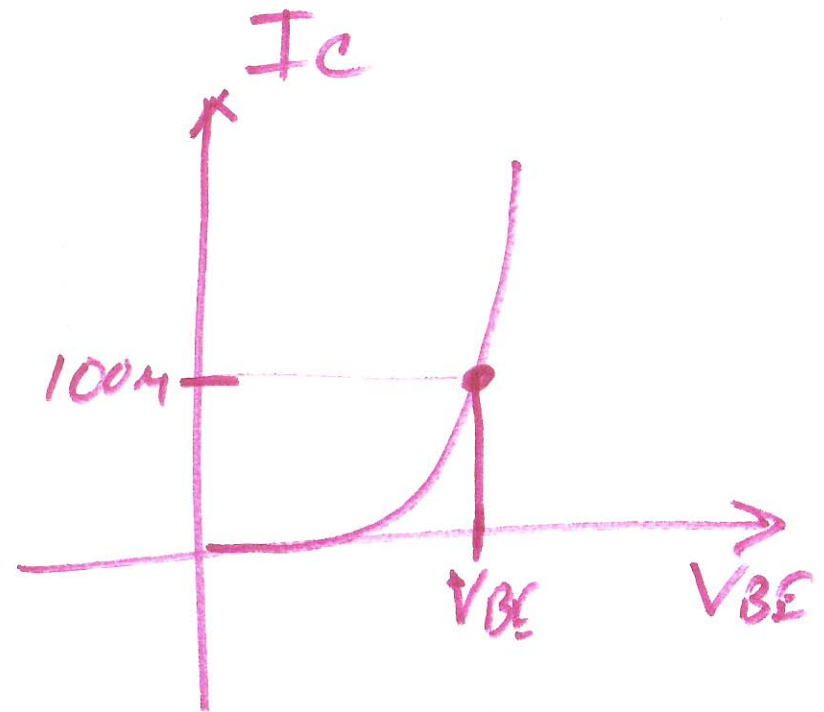

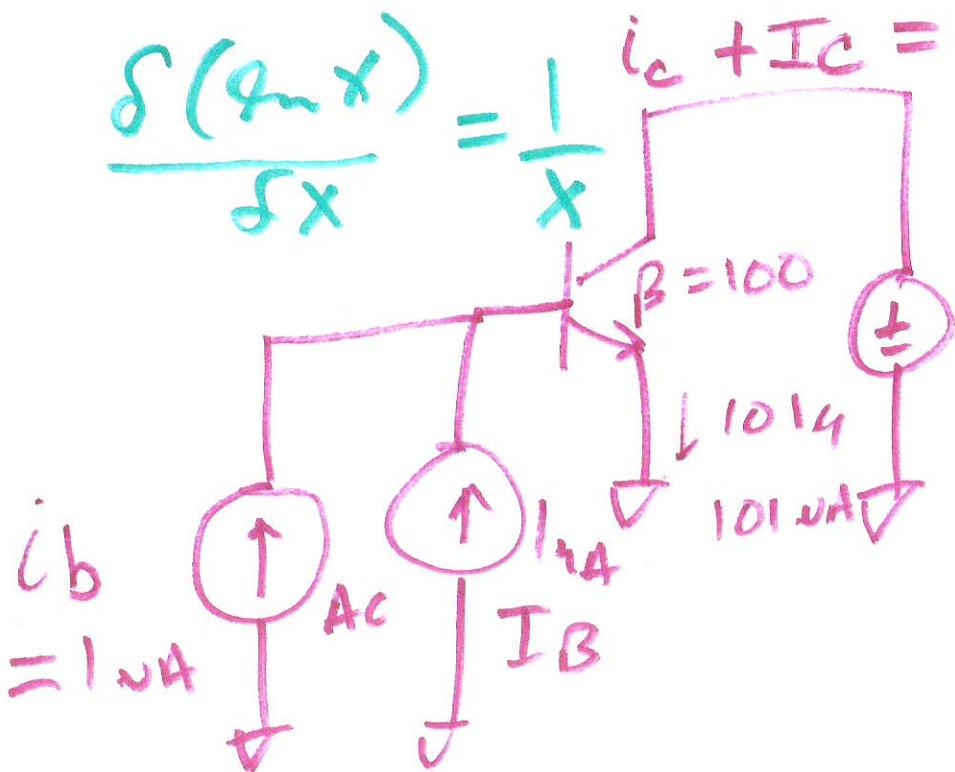6)

$$\frac{\delta(i_c + I_c)}{\delta x} = \frac{1}{x}$$




$$i_c + I_c = 100.4 \mu A = \beta I_B + \beta \cdot i_b = 100 \mu A$$

$$I_0 = I_s (e^{v_{be}/NkT} - 1)$$

forwarded v_{be}/NkT

$$I_0 = I_s e^{v_{be}/NkT}$$

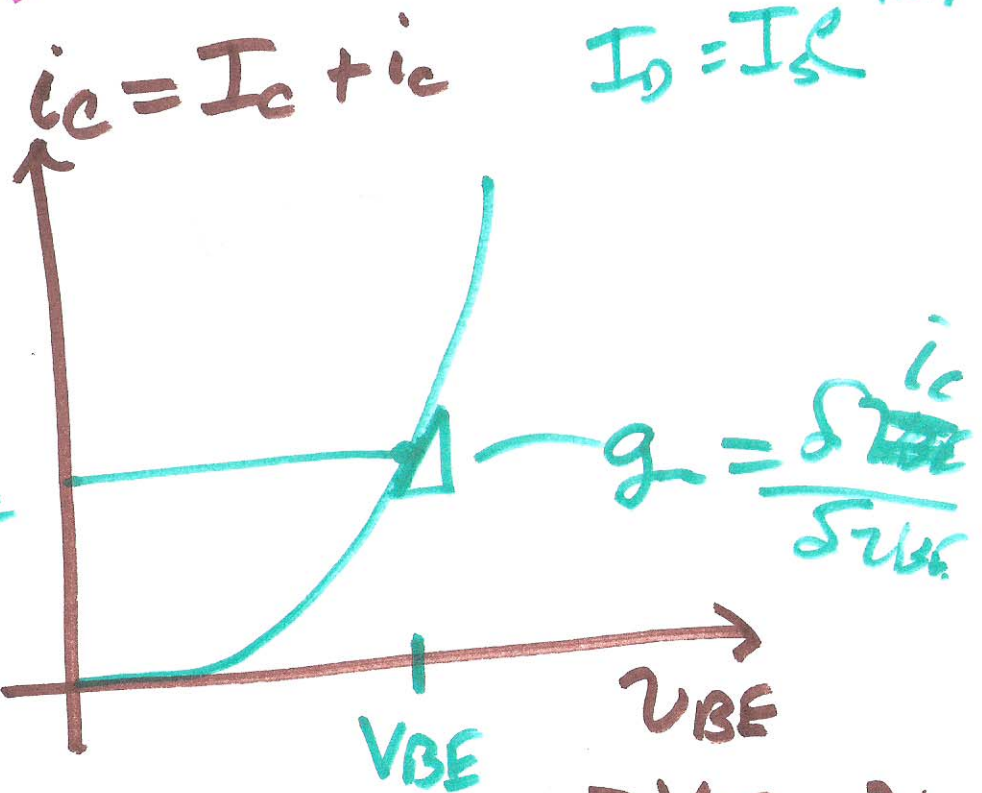

$$\beta I_B = I_c$$

$$I_c = I_s e^{v_{be}/NkT}$$

$$\frac{1}{g} = \frac{\delta v_{be} + v_{be}}{\delta i_c} = NkT \left(\frac{I_c + i_c}{I_c} - \frac{I_s}{I_c} \right) = \frac{1}{g} = \frac{NkT}{I_c + i_c}$$

7)



$$g_m \approx \frac{I_c}{N V_T}$$

$$I_c = \text{~~100 \mu A~~ } 100 \mu A$$

$$g_m = \frac{100 \mu A}{1.25 mV} = 4 \frac{\mu A}{V}$$

$$i_c = v_{be} \cdot g_m$$
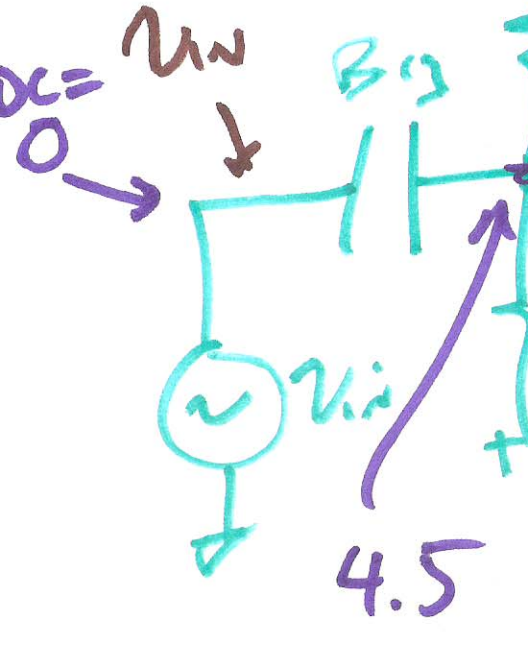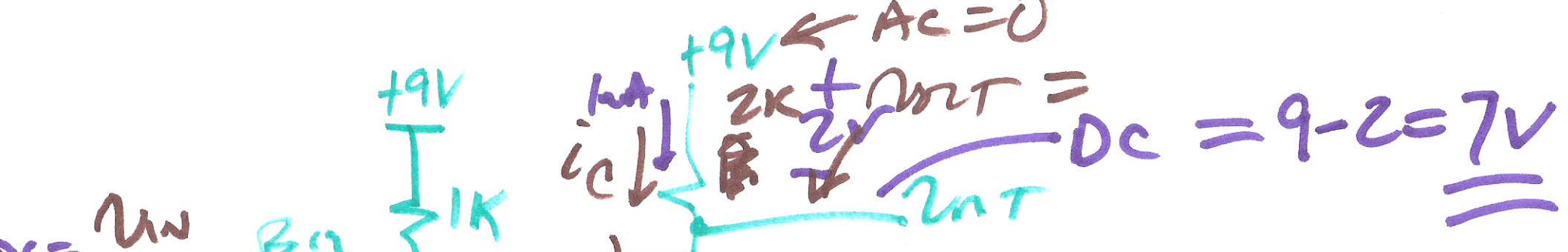
$$i_c = 25 mV \cdot 4 \frac{\mu A}{V} = 100 \mu A$$



$$g_m = 40 \text{ mA/V}$$

$$g_m = \frac{I_c}{V_T} = \frac{1 \text{ mA}}{1.25 \text{ mV}}$$

$$I_E = \frac{3.8}{3.8 \text{ k}} = 1 \text{ mA}$$

$$i_c = g_m v_{in} = g_m v_{be}$$

$$i_c \downarrow \left. \begin{array}{l} 2 \text{ k} \\ 2 \text{ mV} \end{array} \right\} = -i_c \cdot 2 \text{ k}$$

$$= -g_m v_{in} \cdot 2 \text{ k}$$

$$\frac{v_{out}}{v_{in}} = -g_m 2 \text{ k}$$

9)