

Lecture 22



April 15, 2015

EE 320

Engineering
Electronics I

AC DC

$$V_{BE} = v_{be} + V_{BE}$$

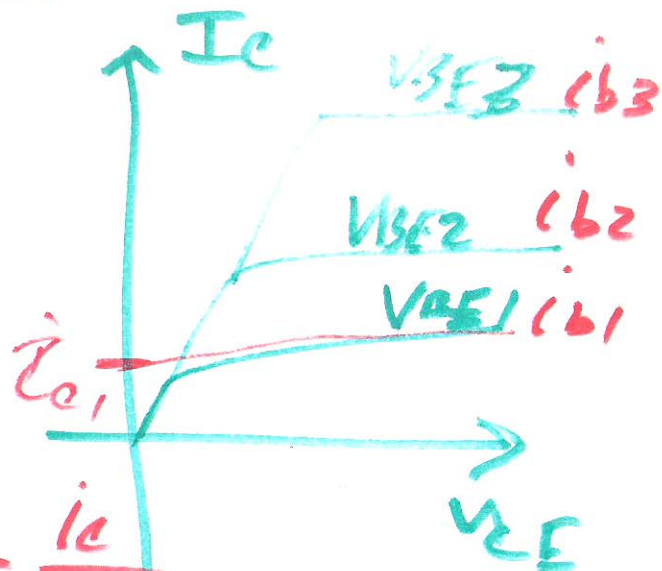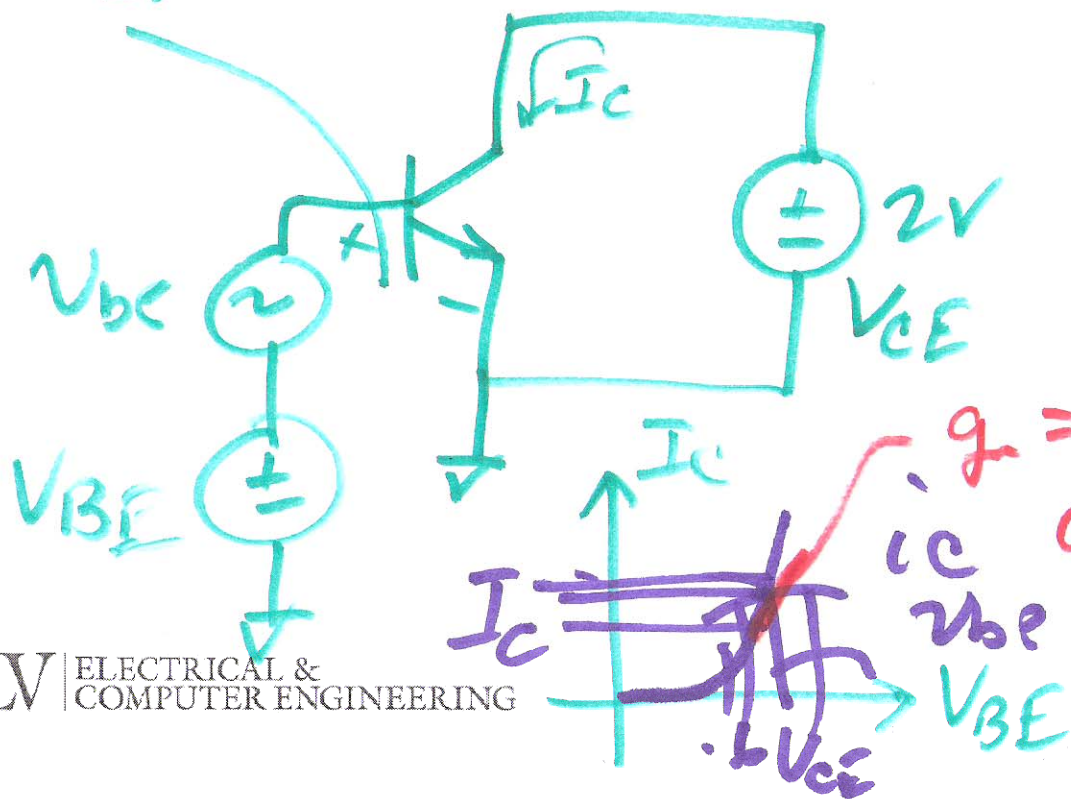

1)

$$i_c = I_c + i_c = I_s e^{\frac{V_{BE}}{n \cdot V_T}} = I_s e^{\frac{V_{BE}}{n V_T}}$$


$$g_m \equiv \frac{\delta i_c}{V_{BE}} \Bigg|_{\substack{I_c = \text{CONST} \\ V_{BE} = \text{CONST}}} = I_s e^{\frac{V_{BE}}{n V_T}} \cdot \frac{\delta \left(\frac{V_{BE}}{n V_T} \right)}{\delta V_{BE}}$$

$$I_c \gg i_c$$

$$g_m \approx \frac{I_c}{V_T \cdot n}$$

$$= \frac{I_s e^{\frac{V_{BE}}{n V_T}}}{n V_T}$$

$$g_m = \frac{I_c + i_c}{n V_T}$$

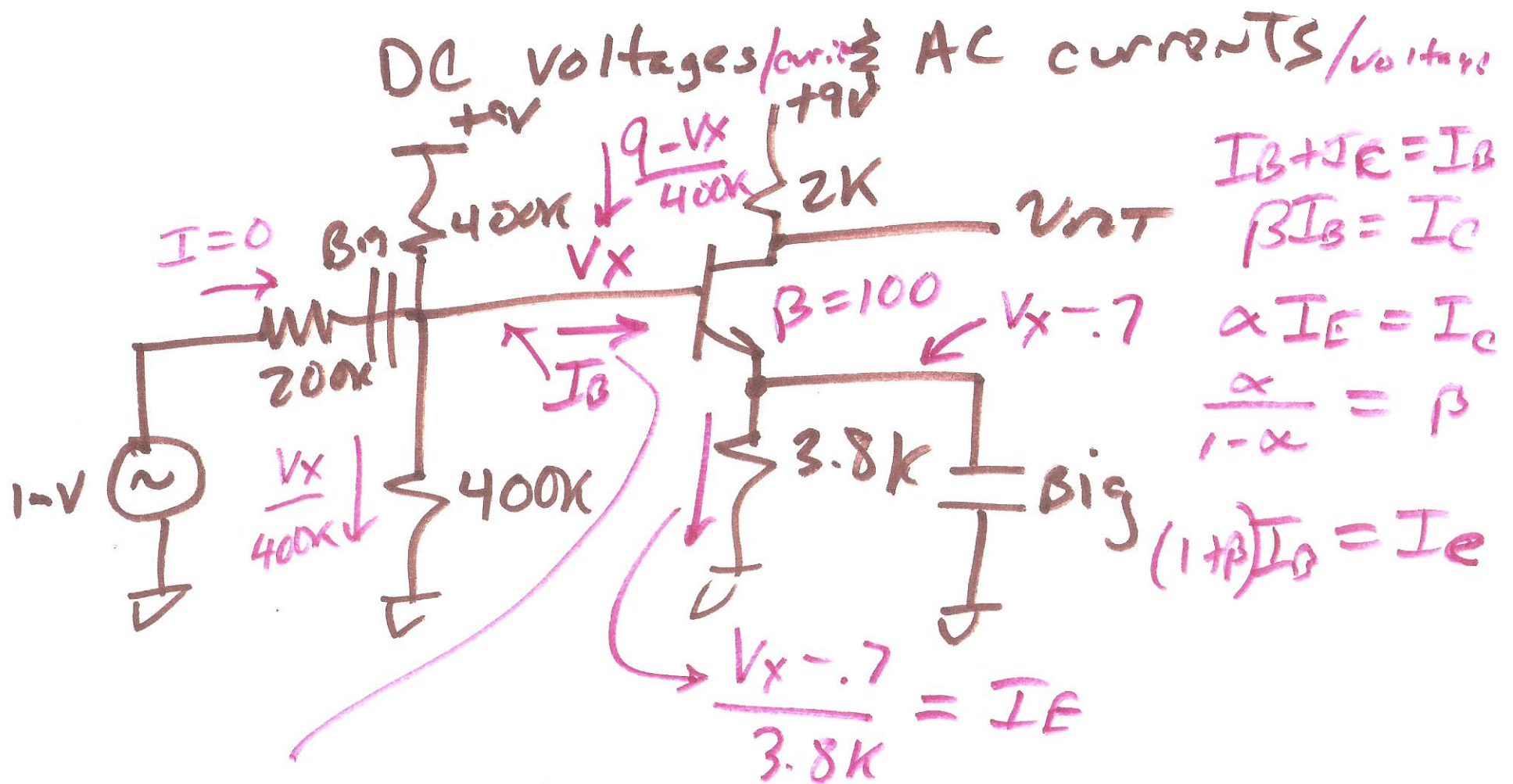

$$I_B = \frac{V_x - 0.7}{3.8k(1 + \beta)}$$

$$= \frac{V_x - 0.7}{3.8k \cdot 101}$$


3)

$$\frac{9 - V_x}{400k} = \frac{V_x}{400k} + \frac{V_x - .7}{3.8k \cdot 101}$$

$$9 - V_x = V_x + (V_x - .7) 1.042$$

$$9.728 = 3.042 V_x \Rightarrow V_x = \frac{4.184}{3.042} \text{V}$$

3.2V

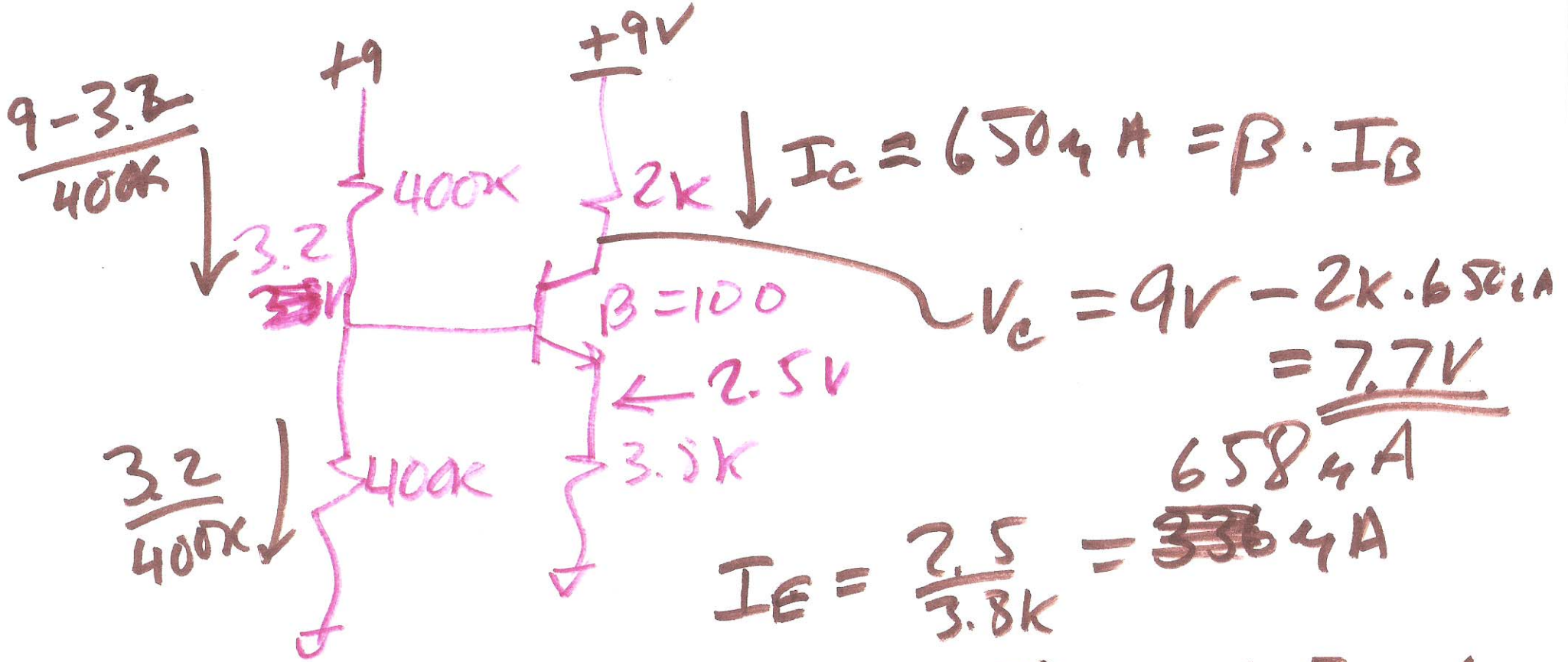

$$I_E = \frac{2.5}{3.8k} = 658 \mu A$$


$$I_B = \frac{658}{104} = 6.5 \mu A$$

$$\beta + 1$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = .99$$

AC

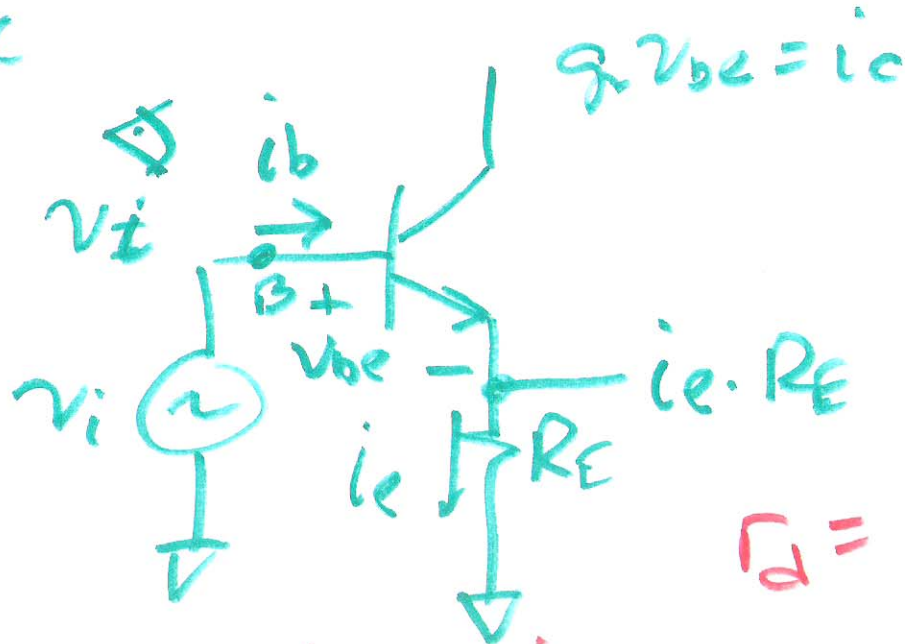

$$v_i = v_{be} + i_e \cdot R_E$$


$$= \frac{i_c}{\beta} + i_c \cdot R_E$$

$$r_d = \frac{N V_T}{I_{DQ}} = \frac{\beta \cdot i_b}{\beta - 1} + (\beta + 1) i_b R_E$$

$$i_c = \beta i_b$$

$$i_e = (\beta + 1) i_b$$
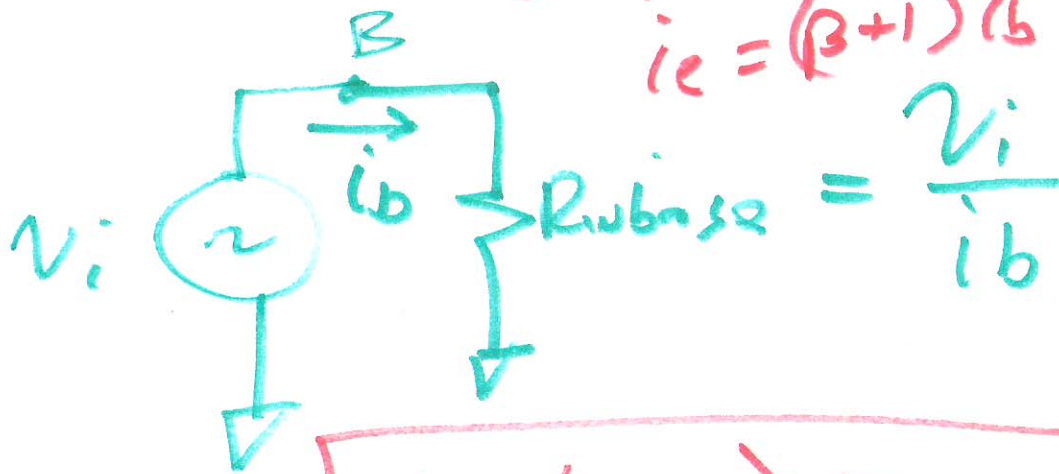
$$g_m = \frac{I_c}{N V_T} \cdot \beta = \frac{I_B}{N V_T}$$




$$\frac{1}{r_{be}} = \frac{1}{r_{\pi}} = \frac{I_B}{N V_T}$$

$$\frac{v_i}{i_b} = (\beta + 1) R_E + r_{be}$$

$$r_e = \frac{N V_T}{I_E}$$


6)

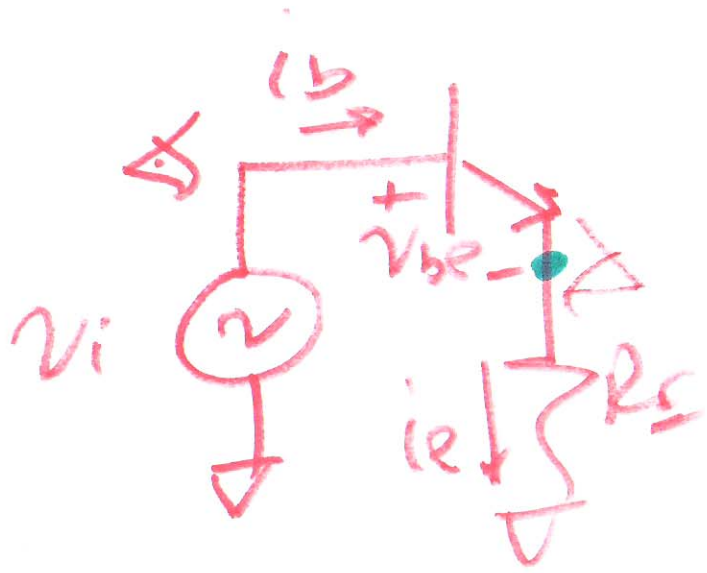

$$r_d = \frac{N V_T}{I_D} \quad \text{+} \quad i_b(\beta+1)$$

$$v_i = i_b \cdot r_e + i_e \cdot R_E$$
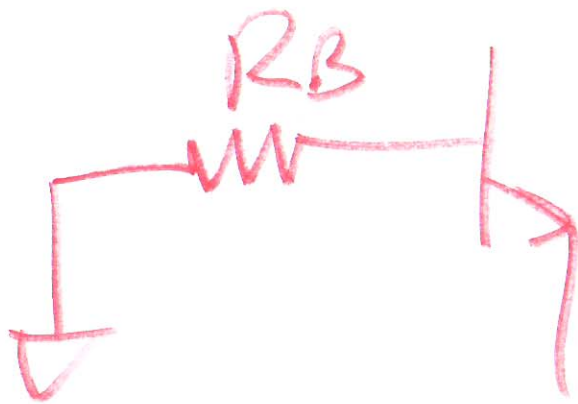
$$\frac{v_i}{i_b} = r_{be} + (\beta+1)R_E$$



$$r_{in(b)} = r_e + \frac{R_B}{\beta+1}$$

$\frac{N V_T}{I_E} \rightarrow \frac{N V_T}{I_B}$

