

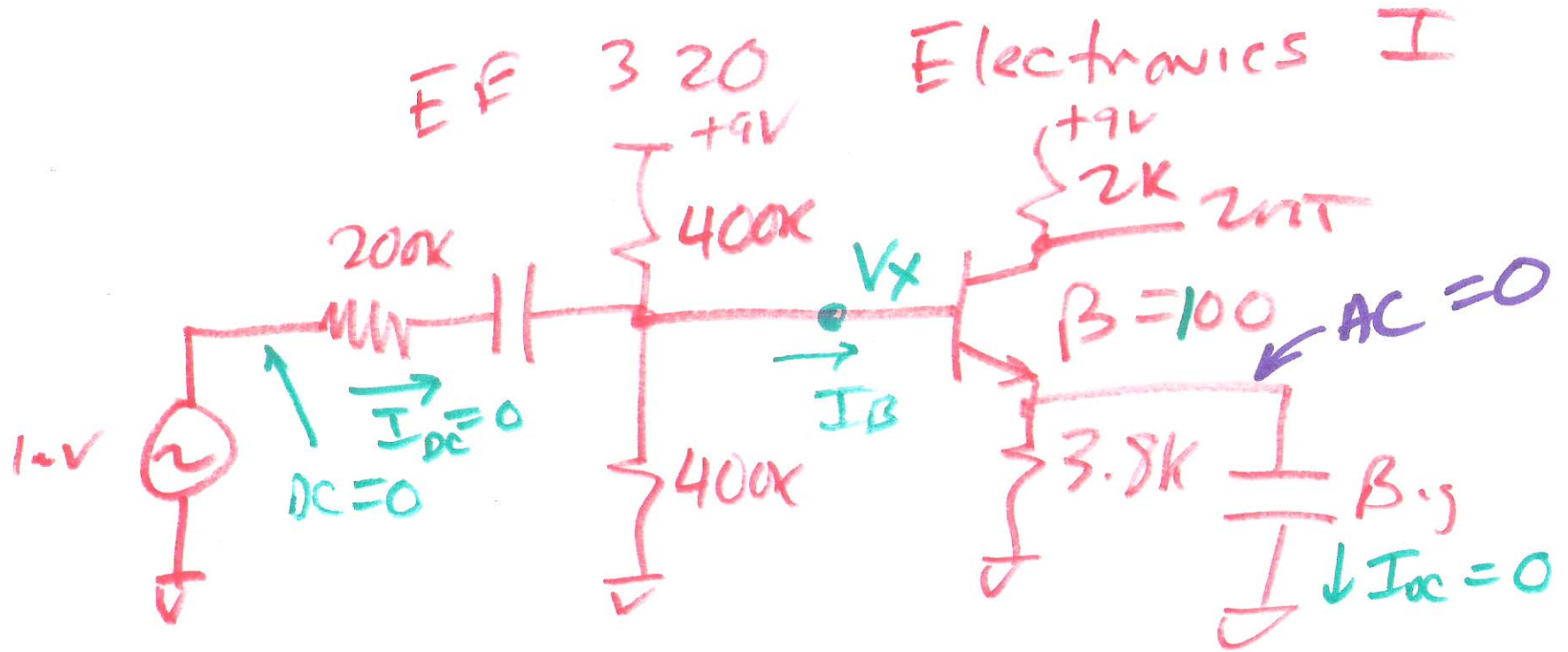


# Lecture 23


April 20, 2015

EE 320 Electronics I

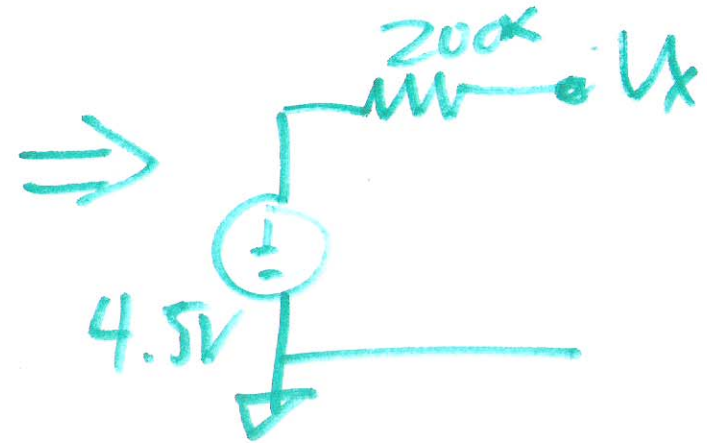

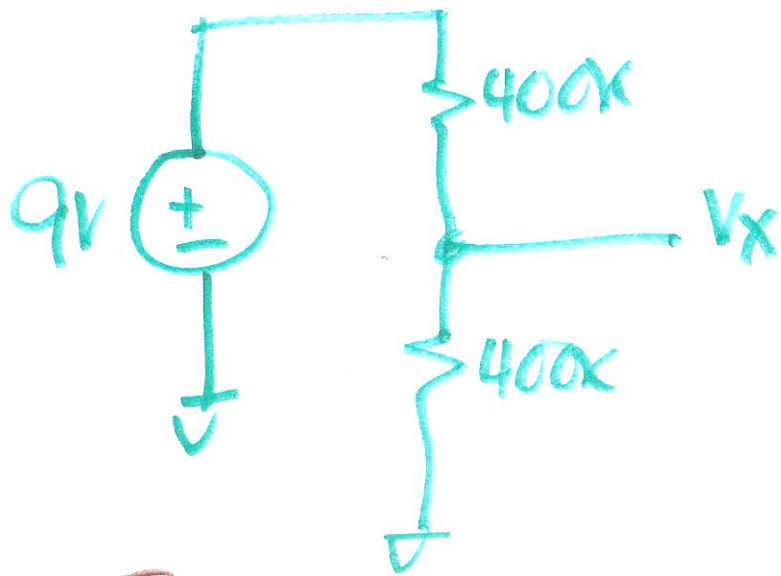

6.54

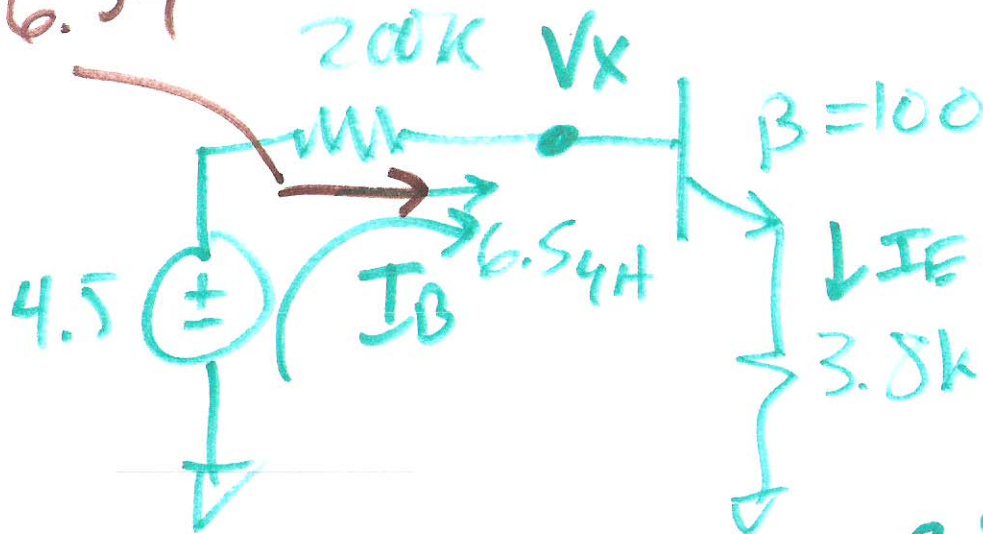

$$4.5 - I_B \cdot 200k - 0.7 - (\beta + 1)I_B \cdot 3.8k = 0$$

$$I_E = (\beta + 1)I_B$$

$$I_E = 101 \cdot 6.54 = \underline{\underline{657.94A}}$$



$$3.8 = I_B (200k + 101 \cdot 3.8k)$$

$$I_B = \frac{3.8}{583.2k} = 6.54A$$

$$V_x = 4.5 - 6.54 \cdot 200k =$$


$$V_x = 3.2V$$

2)

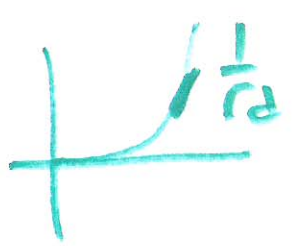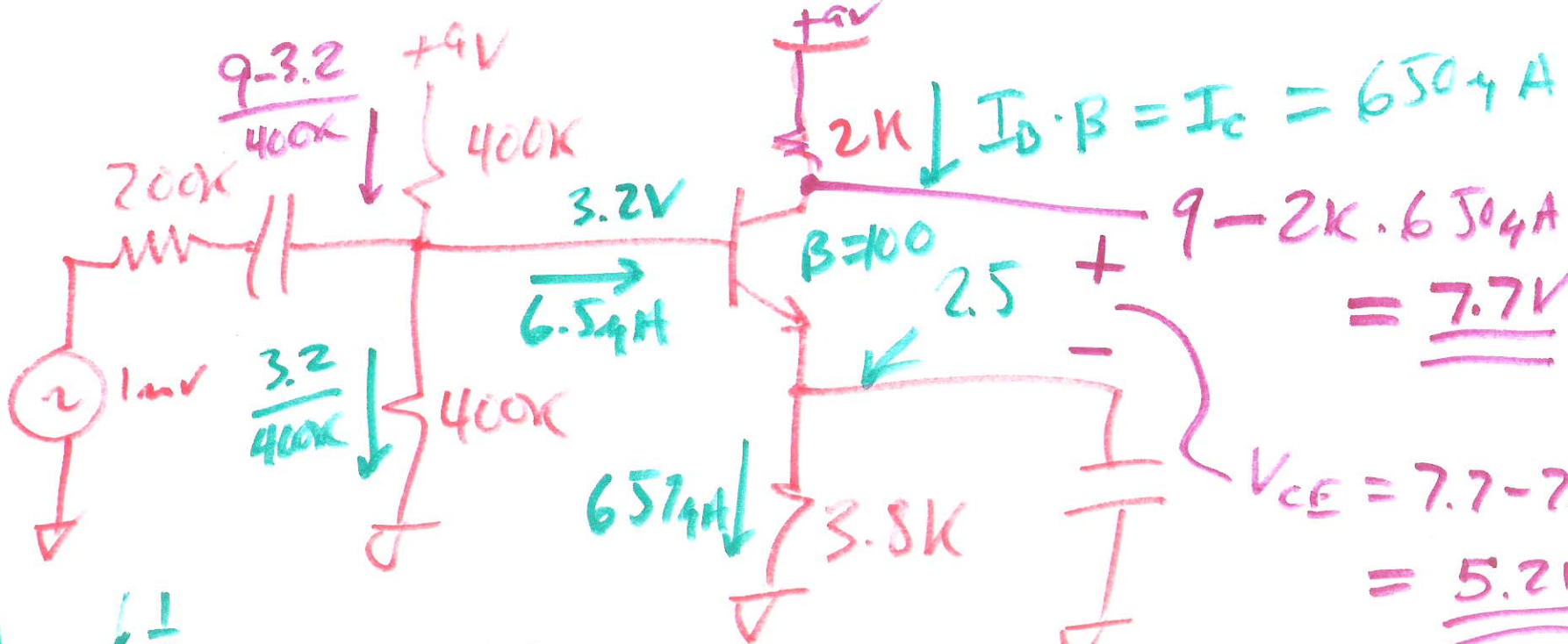


$$r_d = \frac{NkT}{I_D}$$
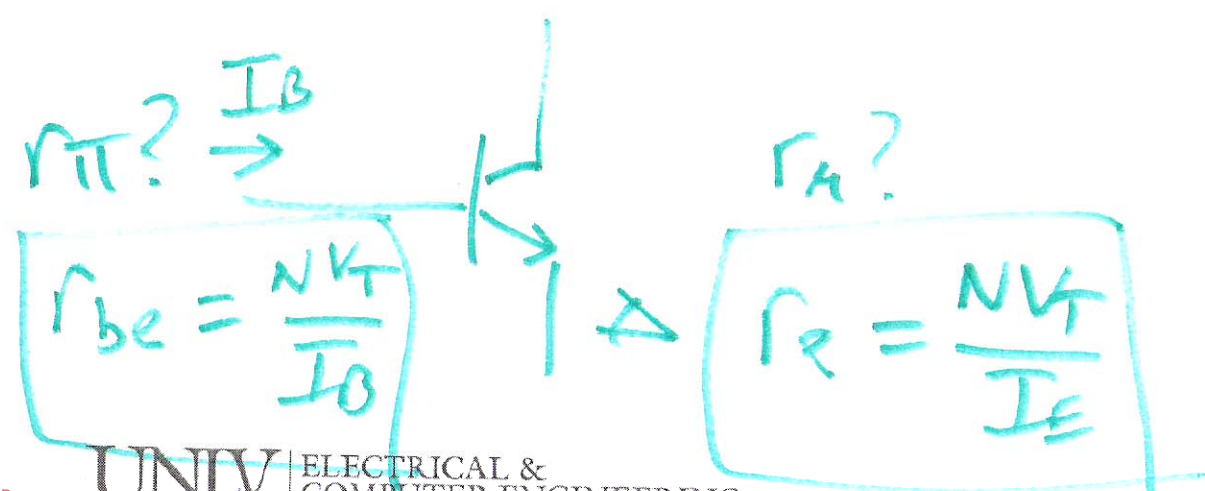
$$g_m = \frac{I_C}{NkT} = \frac{6.504}{25mV} = 26 \frac{mA}{V}$$



3)

AC

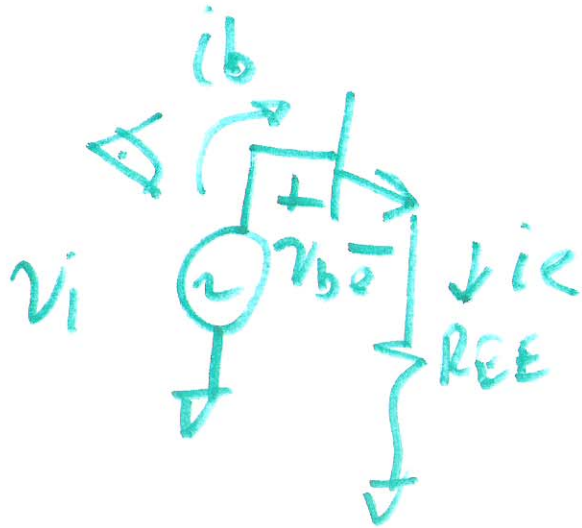

$$v_{be} = i_b \cdot r_{be} = i_b \cdot \frac{NVT}{I_B}$$

$$v_{be} = i_e \cdot r_e = i_e \cdot \frac{NVT}{I_E}$$


$$i_b \cdot (\beta + 1) \quad \downarrow \quad I_B(\beta + 1)$$

$R_{in, base}$

$$= \frac{v_i}{i_b} \Rightarrow v_i = v_{be} + i_e \cdot R_{EE}$$

$$= i_b \cdot r_{be} + i_b(\beta + 1) \cdot R_{EE}$$
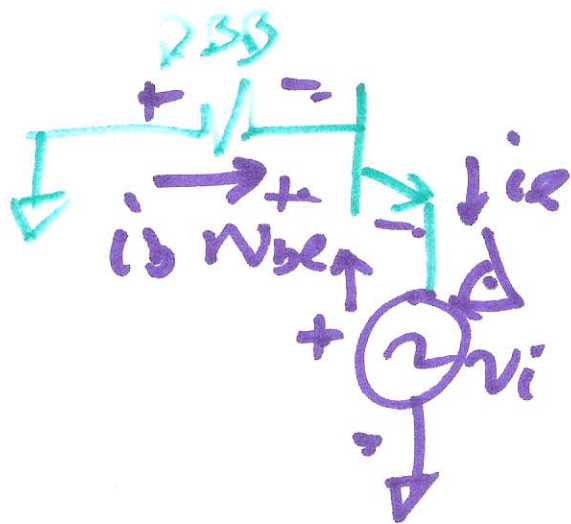
$$R_{in, base} = \frac{v_i}{i_b} = r_{be} + (\beta + 1) R_{EE}$$



$v_i$

$$R_{\text{intemitter}} = \frac{v_i}{-i_e}$$




$$v_i + v_{be} + i_b \cdot R_{BB} = 0$$

$$v_i = -r_e i_e - i_b R_{BB}, \quad i_b = \frac{i_e}{\beta + 1}$$


$$= -i_e \left( r_e + \frac{R_{BB}}{\beta + 1} \right)$$

$$R_{\text{intemitter}} = r_e + \frac{R_{BB}}{\beta + 1}$$

5)

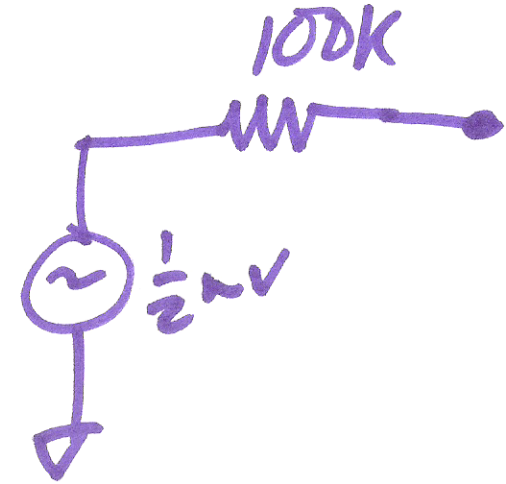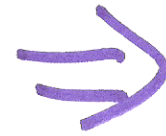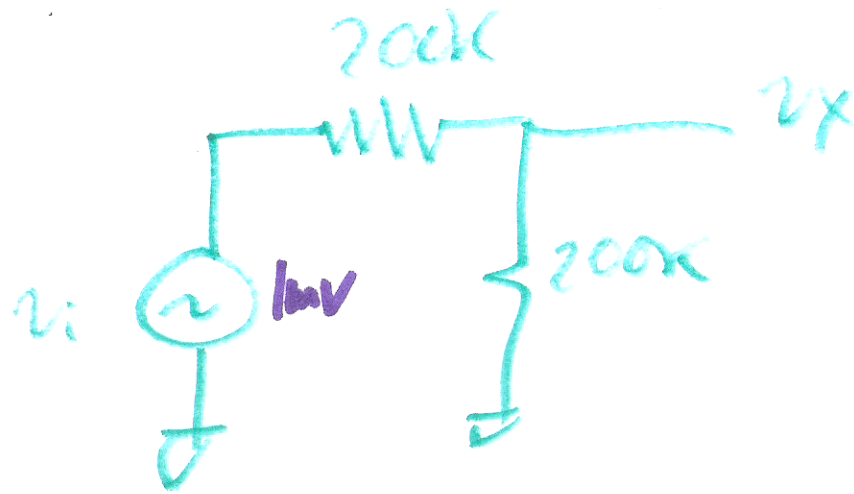

AC - EKT

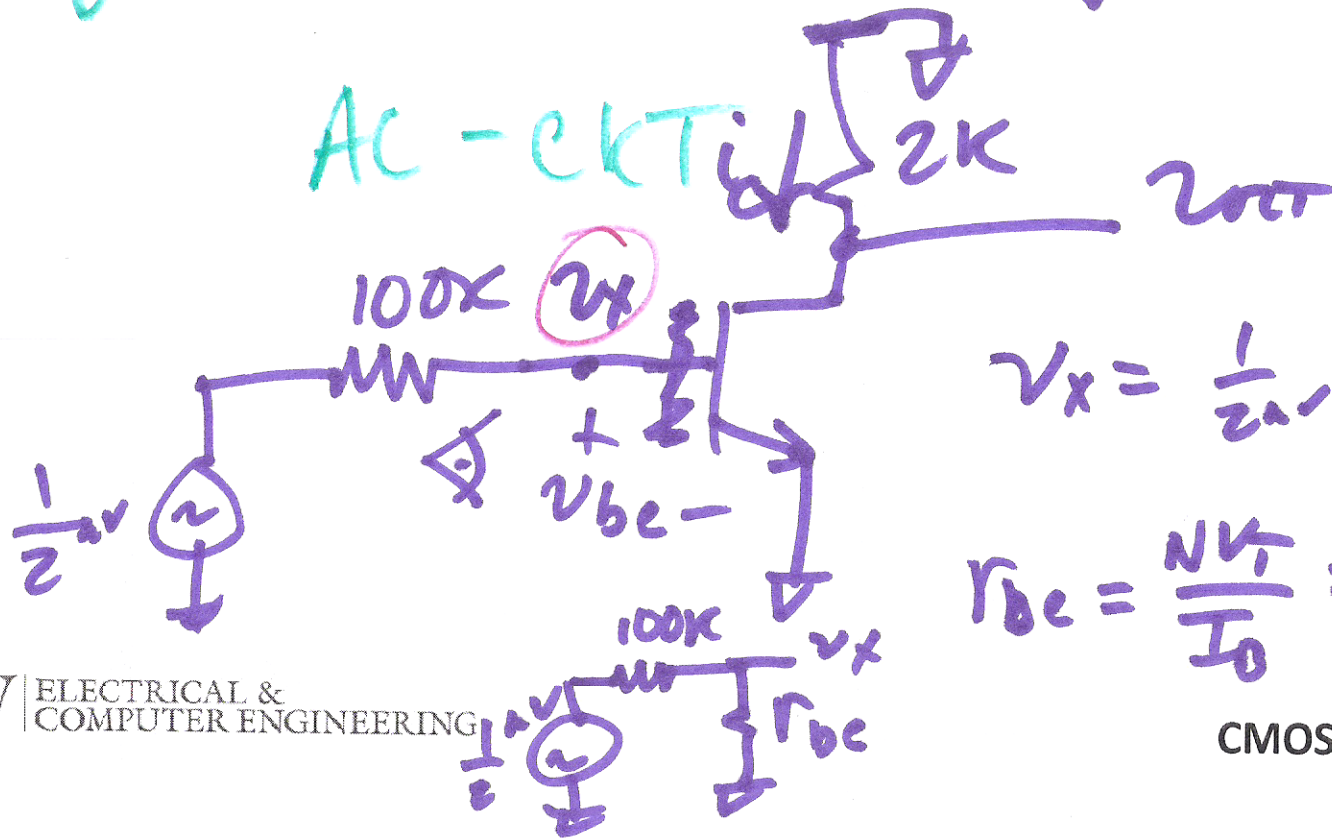




$$v_x = \frac{1}{2} \text{mV} \cdot \frac{r_{be}}{r_{be} + 100k}$$

$$r_{be} = \frac{NV_T}{I_0} = 3.846k\Omega$$

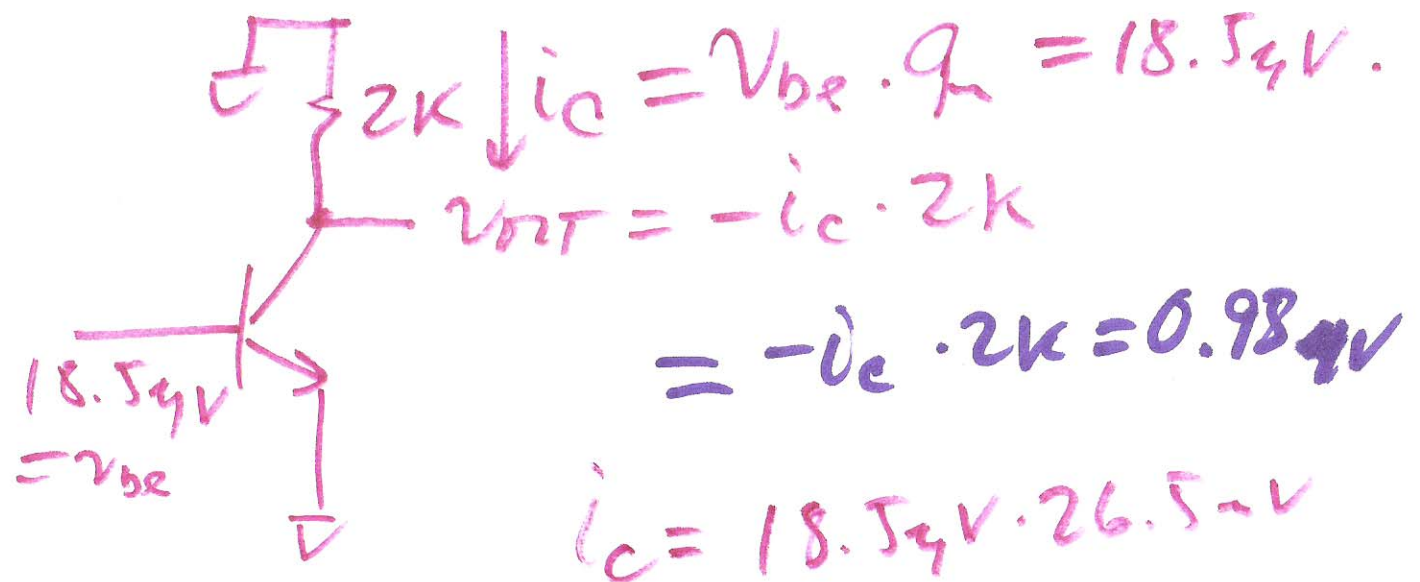6)

$$V_x = \frac{3.84}{103.84} \cdot \frac{1}{2} = \underline{\underline{18.54 \text{ V}}}$$



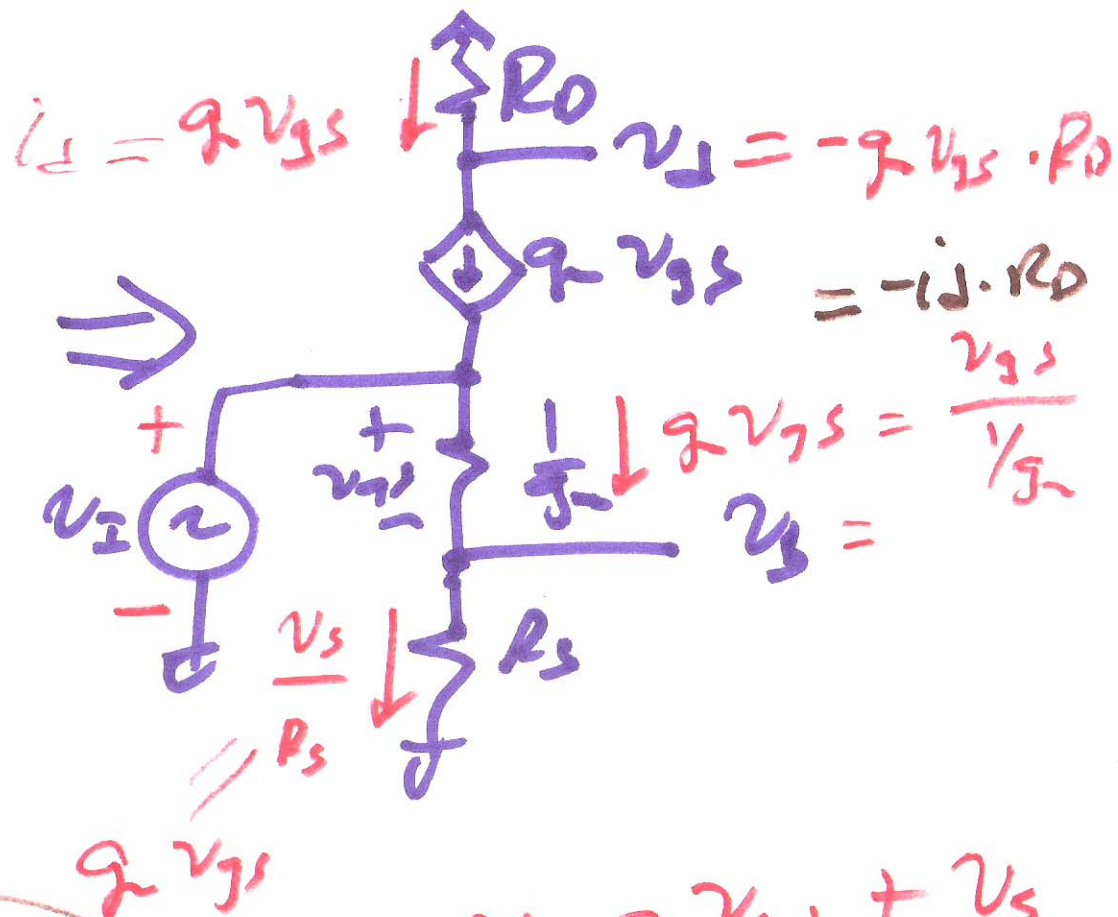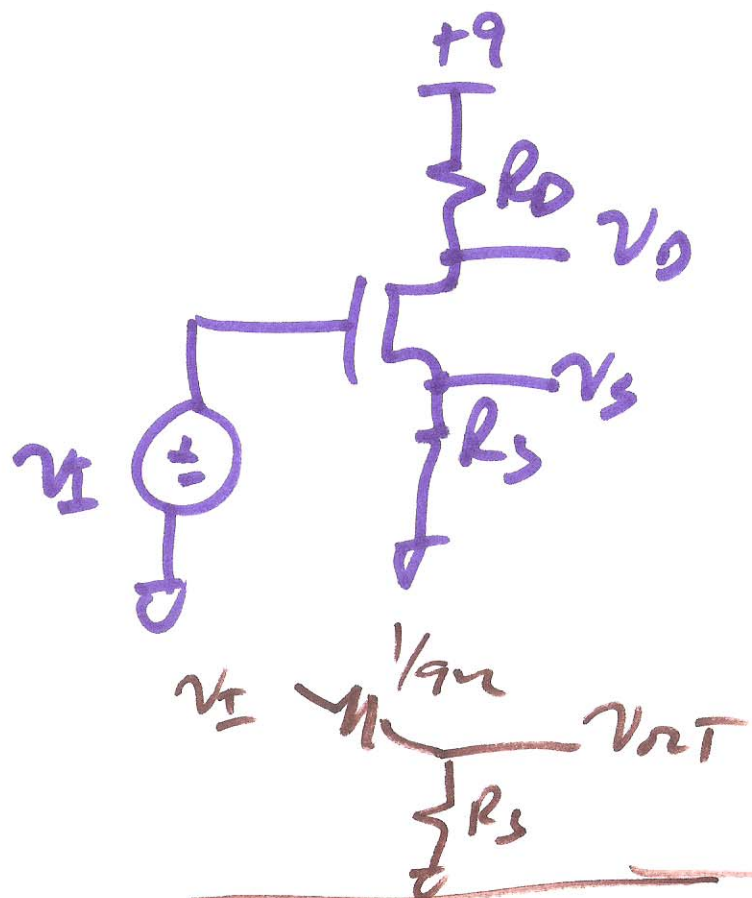

$$\frac{v_S}{v_I} = \frac{R_S}{\frac{1}{g_m} + R_S}$$

$$\frac{v_O}{v_I} = -\frac{R_D \cdot g_m}{\left(\frac{1}{g_m} + R_S\right)}$$

$$v_I = v_{GS} + v_S$$


$$= \frac{i_D}{g_m} + R_S \cdot i_D$$

$$v_S = i_D \cdot R_S$$

8)



7.31

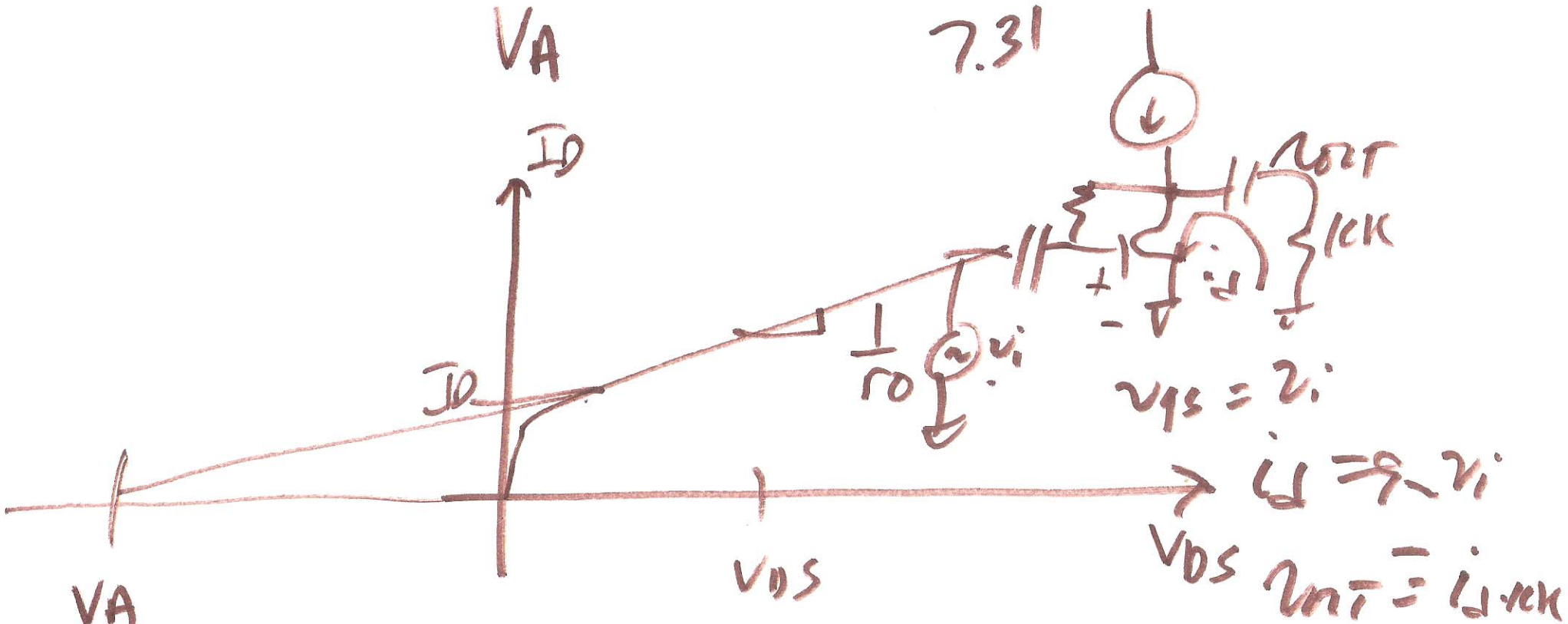

$V_A \gg V_{DS}$

$$\left( \frac{V_A}{I_D} \right)^{-1} = \frac{1}{r_O}$$


$$= \frac{1}{r_O}$$

$$r_O = \frac{V_A}{I_D}$$

$$\lambda = \frac{1}{V_A}$$

$$\frac{v_{out}}{v_i}$$

9)

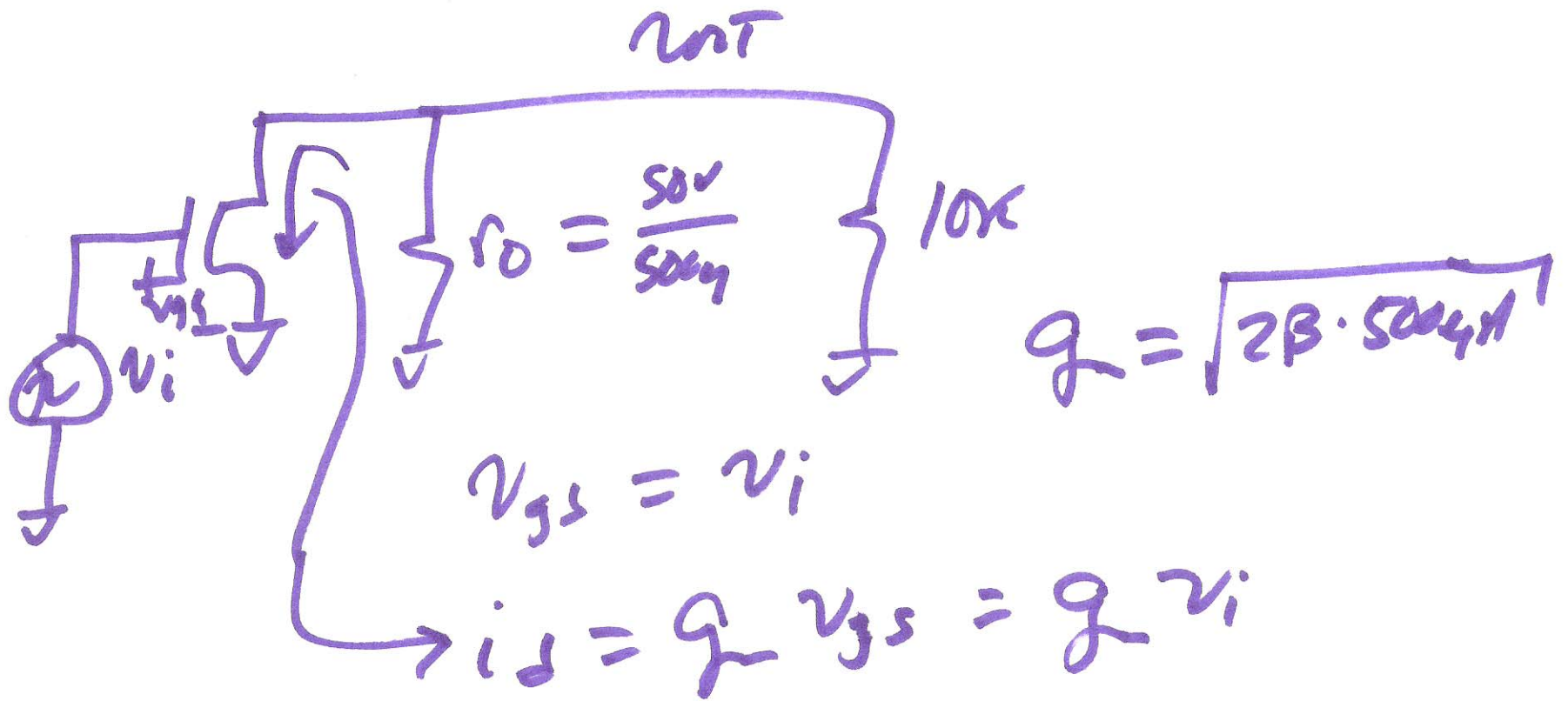

$$v_{DT} = -i_D \cdot (r_D \parallel 100k)$$

$$= -g_m v_i (r_D \parallel 100k)$$

$$\frac{v_{DT}}{v_i} = -g_m (r_D \parallel 100k)$$

10)