


Lecture 25

April 27, 2015

EE 320 Spring 2015



$$\frac{0.3}{2k} = 150\mu A$$

$$= \frac{5 - 4.7}{2k}$$

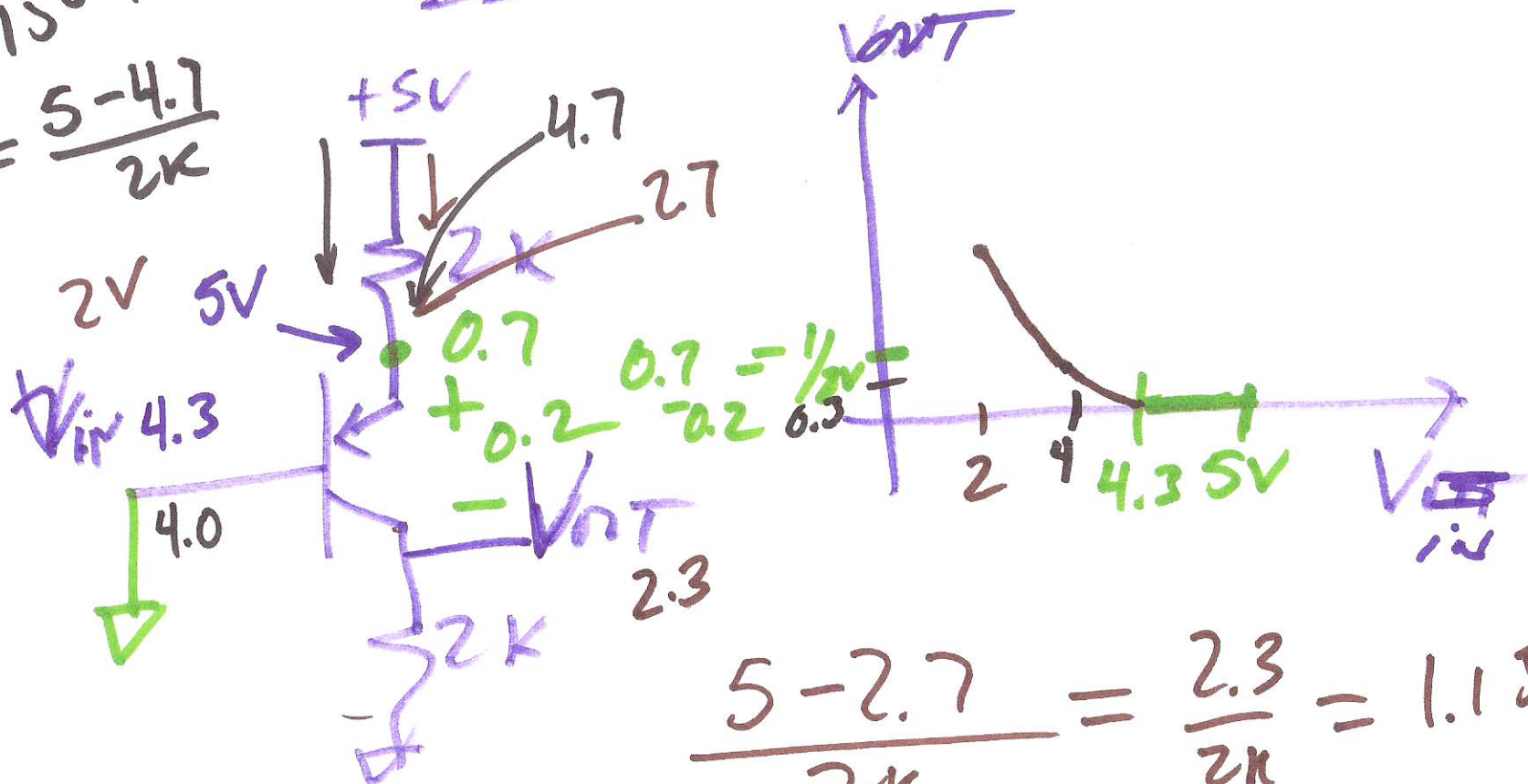



$$\frac{5 - 2.7}{2k} = \frac{2.3}{2k} = 1.15\mu A$$

1)

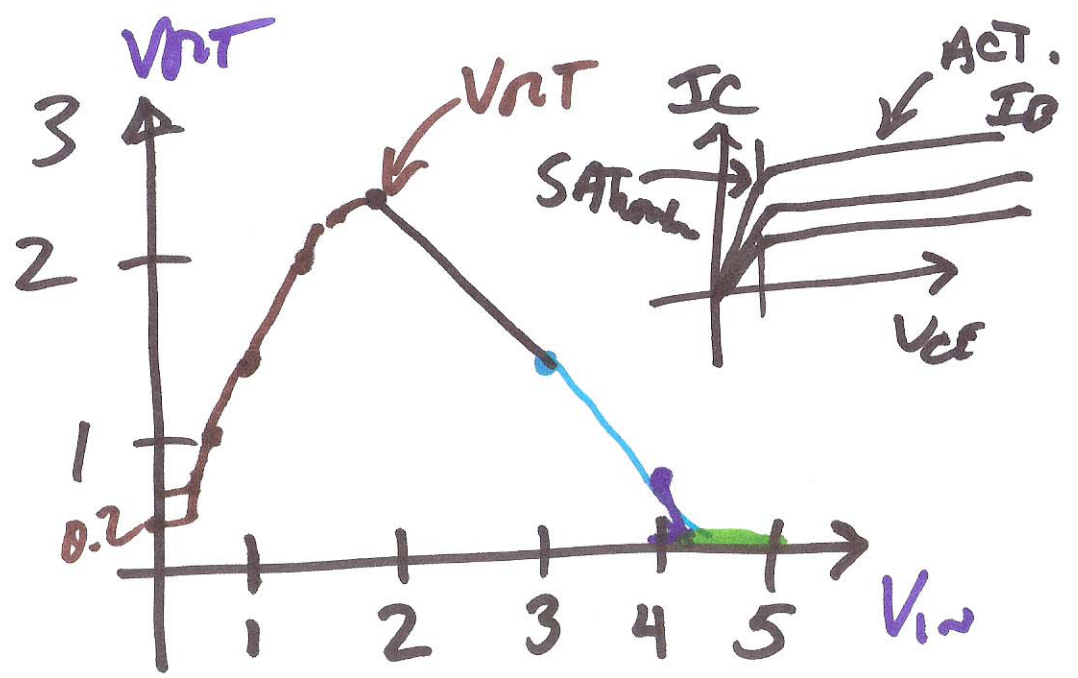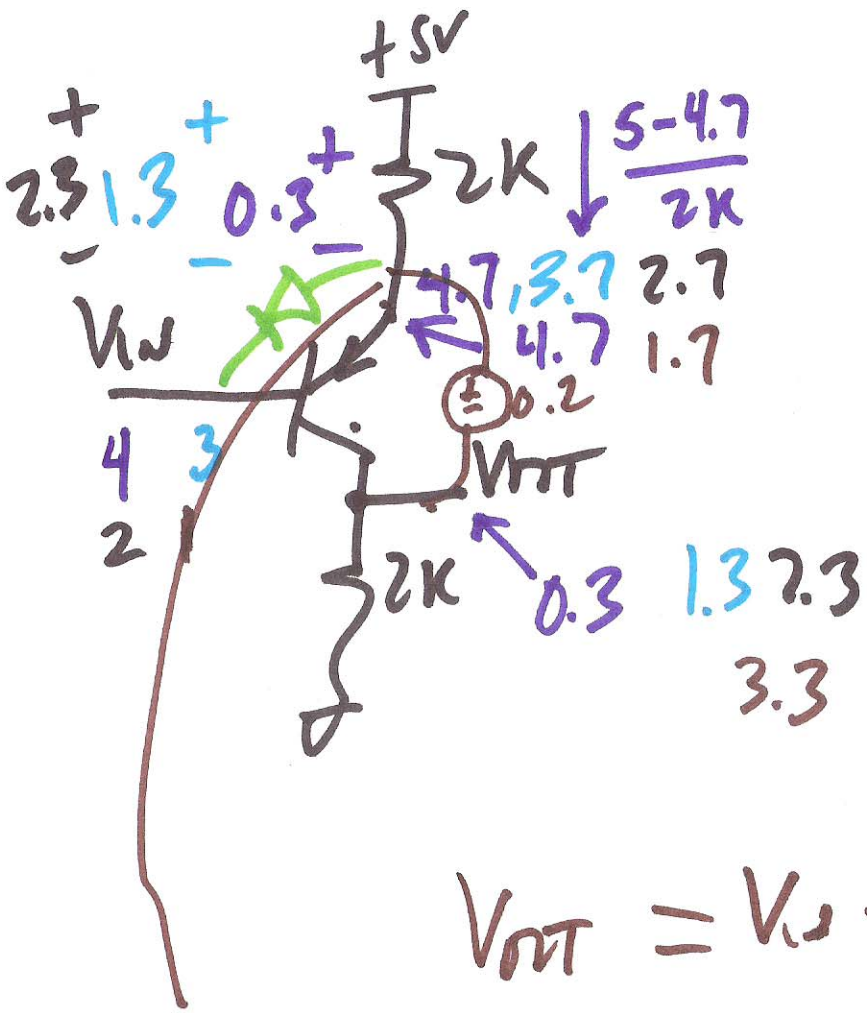


$$V_{OUT} = V_{in} + 0.7 - 0.2 = V_{in} + 0.5$$

$V_{in} + 0.7$

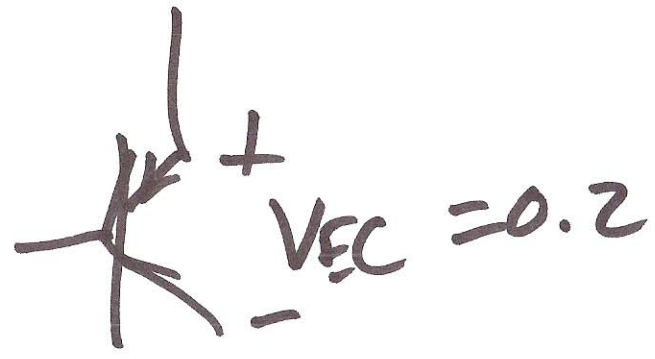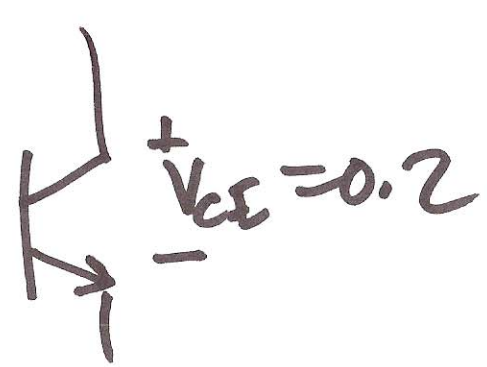

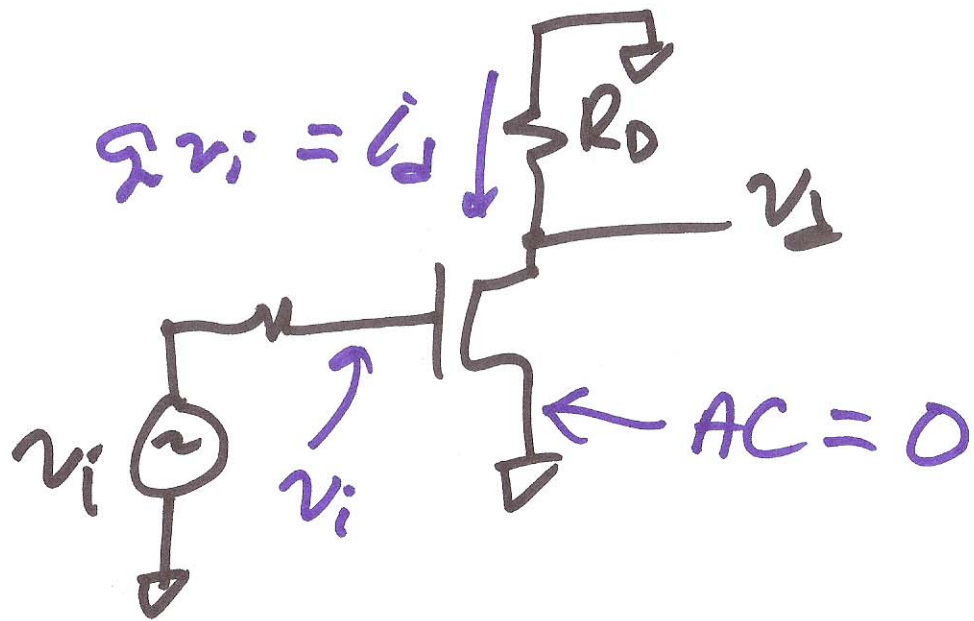2)

$$g_m = \sqrt{2k_p \frac{W}{L} I_D} = k_p \frac{W}{L} (V_{GS} - V_{TH})$$




$$v_{GS} = v_i$$

$$i_D = g_m v_{GS} = g_m v_i$$

$$v_o = -g_m v_i \cdot R_D$$

$$\frac{v_o}{v_i} = -g_m R_D$$

3)

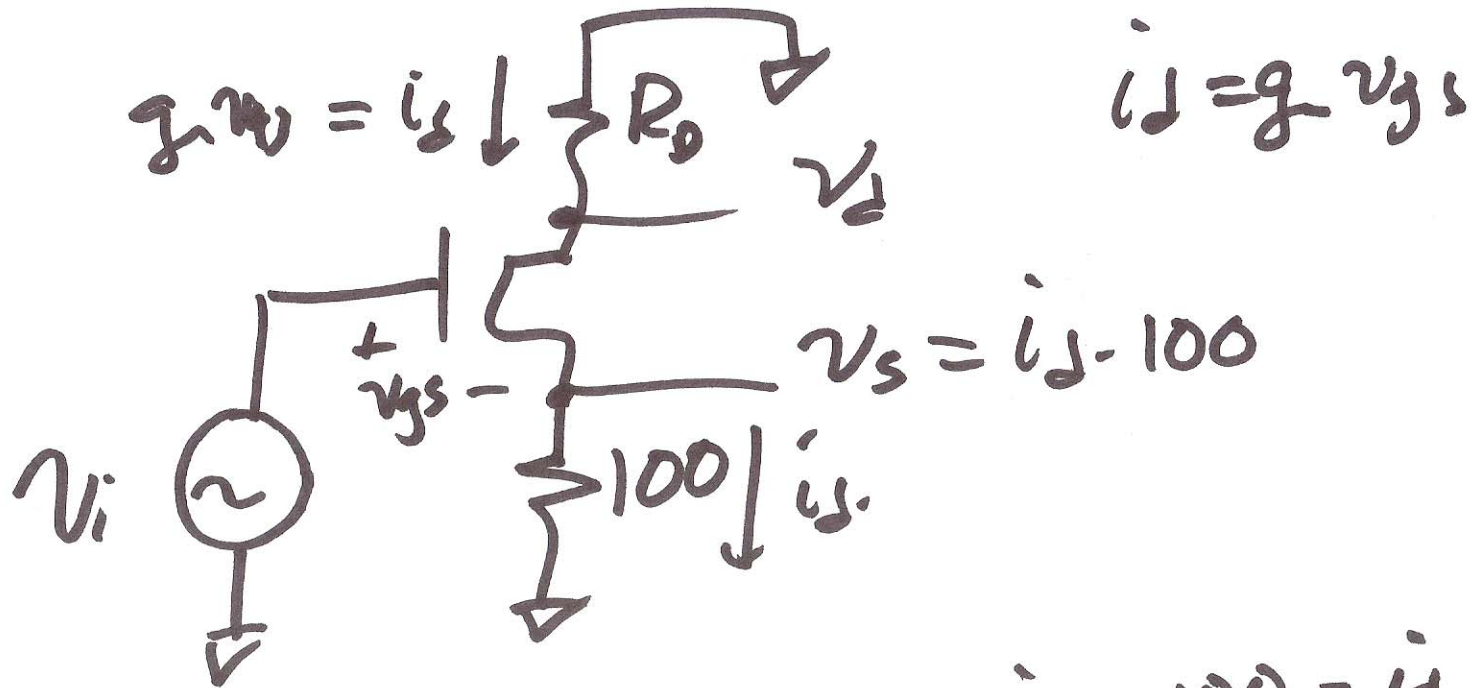


$$\frac{v_d}{v_i} = \frac{-R_D}{\frac{1}{g_m} + 100}$$

$$v_i = v_{gs} + i_d \cdot 100 = \frac{i_d}{g_m} + i_d \cdot 100$$

$$v_{gs} = v_i - i_d \cdot 100$$

$$\begin{aligned}
 v_d &= -i_d \cdot R_D = -g_m v_{gs} \cdot R_D \\
 &= -g_m (v_i - i_d \cdot 100)
 \end{aligned}$$

4)

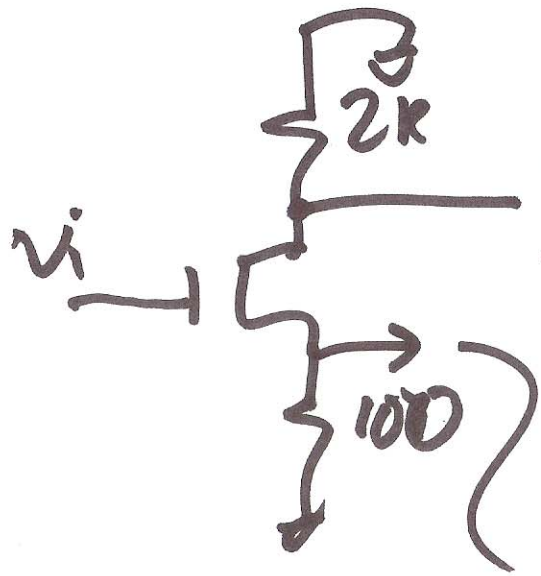

$$g_m = \sqrt{2 \cdot 100\mu \cdot \frac{100}{1} \cdot 1\text{mA}} = \sqrt{2 \cdot 10k \cdot 10^{-9}}$$

$$= \sqrt{20 \cdot 10^{-6}}$$

$$= 4.4 \frac{\text{mA}}{\text{V}}$$

$$\frac{v_d}{v_i} = \frac{2k}{2k + 100} \approx 6.1$$

$$= \frac{2k}{220} \approx \frac{1}{220}$$

$$\frac{1}{g_m} \approx \frac{1}{220}$$

$$\frac{v_s}{v_i} = \frac{100}{100 + 220} = 0.3$$

$$= \frac{R_s}{R_s + \frac{1}{g_m}}$$