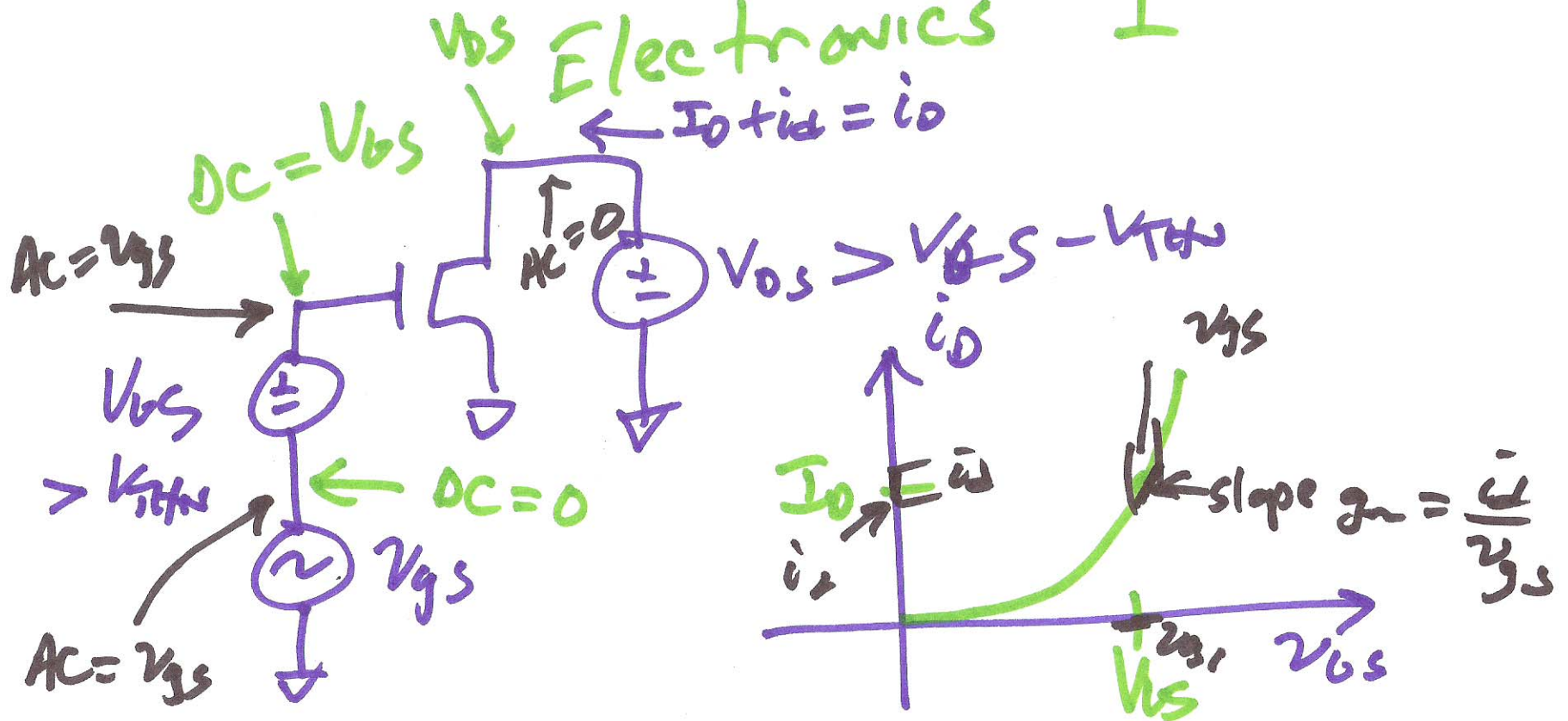


EE 320

April 29, 2015

Lecture 26

Electronics I



1)

$$g_m = \frac{\delta \frac{I_D + i_d}{i_D}}{\delta V_{GS}} \Bigg|_{\substack{V_{DS} = \text{const} \\ I_D = \text{const}}} = \frac{\delta \frac{\beta}{2} (V_{GS} - V_{TH})^2}{\delta V_{GS}}$$



$$\frac{\delta \frac{Kx^2}{2}}{\delta x} = Kx \cdot \frac{\delta x}{\delta x}$$

$$g_m = \beta (V_{GS} - V_{TH})$$

Small-signal Approx

$$V_{GS} \gg V_{TH}$$
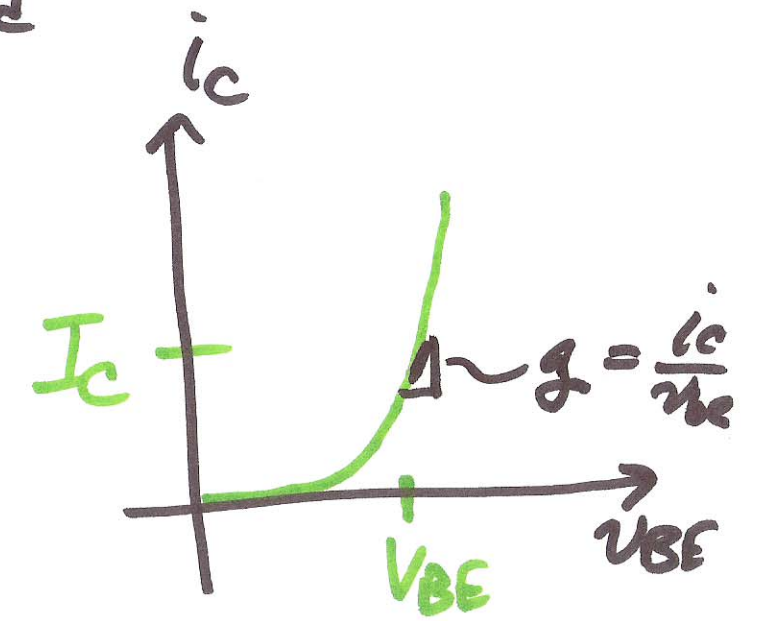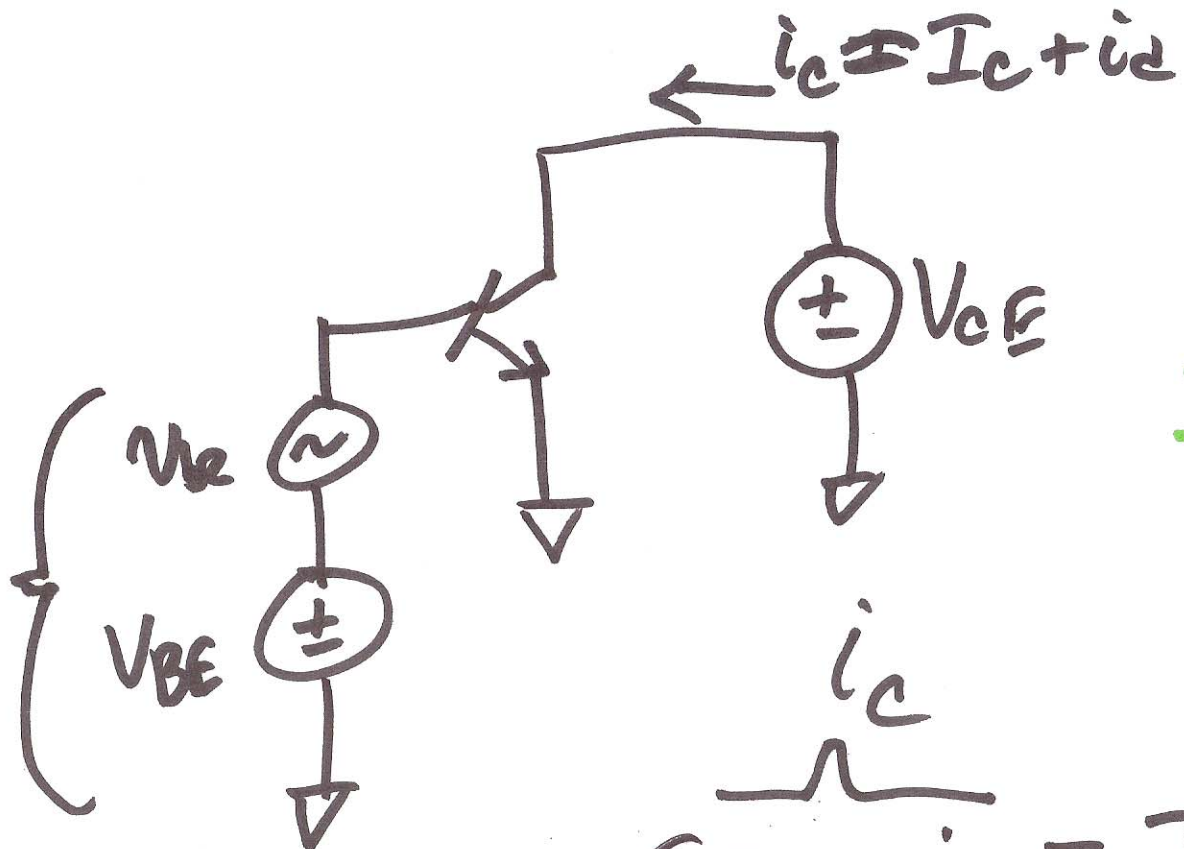
$$\beta = k_p \cdot \frac{W}{L} = \mu_n \cdot C_{ox} \cdot \frac{W}{L} \quad g_m = \beta (V_{GS} - V_{TH})$$



$$g_m = \frac{\delta I_c + i_c}{\delta V_{BE}} = I_S e^{\frac{V_{BE} + v_{be}}{N V_T}} = \frac{1}{N V_T} I_S e^{\frac{V_{BE} + v_{be}}{N V_T}}$$


$$\frac{d}{dx} e^{kx} = k e^{kx}$$

$$\begin{aligned} I_C &= \text{const} \\ V_{BE} &= \text{const} \\ \text{S.S. Approx. } I_C &\gg i_c \end{aligned}$$

$$g_m = \frac{I_C}{N V_T}$$

CMOSedu.com

3)

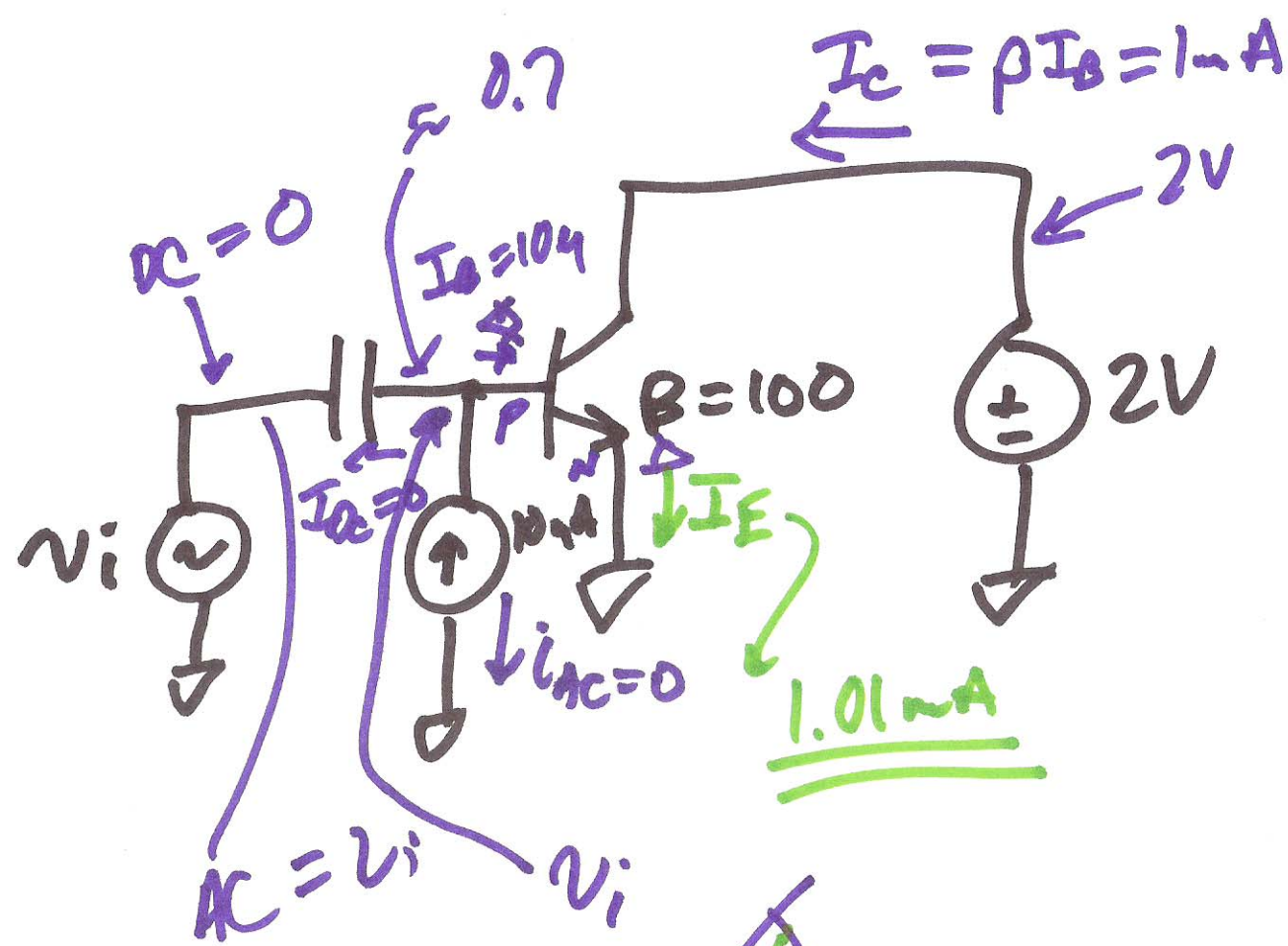


find i_c

$$g_m = \frac{I_C}{V_T} = \frac{40\mu A}{V}$$

$$i_c = g_m v_i$$

$$i_c = 0.04 v_i$$

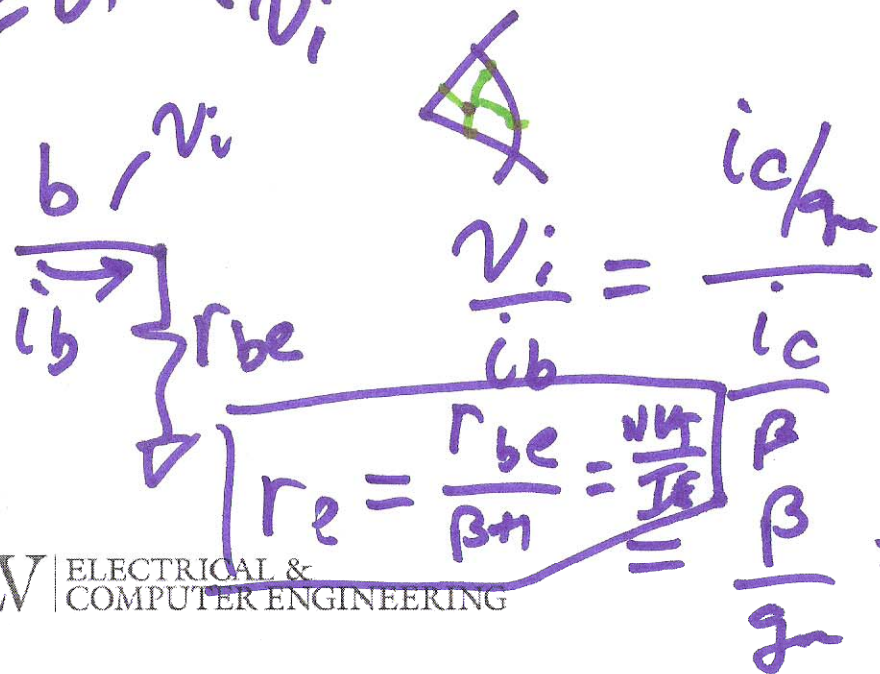

$$r_e = \frac{r_{be}}{\beta + 1} = \frac{V_T}{I_E}$$


$$\frac{v_i}{i_b} = \frac{i_c}{i_b} \cdot \frac{1}{\beta} = \frac{\beta \cdot V_T}{I_C} = \frac{V_T \cdot \beta}{I_C} = r_{be}$$

$$i_b = \frac{i_c}{100} = \frac{i_c}{\beta}$$

$$i_e = i_b + i_c = i_b \cdot (\beta + 1)$$

$$\frac{\beta \cdot V_T}{I_C} = \frac{V_T \cdot \beta}{I_C} = r_{be}$$

4)

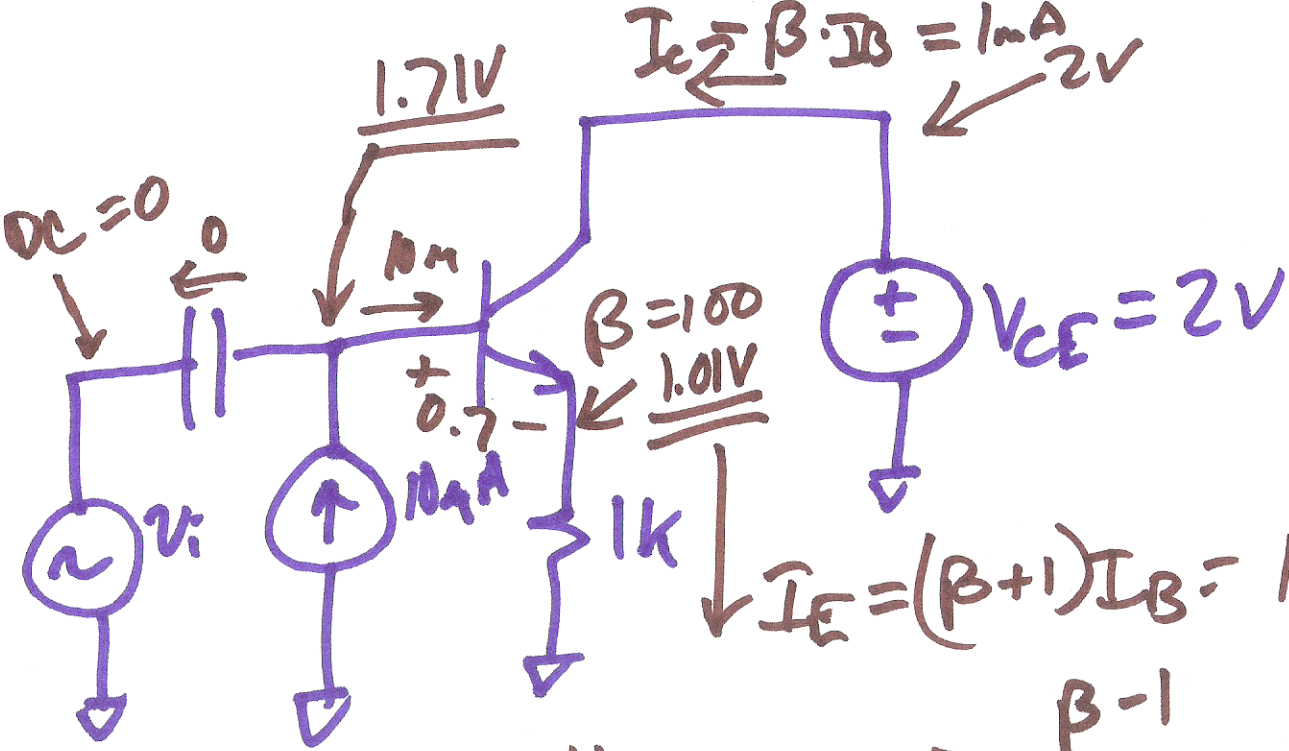


$$i_c = \alpha \cdot i_e$$

$$\beta \cdot i_b = i_c$$

$$(\beta + 1) i_b = i_e$$

$$R_{thbase} = \frac{v_i}{i_b} = \alpha = \frac{\beta - 1}{\beta}$$
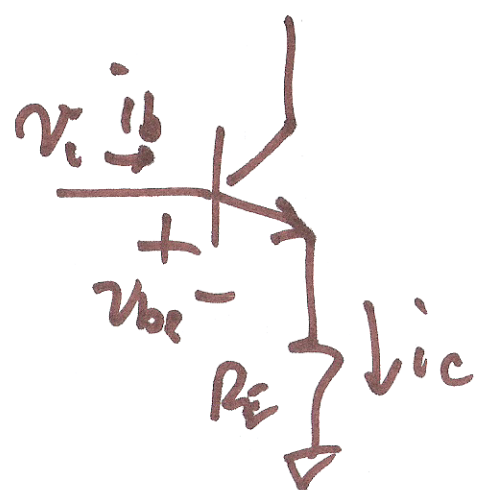
$$v_i = r_{be} \cdot i_b + i_b R_E (\beta + 1)$$



$$v_i = v_{be} + R_E \cdot i_e$$


$$= \frac{i_c}{\alpha} + R_E \cdot i_c \alpha$$

$$v_i = i_c \left(\frac{1}{\alpha} + \alpha R_E \right)$$

5)

$$i_e = \frac{1\text{mV}}{r_e} = \frac{1\text{mV}}{25}$$

$$r_e = \frac{NkT}{I_{Ee}} = 25\Omega$$

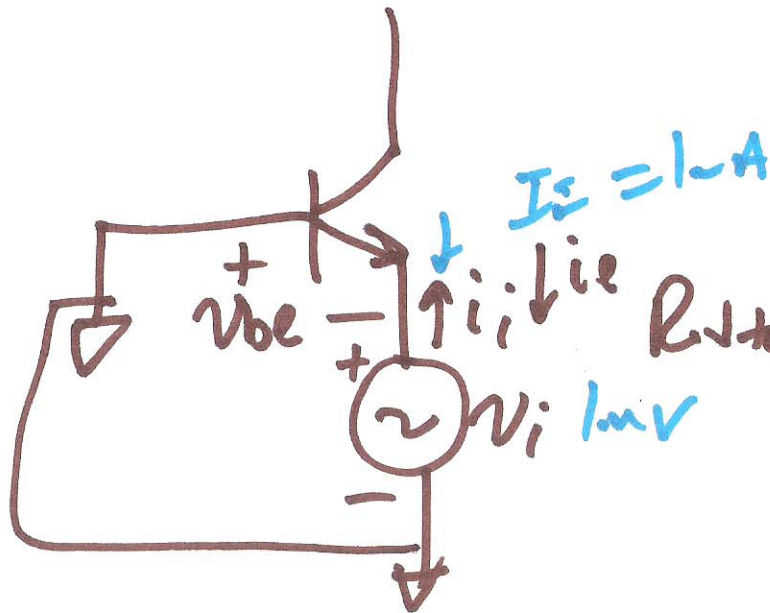

$$R_{\text{input}} = \frac{v_i}{i_i} = \frac{v_{be}}{i_e} \Rightarrow$$

$$v_i = -v_{be}$$


$$i_i = -i_e$$

$$v_i + v_{be} = 0$$

$$R_{\text{input}} = \frac{v_{be}}{i_b \cdot (\beta + 1)} = \frac{r_{be}}{\beta + 1} = r_e$$

$$r_e = \frac{NkT}{I_E} = \frac{NkT}{I_B(\beta + 1)}$$

b)

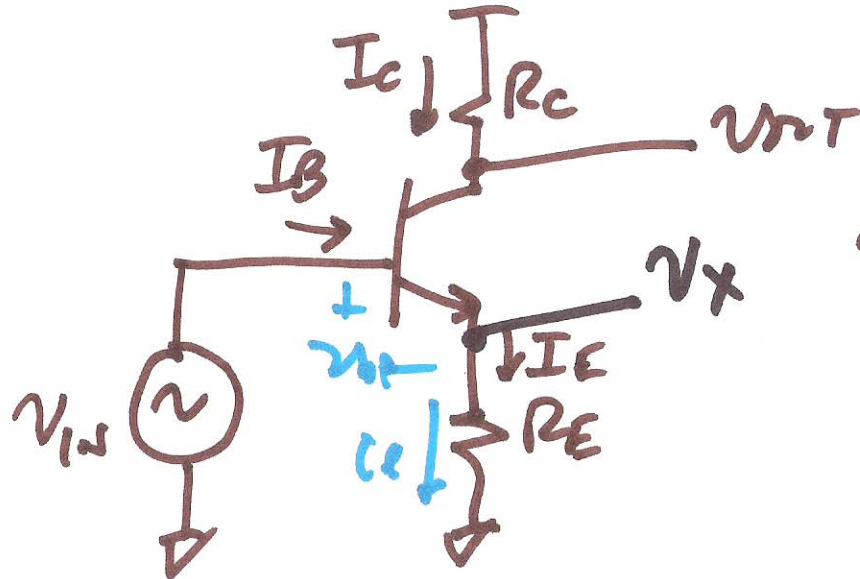

$$\frac{v_{out}}{v_{in}} = ?$$

$$i_c = v_{be} \cdot g$$

$$\frac{v_x}{v_{in}} = \frac{i_e \cdot R_E}{v_{be} + i_e \cdot R_E}$$

$$v_{in} = v_{be} + i_e \cdot R_E$$

$$v_{in} = \frac{i_c}{g} + \frac{i_c}{\alpha} \cdot R_E$$

$$v_{be} = i_b \cdot r_{be}$$

$$= i_e \cdot r_e$$

$$= i_e \cdot \frac{r_e}{\alpha}$$

$$\frac{v_x}{v_{in}} = \frac{R_E}{r_e + R_E}$$


$$v_{out} = -i_c \cdot R_C$$

$$\frac{v_{out}}{v_{in}} = \frac{-R_C}{\frac{1}{g} + \frac{R_E}{\alpha}}$$

$$\frac{I_C}{I_E} = \frac{r_e}{\alpha}$$

$$\frac{I_C}{\alpha} = I_E$$

7)

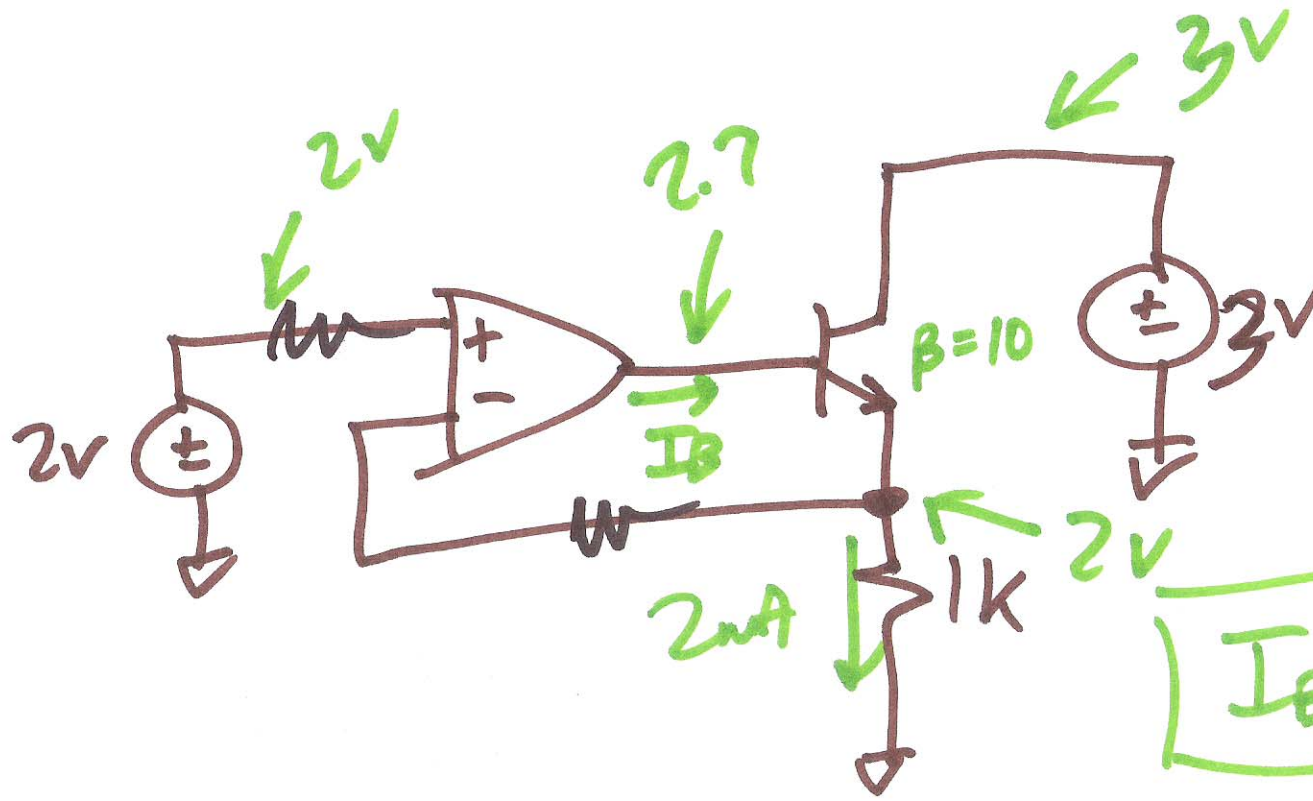

$$I_B \cdot \beta = I_C$$


$$I_B \cdot (\beta + 1) = I_E$$

$$I_E = 2\mu A$$

$$I_B = \frac{2\mu A}{11}$$

$$I_C = \frac{10}{11} \cdot 2\mu A$$


8)

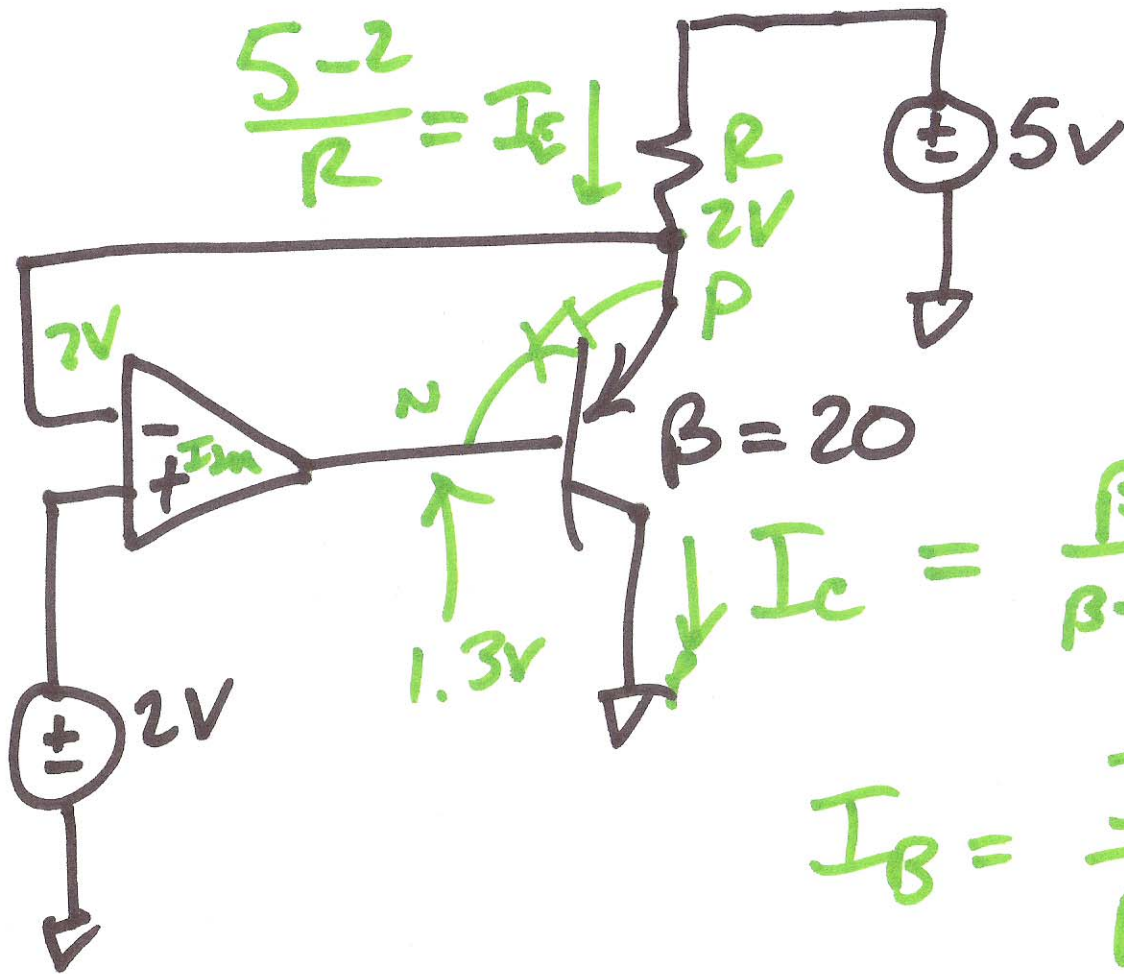

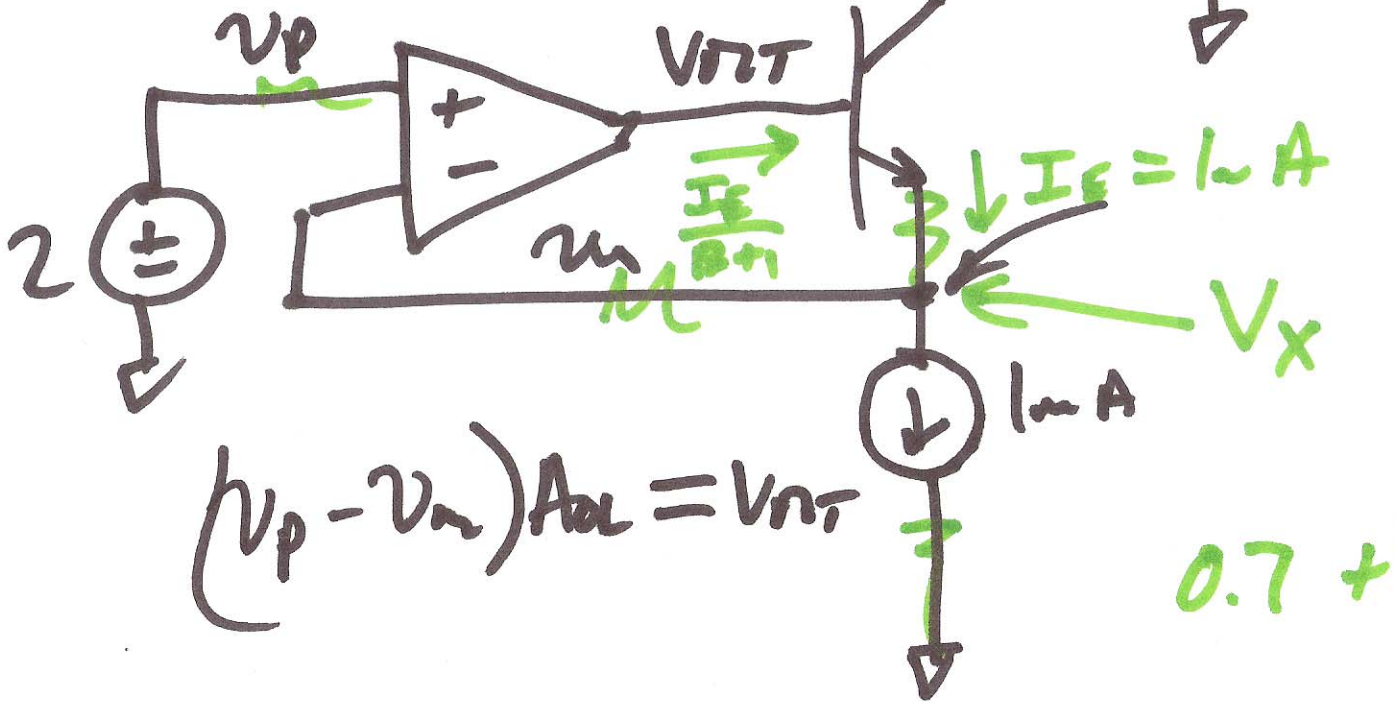9)

OP-Amp has finite gain A_{OL}

$$\frac{\beta}{\beta+1} \cdot I_{mA} = \infty I_E$$




$$V_{OUT} = 0.7 + V_x$$

$$(v_p - v_m) A_{OL} = V_{OUT}$$


$$0.7 + V_x = A_{OL} (2 - V_x)$$

10)

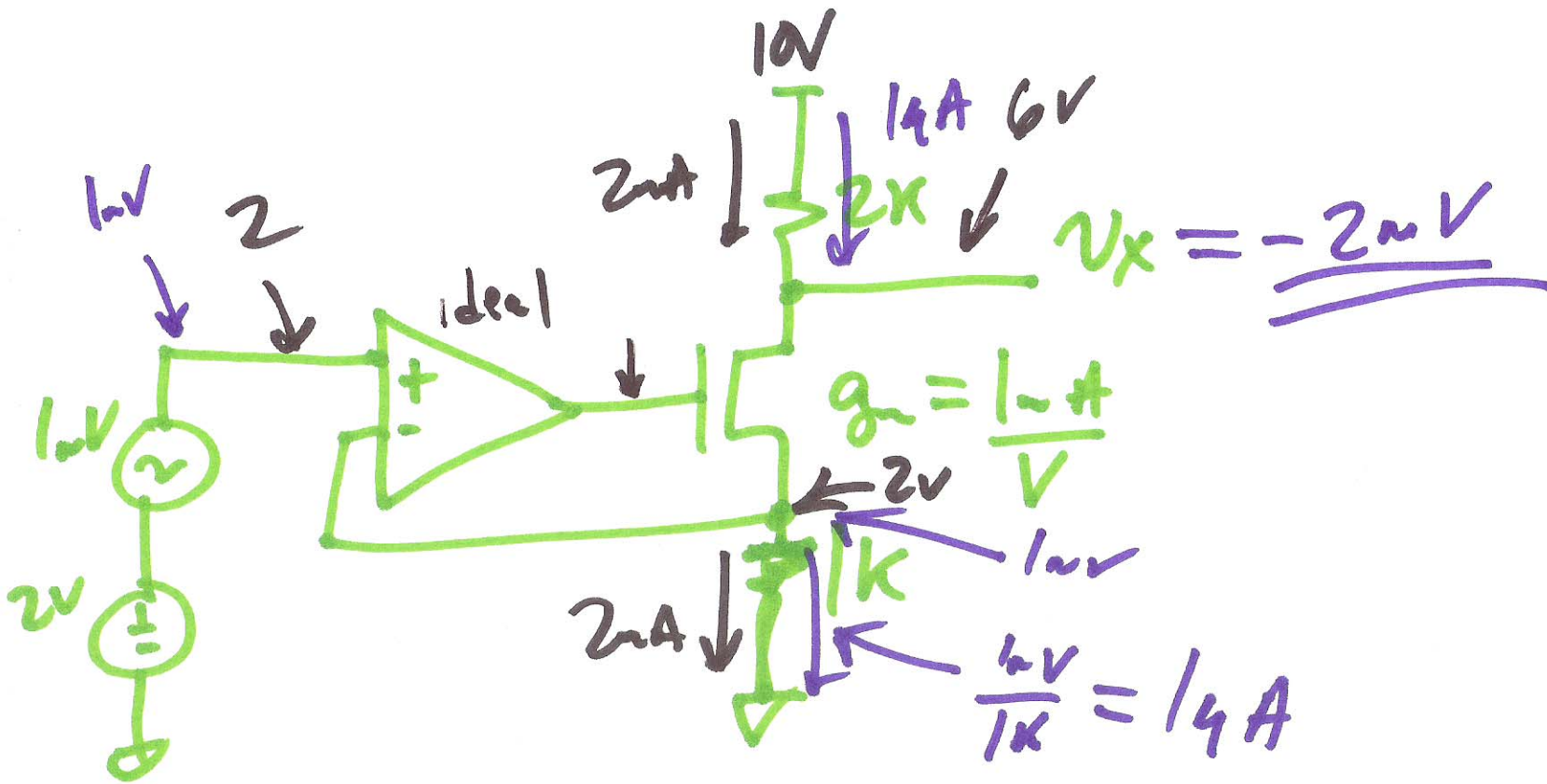

11)

$$i_d = g_m v_{gs}$$

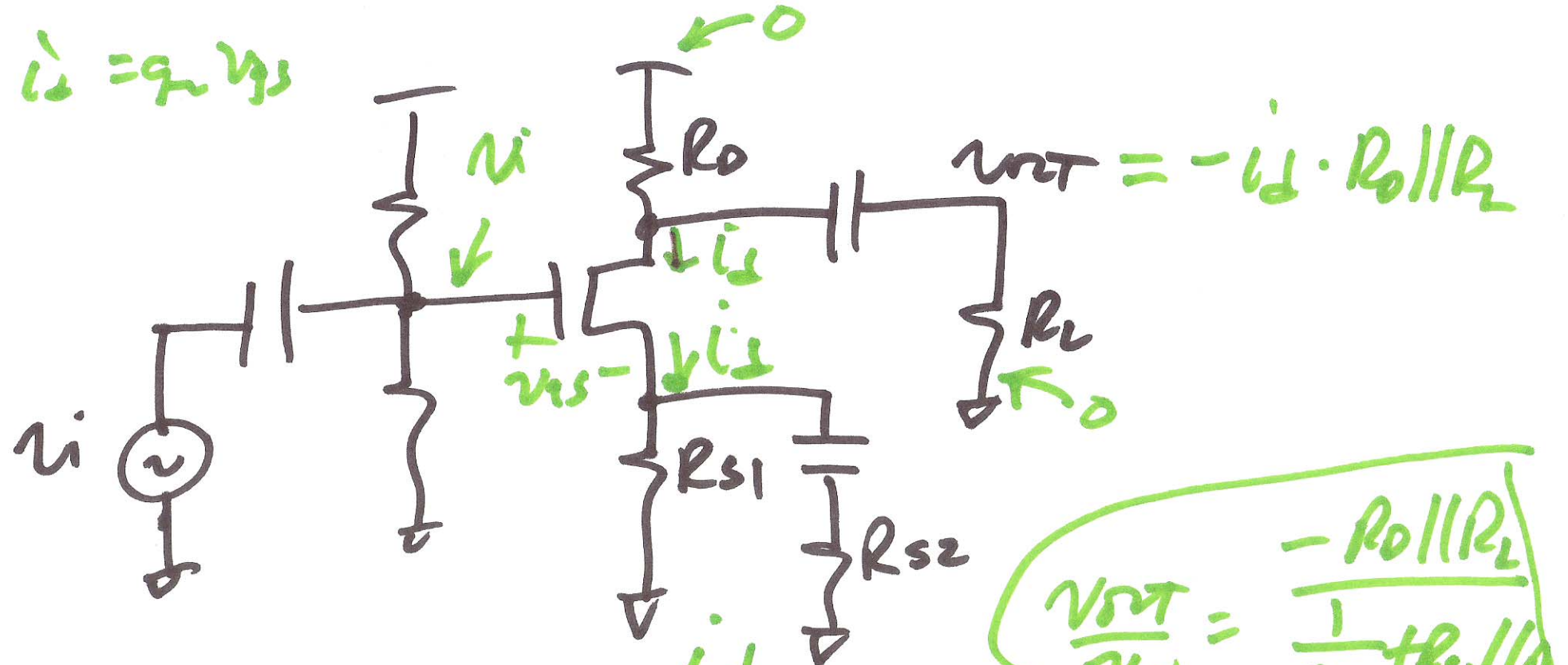

$$v_{out} = -i_d \cdot R_o \parallel R_L$$

$$\frac{v_{out}}{v_i} = \frac{-R_o \parallel R_L}{\frac{1}{g_m} + R_{s1} \parallel R_{s2}}$$

$$v_i = v_{gs} + i_d (R_{s1} \parallel R_{s2})$$

$$v_i = i_d \left(\frac{1}{g_m} + R_{s1} \parallel R_{s2} \right)$$

12)