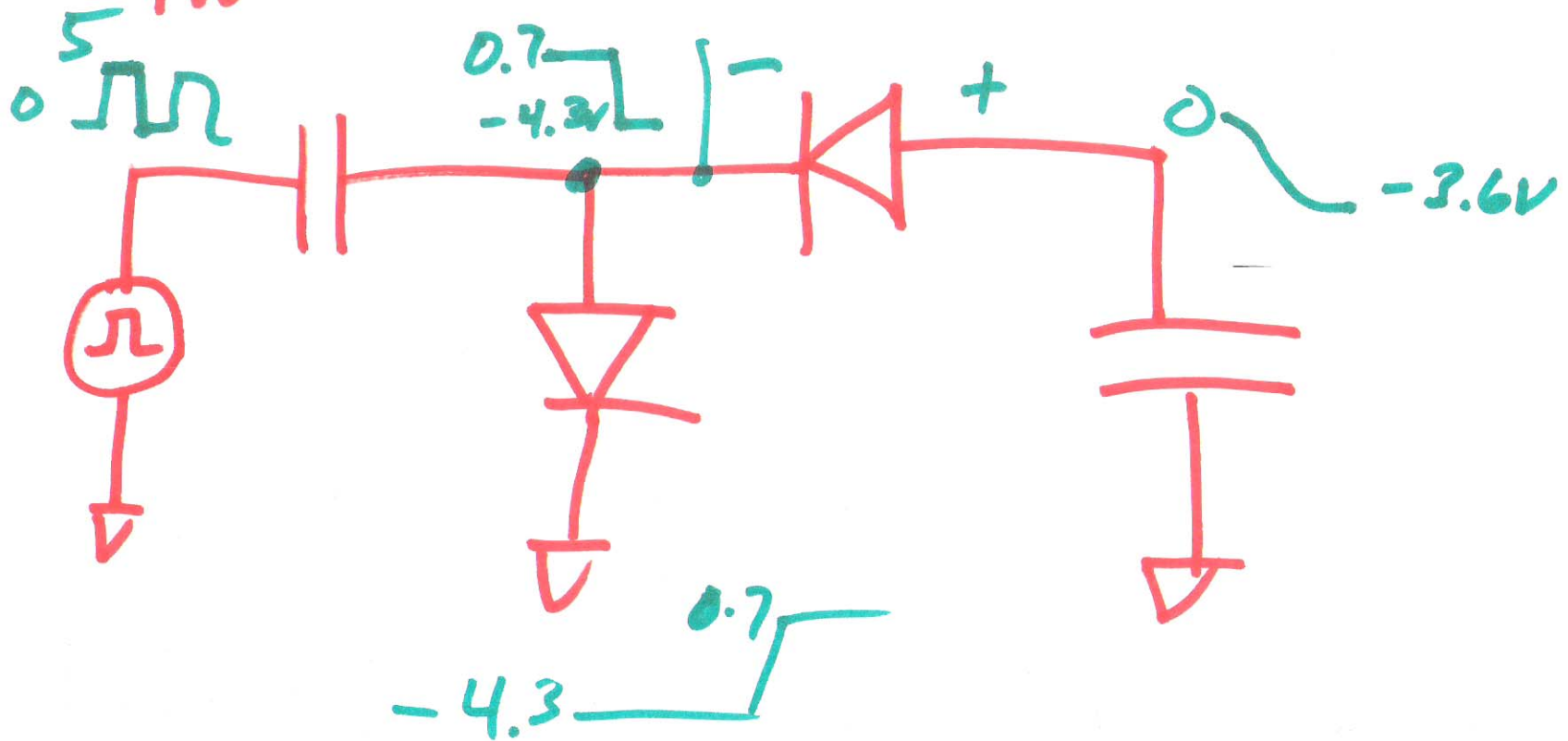


EE 320, Electronics I



Lecture 28

May 6, 2015

MOOP review for final




1)

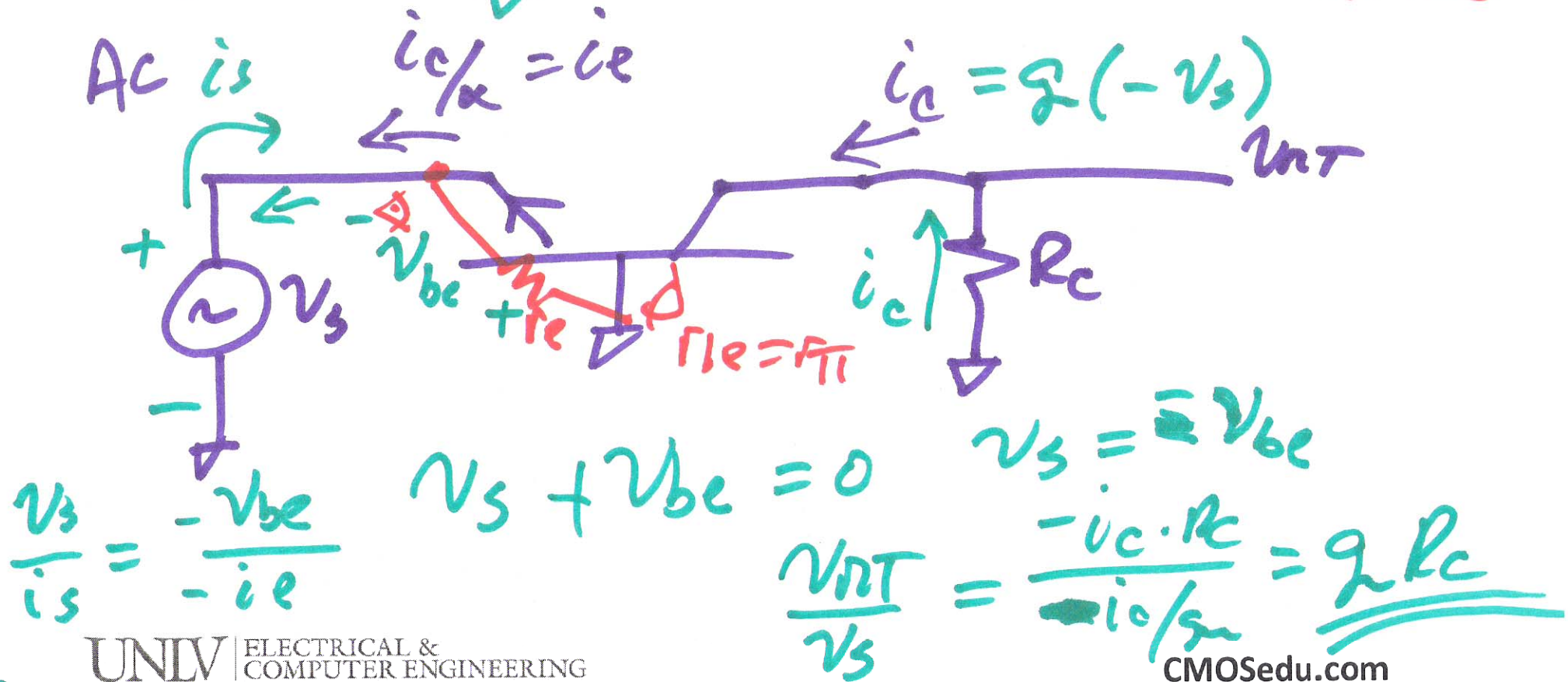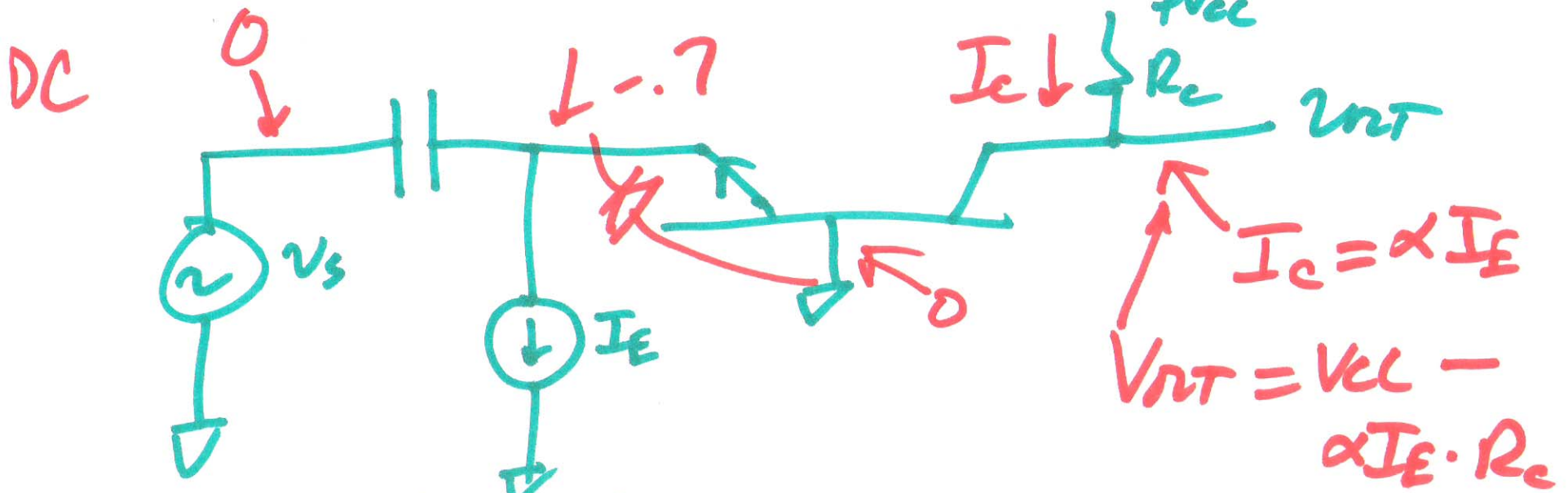


2)

$$R_{in} = \frac{v_s}{i_s} = \frac{-v_{be}}{-i_e} = \frac{i_c/g_m}{i_c/\alpha} = \frac{1}{\beta}$$


$$i_c = g_m v_{be}$$

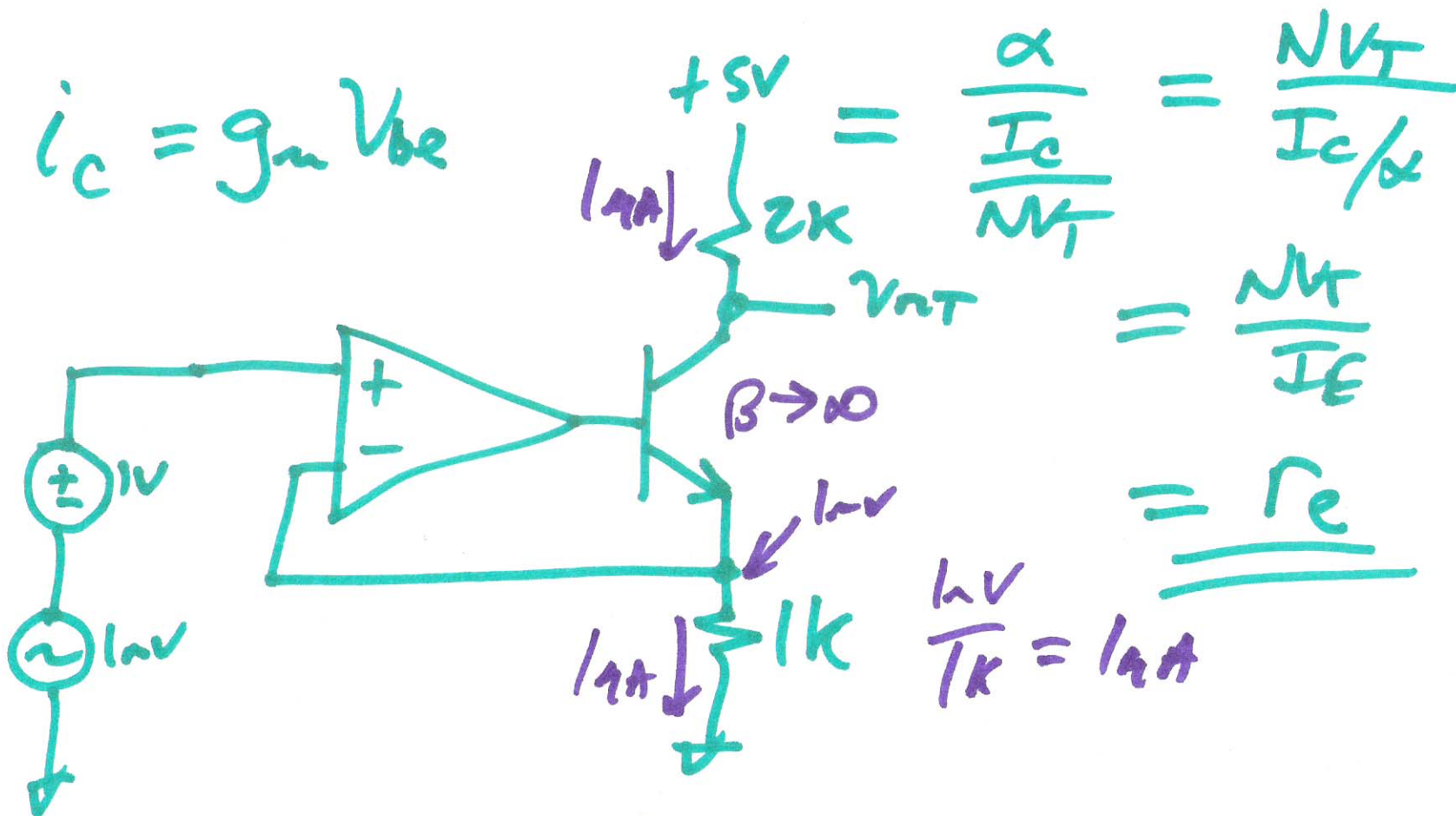
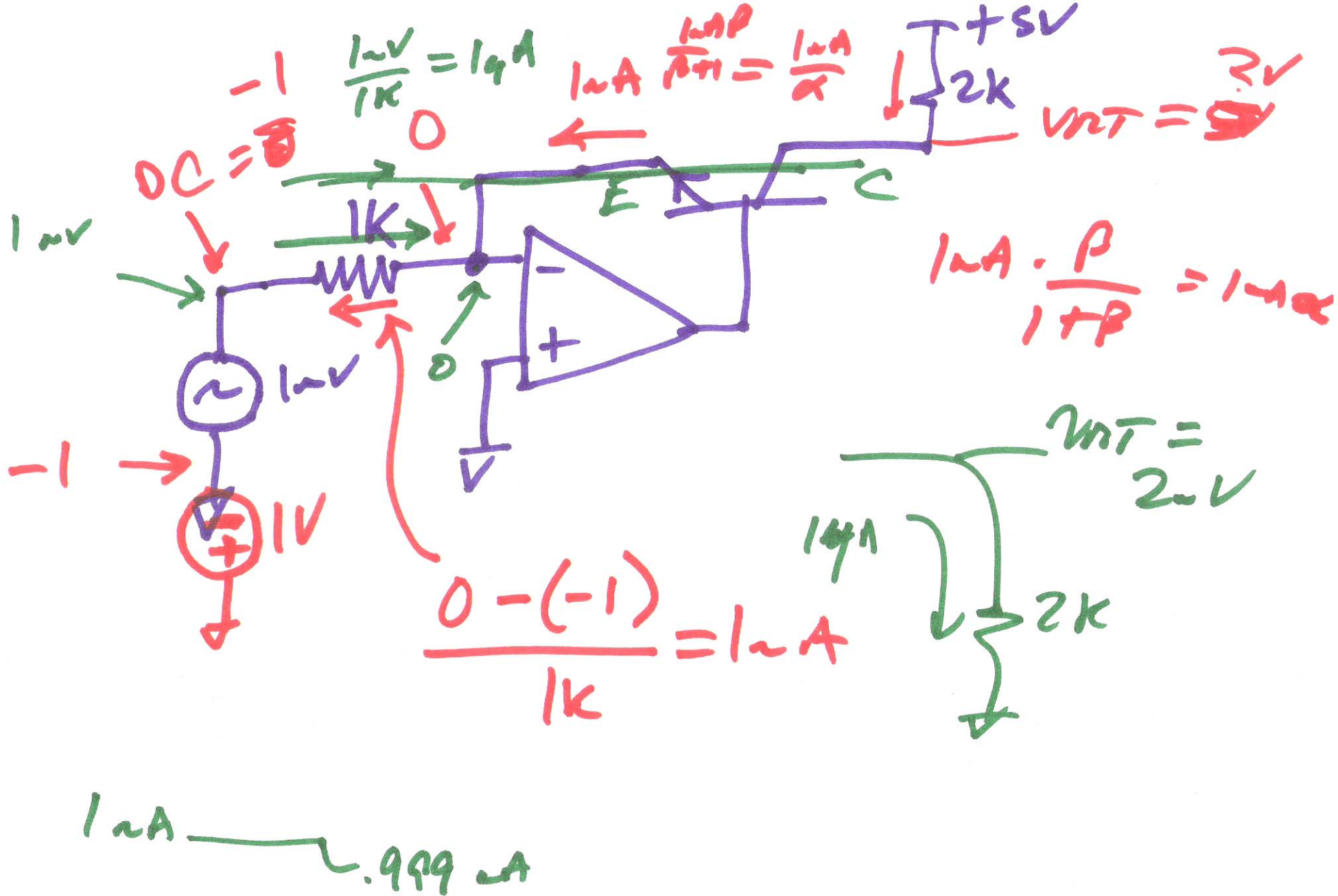
$$v_{NT} = -1\mu A \cdot 2k = \underline{\underline{-2mV}}$$



4)

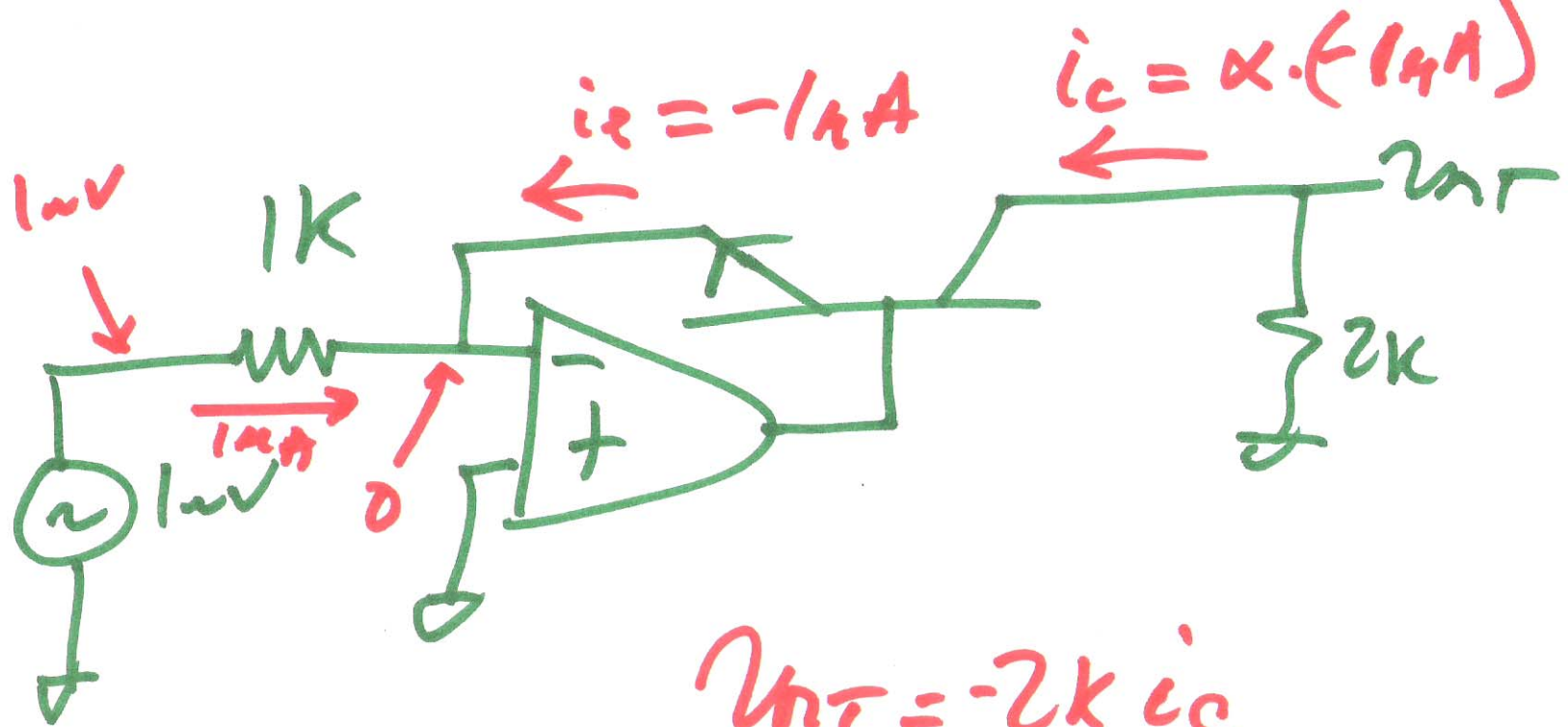


$$V_{mT} = -2\text{k} i_c$$

$$= 2\text{k} \cdot \alpha \cdot 1\mu\text{A}$$

$$\approx \underline{\underline{2\mu\text{V}}}$$

5)

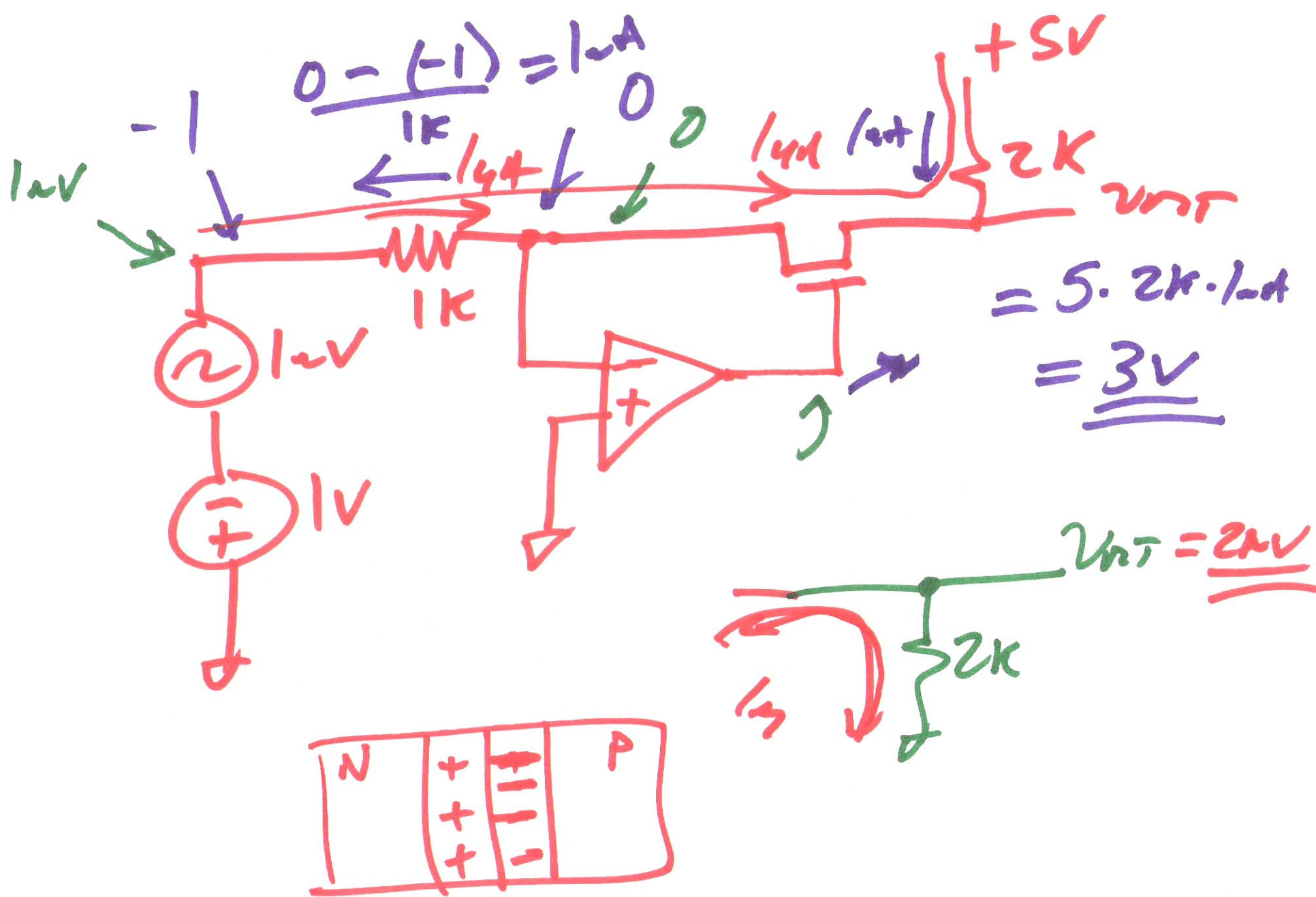

b)