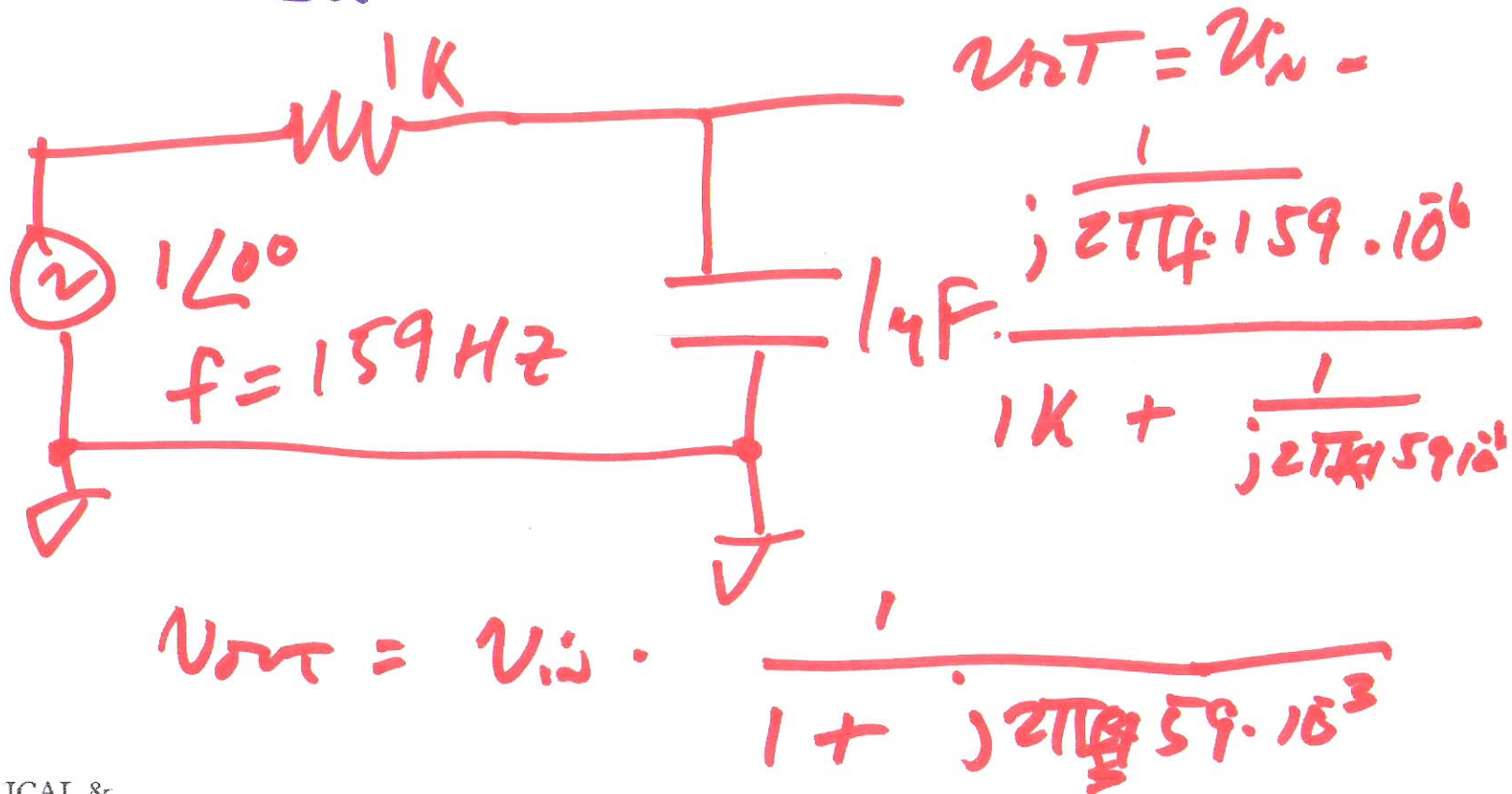


# EE 320

## Engineering Electronics I


### Lecture 3

Jan. 26, 2015



$$V_{out} = V_{in} \cdot \frac{1}{1 + j\omega RC}$$
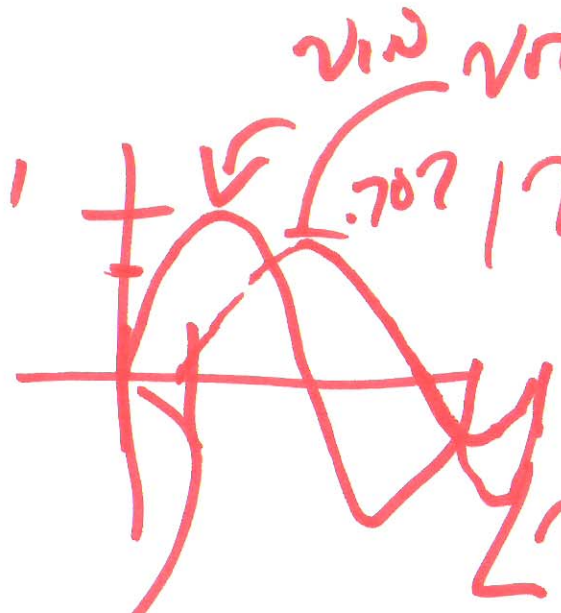
$$V_{out} = \frac{1 \angle 0^\circ}{1 + j}$$





$$|V_{out}| = \frac{1}{\sqrt{1^2 + 1^2}} = \frac{1}{\sqrt{2}} = 0.707$$


$$\angle V_{out} = 0^\circ - \tan^{-1} \frac{1}{1} = -45^\circ$$

$$t_d = \frac{45^\circ}{360} \cdot \frac{1}{159}$$

2)

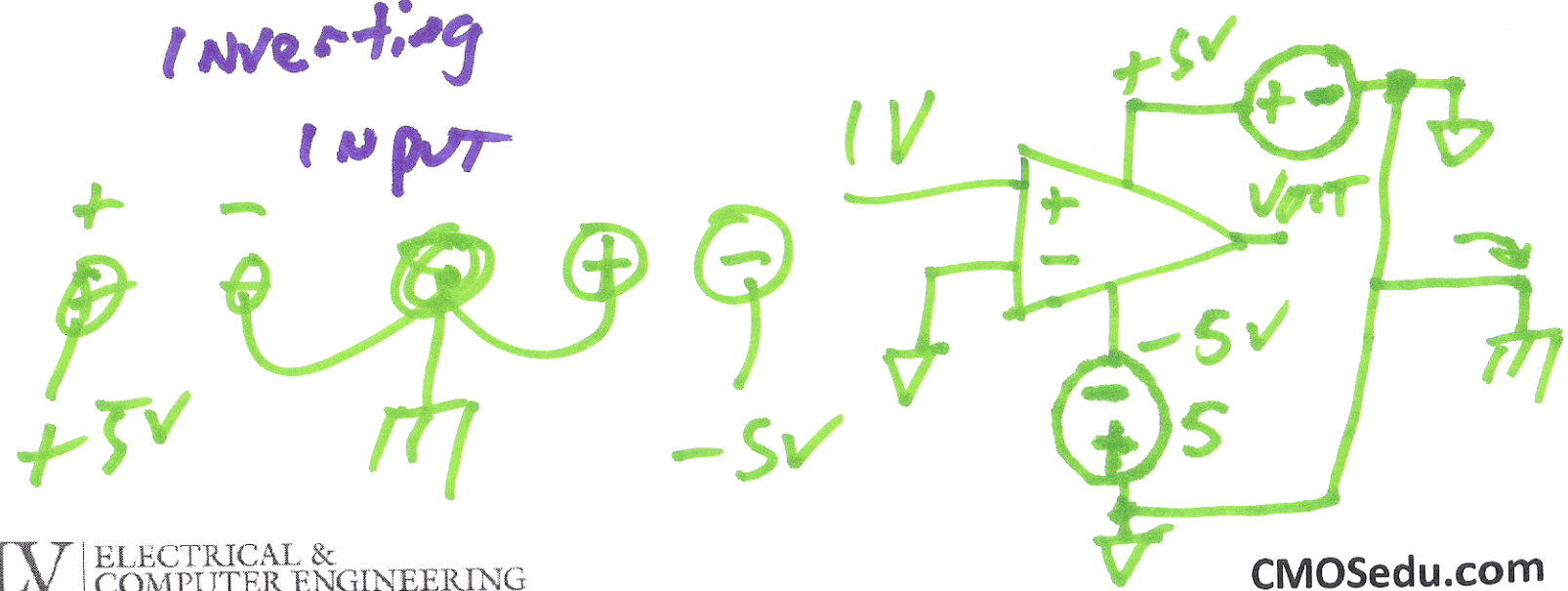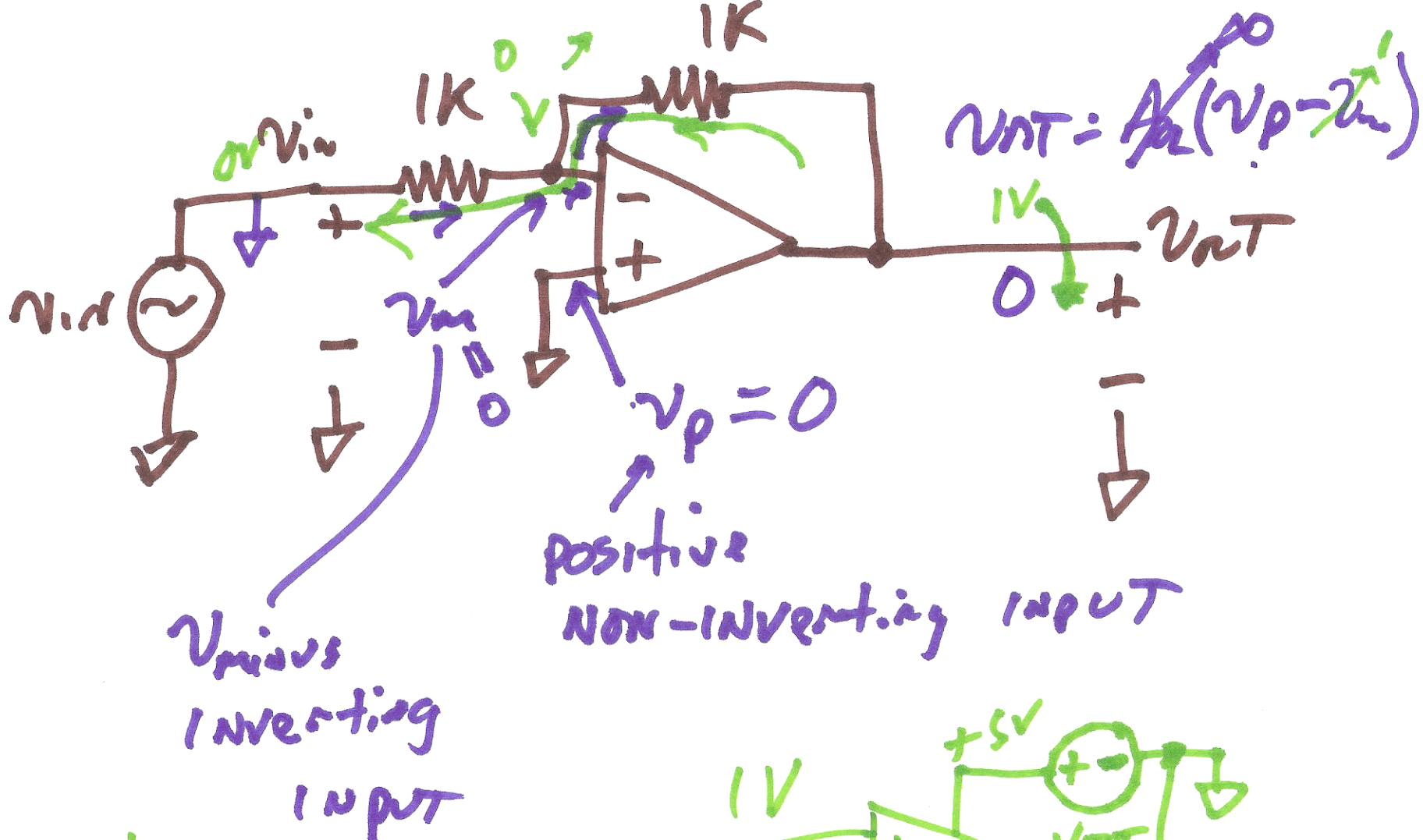

3)

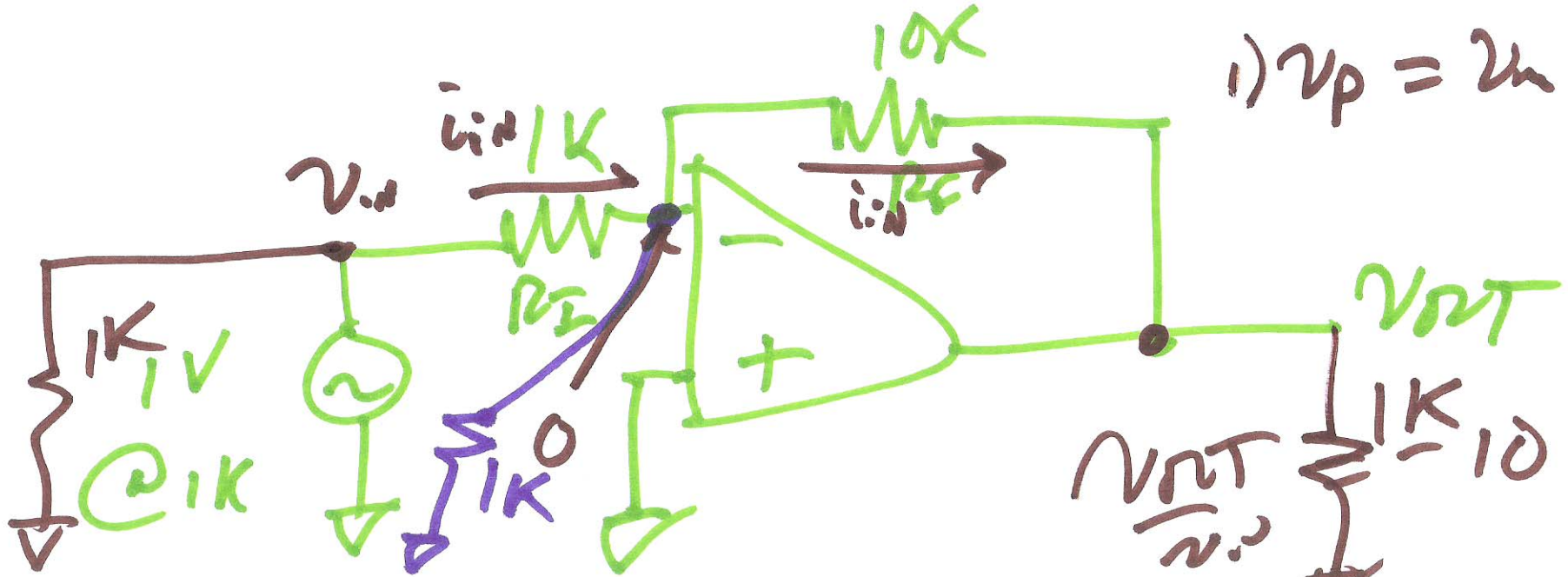


$$i_{in} = \frac{v_i - 0}{1K} = \frac{0 - v_{out}}{10K}$$

inverting  
Amp

$$\frac{R_f}{R_i} = \frac{10K}{1K} = \frac{-v_{out}}{v_i}, \quad \boxed{\frac{v_{out}}{v_i} = -\frac{R_f}{R_i}}$$

inverting  
amp.

4)

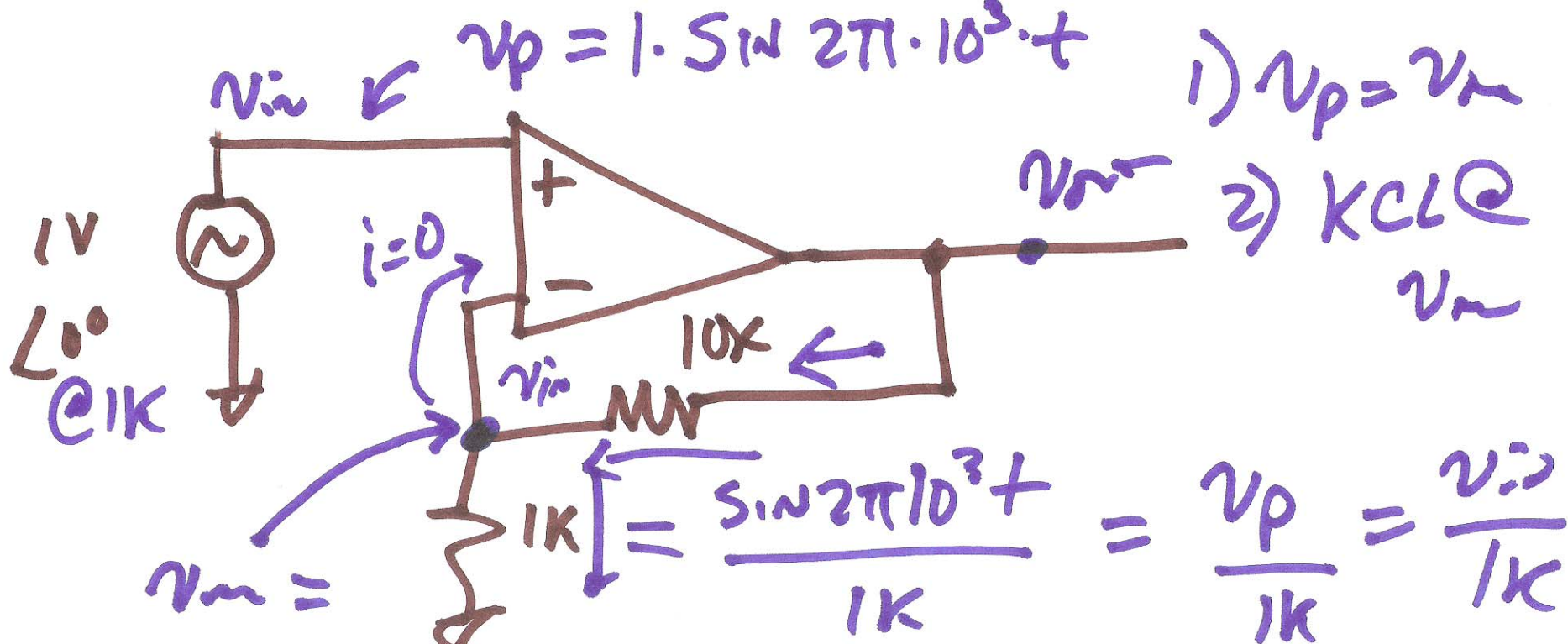

$\sin 2\pi 10^3 t \cdot V$

$\frac{v_{out} - v_{in}}{10K} = \frac{v_{in}}{1K}$

$\frac{v_{out}}{v_{in}} = \frac{10K}{1K} + \frac{10K}{10K}$


$= 10 + 1 = 11$

$\frac{v_{out}}{10K} = \frac{v_{in}}{1K} + \frac{v_{in}}{10K}$

$1 + \frac{R_F}{R_I} = \frac{R_F + R_I}{R_I}$

5)

NON-INVERTING!

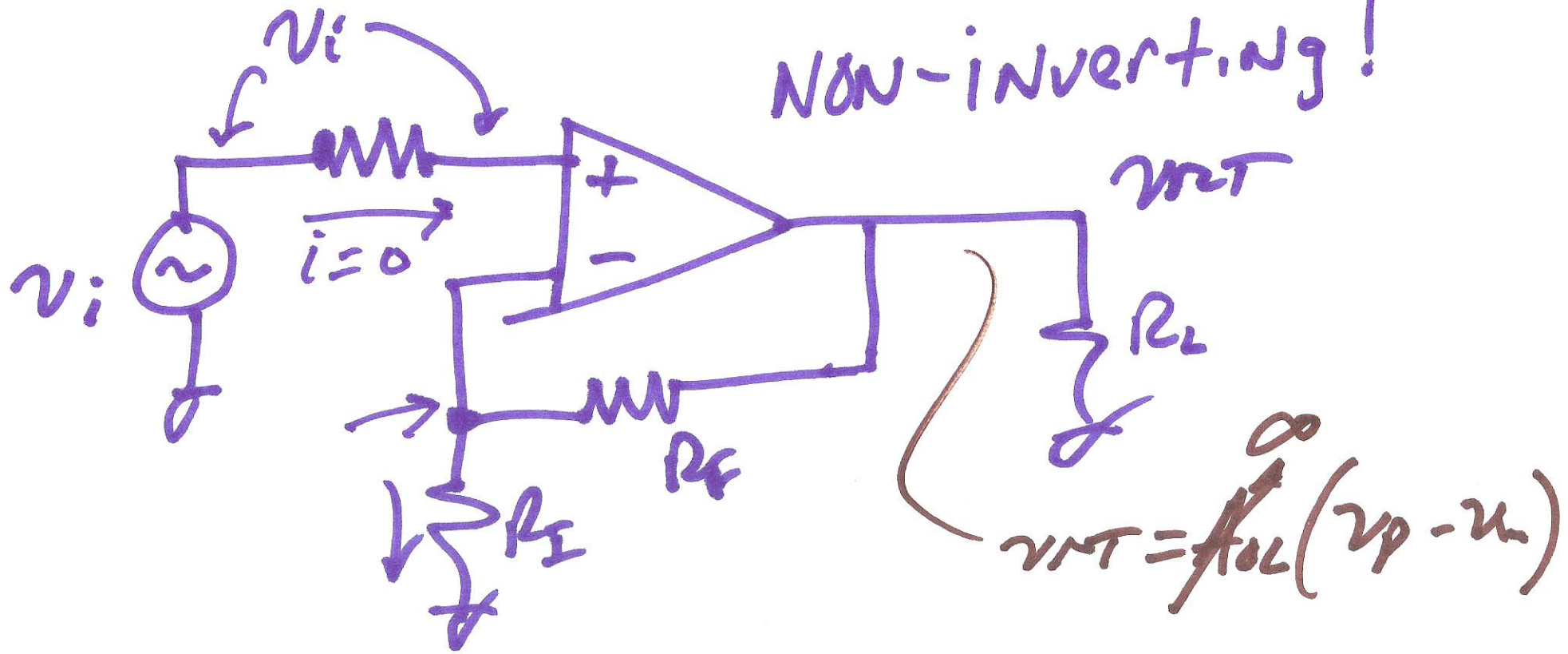


$$\frac{v_i}{R_I} = \frac{v_{OUT} - v_i}{R_F} \Rightarrow \frac{v_{OUT}}{v_i} = 1 + \frac{R_F}{R_I}$$

$$\frac{v_{OUT}}{v_{in}} = \frac{R_I + R_F}{R_I}$$

b)

# Voltage follower

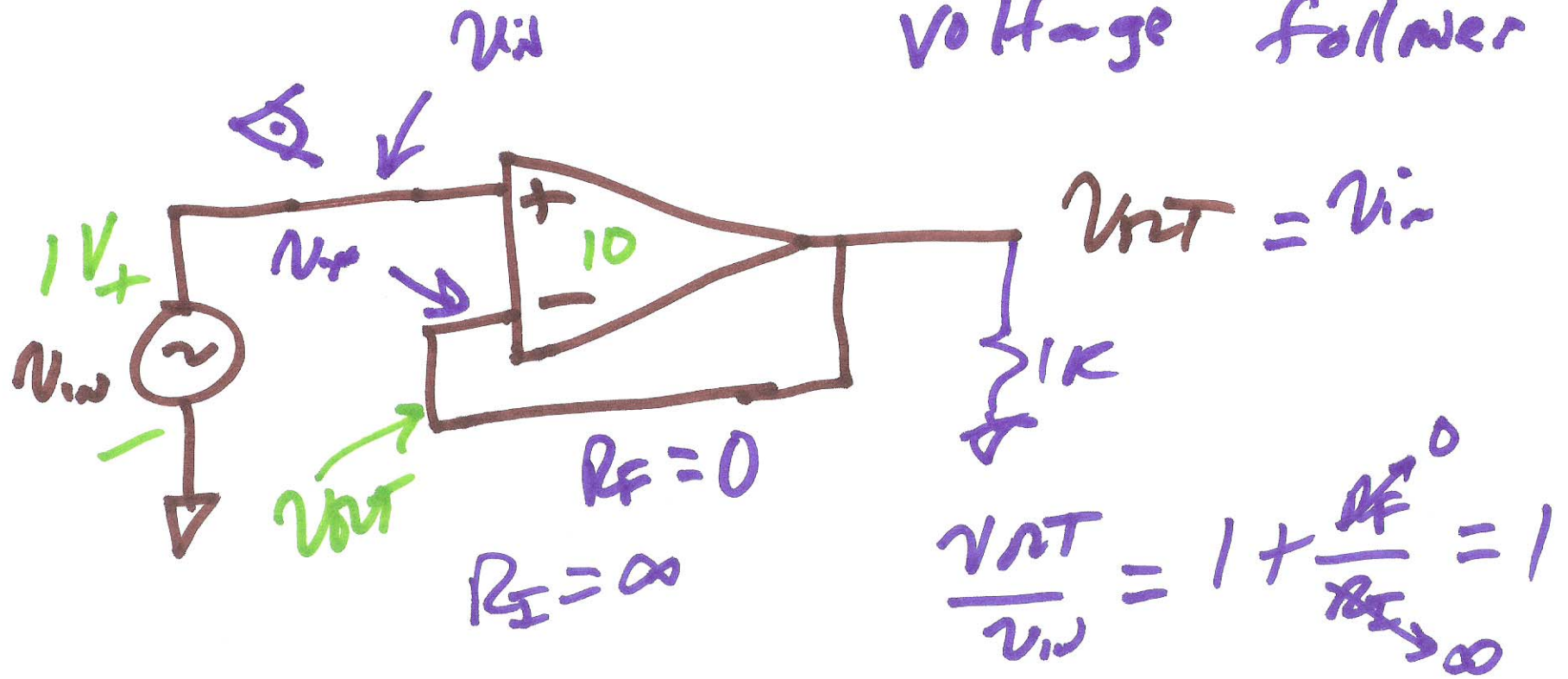

$$v_{out} = 10 \cdot (1 - v_{out})$$

$$v_{out} = 10 - 10v_{out} \quad v_{out} = \frac{10}{11} = .9$$