

# Lecture 7

Feb. 6, 2015

EE 320

\* Extra \*

$v_I = 10 \mu V$  rms  $\rightarrow$  peak  $\rightarrow 14.1 \mu V$


$i_I = 100 \mu A$  rms  $\rightarrow$  peak  $\rightarrow 140 \mu A$


$v_o = 1V$  rms

$R_L = 10K$   
 $R_S = 0$

$10 \mu V = 10^{-5}$   
 $100K = 10^5$

AV  
AI  
PP

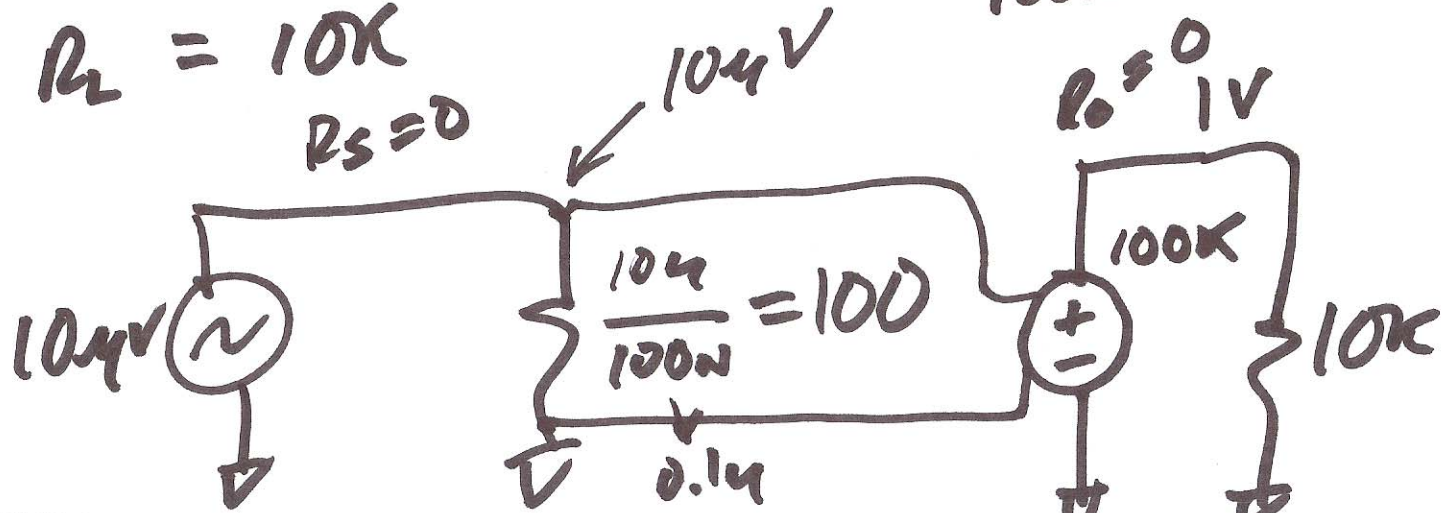

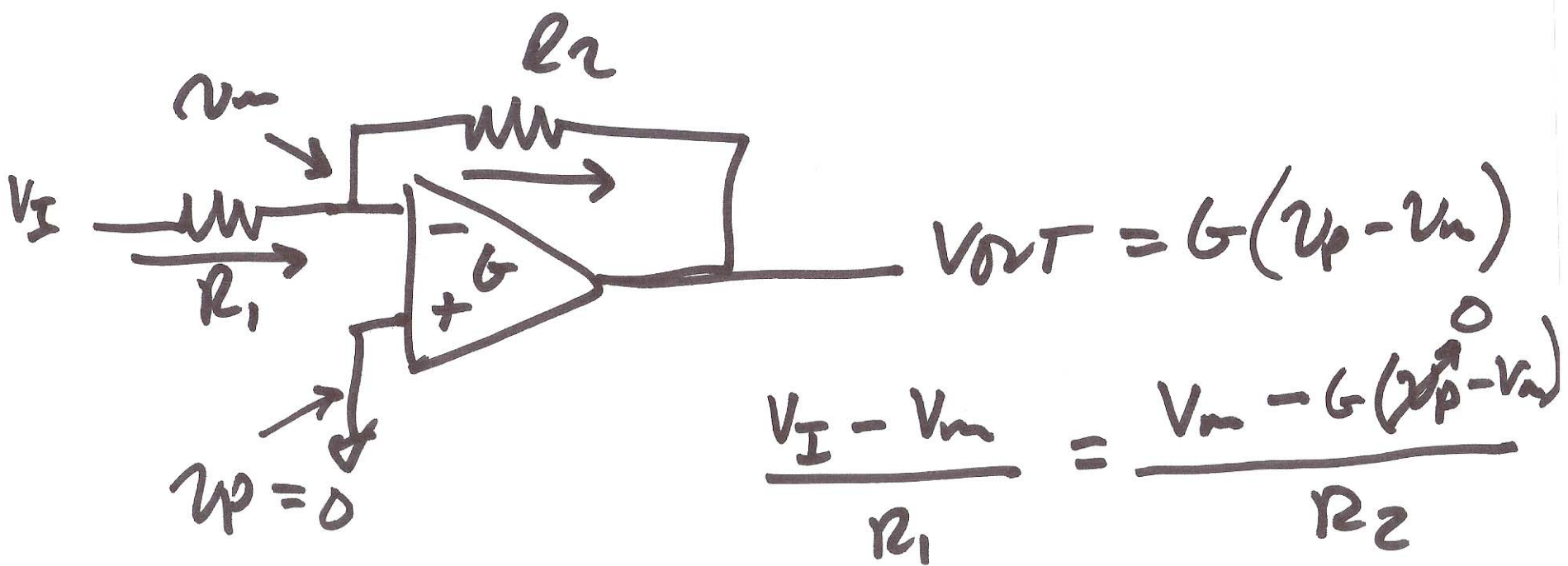

$$\frac{V_{OUT}}{V_I} = \frac{-1}{\frac{1}{G} + \frac{R_1}{G R_2} + \frac{R_1}{R_2}} + V_I - V_n = \frac{R_1}{R_2} V_n + G \frac{R_1}{R_2} V_n$$

$$V_I = V_n \left( 1 + \frac{R_1}{R_2} + \frac{R_1}{R_2} G \right)$$

$$V_{OUT} = \frac{-G V_I}{1 + \left( \frac{R_1}{R_2} + \frac{R_1}{R_2} G \right)}$$

2)

$$V_I = V_{in} \left( 1 + \frac{R_1}{R_2} + G \frac{R_1}{R_2} \right)$$

$$V_{in} = \frac{V_I}{1 + \frac{R_1}{R_2} + G \frac{R_1}{R_2}}$$

$$V_{out} = G(V_{in} - V_{in})$$

$$V_{out} = \frac{-G V_I}{1 + \frac{R_1}{R_2} + G \frac{R_1}{R_2}}$$



$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{G} + \frac{R_1}{G R_2} + \frac{R_1}{R_2}}$$

$$G = \frac{R_2}{R_1}$$

A = Open loop gain

$$\frac{R_c}{R_1} = \frac{A \cdot G}{1 + G}$$

$$\frac{V_{out}}{V_{in}} =$$

$$\frac{-1}{\frac{1}{A} + \frac{R_1 || R_c}{A \cdot R_2} + \frac{R_1 || R_c}{R_2}}$$

$$R_1 || R_c = \frac{1}{\frac{1}{R_1} + \frac{1}{R_c}}$$

$$+ \frac{R_2}{R_1} =$$

$$\frac{-1}{\frac{1}{A} + \frac{R_1 || R_c}{A \cdot R_2} + \frac{R_1 || R_c}{R_2}}$$

$$+ \frac{R_2}{R_1} = \frac{R_1}{R_2} \cdot \frac{1}{G}$$

$$\frac{1}{A} + \frac{1}{A R_2 \left( \frac{1}{R_1} + \frac{1}{R_c} \right)}$$

4)



$$\frac{1}{A} + \frac{1}{A\left(G + \frac{R_2}{R_c}\right)} + \frac{A}{A\left(G + \frac{R_2}{R_c}\right)} = \frac{1}{G}$$

$$\frac{1}{G} - \frac{1}{A} = \frac{A-G}{AG} = \frac{1+A}{A\left(G + \frac{R_2}{R_c}\right)}$$

$$A-G = \frac{G(1+A)}{G + \frac{R_2}{R_c}}, \quad G = \frac{R_2}{R_1}$$

$$\frac{1+A}{1 + \frac{R_1}{R_c}} = \frac{\frac{R_2}{R_1} + A \frac{R_2}{R_1}}{\frac{R_2}{R_1} + \frac{R_2}{R_c}} = \frac{\frac{R_2}{R_1} + A \frac{R_2}{R_1}}{\frac{R_2 R_c + R_1 R_c}{R_1 R_c}}$$


5)

$$A - G = \frac{1 + A}{1 + \frac{R_1}{R_c}} \cdot \frac{R_c/R_1}{\frac{R_c}{R_1}}$$

$$A - G = \frac{\frac{R_c}{R_1} + A \frac{R_c}{R_1}}{\frac{R_c}{R_1} + 1}$$


$$(A - G) \left( \frac{R_c}{R_1} + 1 \right) - A \frac{R_c}{R_1} = \frac{R_c}{R_1}$$
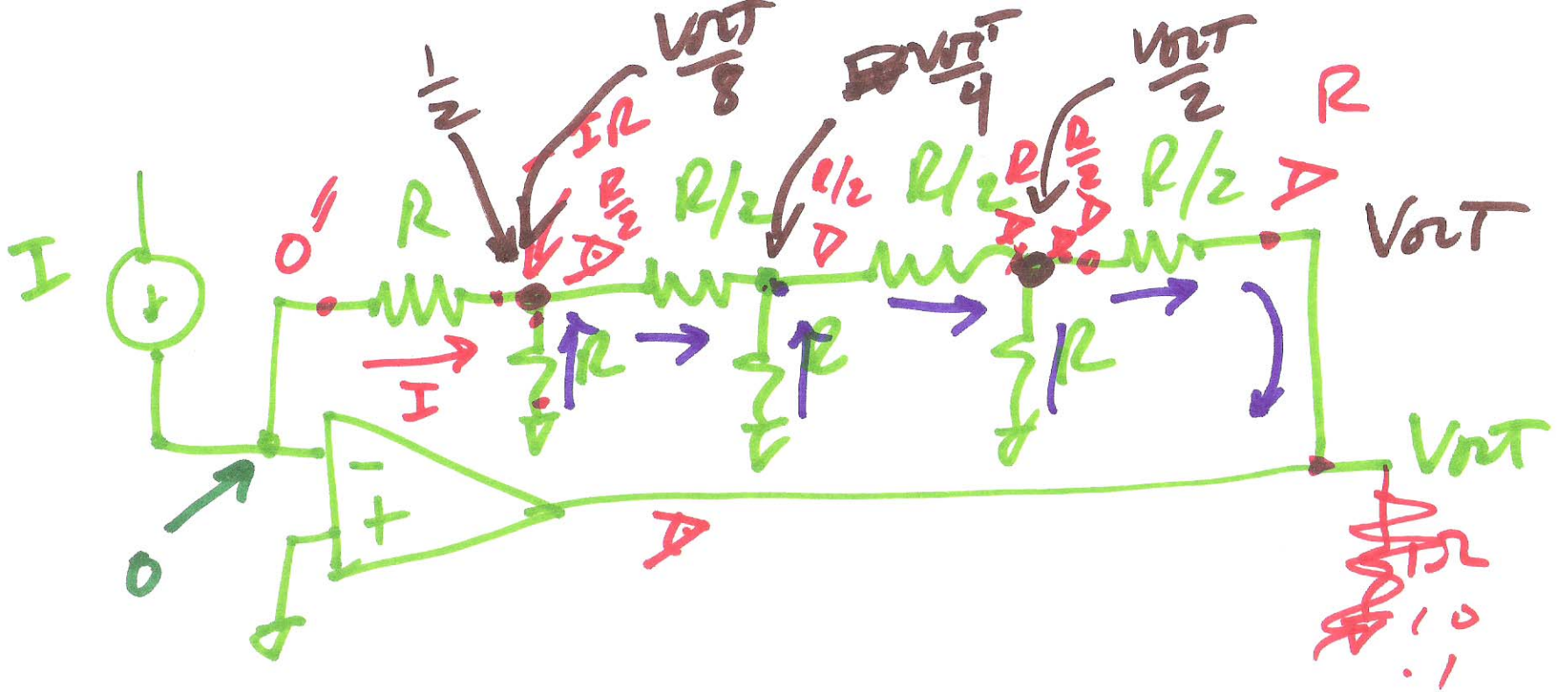
$$(A - G) \frac{R_c}{R_1} + \cancel{A} - G - \cancel{A} \frac{R_c}{R_1} = \frac{R_c}{R_1}$$



$$I \cdot R = -\frac{V_{out}}{8}$$

$$\frac{V_{out}}{I} = -8R$$

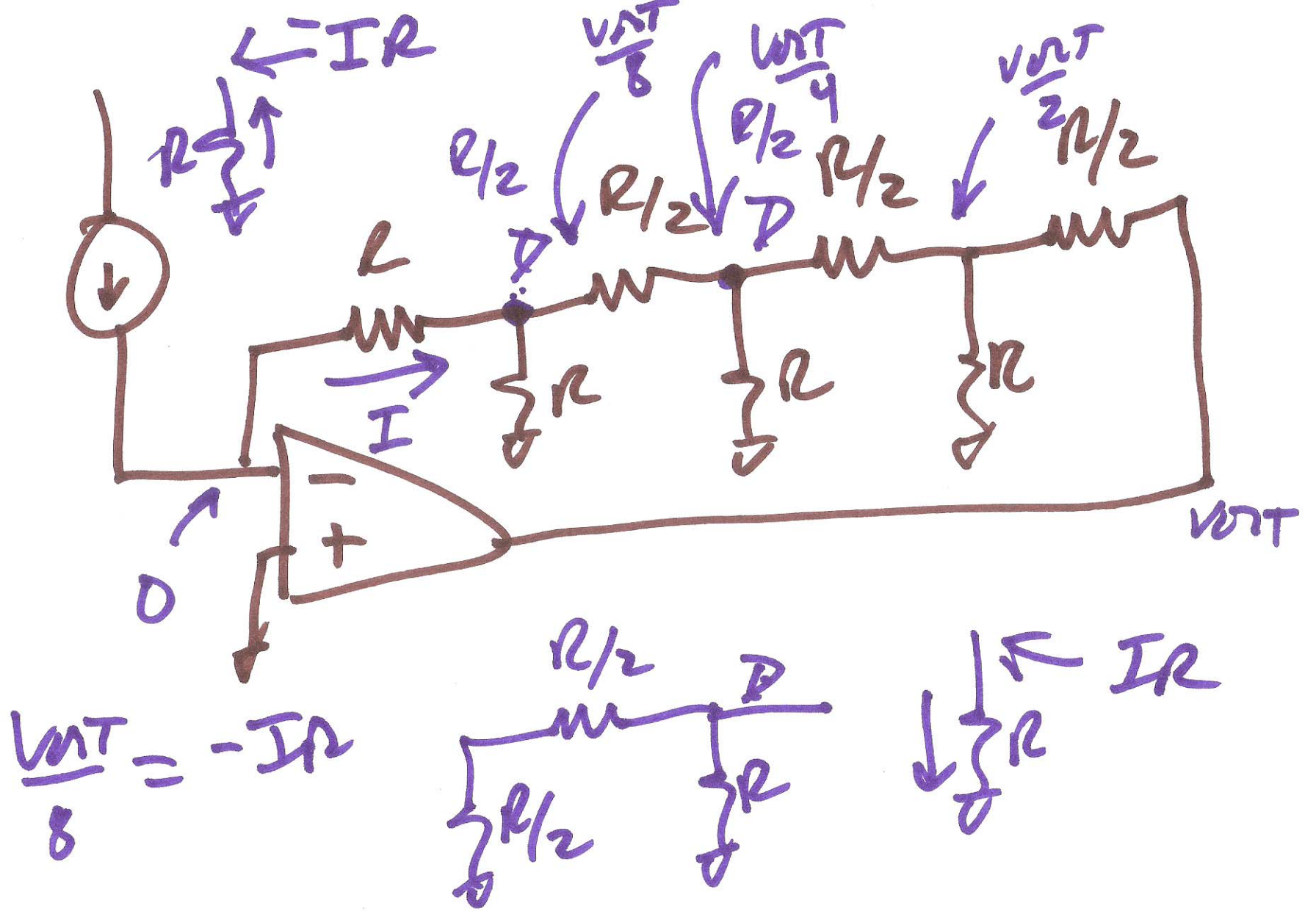

8)