

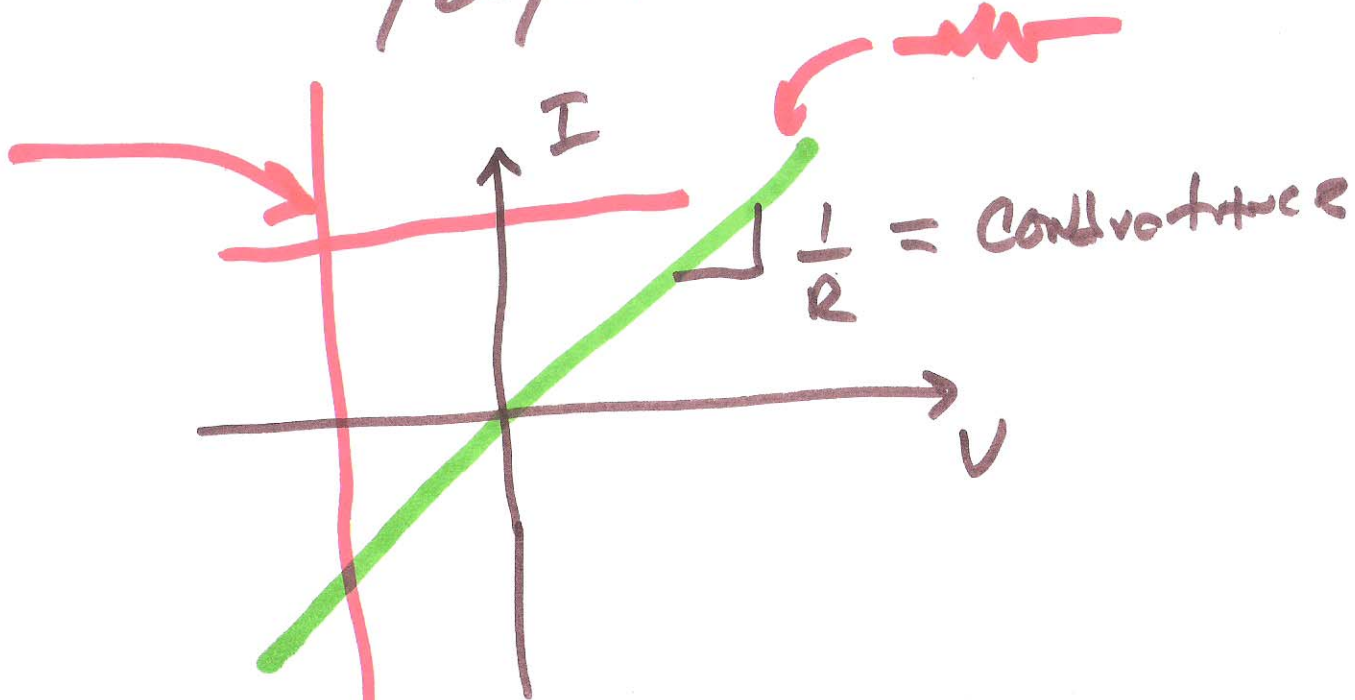
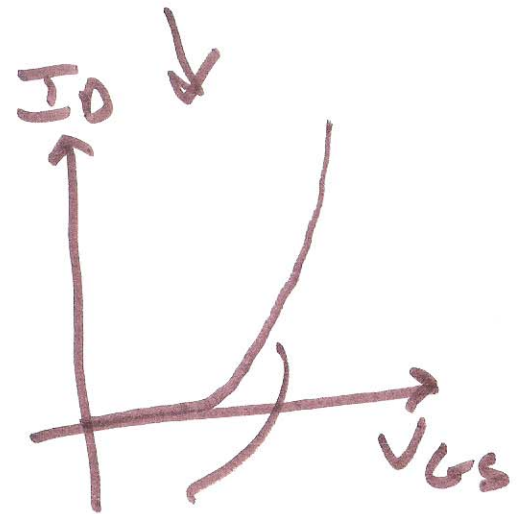
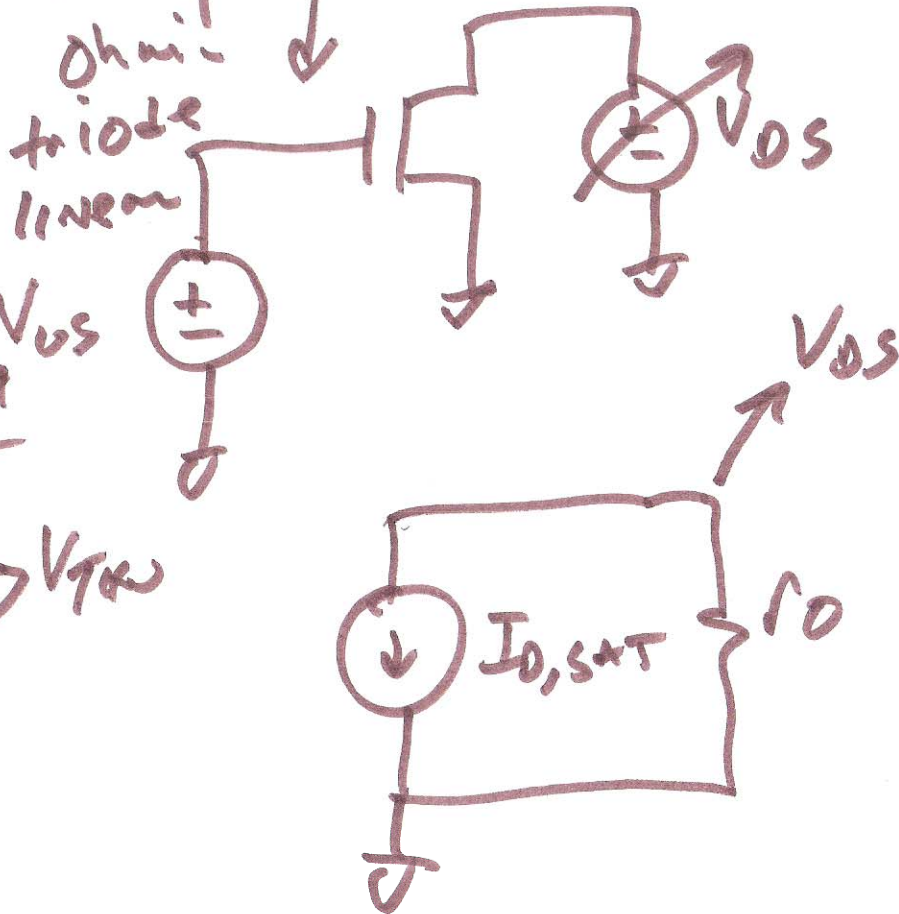


EE 420 / ECE 620

Analog IC Design



1/22/14 Lecture 1

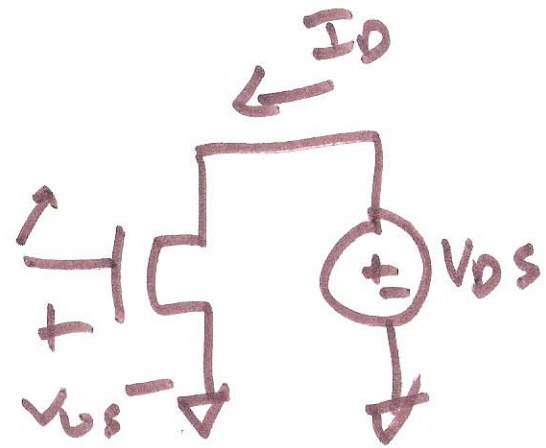



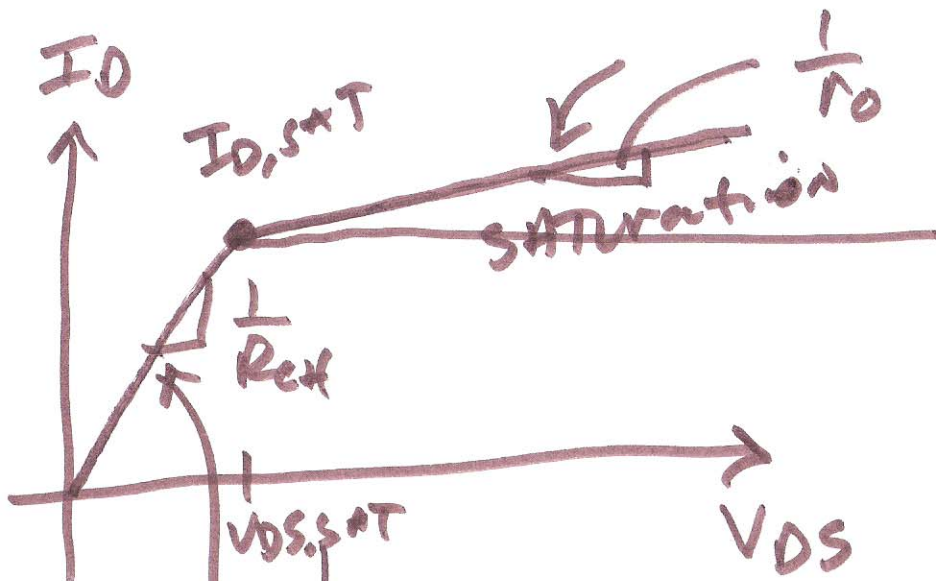


$$I_D = \frac{K P_n}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{GS} > V_{TH}$$

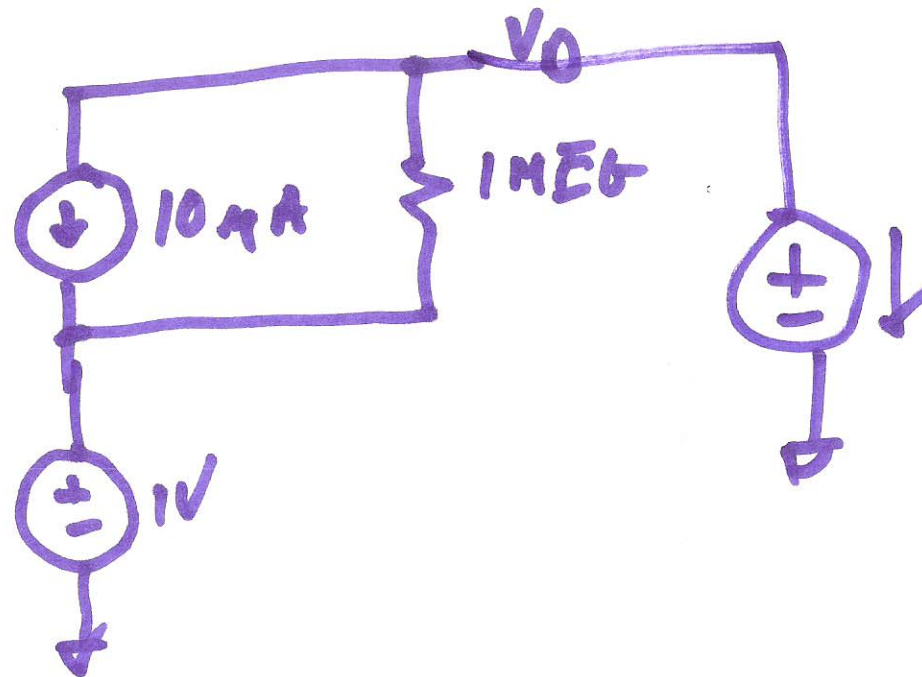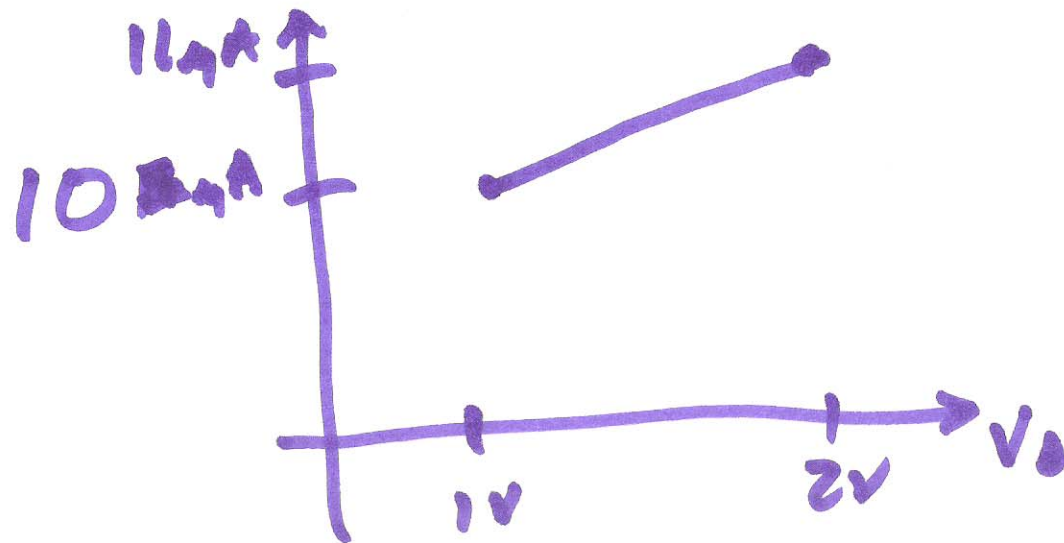

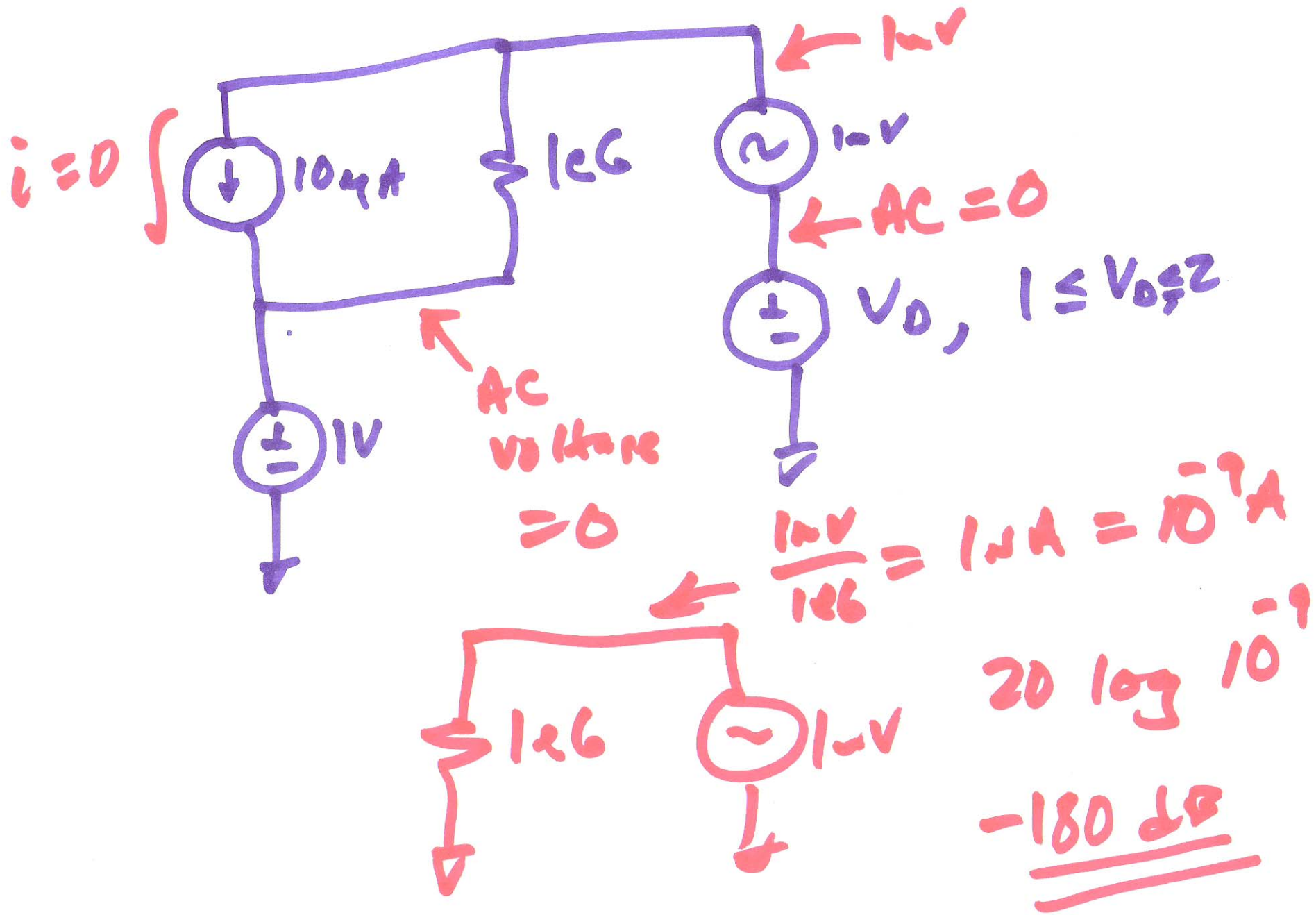

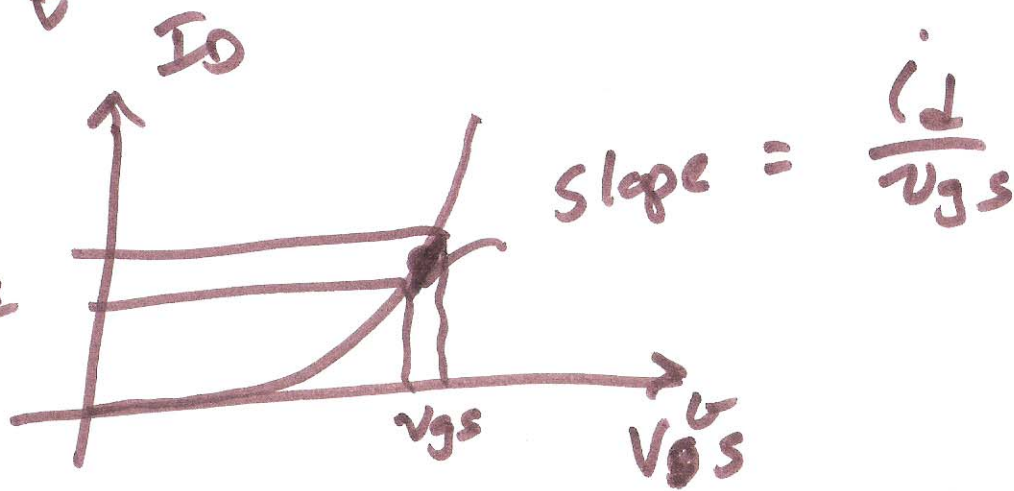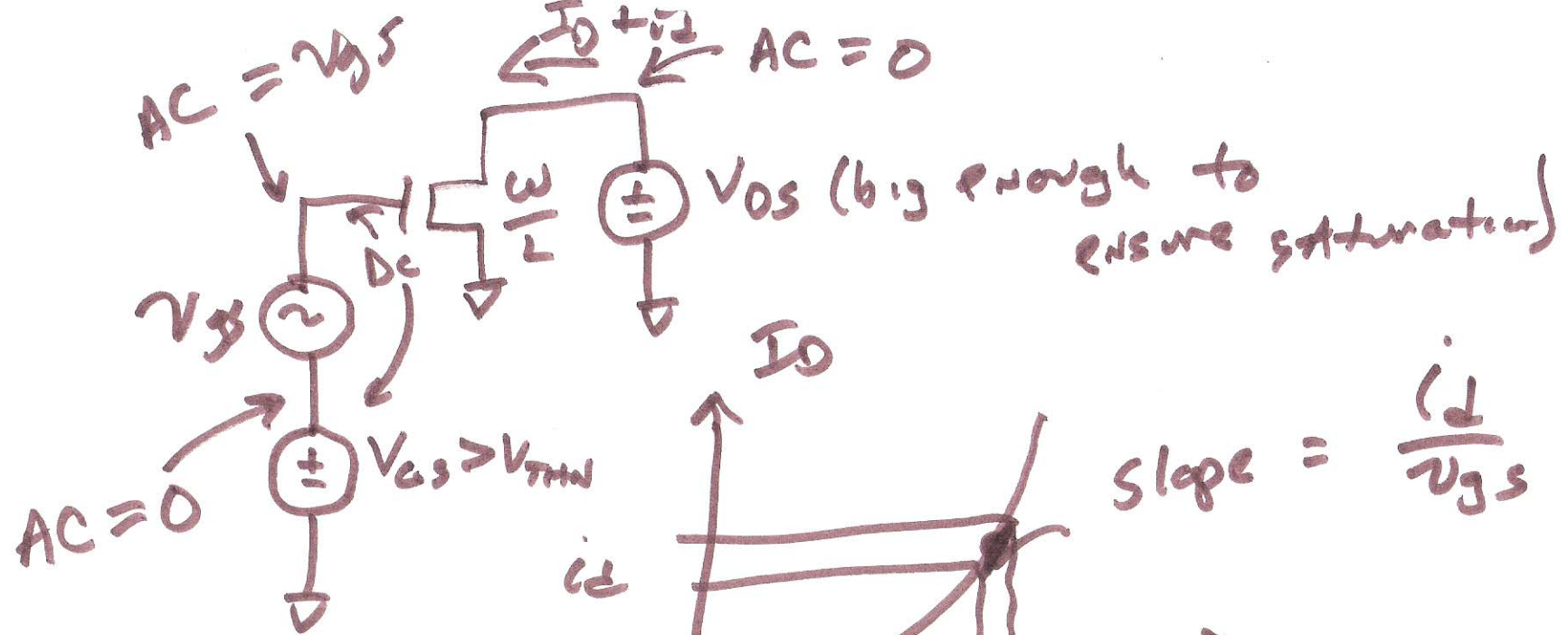

$v_{gs} \ll V_{GS}$

i.c. AC DC

$$i_D = I_D + i_d =$$

$$v_{GS} = v_{gs} + V_{GS}$$

AC + DC

v.c.

$$\frac{K_P}{2} \cdot \frac{W}{L} \cdot \underbrace{(V_{GS} + v_{gs} - V_{THN})^2}_{V_{GS}}$$

$4N \cdot C_{ox}$

5)

$$g_m = \text{slope} = \frac{\delta I_D}{\delta V_{GS}} = \frac{\delta}{\delta V_{GS}} \left( \frac{K_P}{2} \frac{W}{L} (V_{GS} + V_{GS} - V_{THN})^2 \right)$$

$V_{GS} = \text{CONST}$   
 $I_D = \text{CONST}$

$$\frac{\delta}{\delta V_{GS}} \left( \frac{K_P}{2} \cdot \frac{W}{L} \left( \underbrace{V_{GS} + V_{GS}}_{V_{GS}} - V_{THN} \right)^2 \right)$$


$$\beta = K_P \cdot \frac{W}{L} \quad g_m = K_P \cdot \frac{W}{L} (V_{GS} + V_{GS} - V_{THN}) \cdot 1$$

Small-signal Approx  $V_{GS} \Rightarrow V_{GS}$

$$g_m \approx K_P \cdot \frac{W}{L} (V_{GS} - V_{THN})$$

6)

$$K_P = 120 \mu\text{A}/\text{V}^2$$

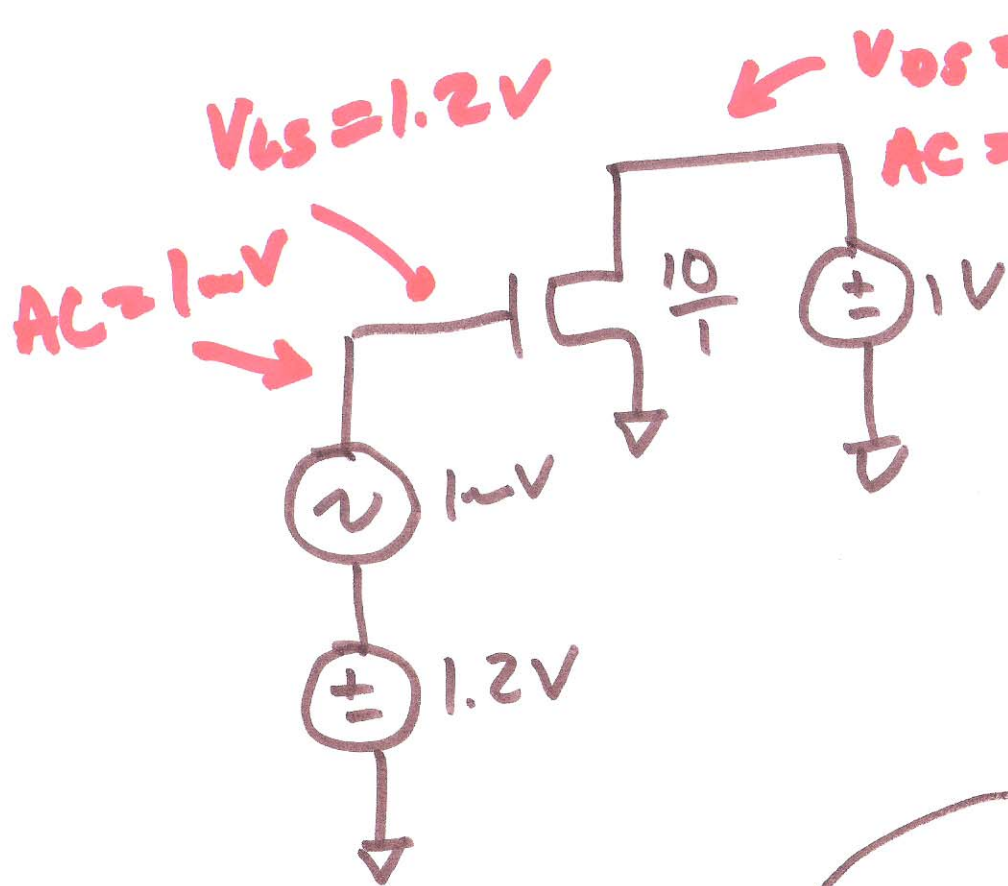

$$V_{THN} = 0.8\text{V}$$

$$V_{GS} > V_{THN}$$

$$V_{DS} \approx V_{GS} - V_{THN}$$

$$1\text{V} \approx 1.2 - 0.8$$

yes!

$$g_m = K_P \cdot \frac{W}{L} (V_{GS} - V_{THN})$$


$$I_D = \frac{120 \mu\text{A}/\text{V}^2 \cdot \frac{10}{1}}{2} (1.2 - 0.8)^2$$

$$1.2 \mu\text{A} \cdot 0.4$$

$$g_m = 480 \frac{\mu\text{A}}{\text{V}}$$

$$600 \mu\text{A} \cdot 0.4 \cdot 0.4$$

$$96 \mu\text{A}$$

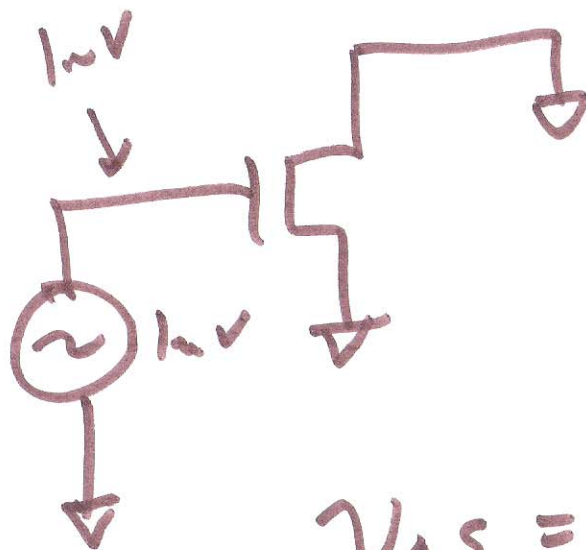

$$g_m v_{gs} = i_d$$


$$v_{gs} = 1\text{mV}$$

$$g_m = 480 \frac{\text{nA}}{\text{V}}$$

$$i_d = 480 \text{ nA}$$

8)



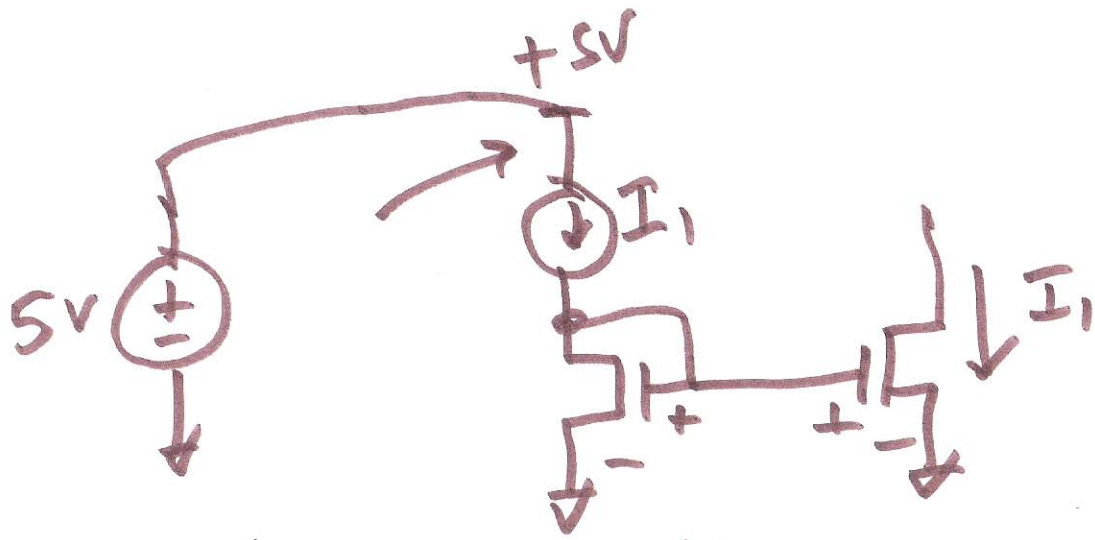

$$V_{GS} > V_{THN}$$

$$V_{DS} \geq V_{GS} - V_{THN}$$

$$V_D - \cancel{V_S} \geq V_G - \cancel{V_S} - V_{THN}$$

KEY POINT  
ALWAYS IN SAT.  
WHEN ON!

$$V_D \geq V_G - V_{THN}$$

$$0 \geq -V_{THN} \text{ ALWAYS TRUE}$$

