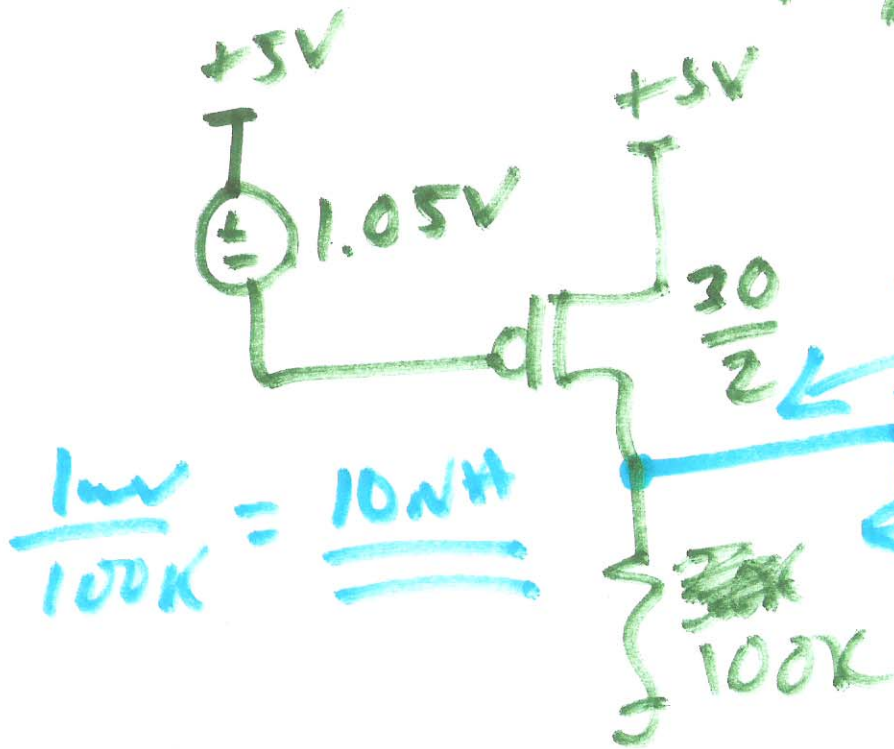


EE 420 / ECL 620

Electronics II

Analog IC Design

2/3/14 Lecture 4



$$\frac{1\mu V}{100K} = \underline{\underline{10nA}}$$

$$I_D = \frac{404}{2} \cdot \frac{30}{2} (1.05 - .9)^2$$


$$I_D = 6.754\mu A$$

$$1\mu V/g_m = 404 \cdot \frac{30}{2} (.15)$$

$$= 904\frac{\mu A}{V}$$

$$11.5T_{nF/g} = \frac{1}{6.754 \cdot 0.0125}$$

CMOSedu.com

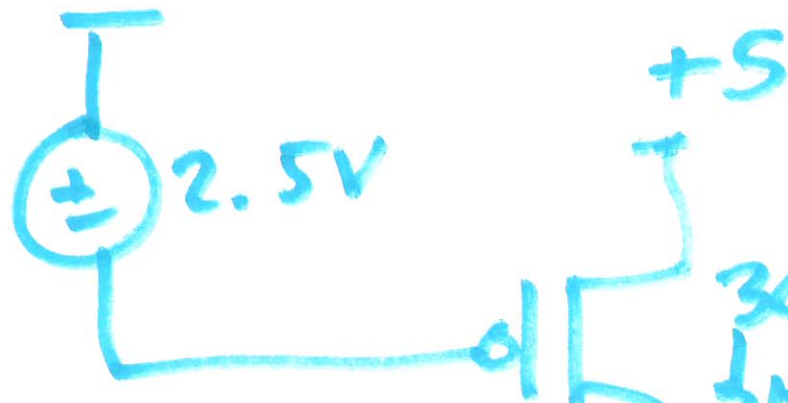

$$R_{OH} = \frac{1}{K_P \frac{W}{L} (2.5 - 0.9)}$$

$$= \frac{1}{40 \mu \text{A} \cdot 15 \cdot 1.6}$$

$$= \frac{1}{960 \mu \text{A}}$$

$$\approx 1 \text{K}$$

$$I_D = K_P \cdot \frac{W}{L} \left((V_{SG} - V_{TH}) V_{SD} \right)$$

$$= 40 \mu \text{A} \cdot 15 \cdot (2.5 - 0.9) V_{SD}$$

$$= \frac{5 - V_{SD}}{300 \text{K}}$$

$$289 V_{SD} = 5$$


$$V_{SD} = \frac{5}{289}$$

$$= \underline{\underline{17 \mu \text{V}}}$$

$$300 \text{K} \cdot 600 \mu \text{A} \cdot 1.6 \cdot V_{SD} = 5 - V_{SD}$$

$$\frac{180 \cdot 1.6}{288} V_{SD} = 5 - V_{SD}$$

Open-ckt gain

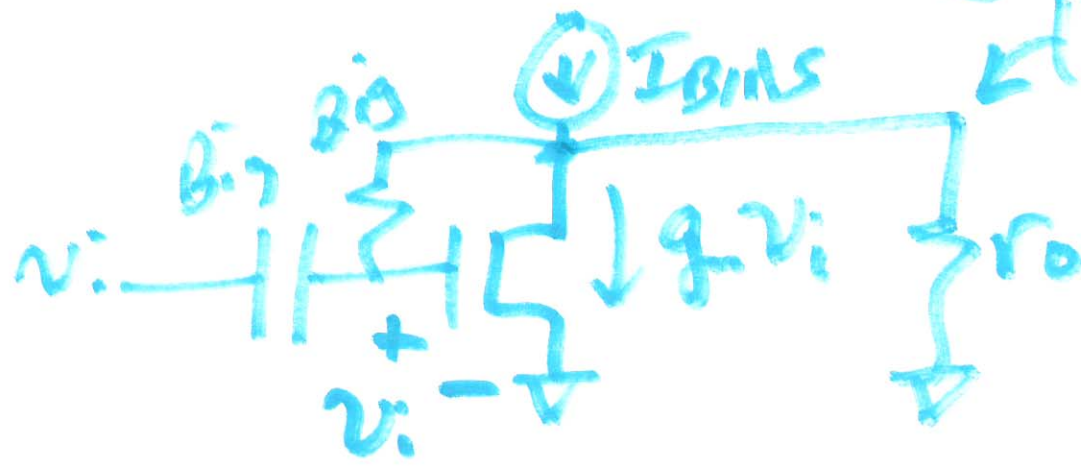

$$v_{out} = g_m v_i r_o$$

$$\left| \frac{v_{out}}{v_i} \right| = g_m r_o$$

open-ckt gain!

I_D

$$g_m r_o \approx \frac{\sqrt{2 I_D \cdot K_P \cdot \frac{W}{L}}}{\lambda I_D} \Rightarrow g_m r_o \propto \frac{1}{\sqrt{I_D}}$$



$\omega/2$

$$g_m r_o = \frac{K_P \cdot \frac{W}{L} (V_{GS} - V_{THN})}{\lambda \cdot \frac{K_P \cdot W}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2}$$

$\uparrow V_{DS, SAT}, V_{OVN} \quad I_D \uparrow \quad g_m r_o \downarrow$

3)

$f_T \rightarrow$ transition freq.

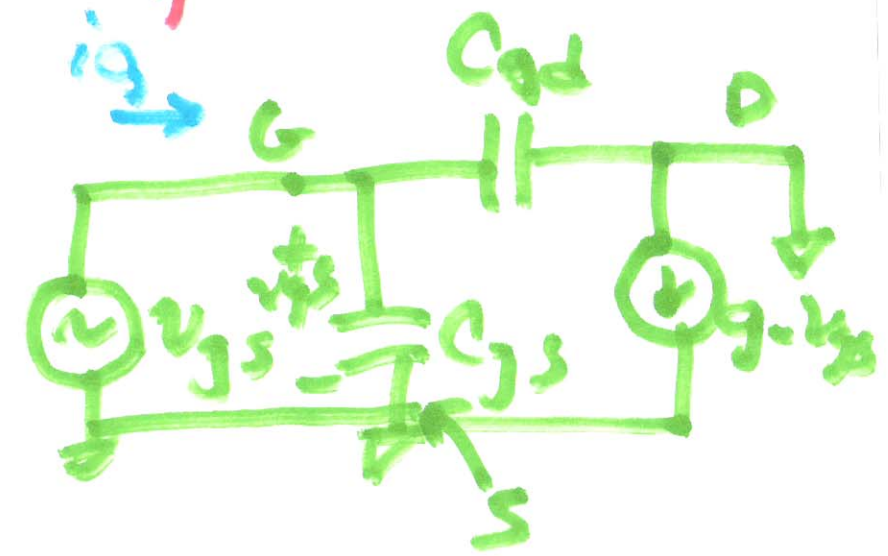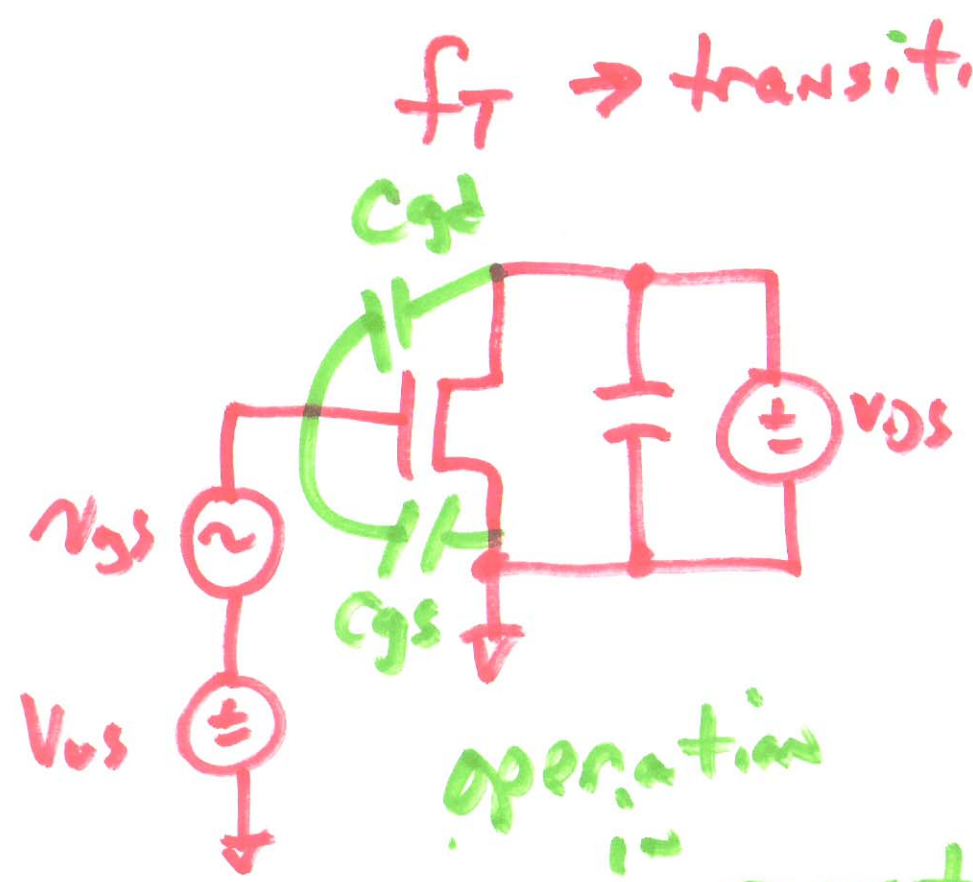

operation
in
saturation

$$i_d = g_m v_{gs}$$

$$v_{gs} = i_g \cdot \frac{1}{j\omega(C_{gd} + C_{gs})}$$

$$1 = \frac{|i_d|}{|i_g|} = \frac{g_m}{2\pi f(C_{gs} + C_{gd})}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$C_{gs} \gg C_{gd}$$

$$f_T \approx \frac{g_m}{2\pi C_{gs}}$$

$$= \frac{\mu_n \cdot \frac{\epsilon_{ox}}{t_{ox}} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})}{2\pi \cdot \frac{2}{3} \cdot \frac{\epsilon_{ox}}{t_{ox}} \cdot W \cdot L}$$

$$f_T \propto \frac{1}{L^2}$$

long channel

short $f_T \propto \frac{1}{L}$

5)

$$GFT = g_m r_o \cdot f_T$$

$$= \frac{\cancel{\mu_n} \cdot \cancel{K} \cdot \cancel{W}}{L} \cdot (V_{GS} - V_{TH}) \cdot \frac{\cancel{\mu_n} \cdot \cancel{K}}{L} \cdot (V_{GS} - V_{TH})$$

General design


set $V_{OVN} = V_{GS} - V_{TH}$
to 5% of V_{DD}

$2 \leq L \leq 5$
high-speed

$$GFT \propto \frac{4}{L^2}$$

$V_{OVN} \rightarrow 10\%$ of V_{DD} on wire
Min L !
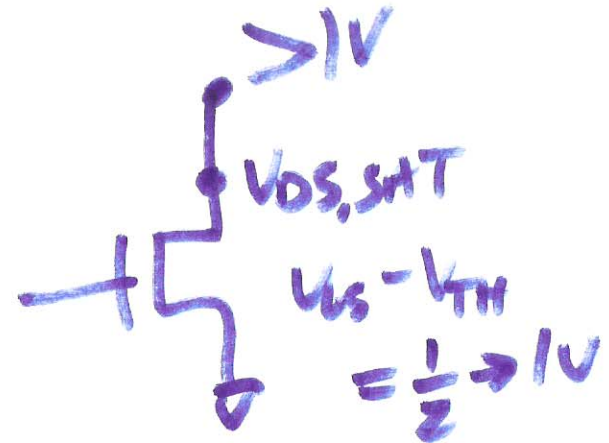
$$\frac{\lambda \cdot \cancel{\mu_n} \cdot \cancel{K}}{2} \cdot \frac{\cancel{W}}{L} \cdot (V_{GS} - V_{TH})^2 \cdot \frac{2}{3} \cdot C_{ox} \cdot W \cdot L$$



Thermal Voltage

$$V_T = \frac{kT}{q} \approx 26 \text{ mV} @ 300 \text{ K}$$


$T \uparrow$

$R \uparrow$

$$R = \frac{1}{q(4n \cdot n + 4p \cdot p)}$$

$T \uparrow$ $n, p \uparrow$

$T \uparrow$ $q \downarrow$

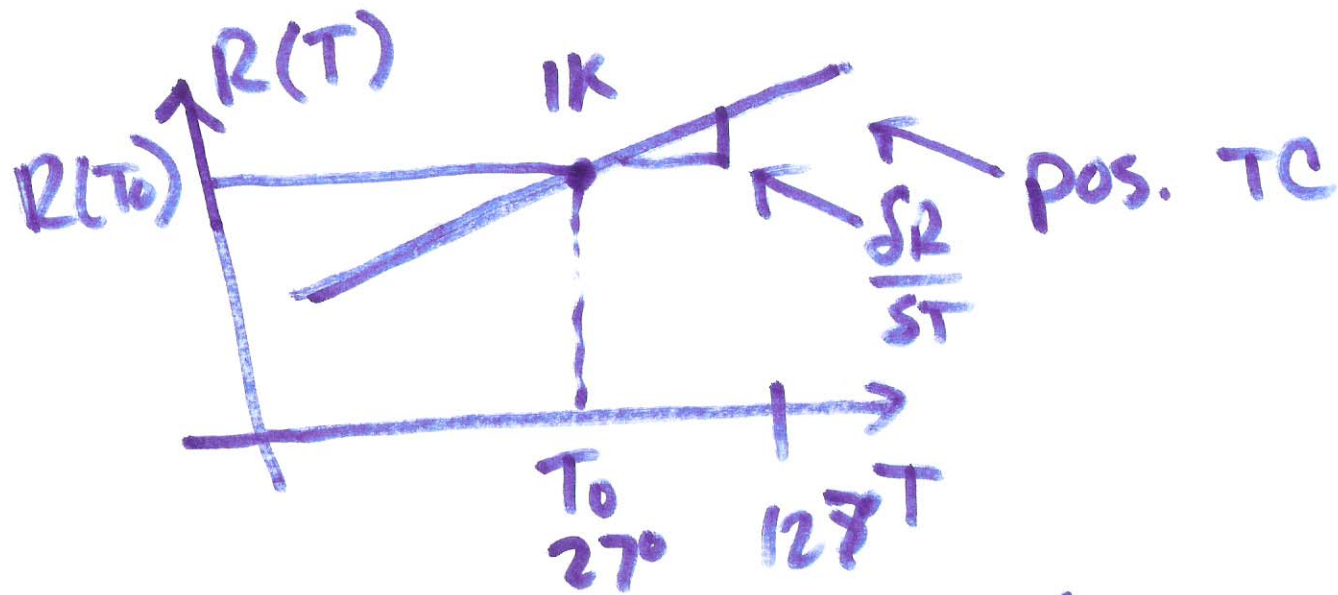

2,000 ppm/°C

$$TCR = 0.002$$

$$R(T) = R(T_0) \left(1 + TCR(T - T_0) \right)$$

$$= R(T_0) + \underbrace{R(T_0) \cdot TCR}_{\text{change in } R} (T - T_0)$$

$$1,000 + 0.002(127 - 27) \cdot 1,000 = \frac{\delta R}{\delta T}$$

$$\underline{\underline{1200 \Omega}}$$

$$TCR = \frac{1}{R} \frac{\delta R}{\delta T}$$

$$I_D = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$TC_{KP} = \frac{1}{KP} \frac{\delta KP}{\delta T} \quad \mu(T) = \mu(T_0) \left(\frac{T_0}{T} \right)^{1.5}$$

$$KP(T) = KP(T_0) \left(\frac{T_0}{T} \right)^{1.5}$$

$$\frac{-1.5}{T} = \frac{1}{KP} \frac{\delta KP(T)}{\delta T} = \frac{\delta}{\delta T} \left(\frac{T_0}{T} \right)^{1.5}$$

$$= \frac{\delta}{\delta T} \left(\frac{T}{T_0} \right)^{-1.5}$$

$$= -\frac{1.5}{T_0} \left(\frac{T}{T_0} \right)^{-2.5}$$