

Lecture 8, May 7

EE 420

EEG 620

Study past H.W., Quizzes, mid-term
project question.

open-book, closed notes

Ch. 9 IV plots

intuitive questions

MOSFET IV curves

body effect

derive g_m & r_o

KNOW Ex. 9.5
and pmos Flavor

trade-offs
device sizes

V_{OV} , f_T , g_m , w , L

G_{FT} , g_{ro}

Temp. effects

$$\frac{S_{KP}}{dT}, \quad \frac{\delta V_{TH}}{dT}$$

V_{TH}
 V_T
B.G.

diode voltage
drop $v_{D1} \downarrow T \uparrow$

Ch. 20

CURRENT MIRROR TOPOLOGIES

DC biasing

Wide swing CURRENT MIRRORS

MATCHING

Calculations Using Square-law
Equations

BMR - operation
stability


TEMP.

CASCODING


KNOW

how to derive output!
RESISTANCE IN FIG.
20.42

$$r_{op} = r_{on} = r_o$$

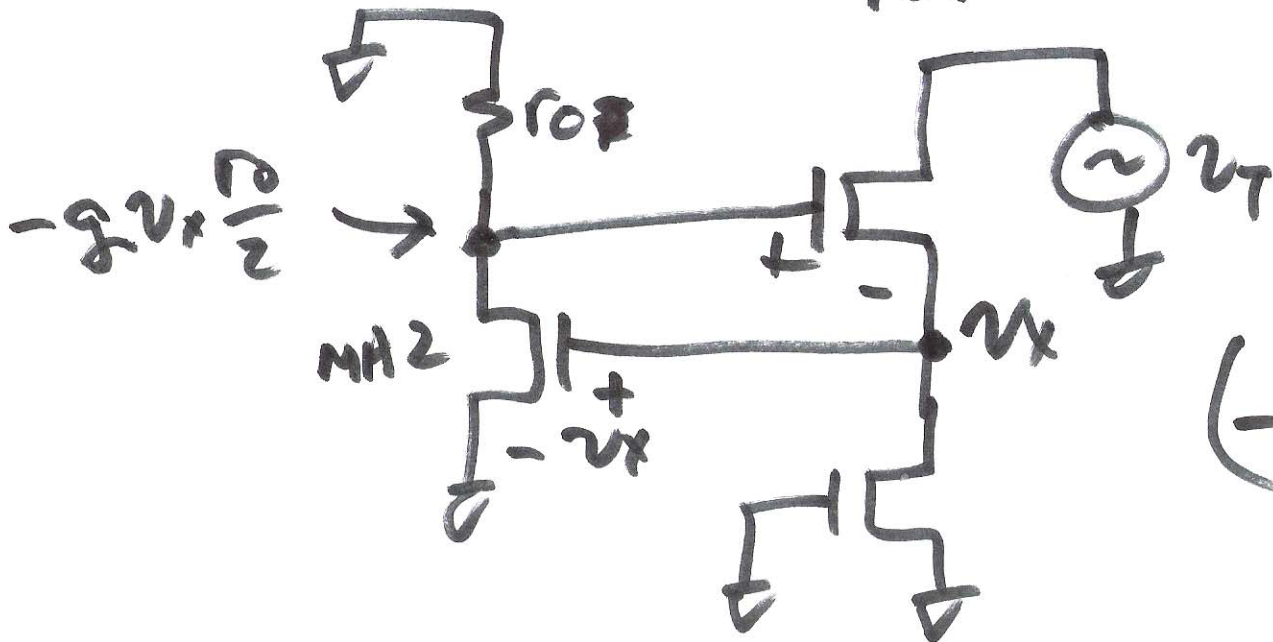
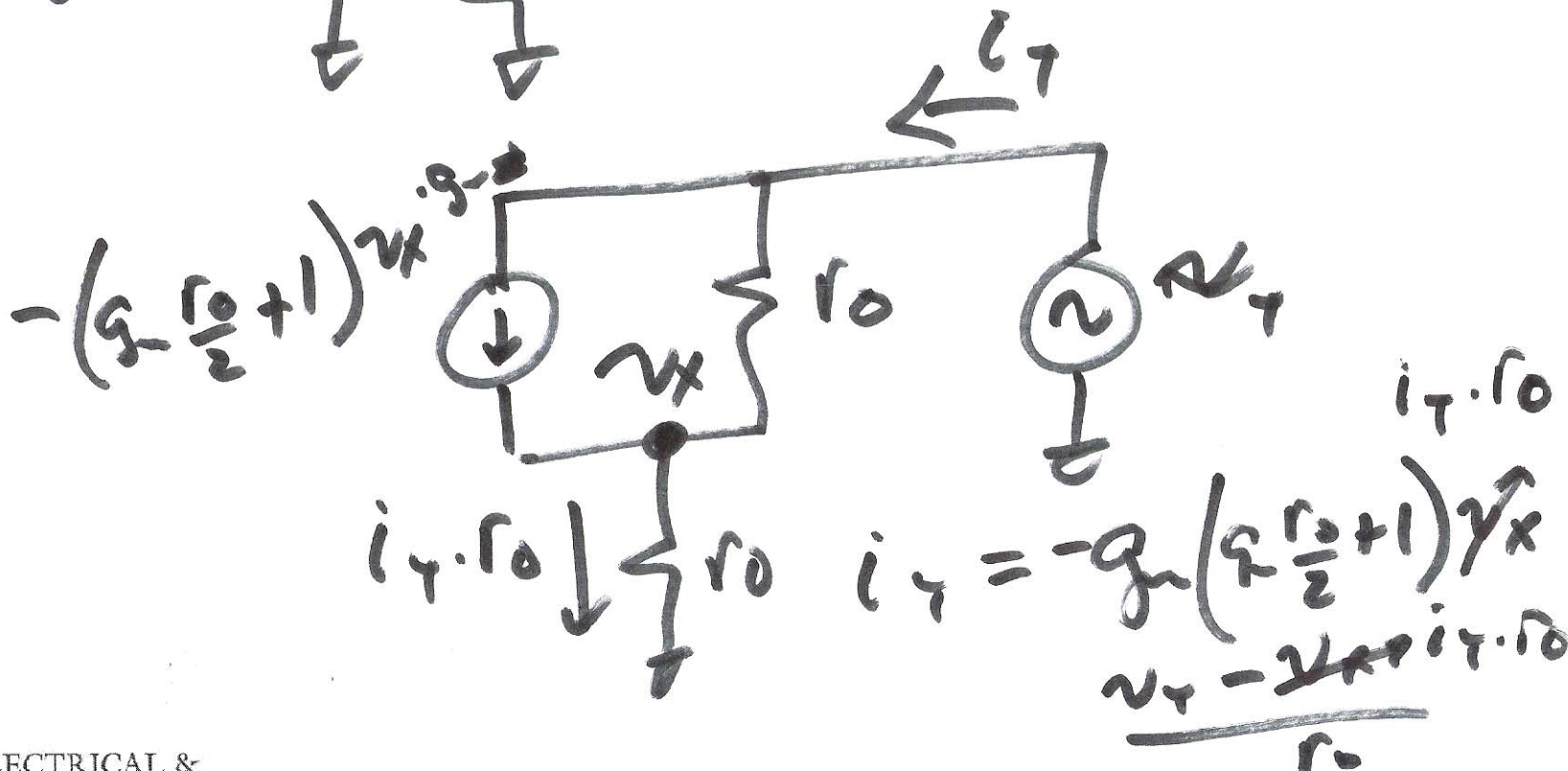
$$\left(-g_m v_x \frac{r_o}{2} - v_T\right)$$



$$i_T = -g_m \left(g_m \frac{r_o}{2} + 1\right) v_x$$

$$v_T = \frac{-v_x + i_T \cdot r_o}{r_o}$$

4)

$$i_T = -g r_o \left(g \frac{r_o}{2} + 1 \right) v_T +$$

$$\frac{v_T}{r_o} - i_T \frac{r_o}{r_o}$$

$$i_T \left(1 + g r_o \left(g \frac{r_o}{2} + 1 \right) + 1 \right) = \frac{v_T}{r_o}$$


$$\begin{aligned} \frac{v_T}{r_T} &= r_o + g r_o^2 \left(g \frac{r_o}{2} + 1 \right) + r_o \\ &\approx g^2 \frac{r_o^3}{2} \end{aligned}$$

Ch. 21

freq. resp

gains

millers theorem

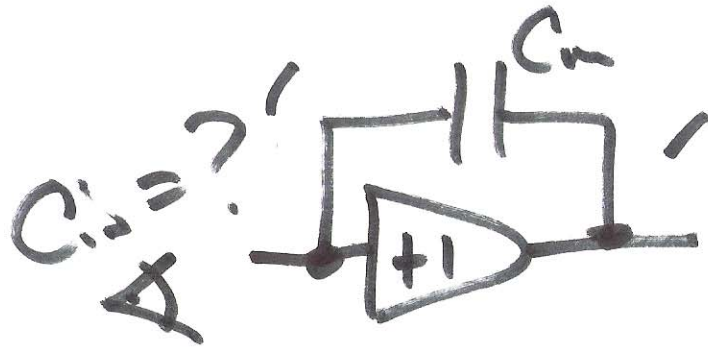


$$i_{in} = \frac{v_{in} - v_{out}}{1/j\omega C_m}$$


$$v_{in} = v_{out} \quad i_{in} = 0$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = \infty$$

6)

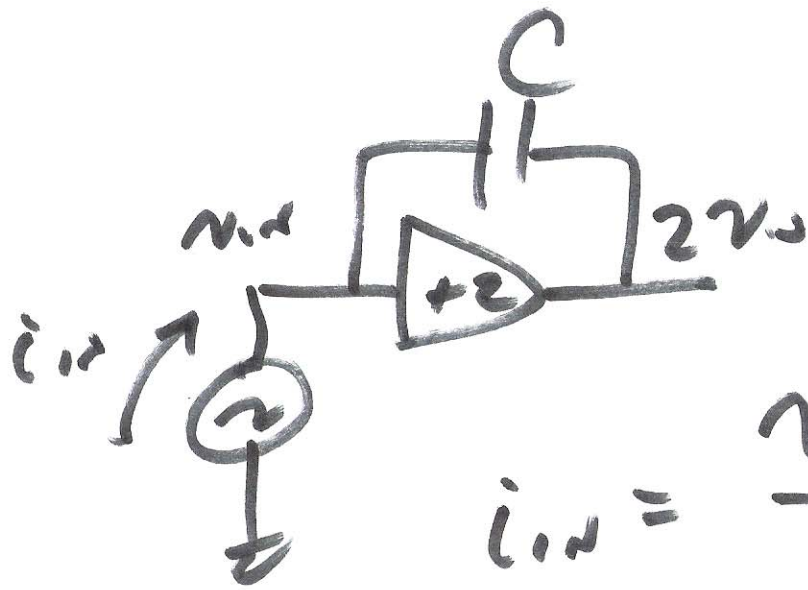
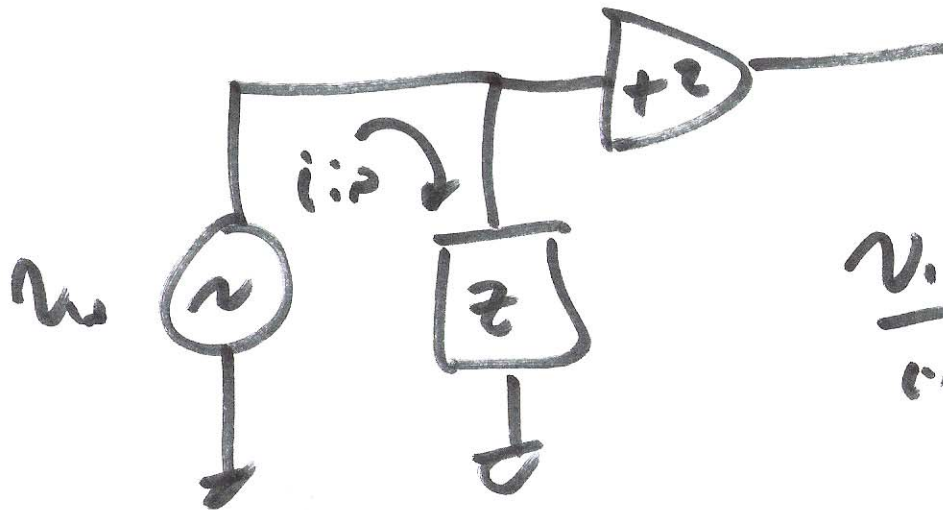
$$i_{in} = \frac{v_{in} - 2v_{in}}{1/j\omega C}$$



$$\frac{v_{in}}{i_{in}} = \frac{1}{j\omega C} \cdot \frac{j}{1} = j \cdot \frac{1}{\omega C}$$

Let $L = \frac{1}{\omega C}$

$$\frac{v_{in}}{i_{in}} = j \cdot \omega \cdot L$$

7)

Ch. 21

gains

C.S.

C.G.

C.D. (S.F.)


output resistance

21.2

$$-g_m \cdot v_{gs} = i_T$$

$$i_T = g_m \cdot v_T$$
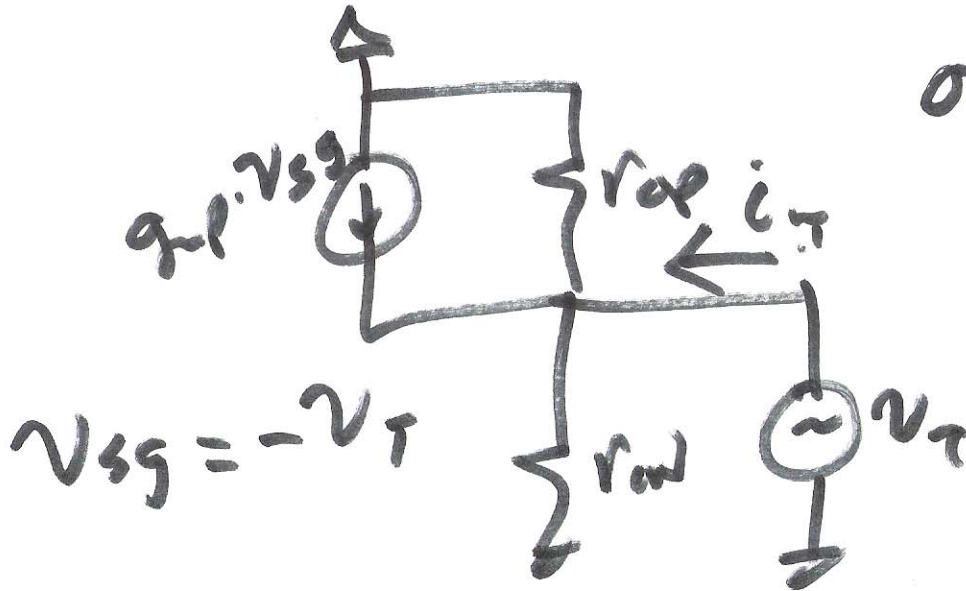
$$\frac{v_T}{i_T} = \frac{1}{g_m} \parallel r_{out}$$



frequency response

Ch. 22

diff amps

CMR
gain etc

Study quiz & H.W
Ch. 23 & 24

Indirect compensation
OTAS

