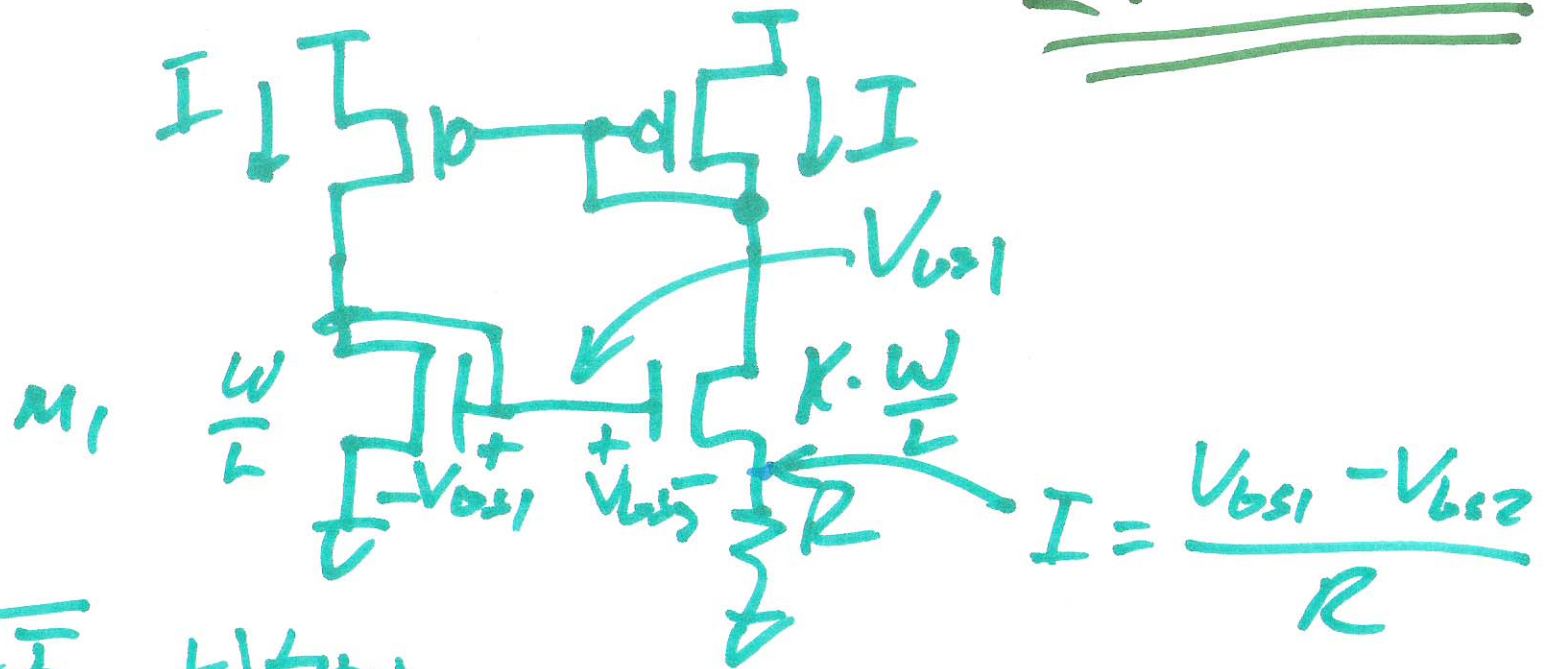


EE 420 / ECG 620

Analog IC Design

$I = \frac{\beta}{2} (V_{GS} - V_{thn})^2$  Feb. 18, 2015

Lecture 10



$$V_{GS1} = \sqrt{\frac{2I}{\beta}} + V_{thn}$$

$$V_{GS2} = \sqrt{\frac{2I}{K \cdot \beta}} + V_{thn}$$


$$I = \sqrt{\frac{2I}{\beta}} \left(1 - \frac{1}{\sqrt{k}}\right) \cdot \frac{1}{R}$$



$$I = \frac{2}{R^2 \beta} \left(1 - \frac{1}{\sqrt{k}}\right)^2$$

$$k = 4$$



$$I = \frac{1}{2R^2 \beta}$$
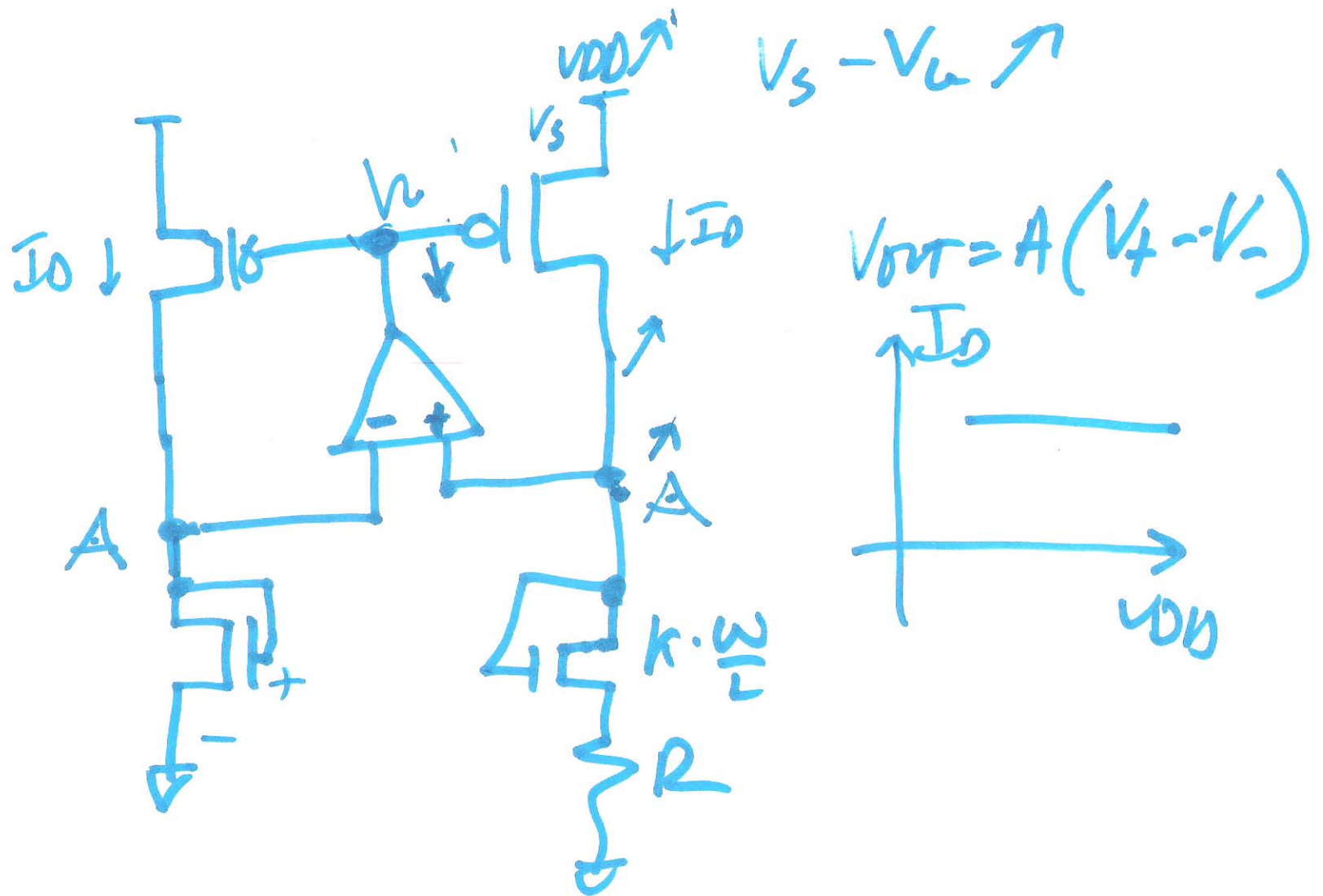
$$\begin{aligned} \frac{1}{R} &= \sqrt{2I \cdot K P \cdot \frac{\omega}{L}} \\ &= g_m = K \cdot \frac{\omega}{L} (V_{GS} - V_{TH}) \\ &= \beta V_{OV} \end{aligned}$$



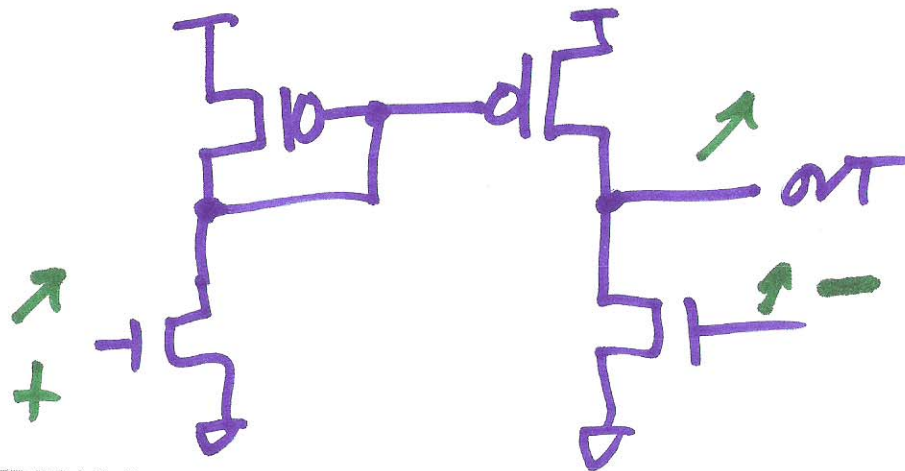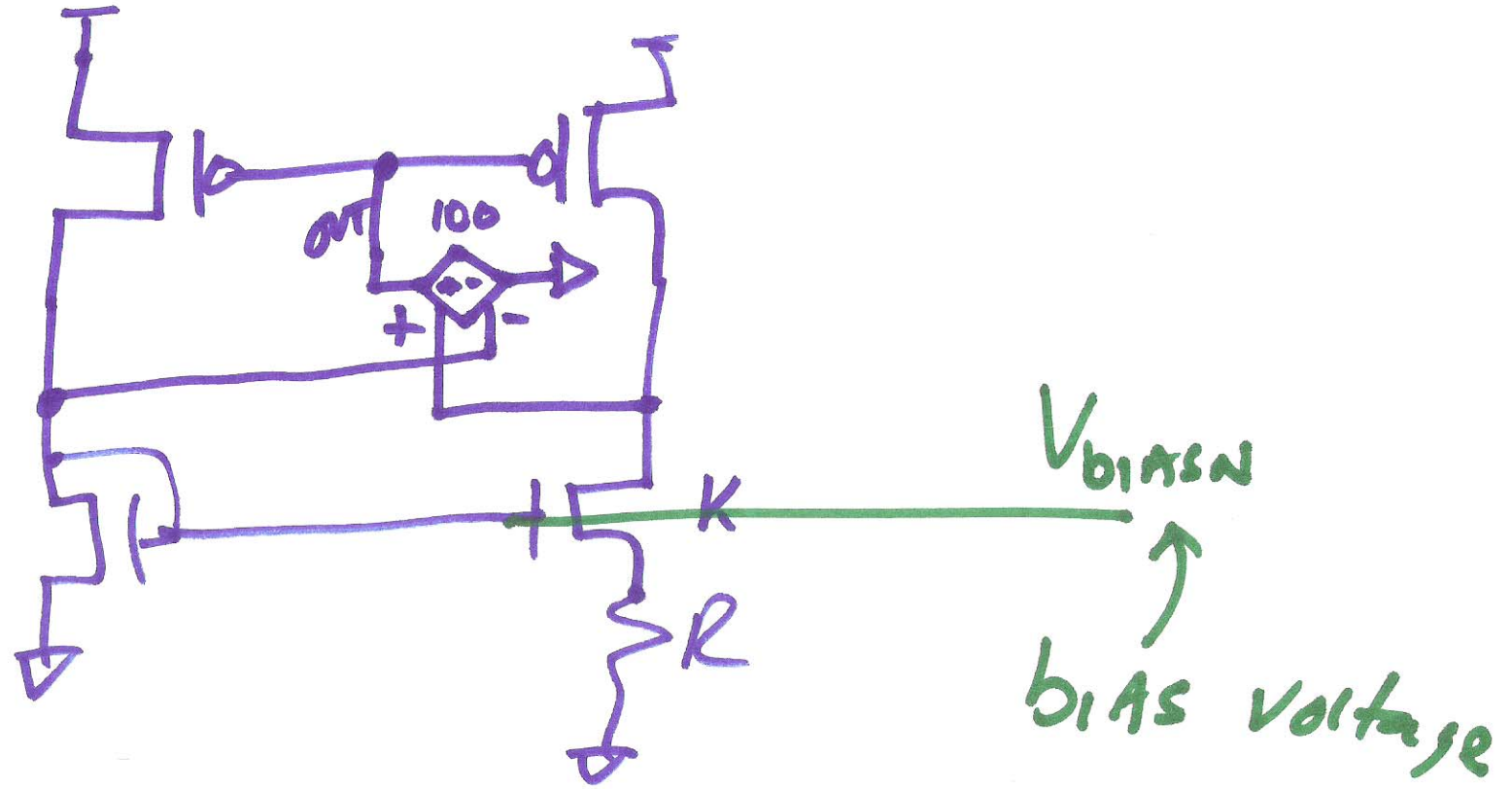

4)

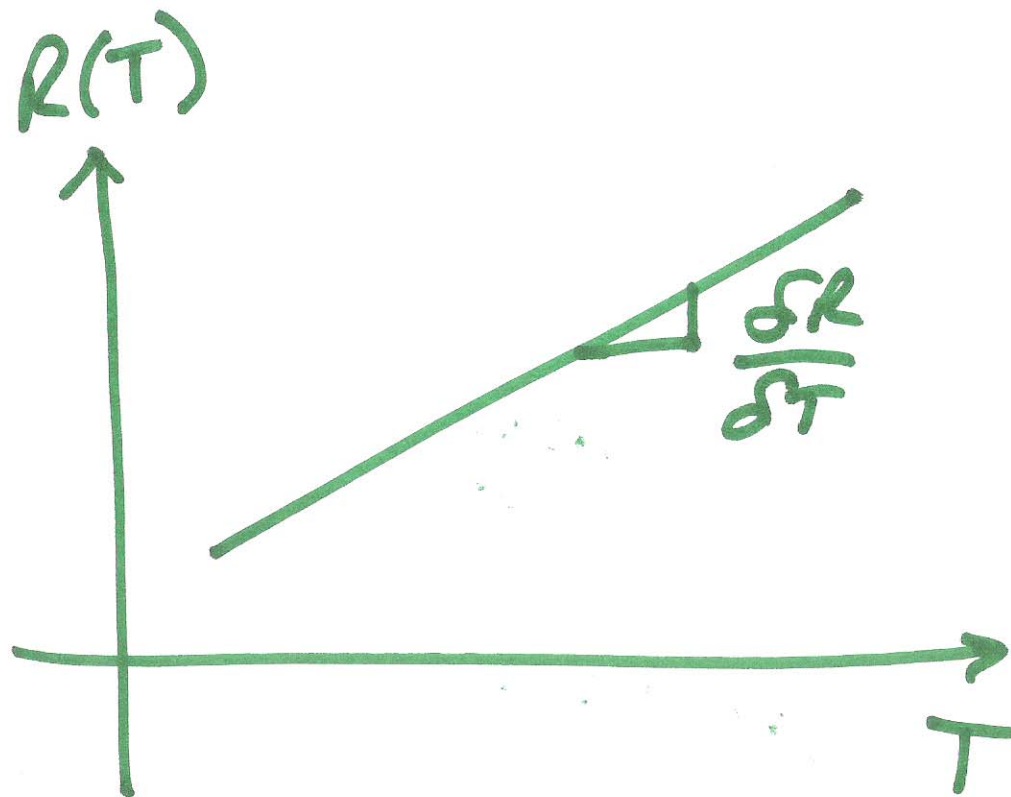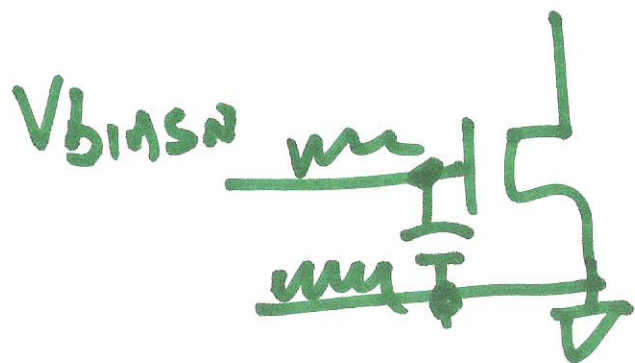

$$R(T) = R(T_0)(1 + TCR \cdot (T - T_0))$$

$$\frac{\delta R}{\delta T} = R(T_0) \cdot TCR$$

$$0.002 = TCR = \frac{1}{R(T_0)} \frac{\delta R}{\delta T} = 2,000 \frac{\text{ppm}}{^\circ\text{C}}$$

5)



$$I_{REF} = \frac{V_{DD} - V_{GS}}{R} = (V_{DD} - V_{GS}) R^{-1}$$

$$\frac{\delta I_{REF}}{\delta T} = R^{-1} \left( \frac{-\delta V_{GS}}{\delta T} \right) + (V_{DD} - V_{GS}) (-1) R^{-2} \frac{\delta R}{\delta T}$$

$$TCR = \frac{1}{R} \frac{\delta R}{\delta T} = 0.002$$

$$= -I_{REF} \cdot \left( \frac{1}{R} \frac{\delta R}{\delta T} \right) - \frac{1}{R} \frac{\delta V_{GS}}{\delta T}$$

$$I_{REF}(T) = I_{REF}(T_0) (1 + TC I_{REF} (T - T_0))$$

$$TC I_{REF} = \frac{1}{I_{REF}} \cdot \frac{\delta I_{REF}}{\delta T}$$

