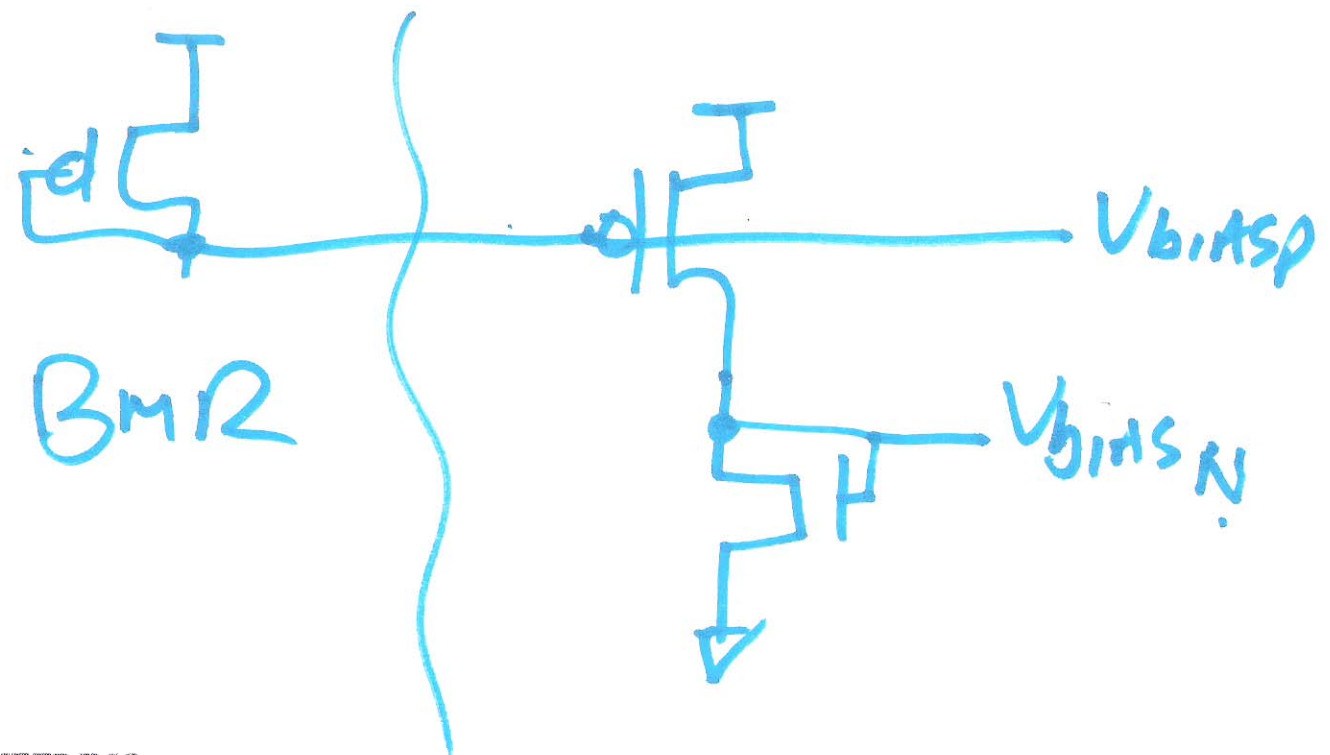



EE 420 / ECE 620

Analog IC Design

Lecture 11

Feb. 23, 2015



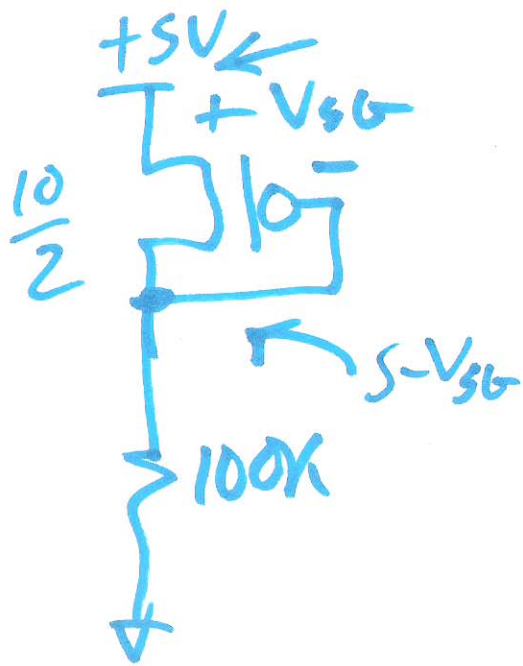

$$V_{sg} = \sqrt{\frac{2I}{K_p \cdot \frac{W}{L}}} + V_{THP}$$

$$\frac{5 - V_{sg}}{100k} = I$$

$$V_{sg} = 5 - 35.1 \cdot 10^{-6} \cdot 10^5$$

$$5 - I \cdot 10^5 = V_{sg} = \underline{\underline{1.49}}$$

4.1


$$5 - I \cdot 10^5 = \sqrt{\frac{2I}{40 \cdot 5}} \quad \text{~~7.9~~}$$

$$\sqrt{I} = \frac{-100 \pm \sqrt{10^4 + 4 \cdot 10^5 \cdot 4.1}}{2 \cdot 10^5} \quad \text{let}$$

$$= \underline{\underline{35.14 \mu A}}$$


$$\sqrt{I} = X$$

$$0 = X^2 \cdot 10^5 + 100X - 4.1$$

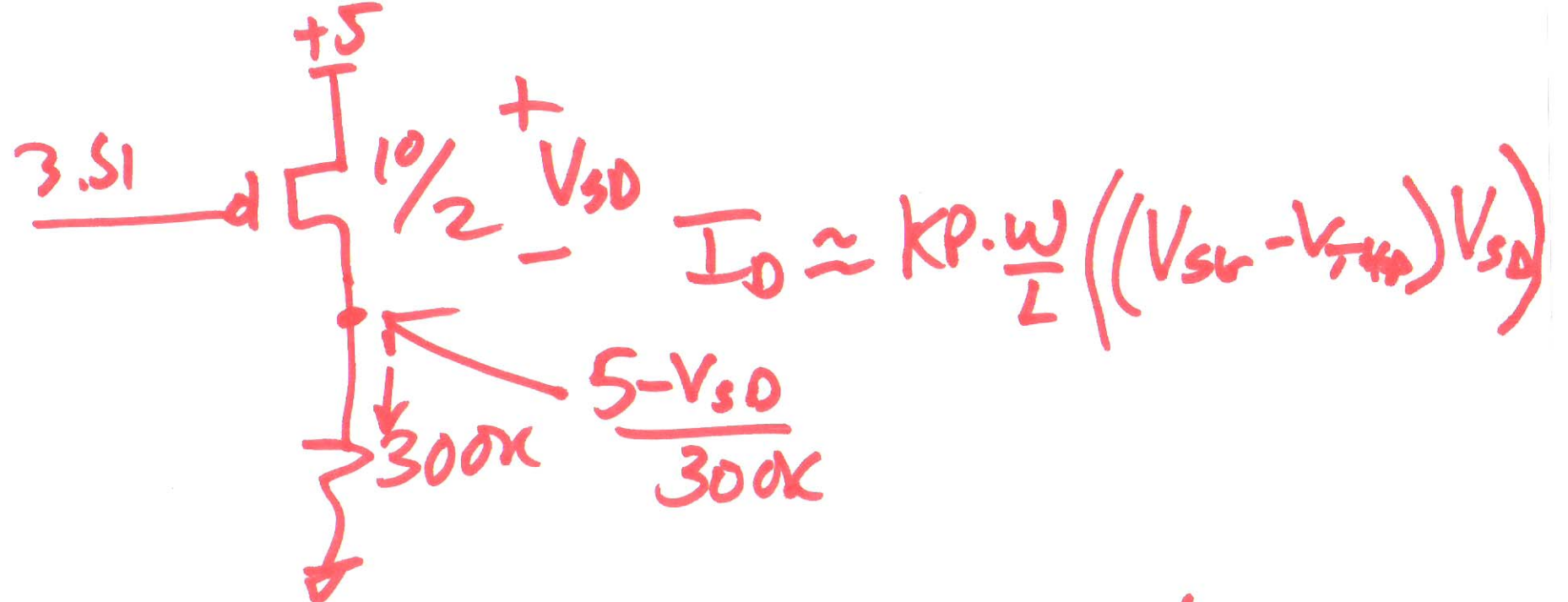

$$\frac{5 - V_{SD}}{300K} = 404.5 (1.49 - .9) V_{SD}$$


$V_{DS, SAT}, V_{OV}, V_{DS} - V_{THP}$

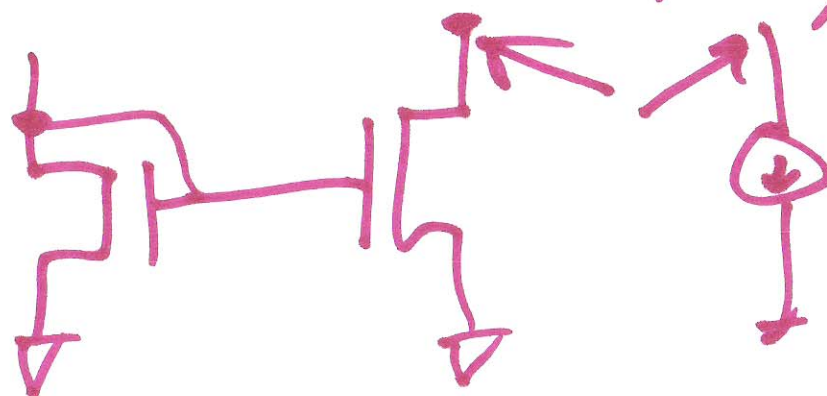

CASCODE $\rightarrow$ Miller killer $\rightarrow$ C.S.

CASCADE COMMON-CATHODE
driving

Common-grid $\rightarrow$ C.G.

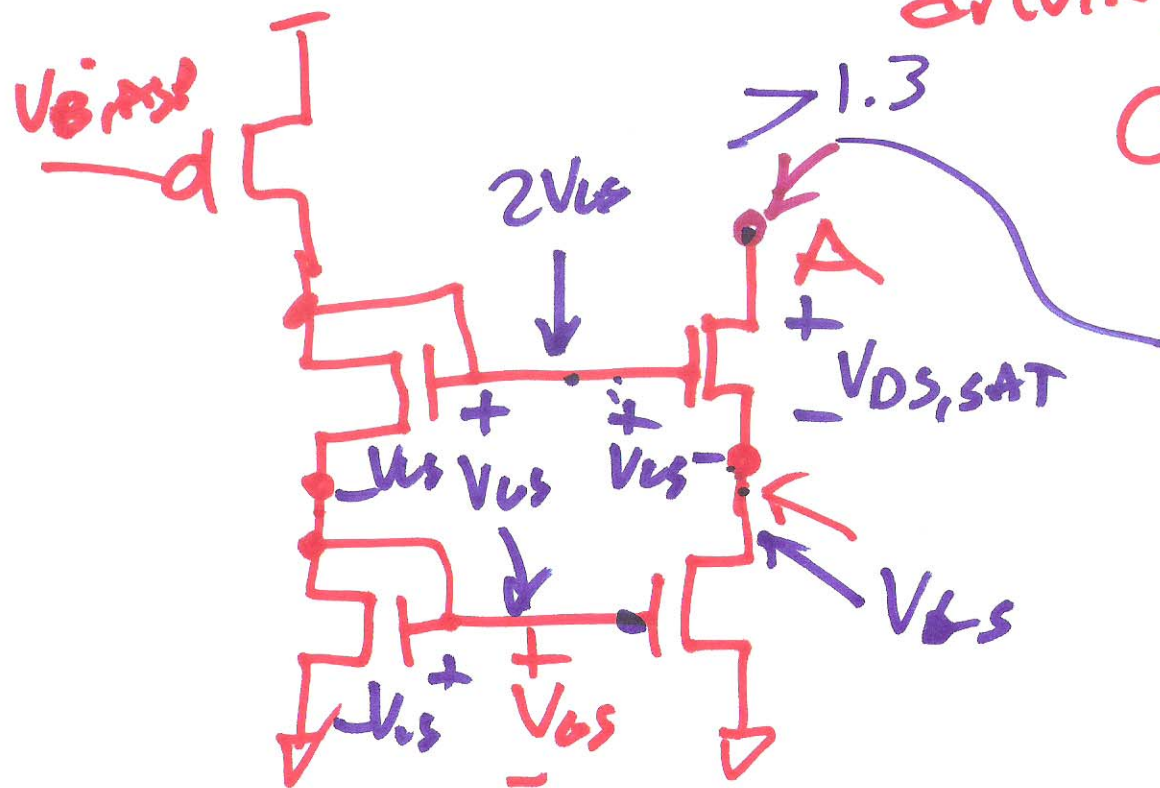

$$V_{DS,SAT} + V_{GS}$$

TABLE 9.1


$$V_{GS} = 1.05$$

$$V_{THN} = .8$$

$$V_{DS,SAT} = .25$$

CASCODE

CURRENT
MIRROR

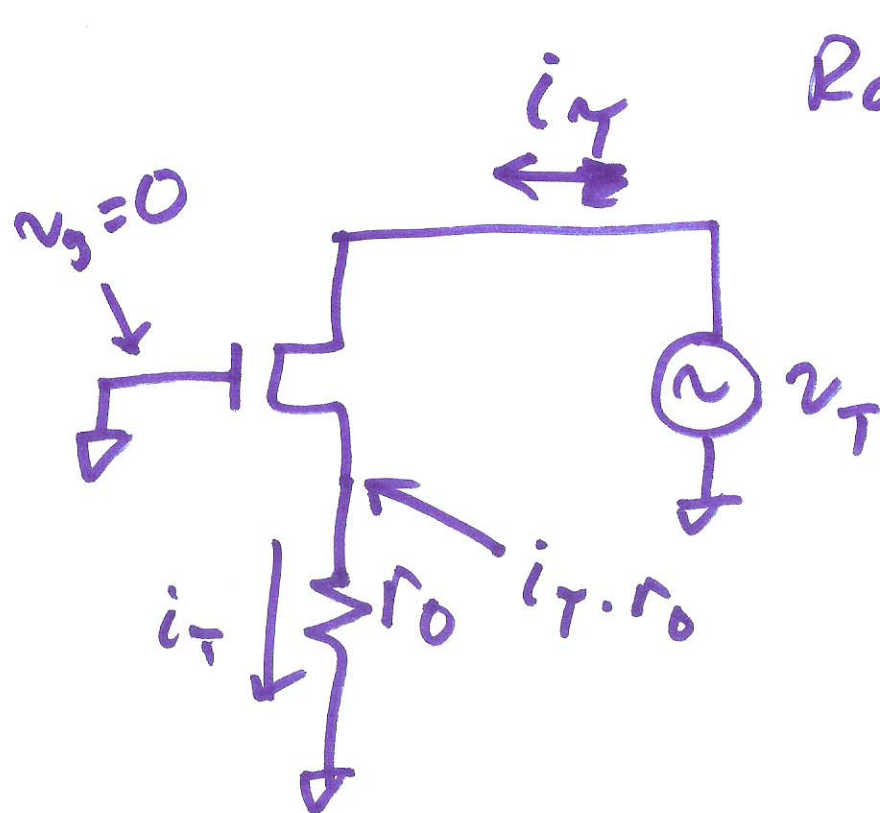


$$R_{oCHS} = \frac{v_T}{i_T}$$

$$v_{gs} = -i_T r_o$$

$$i_T = g_m(-i_T r_o) + \frac{v_T - (i_T r_o)}{r_o}$$
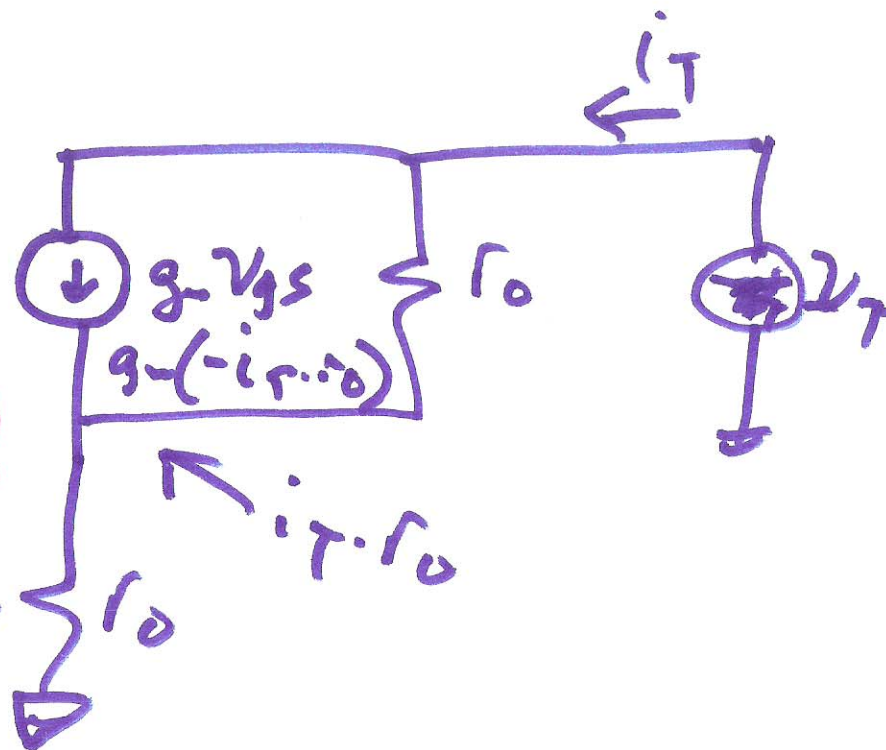
$$i_T r_o = -g_m i_T r_o^2 + v_T - i_T r_o$$



$$i_T (r_0 + g_m r_0^2 + r_0) = v_T$$

$$R_{ocms} = \frac{v_T}{i_T} = r_0 (1 + g_m r_0) + r_0$$

$$\approx g_m r_0^2$$


TABLE 9.1

$$g_m = 1 \text{ mA/V}$$

$$r_0 = 5 \text{ M}\Omega$$

$$R_{ocms} \approx 3.75 \text{ G}\Omega$$

6)

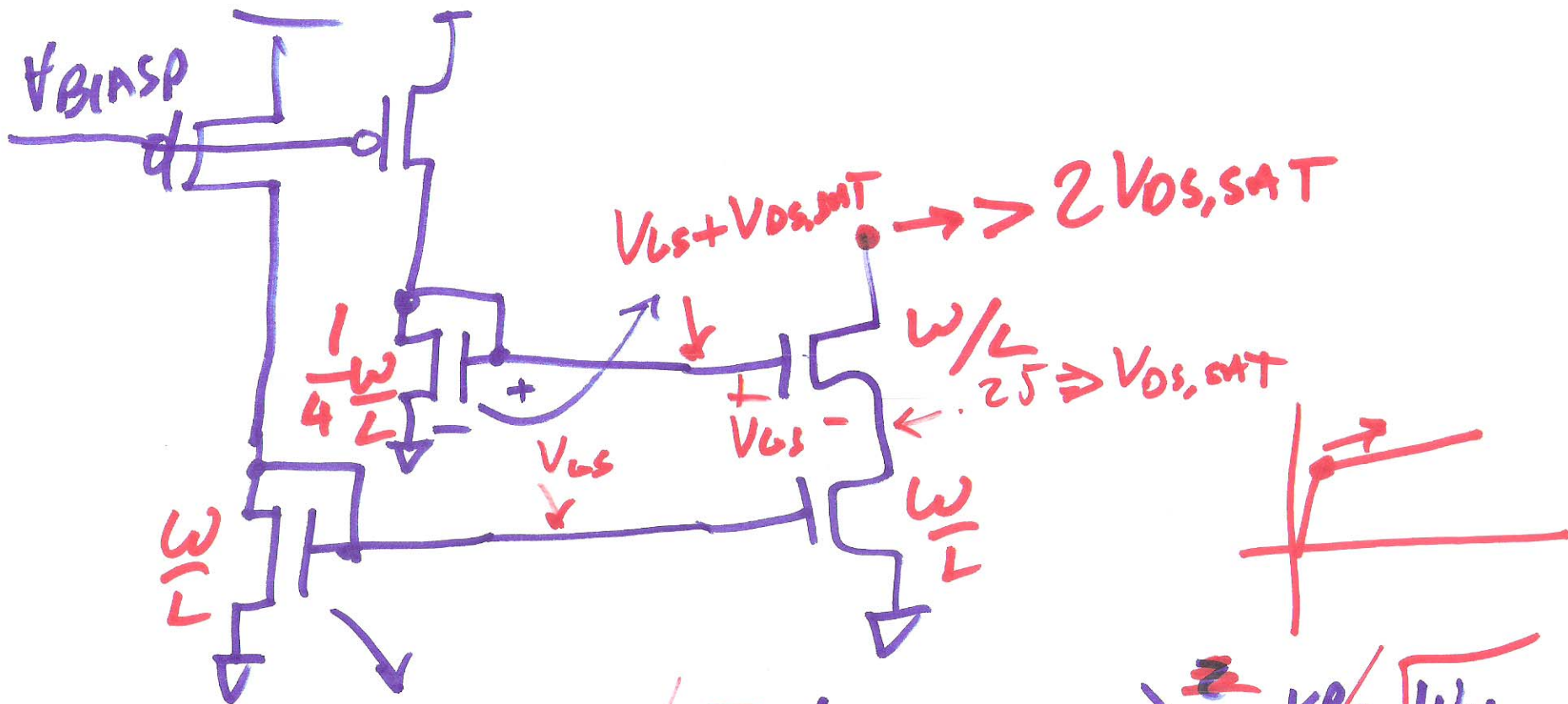

$$I_0 = \frac{K_{PN}}{2} \cdot \frac{W}{L} \cdot (V_{gs} - V_{THN})^2 = \frac{K_{PN}}{2} \cdot \frac{W}{L}$$

$$2(V_{gs} - V_{THN}) \leftarrow (V_{gs} + V_{ds,sat} - V_{THN})$$

$V_{gs} - V_{THN}$

$$\sqrt{w} (\cancel{V_{DS}} - V_{TH}) = \sqrt{w_n} \cdot 2 \cdot (\cancel{V_{DS}} - V_{TH})$$

$$\sqrt{w} = \sqrt{k \cdot w} \cdot 2$$

$$k = \frac{1}{4}$$