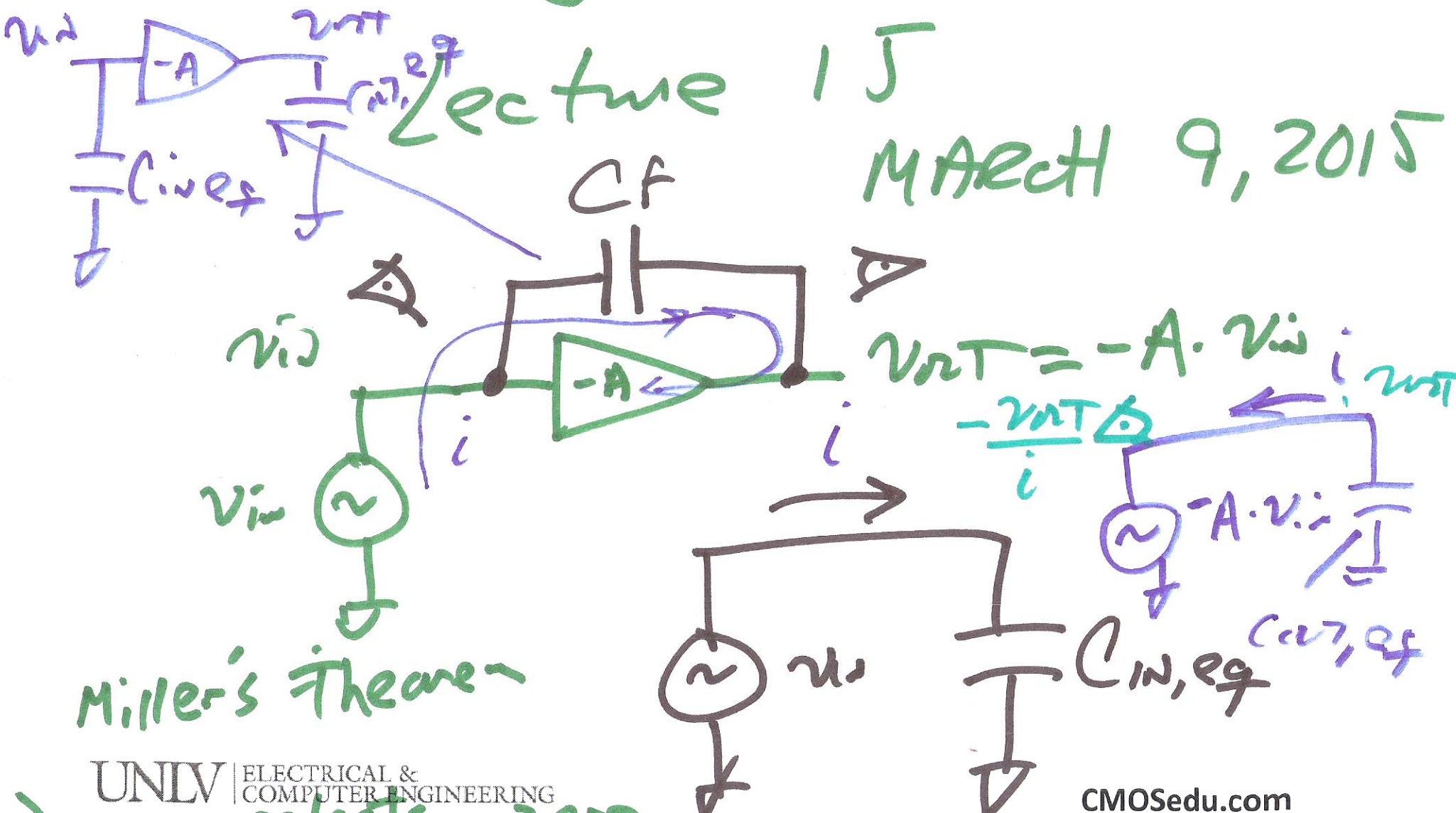


EE 420 / ECG 620

Analog IC Design

Lecture 15

MARCH 9, 2015




Miller's Theorem

neglects zero

$$i = C \frac{dv}{dt}$$


$$\frac{v_i}{i}$$

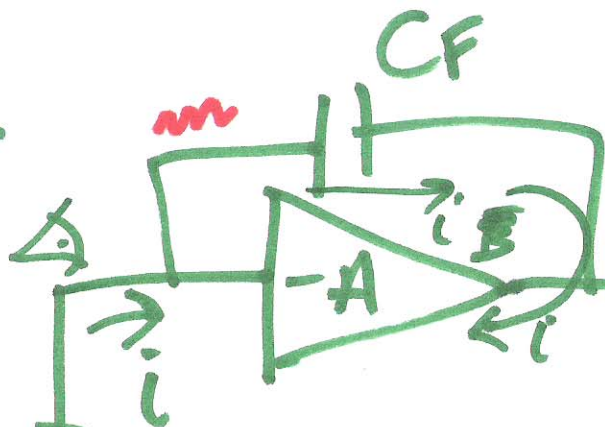

$$v_{out} = -A v_i$$



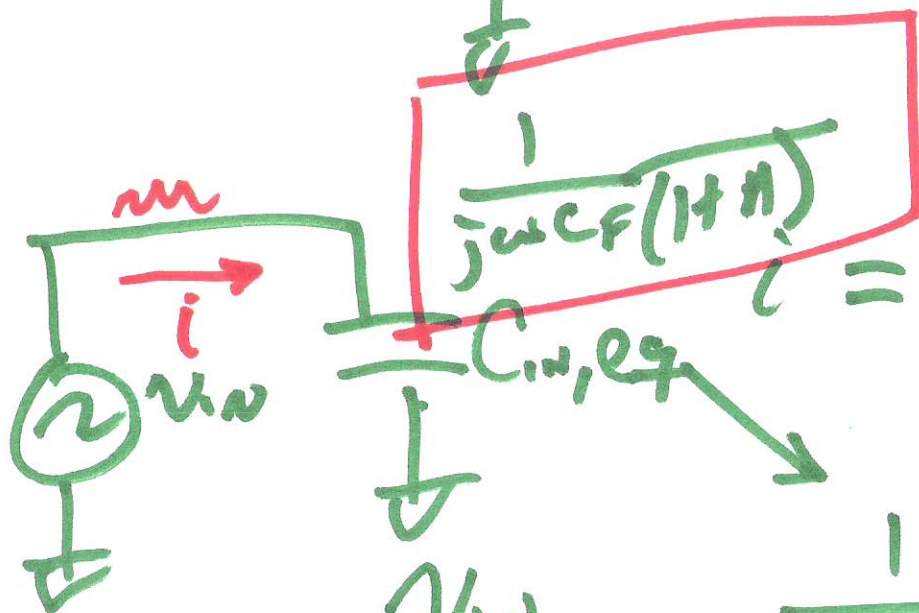
$$i = \frac{v_i - v_{out}}{1/j\omega C_F}$$



$$i = \frac{v_i (1 + |A|)}{1/j\omega C_F}$$


$$\frac{v_i}{i} = \frac{1}{j\omega C_F (1 + |A|)} = C_{in,eq}$$


$$V_{in} = \frac{V_{out}}{-A}$$

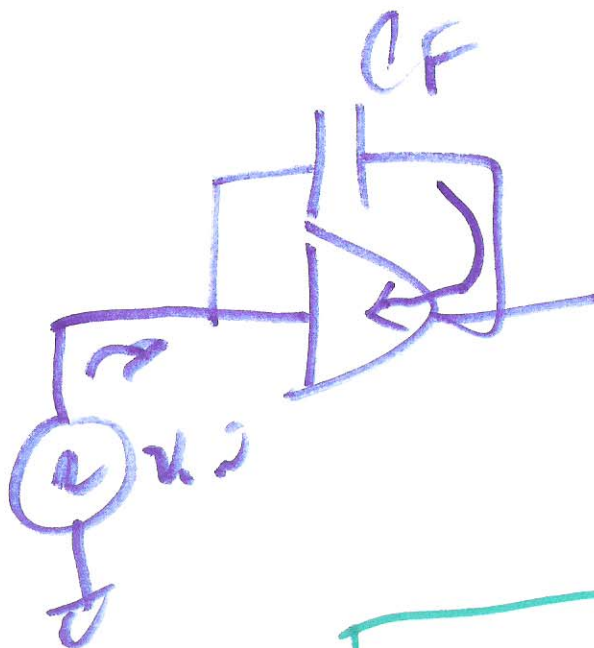



$$i = -V_{out} \left(1 + \frac{1}{|A|} \right)$$

$$\frac{V_{out}}{-i} = \frac{1}{j\omega C_F \left(1 + \frac{1}{|A|} \right)} = C_{out,ef}$$

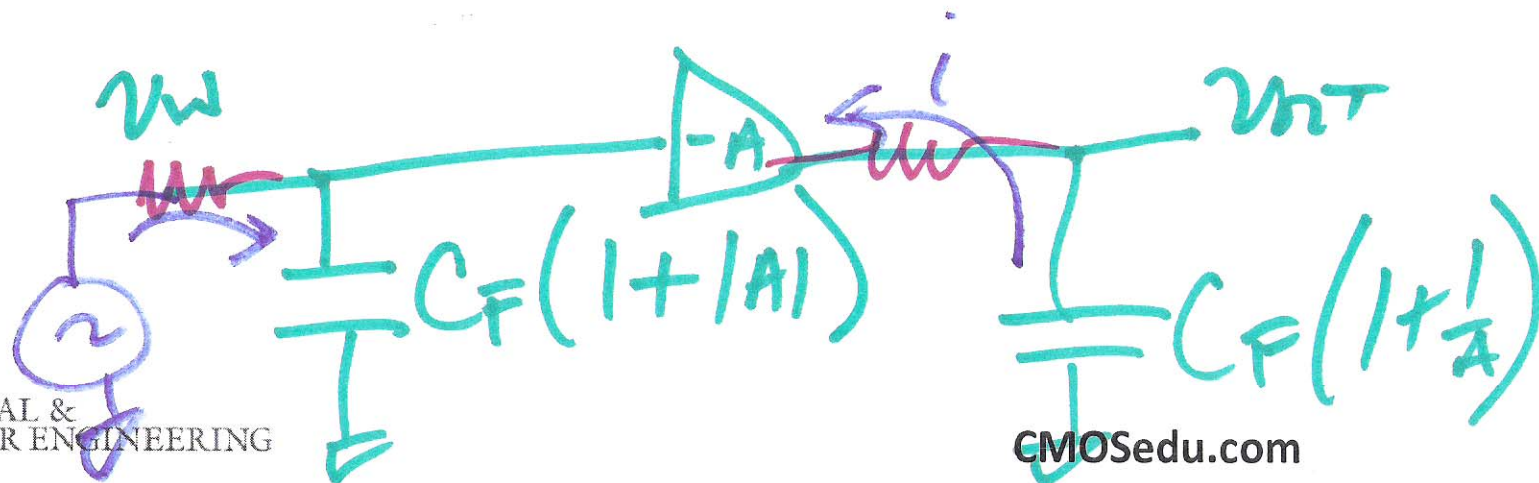

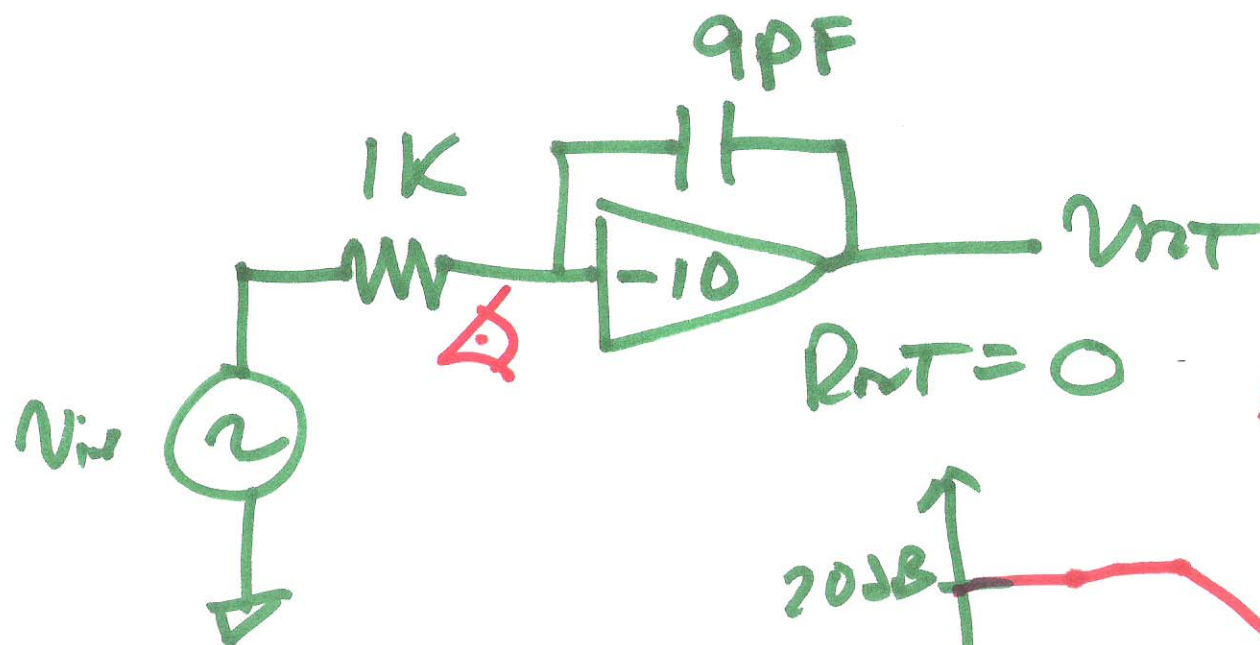
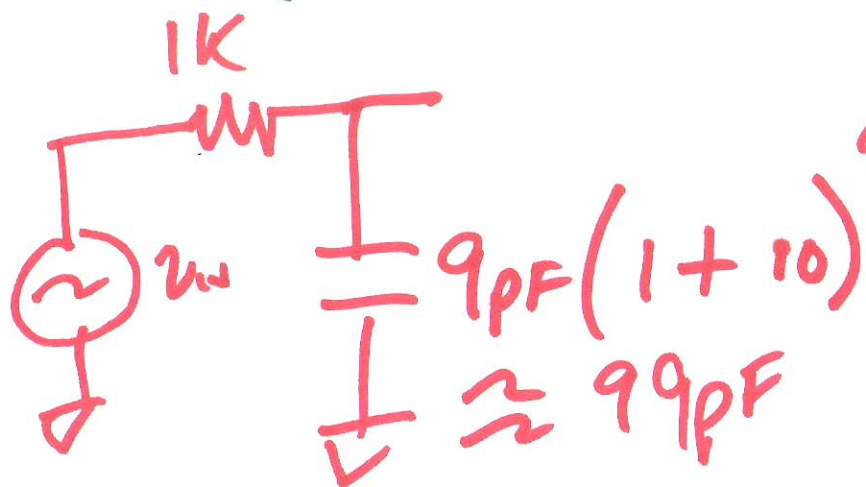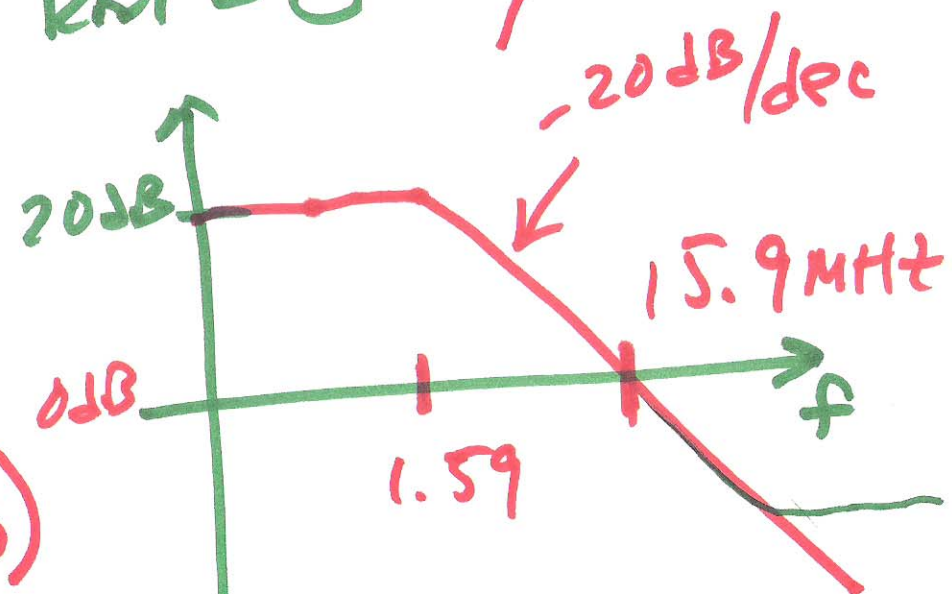
$$\frac{V_{out}}{V_{in}} = \frac{-10}{1 + j \frac{f}{1.59 \text{ MHz}}}$$




$$\approx 99pF$$



$$f_{3dB} = \frac{1}{2\pi \cdot 1K \cdot 99pF} = 1.59 \text{ MHz}$$

Phase markers on the plot: 180° at 1.59 MHz and 235° at 15.9 MHz.

4)

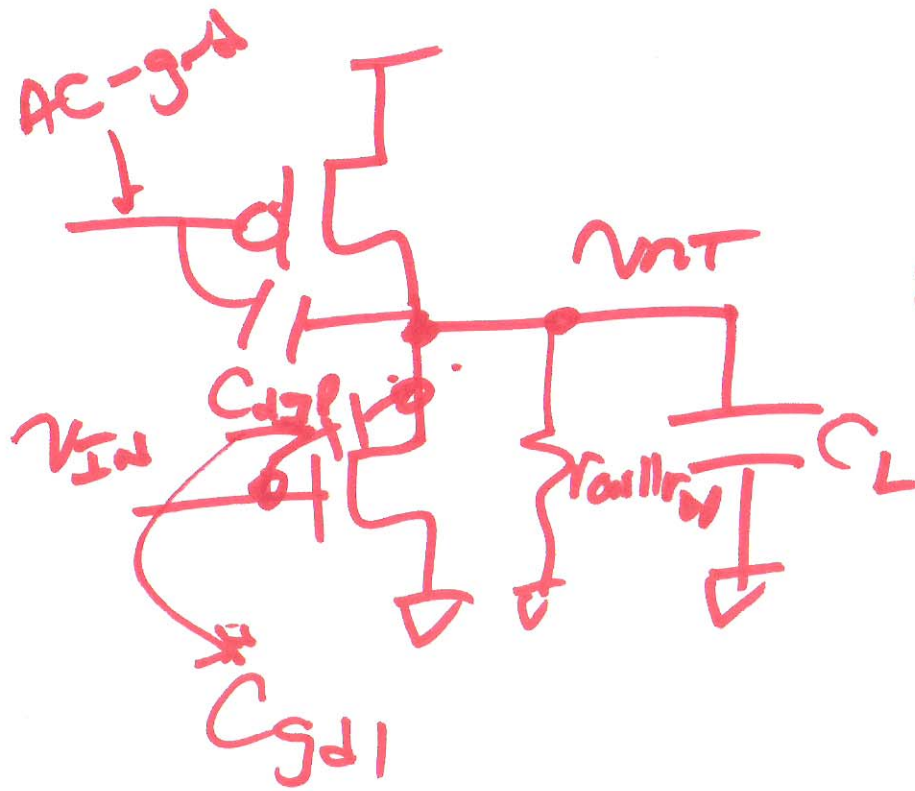

$\Rightarrow$

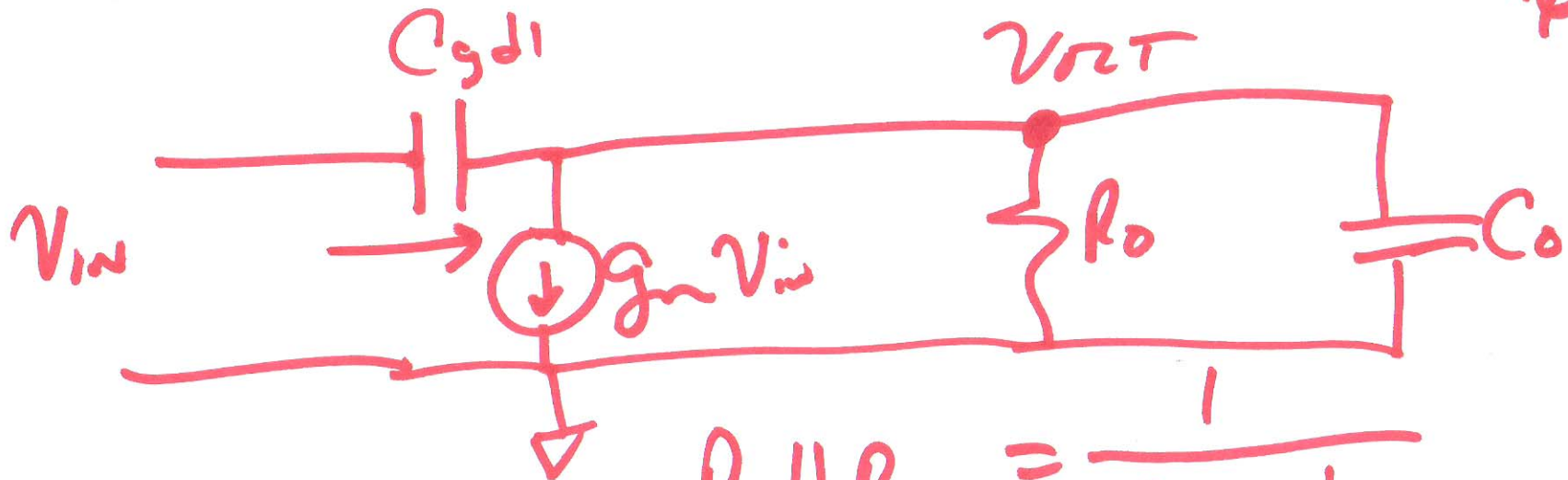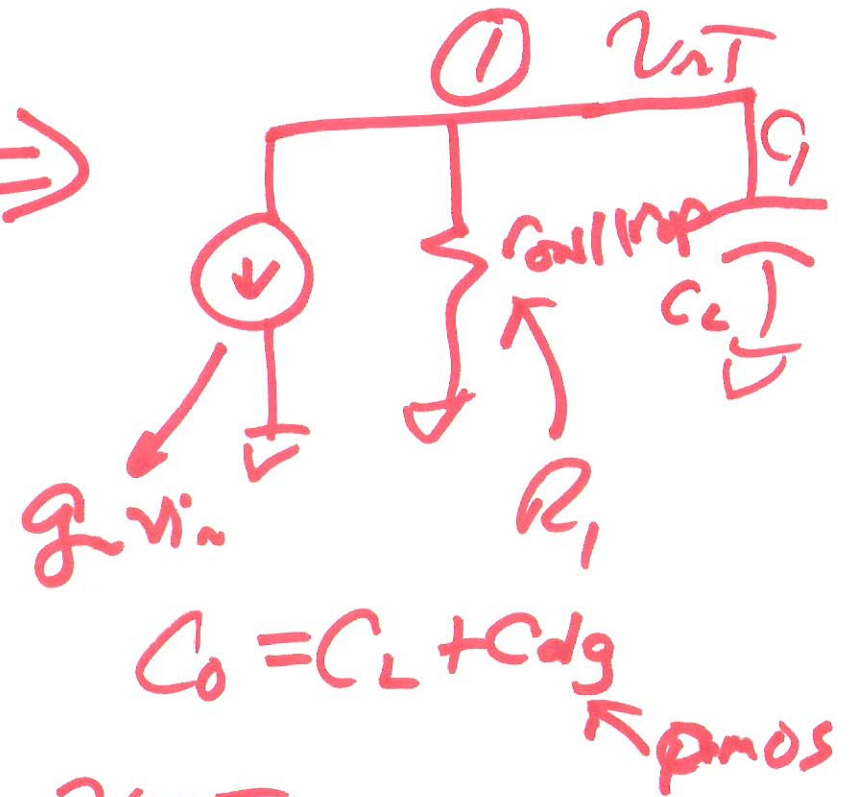

$$R_1 || R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\frac{v_{in} - v_{out}}{1/j\omega C_{gd}} = g_m v_{in} + \frac{v_{out}}{R_o \parallel 1/j\omega C_o}$$

$$j\omega C_{gd} \cdot v_{in} - j\omega C_{gd} \cdot v_{out} = g_m v_{in} + \frac{v_{out}}{R_o} + v_{out} j\omega C_o$$

$$v_{in} (j\omega C_{gd} - g_m) = v_{out} \left(\frac{1}{R_o} + j\omega (C_o + C_{gd}) \right)$$

$$\frac{v_{out}}{v_{in}} = \frac{-(g_m - j\omega C_{gd})}{\frac{1}{R_o} + j\omega (C_o + C_{gd})}$$

6)

$$\frac{v_{out}}{v_{in}} = \frac{(-g_m R_o)(1 - j\omega \frac{C_{gd}}{g_m})}{1 + j\omega R_o(C_o + C_{gd})}$$

$$\omega_z = + \frac{g_m}{C_{gd}}$$


RHP zero

zero

$$1 - j \frac{\omega}{\omega_z}$$


$$1 - j \frac{\omega}{\omega_p}$$
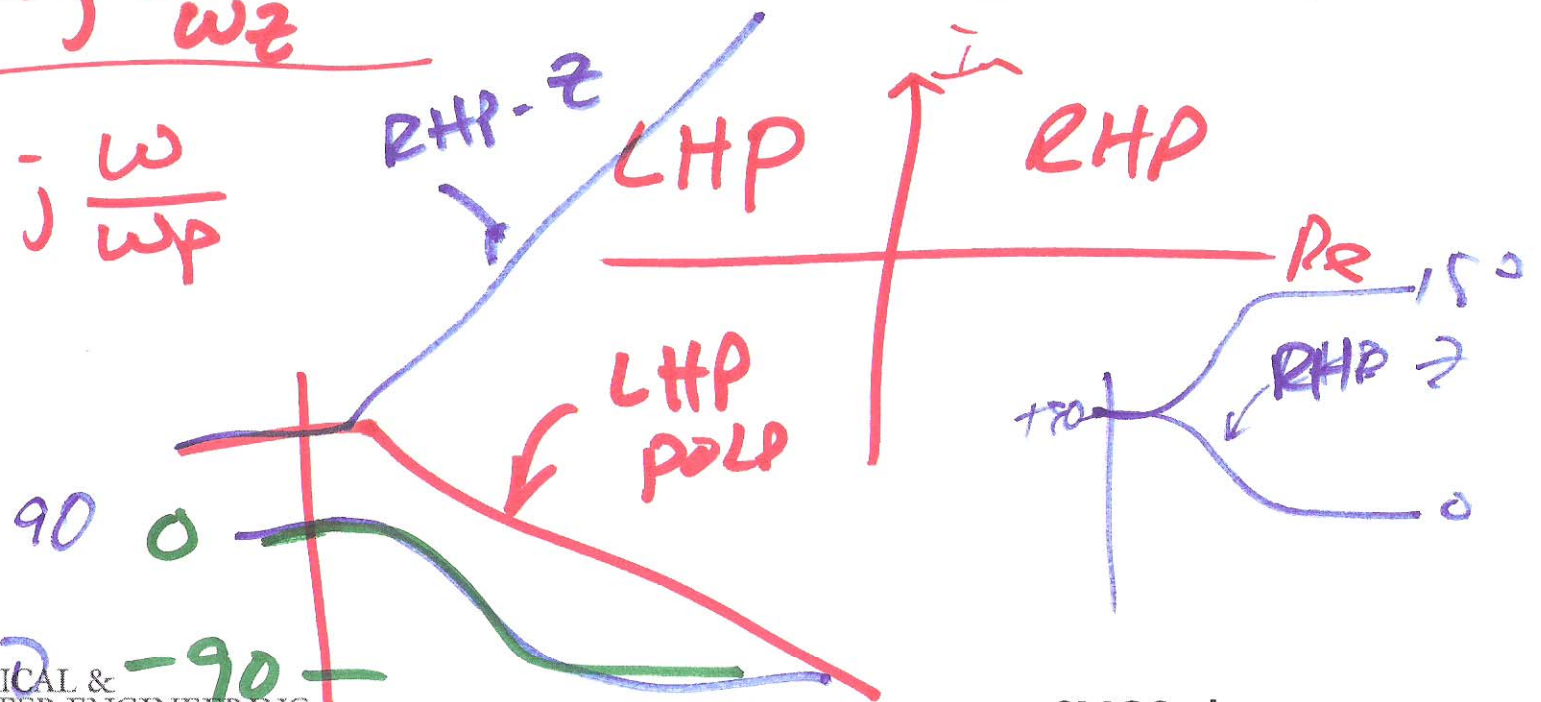
$$\omega_p = \frac{-1}{R_o(C_o + C_{gd})}$$



$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{g_m R_o \left(\sqrt{1 + \left(-\omega \frac{C_{gd1}}{g_m} \right)^2} \right)}{\sqrt{1 + \left(2\pi f \cdot R_o (C_{out}) \right)^2}}$$


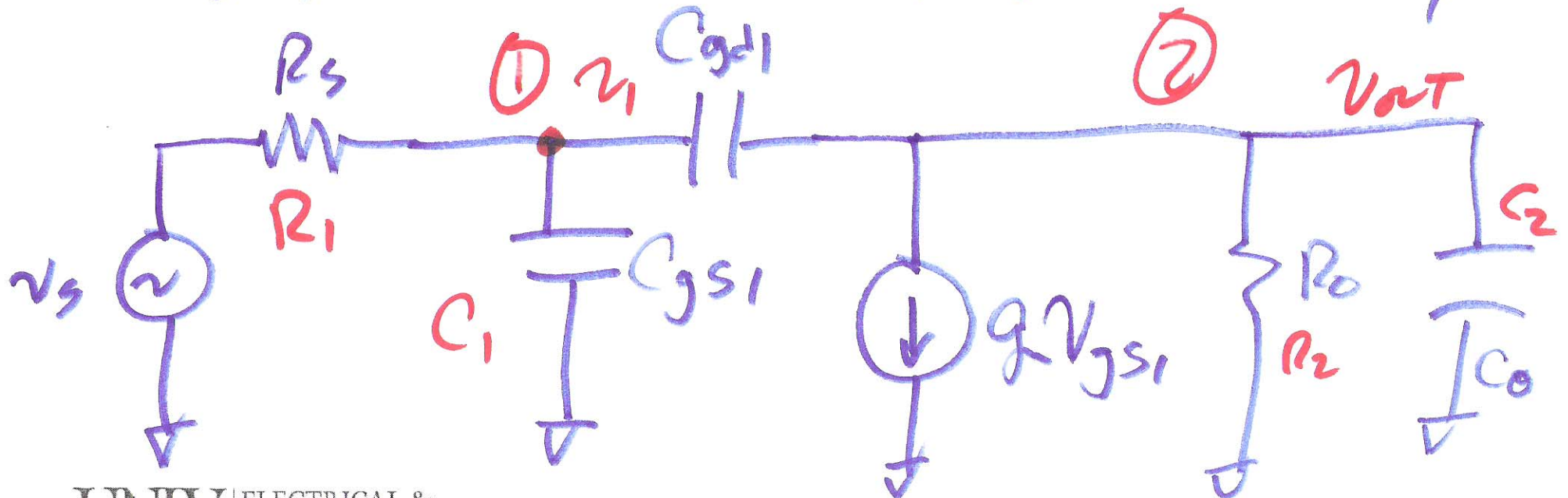
$$\angle \frac{v_{out}}{v_{in}} = \tan^{-1} \left(-\omega \frac{C_{gd1}}{g_m} \right) - \tan^{-1} \frac{\omega R_o (C_{out})}{1}$$



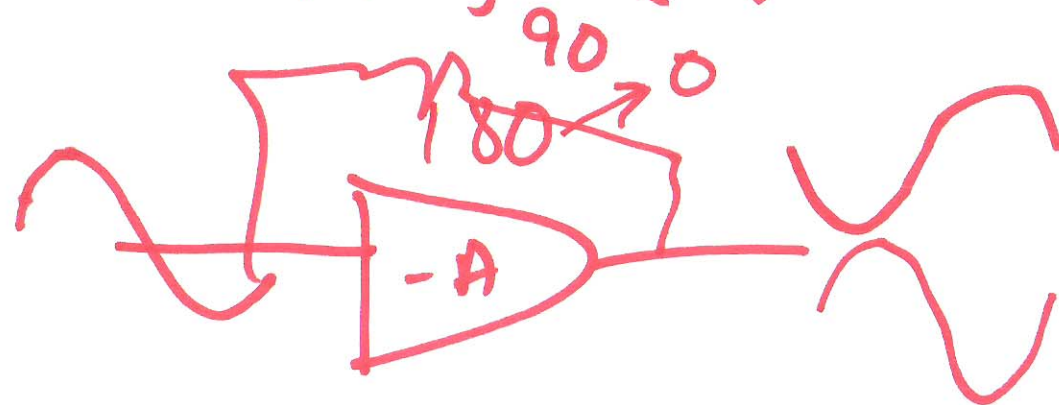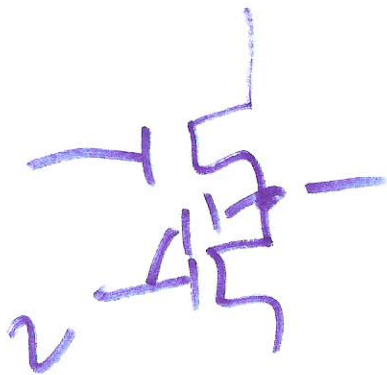8)

$$\frac{v_s - v_i}{R_s} = \frac{v_i}{1/j\omega C_{gs1}} + \frac{v_i - v_{out}}{1/j\omega C_{gd1}}$$

$$\frac{v_{out}}{v_i} = \frac{-g_m R_o \cdot \left(1 - j\omega \frac{C_{gd1}}{g_m}\right)}{1 + j\omega (C_{gd1} + C_o) \cdot R_o}$$



9)