

EE420/ECG 620



March 16, 2015

Lecture 17

S.F. = Common - Drain

No Body effect


AC gain

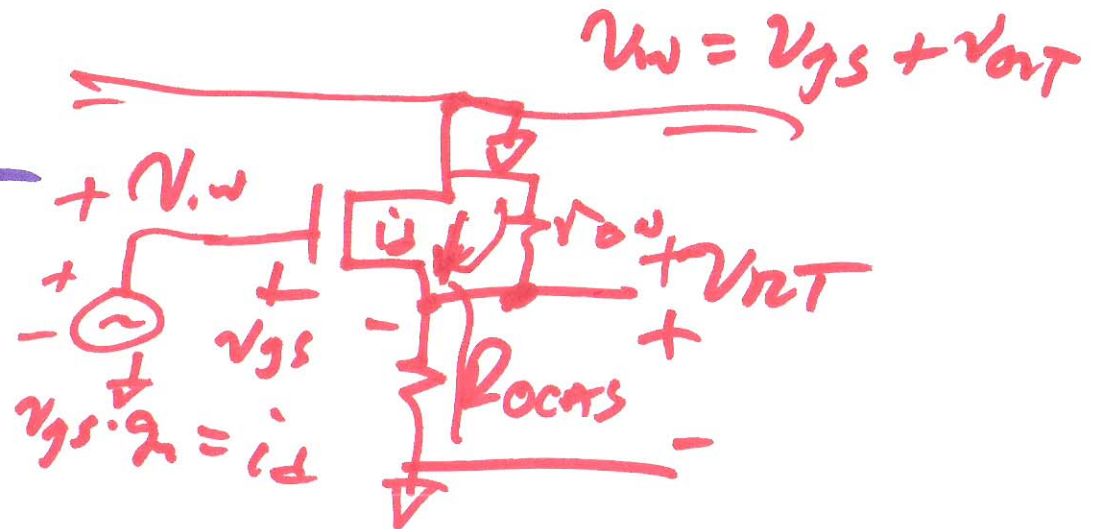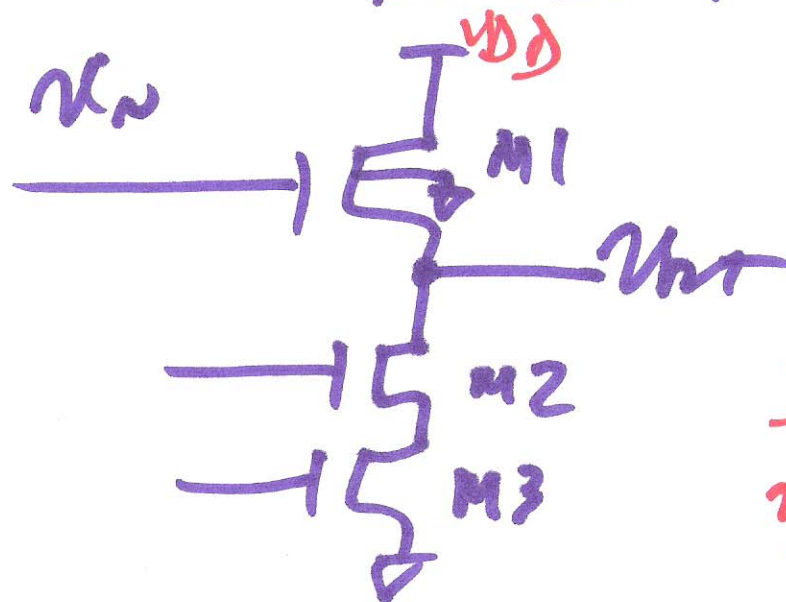

$$V_{in} = V_{gs} + V_{nt} = i_d \left(\frac{1}{g_m} + R_{ocns} \parallel r_{on} \right)$$




$$i_d = g_m V_{gs}$$
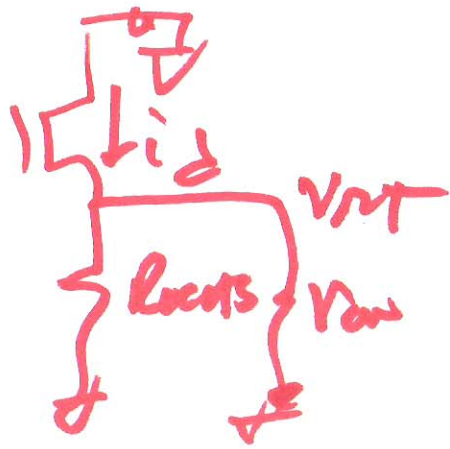
$$V_{nt} = r_{on} \parallel R_{ocns} \cdot i_d$$




$$\frac{V_{nt}}{V_{in}} = \frac{i_d \cdot r_{on} \parallel R_{ocns}}{i_d \left(\frac{1}{g_m} + R_{ocns} \parallel r_{on} \right)}$$
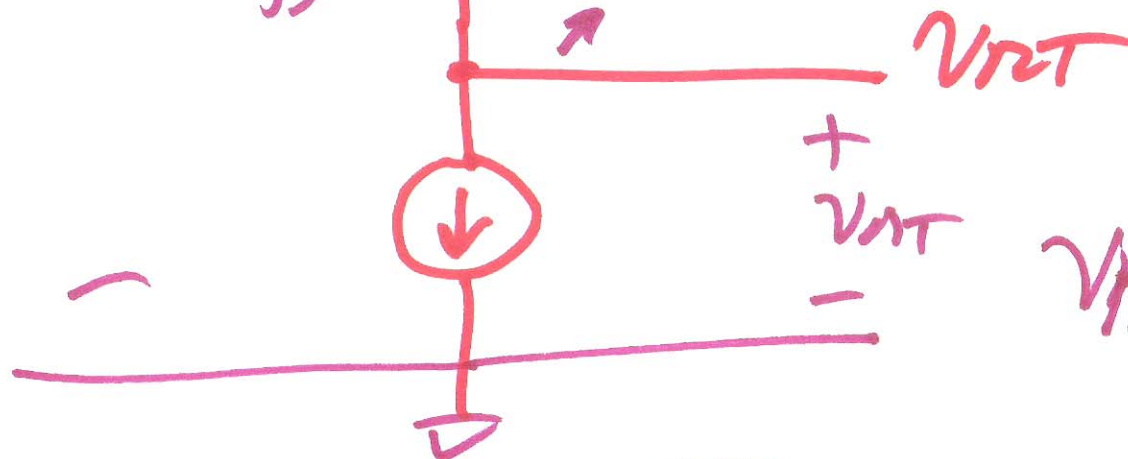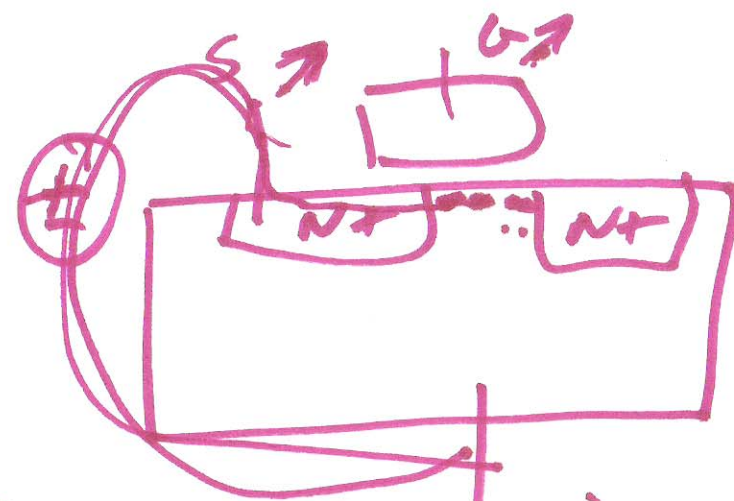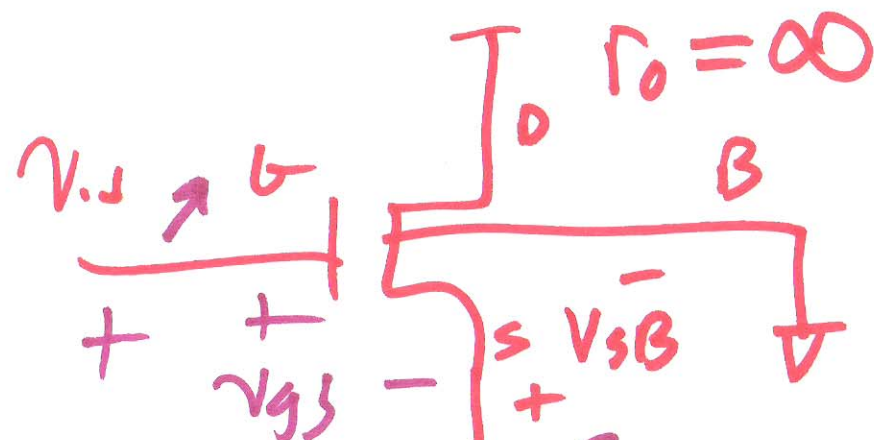
$$V_{nt} = V_{in} \cdot \frac{R_{ocns} \parallel r_{on}}{\frac{1}{g_m} + R_{ocns} \parallel r_{on}}$$



$$V_{TN} = V_{gs} + V_{NT}$$

$$g_m V_{gs} = g_b V_{NT}$$

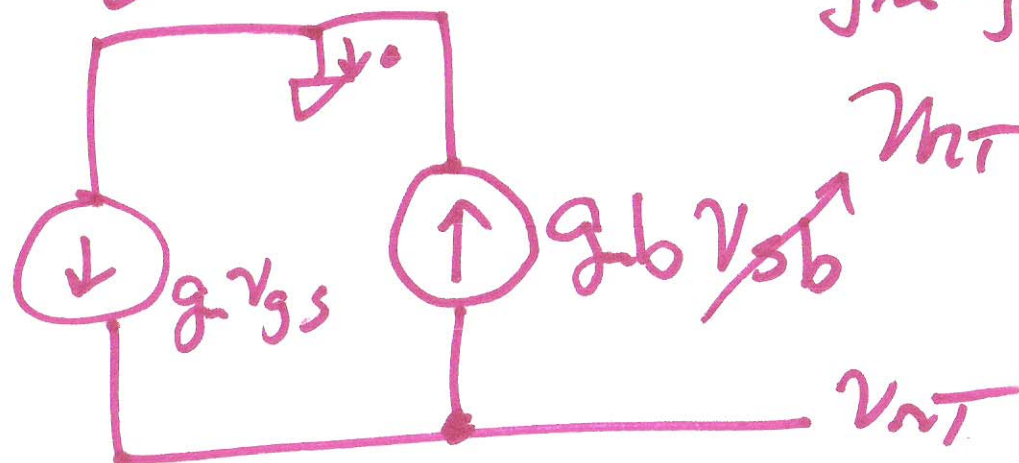

$$V_{in} = V_{gs} + V_{out}$$



$$g_m V_{gs} = g_{mb} \cdot V_{out}$$

$$V_{gs} = \frac{g_{mb}}{g_m} \cdot V_{out}$$

$$V_{in} = \frac{g_{mb}}{g_m} \cdot V_{out} + V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{g_{mb}}{g_m}}$$

$$A \approx 0.7$$

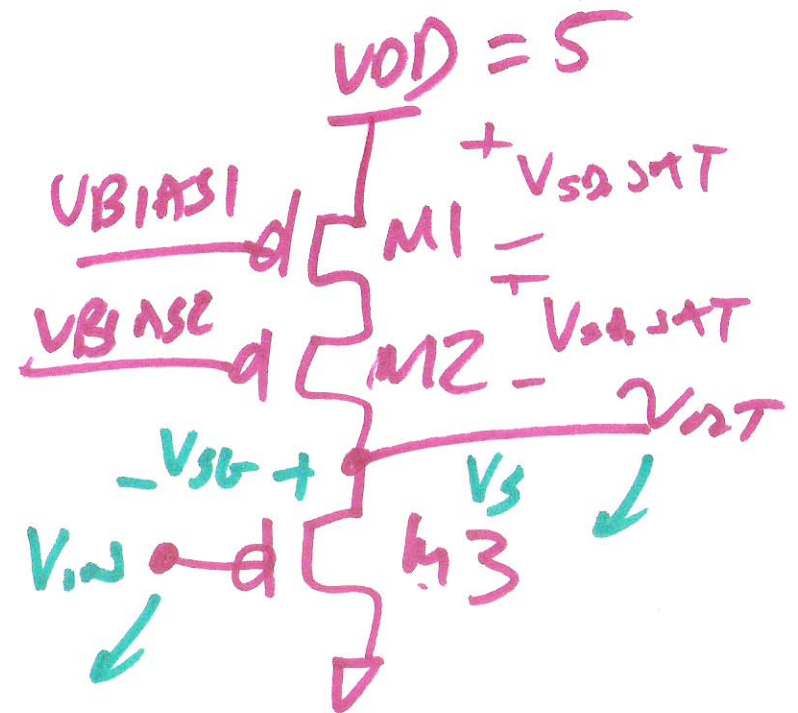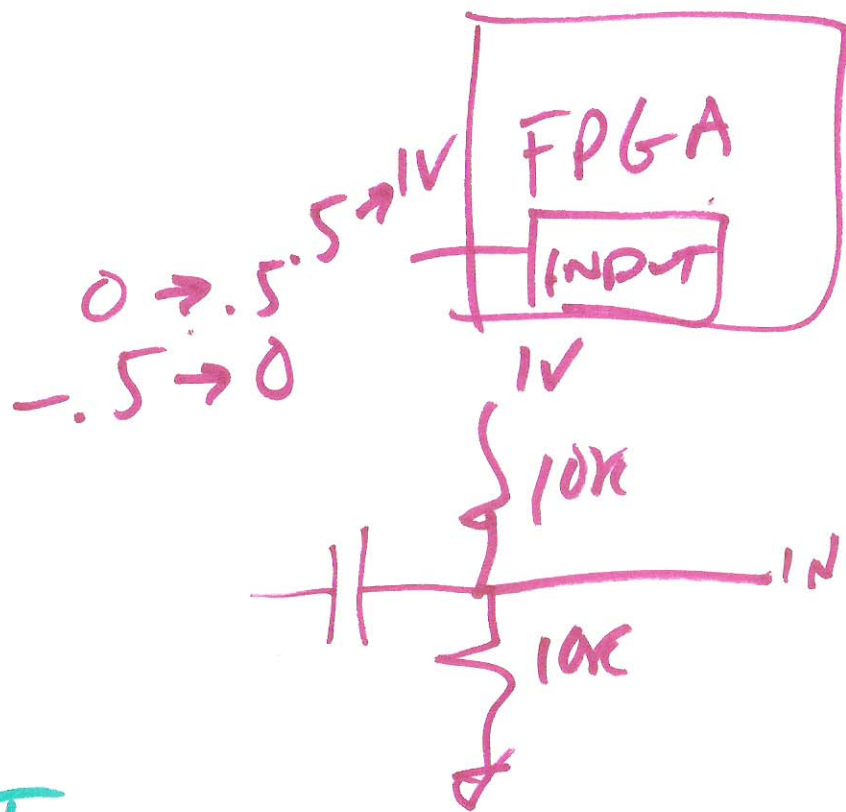

SAT

$$V_{DD} - V_{SD} \geq V_{SG} - V_{THP}$$

$$V_{DD} - V_{SD} \geq V_{SG} - V_{THP}$$


$$V_{IN, MAX} = V_{DD} - 2V_{SD, SAT} - V_{SG}$$

$$V_{IN, MIN} =$$




$$V_{IN} \geq -V_{THP}$$

$$0 \geq -V_{IN} - V_{THP}$$

CMOSedu.com

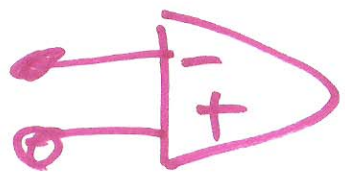



S.F. ON output buffer
for op-amp

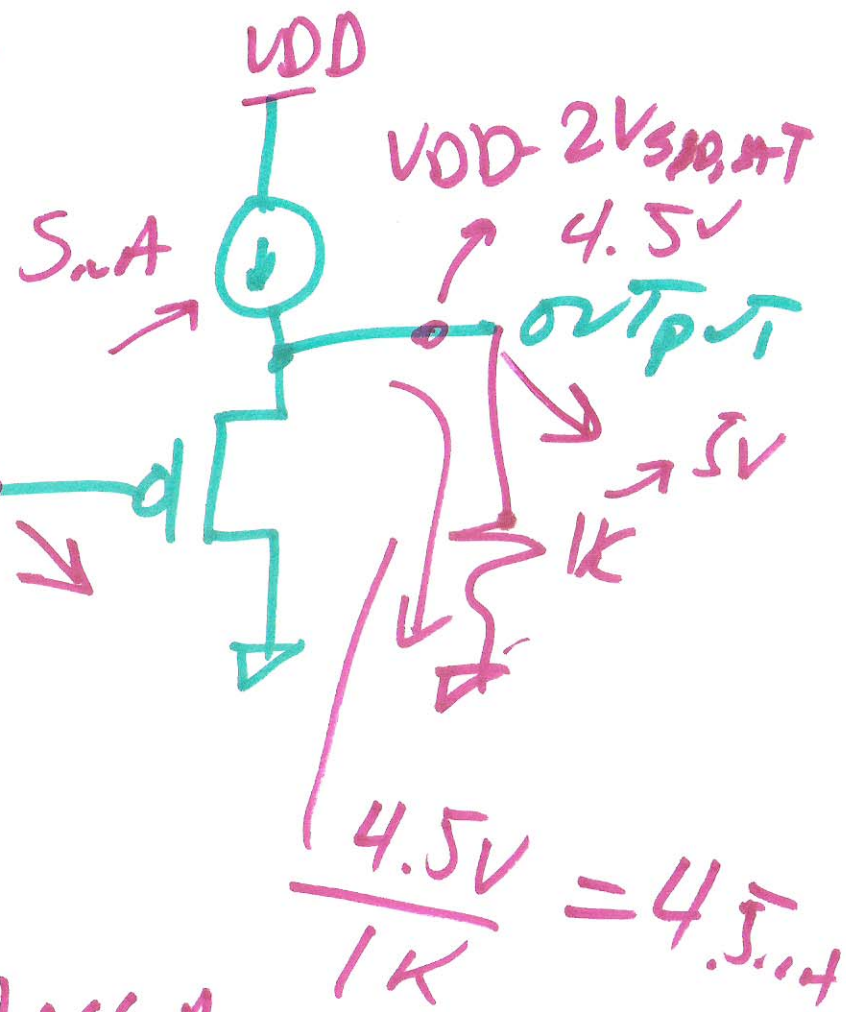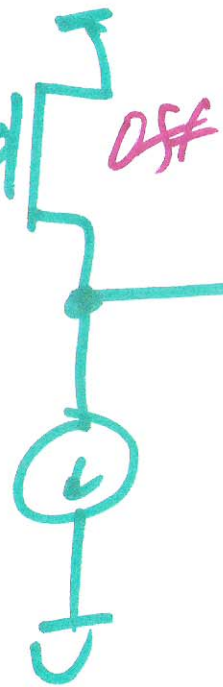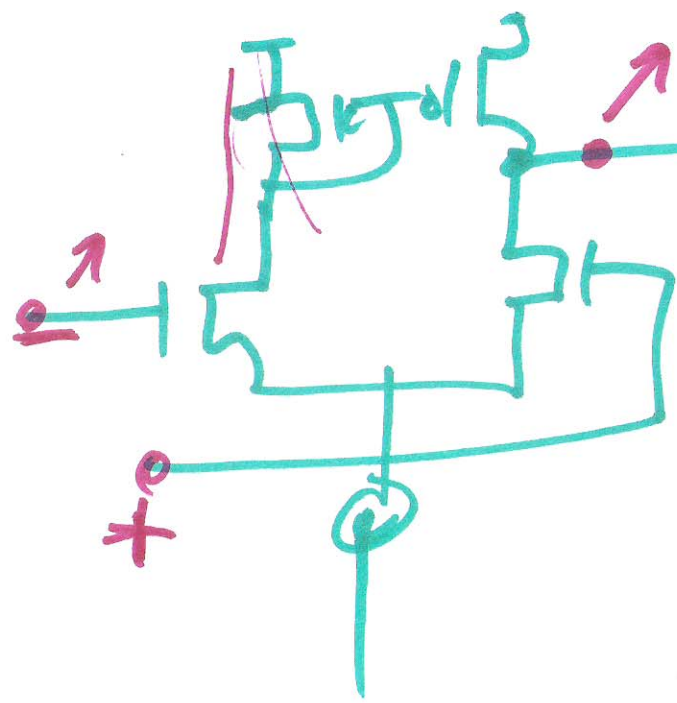

CLASS A


6)

Table 9.2
 50 nm process
 $\mu_{n05} - 100/2$
 $\mu_{p05} - 50/2$

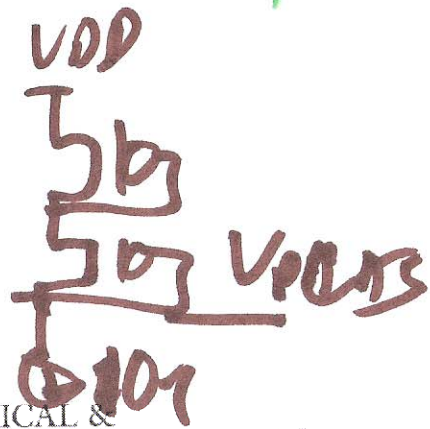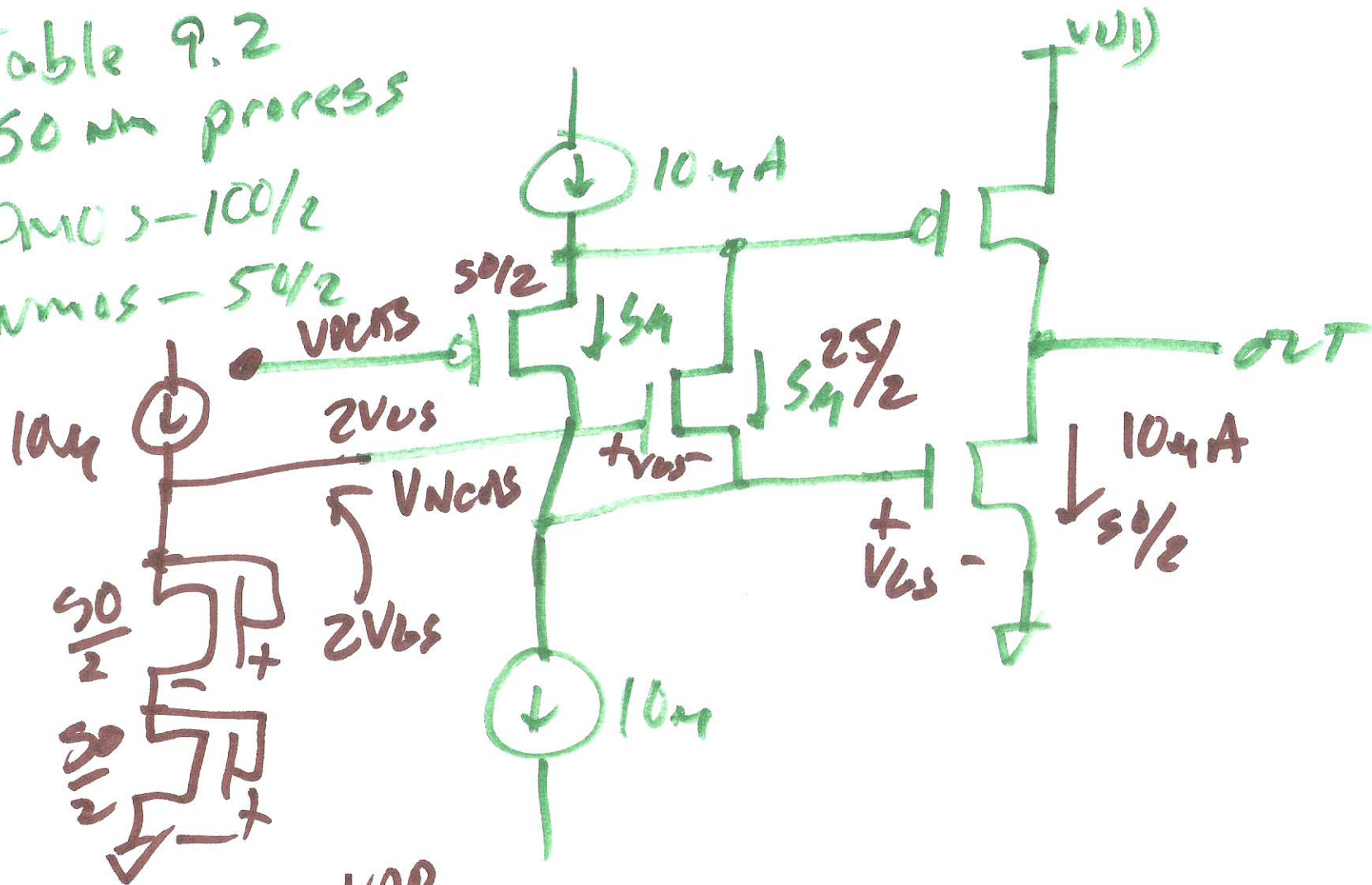

$$g_m V_{gs} = i_d$$

$$g_m (-v_x) = i_d$$

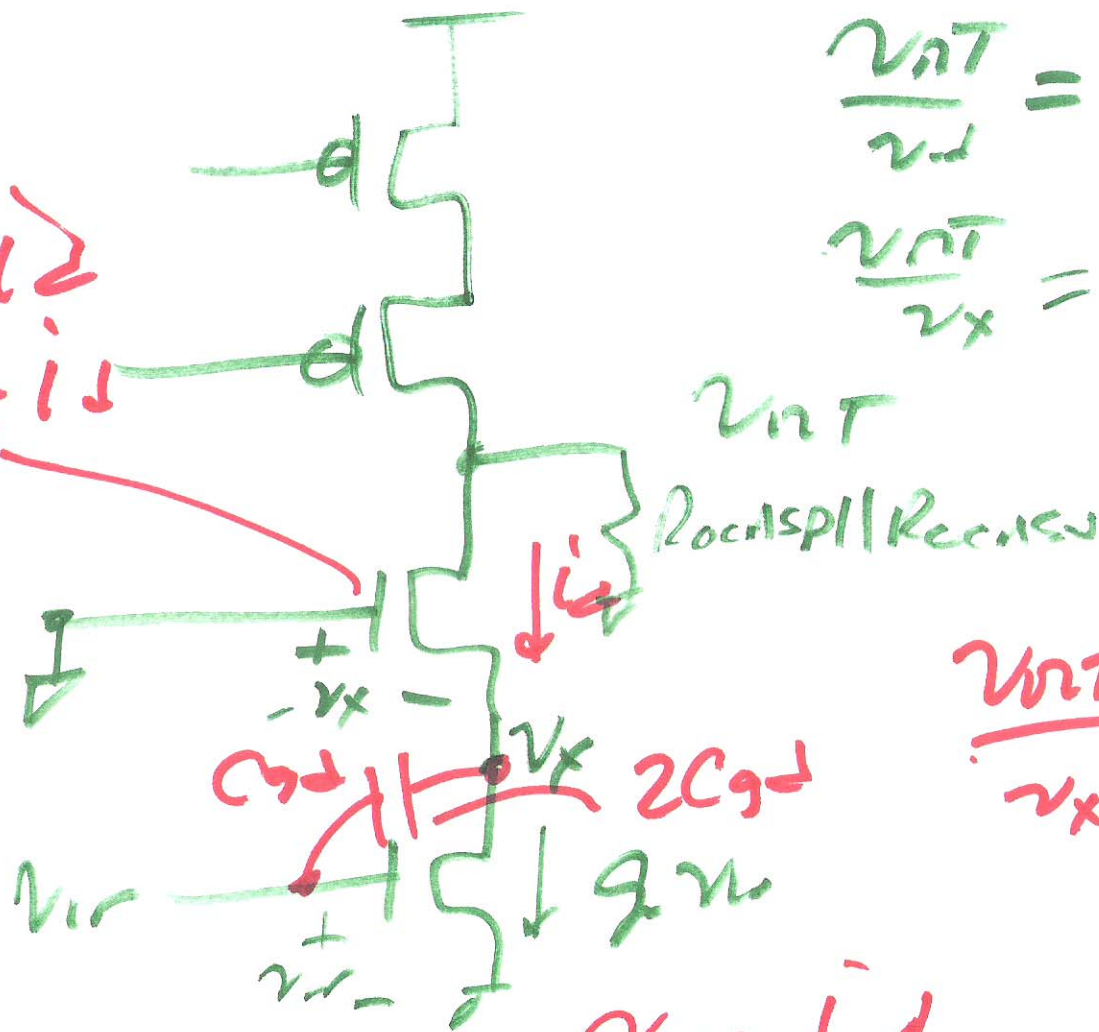

$$\frac{v_{nt}}{v_{in}} = \frac{-i_d \cdot R_{out} \parallel R_{in}}{i_d \cdot 1/g_m}$$

$$\frac{v_{nt}}{v_x} = \frac{-1/g_m}{1/g_m} = -1$$

$$\frac{v_{nt}}{v_x} = \frac{-i_d \cdot 1/g_m}{i_d/2}$$

$$v_{in} = \frac{i_d}{g_m}$$

Miller
Killer

9)