


EE 420 / ECG 620


Analog IC Design

MARCH 23, 2015

Lecture 19


Study H.W. & Quizzes

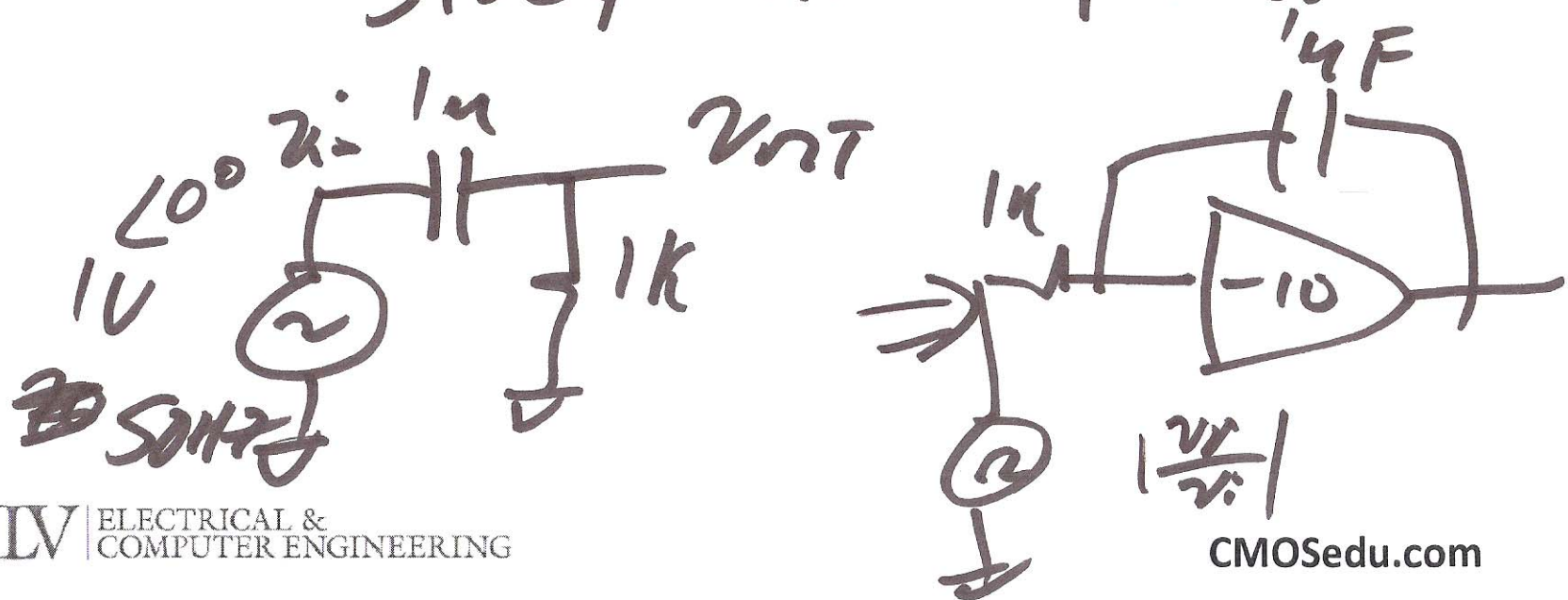

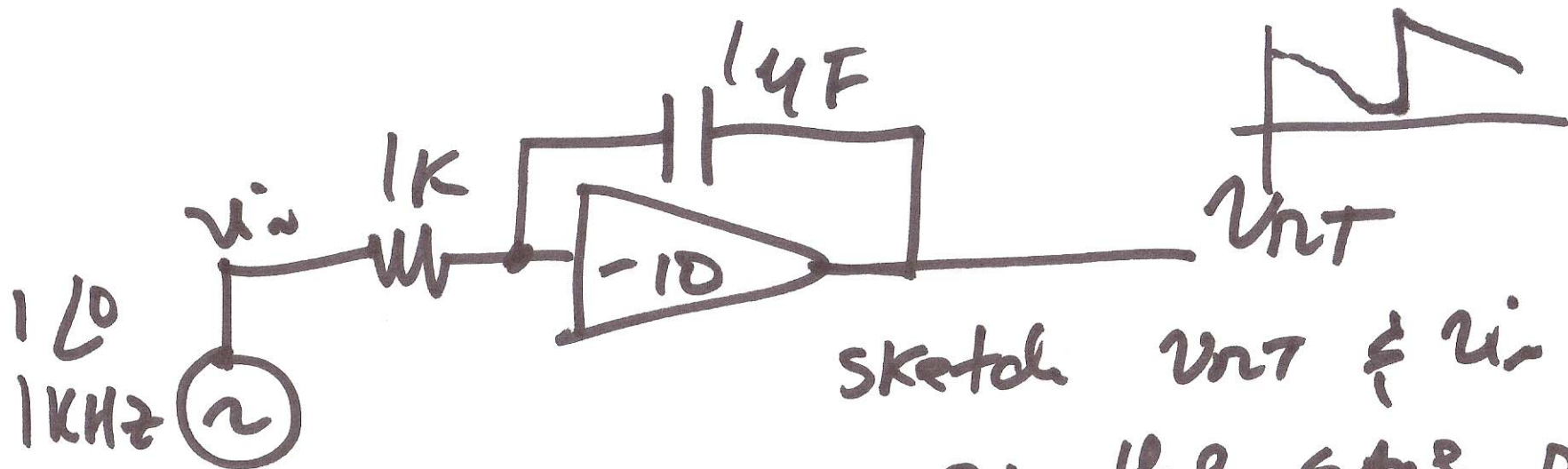


$$\left| \frac{v_{out}}{v_{in}} \right|_{f=0} = 10$$

$$\angle \frac{v_{out}}{v_{in}} \bigg|_{f=0} = \pm 180$$

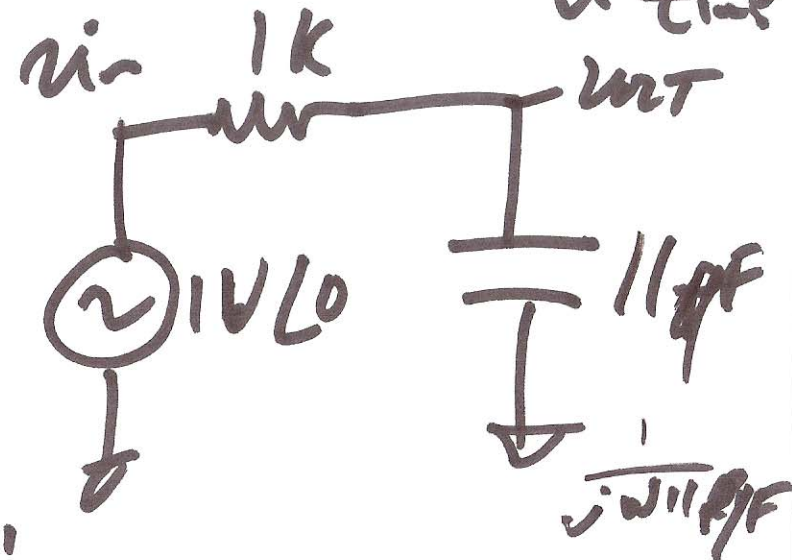

$$v_{out} = v_{in} \cdot \frac{1}{j\omega 14F + 1K}$$
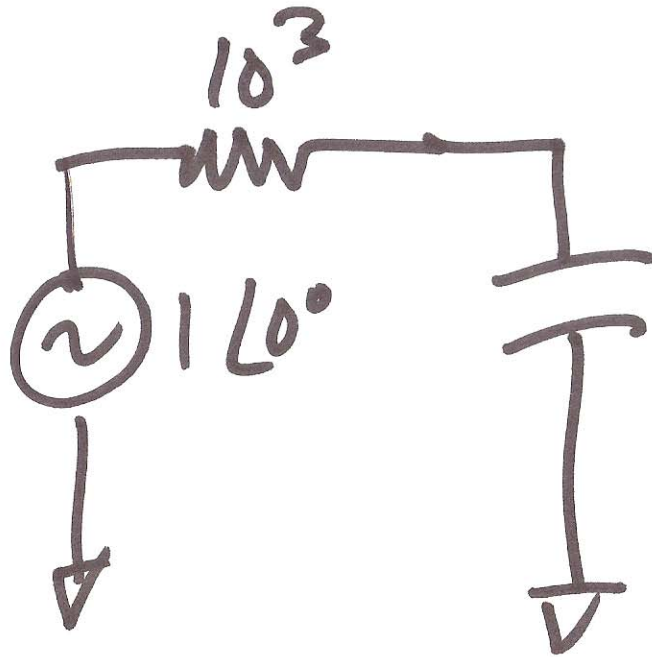
$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j \cdot 2\pi \cdot 10^3 \cdot 10^3 \cdot 11 \cdot 10^{-6}}$$



$$\frac{1}{j 2\pi \cdot 10^3 \cdot 11 \cdot 10^{-6}} = \frac{1}{j 2\pi \cdot 11 \cdot 10^3}$$

$$= -j 14.5$$

$$\frac{V_{out}}{V_{in}} = \frac{-j 14.5}{-j 14.5 + 10^3}$$

$$= \frac{1}{1 + j \cdot \frac{10^3}{14.5} \rightarrow 69}$$


$$\frac{V_{out}}{V_{in}} = \frac{-10 + j0}{1 + j \cdot 69}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{10}{\sqrt{1^2 + (69^2)}} \approx \frac{10}{69} \approx .145$$

$$\angle \frac{V_{out}}{V_{in}} = 180 - \tan^{-1} \frac{69}{1} \approx 90^\circ = -270^\circ$$

$$\theta = 90^\circ = \frac{t_d}{t_s} \cdot 360$$

$$t_d = 250 \mu s$$

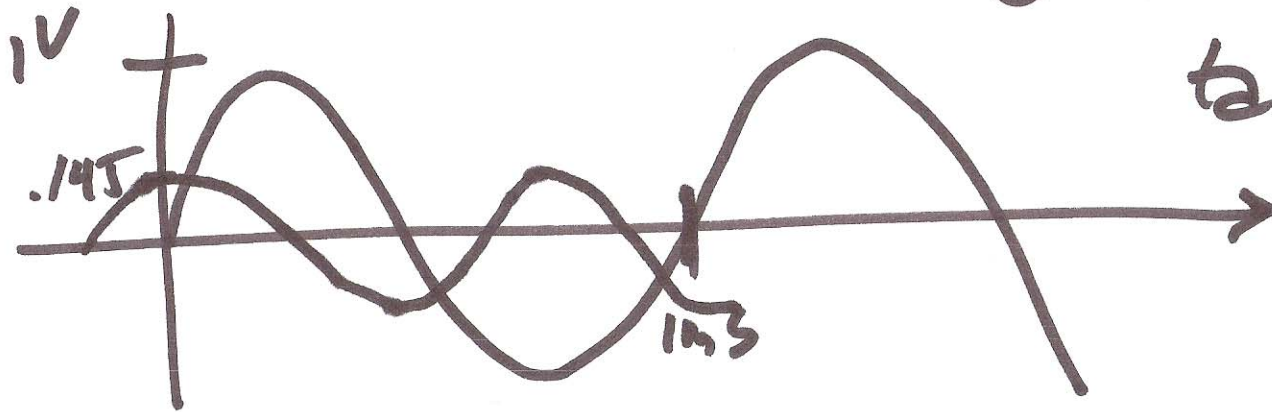

4)



Ex. 9.5 (pmos Flavor)

freq. response


slow rate


Ch. 9
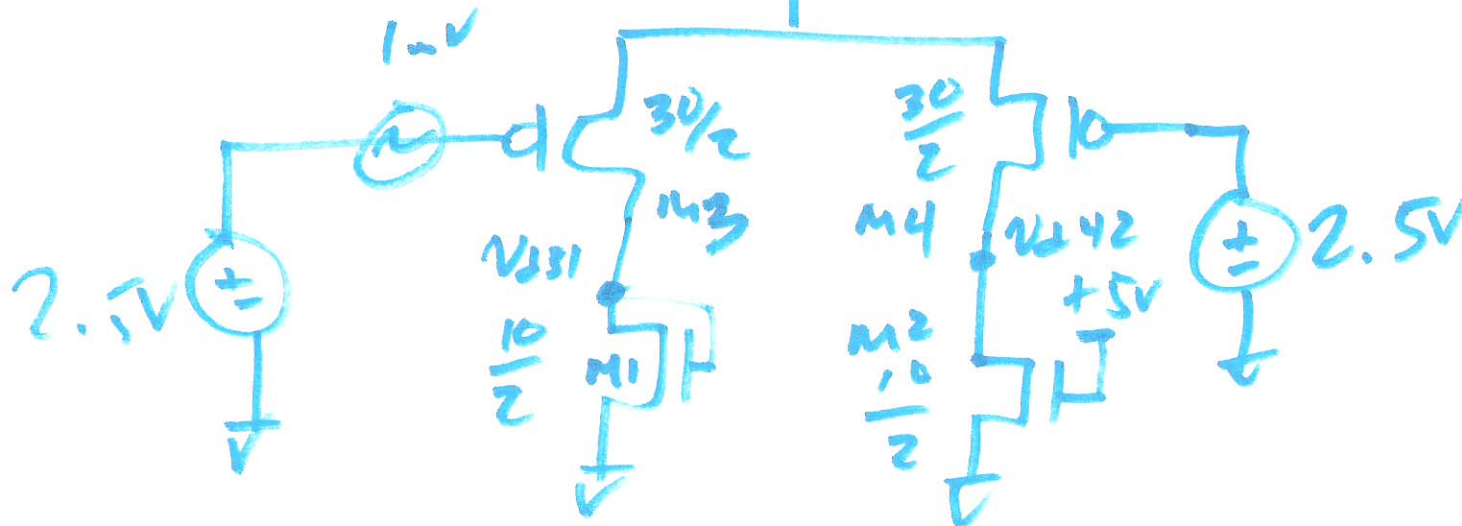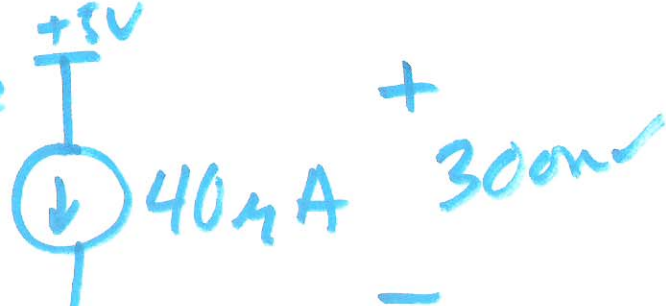
$$I_D = \frac{4\mu C_{ox} W}{2L} (V_{GS} - V_{TH})^2$$



Calculate the gain, $\frac{v_o}{v_i}$

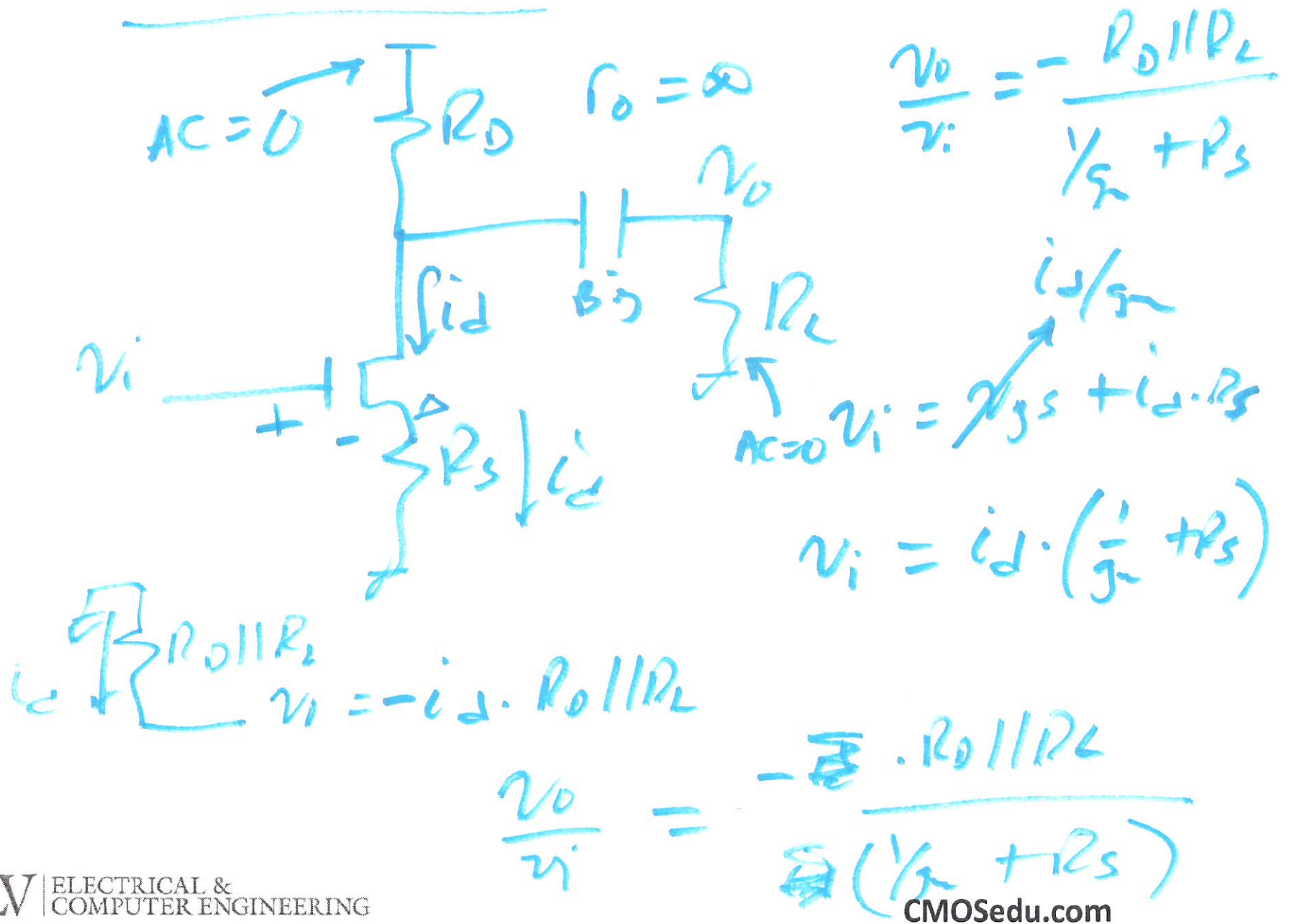

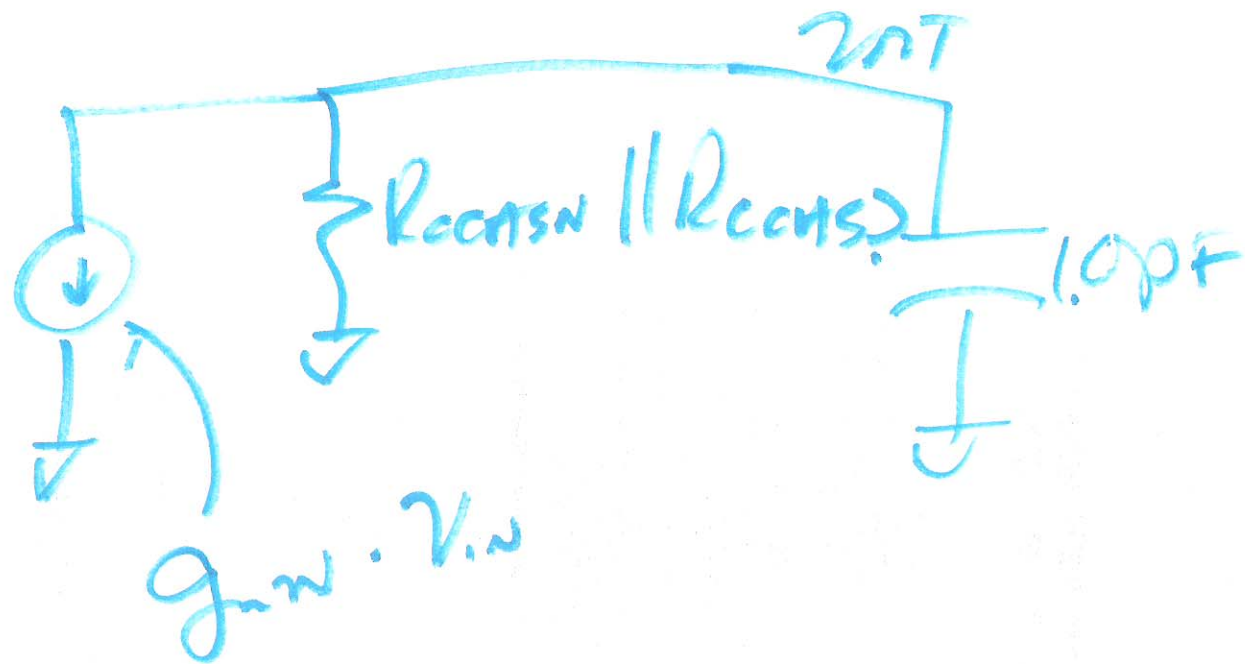

$$\begin{aligned}
 & -g_m \cdot R_{\text{load}} \parallel R_{\text{out}} \\
 &= \frac{-R_{\text{load}} \parallel R_{\text{out}}}{1/g_m}
 \end{aligned}$$