

EE 420 / ECG 620

$x + y = z$ Analog IC Design

$$x = 10$$

$$y = 11$$

$$z = ? \quad ?1$$

$$x = 9$$

$$y = 12$$

April 6, 2015

Lecture 20

$$\frac{R_1 R_2}{R_1 + R_2}$$

↓
1

$$R_1 || R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$I_{in} = \frac{V_x}{R_1} + \frac{V_x}{R_2} = V_x \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_x = I_{in} \cdot R_1 || R_2$$



$$I_x = \frac{V_x}{R_2}$$

$$V_x = R_2 I_x$$

$$I_{in} = I_x \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$I_x = I_{in} \cdot \frac{R_1}{R_1 + R_2}$$

CMOSedu.com

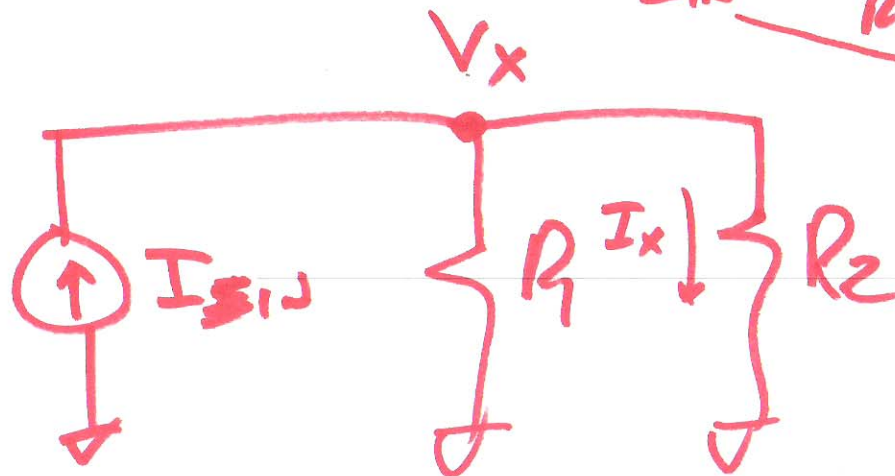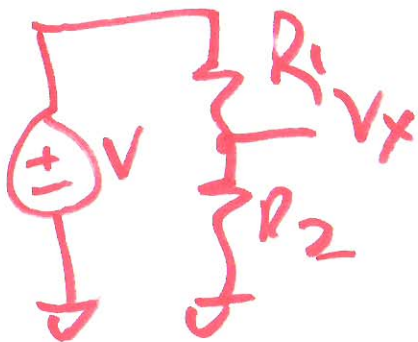

1)

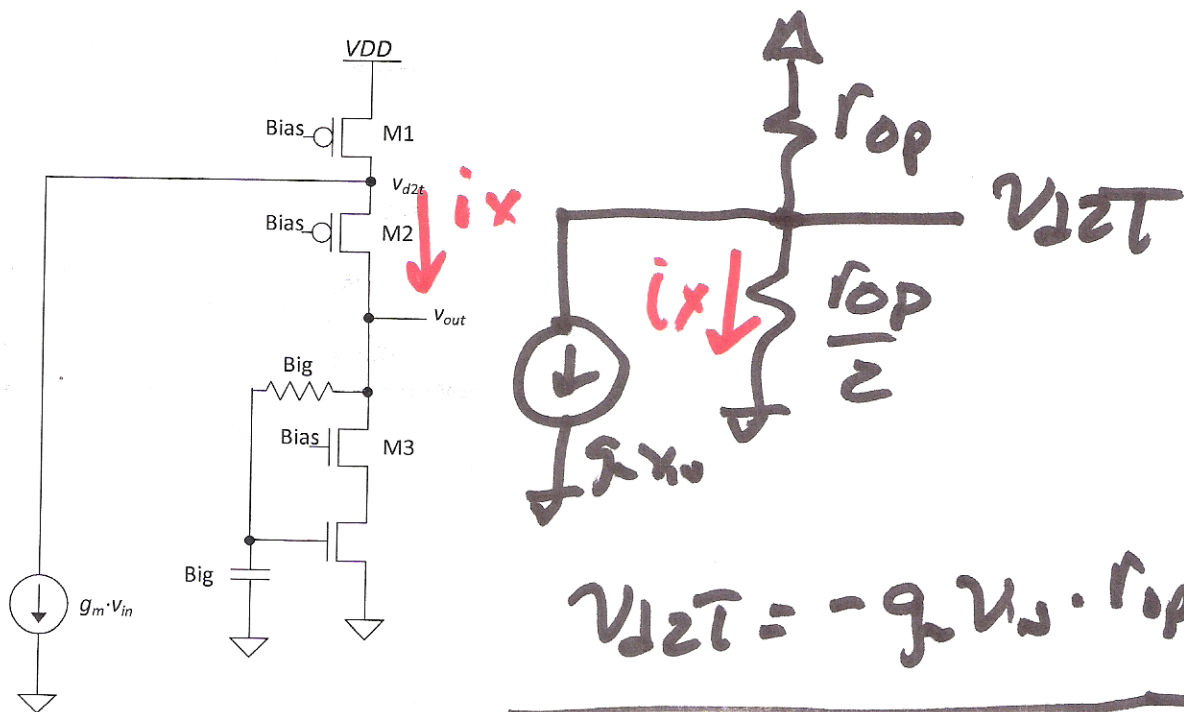4. Estimate the gains, v_{out}/v_{in} , v_{d2t}/v_{in} , and v_{out}/v_{d2t} in the following circuit using R_{ocasn} , r_{op} , g_{mp} , and g_m . You can assume the small-signal resistance looking into: the drain of M1 is r_{op} , the source of M2 is $r_{op}/2$, and the drain of M3 is R_{ocasn} . (20 points)



$$v_{d2t} = -g_m v_{in} \cdot r_{op} \parallel \frac{r_{op}}{2}$$

$$\boxed{\frac{v_{d2t}}{v_{in}} = -g_m r_{op} \parallel \frac{r_{op}}{2}}$$

$$v_{out} = i_x \cdot R_{ocasn}$$

$$i_x = -g_m v_{in} \frac{r_{op}}{r_{op} + \frac{r_{op}}{2}}$$


$$\frac{v_{out}}{v_{in}} = -g_m \frac{r_{op}}{r_{op} + \frac{r_{op}}{2}}$$

$$\frac{v_{out}}{v_{in}} = -g_m \frac{2}{3}$$

$$\boxed{\frac{v_{out}}{v_{in}} = -g_m \cdot \frac{2}{3}}$$

$$\boxed{\frac{v_{out}}{v_{d2t}} = g_m^2 \left(\frac{2}{3} \right)^2 R_{ocasn}}$$

2)

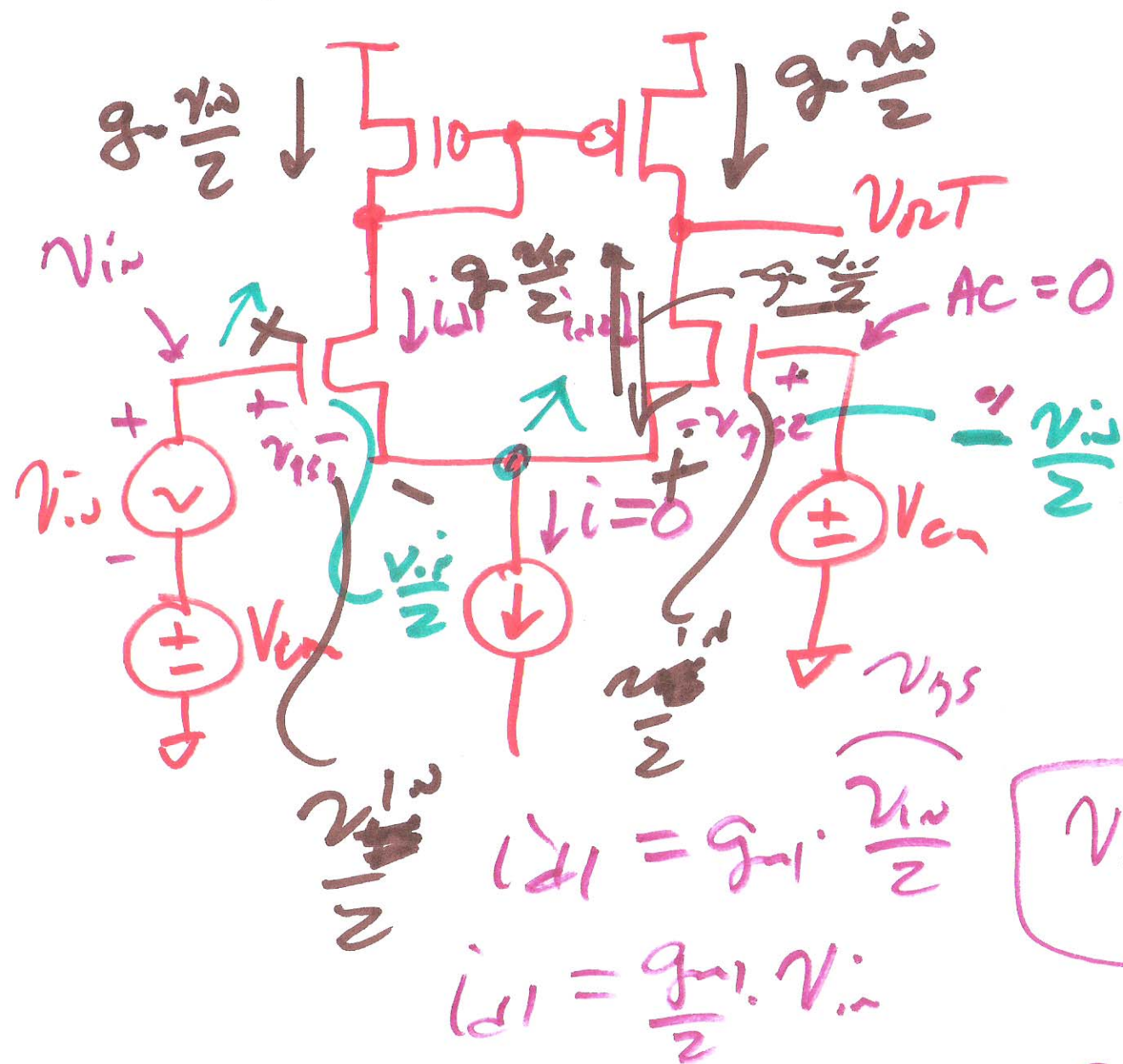

$$V_w - V_{gs1} + V_{gs2} = 0$$

$$V_w = V_{gs1} - V_{gs2}$$

$$i_{d1} = -i_{d2}$$

$$-i_{d1} = i_{d2}$$

$$V_{gs} = \frac{i_d}{g_m}$$


$$V_w = \frac{i_{d1}}{g_{m1}} - \frac{i_{d2}}{g_{m2}}$$

$$i_{d1} = g_{m1} \cdot \frac{V_w}{2}$$


$$i_{d1} = \frac{g_{m1}}{2} \cdot V_{in}$$

$$V_w = i_{d1} \left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right)$$

$$V_w = i_{d1} \cdot \frac{Z}{g_{m1}}$$

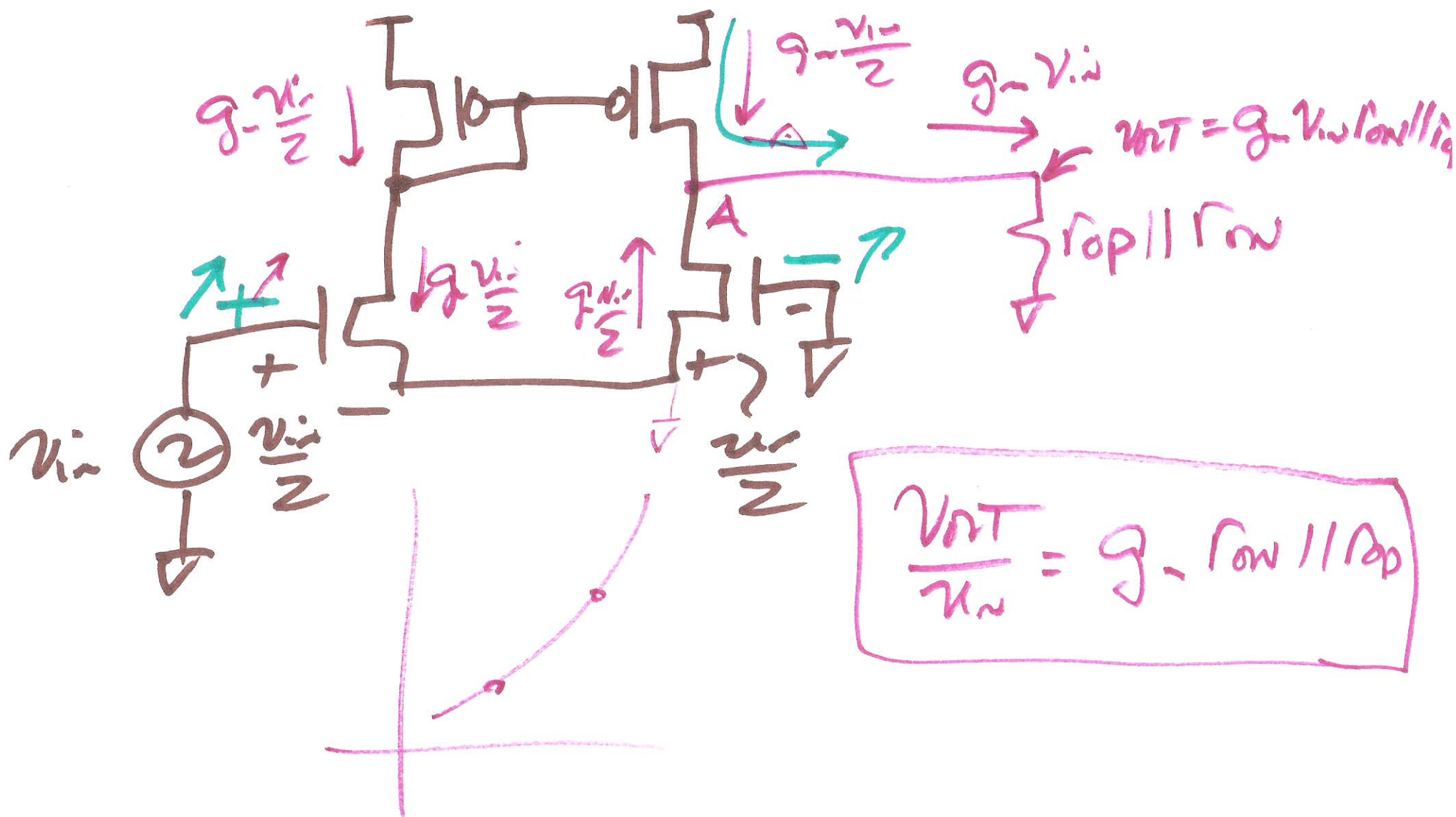

4)

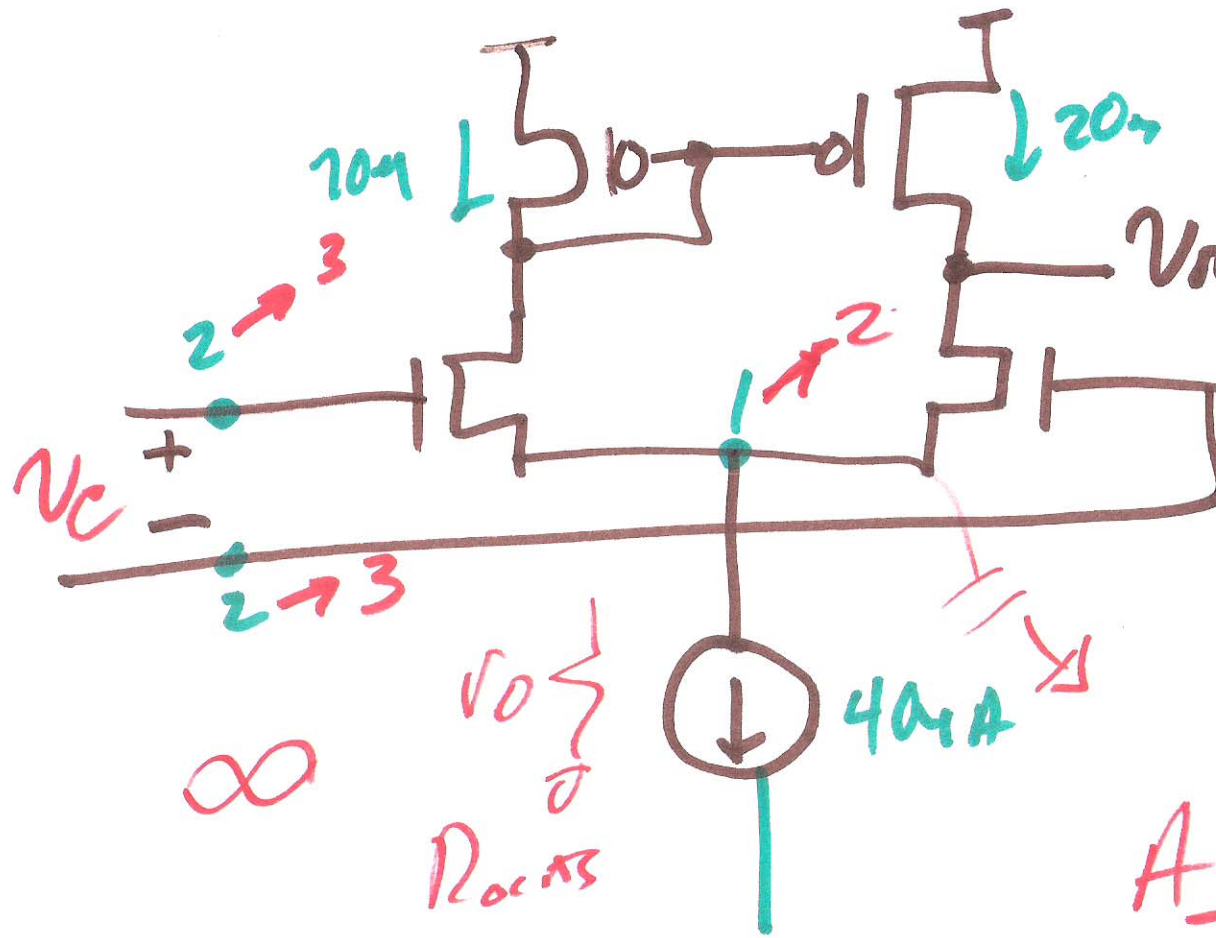


$$A_c = \frac{v_{out}}{v_c} = \text{Common mode gain}$$

$$CMRR = 20 \log \frac{A_d}{A_c}$$

$$A_d = g_m r_{out} || R_p$$

↑
difference

Calculating
Common-mode
gain, A_c

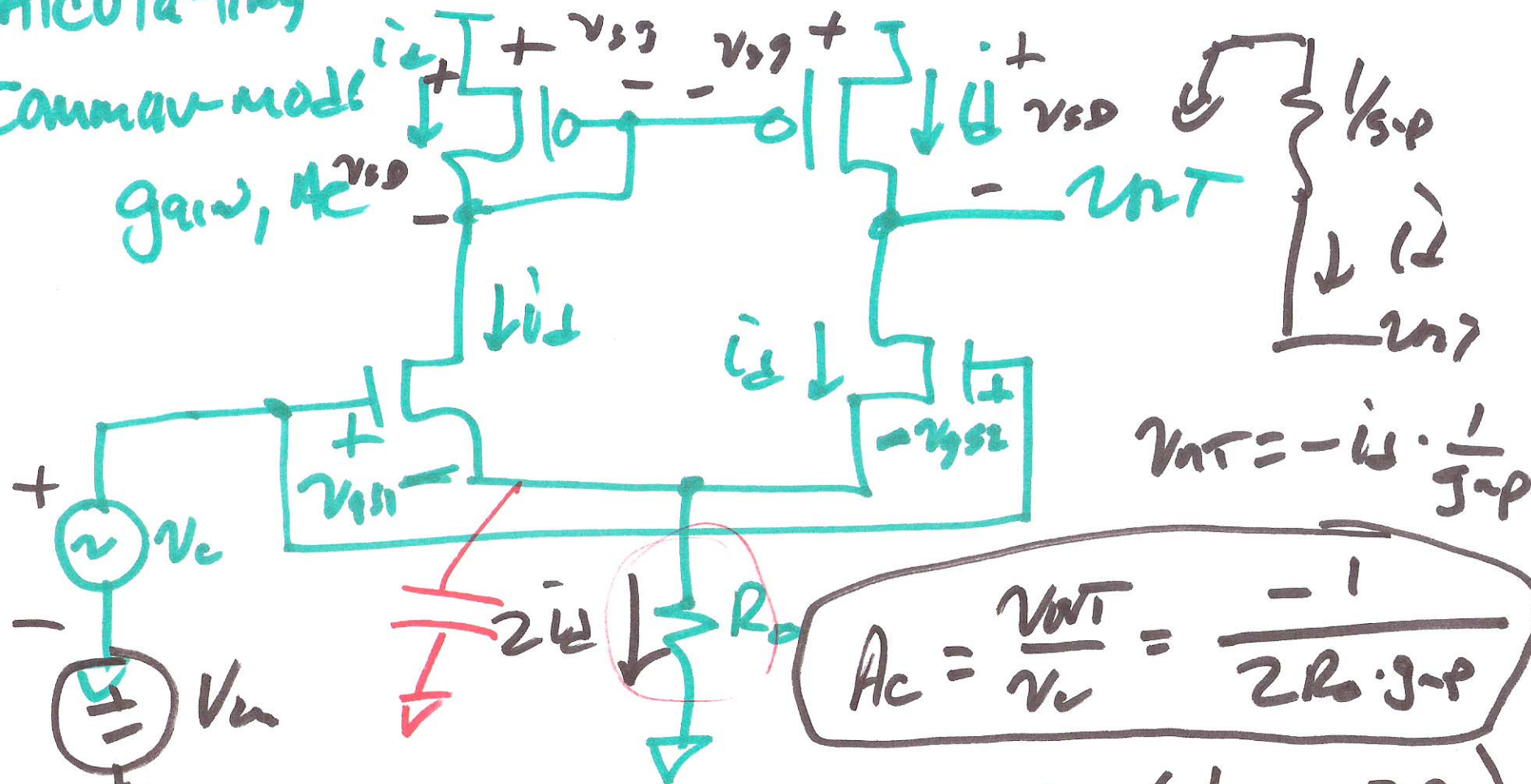

$$V_c = V_{gs1,2} + 2i_d \cdot R_o = i_d \left(\frac{1}{g_m} + 2R_o \right)$$

$$V_c \approx i_d \cdot 2R_o$$

