



EE 420 / ECE 620


Analog IC Design

April 8, 2015

Lecture 21

References

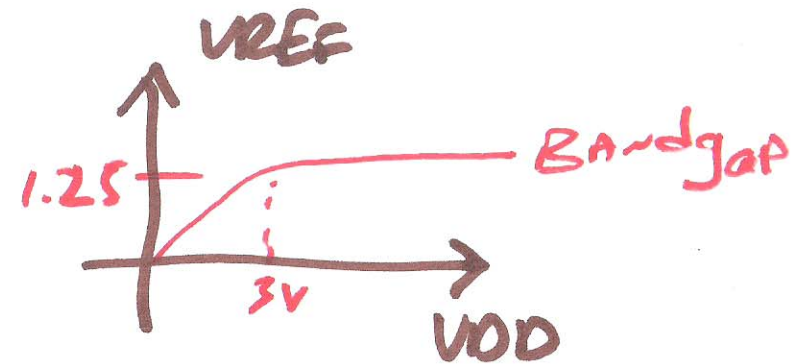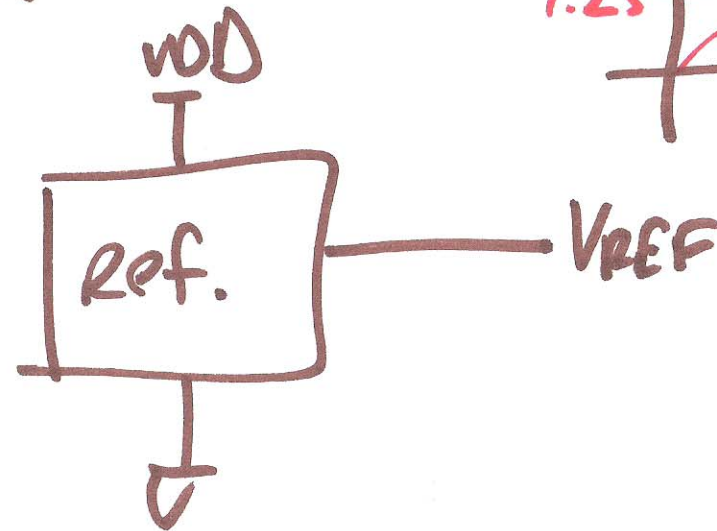

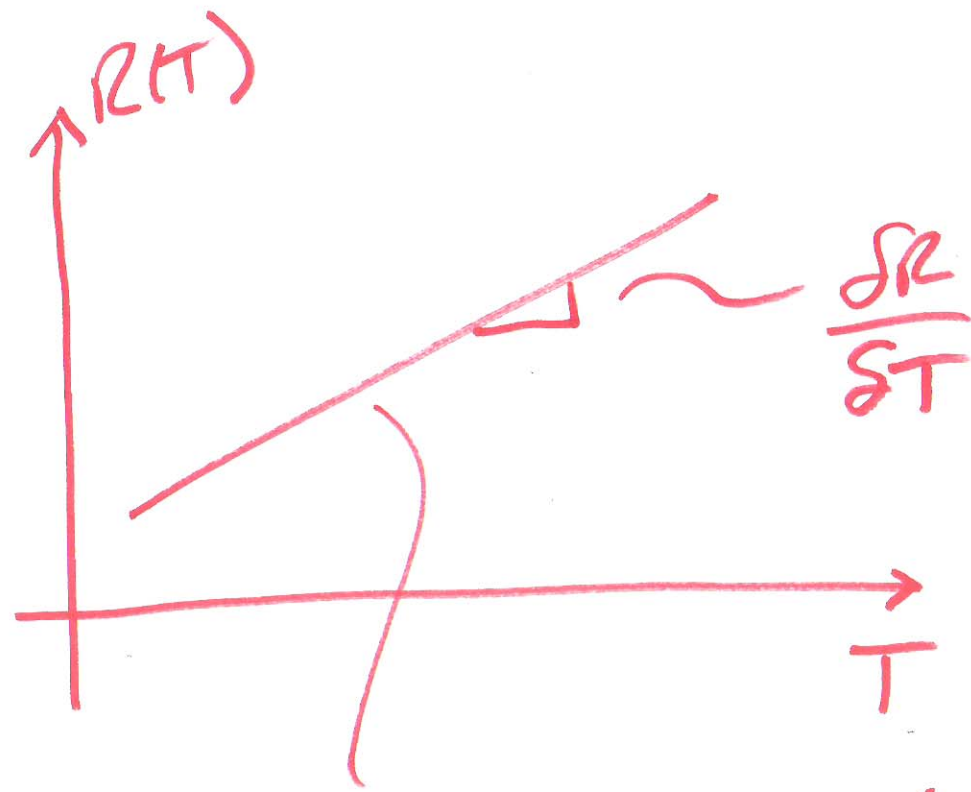


$$R(T) = R(T_0) \left(1 + TCR(T - T_0) \right)$$

$\times 10^6$


$$R(T_0) \cdot TCR = \frac{\delta R}{\delta T}$$

$$0,002 = 2,000 \frac{\mu\Omega}{^\circ\text{C}} = TCR = \frac{1}{R} \frac{\delta R}{\delta T}$$

Diodes

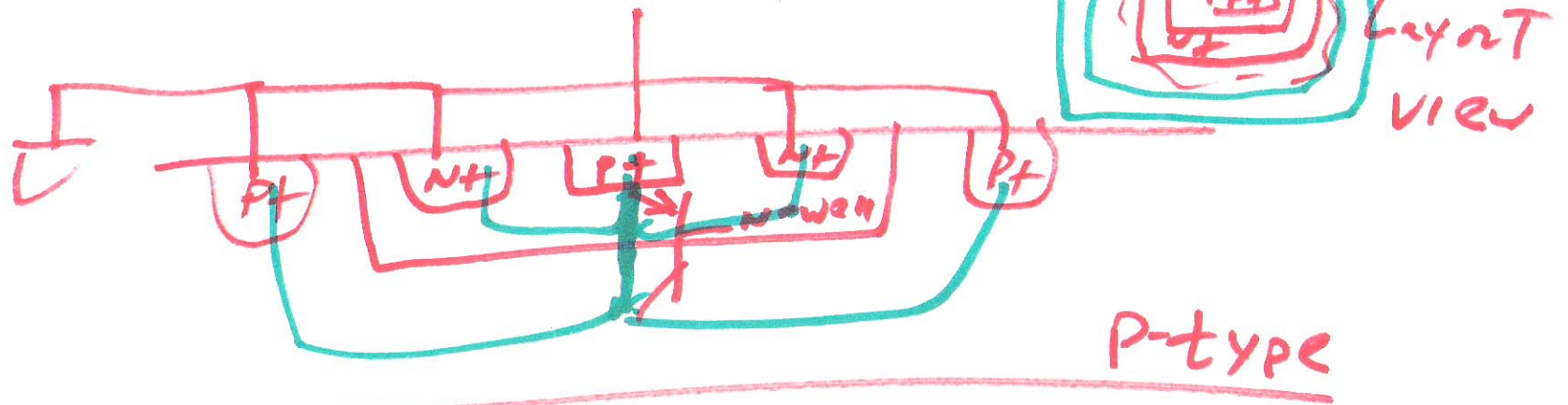


PARASITIC PNP

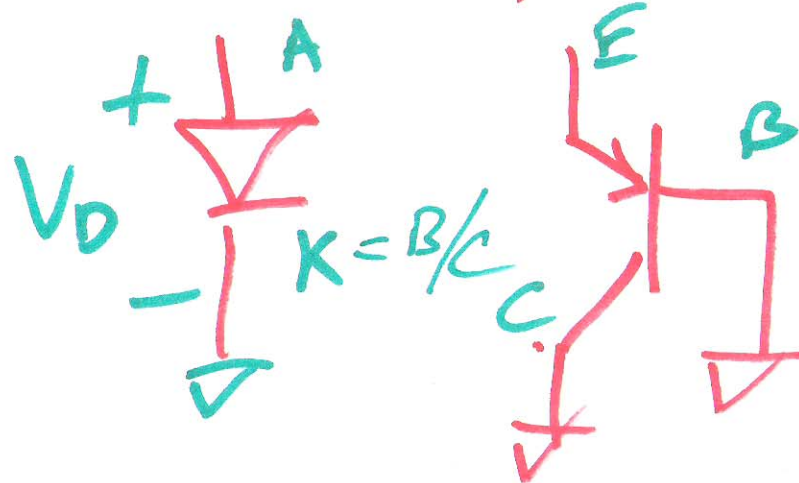



$$I_D = I_S e^{V_D / N V_T}$$

forward bias

$$V_D = N V_T \ln \frac{I_D}{I_S}$$

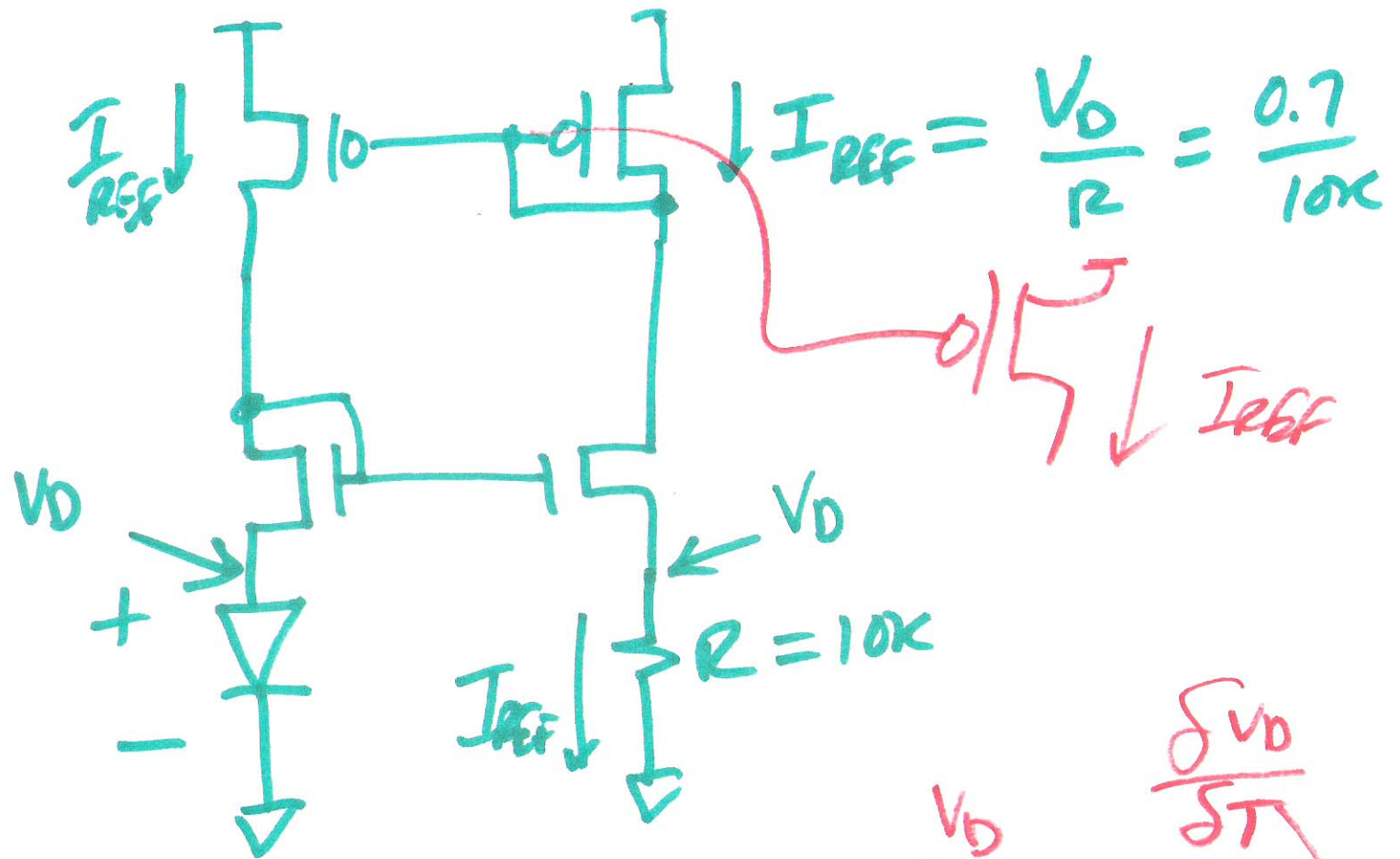

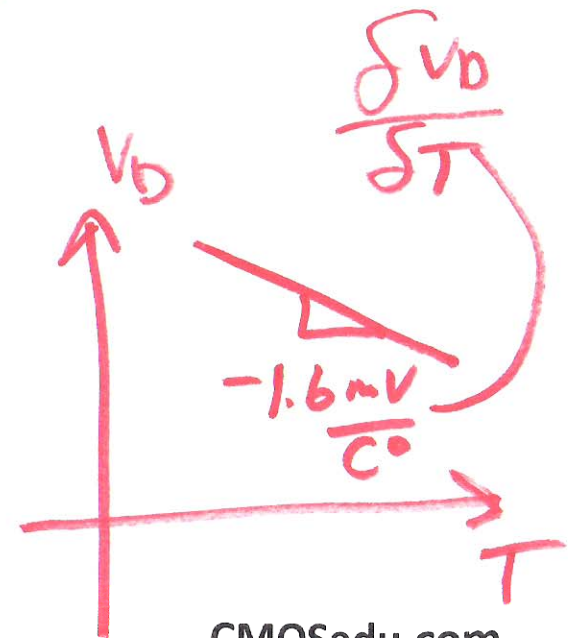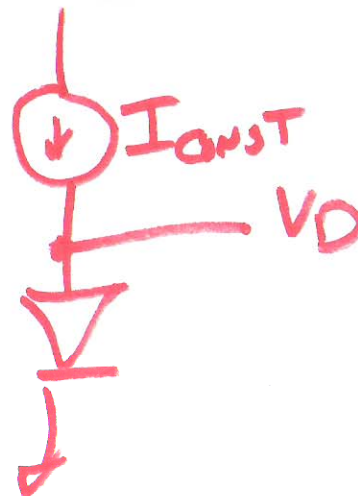
$$V_{bi} = \frac{KT}{q} \ln \frac{N_A N_D}{N_i^2}$$



$$\frac{\delta I_{REF}}{\delta T} = \frac{\delta \frac{V_D}{R}}{\delta T} = \frac{\delta}{\delta T} V_D R^{-1}$$
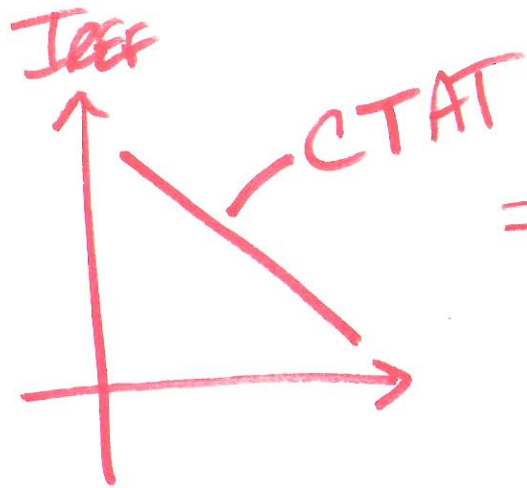
$$= \frac{\delta V_D}{\delta T} \cdot R^{-1} + V_D \cdot (-1) R^{-2} \frac{\delta R}{\delta T}$$



$$= \frac{1}{V_D R} \frac{\delta V_D}{\delta T} + - \frac{V_D}{R} \cdot \frac{1}{R} \frac{\delta R}{\delta T}$$

$$TCI_{REF} = \frac{-0.0016}{0.7} - 0.002$$


$$TCI_{REF} = \frac{1}{I_{REF}} \frac{\delta I_{REF}}{\delta T} = \frac{1}{V_D} \frac{\delta V_D}{\delta T} - \frac{1}{R} \frac{\delta R}{\delta T}$$

$$I_{REF}(T) = I_{REF}(T_0) \left(1 + TCI_{REF}(T - T_0) \right)$$

$$I_{REF} = \frac{V_{O1} - V_{O2}}{R}$$

$$\ln a - \ln b = \ln \frac{a}{b}$$

$$I_{REF} = \frac{N V_T R_K}{R}$$

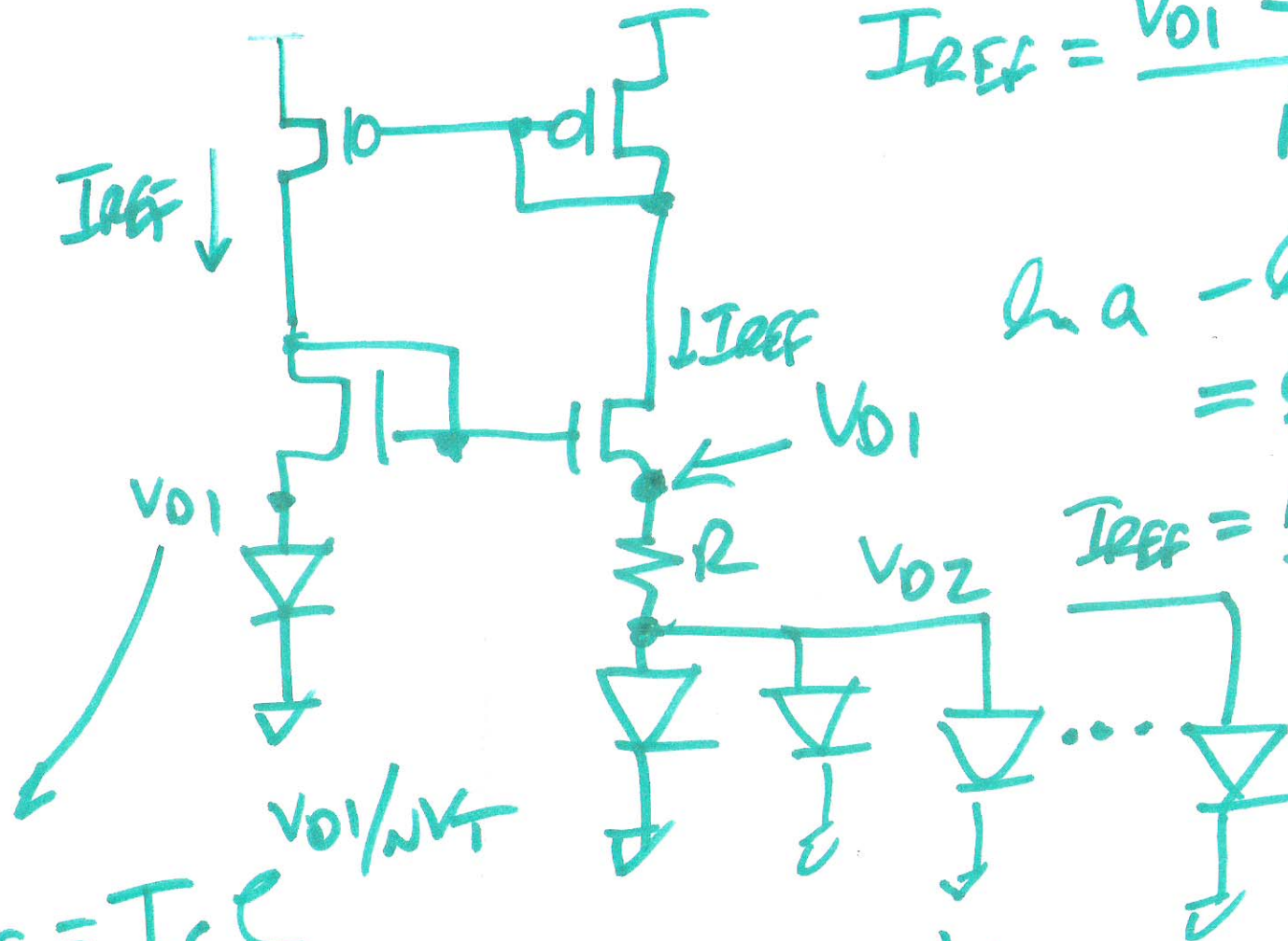


$$I_{REF} = I_S e^{\frac{V_{O1}}{N V_T}}$$

$$V_{O1} = N V_T R \ln \frac{I_{REF}}{I_S}$$

$$I_{REF} = K I_S e^{\frac{V_{O2}}{N V_T}}$$

$$V_{O2} = N V_T R \ln \frac{I_{REF}}{K I_S}$$

6)

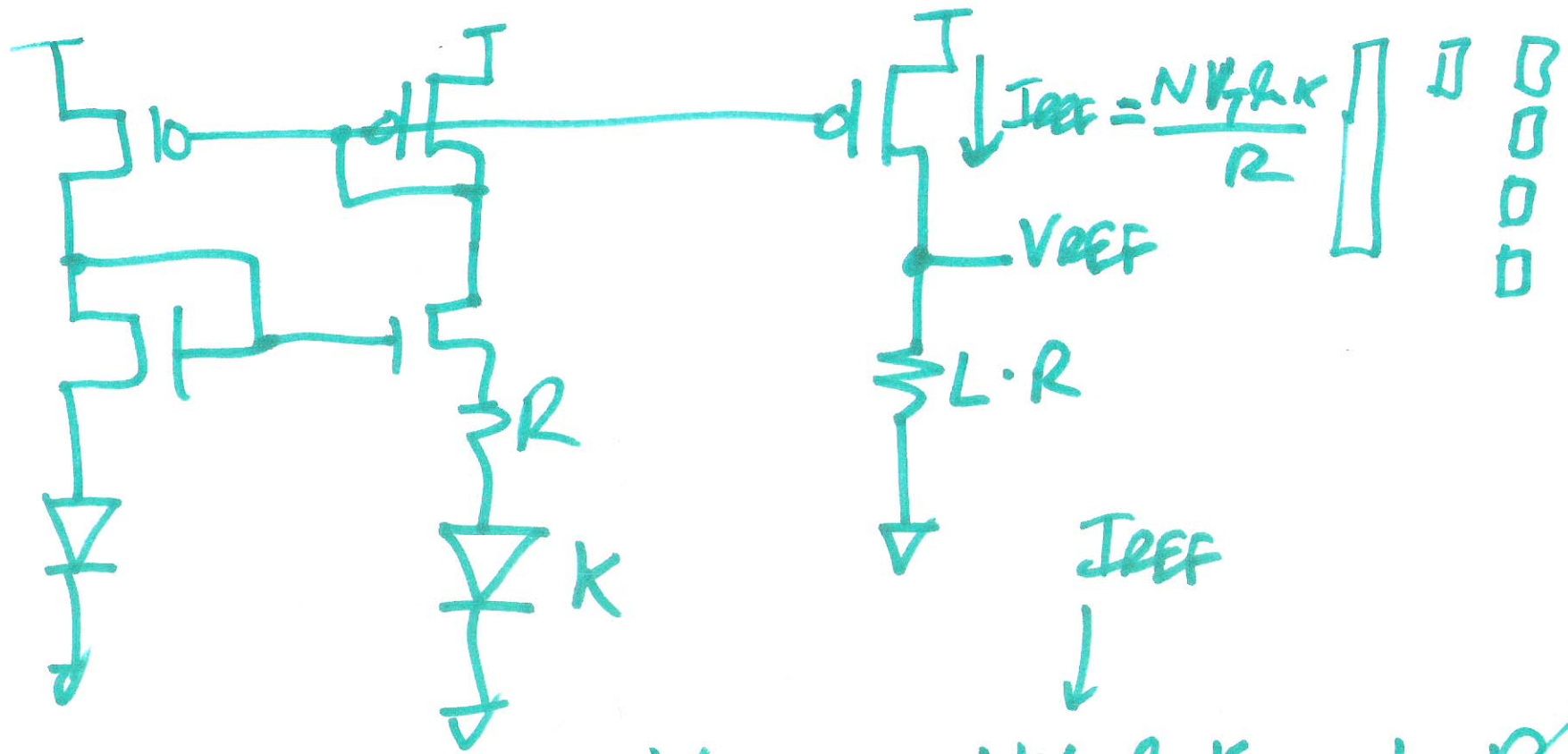

$$V_{REF} = \frac{N V_T \ln K}{\cancel{R}} \cdot L \cdot \cancel{R}$$

$$V_T = \frac{kT}{q}$$


$$\frac{\delta V_T}{\delta T} = \frac{k}{q} \quad +0.085 \text{ mV/}^\circ\text{C}$$


$$V_{REF} = N V_T (\ln K) \cdot L$$

$$V_{REF} = NV_T I_{REF} \cdot L$$

$$\frac{\delta V_{REF}}{\delta T} = N \cdot \frac{k}{q} \cdot \underbrace{L}_{K=8} \cdot \underbrace{k \cdot L}_{\downarrow}$$
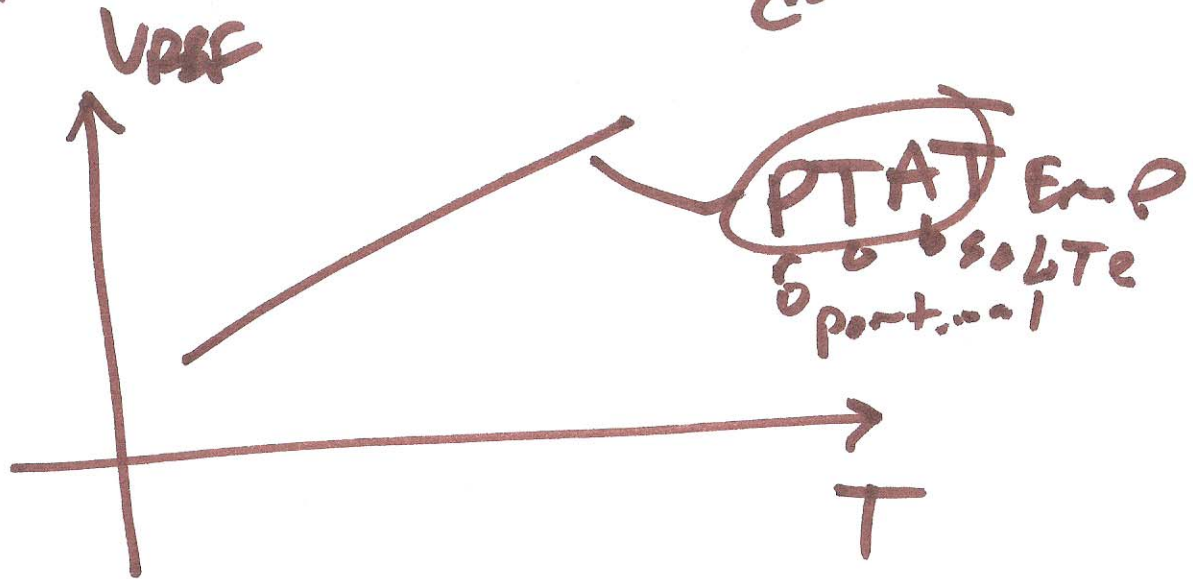
$$\frac{1}{V_{REF}} \cdot \frac{f_{VREF}}{\delta T} = \text{const} \quad \checkmark \quad +.085 \frac{\text{mV}}{^\circ\text{C}} \quad 2 \quad 10$$



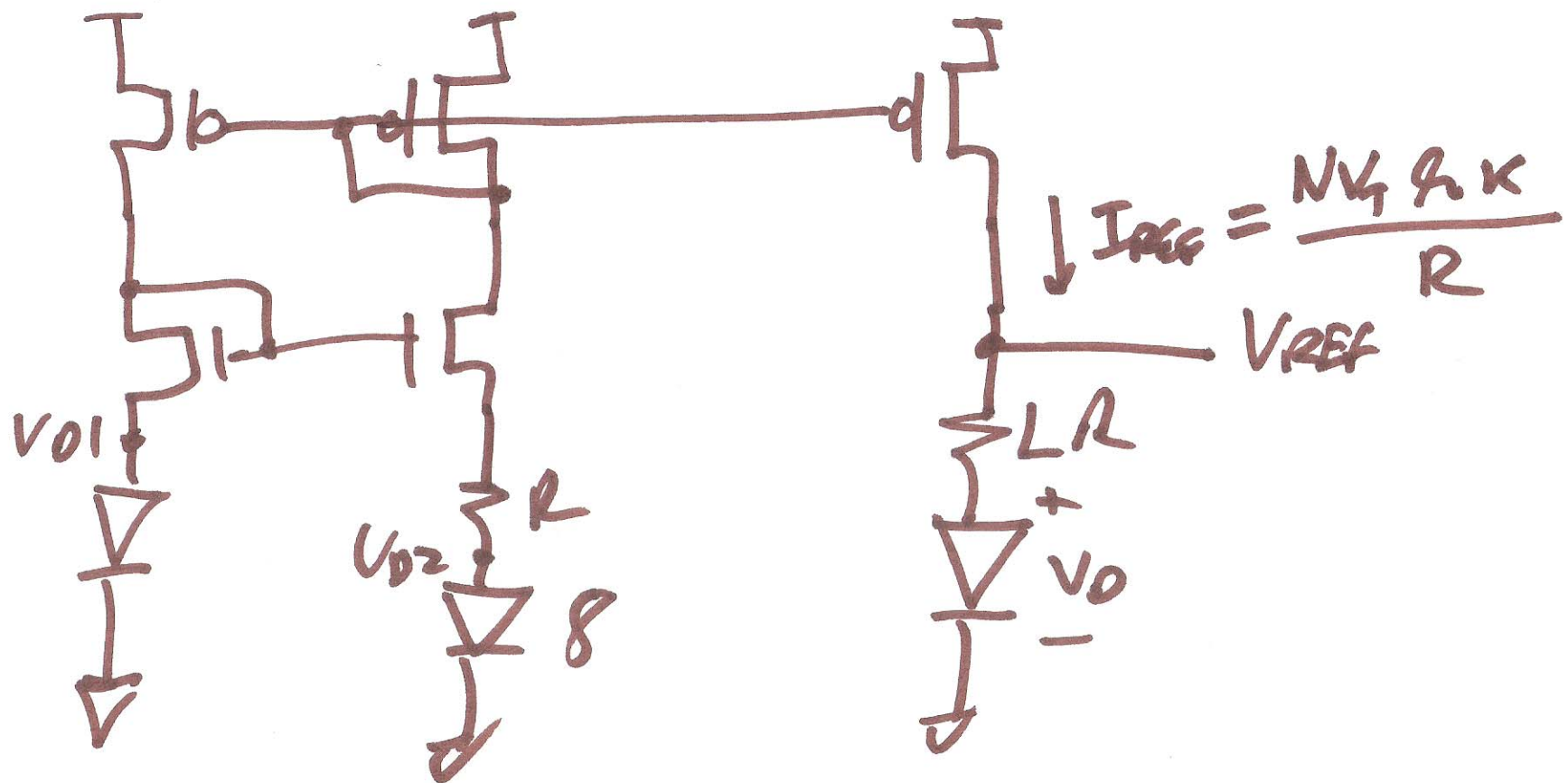


$$V_{REF} = L \cdot N V_T R K + V_D$$

$$\frac{\delta V_{REF}}{\delta T} = \frac{\delta L \cdot N \cdot V_T \ln K}{\delta T} + \frac{\delta V_D}{\delta T} = 0$$

$$L \cdot \frac{1}{9} \cdot \frac{K}{9} \cdot \frac{Q}{K} - 1.6 \frac{mV}{C^\circ} = 0$$

$+0.085 \frac{mV}{C^\circ}$
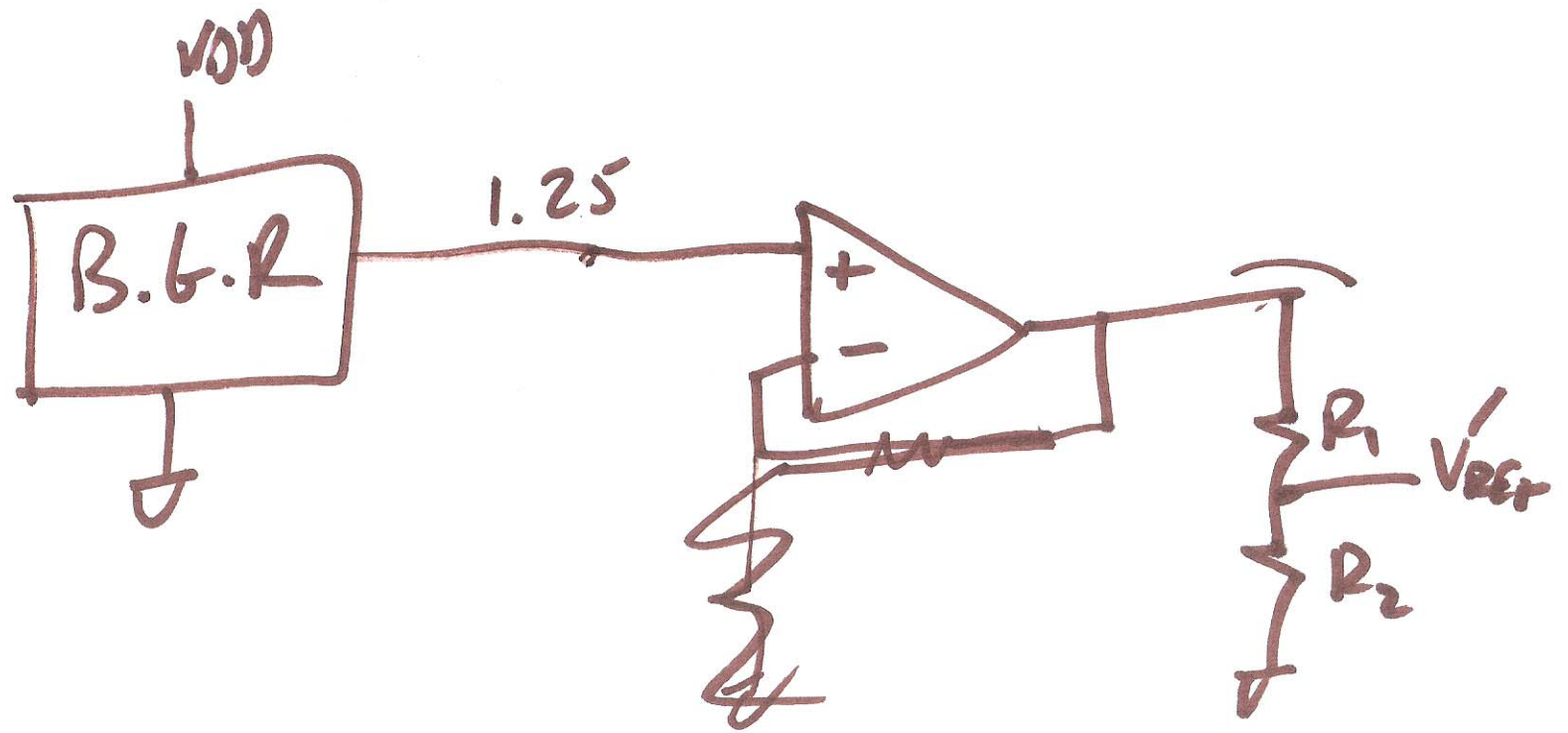
$$L = \frac{1.6 mV}{2 \cdot 0.085 mV} = \underline{\underline{9.4}}$$



$$V'_{REF} = 1.25 \cdot \frac{R_2}{R_1 + R_2} = \frac{R_2(1 + T_{CR}(T - T_0))}{(R_1 + R_2)(1 + T_{CR}(T - T_0))}$$