

Lecture 22

April 13, 2015

EE 420 / ECE 620

Analog IC Design

A23.7

$$V_{D1} = NV_T \ln \frac{KI_{REF}}{I_S}$$

$$V_{D2} = NV_T \ln \frac{I_{REF}}{I_S}$$

$$I_{REF} = \frac{V_{D1} - V_{D2}}{R} = \frac{NV_T \ln K}{R}$$

1)

$$V_{REF} = I_{REF} \cdot L R + V_{D3}$$

$$V_{REF} = L \cdot N V_T R_K + V_{D3}$$

is it a BGR? YES.

$$\frac{\delta V_{REF}}{\delta T} = L \cdot N \left(\frac{K}{T} \right) R_K + \frac{\delta V_{D3}}{\delta T}$$

$0.055 \frac{mV}{^\circ C}$

$-1.6 \frac{mV}{^\circ C}$

$$TCV_{REF} = \frac{1}{V_{REF}} \cdot \frac{\delta V_{REF}}{\delta T}$$

$$I_{REF} = R^{-1} N V_T R K = \frac{N V_T R K}{R}$$

$$\frac{\delta I_{REF}}{\delta T} = (-1) R^{-2} \frac{\delta R}{\delta T} N V_T R K +$$



$$R^{-1} N \left(\frac{K}{T} \right) R K$$

$$V_T = \frac{K T}{q}$$

$$= \left(-\frac{1}{R} \frac{\delta R}{\delta T} \right) \underbrace{\frac{N V_T R K}{R}}_{I_{REF}} + \frac{N \left(\frac{K}{T} \right) R K}{R}$$

$$\frac{1}{I_{REF}} \frac{\delta I_{REF}}{\delta T} = -\frac{1}{R} \frac{\delta R}{\delta T} + \frac{1}{T} ?$$


OP - Amp Design

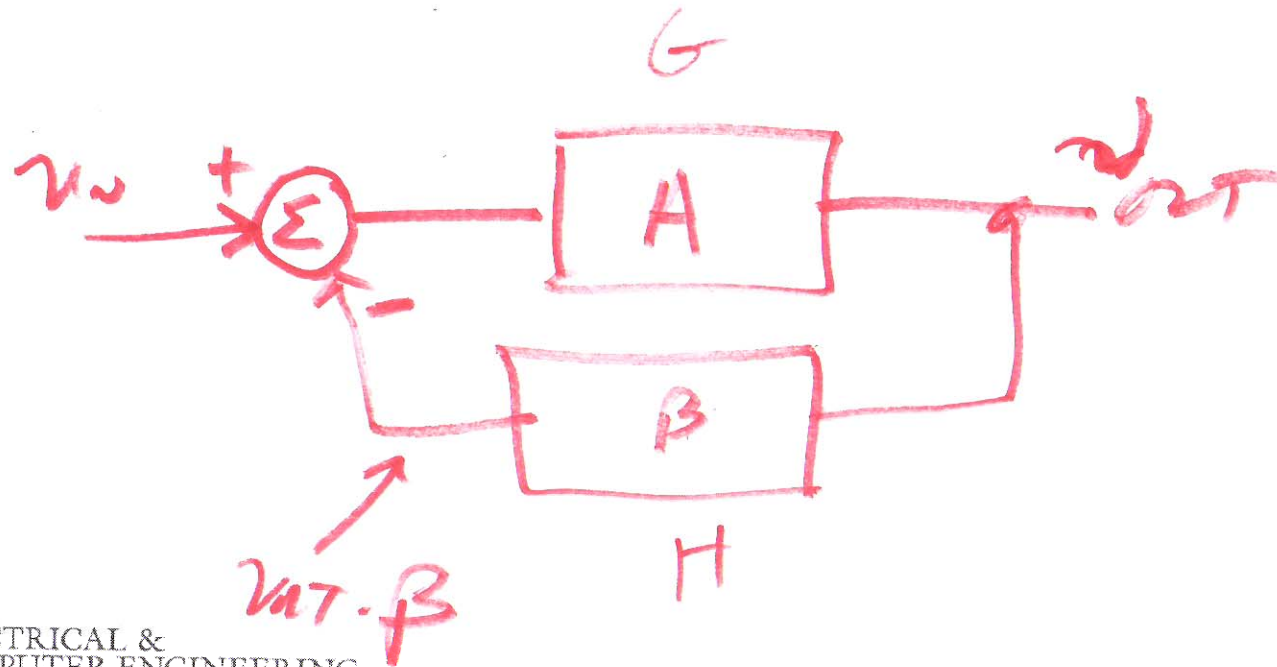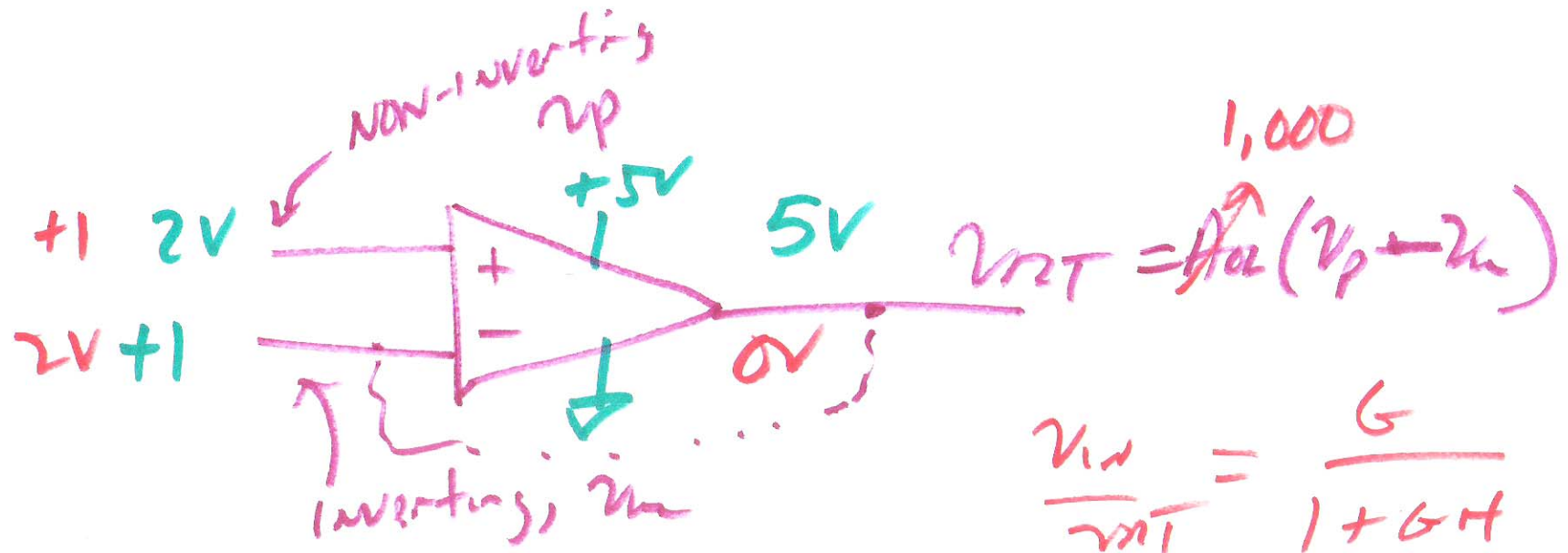

$$\frac{V_{NT}}{V_{in}} = \frac{1}{\frac{1}{A_{OL}} + \frac{1}{10^5}}$$

NON-INVERTING = $1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$

series-shunt V-V

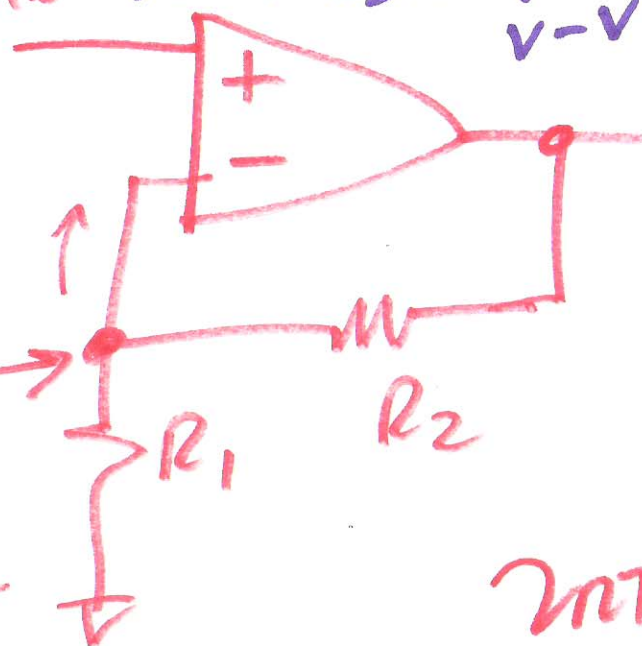

$$V_{NT} = A_{OL}(v)$$


$$(V_p - V_m)$$

$$V_f = V_{NT} \cdot \frac{R_1}{\frac{R_1 + R_2}{\beta}}$$

$$V_{NT} = A_{OL} \cdot (V_{in} - \beta V_{NT})$$

$$V_f = V_{NT} \cdot \beta$$

shunt-shunt

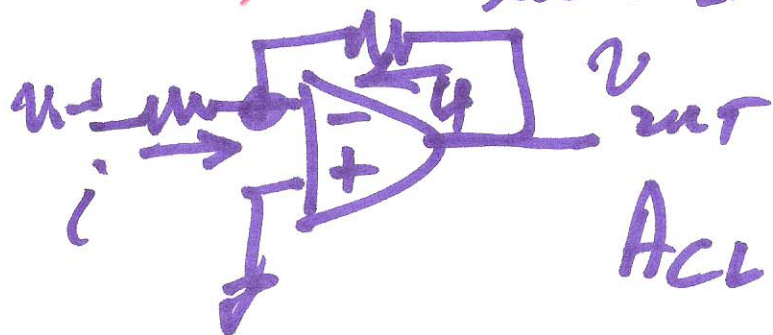

$$V_{NT} = (1 + \beta A_{OL}) = A_{OL} \cdot V_{in}$$

$$A_{CL} = \frac{V_{NT}}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}} \xrightarrow{A_{OL} \rightarrow \infty} \frac{1}{1 + \beta}$$

$$A_{CL}|_{ideal, A_{OL} = \infty} = \frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$$

CMOSedu.com

2

$$A_{CL} = \frac{v_{out}}{v_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}}$$


When UNSTABLE

$\beta = 1$ worst case

$$\beta A_{OL} = -1 \rightarrow A_{OL} = -1$$

$$|\beta A_{OL}| = 1 \quad \angle \beta A_{OL} = \pm 180^\circ$$

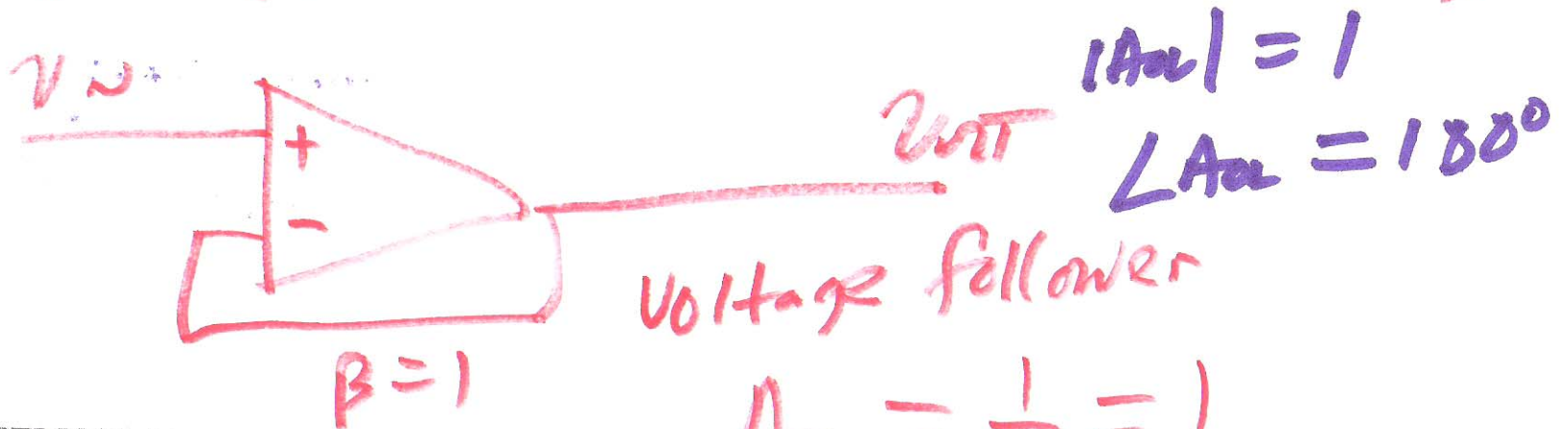$\beta = 1$ (All of the output feed back)



$$|A_{OL}| = 1$$


$$\angle A_{OL} = 180^\circ$$

$$A_{CL} = \frac{1}{\beta} = 1$$

CMOSedu.com

6)

OP-AMP

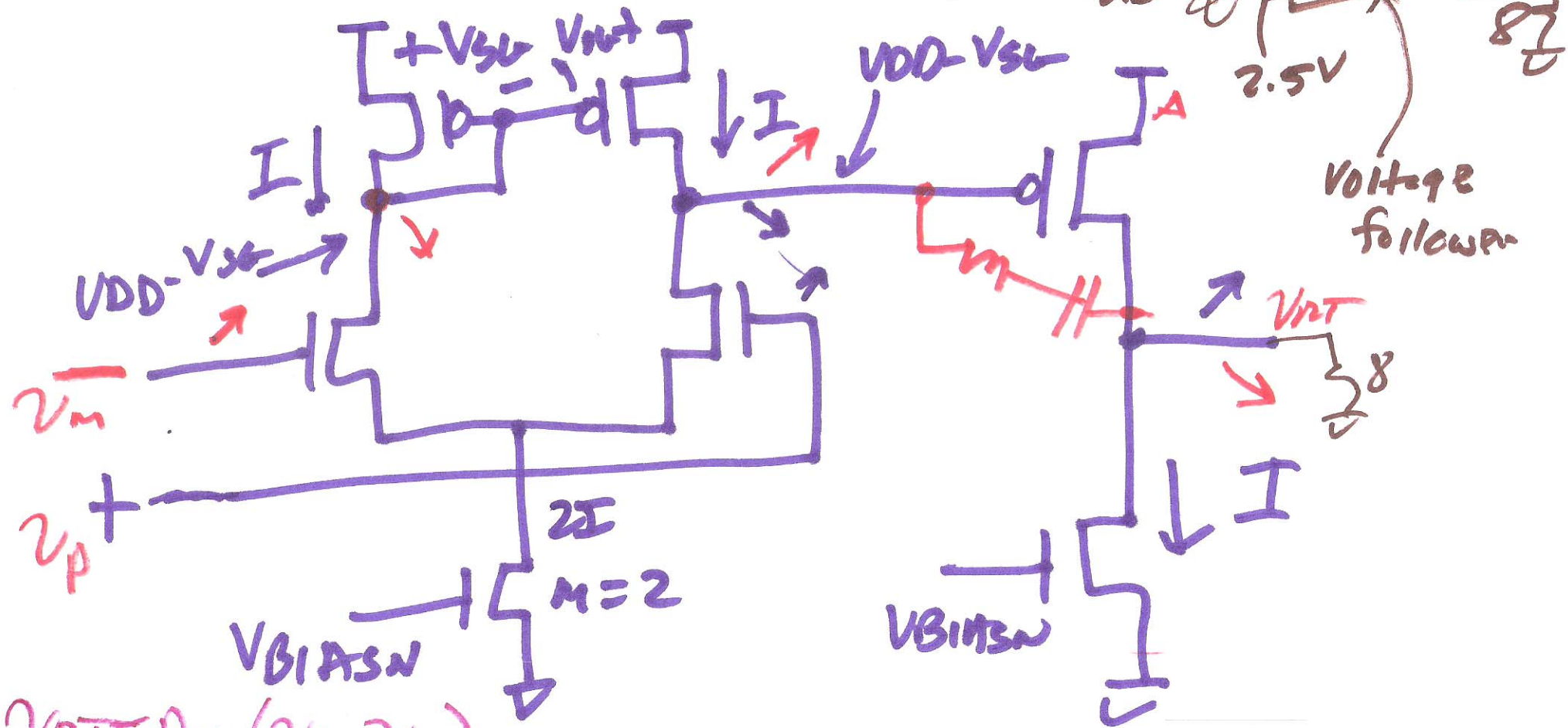

$$V_{OUT} = A_{OL}(V_p - V_m)$$

$$A_{OL} = A_d \cdot A_{cs} = \frac{V_{OUT}}{V_p - V_m} = g_{m1} r_{o1} || r_{o2} \cdot g_{m3} r_{o3}$$



UNLV | ELECTRICAL & COMPUTER ENGINEERING

