

EE 420 / ECG 620

CMOS Analog IC Design

April 22, 2015



Lecture 25

$$C_{ox}' = \frac{\epsilon_{ox}}{t_{ox}} = 3.9 \cdot 8.85 \text{ aF/nm}^2$$

$$K_{PN} = \mu_n \cdot C_{ox}'$$

$$K_{PP} = \mu_p \cdot C_{ox}'$$
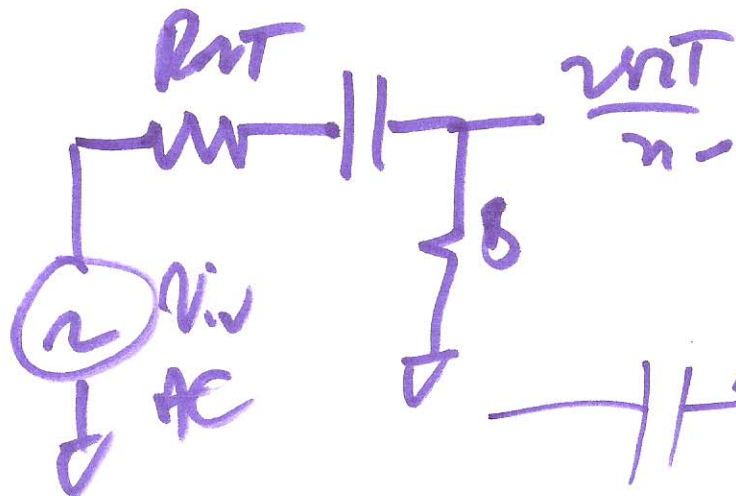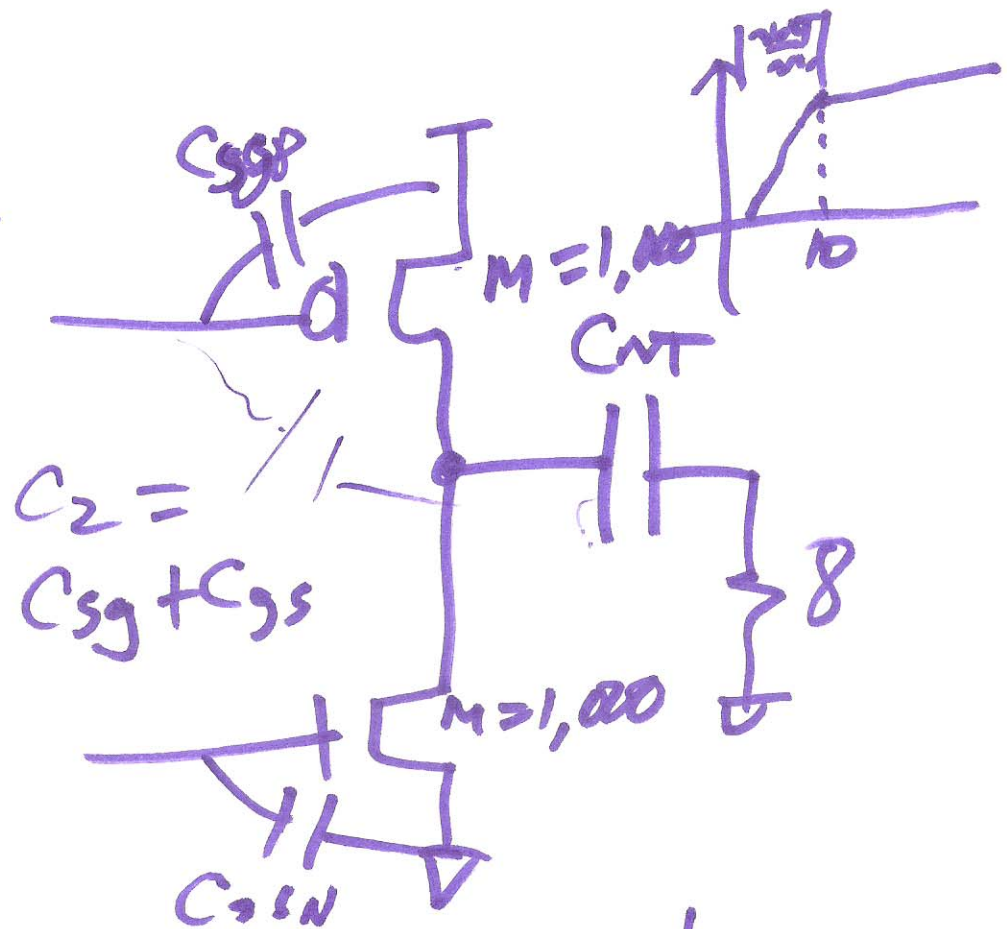
$$A_{OL} = g_{m1} \cdot R_1 \cdot g_{m2} \cdot R_2$$




$$f_{3dB} = \frac{1}{2\pi C_{in} (8 + R_{int})}$$

$R_{int} = 0$
worst
case

$$\beta = \frac{R_A}{R_A + R_B}$$



$$A_{OL} = g_{m1} \cdot R_1 \cdot g_{m2} \cdot R_2$$

$$\beta \cdot v_{inT} = v_f$$

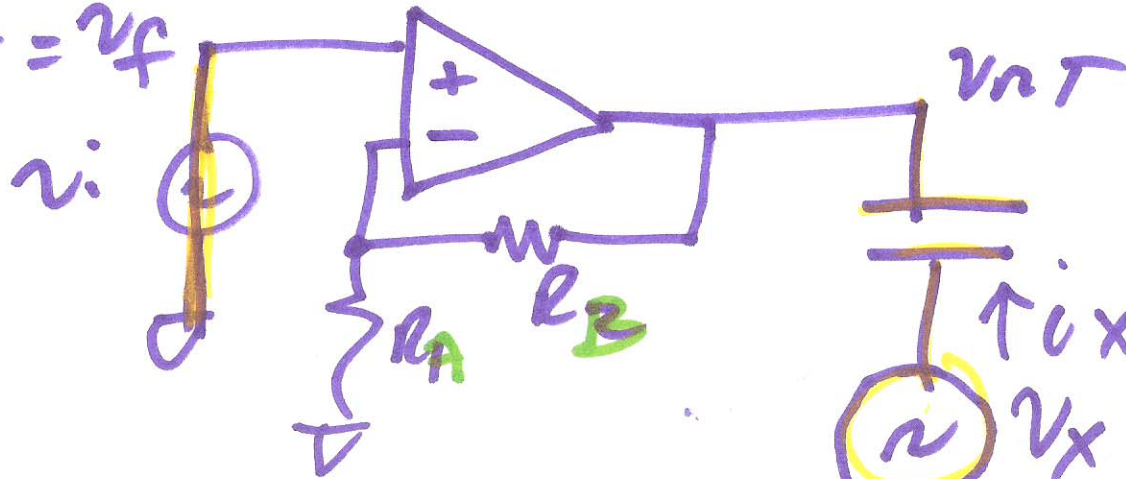

$$R_{out} = \frac{v_x}{i_x}$$

$$AC \beta \cdot v_x$$

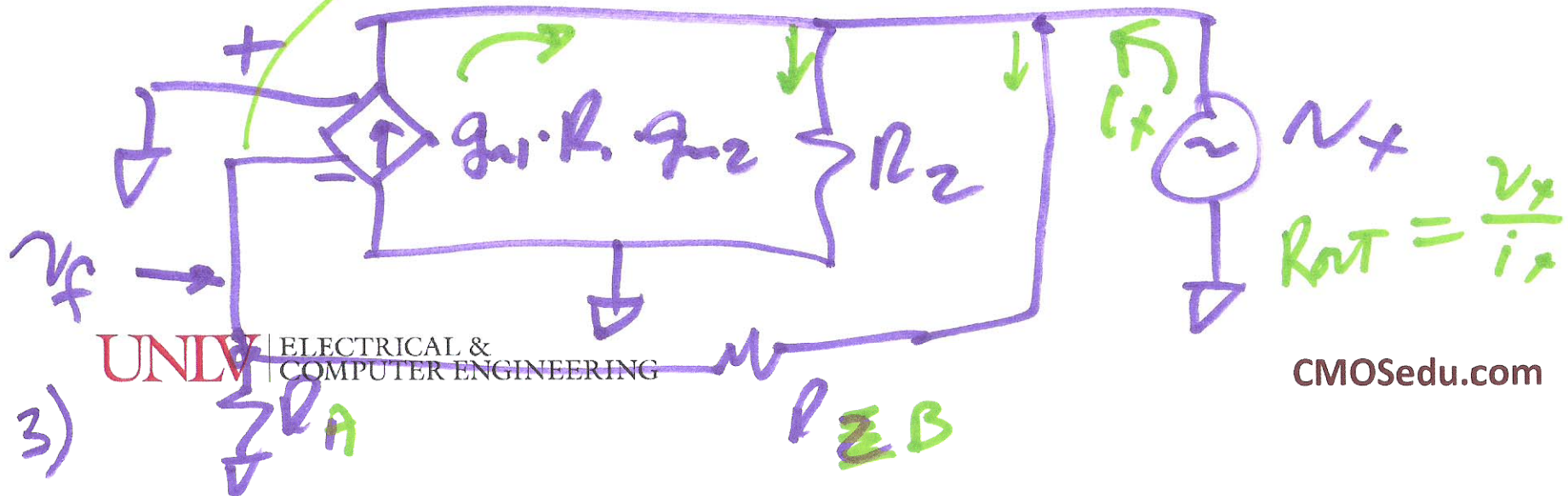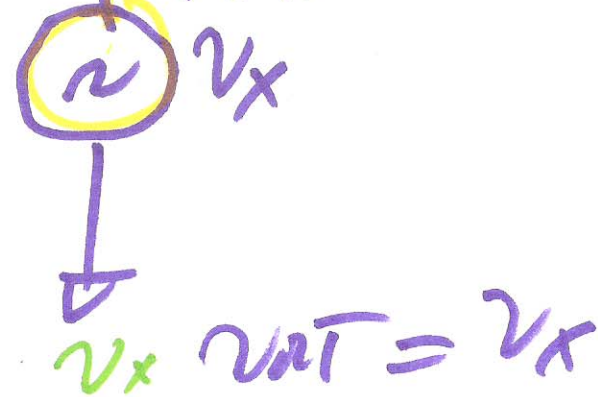

$$i_x + (0 - \beta v_x) g_{m1} \cdot R_1 \cdot g_{m2} = \frac{v_x}{R_2} + \frac{v_x}{R_A + R_B}$$

$$i_x = v_x \left(\beta g_{m1} R_1 g_{m2} + \frac{1}{R_2} + \frac{1}{R_A + R_B} \right)$$

$$R_2 i_x = v_x \left(\beta A_{OL} + 1 + \frac{R_2}{R_A + R_B} \right)$$

$$\frac{v_x}{i_x} = \frac{R_2}{1 + \beta A_{OL} + \frac{R_2}{R_A + R_B}}$$

$$\approx \frac{1}{g_{m1} \cdot R_1 \cdot g_{m2}}$$

4)

