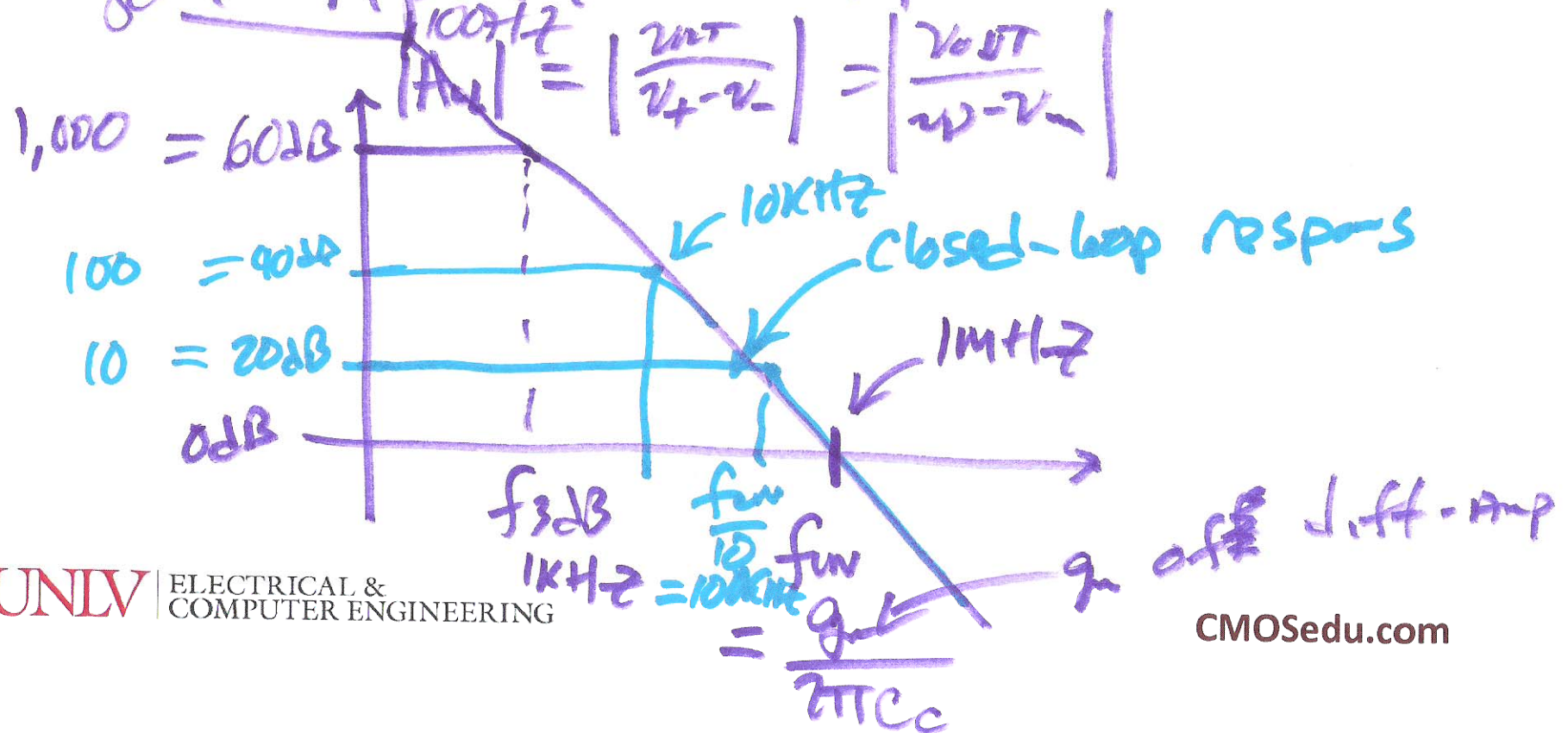



EE 420 / ECG 620

Analog IC Design

Lecture 26

802B April 27, 2015



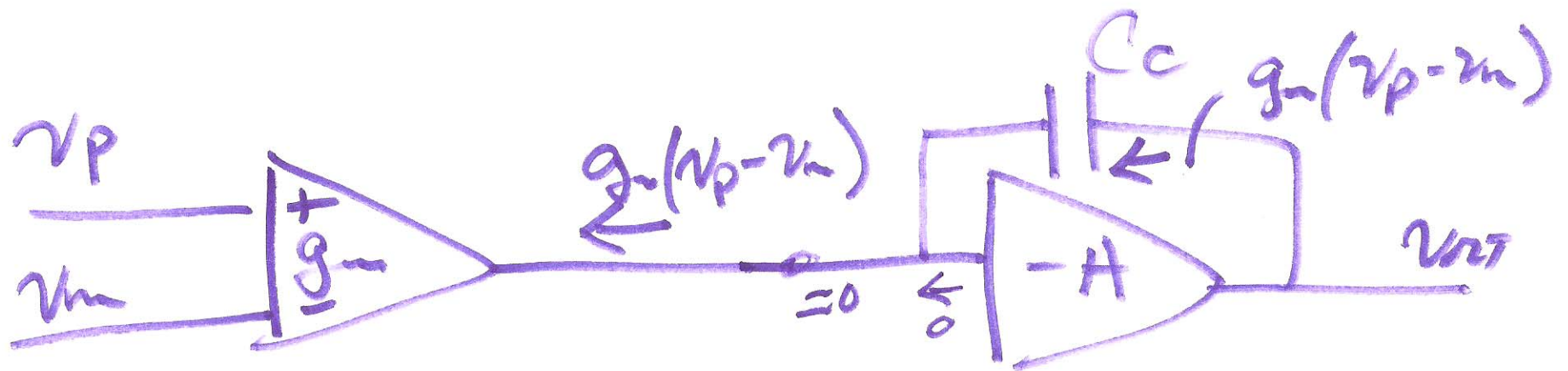


$$v_{out} = \frac{1}{j\omega C_c} g_m (v_p - v_m)$$

$$f_{un} = \frac{g_m}{2\pi C_c}$$

$$\left| \frac{v_{out}}{v_p - v_m} \right| = \left| \frac{g_m}{j \cdot \omega_c C_c} \right| = 1$$
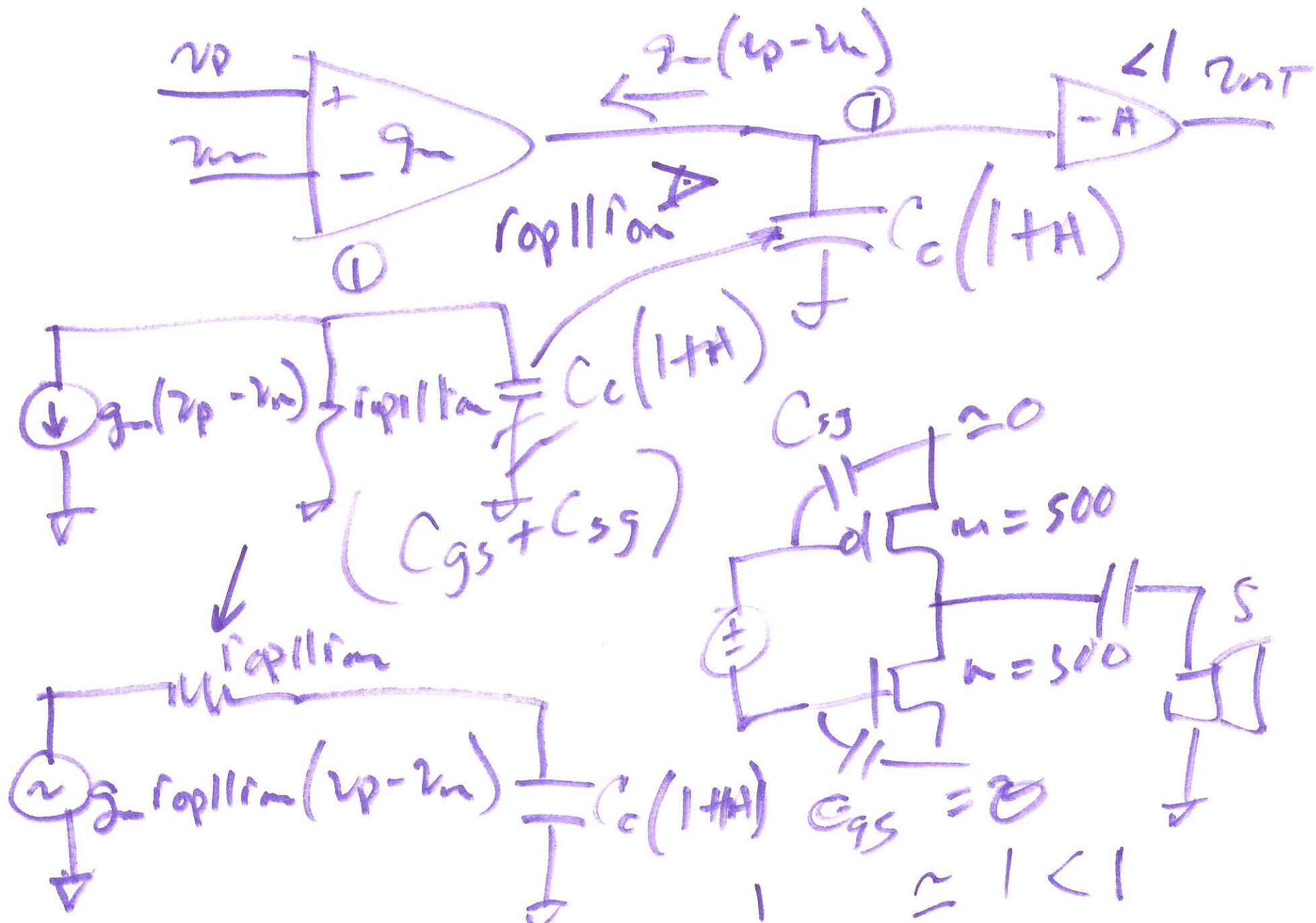
$$\frac{g_m}{2\pi f_{un} \cdot C_c} = 1$$



$$f_{3dB} = \frac{1}{2\pi r_{o||r_a} C_c (1+A)}$$

$$A_{CL}(s) \frac{v_{OUT}}{v_p - v_m} = \frac{g_{m1} \cdot R_1 \cdot g_{m2} \cdot R_2}{1 + j \frac{f}{f_1}}$$

$$10^3 = 10 \text{ kHz}$$

$$A_{CL} = 200, f_{GLBW} = \frac{10 \text{ kHz}}{200} = 50 \text{ kHz}$$

$$A_{OL}(s) = \frac{A_{OL}}{1 + j \frac{f}{f_{3dB}}} = \frac{10^3}{1 + j \frac{f}{10^3}}$$

$$f \gg 1 \text{ kHz}$$

Gain BW

$$f_{BW} = A_{OL} \cdot f_{3dB}$$


$$\frac{10^3 \cdot 10^4}{j \cdot \frac{f_{BW}}{10^3} \cdot 10^2} \approx 1$$

$f_{BW} = 10^6$


$L \rightarrow 2 \text{ to } 5$


$$\frac{W}{L} = 5$$
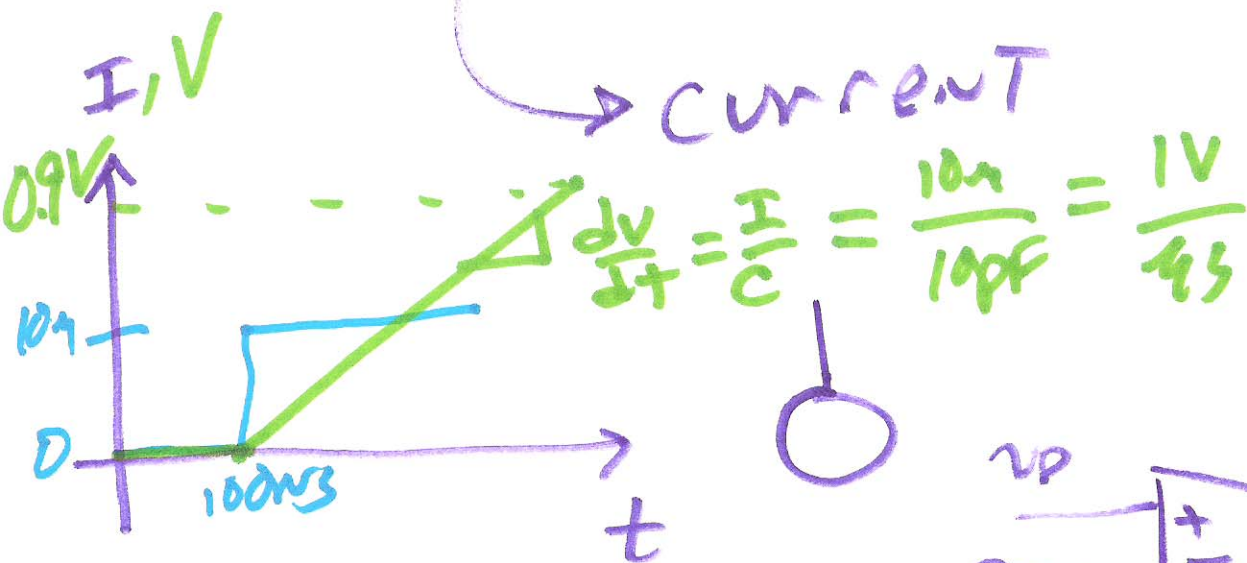
$$V_{ov} = 100\text{mV} = V_{DS, \text{SAT}} = V_{GS} - V_{TH}$$


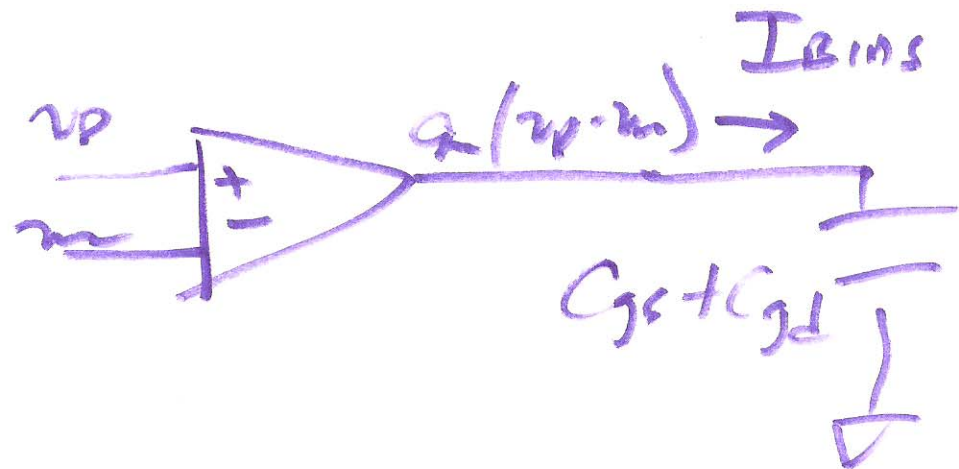
$$\frac{dV}{dt} = \frac{I_{\text{BINS}}}{C_{gs} + C_{gd}}$$



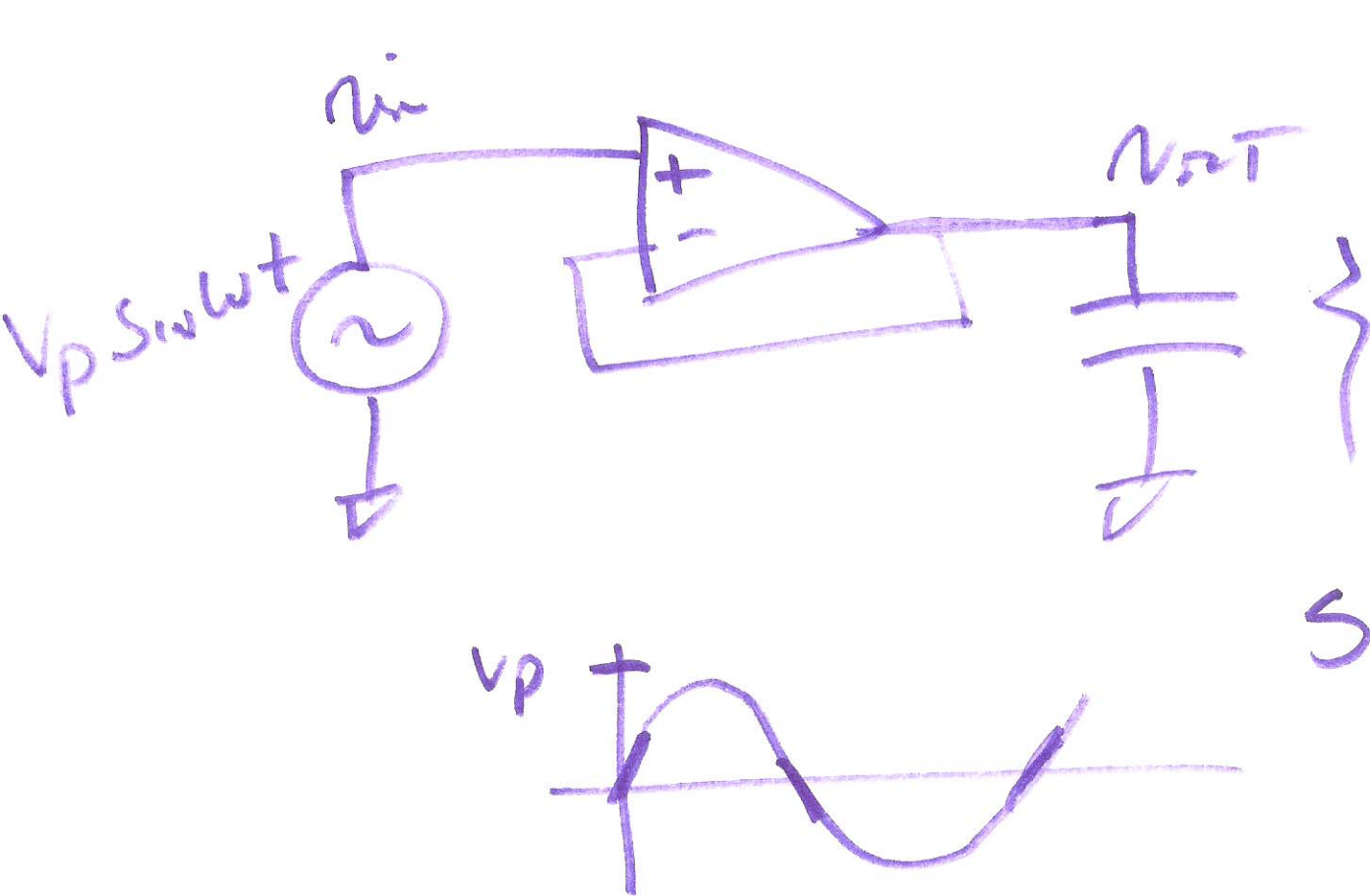

$$\frac{2V}{8} = I$$


$$SR|_{\max} = V_p 2\pi \cdot f$$


$$= \frac{I_{B115}}{C_{gs} + C_{gd}}$$

$$\frac{d}{dt} V_p \sin 2\pi f \cdot t$$

$$= V_p \cdot 2\pi f \cdot \cos 2\pi f t$$

max SR

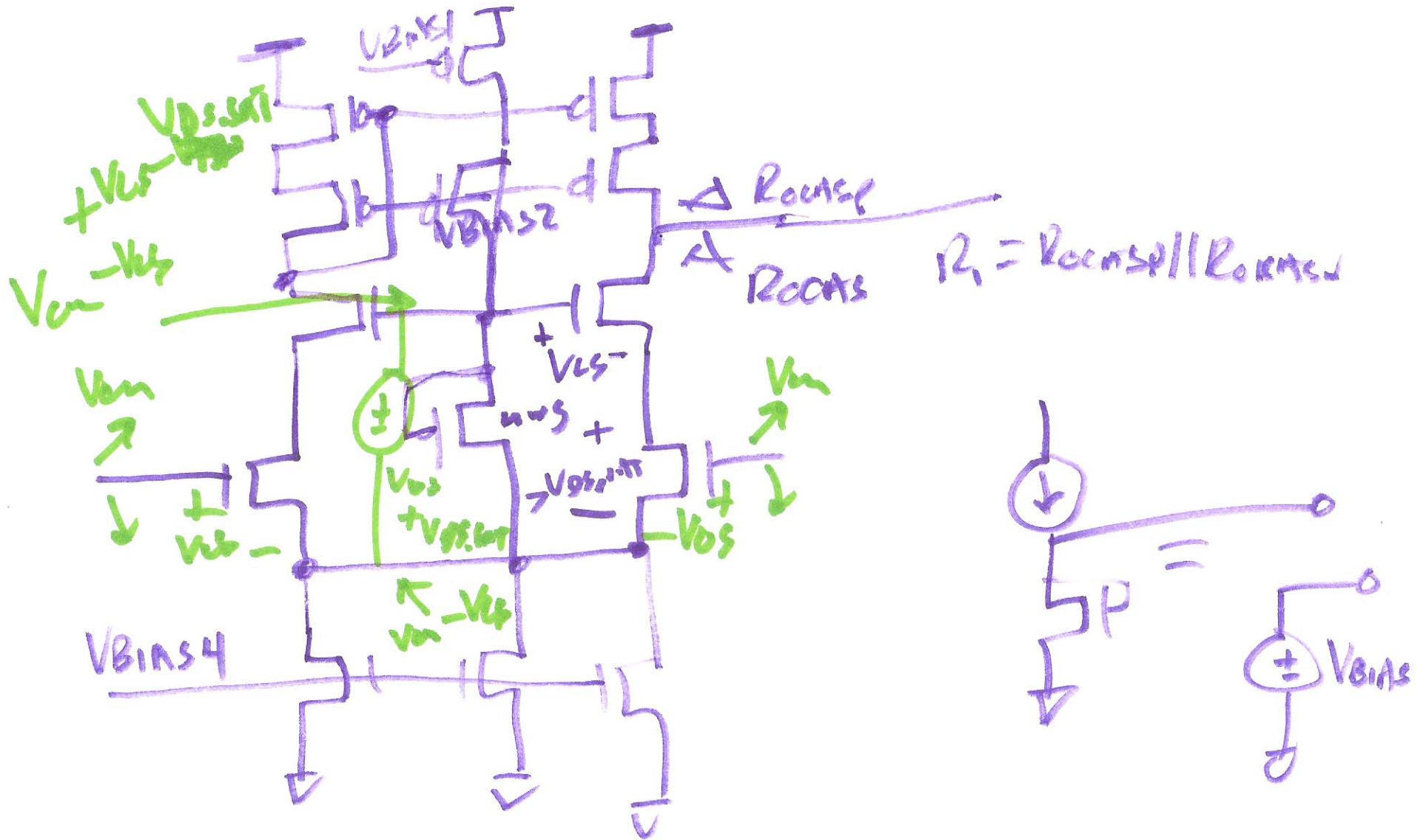


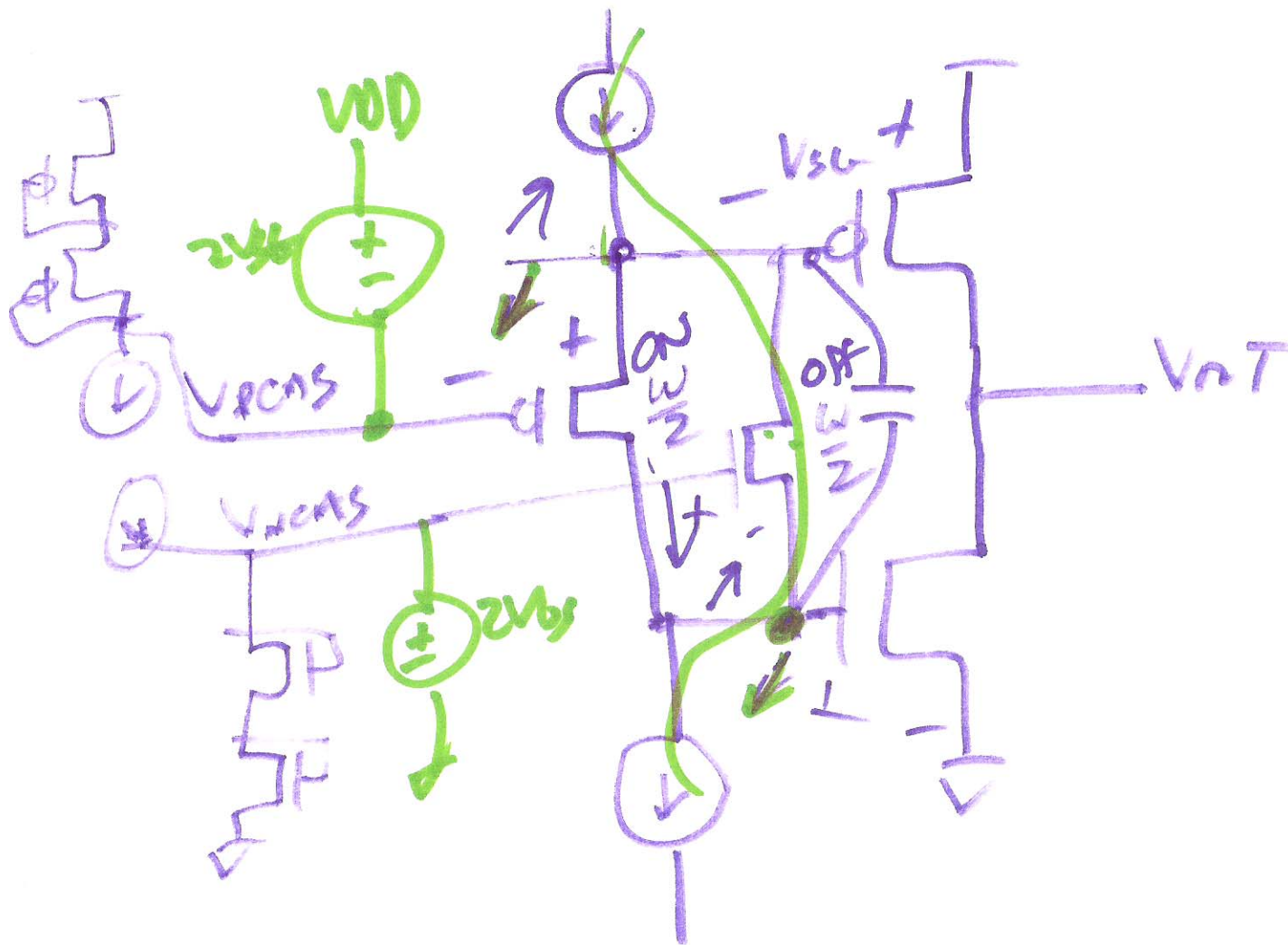

OTA - Operational

transconductance

two high impedance nodes ^{Amplifier}

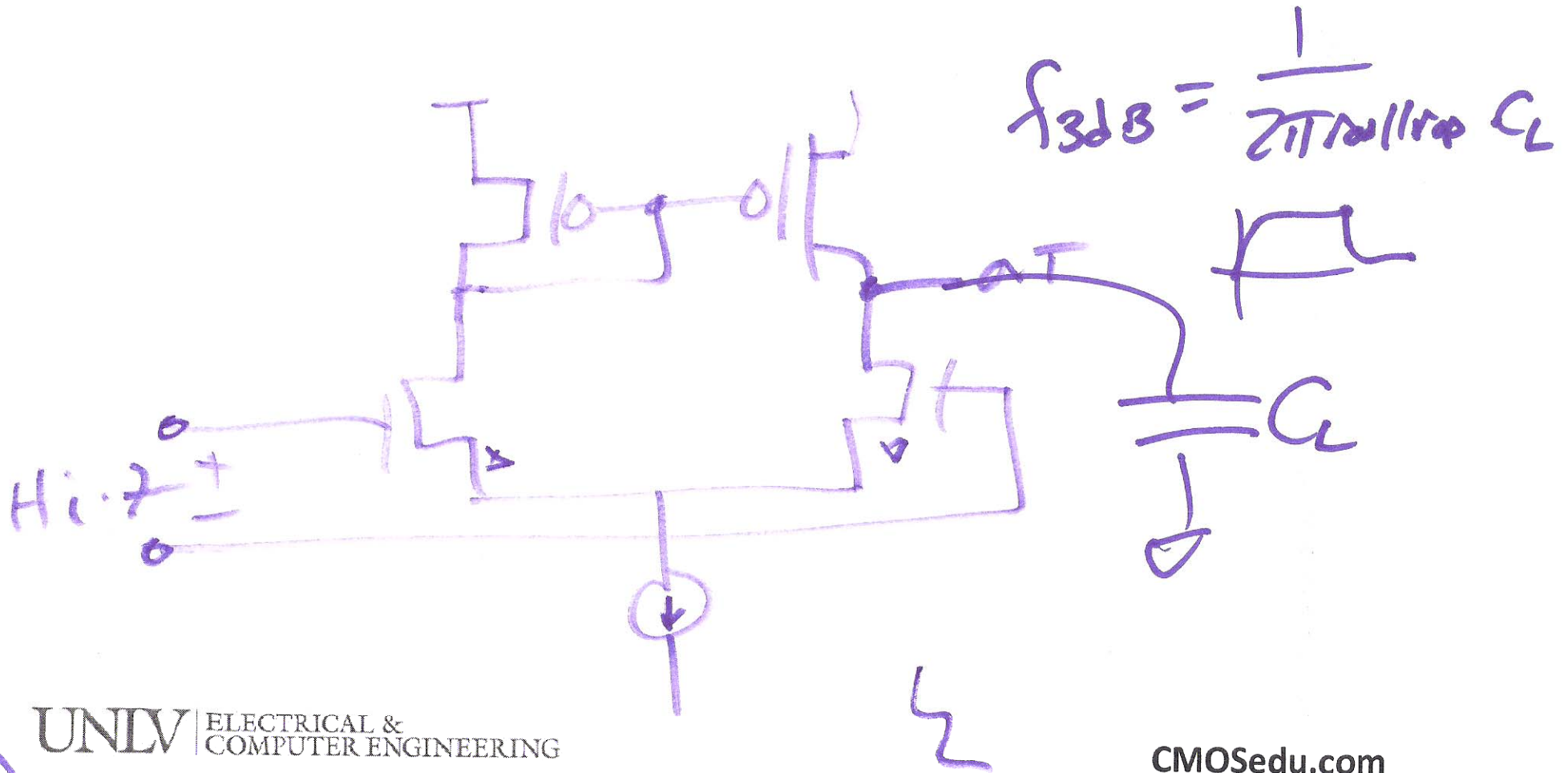

10)