

EE 420 / ECG 620

Analog IC Design

May 6, 2015

Lecture 29


Review for final

1 to 3 pm

Monday May 11, 2015

study for the final

→ H.W. & Quizzes ←

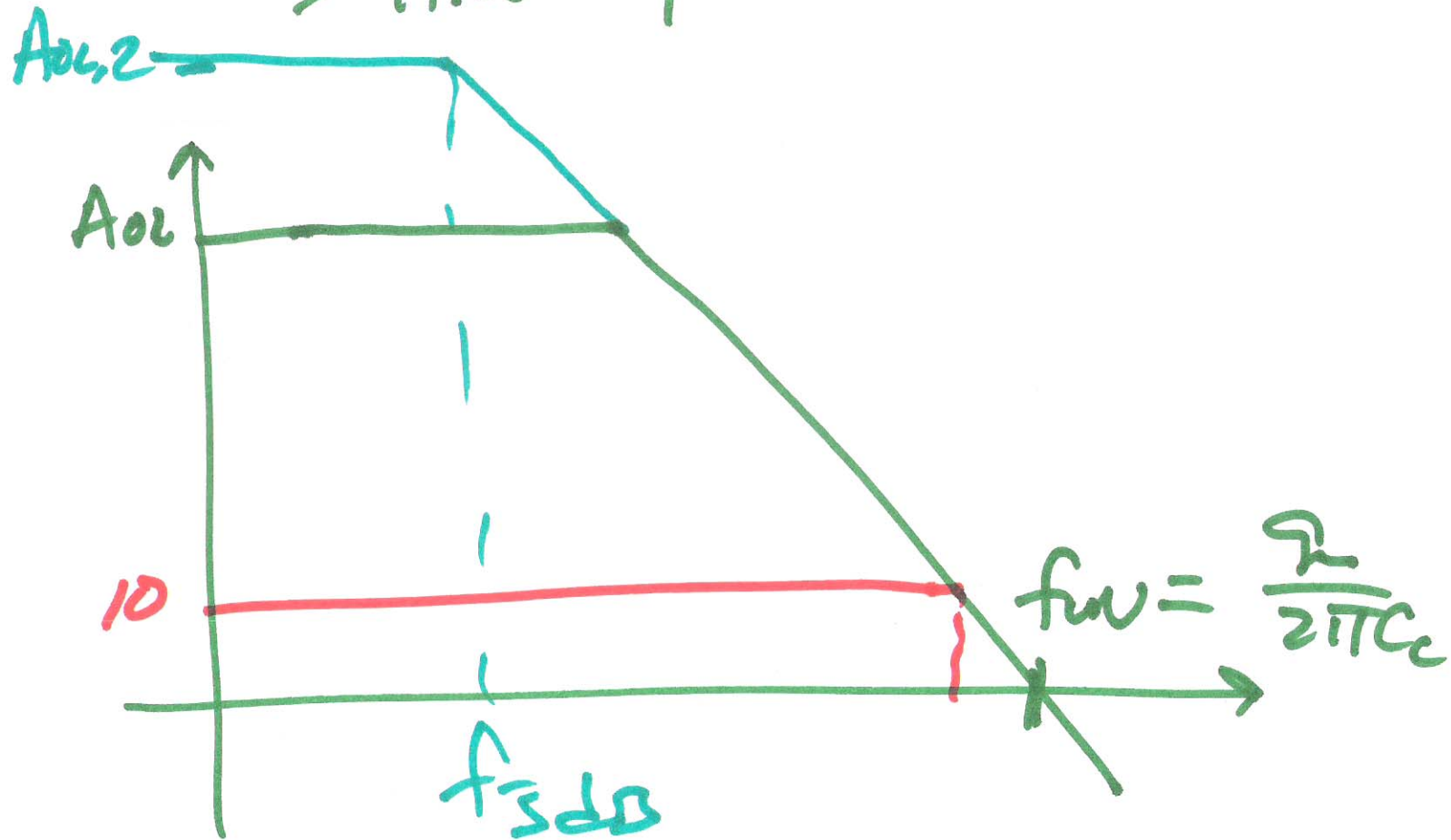

Ch. 9 →

EX 9.5

width — current


Length — speed, gain

overdrive — speed

output swing


f_T

Ch. 20 → current mirrors

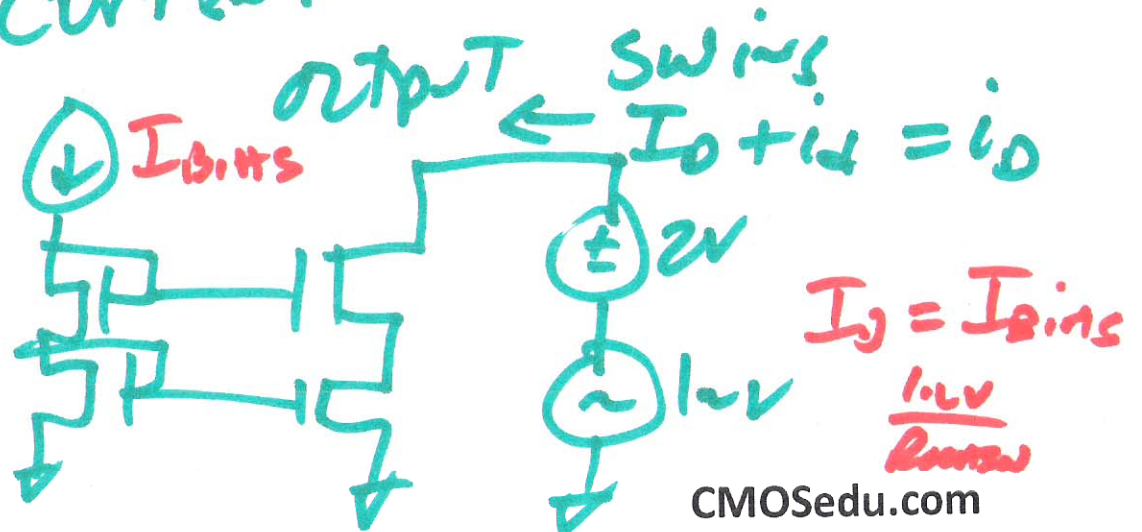

CMOSedu.com


Regulated Drain topology

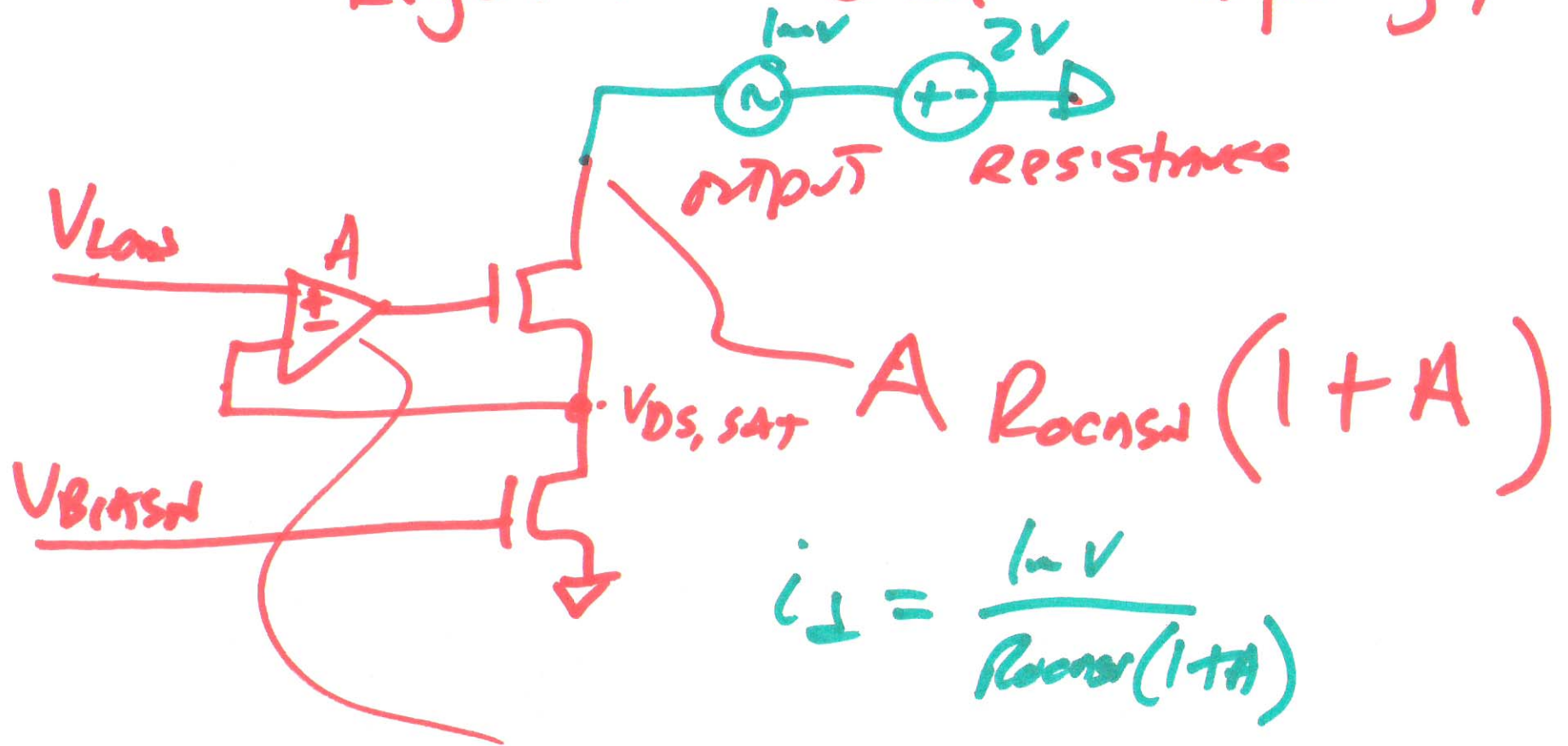


Ch. 21 Amplifiers

derive g

Gains for C.S., C.D., C.G.

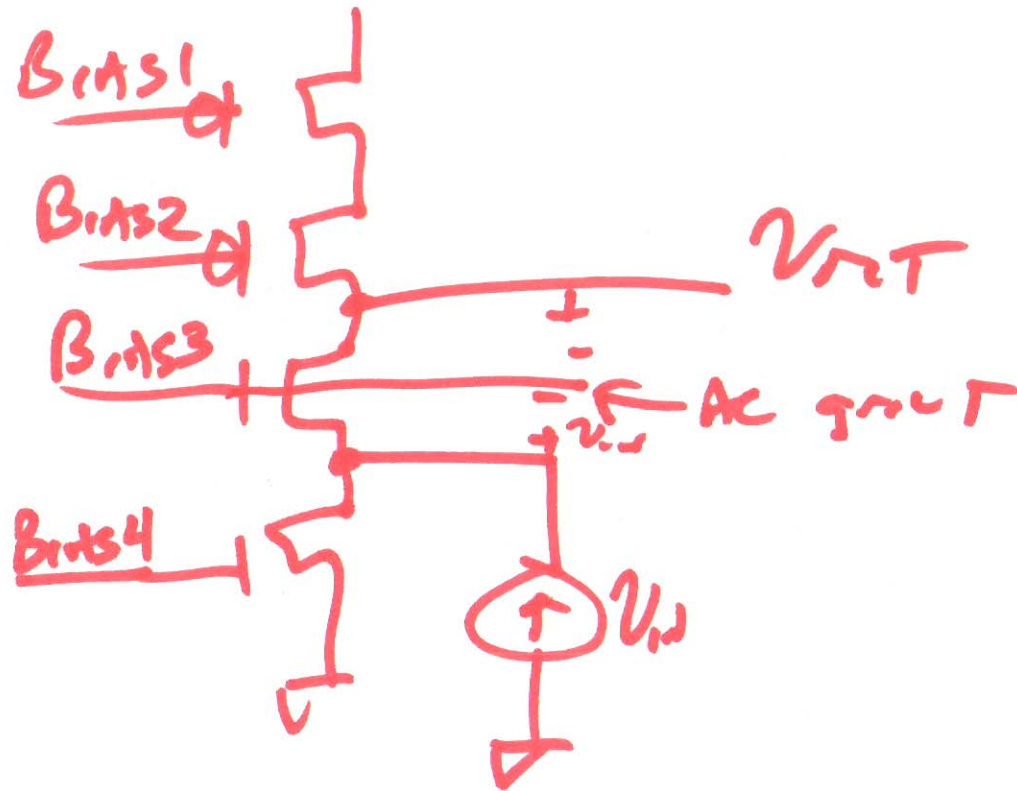

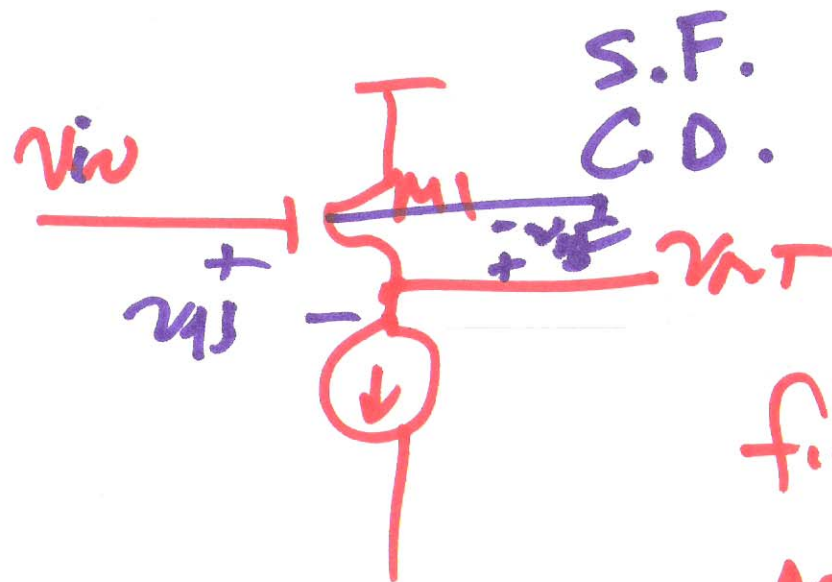


$$V_{gs} = v_w - v_{nt}$$


$$V_{sb} = v_{nt}$$

find $\frac{v_{out}}{v_w}$

NOT M_1 has body effect.

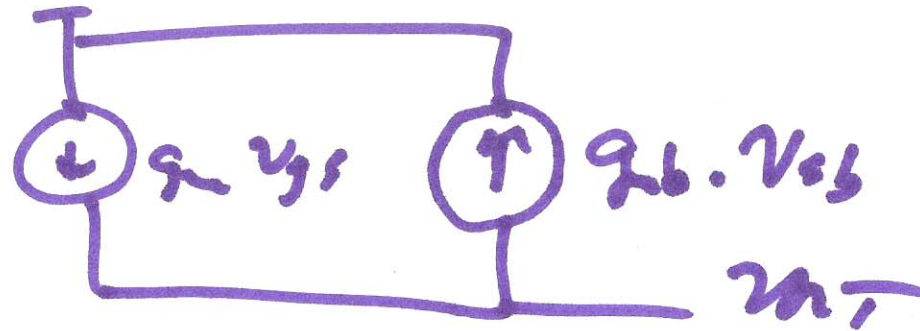

b)

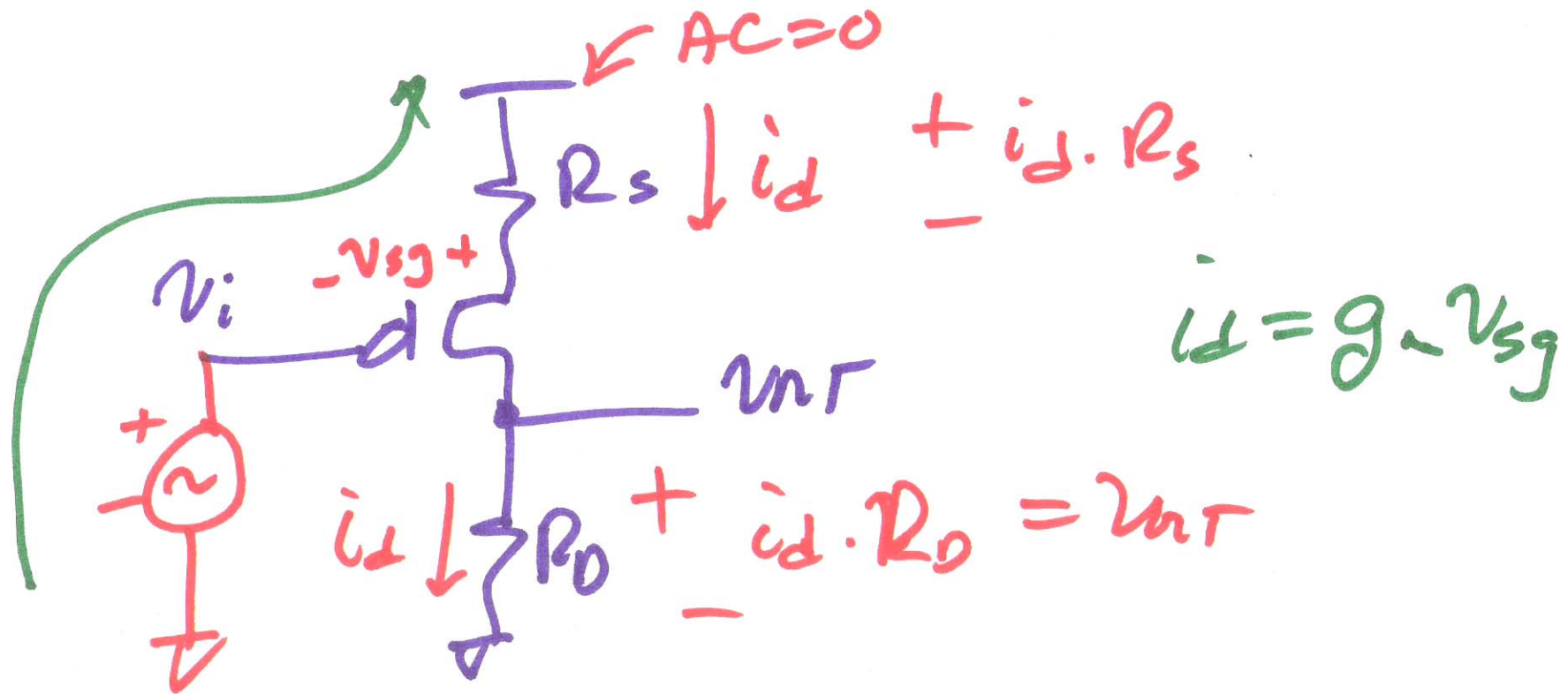


$$v_i + v_{sg} + i_d \cdot R_s = 0$$

$$v_i = -i_d \left(\frac{1}{g_m} + R_s \right)$$

$$\frac{v_{DS}}{v_i} = \frac{-R_D}{\frac{1}{g_m} + R_s}$$

Diff - Amps $V_{NT-} = -G_2 \cdot R_2$

$$V_{NT-} = -U_2 \cdot R_2$$

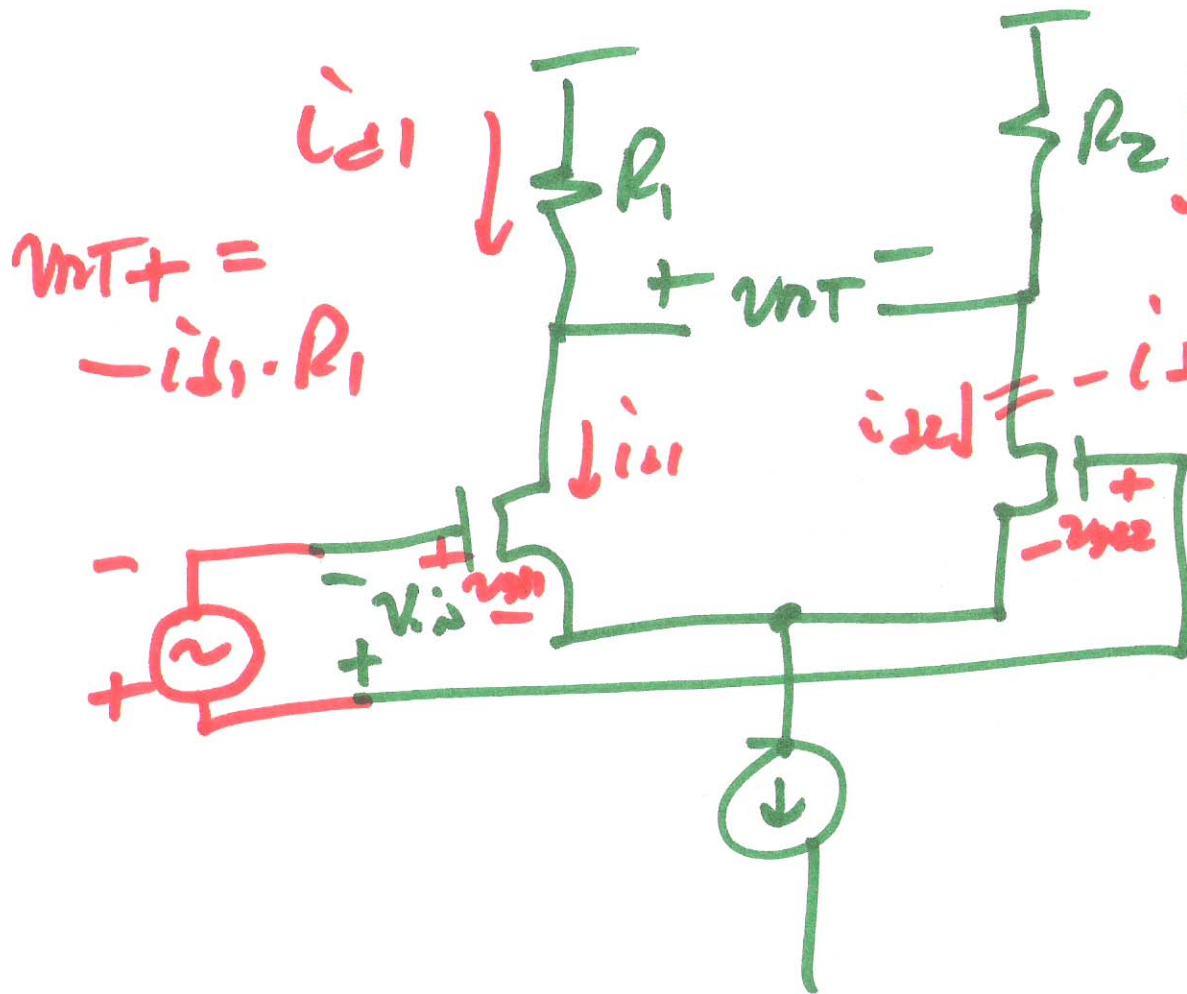


$$\frac{v_{NT}}{v_{in}} = \frac{-i_{d1} \cdot R_1 + i_{d2} \cdot R_2}{v_{gs} \cdot (-i_{d1} \cdot R_1 + i_{d2} \cdot R_2)}$$

$$V_{IN} = V_{GS2} - V_{GS1}$$

$$= \frac{122}{9} - \frac{121}{9}$$

$$-V_{in} - V_{gs1} + V_{gs2} = 0 \quad V_{gs2} = -V_{gs1} - V_{in} = -i\omega C_1 \cdot \frac{2}{g_m}$$

freq. Response $1+j0$

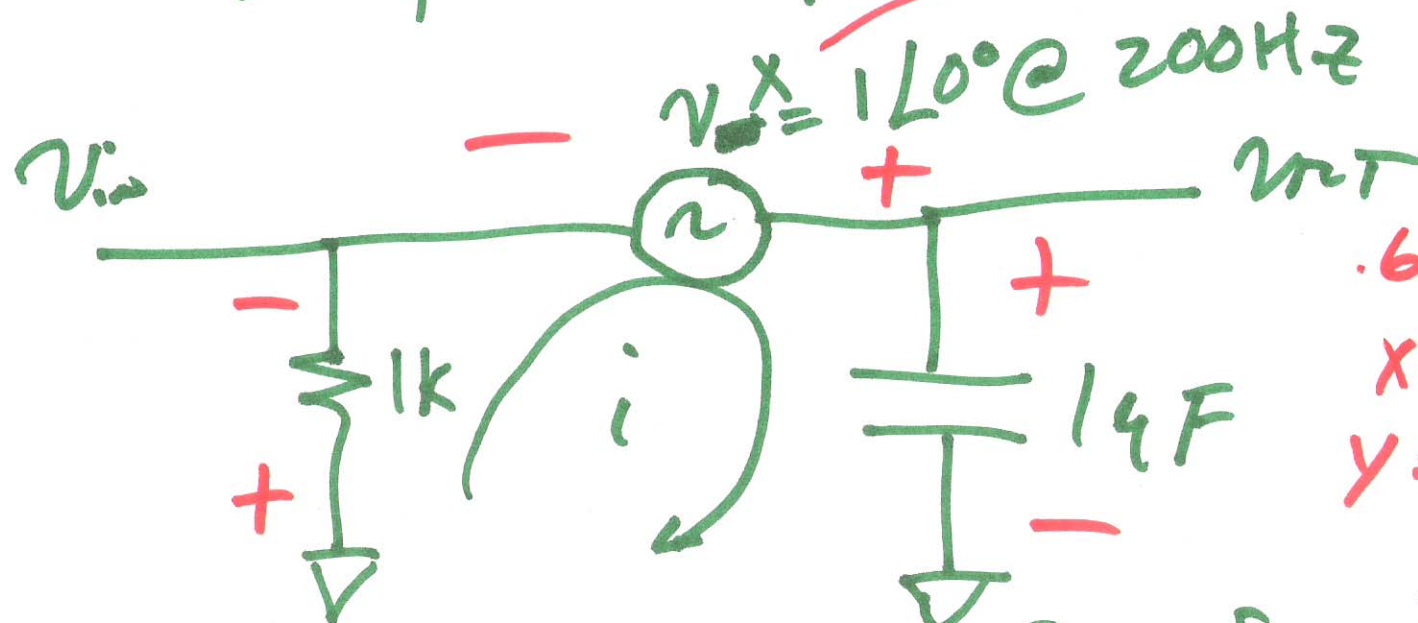

$$\begin{aligned} &.6 \angle -45^\circ \\ &x = .6 \cos(-45^\circ) \\ &y = .6 \sin(-45^\circ) \end{aligned}$$

$$v_{in} = ? \quad v_{out} = ? \quad \phi = ?$$

$$-i \cdot 1k + v_x - v_{out} = 0$$

$$-i \cdot 1k + 1\angle 0^\circ - i \cdot \frac{1}{j\omega C} = 0$$

$$v_{out} = i \cdot \frac{1}{j\omega C}$$

$$i(1k + \frac{1}{j\omega c}) = 1 + j0$$

$$i = \frac{1 + j0}{1k + \frac{1}{j\omega c}}$$

$$= \frac{0 + j\omega c}{1 + j\omega c \cdot 10^3}$$

$$= \frac{0 + j2\pi f \cdot 10^{-6}}{1 + j2\pi f \cdot 10^{-3}}, C = 10^{-6}$$

$$L = \tan^{-1}(\infty) = 90^\circ$$

$$- \tan^{-1} 2\pi f \cdot 10^{-3}$$

$$|i| = \frac{\sqrt{0 + (2\pi \cdot 200 \cdot 10^{-6})^2}}{\sqrt{1^2 + (2\pi \cdot 200 \cdot 10^{-3})^2}}$$

$$f = 200 \text{ Hz}$$

10)

Pole - splitting Miller's Theorem

$$\begin{array}{ccccc} R_1 & C_1 & C_2 & R_2 \\ \omega_{n1} & & & \omega_{n2} \\ f_1 & & & f_2 \end{array}$$

Op-Amp $\rightarrow$ design