
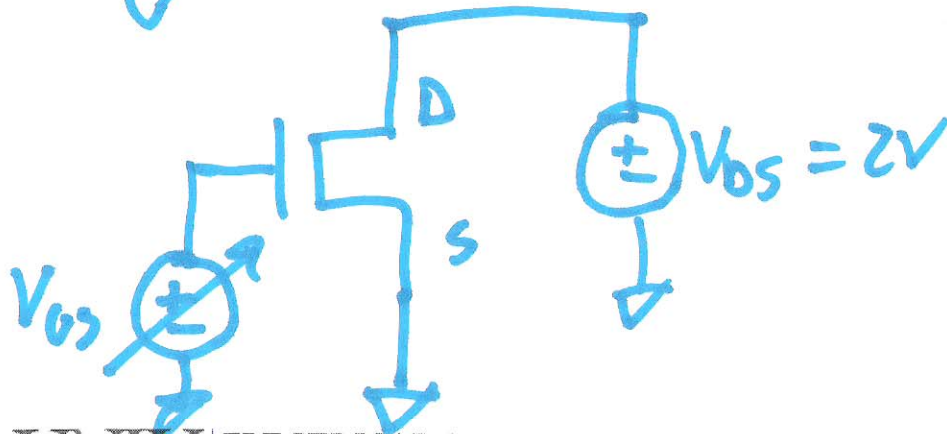



EE 420/ECG 620

Lecture 2

January 23, 2015

Square-law Equations

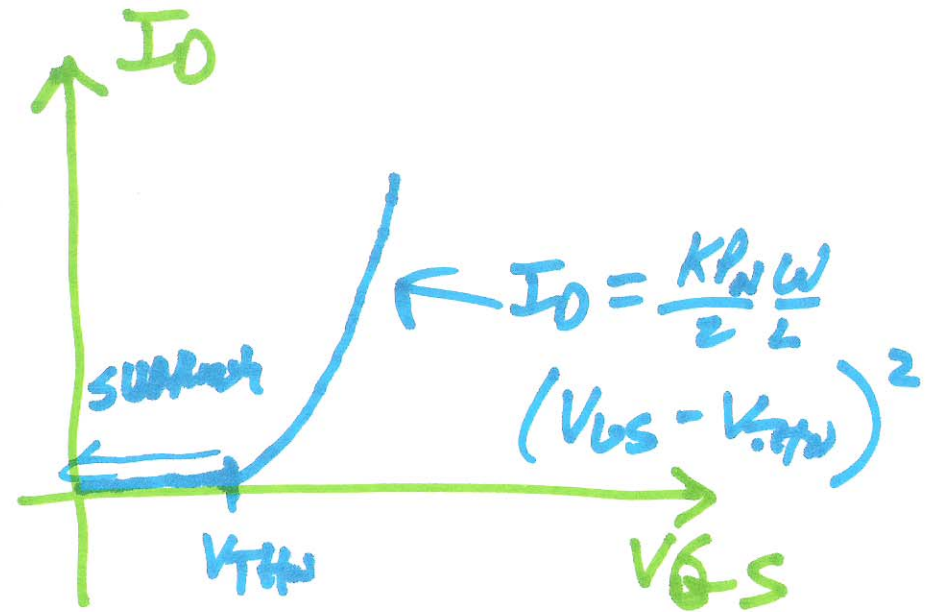

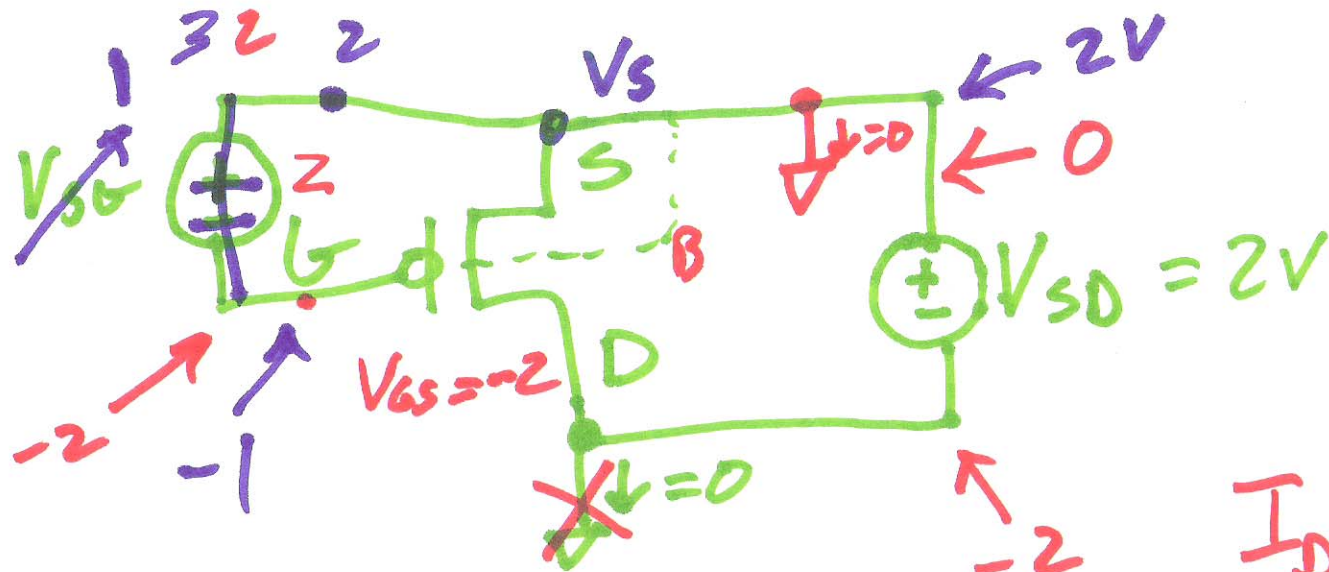



$$V_D - V_S = V_{DS}$$

$$V_{SD}$$



$$V_S - V_D = 2$$


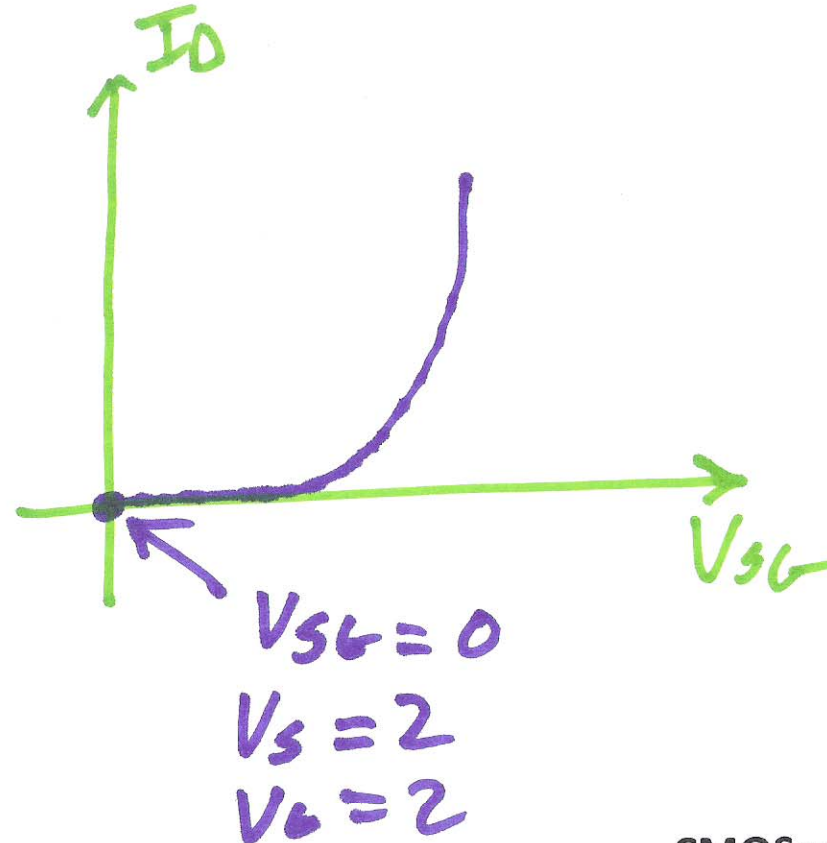
$$I_D = \frac{K_P}{2} \frac{W}{L} (V_{SG} - V_{TH})^2$$



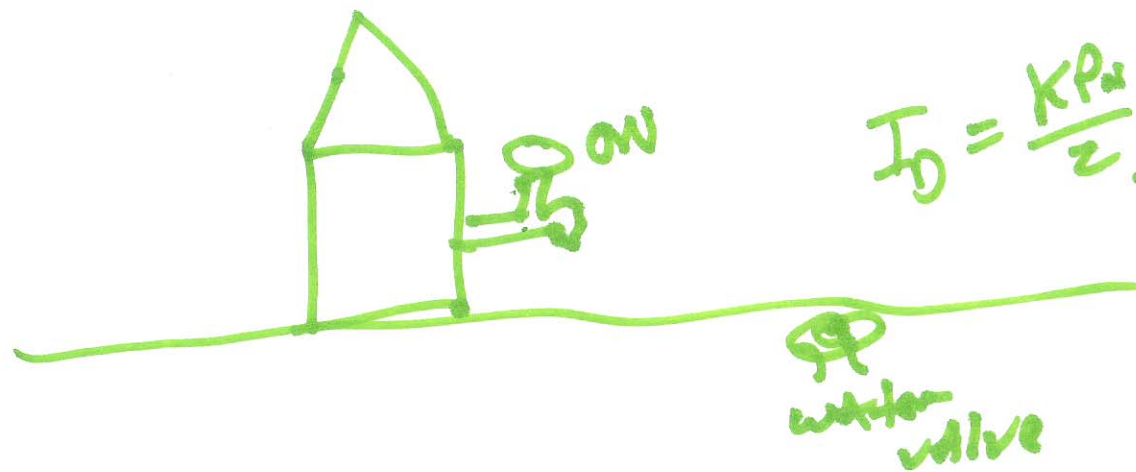
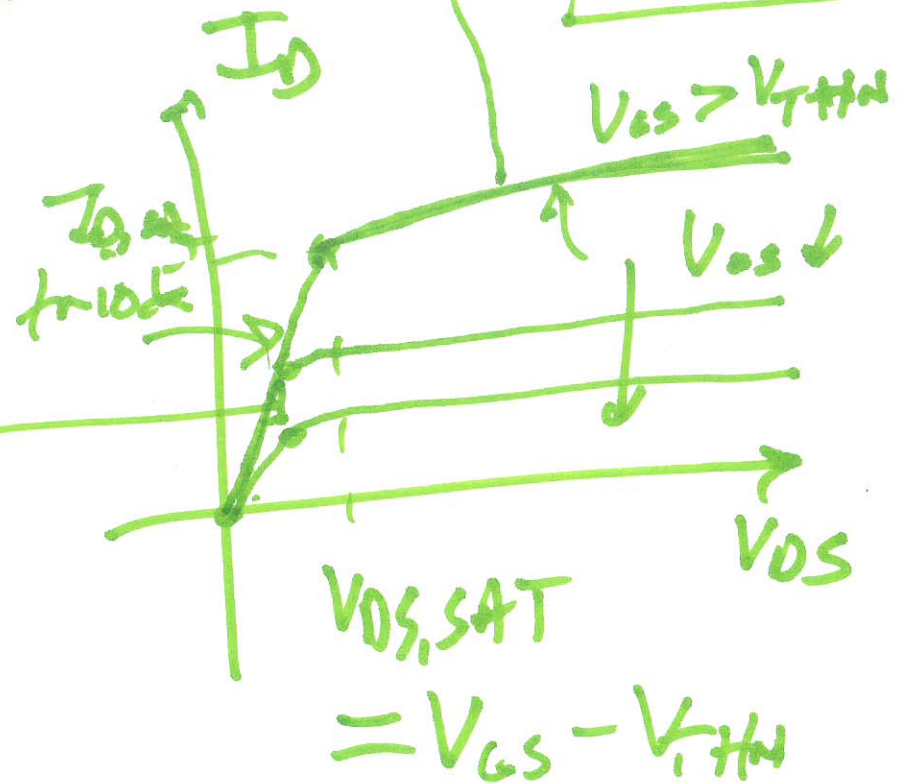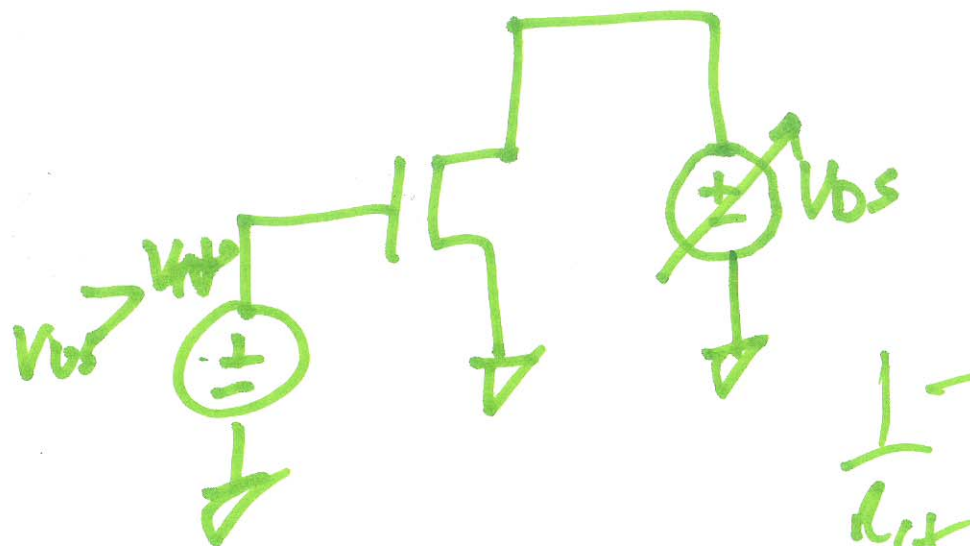
$$I_D = \frac{K P_n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 (1 + \lambda (V_{DS} - V_{DS,SAT}))$$



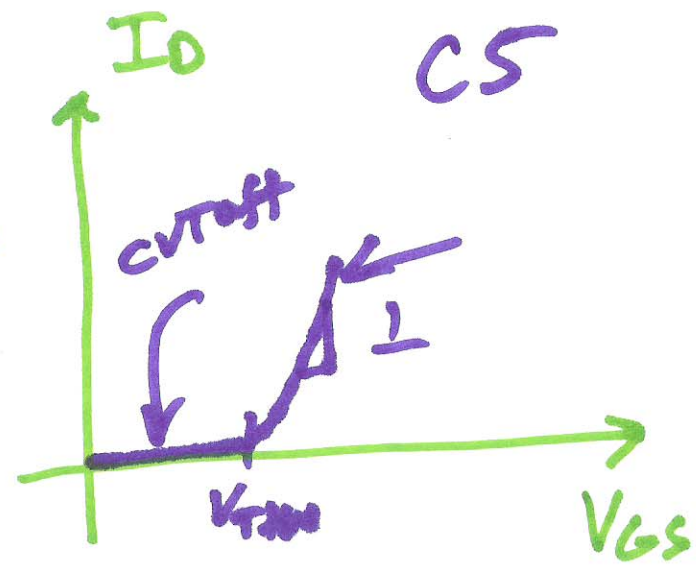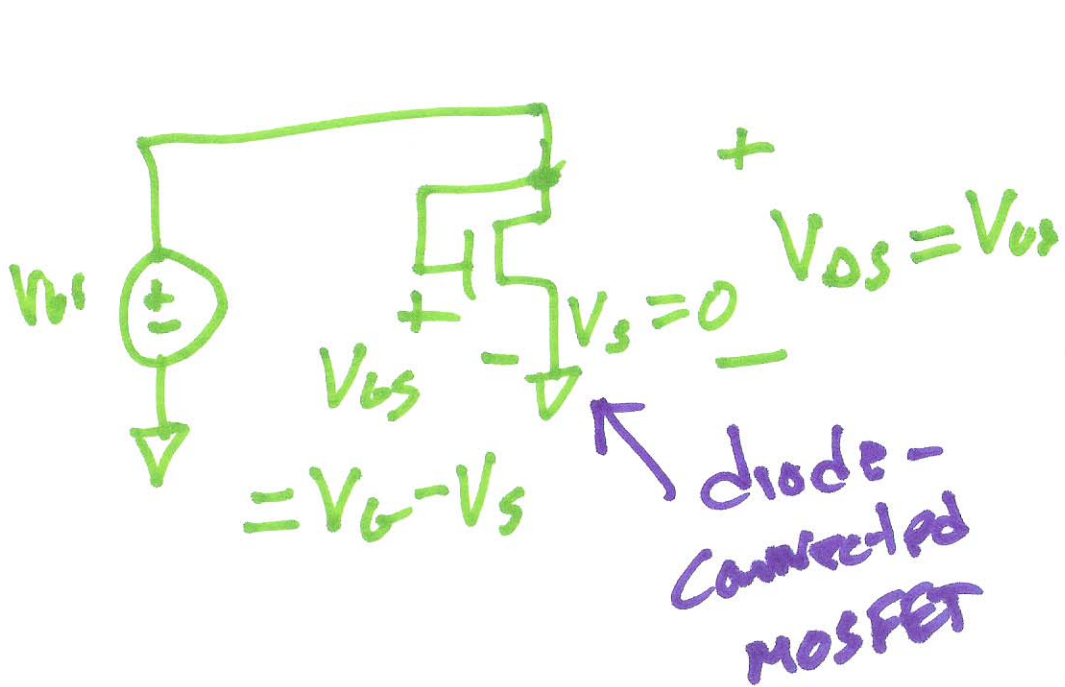

$$\left. \begin{aligned} V_{DS} &> V_{GS} - V_{TH} \\ V_{DS} &> V_{DS,SAT} \end{aligned} \right\} \text{Saturation}$$

$$V_D - V_S > V_G - V_S - V_{TH}$$

$$V_D = V_G$$

$$0 > -V_{TH}$$

Saturation

$$I_0 = \frac{K P_N}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$I_0 = \frac{K P_N}{2} \cdot 10 (V_{GS} - 0.8)^2$$

$$470 \mu A = K P_N \cdot 5 (1.8 - 0.8)^2$$

$$K P_N = 94 \frac{\mu A}{V^2} \approx \frac{100 \mu A}{V^2} = \mu_n \cdot C_{ox}$$

$$V_{THN} = \underline{\underline{800 mV}}$$


$\frac{C_{ot}}{C_{ox}}$
↑

5)

$$\frac{\delta(x-A)}{\delta x} = I_0 + i_d$$

$$I_{DQ} = 470 \mu A$$

$$AC = 1 \mu V$$

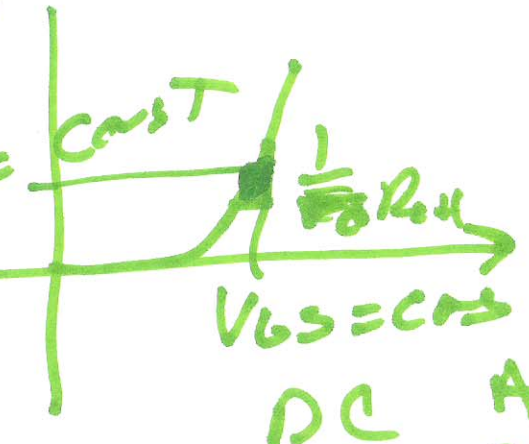

$$V_{GS} = 1.8$$

$$AC = 0$$



$$V_{GS} = V_{GS} + v_{gs}$$

$$\frac{\delta i_D}{\delta V_{GS}} = \frac{\delta I_D + i_d}{\delta V_{GS}} = \frac{K P_N}{2} \frac{W}{L} \left(\underbrace{V_{GS} + v_{gs}}_{= V_{GS}} - V_{THN} \right)^2$$

DC AC

$I_D = \text{const}$

$V_{GS} = \text{const}$

$\frac{1}{R_{eff}} = K P_N \cdot \frac{W}{L} (V_{GS} + v_{gs} - V_{THN})$

$1.8 + 1 \mu V$

~~$$R_{CH} = \frac{1}{\frac{100 \mu A}{V_{TH}} \cdot 10 (1.8 - 0.8) V}$$~~


$$R_{CH} = \frac{1}{K_P \cdot \frac{W}{L} (V_{GS} - V_{TH})}$$

$$R_{CH} = \frac{1}{\frac{1 mA}{V_{TH}}} = \underline{\underline{1 k\Omega}}$$

$$1\mu\text{V}/1\text{k} = 1\mu\text{A} \Rightarrow 20 \log 1\mu$$

$$20 \log 10^{-6}$$
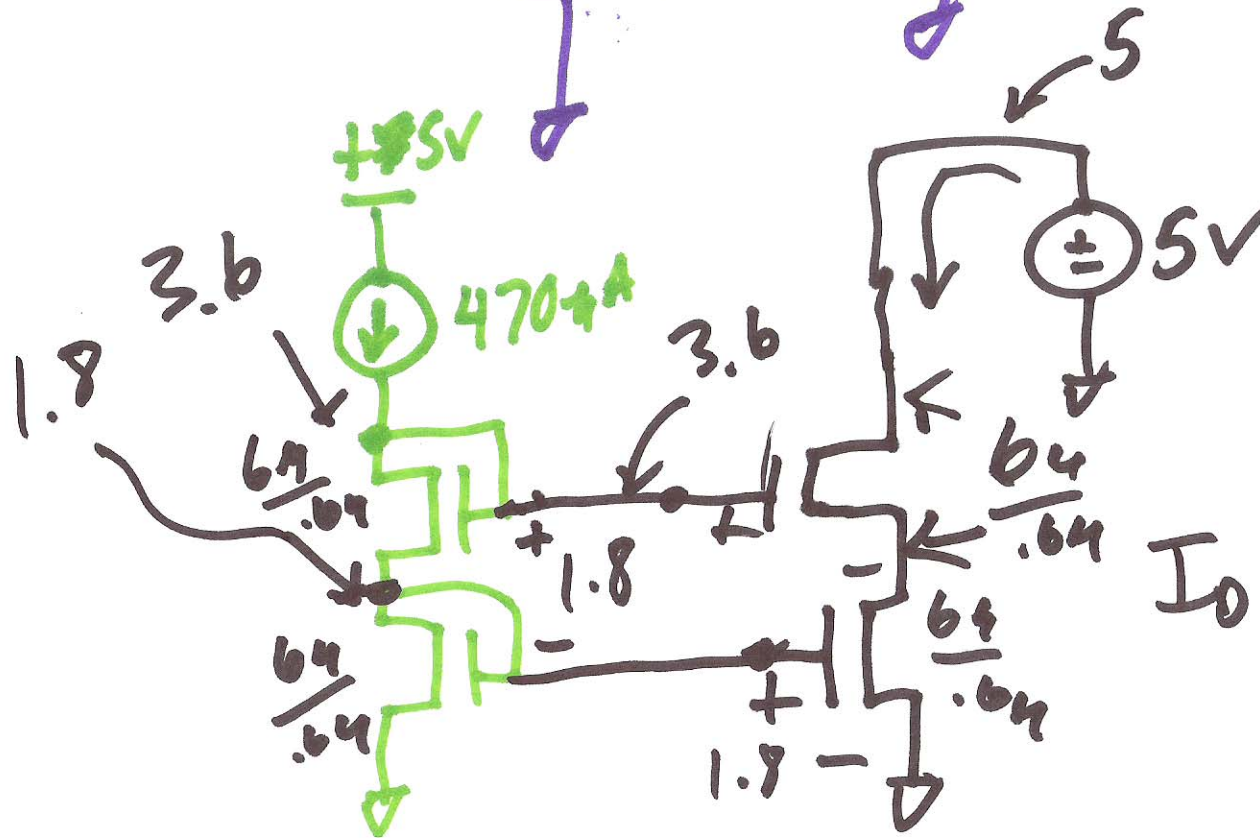
$$\underline{\underline{-120\text{dB}}}$$



$$I_D = \frac{K_P}{2} \frac{W}{L} (1.8 - 0.8)^2$$

