




EE 420 / ECE 620

Analog IC Design

Lecture 3

JANUARY 26,


2015

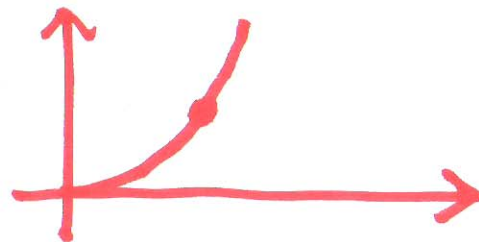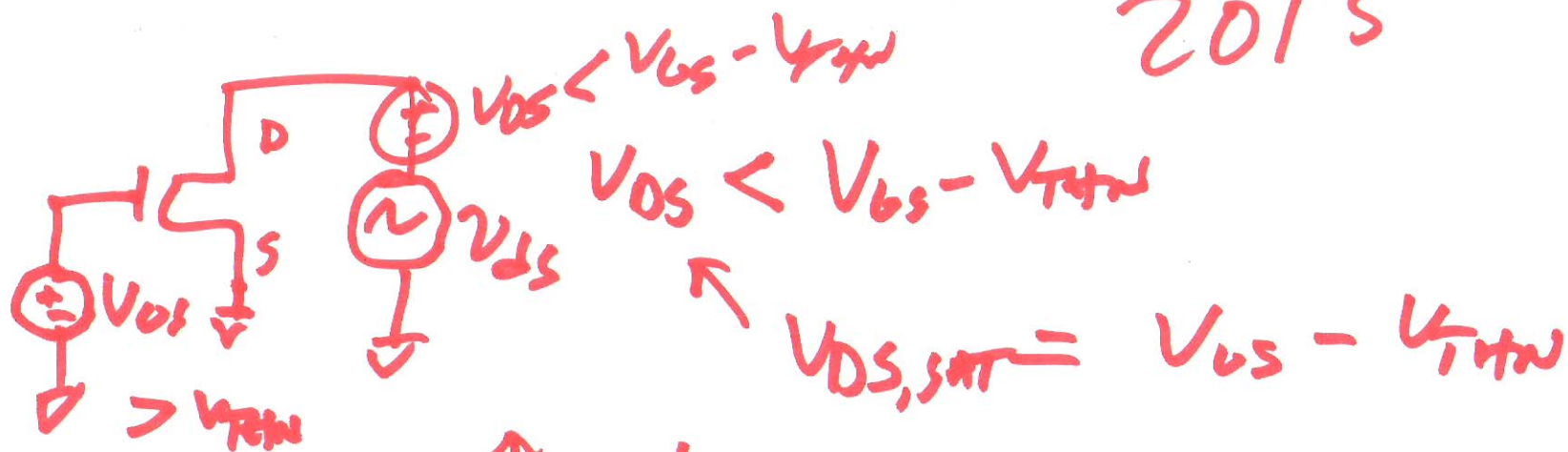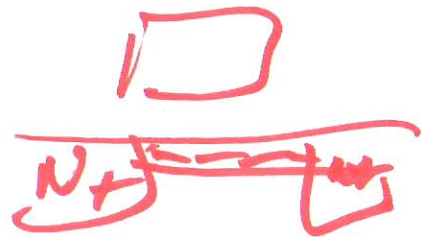



$$V_{DS} = 0$$
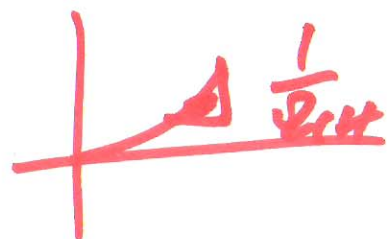
$$I_D = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH}) V_{DS}$$



$$I_D = K_P \cdot \frac{W}{L} \left((V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$i_D = I_D + \dot{i}_d = K_P \frac{W}{L} \left((V_{GS} - V_{TH}) (V_{DS} + v_{ds}) - \frac{(V_{DS} + v_{ds})^2}{2} \right)$$


$$\frac{1}{R_{CH}} = \left. \frac{\partial i_D}{\partial V_{DS}} \right|_{\substack{V_{GS} = \text{const} \\ I_D = \text{const}}} = K_P \frac{W}{L} \left(V_{GS} - V_{TH} \right) \frac{1}{L} \cdot \frac{V_{DS}}{L}$$

2)

$$\frac{1}{R_{CH}} = KP \frac{W}{L} \left[(V_{GS} - V_{TH}) - V_{DS} \right]$$

$$V_{DS} \ll V_{GS} - V_{TH}$$
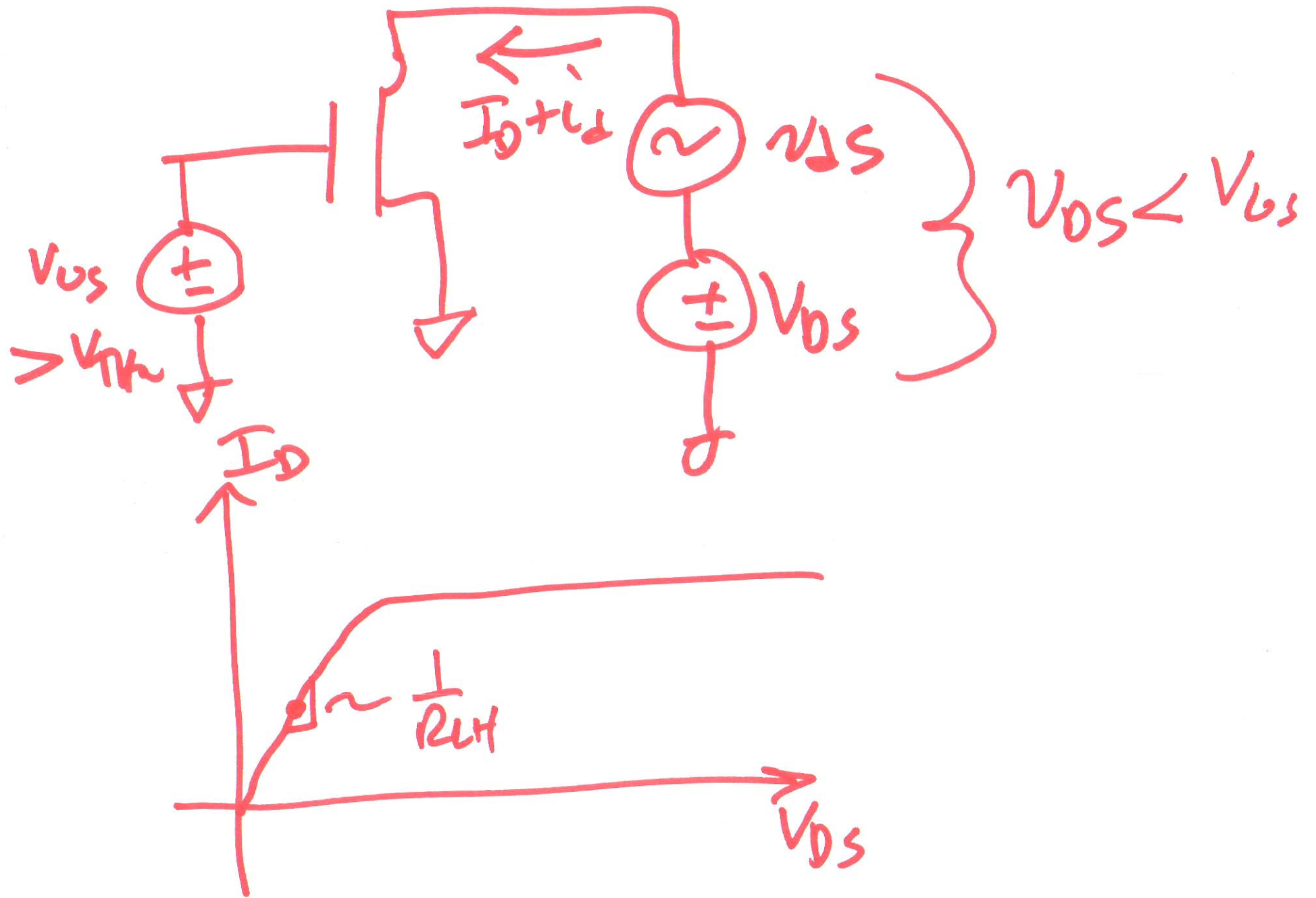
$$R_{CH} \approx \frac{1}{KP \cdot \frac{W}{L} (V_{GS} - V_{TH})}$$



4)

$$\frac{1}{R_{ch}} = \frac{\delta I_D}{\delta V_{DS}} \quad \left| \begin{array}{l} I_D = \text{CONST} \\ V_{GS} = \text{CONST} \end{array} \right.$$

$$\frac{\delta \left(K_P \cdot \frac{W}{L} \left((V_{GS} - V_{THN}) \underbrace{(V_{DS} + V_{DS})}_{V_{DS}} - \frac{(V_{DS} + V_{DS})^2}{2} \right) \right)}{\delta V_{DS}}$$


$$V_{DS} \gg V_{DS} \rightarrow = V_{DS}$$

$$\frac{1}{R_{ch}} = (V_{GS} - V_{THN}) \frac{K_P \cdot W}{L} - \frac{K_P W}{L} (V_{DS} + V_{DS})$$

$$R_{\text{eff}} = \frac{1}{K_P \cdot \frac{W}{L} \left[(V_{GS} - V_{THN}) - (V_{DS} + V_{GS}) \right]}$$

$$V_{GS} \gg V_{DS}$$
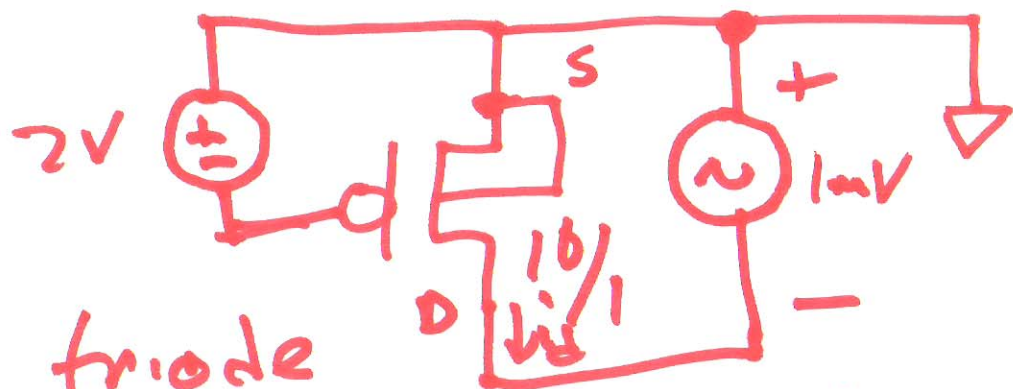
$$R_{\text{eff}} \approx \frac{1}{K_P \cdot \frac{W}{L} (V_{GS} - V_{THN})}$$



$$I_D = ? \quad \underline{\underline{0}}$$


$$i_d = ?$$

for triode

$$V_{SD} < V_{SG} - V_{THP}$$

$$\text{OR } V_{SG} > V_{SD} + V_{THP}$$

$$V_{SG} > V_{SD} + V_{THP}$$

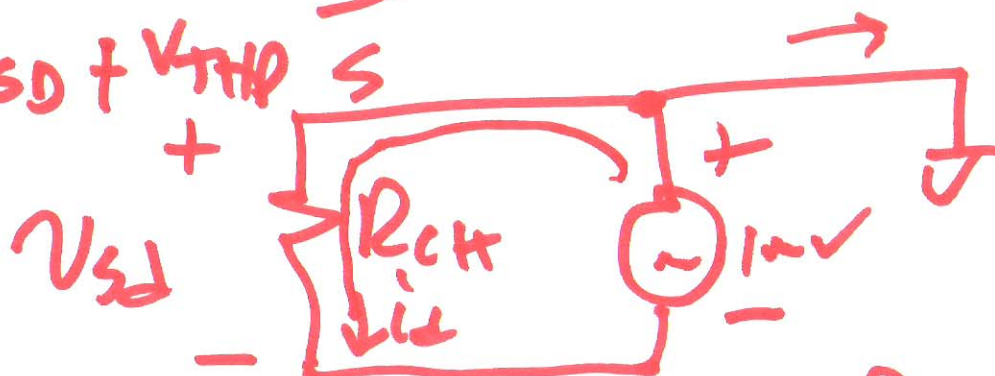

$$i_d = \frac{1mV}{2.2K} = 440nA = \underline{\underline{0.44\mu A}}$$

$$2.27K = R_{ch} = \frac{K_P \cdot 10}{\sqrt{2}} (2 - .9)$$


$$2 > -.9V$$

$$\text{triode } V_{SG} > V_{SD} - V_{THP}$$

$$.2 \geq 2 - .9$$

yes!

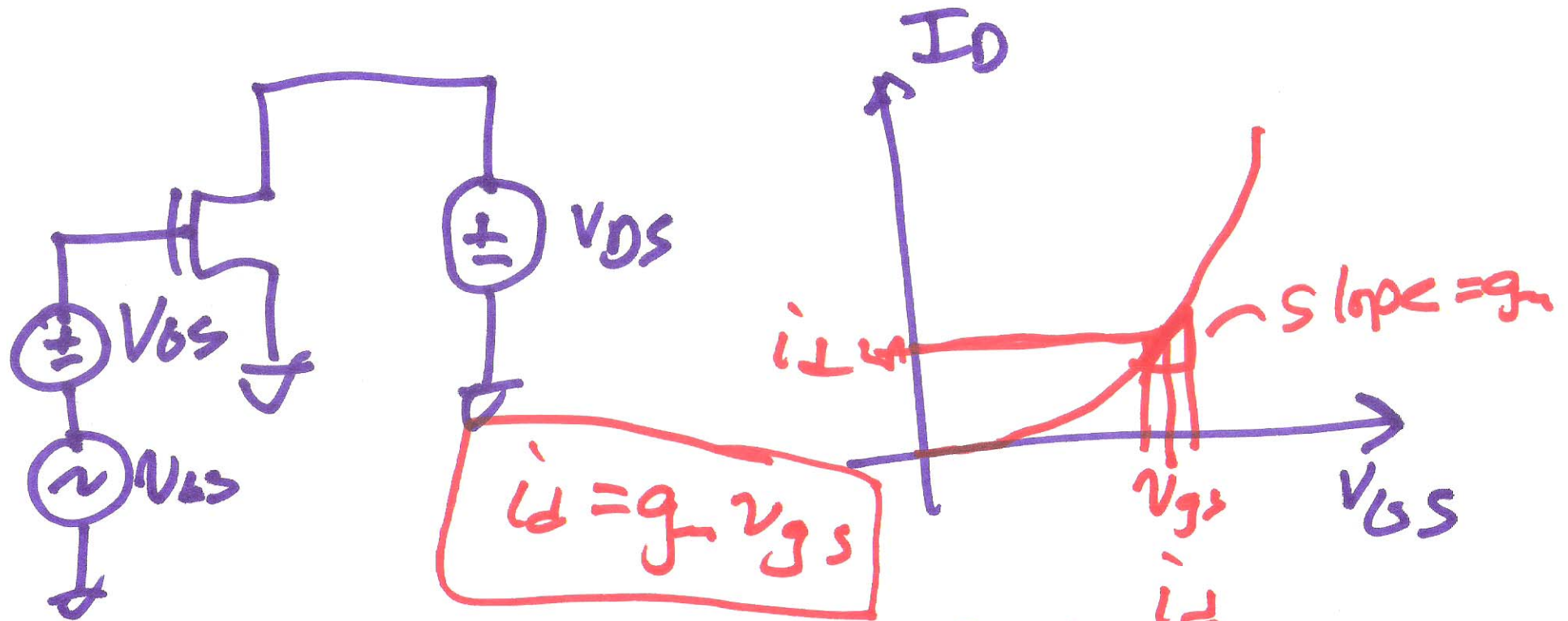for saturation $V_{DS} \geq V_{GS} - V_{THN}$



$$\frac{\partial i_d + I_D}{\partial V_{GS}} = \frac{\partial \frac{K_P W}{2 L} (V_{GS} + v_{gs} - V_{THN})^2}{\partial V_{GS}} \quad V_{GS} \gg v_{gs}$$

$$g_m = \frac{i_d}{v_{gs}} = K_P \frac{W}{L} (V_{GS} - V_{THN})$$


$$g_m = k_P \cdot \frac{W}{L} (V_{GS} - V_{THN})$$

$$I_D = \frac{k_P \cdot W}{2L} (V_{GS} - V_{THN})^2$$

$$V_{GS} - V_{THN} = \sqrt{\frac{I_D \cdot 2}{k_P \cdot \frac{W}{L}}}$$

$$g_m = \sqrt{2 \cdot k_P \cdot \frac{W}{L} I_D}$$
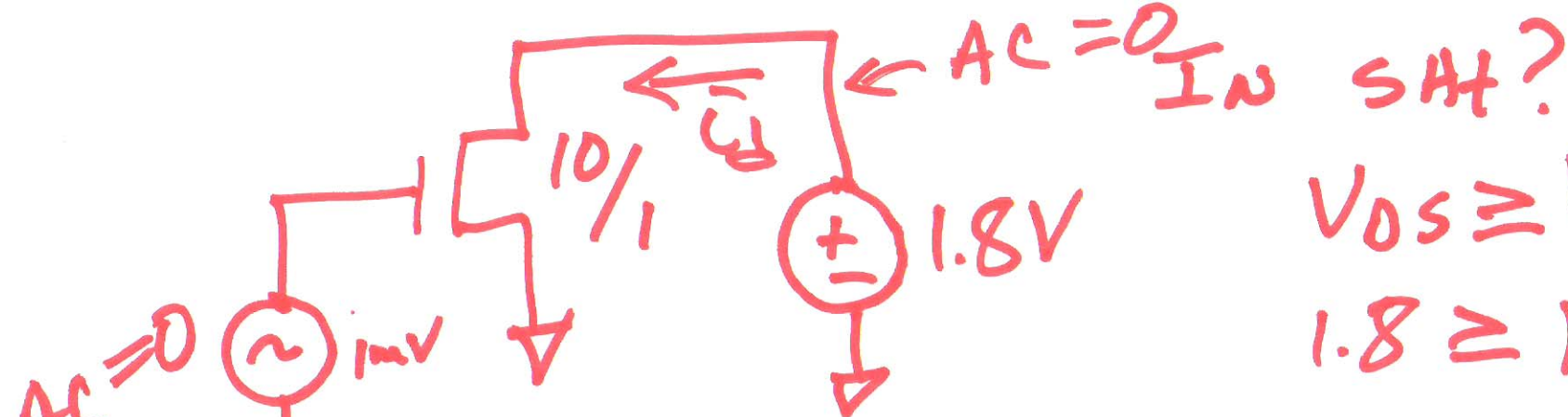
$$= \sqrt{2 \beta I_D}, \quad \beta = k_P \cdot \frac{W}{L}$$



$$V_{DS} \geq V_{GS} - V_{TH}$$

$$1.8 \geq 1.8 - .8$$

yes!

$$g_m = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH})$$

$$= \frac{1204}{\sqrt{2}} \cdot \frac{10}{1} (1.8 - .8)$$

$$g_m = \frac{1.2 \text{ mA}}{\sqrt{2}}$$

$$i_d = g_m v_{gs}$$

$$i_d = 1.2 \mu\text{A} = \frac{1.2 \text{ mA}}{\sqrt{2}} \cdot 1 \text{ mV}$$

Ex.

9.5

