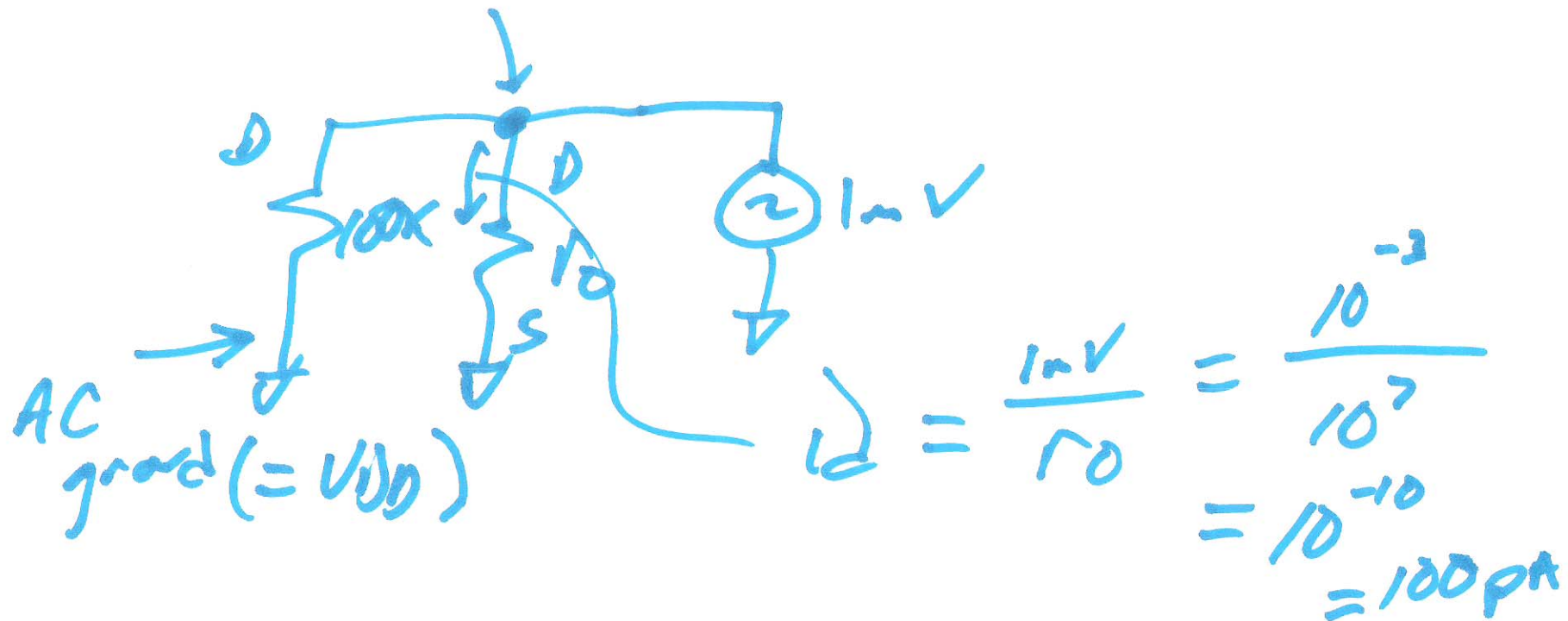



EE 420 / ECE 620

Engr. Elec. II

Lecture 5


1st Feb. 2, 2015



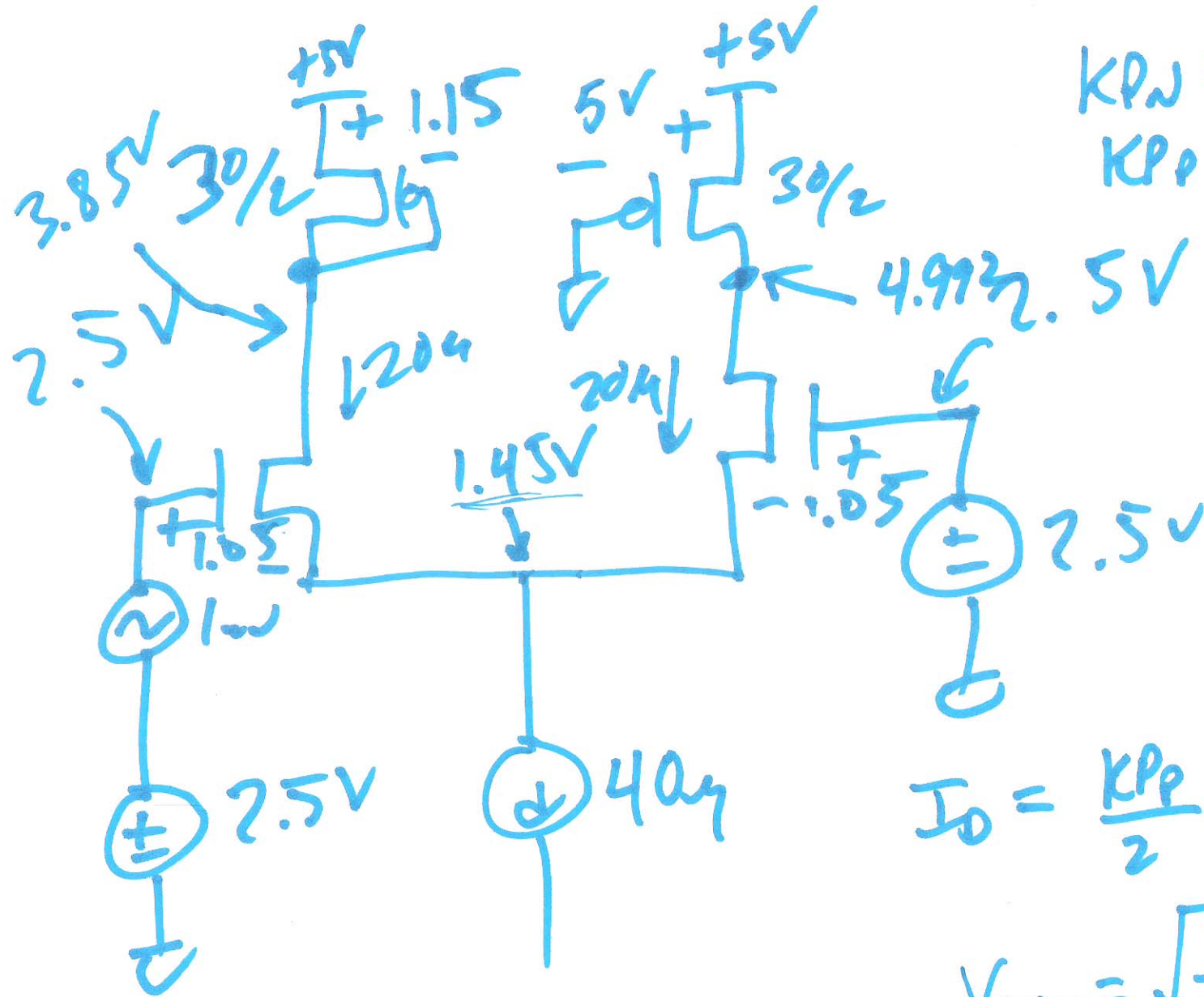

$$I_D = \frac{K_{PP}}{2} \cdot \frac{W}{L} (V_{SG} - V_{THP})^2$$
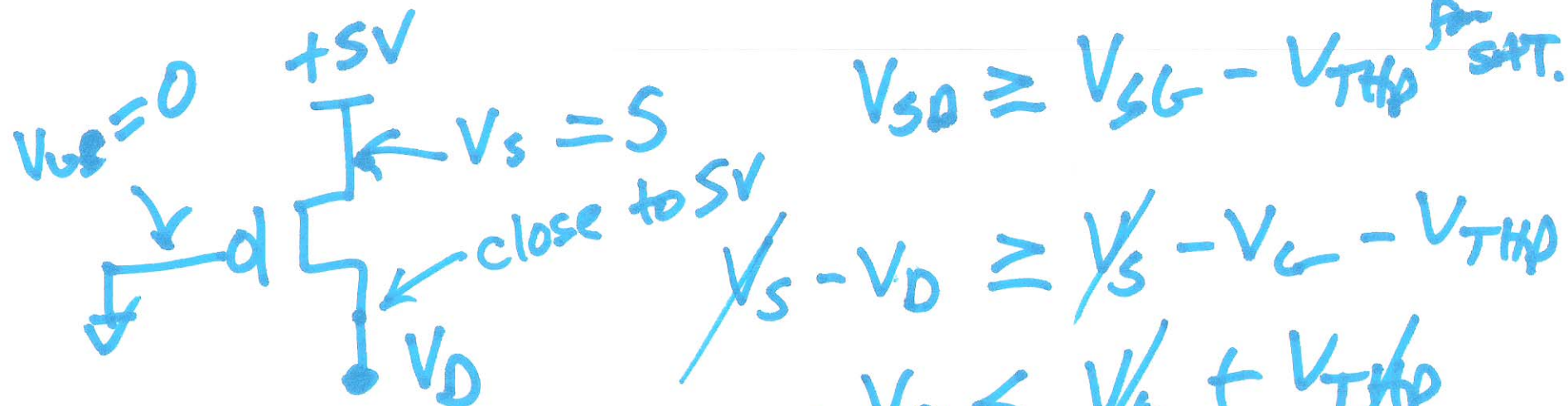
$$V_{SG} = \underbrace{\sqrt{\frac{2I_D}{K_{PP} \cdot \frac{W}{L}}}}_{\text{overdrive}} + V_{THP}$$



$$V_{SD} \geq V_{SG} - V_{THP} \text{ for SAT.}$$

$$V_S - V_D \geq V_S - V_G - V_{THP}$$


$$V_D \leq V_G + V_{THP}$$

$$I_D = K_P \frac{W}{L} \left((V_{SG} - V_{THP}) V_{SD} - \frac{V_{SD}^2}{2} \right)$$


$$20 \mu A \approx 20 \mu A \cdot \frac{30}{2} \left((5 - .9)(5 - V_D) \right) V_D \leq .9 \text{ for SAT.}$$

$$5 - V_D = \frac{1}{123}$$

$$V_D = 5 - \frac{1}{123} = \underline{\underline{4.99V}}$$

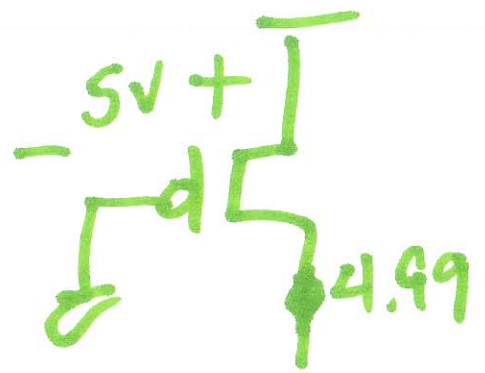
 $\Rightarrow$


 $R_{ch} = \frac{1}{K_P \frac{W}{L} (V_{SG} - V_{TH})}$

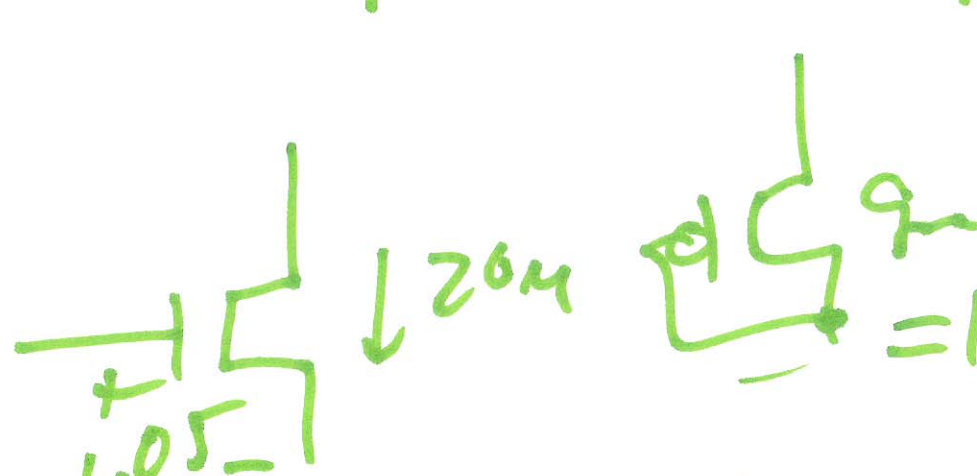
 $= \frac{1}{\frac{40 \mu A}{V^2} \cdot \frac{30}{2} (4.1)}$

$$g_m = K_P \frac{W}{L} (1.05 - .8)$$

$$= 150 \frac{\mu A}{V}$$
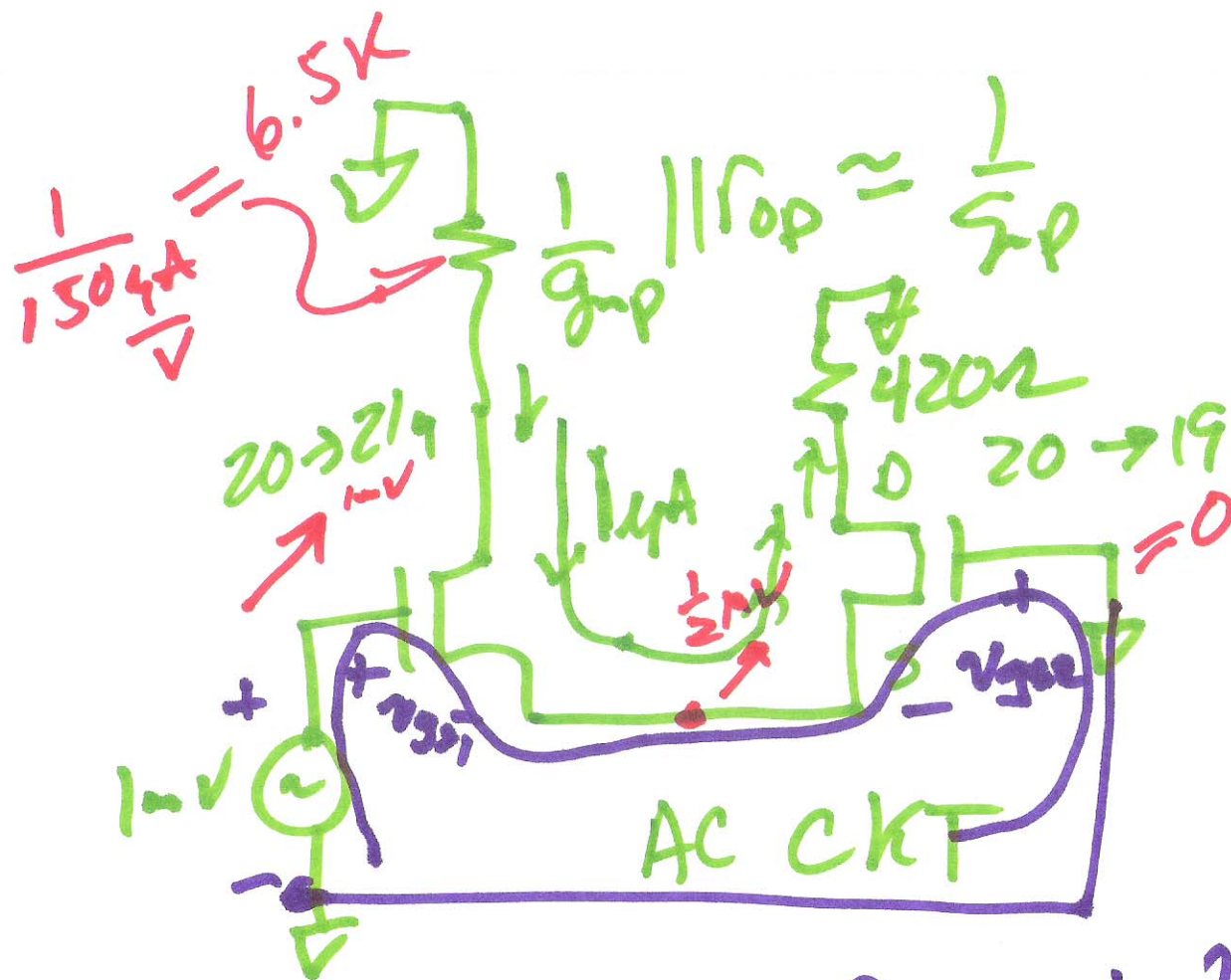
$$= \frac{1}{2.460 \frac{\mu A}{V}} \approx \underline{\underline{420 \Omega}}$$



$$i_d = g_m v_{gs}$$

$$v_{gs} = \frac{i_d}{g_m}$$

$$i_{d1} = i_{d2}$$


$$v_{gs1} = -v_{gs2}$$

$$1mV - v_{gs1} + v_{gs2} = 0$$


$$v_{gs1} - v_{gs2} = 1mV$$


$$\frac{i_{d1}}{g_{m1}} - \frac{i_{d2}}{g_{m2}} = 1mV$$

CMOSedu.com

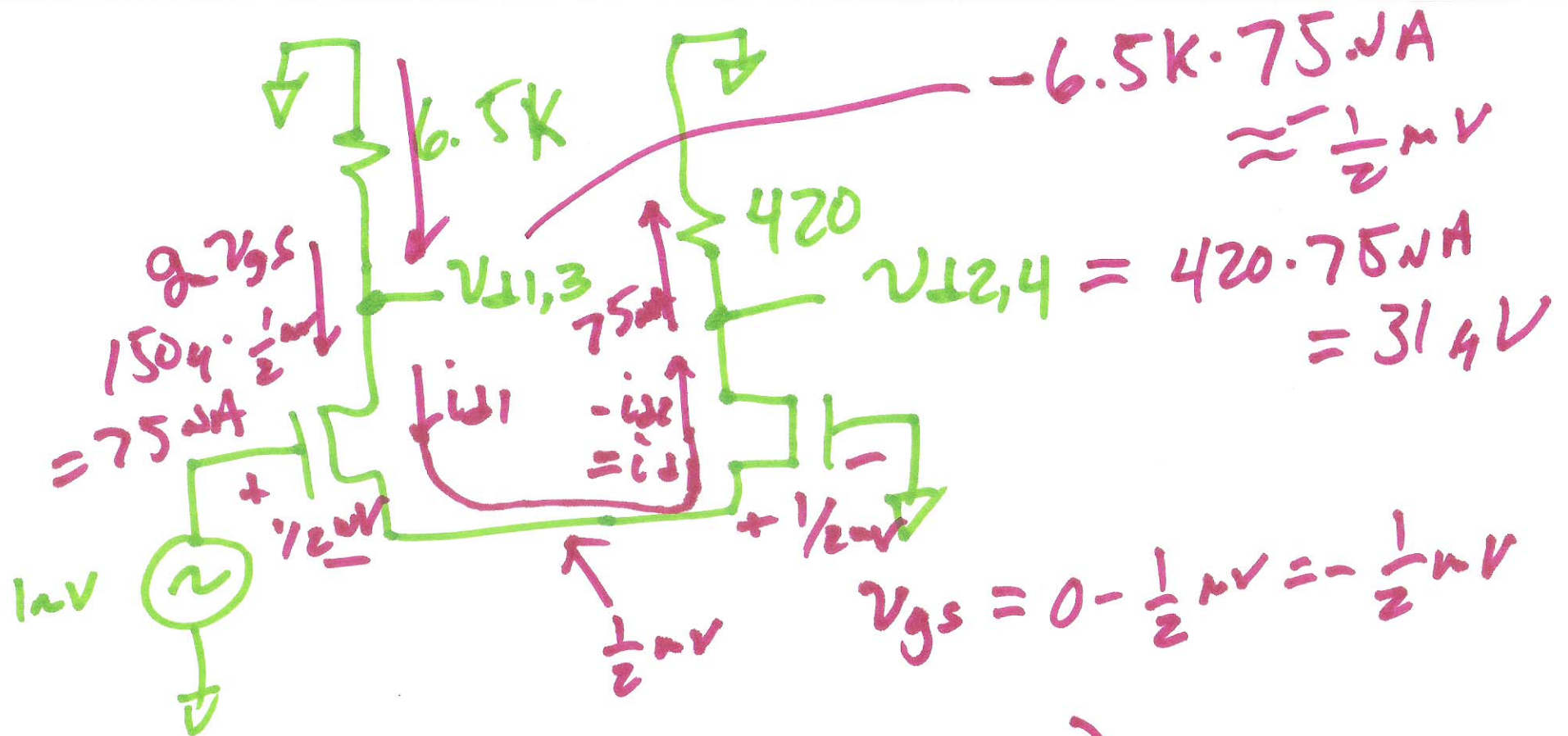
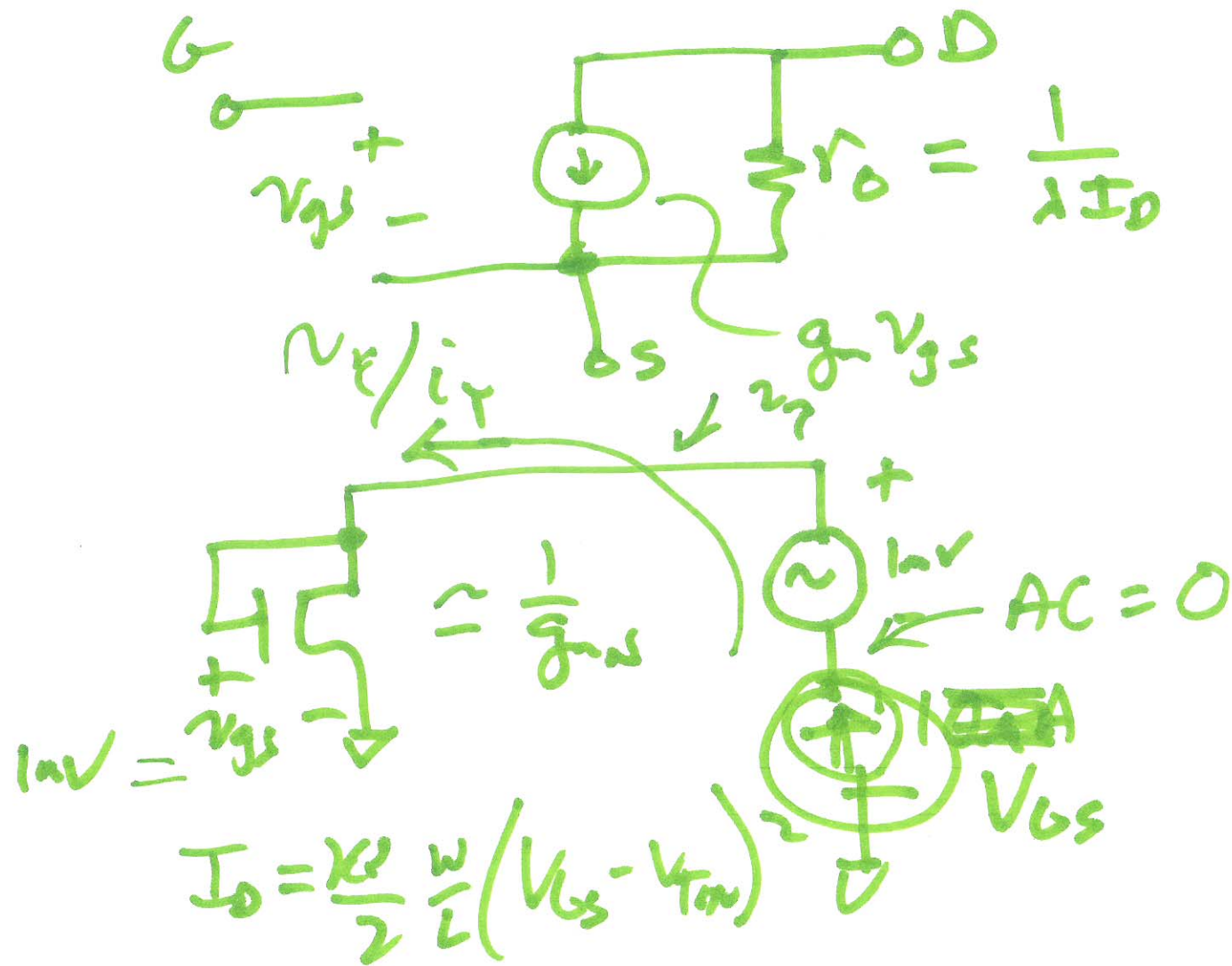
$$20 \mu A + 75 \mu A \cdot \cos(2\pi \cdot f \cdot t)$$



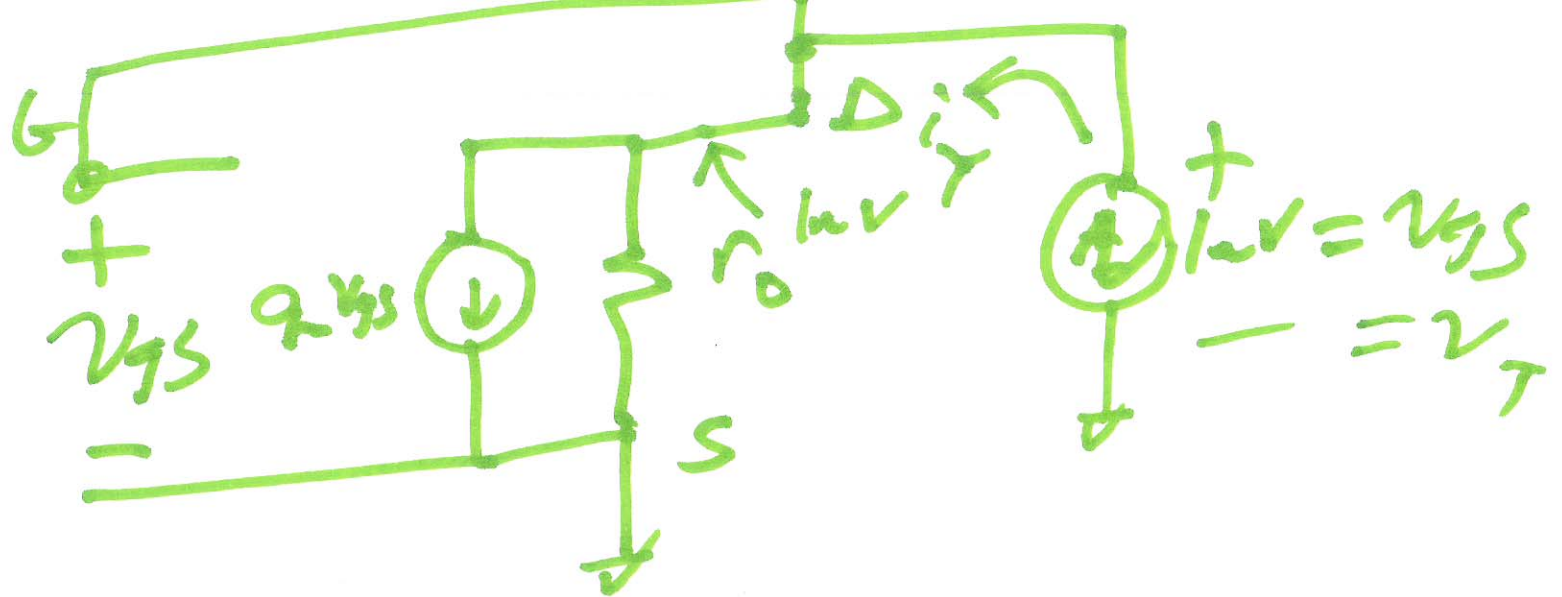

$$i_T = \frac{v_T}{r_o} + g_m v_T$$

$$\frac{v_T}{i_T} = \frac{1}{\frac{1}{r_o} + \frac{1}{g_m}} = \frac{1}{\frac{1}{g_m} \parallel r_o} \approx \frac{1}{g_m}$$