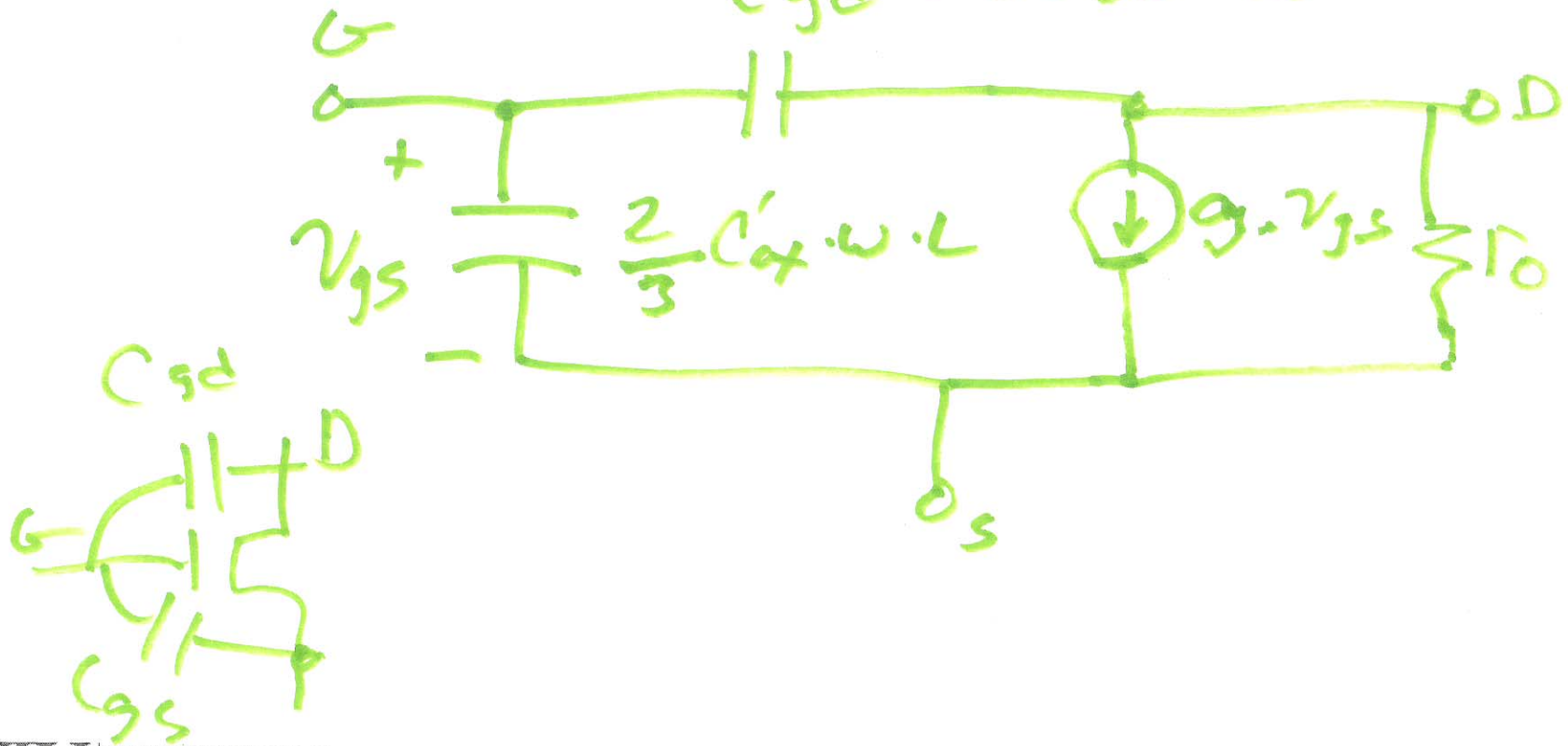


EE 420 ECL 620


## Lecture 6

for snt. Feb. 4, 2015


$$C_{gd} = C_{GD0} \cdot W$$



# transition frequency

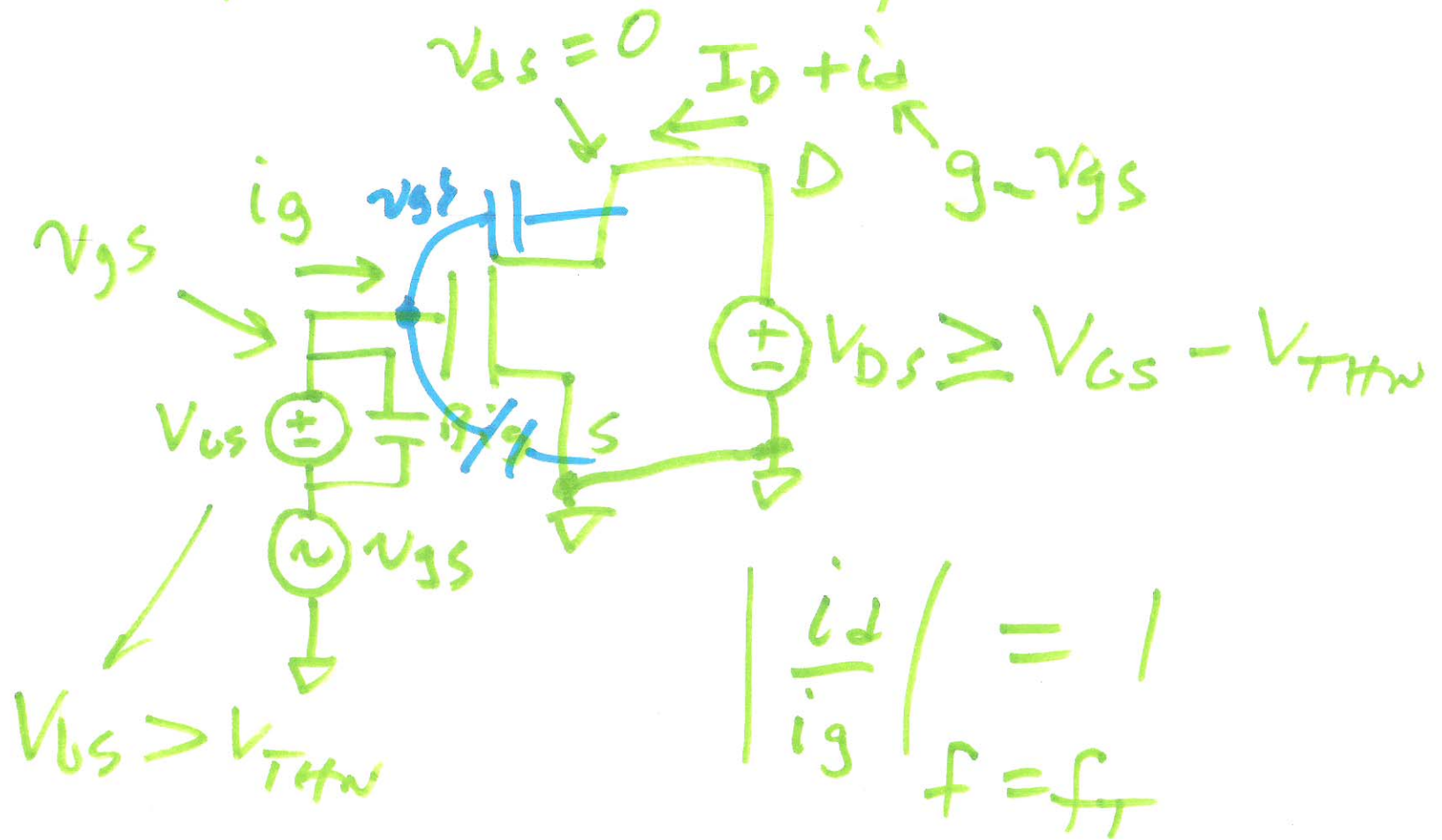


# AC CKT

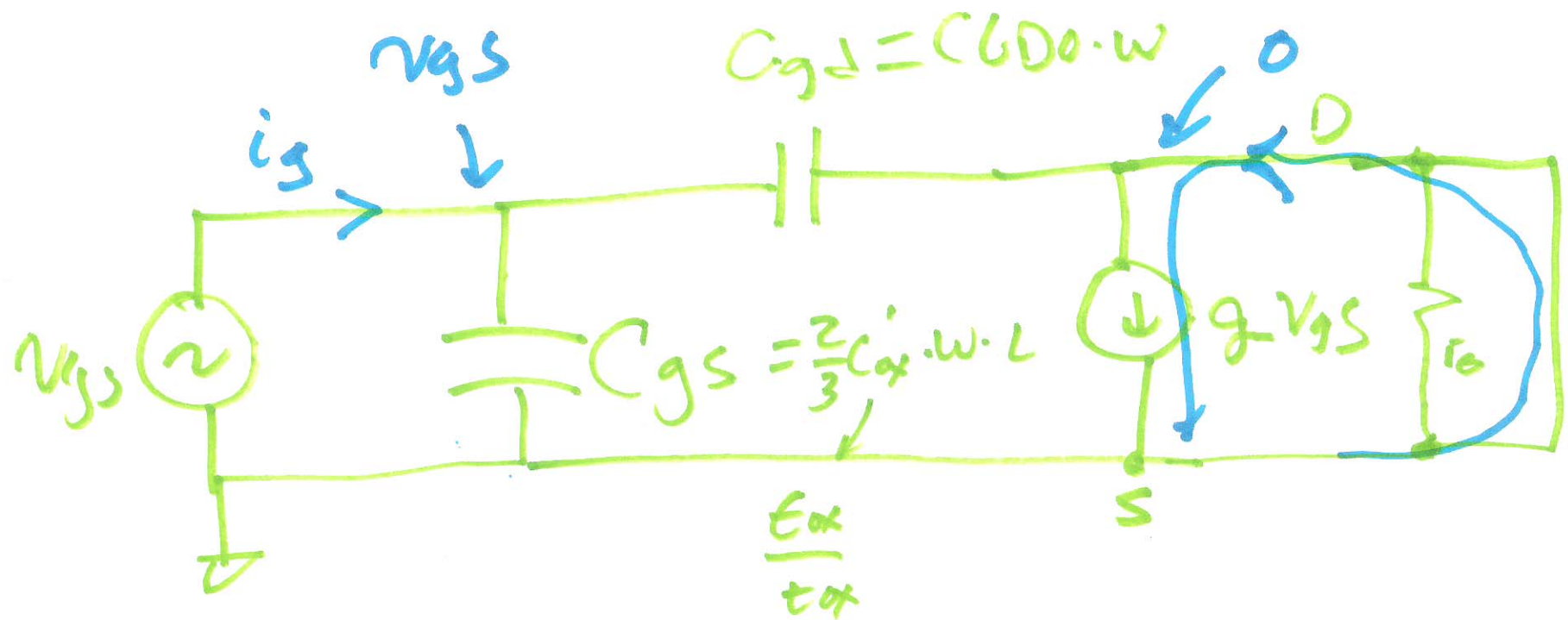

$$i_g = \frac{v_{gs}}{j\omega(C_{gd} + C_{gs})}, \quad i_d = g_m v_{gs}$$


$$\frac{i_d}{i_g} = \frac{g_m v_{gs}}{v_{gs} \cdot j\omega(C_{gd} + C_{gs})}$$
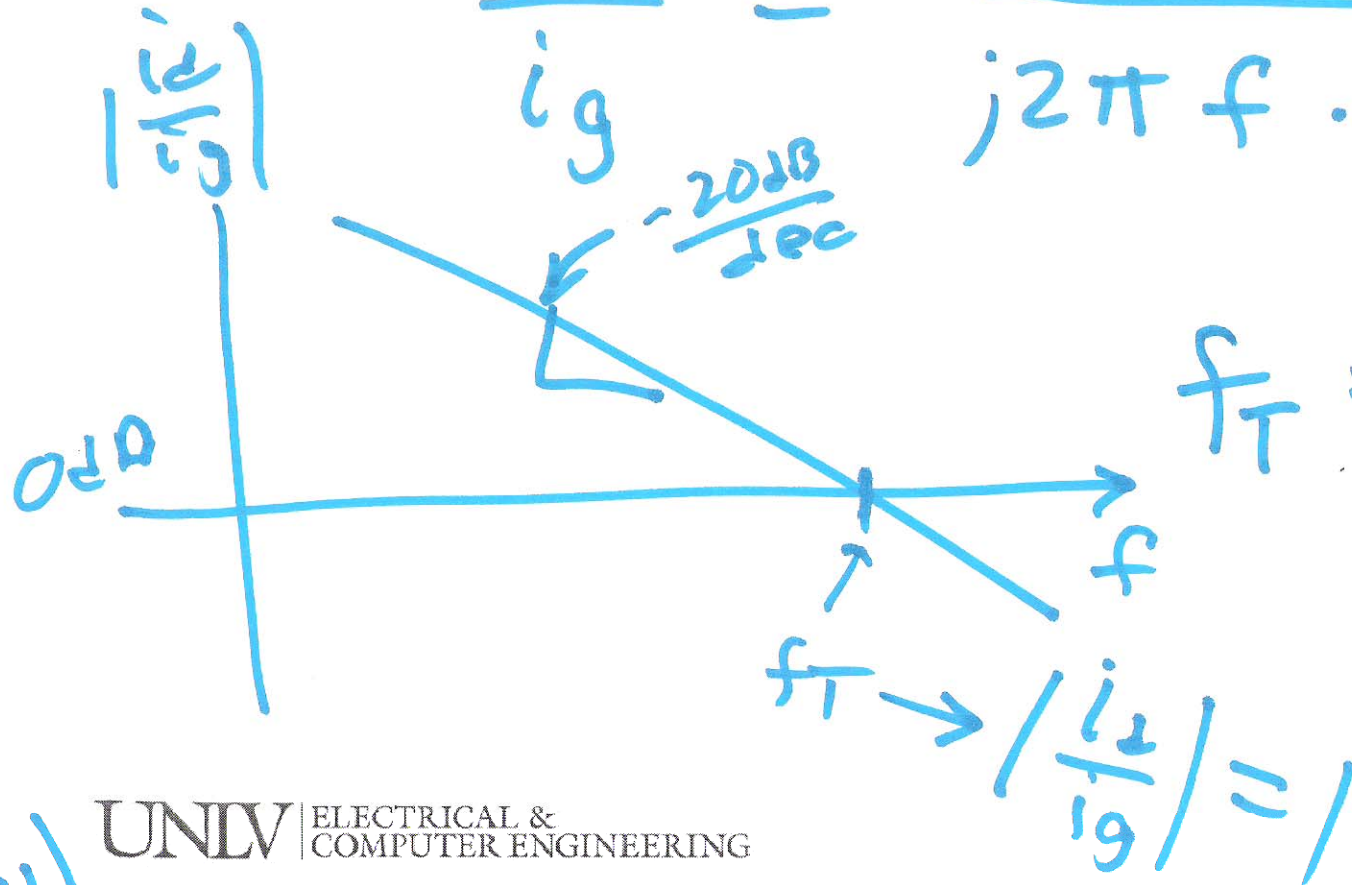
$$\frac{i_d}{i_g} = \frac{g_m}{j2\pi f \cdot (C_{gd} + C_{gs})}$$



$$f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})}$$

4)

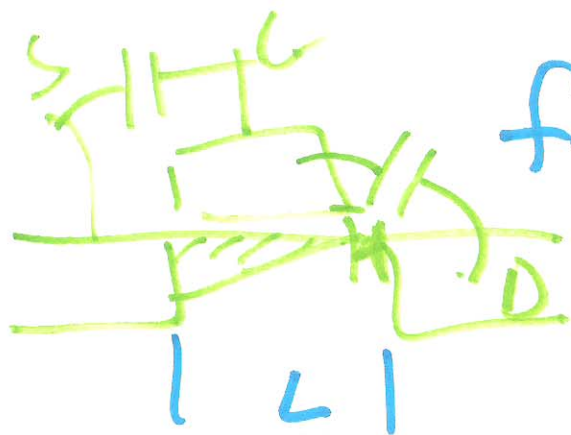

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$



$$I \rightarrow \frac{1}{T} C$$

$$\frac{dv}{dt} = \frac{I}{C}$$

$$\approx \frac{4nC_{ox} \cdot \frac{W}{L} (V_{GS} - V_{THN})}{2\pi \left( \frac{2}{3} C_{ox} \cdot W \cdot L \right)}$$

$C_{gs} \gg C_{gd}$

$V_{DS,sat}$   
 $V_{OVN}$   
 Excess gate voltage

inherent speed not dep. on  $W$ !


$$f_T \propto \frac{1}{L^2}$$

$$f_T \propto V_{OVN}$$

$$f_T \uparrow \quad L \downarrow$$

$$V_{GS} \uparrow \quad f_T \uparrow$$



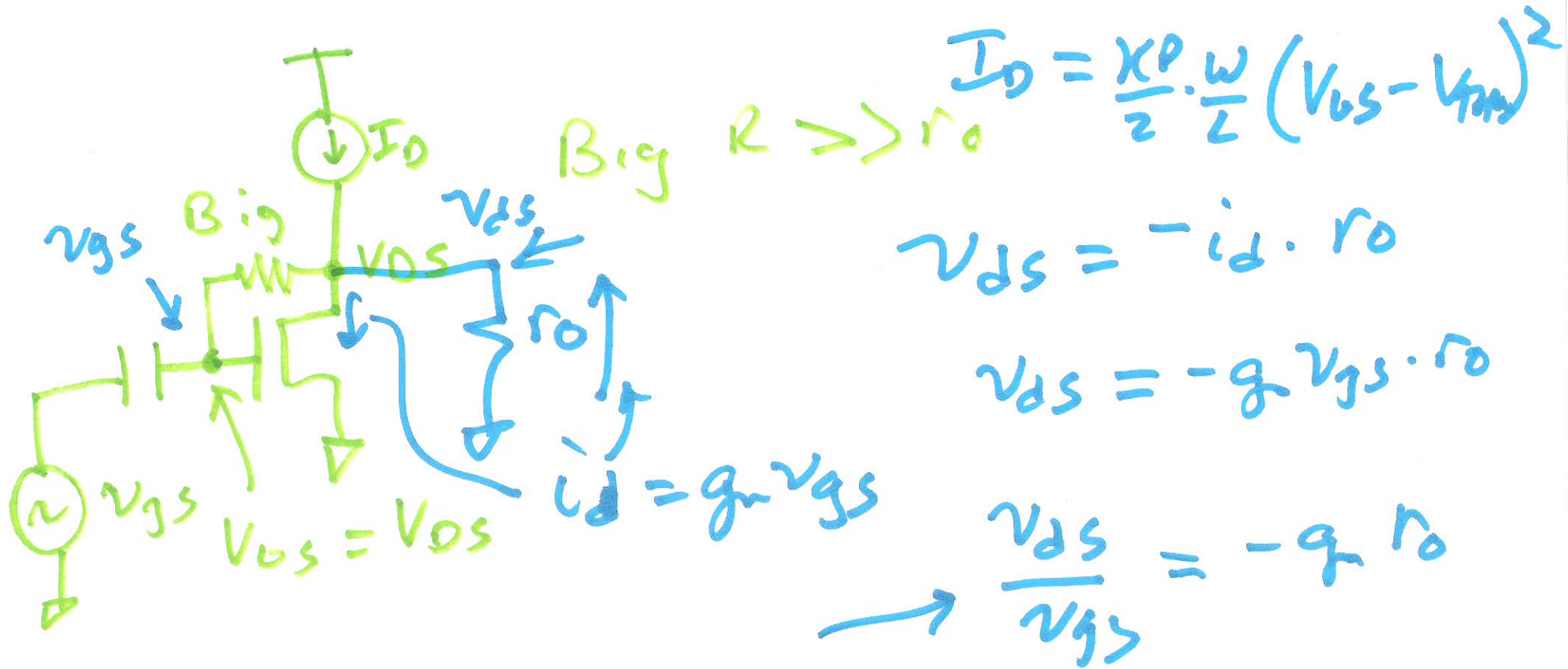

open ckt gain

$$\left| \frac{v_{ds}}{v_{gs}} \right| = \frac{\sqrt{2 \cdot K_P \frac{W}{L} \cdot I_D}}{\lambda I_D} = \frac{\sqrt{2 g_m C_{ox} \frac{W}{L}}}{\lambda \sqrt{I_D}} \propto \frac{C}{V_{GS} - V_{TH}}$$

$I_D \uparrow$  GAIN  $\downarrow \propto \frac{L}{W}$   $V_{GS} \uparrow$  GAIN  $\downarrow$

6)

$$G_{A.N} \propto \frac{\sqrt{\frac{1}{L}}}{\frac{1}{L}} = \sqrt{L}$$

$L \nearrow \quad G_{A.N} \nearrow$

GAIN  $\cdot f_T$  (GFT product)

$$GFT = g_m r_o \cdot \frac{g_m}{2\pi C_{gs}}$$

$$= \frac{g_m^2}{\lambda I_0 \cdot 2\pi \cdot \frac{2}{3} C_{ox}' \cdot W \cdot L}$$

$$g_m^2 = \left( \sqrt{2 \cdot K_P \cdot \frac{W}{L} I_0} \right)^2 = 2 K_P \cdot \frac{W}{L} \cdot I_0$$

GAIN  $\cdot BW$



$$GFT = \frac{2 \cancel{4\mu} C_{ox}' \cdot \cancel{\frac{W}{L}}}{\lambda \cdot 2\pi \cdot \frac{2}{3} \cancel{C_{ox}'} \cdot \cancel{\frac{W}{L}} \cdot L}$$

$$GFT \propto \frac{\mu}{L}$$



# Thermal Voltage

$$V_T = \frac{kT}{q}$$

$T \uparrow \quad V_T \uparrow$

# Threshold voltage

$T \uparrow \quad V_{THN} \downarrow$

9)