
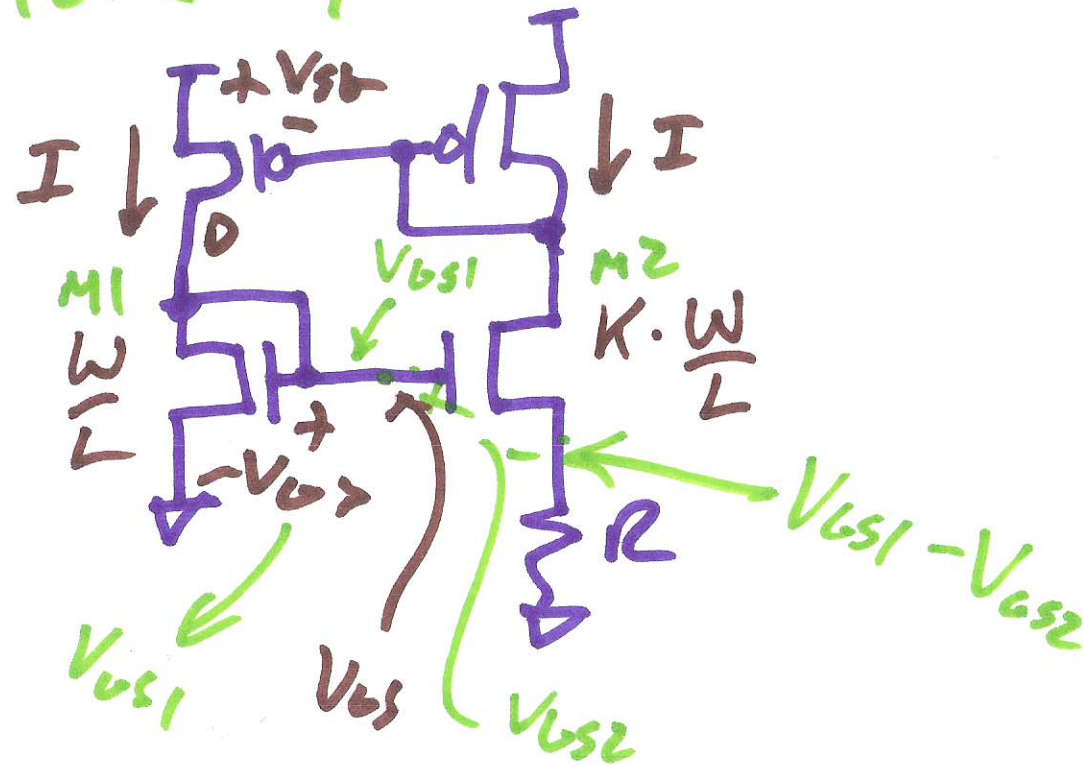
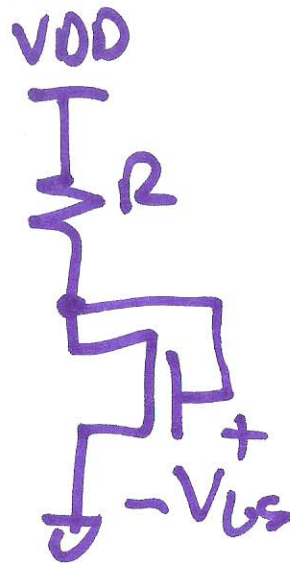



EE 420/ECG 620

Analog IC Design

Feb. 11, 2015

Lecture 9

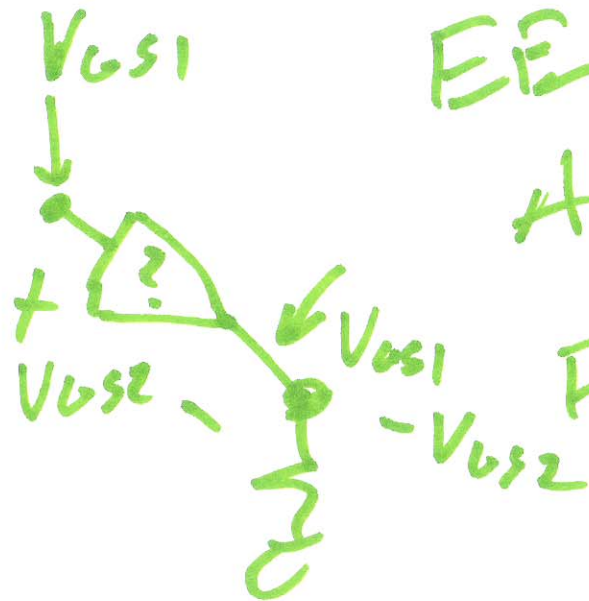

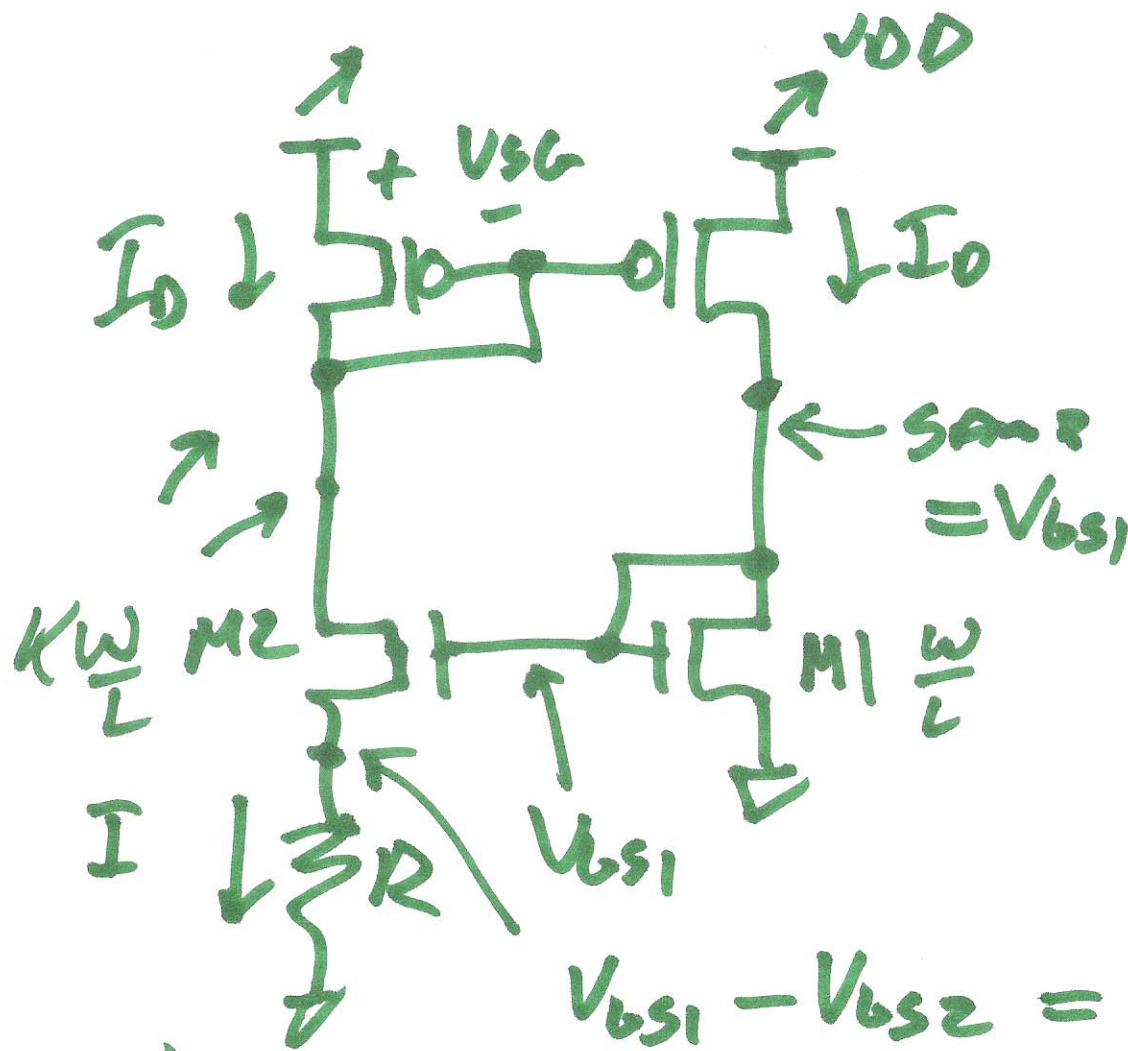

$$V_{GS} = \sqrt{\frac{2I_O}{K_P \cdot \frac{W}{L}}} + V_{THN}$$

$$V_{GS1} - V_{GS2} = I \cdot R$$

$$\sqrt{\frac{2I}{K_P \cdot \frac{W}{L}}} \left(-\frac{1}{\sqrt{K}} \right) = \sqrt{\frac{2I}{K_P \cdot \frac{W}{L}}} + V_{THN} - \sqrt{\frac{2I}{K_P \cdot K \cdot \frac{W}{L}}} + V_{THN} = IR$$

$$\sqrt{\frac{2I}{K_P \cdot \frac{\omega}{L}}} \left(1 - \frac{1}{\sqrt{K}}\right) = IR$$

$$\frac{2I}{K_P \cdot \frac{\omega}{L}} \left(1 - \frac{1}{\sqrt{K}}\right)^2 = I^2 \cdot R^2$$

$$I = \frac{1}{R^2 \cdot \frac{K_P}{2} \cdot \frac{\omega}{L}} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

if $K=4$

$$I = \frac{1}{2R^2 \cdot K_P \cdot \frac{\omega}{L}}, \quad 2I \cdot K_P \cdot \frac{\omega}{L} = \frac{1}{R^2}$$

$$I = \sqrt{2I \cdot K_P \cdot \frac{\omega}{L}} = \frac{1}{R}$$

3)




$$I = \frac{1}{R^2 \cdot \frac{KP}{2} \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$\frac{KP \cdot W}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2 = \frac{1}{R^2 \cdot \frac{KP}{2} \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$


$$\frac{R}{2} \cdot KP \cdot \frac{W}{L} (V_{GS} - V_{THN})^2 = \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$g_m = KP \cdot \frac{W}{L} (V_{GS} - V_{THN}) = \frac{1}{R} \quad K=4$$


$V_{OVN} = V_{DS,SAT}$

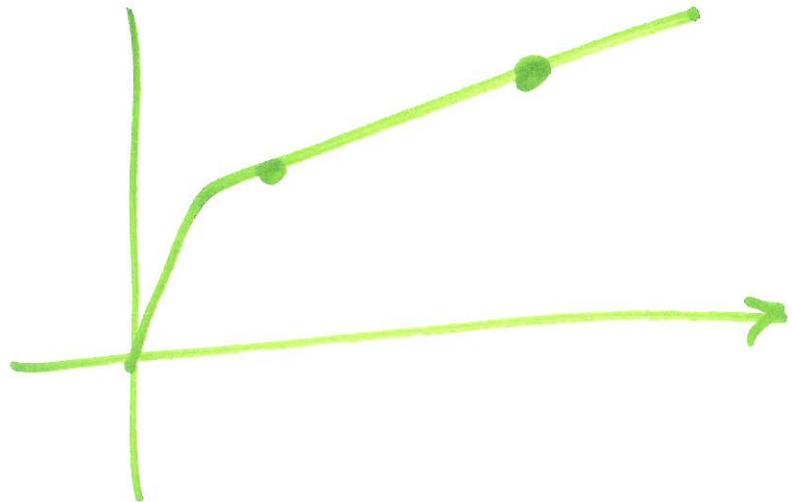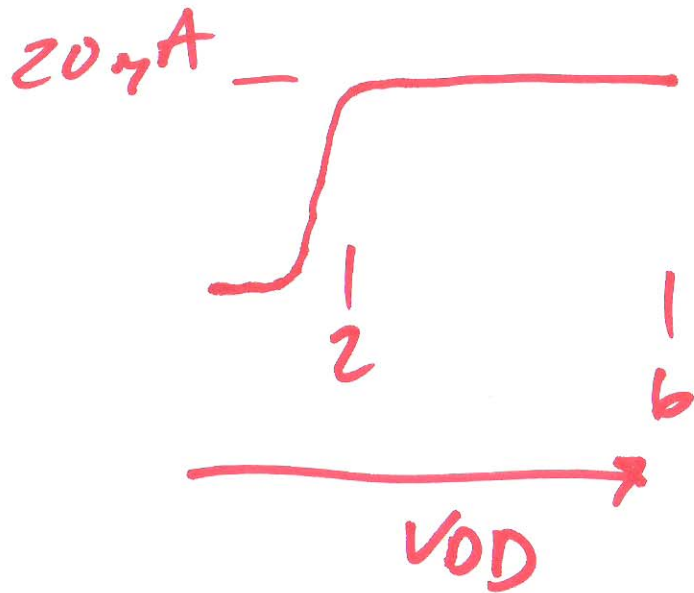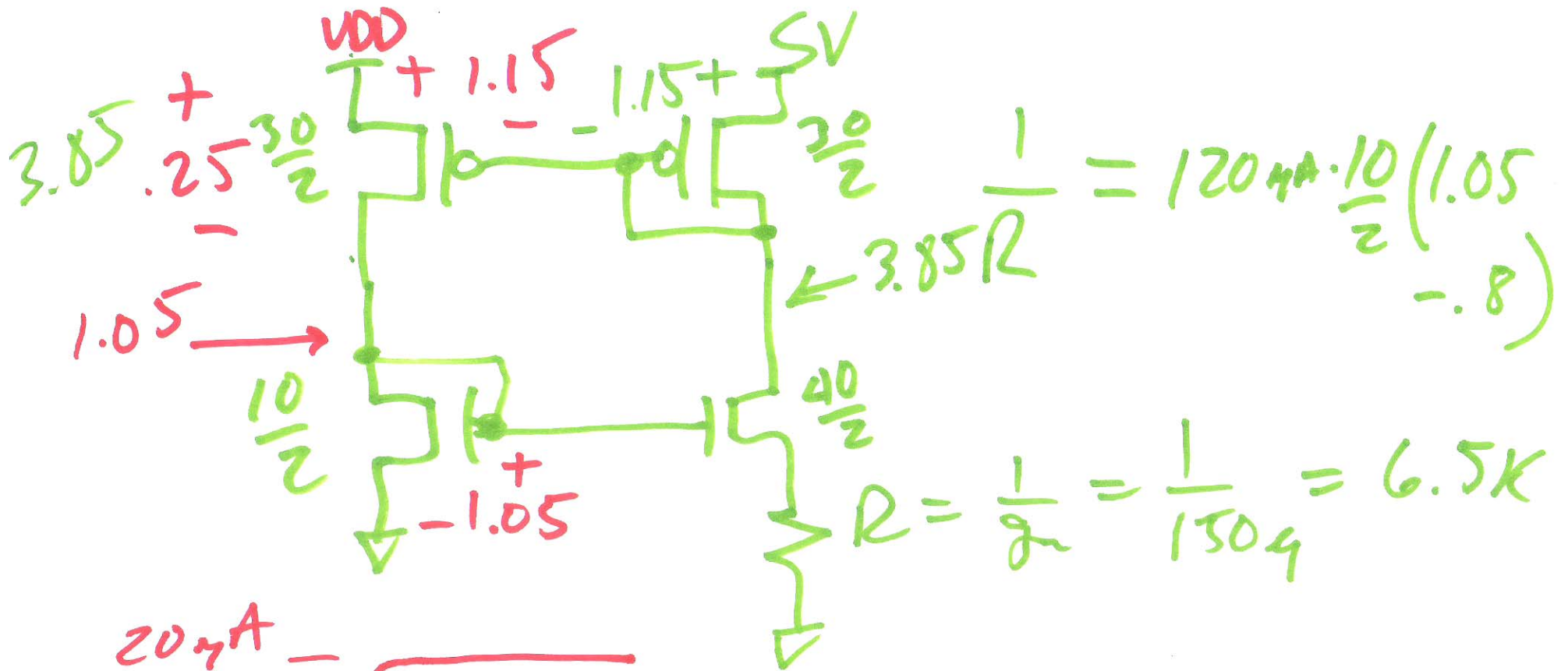


Beta - multiplien - reference

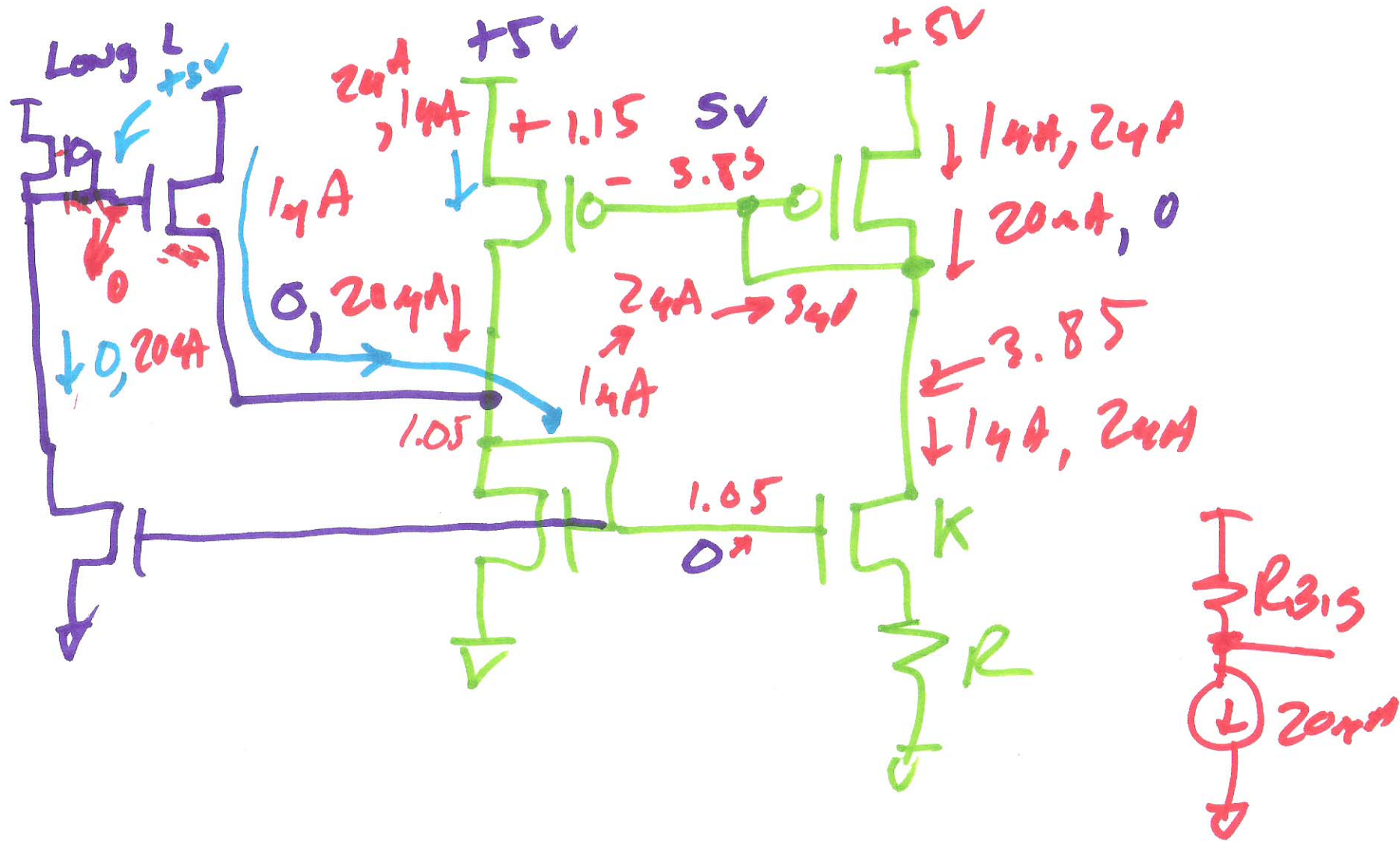

6)

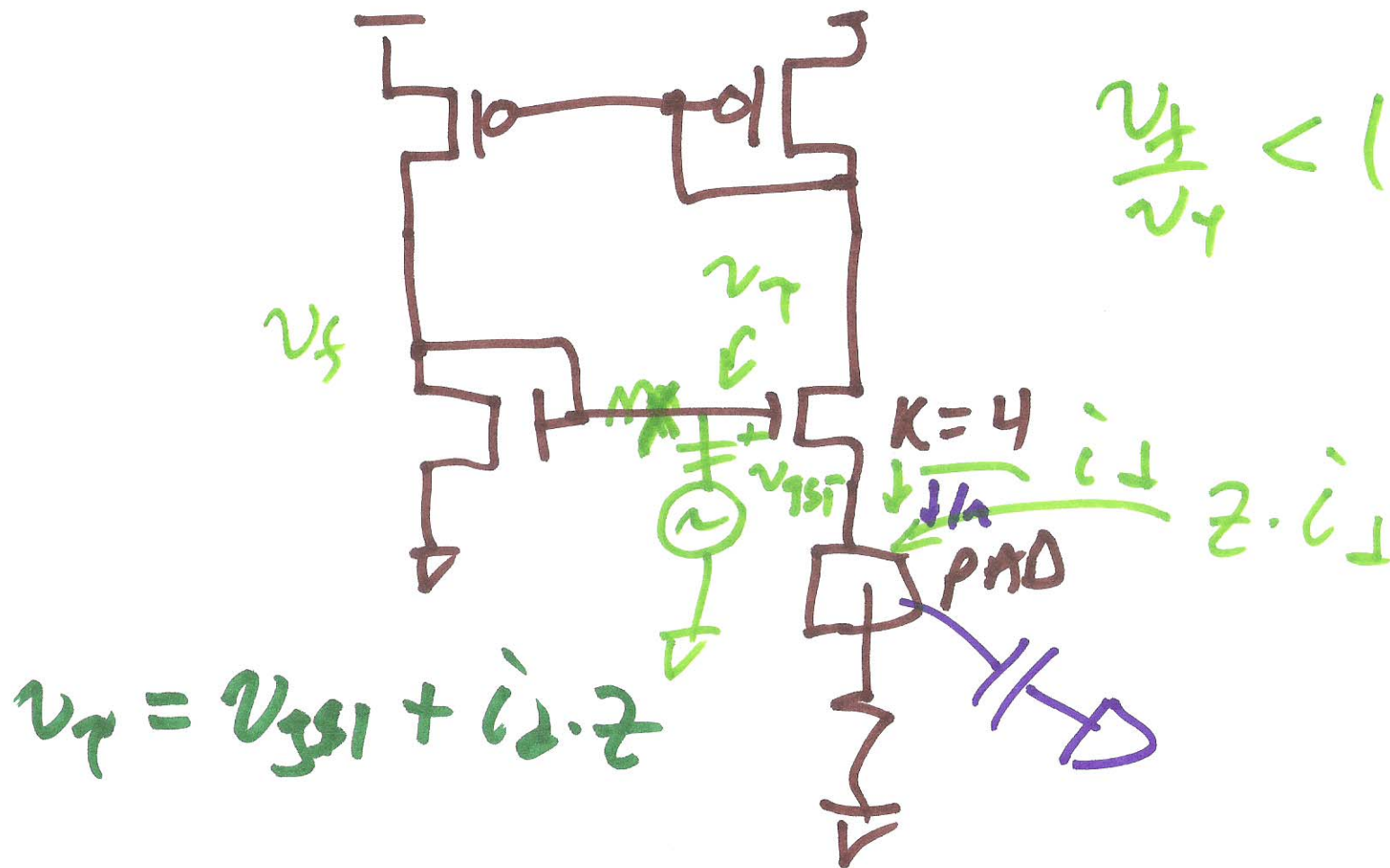

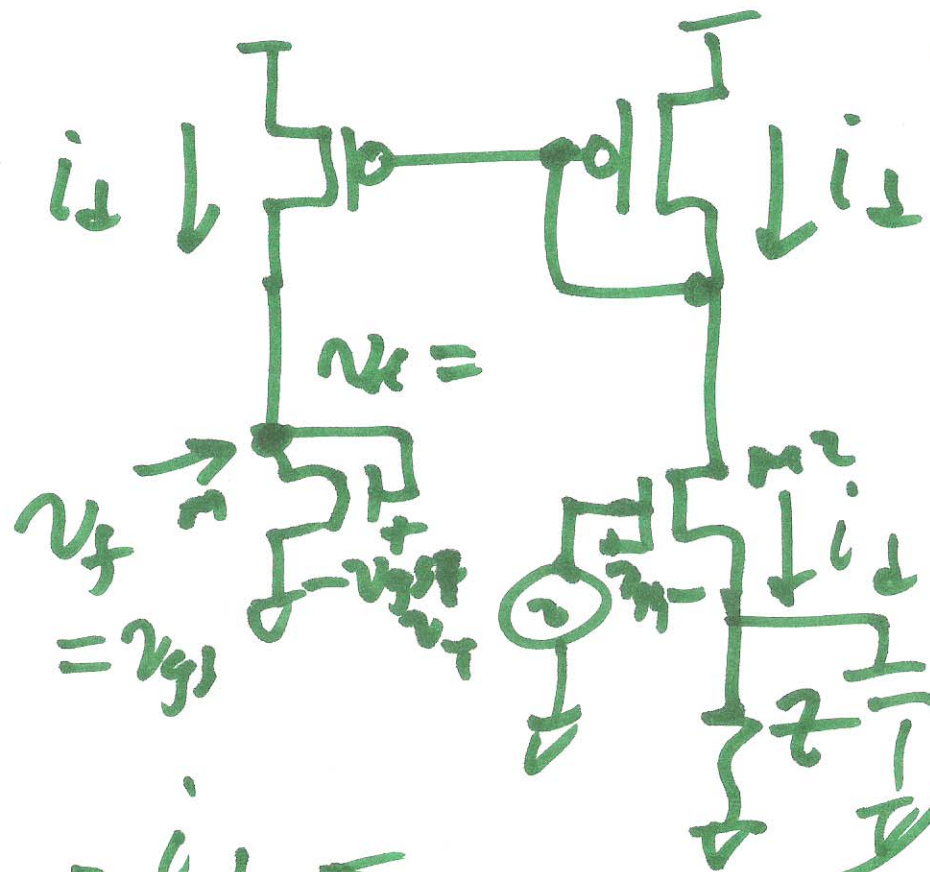

$$v_T = v_{gs2} + i_d \cdot r$$

$$= i_d \left(\frac{1}{g_{m2}} + r \right)$$

$$g_{m1} = \sqrt{2I \cdot K_P \cdot \frac{W}{L}}$$

$$g_{m2} = \sqrt{2I \cdot K_P \cdot \frac{W}{L} \cdot K}$$

$$\sqrt{K} g_{m1} = g_{m2}$$

$$v_f = v_{gs} = \frac{i_d}{g_{m1}}$$

$$v_f = \frac{v_T}{\frac{1}{g_{m2}} + r} \cdot \frac{1}{g_{m1}} \Rightarrow \frac{v_f}{v_T} = \frac{1}{\frac{1}{\sqrt{K}} + r \cdot \frac{g_{m1}}{W/L}}$$

8)