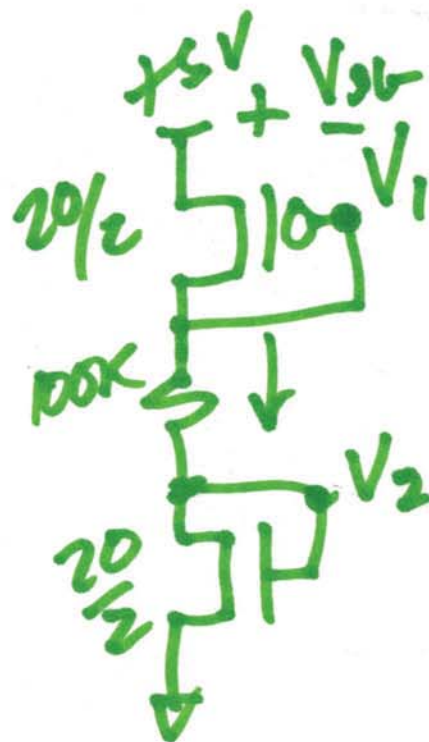


Lecture 11

EE 420 / ELG 620

Feb. 23, 2016



$$V_{gs} = 5 - V_1$$

$$V_{gs} = V_2$$

$$I_D = \frac{V_1 - V_2}{100K}, \quad V_1 - V_2 = 10^5 I_D$$

$$V_{DD} - V_{gs} - I_D \cdot 100K - V_{gs} = 0$$

$$V_2 = \sqrt{\frac{2I_D}{K_n \cdot \frac{20}{2}}} + V_{THN}$$

$$V_{gs} = V_{DD} - V_1 = \sqrt{\frac{2I_D}{K_n \cdot \frac{20}{2}}} + V_{THP}$$

$$I_D \cdot 10^5 = -\sqrt{\frac{2I_D}{K_P \cdot \frac{20}{2}}} - \cancel{V_{THP}} + \cancel{V_{DD}}$$

$$-\sqrt{\frac{2I_D}{K_P \cdot \frac{20}{2}}} - \cancel{V_{THN}} \sqrt{\frac{1}{2004}} = \frac{1}{14 \cdot 10^3}$$

$$I_D \cdot 10^5 = 3.3 - \sqrt{\frac{2I_D}{40 \mu A \cdot 10}} \left(1 + \frac{1}{\sqrt{3}}\right)$$

$$\text{let } x = \sqrt{I_D}, x^2 = I_D$$




$$x^2 \cdot 10^5 + x \cdot \frac{10^3(1 + \frac{1}{1.7})}{14 \cdot 10^3} - 3.3 = 0$$

$$x = \frac{-10^{-3} \pm \sqrt{10^{-6} + 4(3.3)10^{-5}}}{2}$$

$$x^2 + x \cdot \frac{10^{-2}(1 + \frac{1}{1.7})}{14} - 3.3 \cdot 10^{-5} = 0$$

$$x = \sqrt{I_D}$$

2)

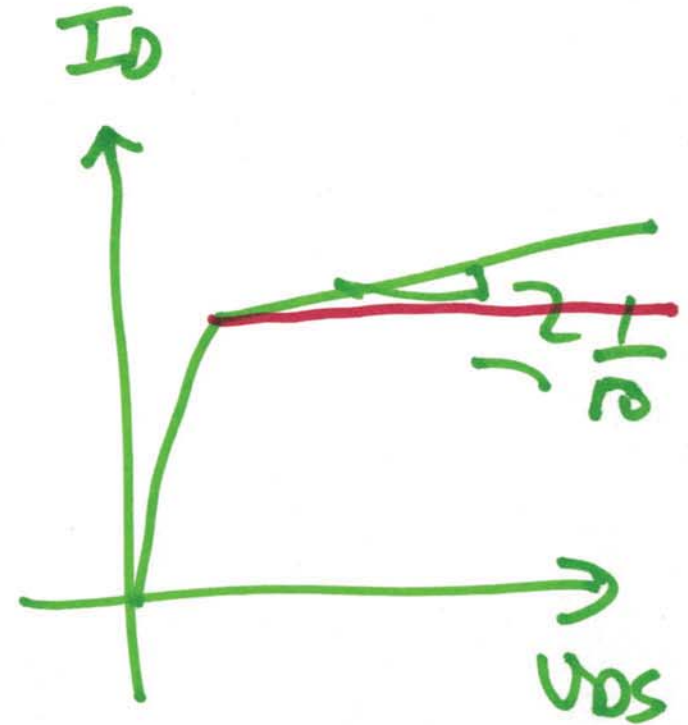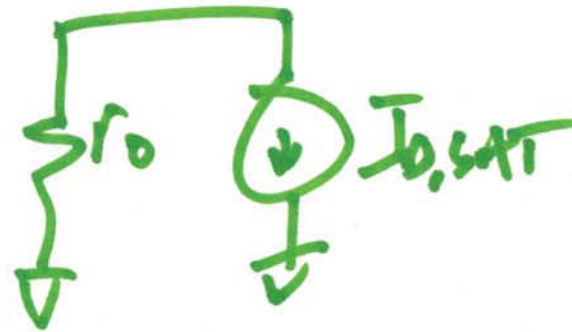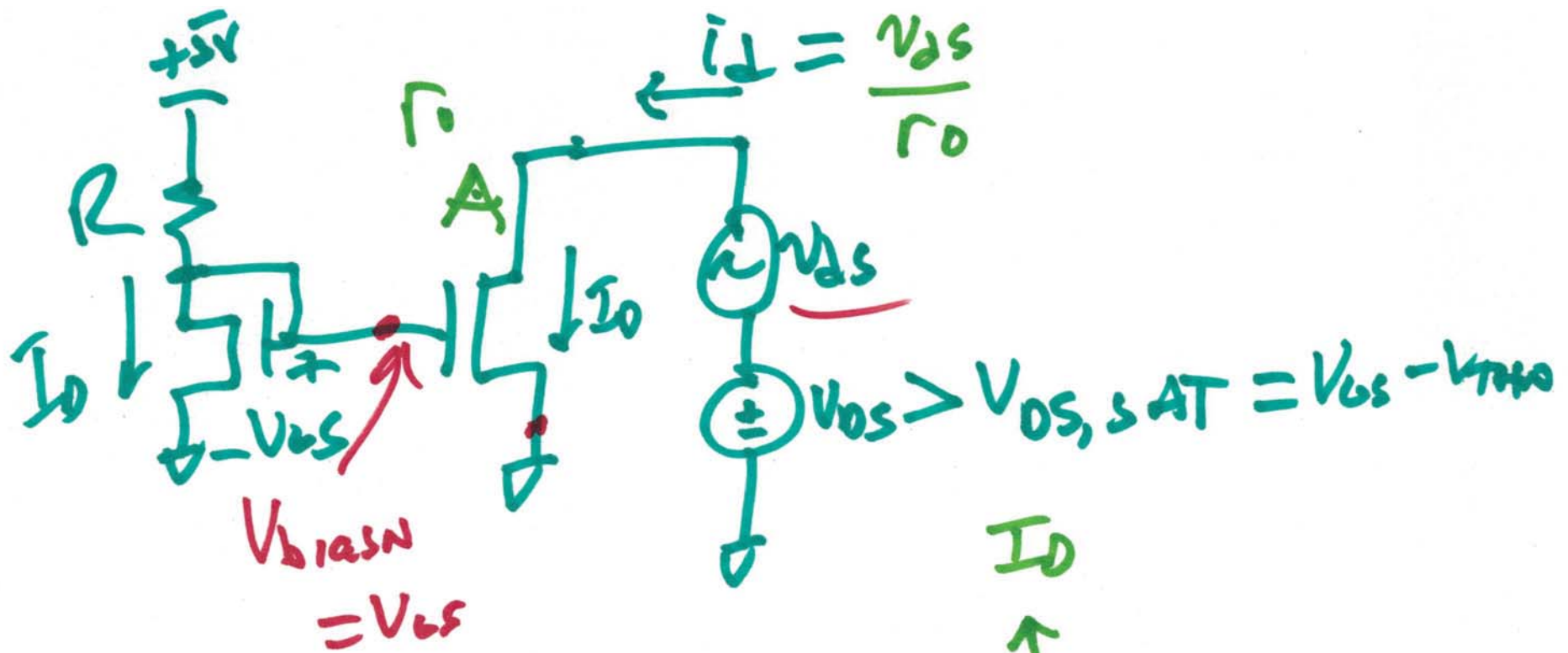


3)


## CASCODE →


Common - ~~CATHODE~~  
driving a common-  
SOURCE

~~Grid~~ GATE

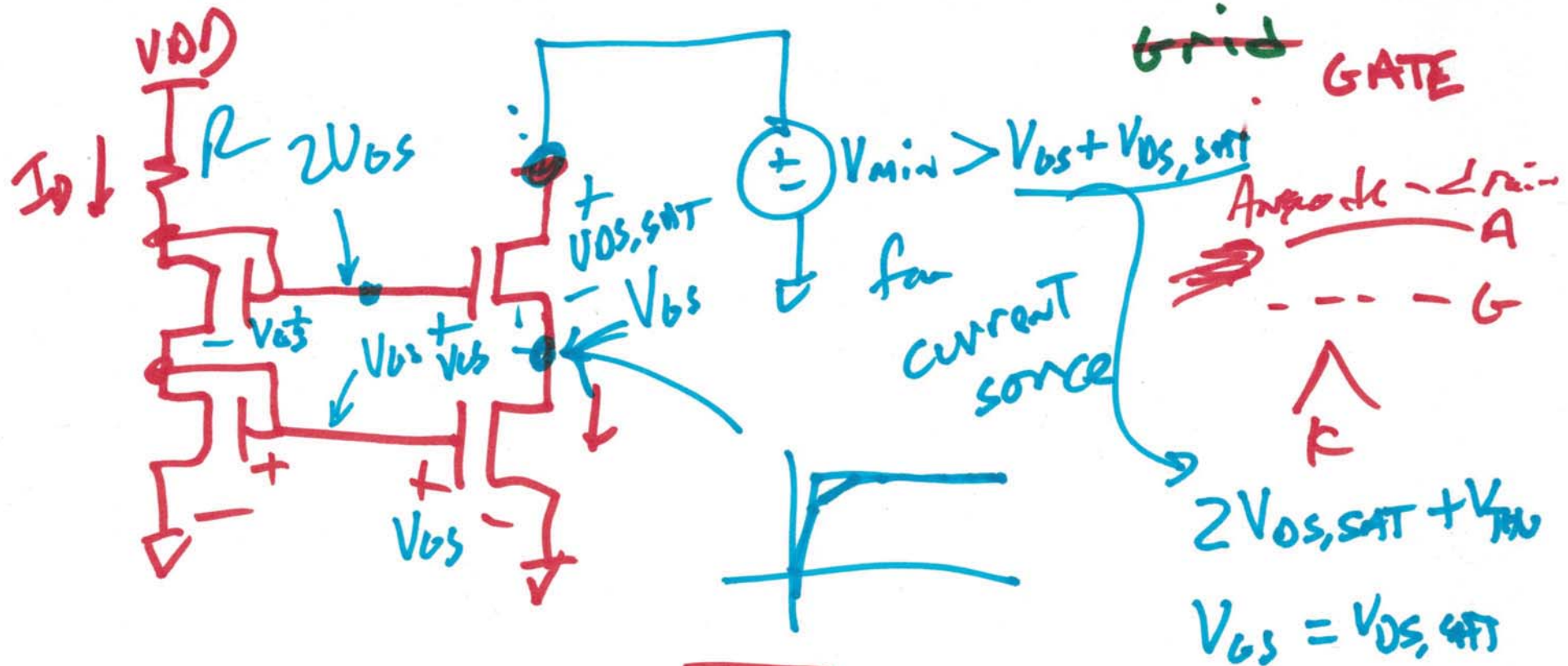
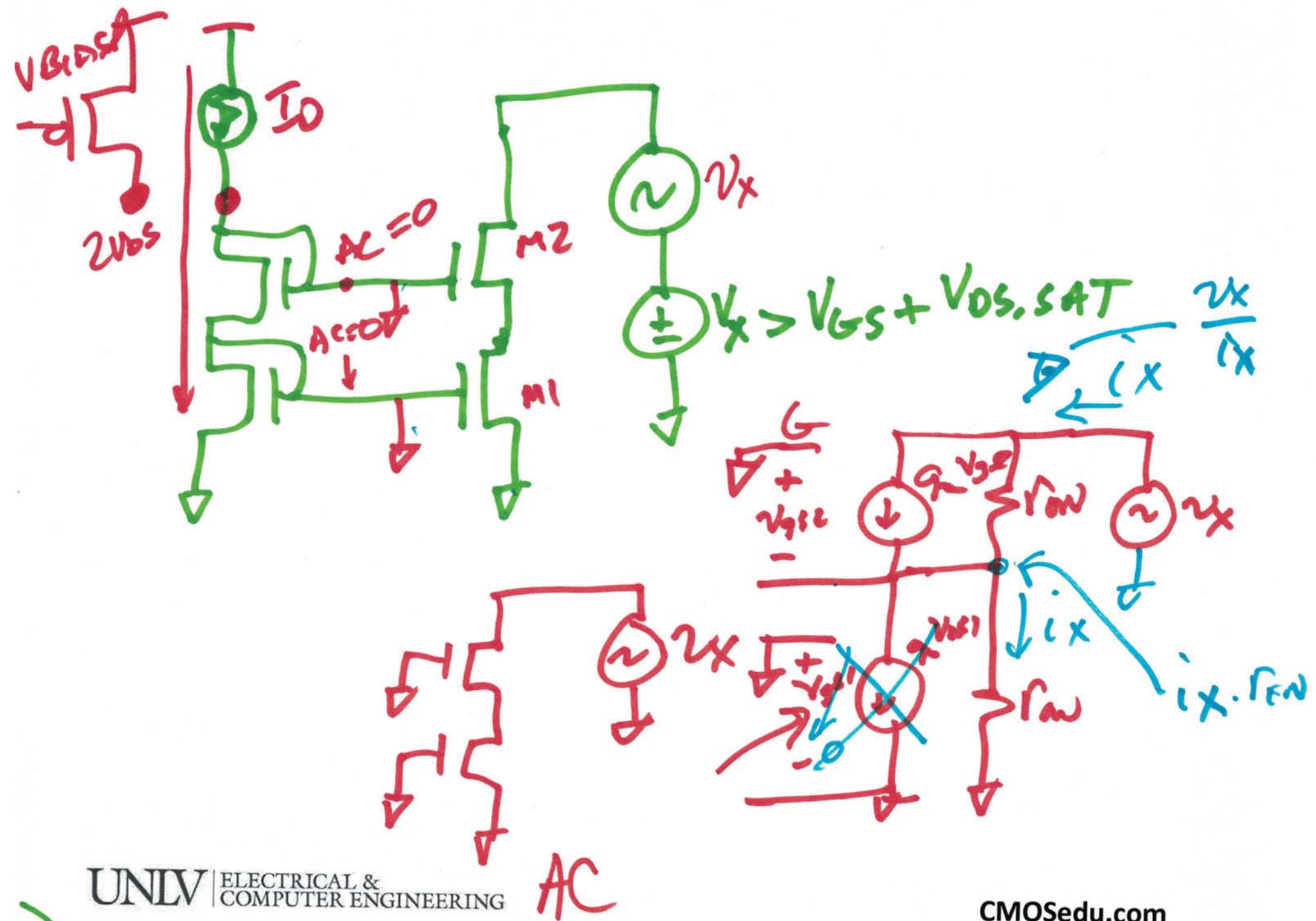
$$V_D = \frac{V_{DD} - 2V_{GS}}{R}, V_{GS} = \sqrt{\frac{2I_D}{\beta_n}} + V_{THN}$$



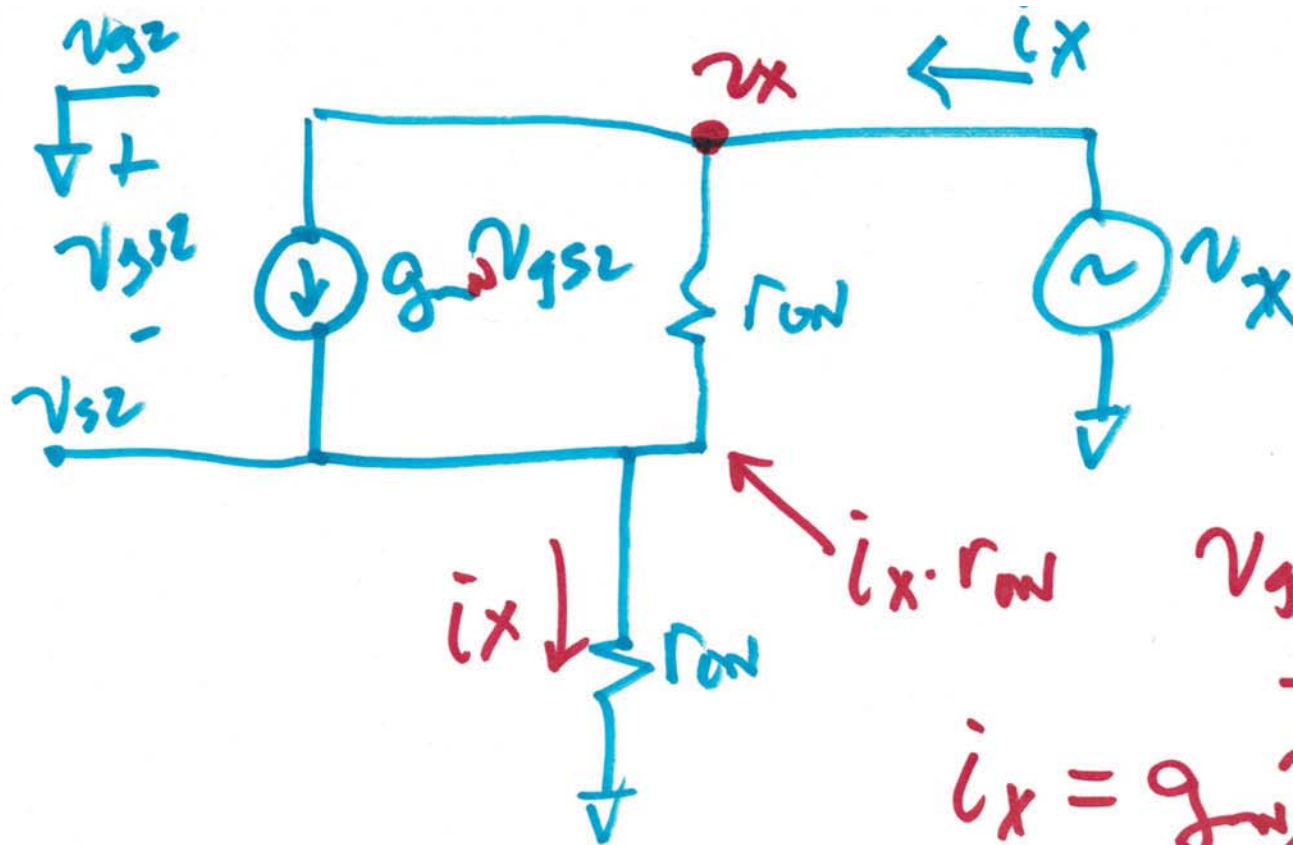

$$R_{out} = \frac{v_x}{i_x}$$

$$v_{gs2} = -i_x \cdot r_{on}$$

$$i_x = g_m v_{gs2} + \frac{v_x - i_x r_{on}}{r_{on}}$$

to C.M.

$$i_x (1 + r_{on} g_m + 1) = v_x \cdot \frac{1}{r_{on}}$$

$g_m r_{on} \cdot r_{on}$  cascode  
 $v_{out} \rightarrow v_{in}$

$$\frac{v_x}{i_x} = 2r_{on} + g_m r_{on}^2 \approx \underline{\underline{g_m r_{on}^2}}$$

