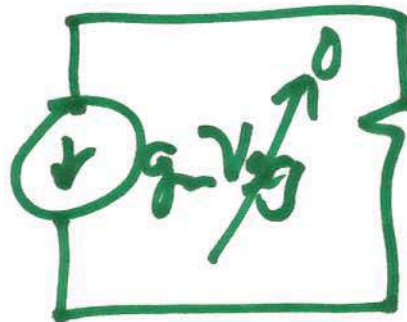


720.15


EE 420 / ECE 620

$$i_c = \frac{10^{-3}}{4 \text{ M}\Omega} = 250 \text{ nA}$$




Lecture 13

March 1, 2016

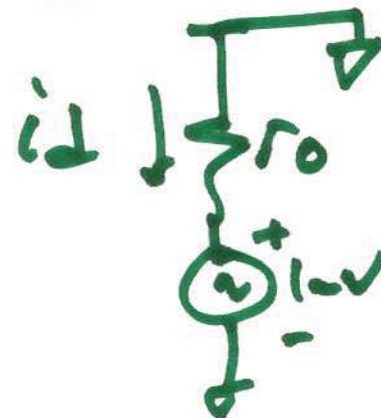

$$i_d = -\frac{v_g}{r_o}$$

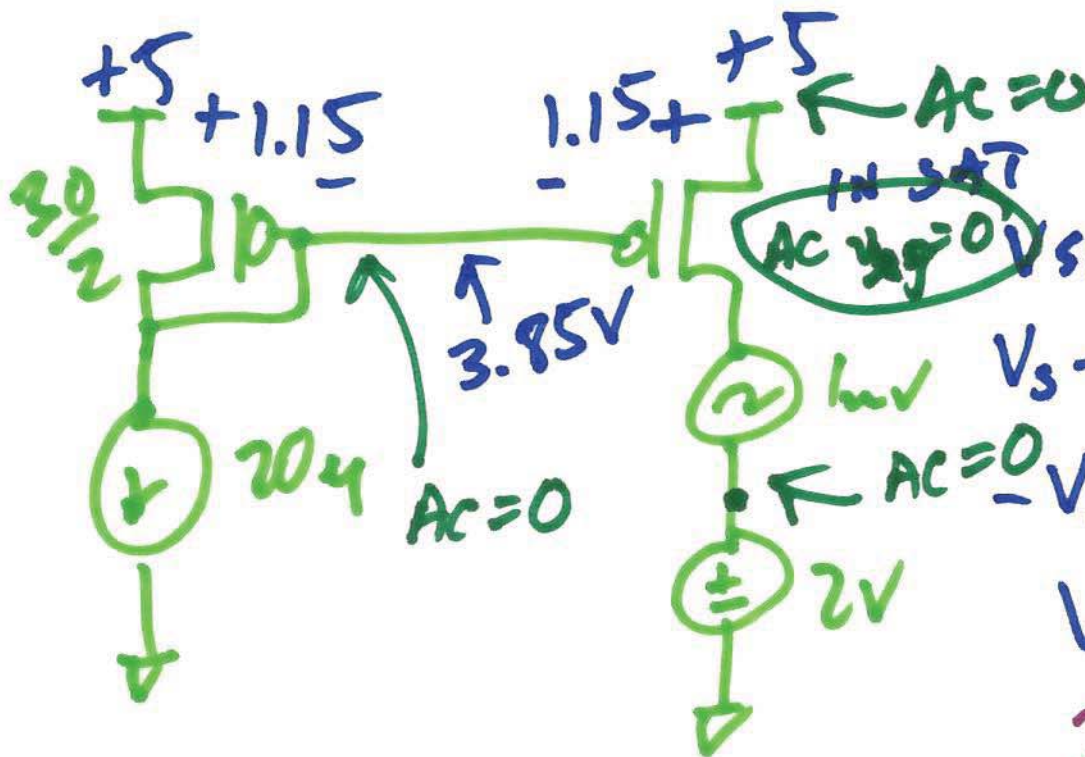

$$V_{SD} \geq V_{SD} - V_{THP}$$

$$V_S - V_D \geq V_S - V_G - V_{THP}$$


$$V_D \geq -V_G - V_{THP}$$

$$V_D \leq V_G + V_{THP}$$

$$2 \leq 3.85 + .9$$

CMOSedu.com

yes! IN SAT

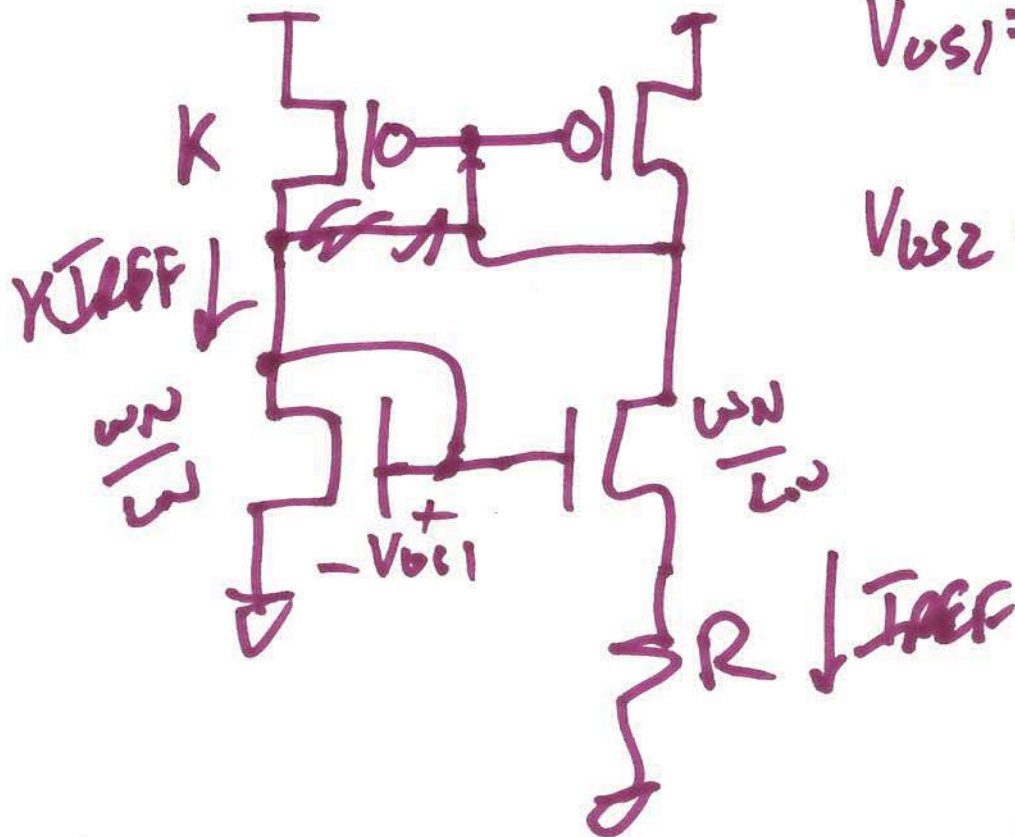



$$V_{GS1} = \sqrt{\frac{K I_{DEF} \cdot 2}{\beta_N}} + V_{THN}$$

$$V_{GS2} = \sqrt{\frac{I_{DEF} \cdot 2}{\beta_N}} + V_{THN}$$

$$I_{DEF} = \frac{V_{GS1} - V_{GS2}}{R} = \sqrt{\frac{K I_{DEF} \cdot 2}{\beta_N R^2}} - \sqrt{\frac{I_{DEF} \cdot 2}{\beta_N R^2}}$$


$$\sqrt{I_{DEF}} = \sqrt{\frac{2}{\beta_N R^2}} (\sqrt{K} - 1)$$
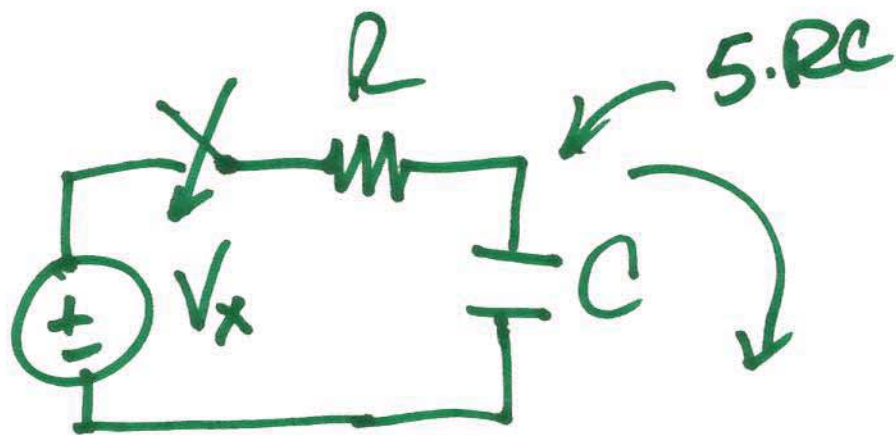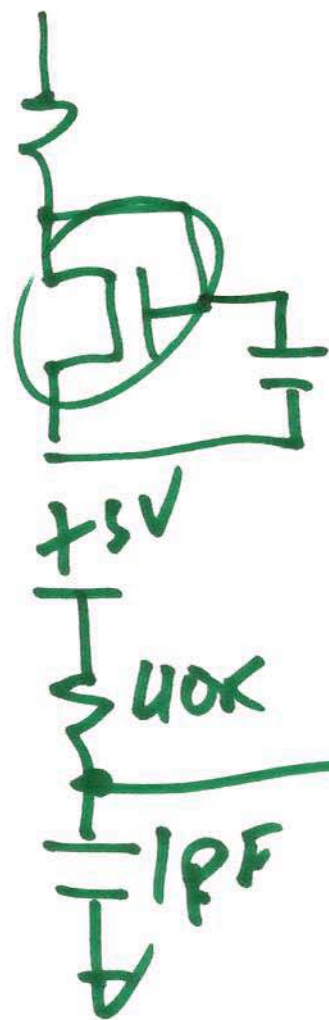
$$I_{DEF} = \frac{2}{\beta_N R^2} (\sqrt{K} - 1)^2, K > 1$$




$$V_{out} = V_x \left(1 - e^{-t/RC} \right)$$

20ns

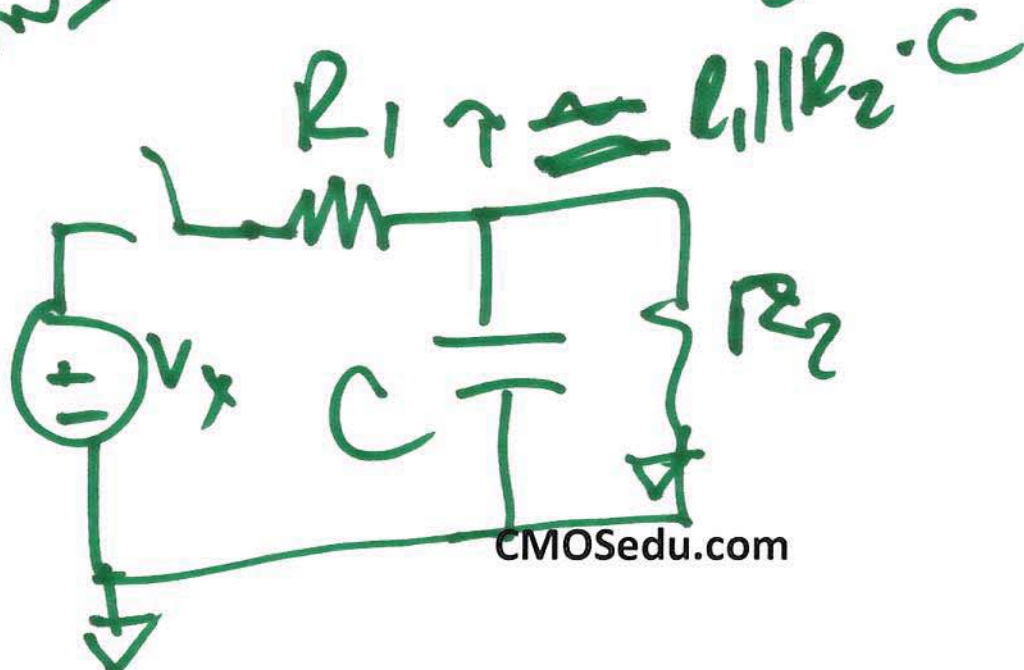


9)

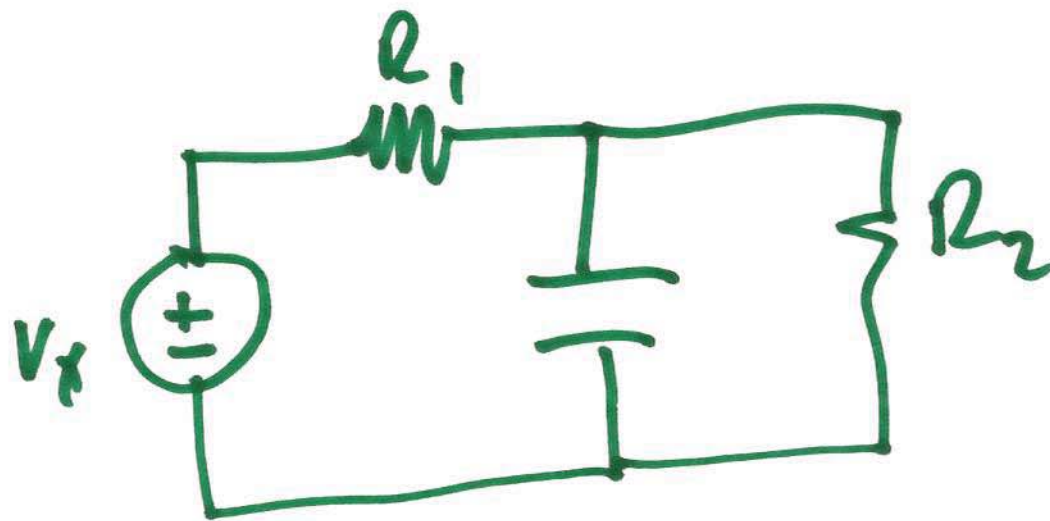

$$V_{TH} = V_{oc}$$


$$= V_X \cdot \frac{R_2}{R_1 + R_2}$$

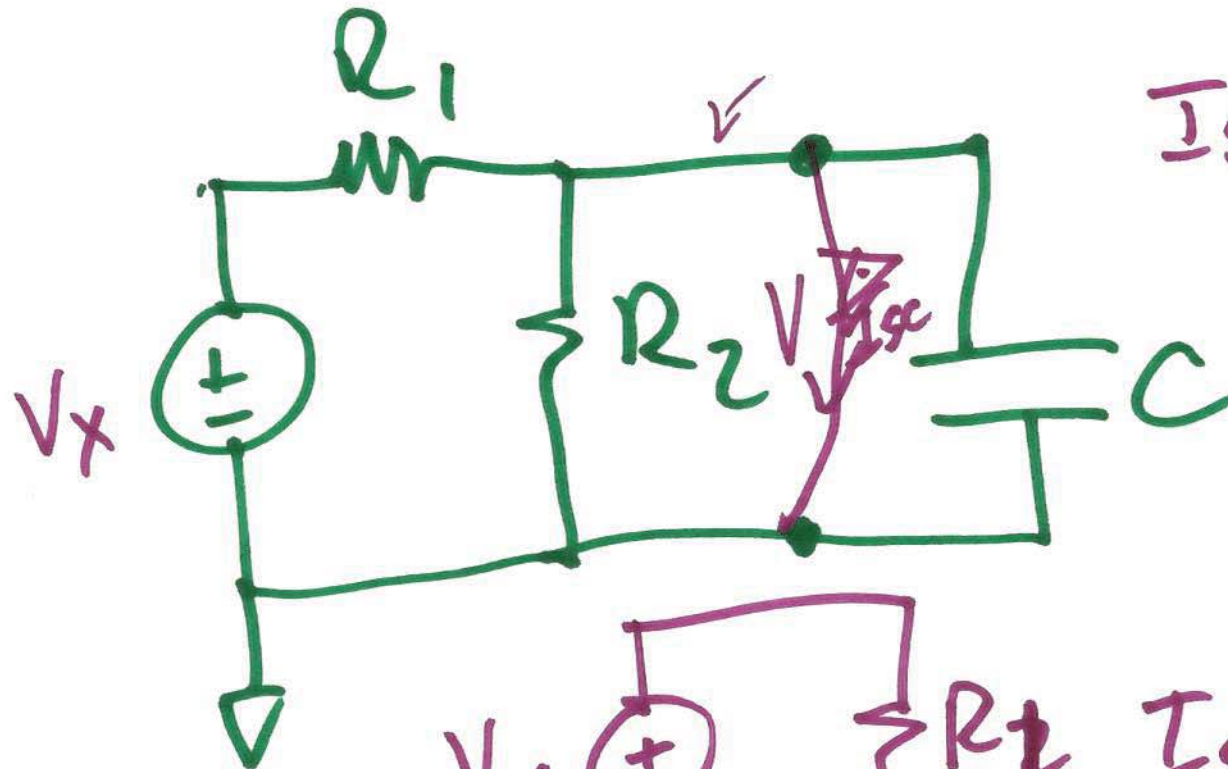

$$I_{sc} = \frac{V_X}{R_1}$$


$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

$$= \frac{R_1 \cdot R_2}{R_1 + R_2}$$

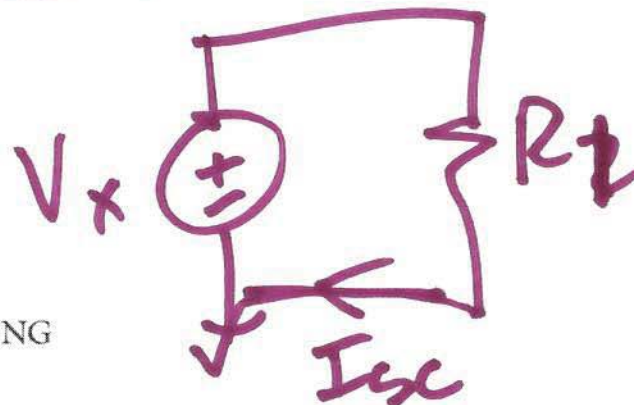



$$I_{sc} = \frac{V_X}{R_1}$$

$$\frac{V_X \cdot R_2}{R_1 + R_2}$$

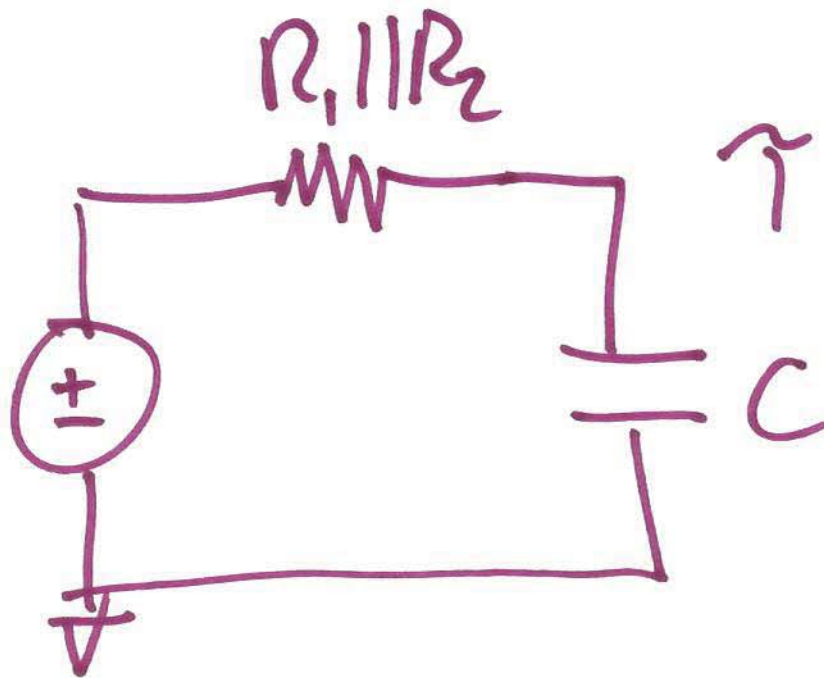


$$\tau = R_1 || R_2 \cdot C$$

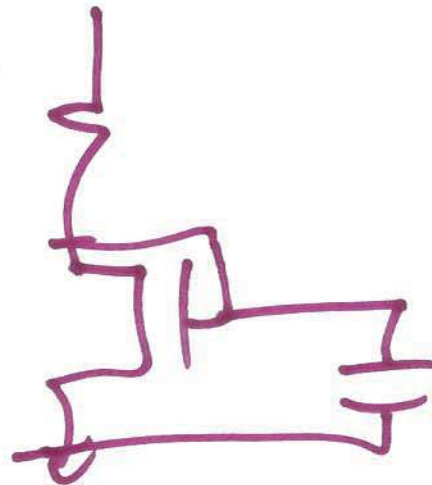

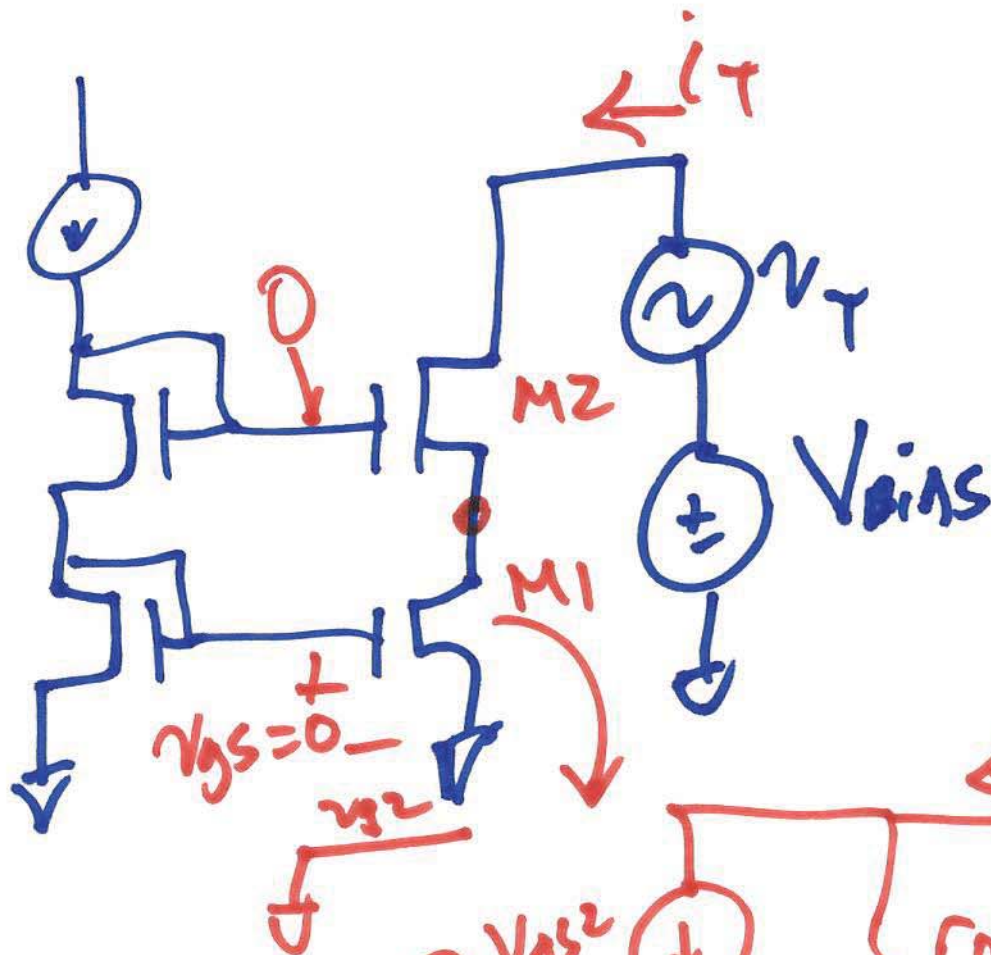



$$i_T = g_m(-i_T r_{o1}) + \frac{v_T - (-i_T r_{o1})}{r_{o2}}$$
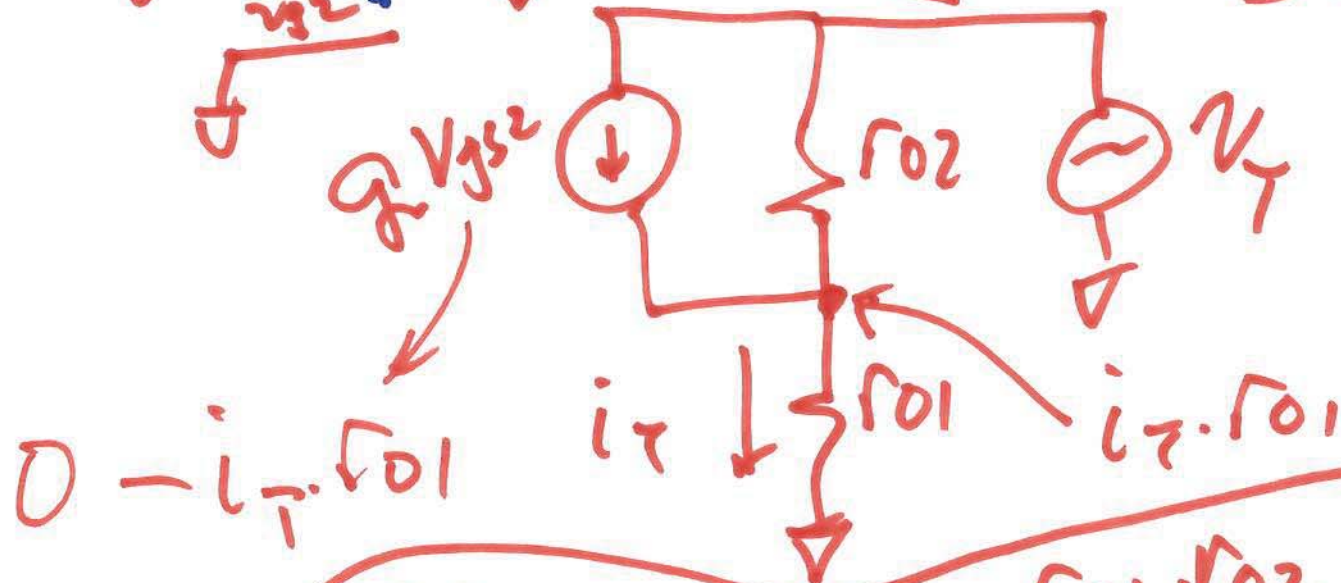
$$i_T \left(1 + g_m r_{o1} + \frac{r_{o1}}{r_{o2}} \right) = v_T / r_{o2}$$


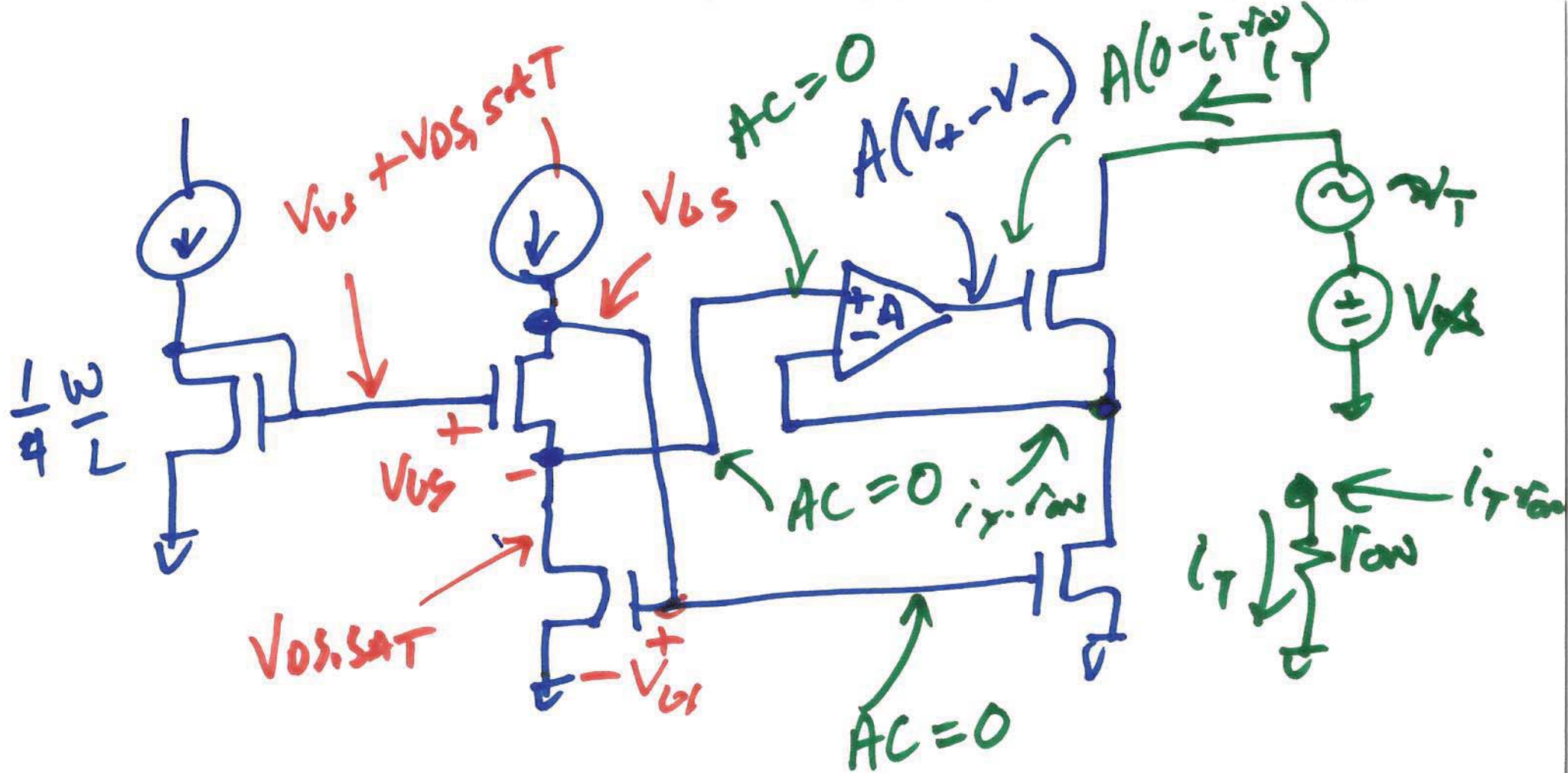
$$\frac{v_T}{i_T} = r_{o2} + g_m r_{o1} r_{o2} + r_{o1}$$



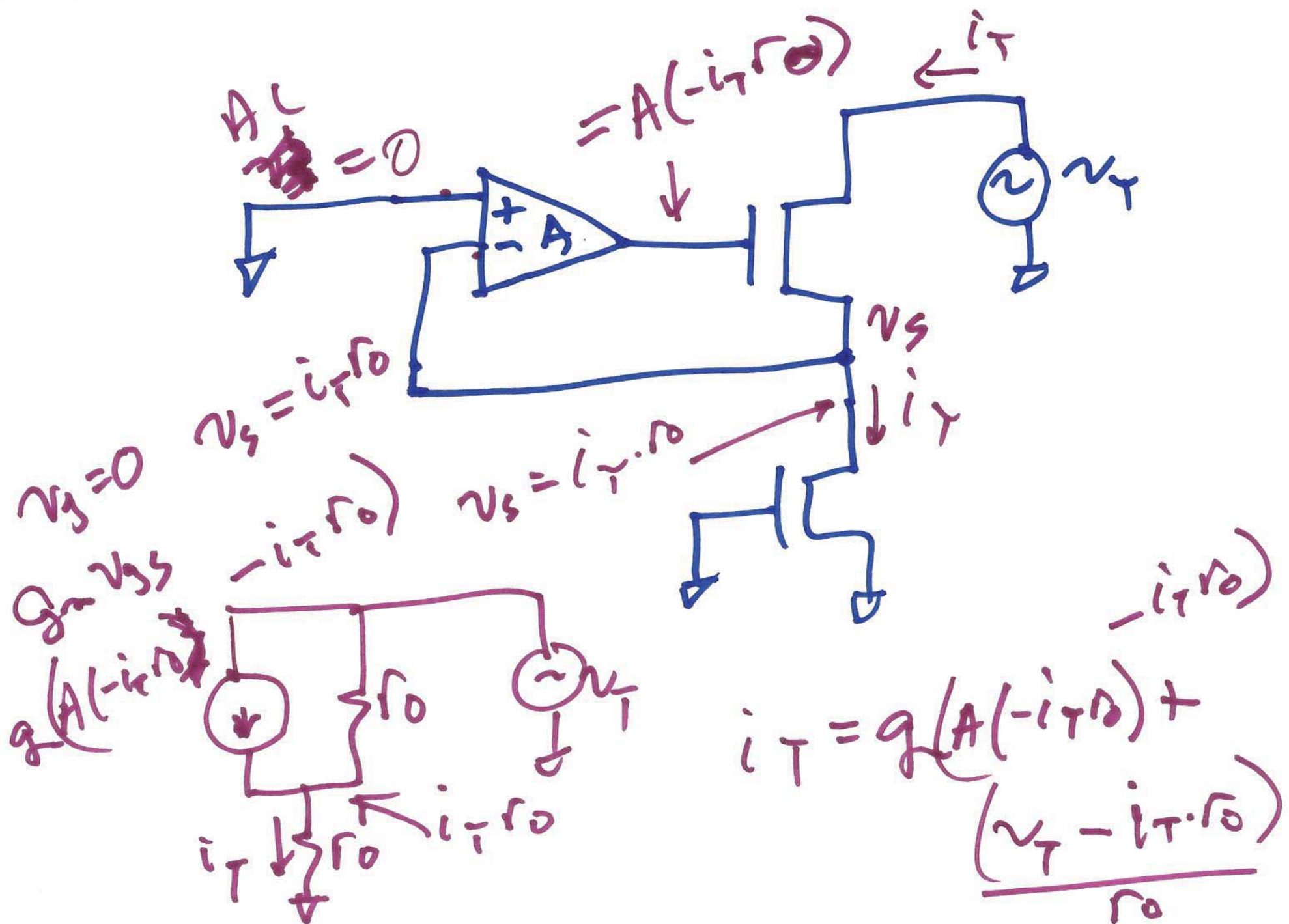

$$i_T = g_m(-i_T r_o(1+A)) + \frac{v_T}{r_o} - i_T$$

$$i_T(1 + 1 + g_m r_o(1+A)) = \frac{v_T}{r_o}$$

$$\frac{v_T}{i_T} = g_m r_o^2(1+A) + \cancel{2r_o}$$