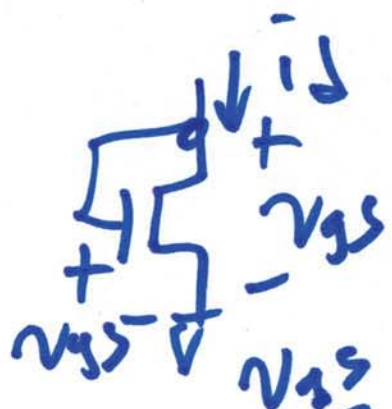


EE 420 / ECG 620

Analog IC Design

Lecture 16

March 15, 2016




$$\frac{v_{gs}}{i_d} = \frac{1}{g}$$


$$\frac{v_{nt}}{v_{in}} = -g_m r_{on} || r_{op}$$

$$= -1.5 \mu A \cdot 5 M\Omega$$

$$= -150 \cdot 2.2$$

$$= -330 \frac{V}{V}$$

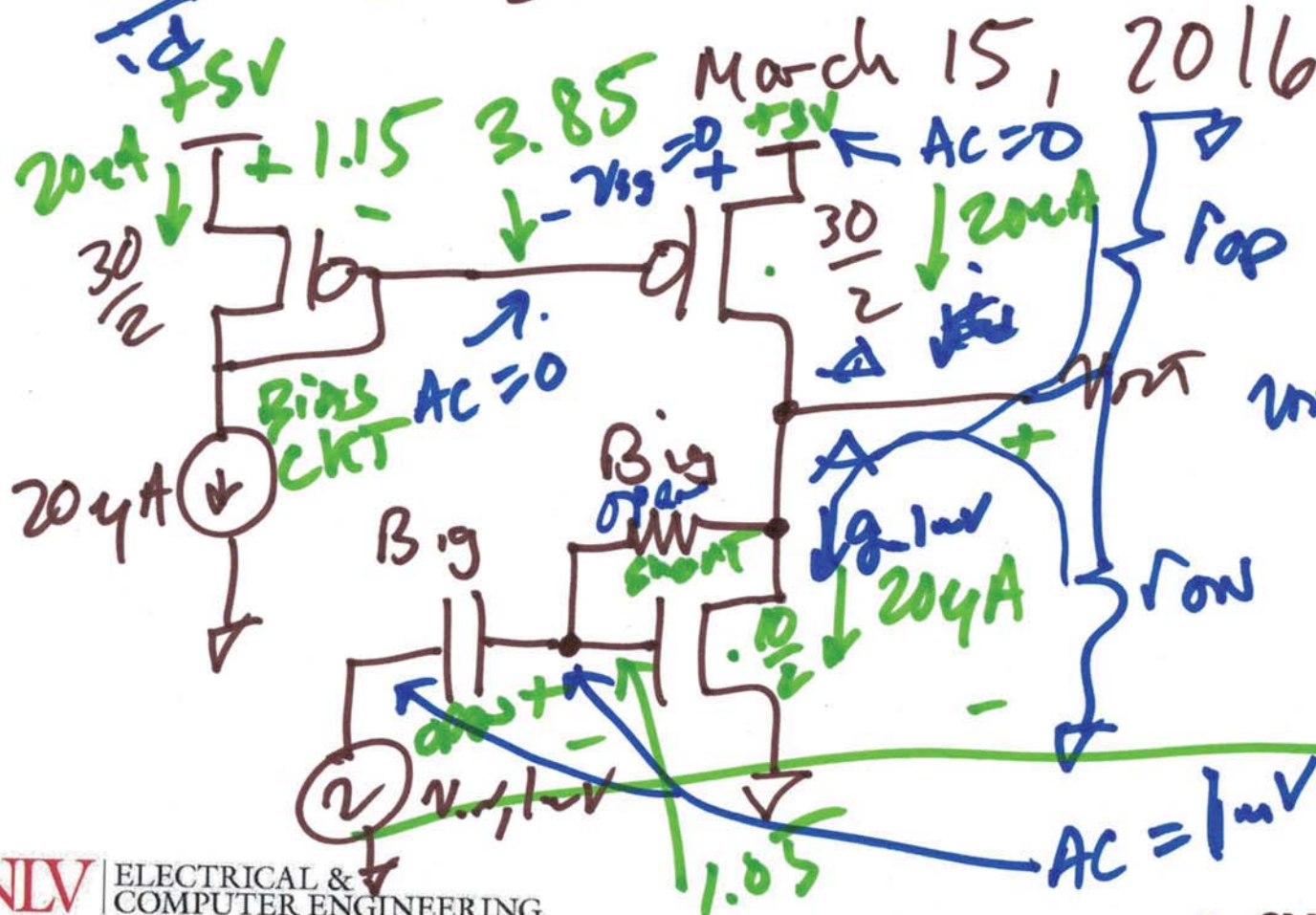

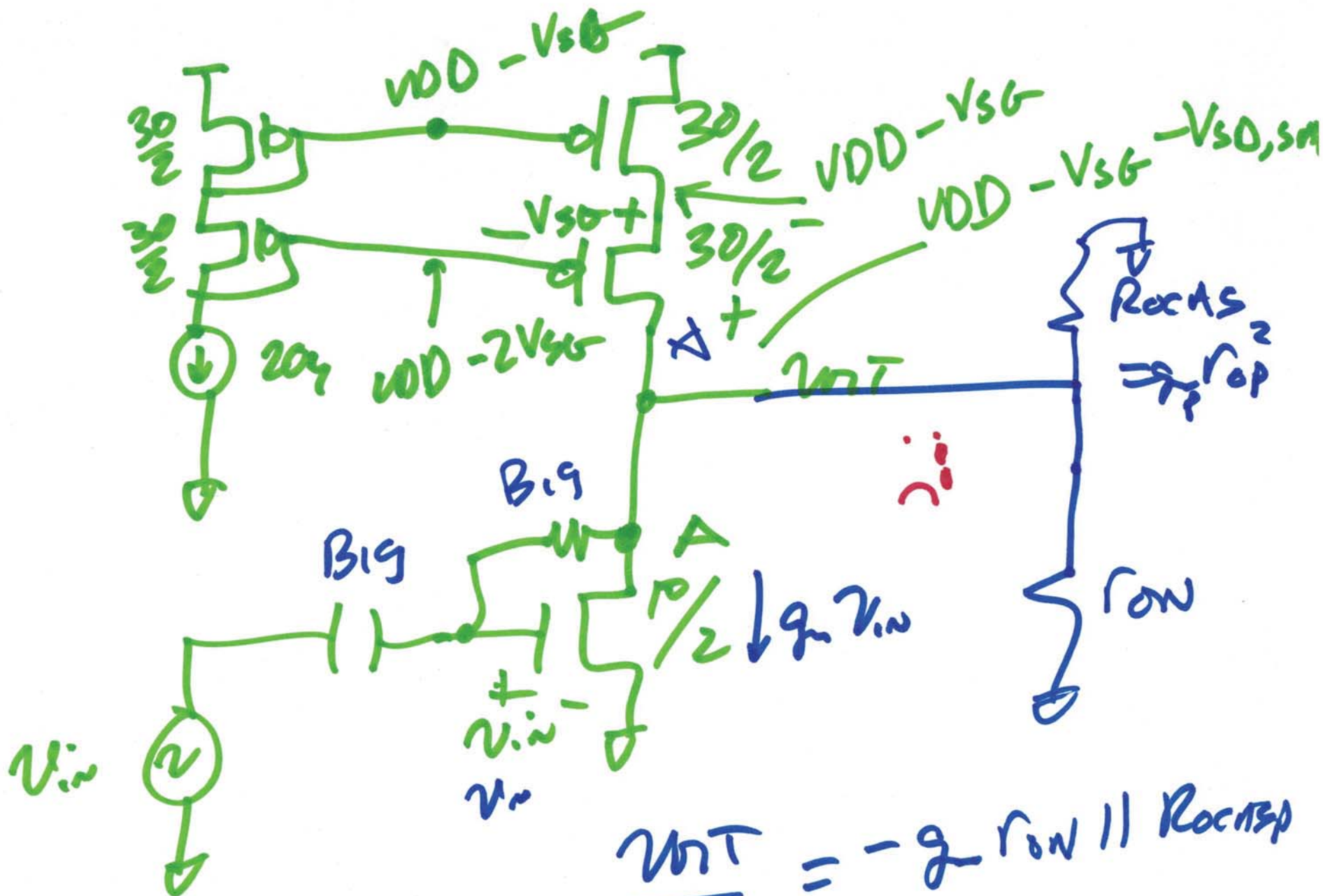

$$\frac{v_{out}}{v_{in}} = -g_m r_{on} \parallel R_{out,DM}$$

$$\approx -g_m r_{on}$$

2)

$$V_{GS} = \frac{18.2 + 14.36}{24}$$

$$V_{GS} = 1.36V$$

$$V_{in} = 2V$$

$$+5V$$

$$100k \text{ DC} = 1.36$$

12

$$V_{out} = ? \quad \frac{V_{out}}{V_{in}} = -g_m (r_{out} || 100k)$$

$$\frac{5 - V_{GS}}{100k} = \frac{120 \mu A/V^2 \cdot \frac{1}{2} (V_{GS} - 0.8)^2}{100k}$$

$$g_m = \sqrt{2 \cdot 120 \mu A/V^2 \cdot \frac{10}{5} \cdot 30 \mu A} = \sqrt{10^{-5} \cdot 120 \cdot 10^{-6}} = 0.8$$

$$V_{GS} = \frac{18.2}{24} \quad 5 - V_{GS} = 12(V_{GS}^2 - 1.6V_{GS} + 0.64)$$

$$0 = V_{GS} - 5 + 12V_{GS}^2 - 19.2V_{GS} + 7.6$$

24

$$= 12V_{GS}^2 - 18.2V_{GS} + 2.6$$

$$I_D = \frac{5 - 1.36}{100k} = 36.4 \mu A = I_D$$

CMOSedu.com

3)

