

EE 420 / ECG 620

Analog IC Design

Lecture


22

April 12,

2016

$$f_{3dB} = \frac{1}{2\pi R_{in} || R_{out} \cdot 100F}$$


$$I_{nv} + V_{sg1} - V_{sg2} = 0$$

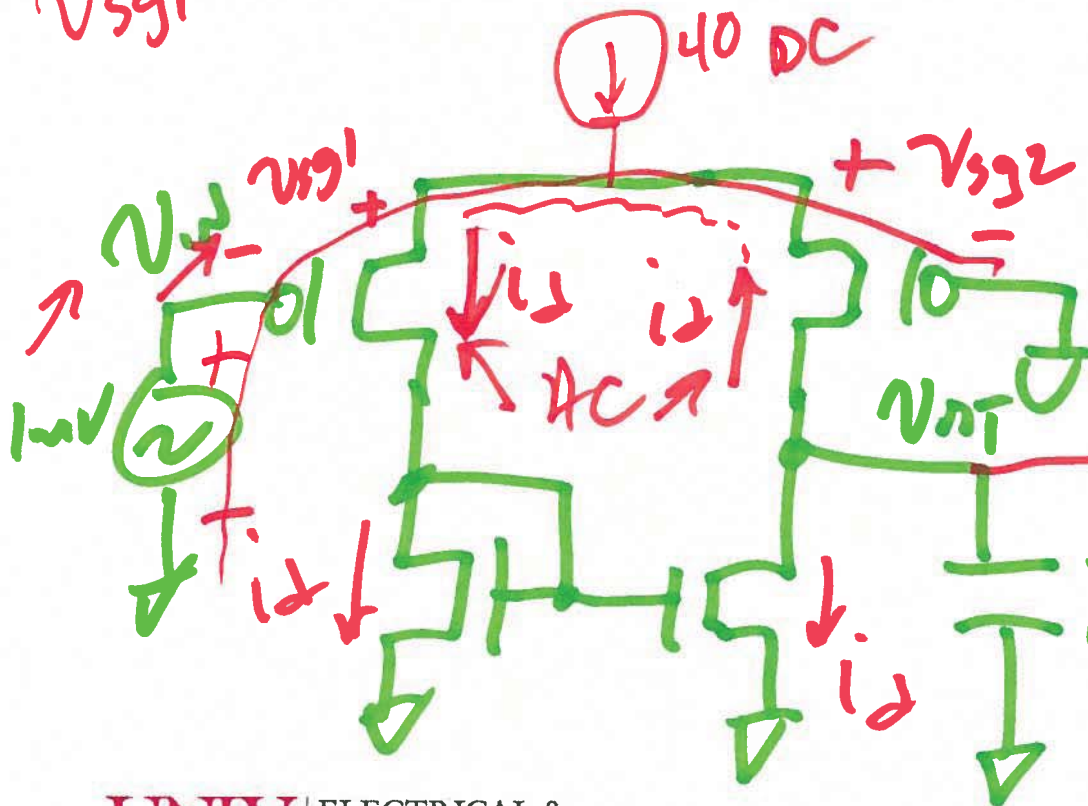

$$1\text{mV} = -2V_{SG1}$$


CMOSedu.com

$V_{SS} = -\frac{1}{2} \text{ mV}$

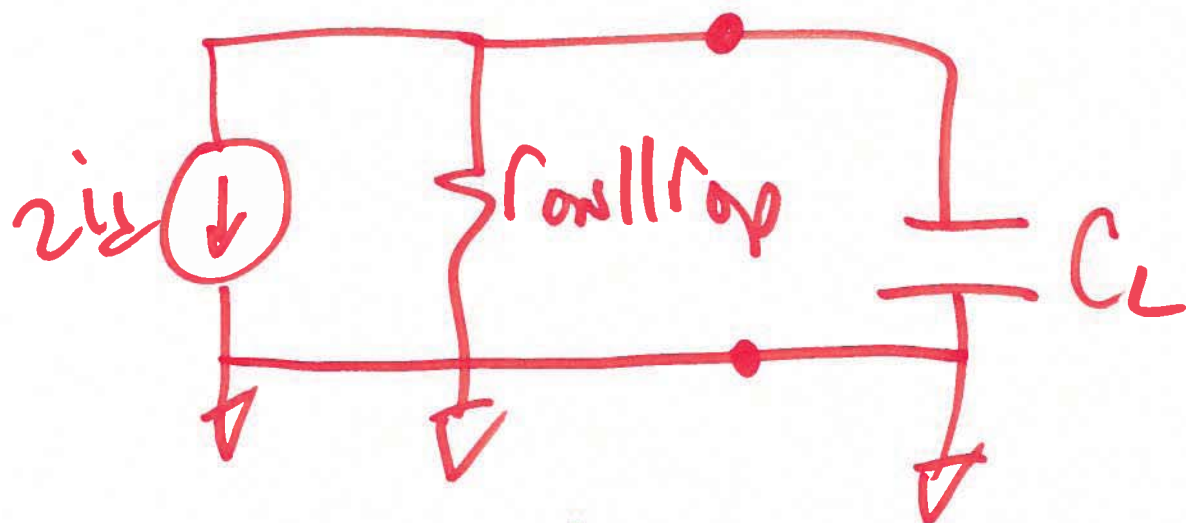

$$1 = 2\pi f_{3dB} \cdot C_L r_{on||rop}$$

$$f_{3dB} = \frac{1}{2\pi C_L \cdot r_{on||rop}}$$

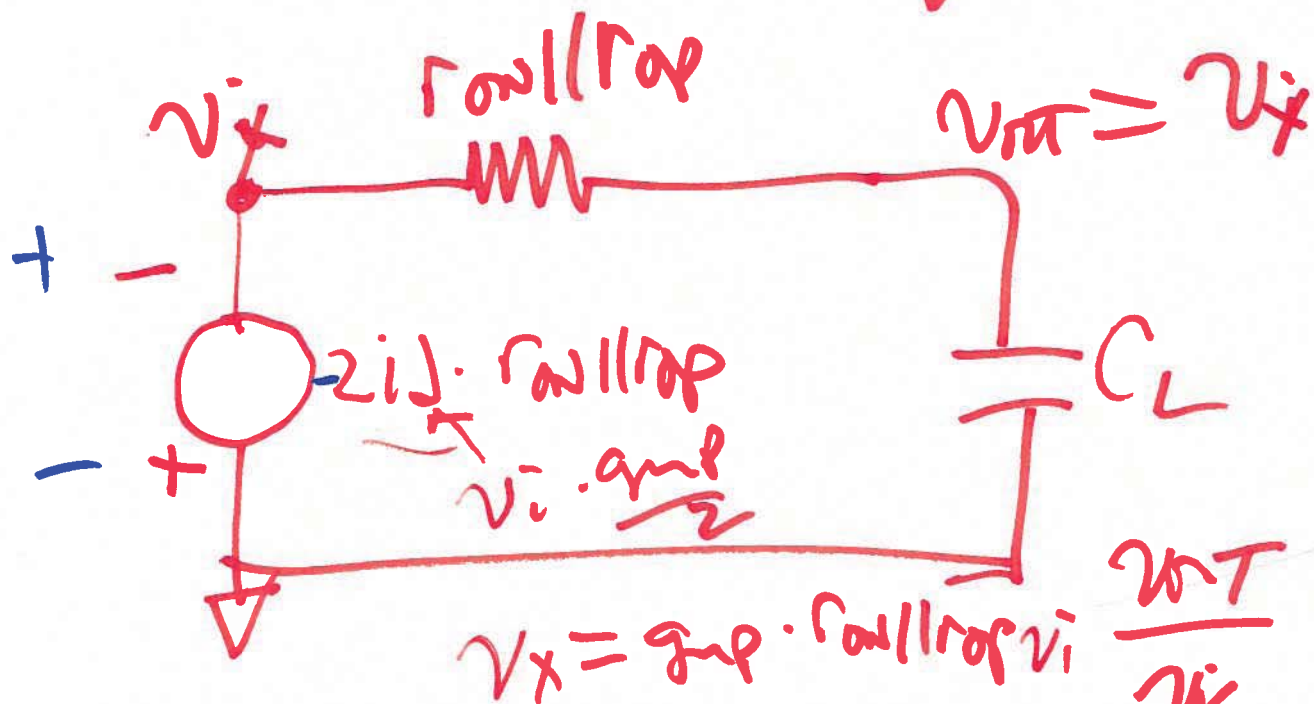


$$v_{out} = v_x \cdot \frac{1/j\omega C_L}{1/j\omega C_L + r_{on||rop}}$$

$$\frac{v_{out}}{v_x} = \frac{1}{1 + j\omega C_L r_{on||rop}}$$

$$= \frac{1}{1 + j \frac{f}{f_{3dB}}}$$


2)

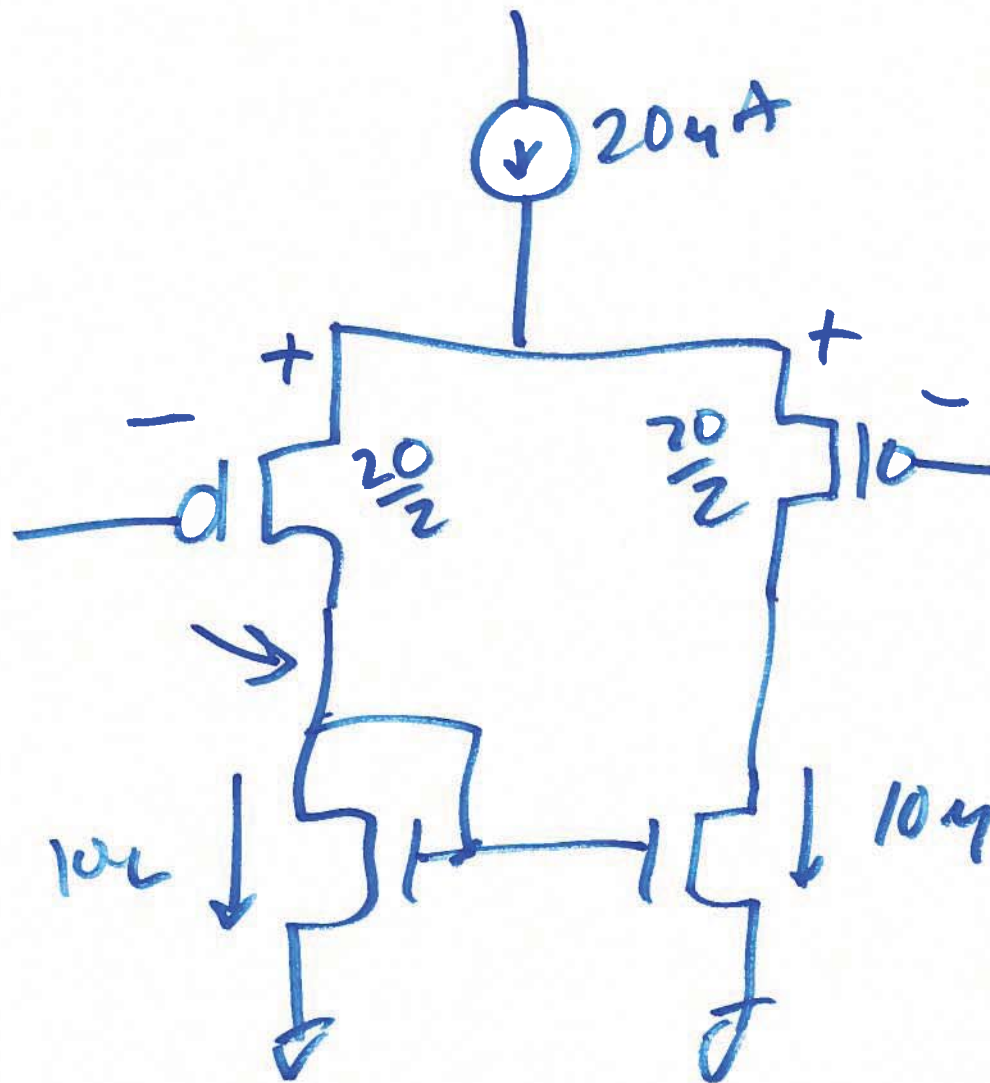

$$V_{SG} = \sqrt{\frac{2 \cdot 10 \mu A}{410 \mu \cdot \frac{20}{2}}} + 0.9$$
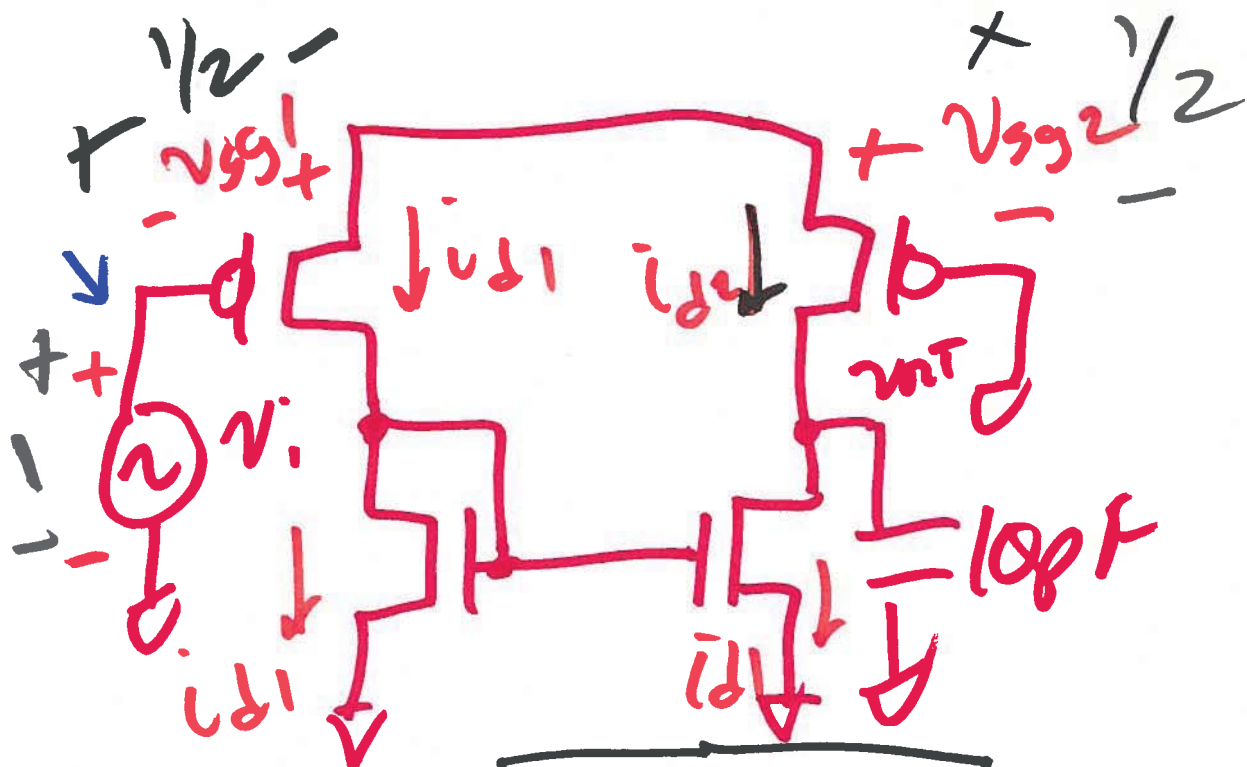
$$V_{SG} = \sqrt{\frac{2 \cdot 10 \mu A}{120 \mu \cdot \frac{10}{2}}} + 0.8$$





$$g_{mp} = \sqrt{2 \cdot 40 \mu \cdot \frac{20}{2} \cdot 10 \mu}$$

$$\left(g_{mp} \cdot \frac{1}{2} \mu V \right) \cdot 2 = g_{mp} \cdot v_i$$

$$v_{oT} = g_{mp} \cdot v_i \cdot r_{oN} \parallel r_{op}$$

$$i_{D1} = -i_{D2}$$

$$v_{SG1} = -v_{SG2}$$

$$v_i + v_{SG1} = v_{SG2}$$

$$v_i = 1 \mu V$$

$$v_{SG1} = -\frac{1}{2} \mu V$$

$$v_{SG2} = +\frac{1}{2} \mu V$$

$$i_{D1} = g_{mp} \cdot \left(-\frac{1}{2} \mu V \right)$$

$$i_{D2} = g_{mp} \cdot \frac{1}{2} \mu V$$

$$V_{out} = g_{mP} \cdot V_i \cdot r_{on} \parallel r_{op} \parallel \frac{1}{j\omega C_L}$$

$$\frac{V_{out}}{V_i} = g_{mP} \cdot \frac{(r_{on} \parallel r_{op}) \cdot \frac{1}{j\omega C_L}}{r_{on} \parallel r_{op} + \frac{1}{j\omega C_L}}$$


$$f_{u\omega} = \frac{g_{mP}}{2\pi C_L}$$


=

$$g_{mP} \cdot r_{on} \parallel r_{op}$$

$$1 + j\omega r_{on} \parallel r_{op} \cdot C_L$$
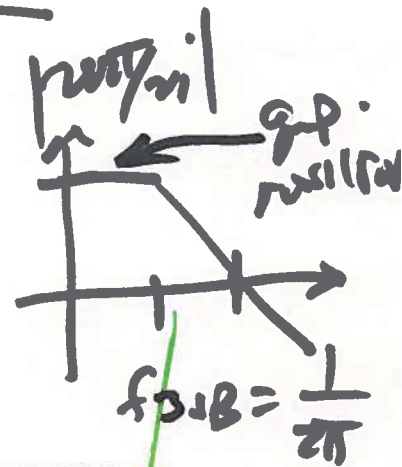
$$\approx \frac{g_{mP} \cdot r_{on} \parallel r_{op}}{2\pi f_{u\omega} \cdot r_{on} \parallel r_{op} \cdot C_L}$$



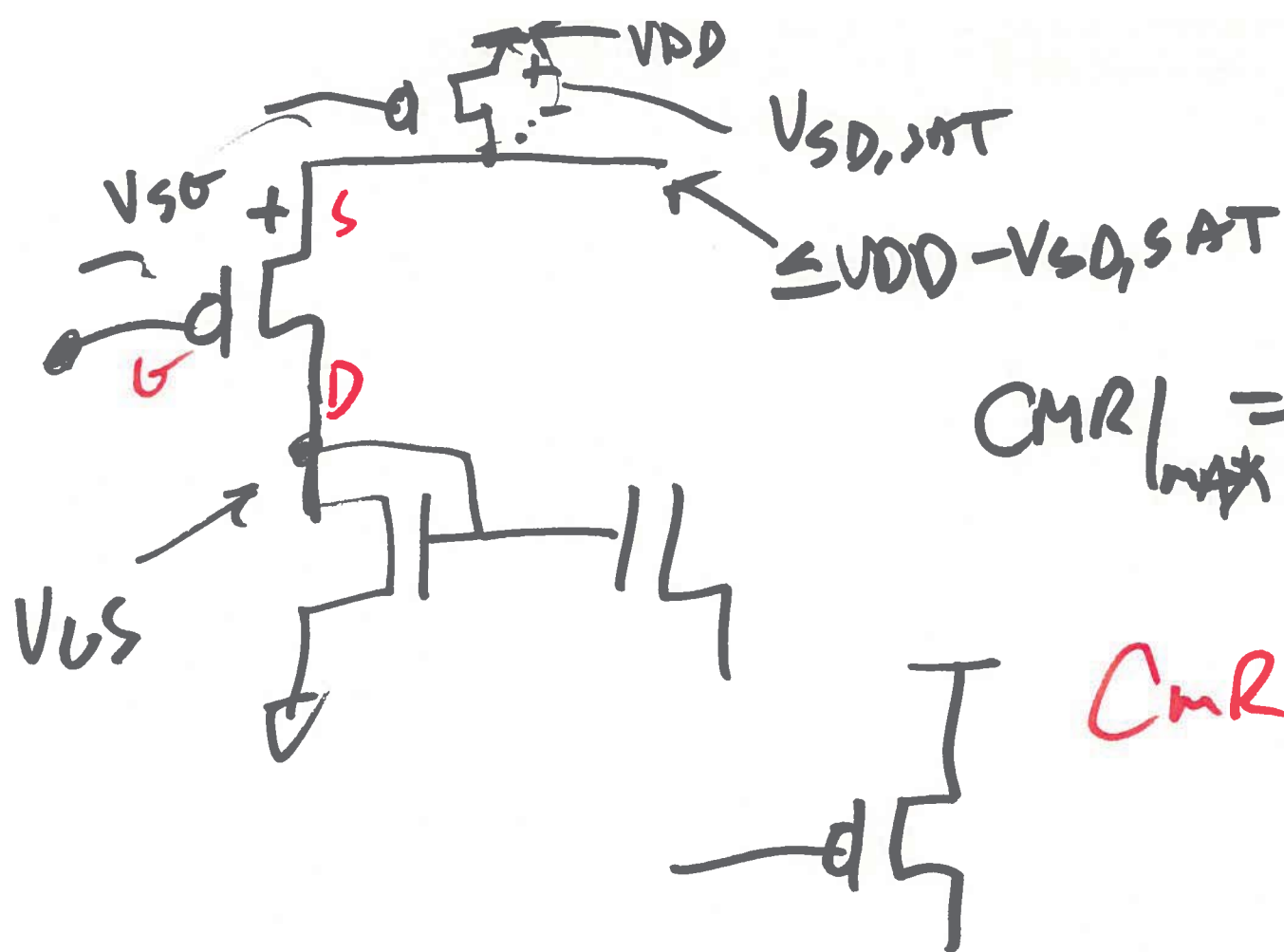

$$CMR|_{max} = V_{DD} - V_{SD,sat} - V_{SG}$$



$$CMR_{min} = V_{GS} - V_{THP}$$

$$V_{SD} \geq V_{SG} - V_{THP}$$

$$V_{GS} \leq V_G + V_{THP}$$

$$V_G \geq V_{GS} - V_{THP}$$




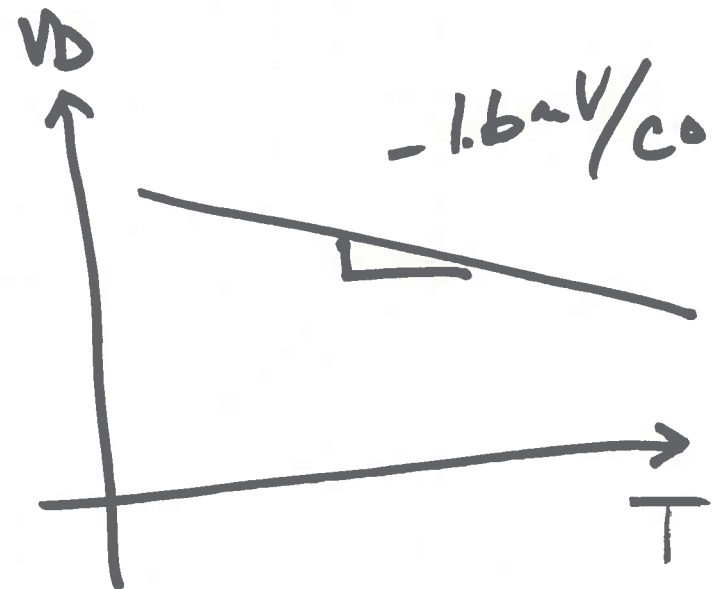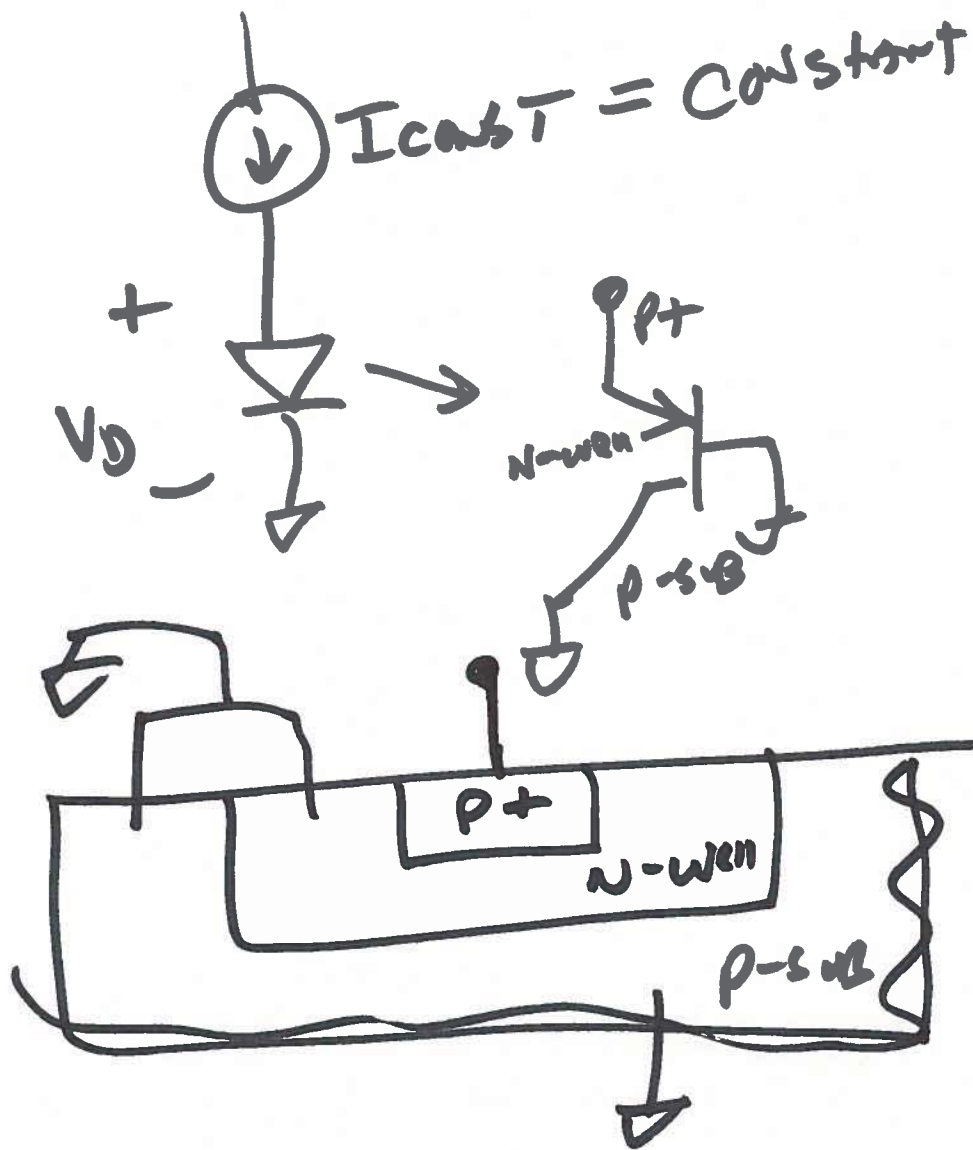

$$V_{fn} = \frac{KT}{q} \ln \frac{N_D}{n_i}$$

$$V_{fp} = \frac{KT}{q} \ln \frac{N_A}{n_i}$$
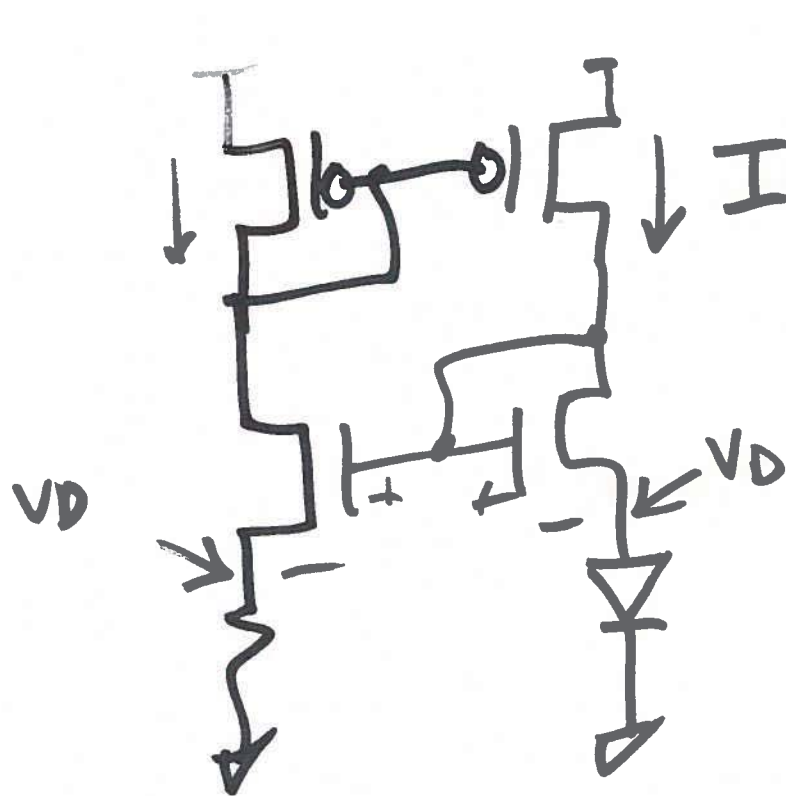
$$V_{bi} = V_{fn} - V_{fp} = \frac{KT}{q} \ln \frac{N_D N_A}{n_i^2}$$



$$I_{REF} = \frac{V_D}{R} = V_D \cdot R^{-1}$$

$$\frac{\delta I_{REF}}{\delta T} = \frac{\delta V_D}{\delta T} \cdot \frac{1}{R} + V_D \cdot (-1) \cdot \frac{1}{R^2} \frac{\delta R}{\delta T}$$

$$TCI_{REF} = \frac{1}{I_{REF}} \cdot \frac{\delta I_{REF}}{\delta T} = \frac{1}{V_D} \cdot \frac{\delta V_D}{\delta T} - \frac{1}{R} \frac{\delta R}{\delta T}$$

$$\frac{1}{I_{REF}} = \frac{R}{V_D}$$

$$\frac{-1.6mV}{^{\circ}C} \parallel \frac{2,000ppm}{^{\circ}C}$$

$$I(T) = I(T_0) \left(1 + TCI_{REF} (T - T_0) \right)$$

$$0.002$$

$$I_{a-b} = I_{n \frac{e}{b}}$$

$$V_{D1} = N V_T \ln \frac{I_0}{I_S}$$

$$V_{D2} = N V_T \ln \frac{I_0}{K \cdot I_S}$$



$$V_{D1} - V_{D2} = N V_T \ln K$$

$$I_{DEF} = \frac{V_{D1} - V_{D2}}{R}$$

$$I_{DEF} = \frac{N V_T \ln K}{R}$$


Voltage reference

CMOSedu.com

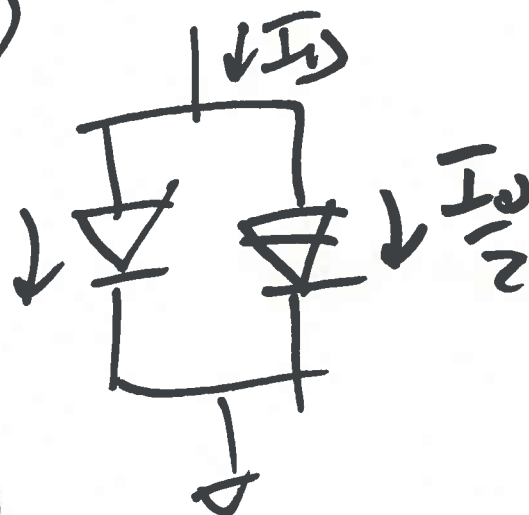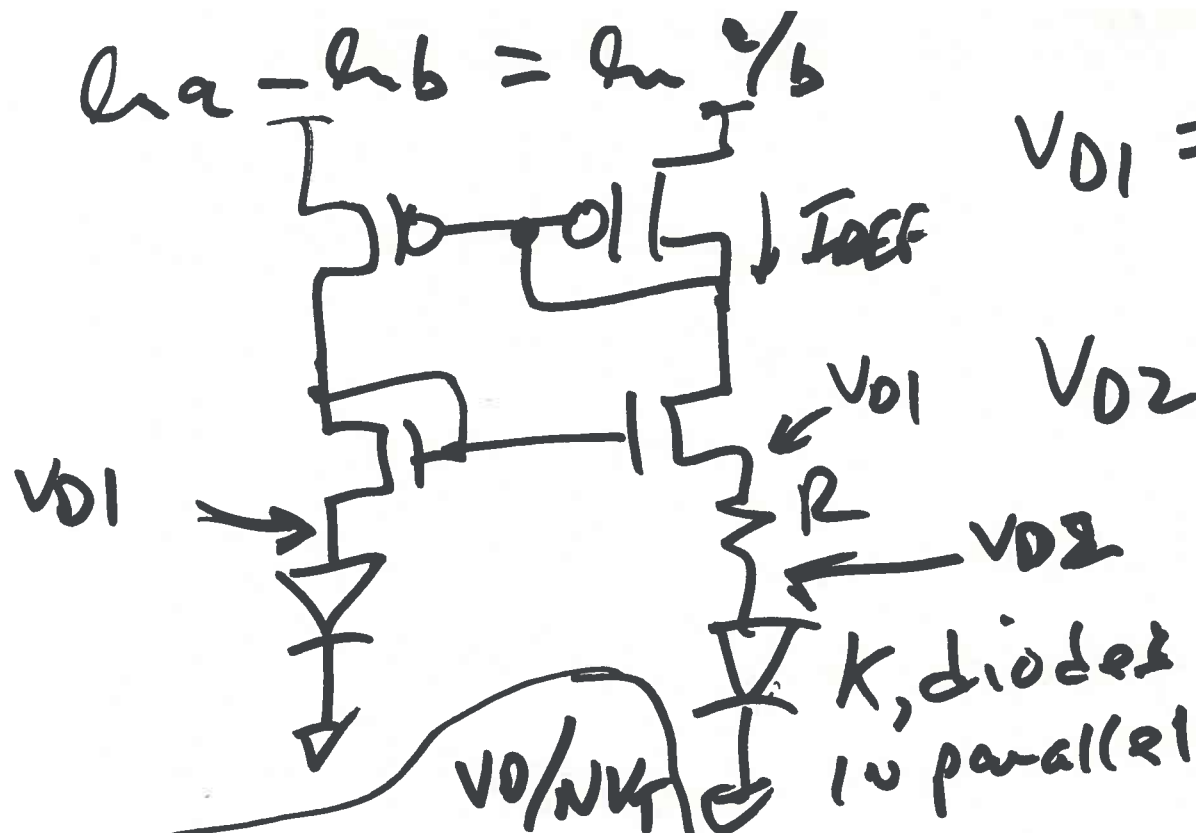

Thermal

$I_0 = I_S R$
forward biased

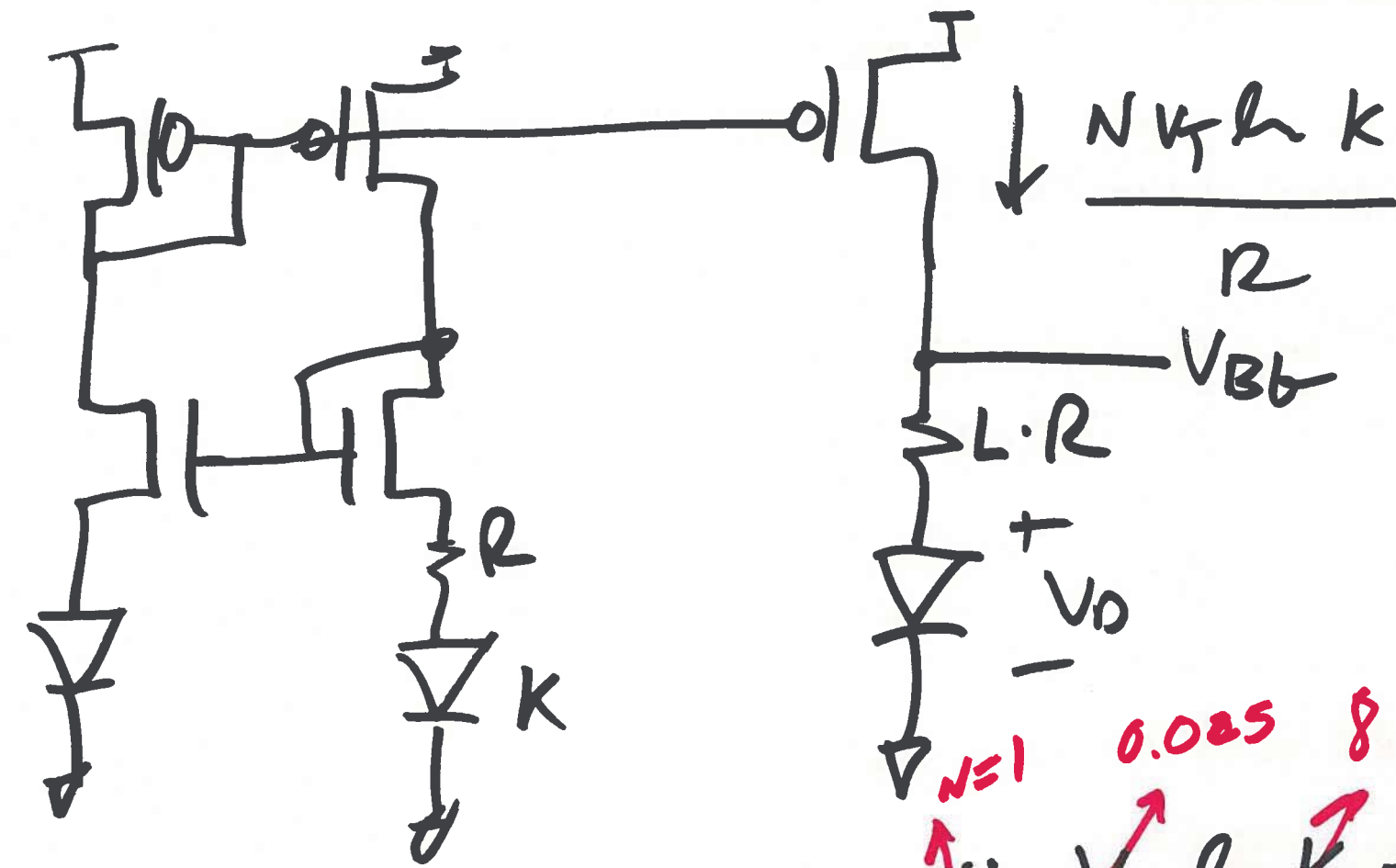

Thermal voltage
reference

$$V_{BG} = N L \cdot V_T \ln K + V_D$$

$N=1$ 0.025 8 $-1.6mV/^\circ C$

$$L = 9.41$$