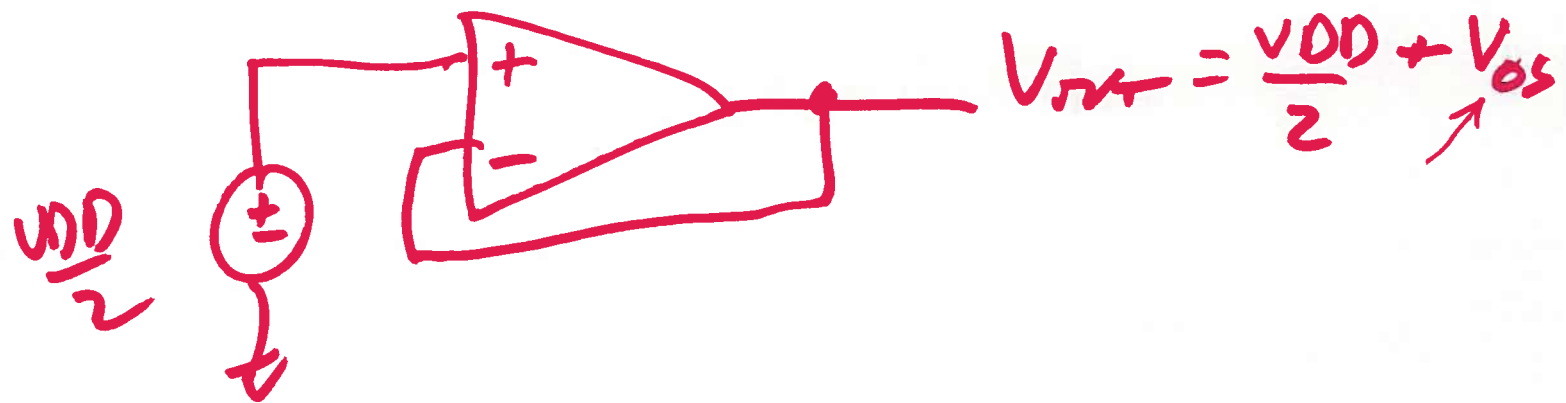



Lecture 26

April 26, 2016

EE420/ECG 620

Analog IC Design



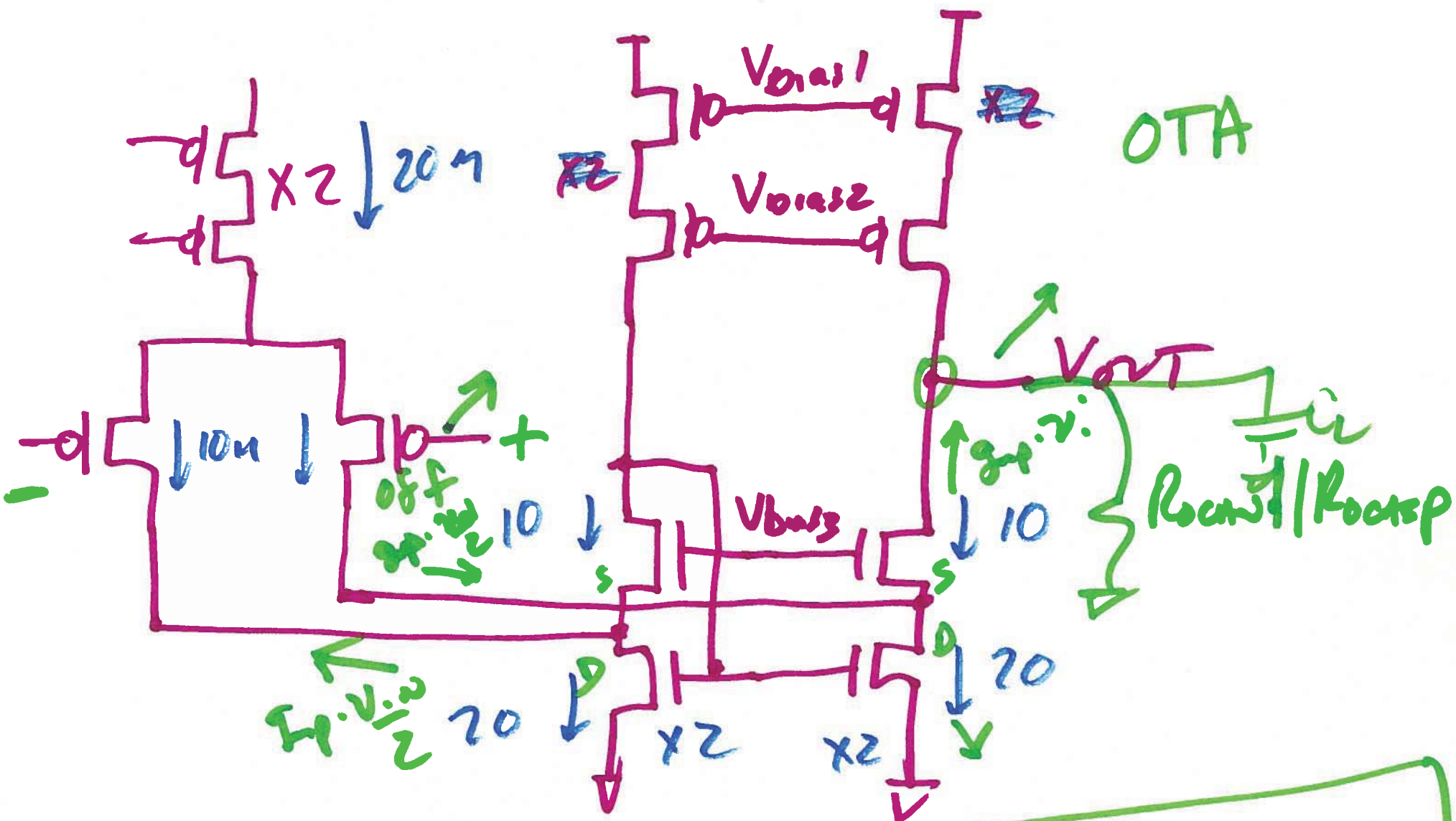

$$\frac{v_{out}}{v_{in}} = g_m \cdot R_{outN} \parallel R_{outP}$$

2)