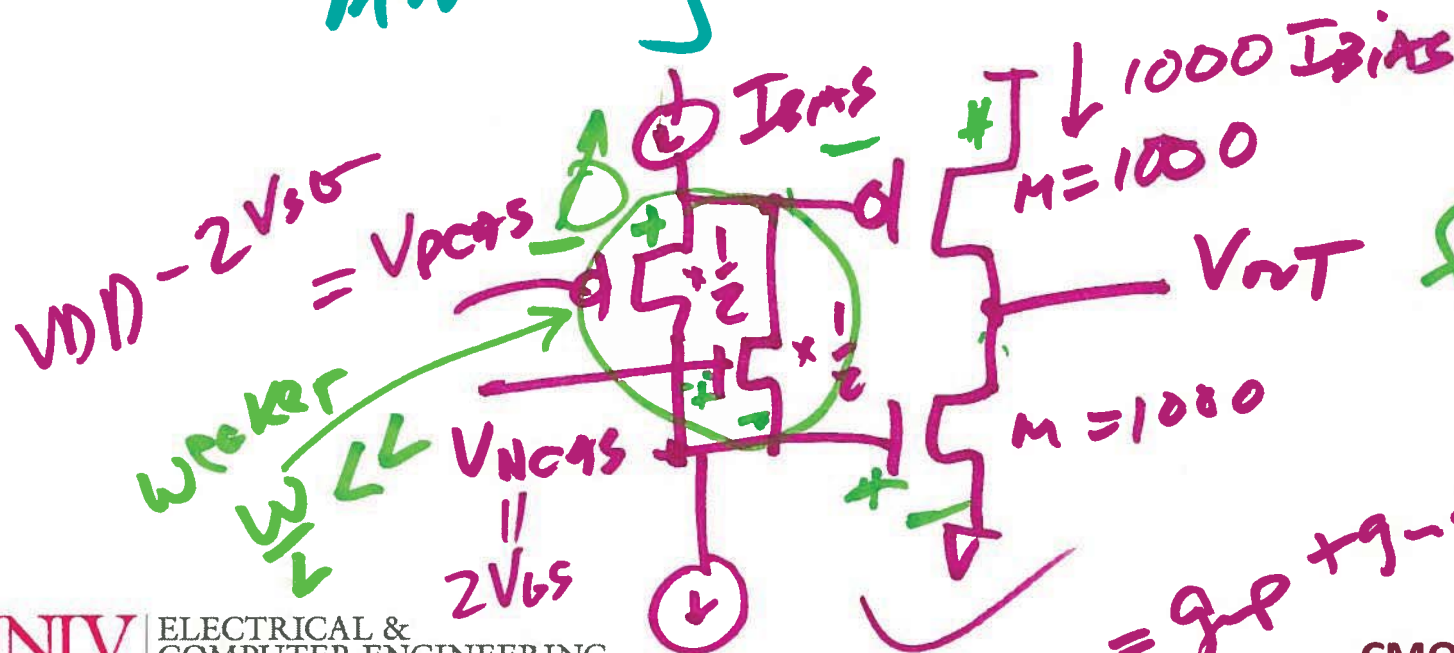


Lecture 28

May 3, 2016

EE 420 / ECE 620

Analog IC Design



$$g_m = K_P \cdot \frac{W}{L} (V_{DS} - V_{th})$$

$$f_2 \propto g_{m2}$$

$$V_{GS}/V_{DS} \downarrow$$



$$g_{m2} \downarrow$$

$$I_D \downarrow$$

$$g_{m2} = g_{mP} + g_{mN}$$

CMOSedu.com

1

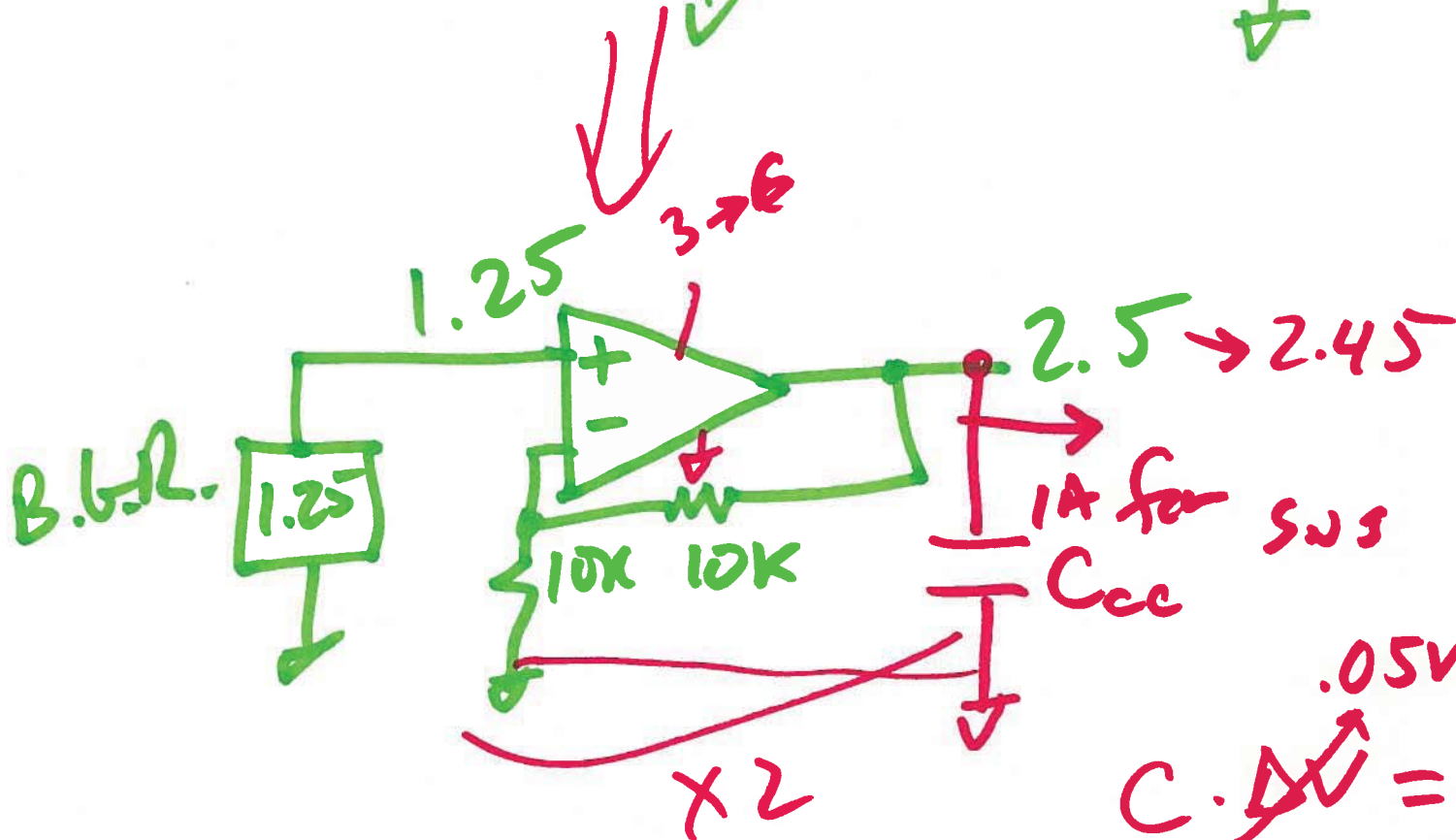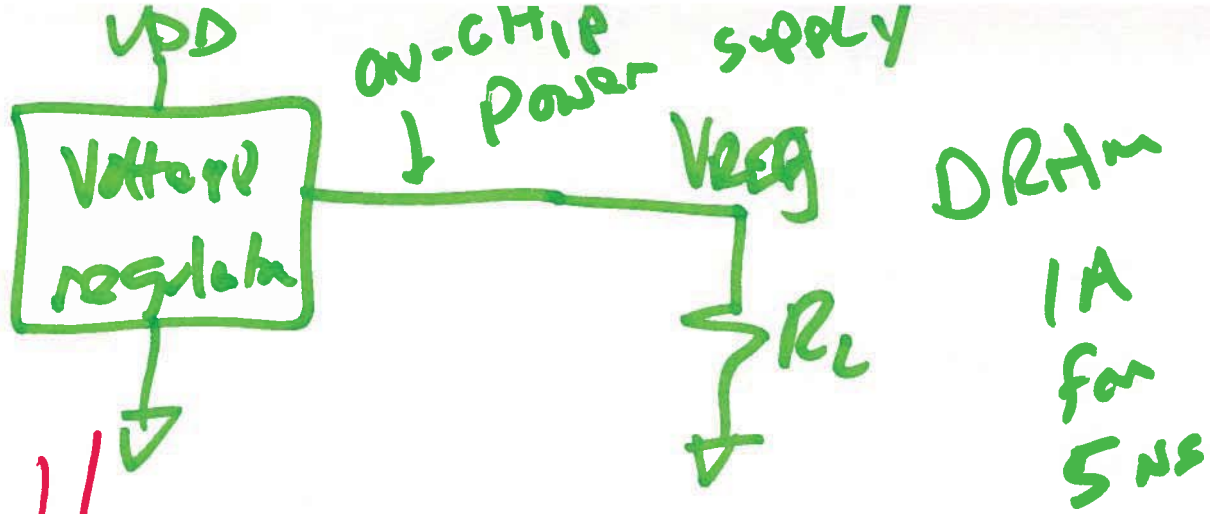

$CV = Q$
 $I = \frac{Q}{T}$
 $Q = 1A \cdot 5ns = 5nC$

$C \cdot \Delta V = 5nC$
 $C = \frac{5}{.05} nF = \underline{\underline{100nF}}$

2)

