

EE 420 / ECU 620

Analog IC Design

May 5, 2016

Lecture 29

Ch. 9

IV curves

CHTS.

ft, overdrive, widths

~~9.10~~ 9.10

AC & DC calculations

I_{D1}

I_{D2}

Ex. 9.5

study

old

Quizzes

&

H.W.

study

EOC


problems

Ch. 20

CURRENT MIRRORS
 μ_{2503} DC operation
 μ_{2503} DMR

→ BMR

BMR
OUTPUT Resistance
is regulated

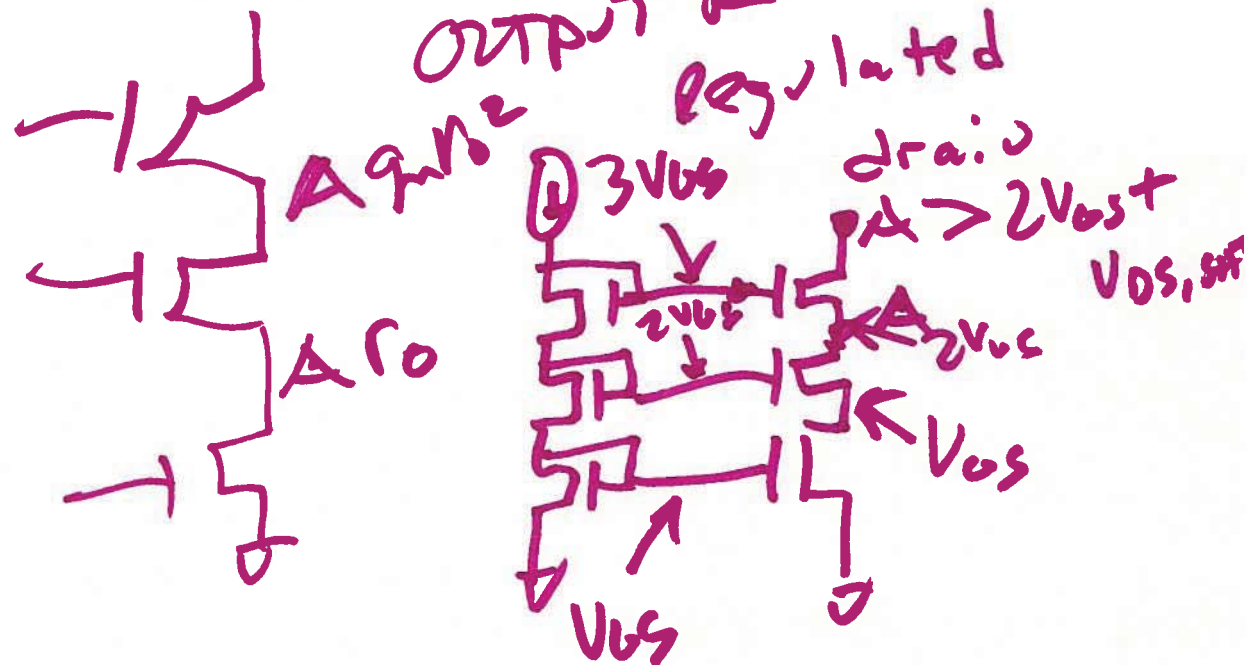

$$\rightarrow g_m^2 r_o^3$$


$$R_{out} \approx g_m r_o^2$$
 CMOS

Ch. 2 1/2 Amplifiers topologies

gains


INPUT CMR
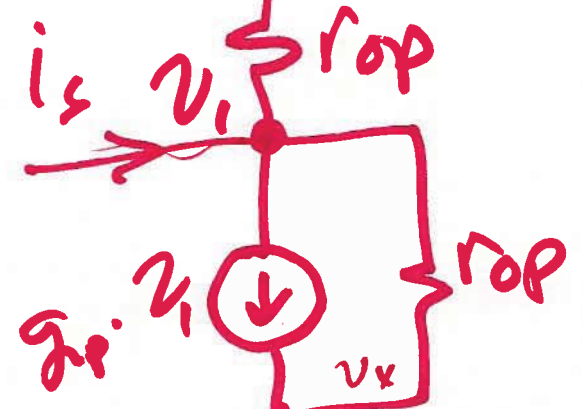
$$\frac{v_1}{i_s} \approx \frac{1}{g_{mp}}$$



$$i_s = \frac{v_1}{r_{op}} + g_m v_1$$
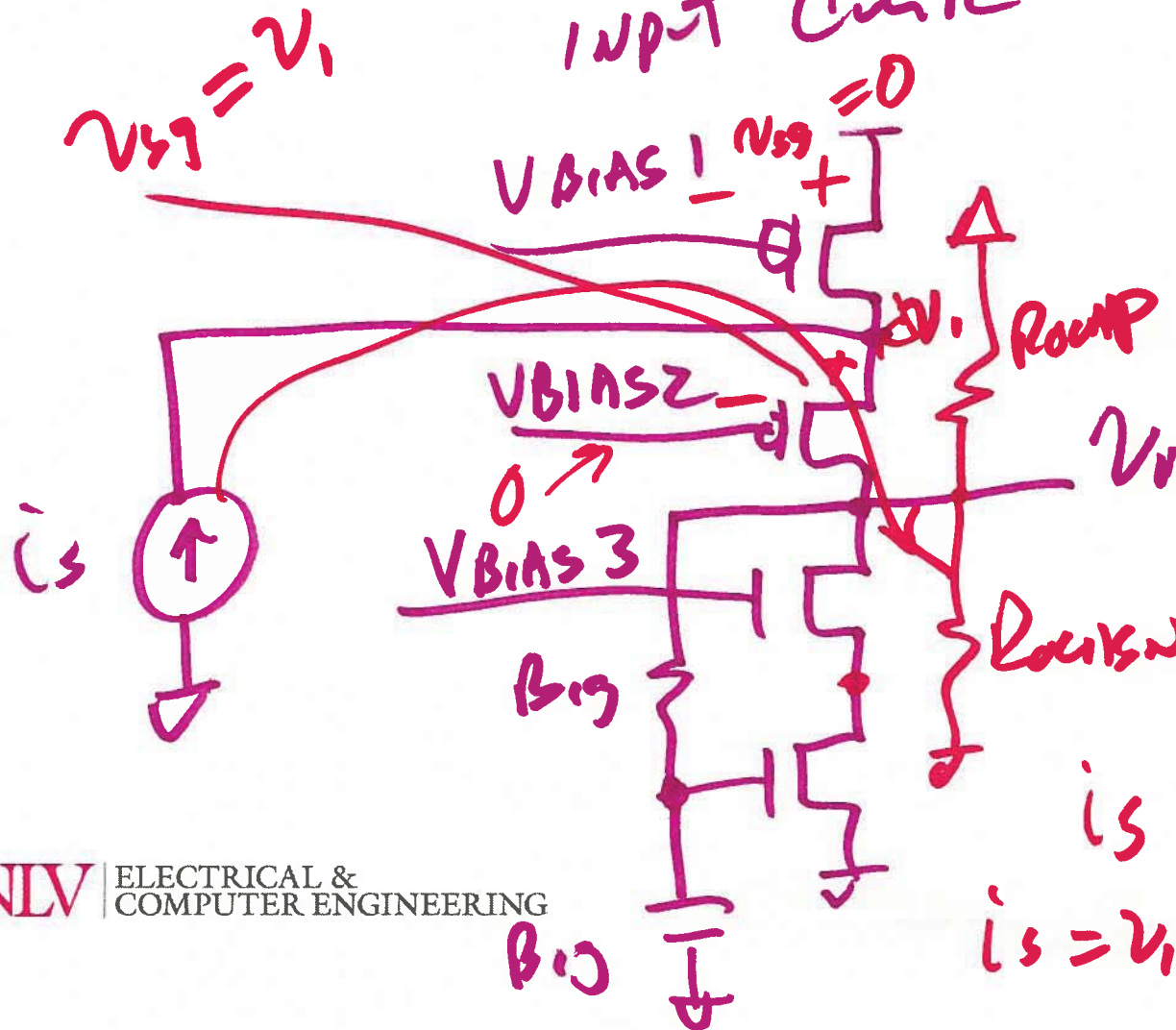
$$v_{out} = i_s \cdot R_{out} \parallel R_{o, \text{const}}$$



$$i_s = \frac{v_1}{r_{op}} + g_{mp} \cdot v_1$$

$$i_s = v_1 \cdot \left(\frac{1}{r_{op}} + g_{mp} \right)$$

Ch. 24

$$|A_{OL}\beta| = 1$$

$$\angle A_{OL}\beta = 180^\circ$$

Compensation

frequency response

OP-Amp topologies

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

$$A_{CL} = \frac{1}{\frac{1}{A_{OL}} + \beta}$$

$$f_{in} = \frac{Q}{2\pi C_L}$$

$$f_2 \propto \omega$$

