

EE 420 / ECG 620


Analog IC Design

JAN. 26, 2016

Lecture 3

$$V_G - V_S = V_{GS} = 3V$$

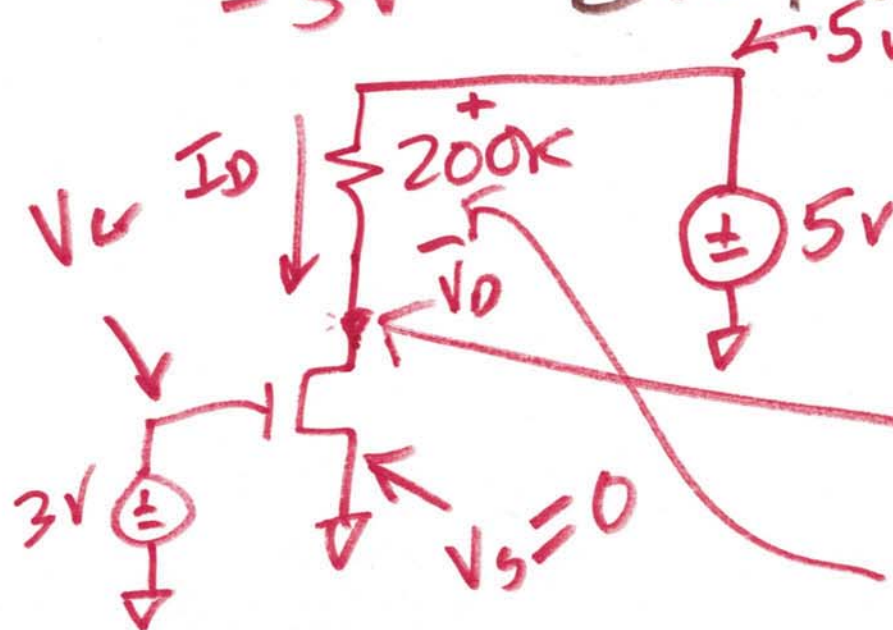$I \downarrow \uparrow \overset{+}{V} = IR$



$$V_{GS} = 3V$$



$$5 - I_0 \cdot 200K = V_{DS} = V_D - V_S$$

$I_0 = 200\text{K}$


ה

Show your work for credit.

ur

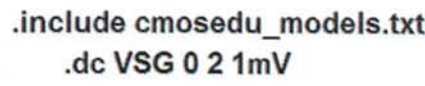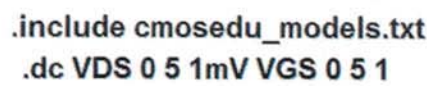

2)

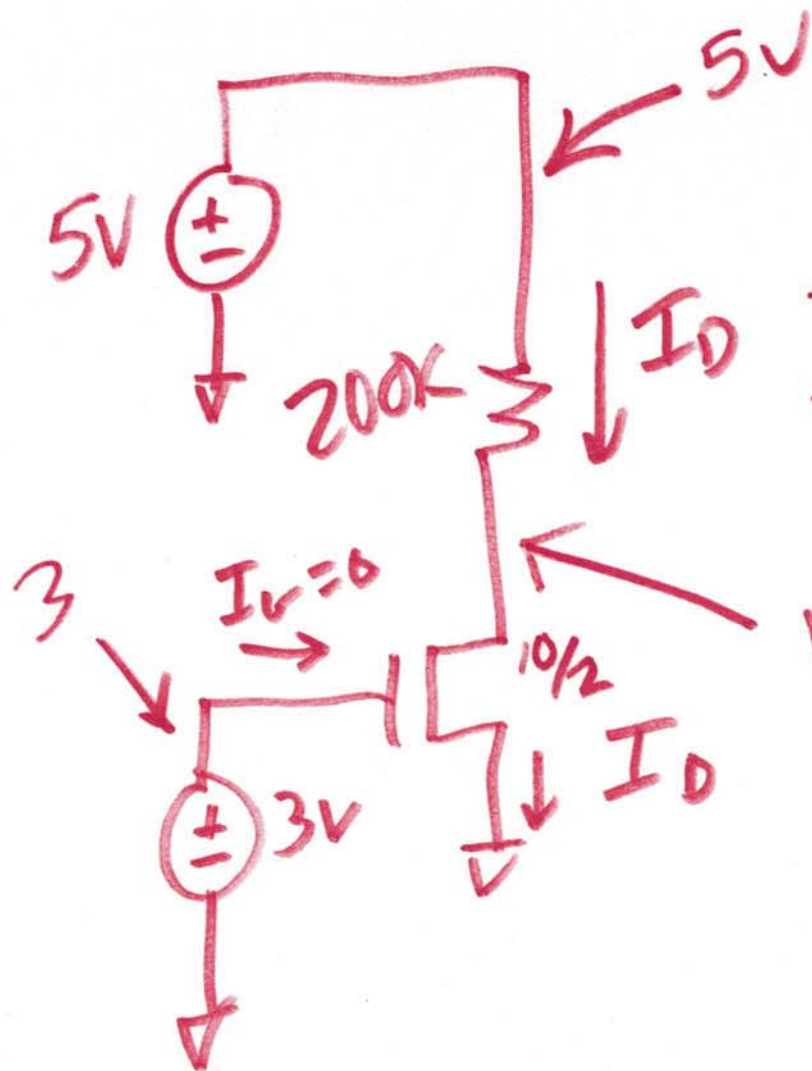

$$V_{THN} = 0.8V$$

$$K_P = 120 \mu A/V^2$$

$$+200k \cdot 1.45 \mu A$$

$$V_{GS} > V_{THN}?$$

$$3 > 0.8 \text{ yes!}$$

$$V_{DS} = 5 - 200k \cdot I_D$$

$$V_{DS} \geq V_{GS} - V_{THN} =$$


$$V_{DS} \geq \underline{\underline{2.2V}}??$$

$$I_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{THN})^2$$


$$\text{NOT in SAT} = 604 \cdot 5 \cdot (2.2)^2$$

$$= \underline{\underline{1.45 \mu A}}$$


CMOSedu.com

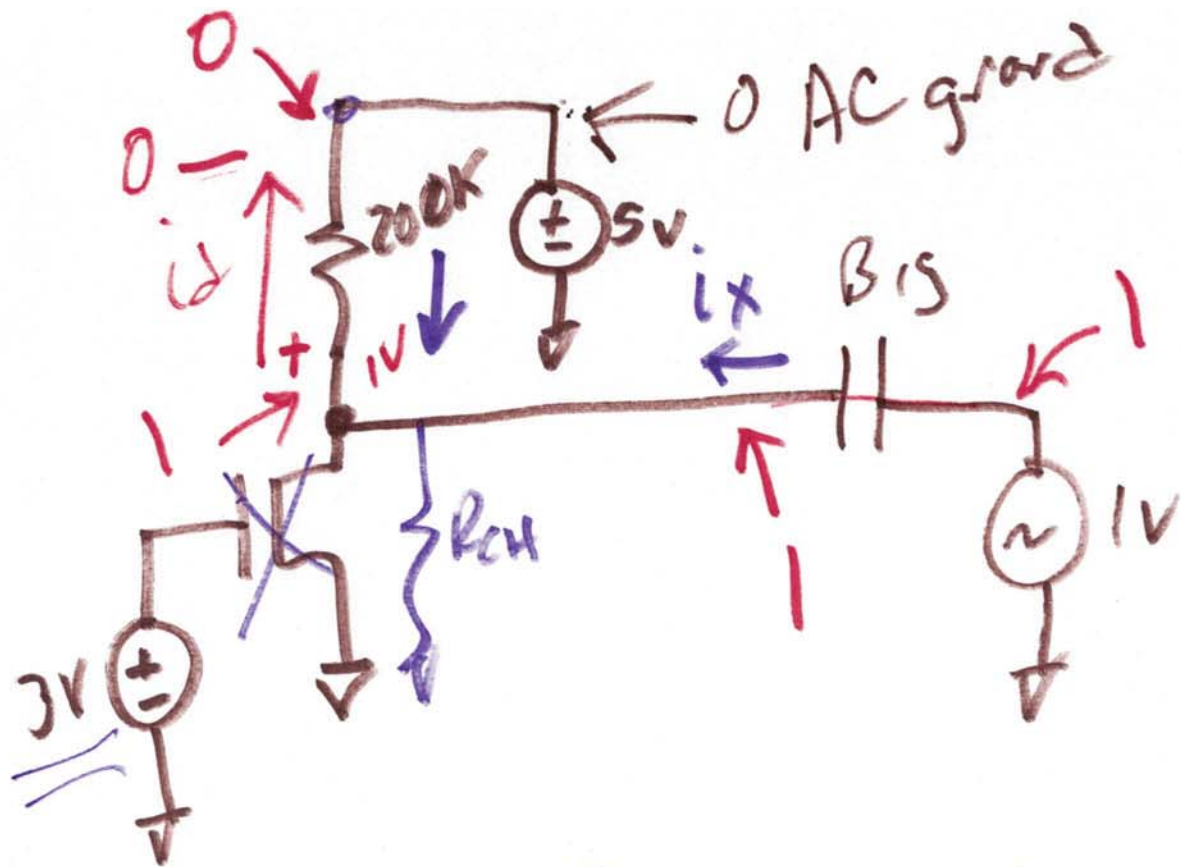


$$i_x = \frac{1V}{200k} = 5\mu A$$

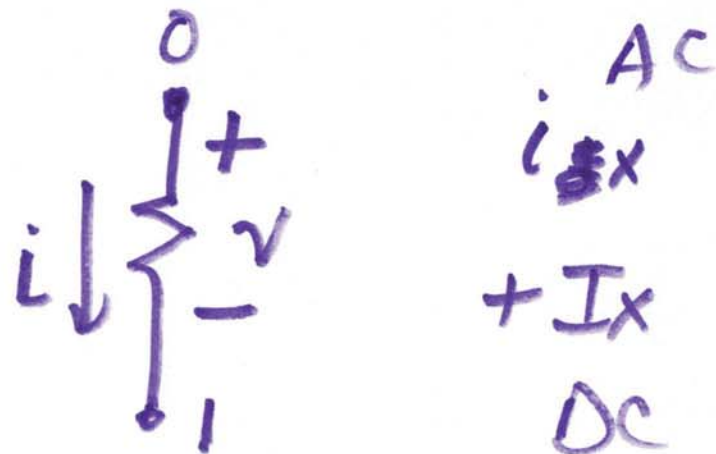

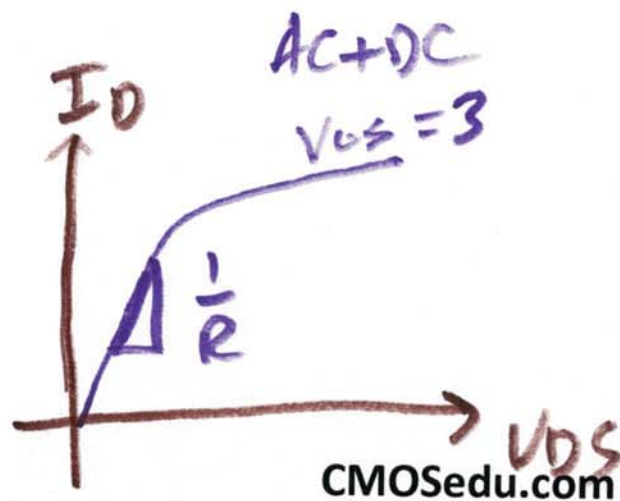
$$\frac{v}{R} = \frac{0-1}{200k} = i = -5\mu A \quad i_x = I_x + i_x$$



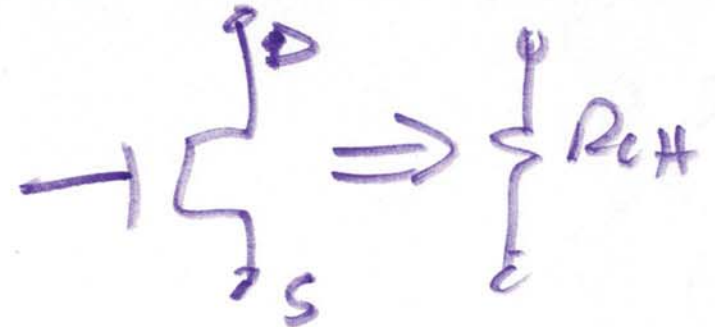R_{eff} = RESISTANCE between D & S when in triode



$$R_{eff} = \frac{V_{ds}}{i_d}$$

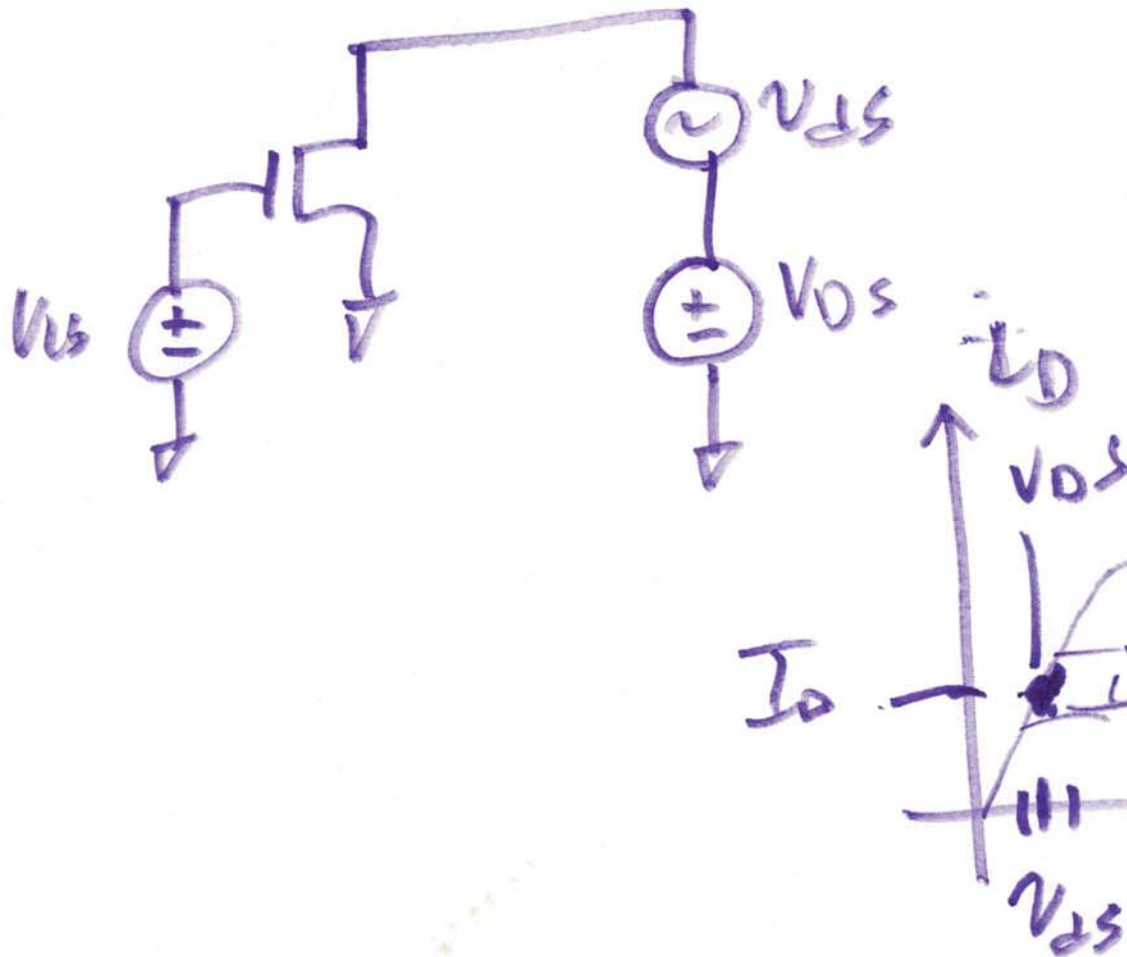

$$i_D = I_D + i_d = k_P \mu \frac{W}{L} \left((V_{GS} - V_{THN}) \cdot \left(\overbrace{V_{DS} + v_{ds}}^{\approx V_{DS}} - \frac{(V_{DS} + v_{ds})^2}{2} \right) \right)$$

$$R_{CH}^{-1} = \frac{\delta i_D}{\delta v_{ds}} \bigg|_{\substack{I_D = \text{const} \\ V_{GS} = \text{const}}}$$

$$\frac{\delta}{\delta x} k \cdot x = k \frac{\delta y}{\delta x}$$



$$R_{CH}^{-1} = k_P \mu \frac{W}{L} \left((V_{GS} - V_{THN}) - \overbrace{V_{DS} + v_{ds}}^{\approx V_{DS}} \right)$$

$$R_{CH} = \frac{k_P \mu \frac{W}{L} \left((V_{GS} - V_{THN}) - V_{DS} \right)}{\text{Small-signal App.}}$$

$$R_{CH} = \frac{1}{K_P \cdot \frac{W}{L} (V_{GS} - V_{THN}) - V_{DS}}$$

$$\approx \frac{1}{K_P \cdot \frac{W}{L} (V_{GS} - V_{THN})}$$

$$V_{DS} \ll V_{GS} - V_{THN}$$

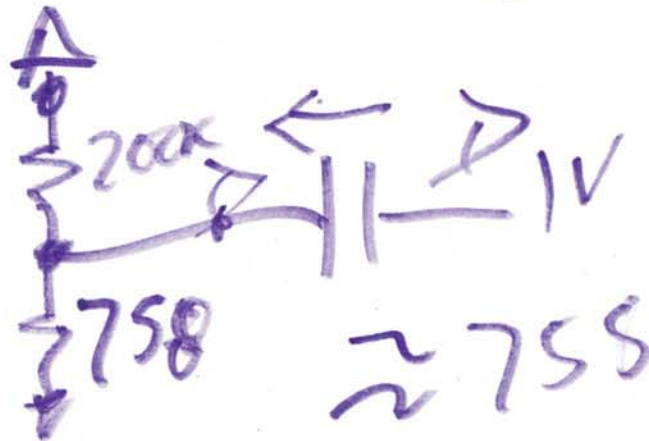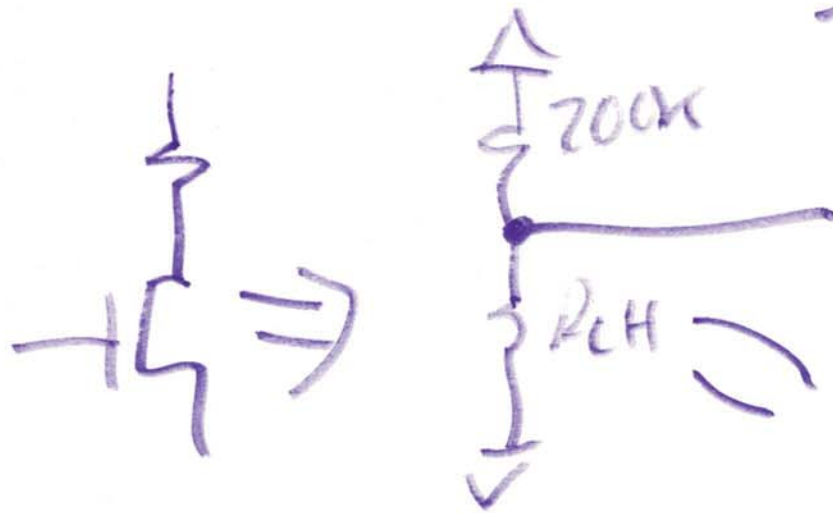

$$\approx 758$$

$$\frac{1}{758}$$

$$120\mu \cdot 5 \cdot 2.2$$

$$847.2$$

$$i = 1.3 \text{ mA}$$

EE 420/ECG 620


Analog IC Design

JAN. 26, 2016

Lecture 3

$$V_G - V_S = V_{GS} = 3V$$


$$I \downarrow \uparrow V = IR$$

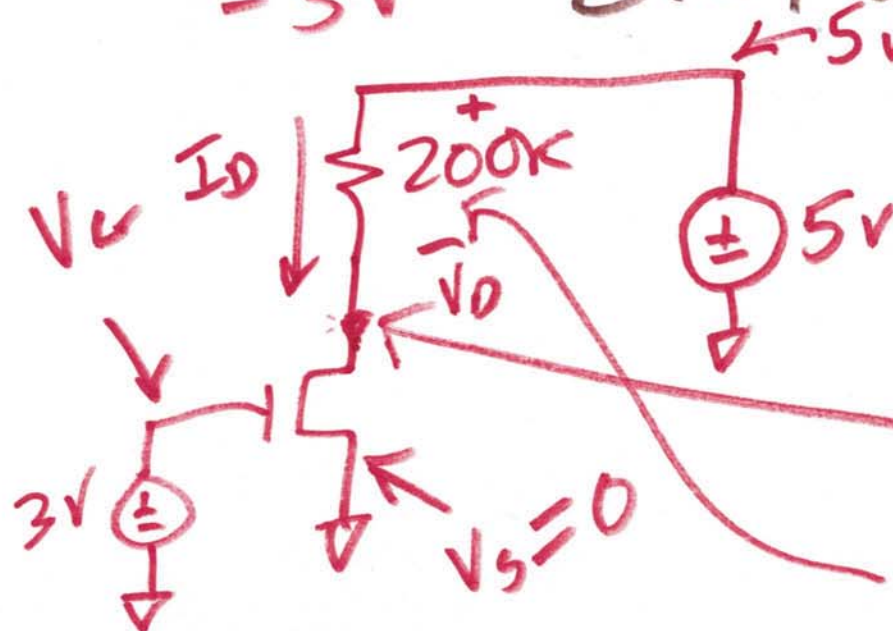

$$V_{GS} = 3V$$

$$5 - I_D \cdot 200k = V_{GS} = V_O - V_S$$

$$I_D \cdot 200k$$

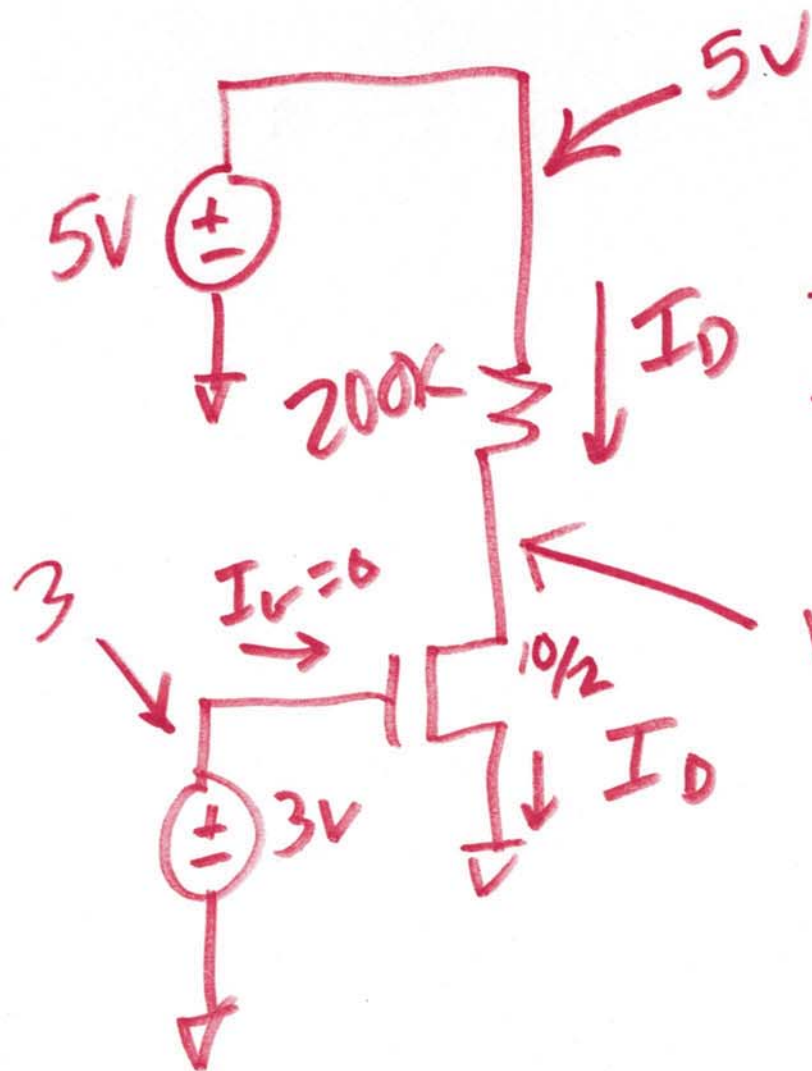

$$V_{THN} = 0.8V$$

$$K_P = 120 \mu A/V^2$$

$$+200k \cdot 1.45 \mu A$$

$$V_{GS} > V_{THN}?$$

$$3 > 0.8 \text{ yes!}$$

$$V_{DS} = 5 - 200k \cdot I_D$$

$$V_{DS} \geq V_{GS} - V_{THN} =$$


$$V_{DS} \geq \underline{\underline{2.2V}}??$$

$$I_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{THN})^2$$


$$\text{NOT in SAT} = 604 \cdot 5 \cdot (2.2)^2$$

$$= \underline{\underline{1.45 \mu A}}$$


CMOSedu.com

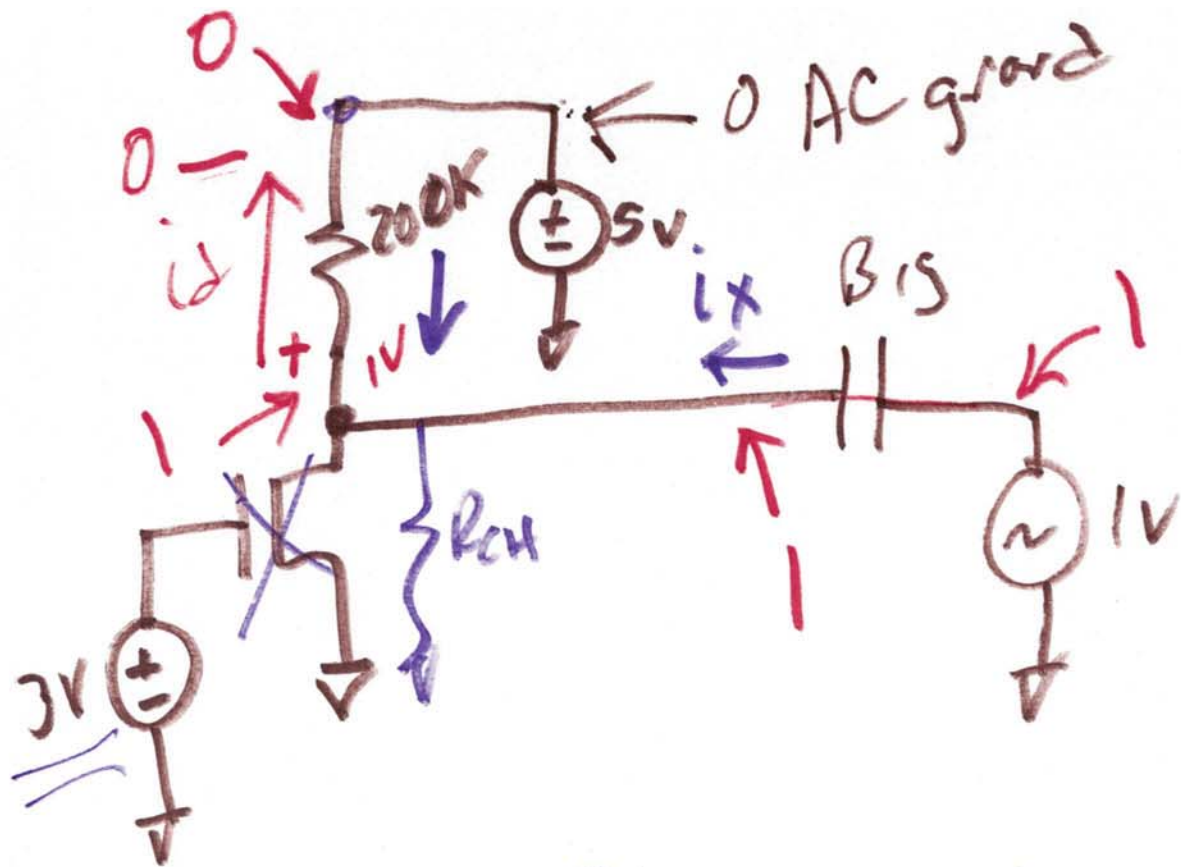


$$i_d = \frac{1V}{200k} = 5\mu A$$

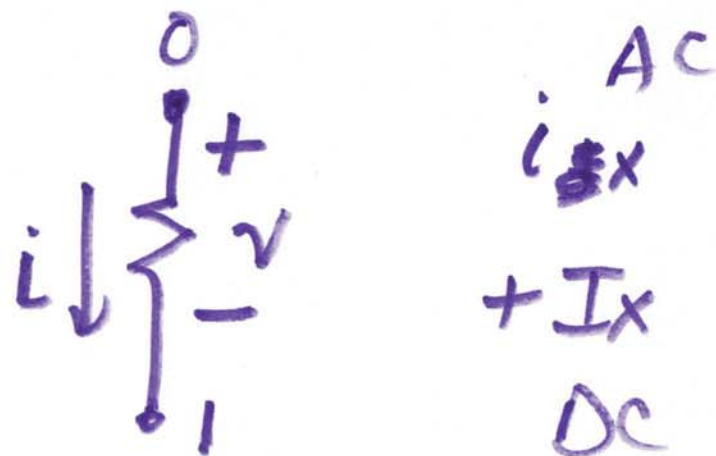

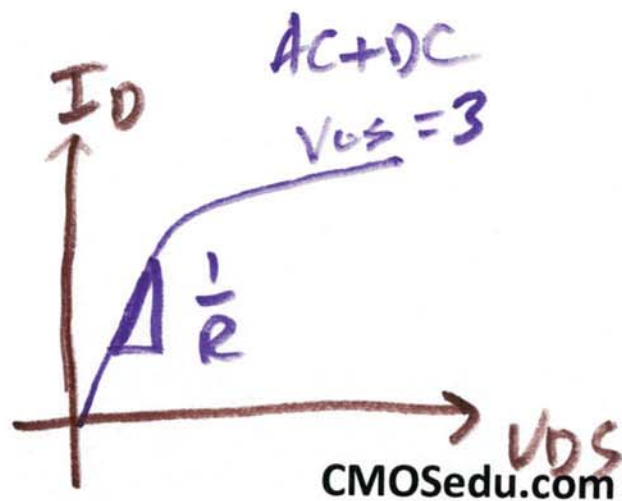
$$\frac{v}{R} = \frac{0-1}{200k} = i = -5\mu A \quad i_x = \bar{i}_x + \dot{i}_x$$



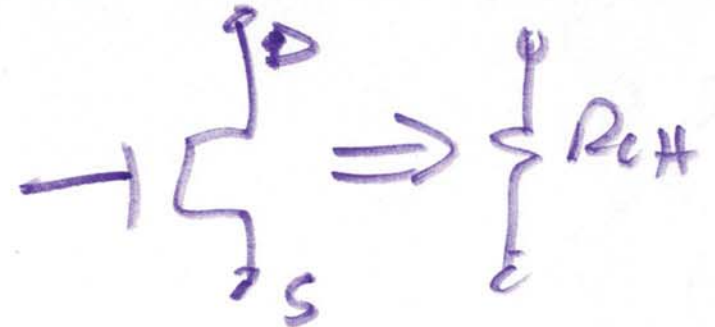R_{eff} = RESISTANCE between D & S when in triode



$$R_{eff} = \frac{V_{ds}}{i_d}$$

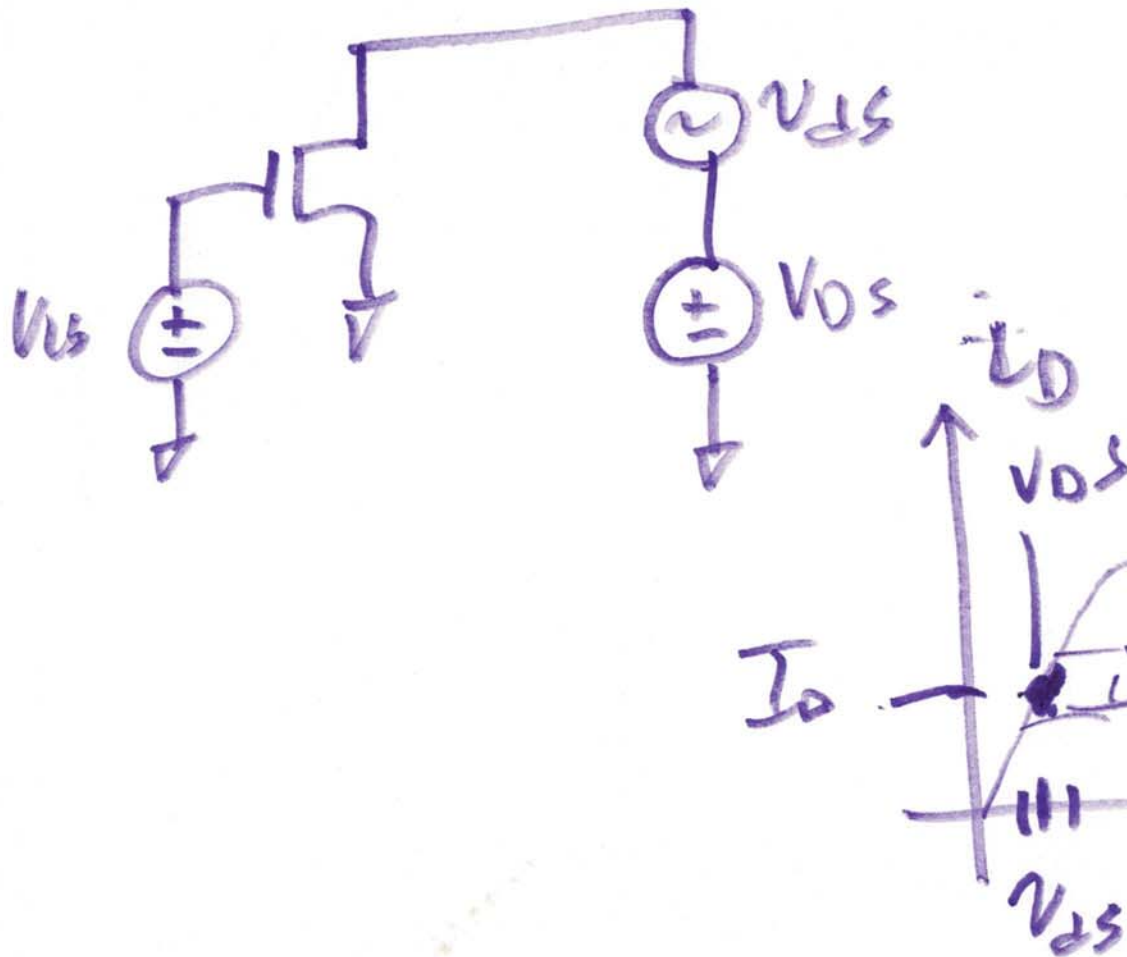

$$R_{eff}^{-1} = \frac{i_d}{v_{ds}} = \text{slope}$$

5)



$$i_D = I_D + i_d = k_P \mu \cdot \frac{W}{L} \left((V_{GS} - V_{THN}) \cdot \left(\overbrace{V_{DS} + v_{ds}}^{\approx V_{DS}} - \frac{(V_{DS} + v_{ds})^2}{2} \right) \right)$$

$$R_{CH}^{-1} = \frac{\delta i_D}{\delta v_{ds}} \bigg|_{\substack{I_D = \text{const} \\ V_{DS} = \text{const}}}$$

$$\frac{\delta}{\delta x} k \cdot x = k \frac{\delta y}{\delta x}$$

$$R_{CH}^{-1} = k_P \cdot \frac{W}{L} \left((V_{GS} - V_{THN}) - \overbrace{V_{DS} + v_{ds}}^{\approx V_{DS}} \right)$$
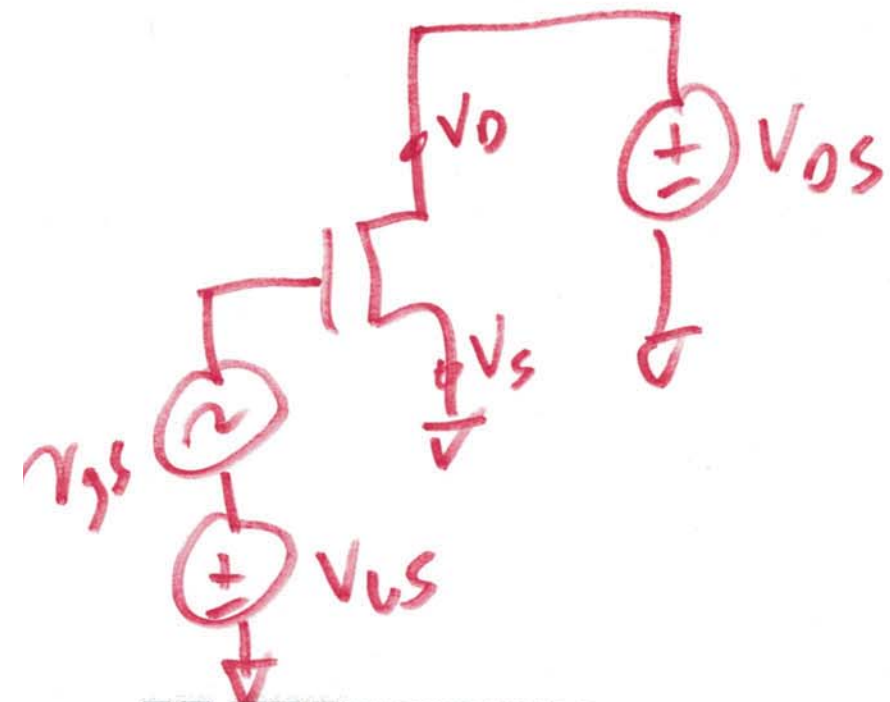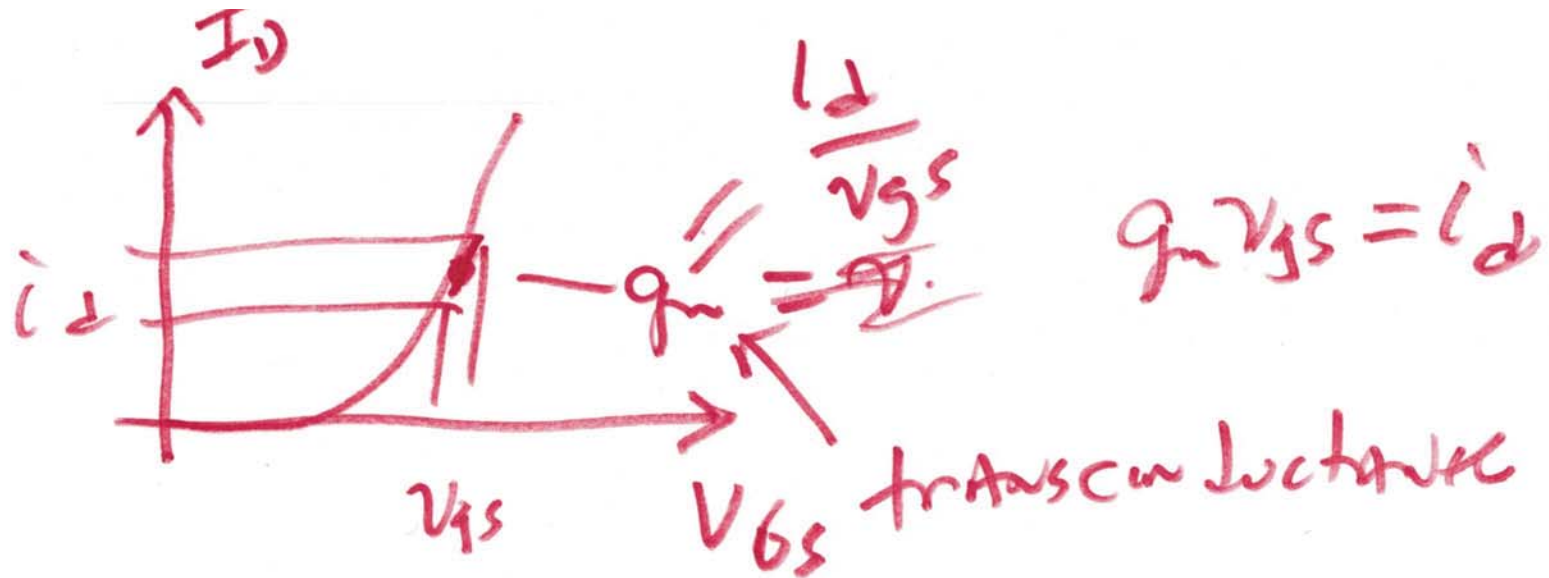
$$R_{CH} = \frac{k_P \mu \frac{W}{L} \left((V_{GS} - V_{THN}) - V_{DS} \right)}{\text{Small-signal App.}}$$



8)