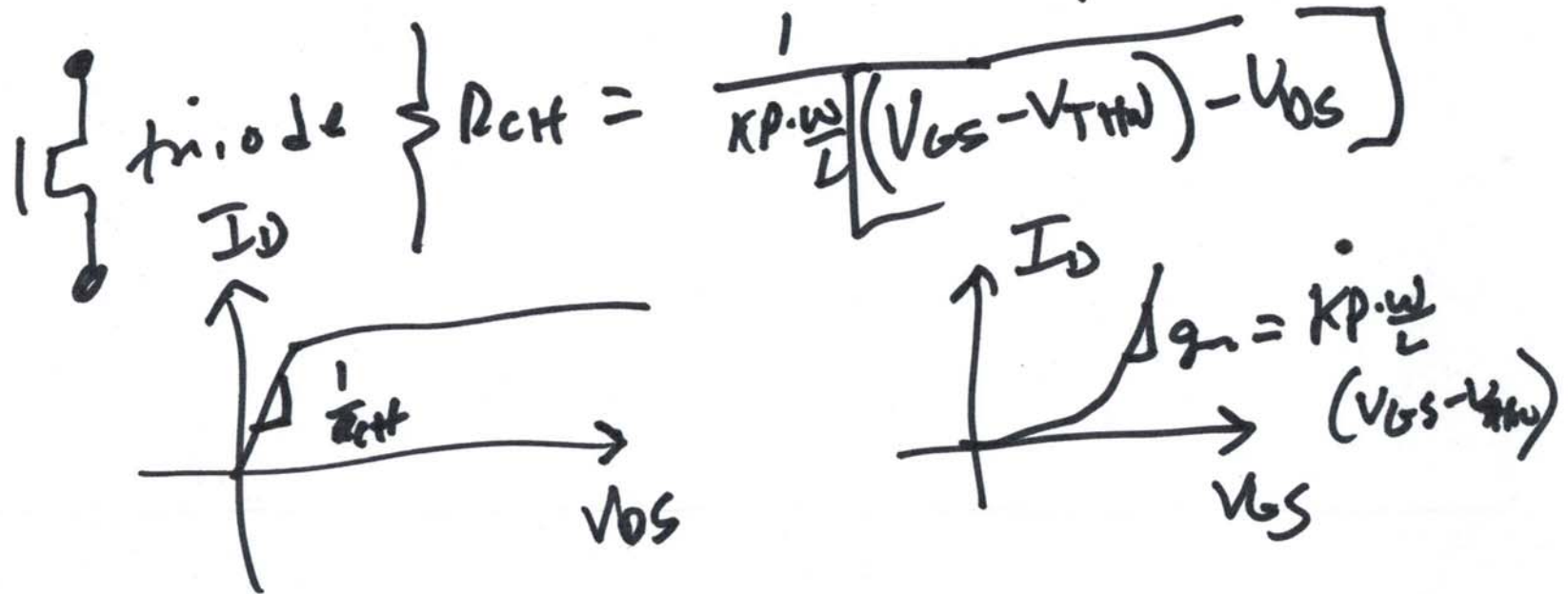


EE 420 / ELG 620

Analog IC Design


Lecture 4

Jan. 28, 2016




What is the voltage drop across I?

5 - 2V_{GS} I_n Amps

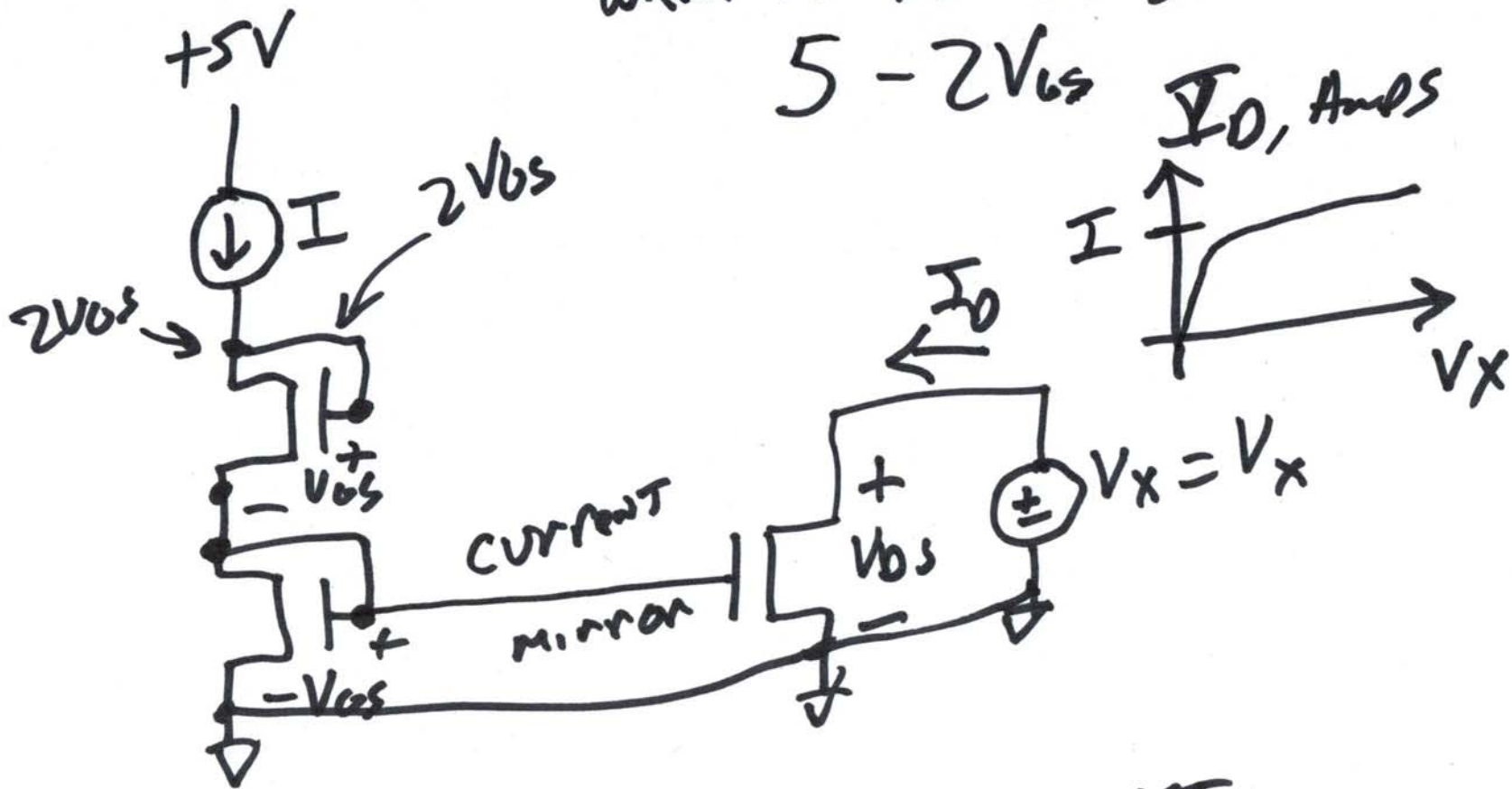

$$V_{GS} = \sqrt{\frac{2I}{K_P \cdot \frac{W}{L}}} + V_{THN} \quad \overset{\text{CONST}}{I} = \frac{\beta_D}{2} \left(\overset{\text{CONST}}{V_{GS}} - V_{THN} \right)^2$$
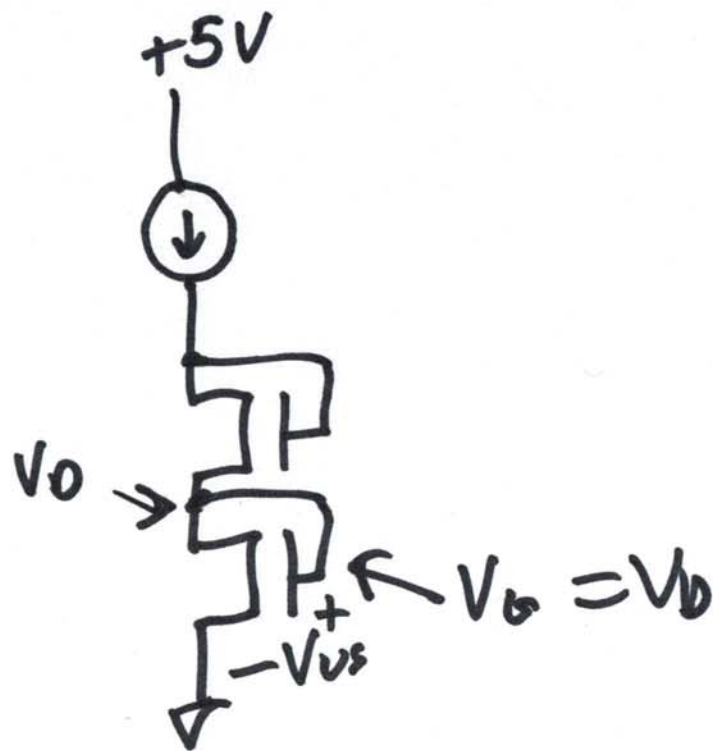
$$\beta_2 = \kappa P \cdot \frac{\omega}{L}$$



SAT!

$$V_D - V_S \geq V_G - V_S - V_{THN}$$

$$V_O \geq V_G - V_{THN}$$

$$0 \geq -V_{THN}$$

YES

$$V_{GS} = \sqrt{\frac{2I}{\beta_N}} + V_{THN}$$


$$I = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2$$

SAT.


$$V_{DS} \geq V_{GS} - V_{THN}$$

$$V_{GS} > V_{THN}$$

CMOSedu.com

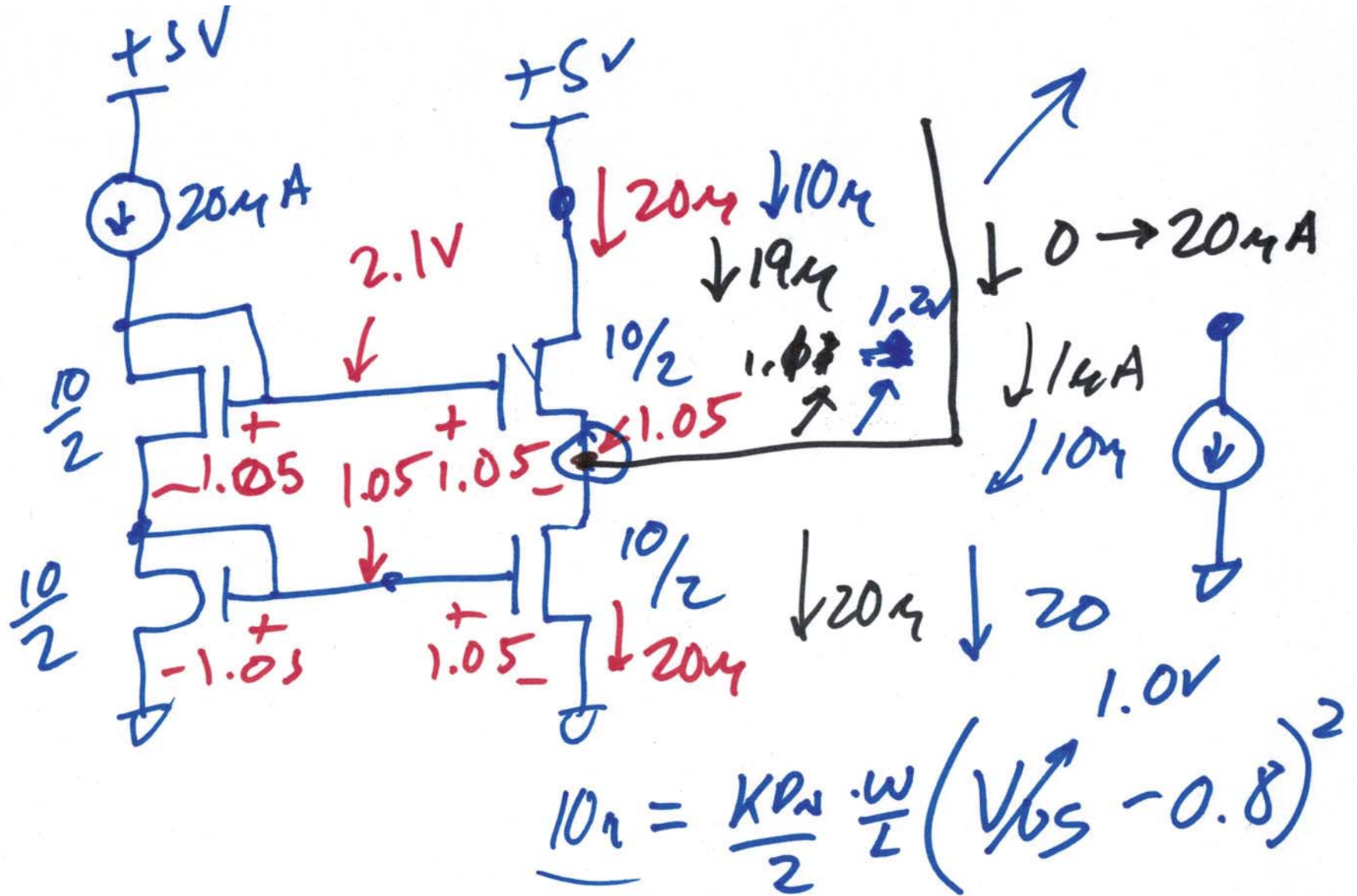

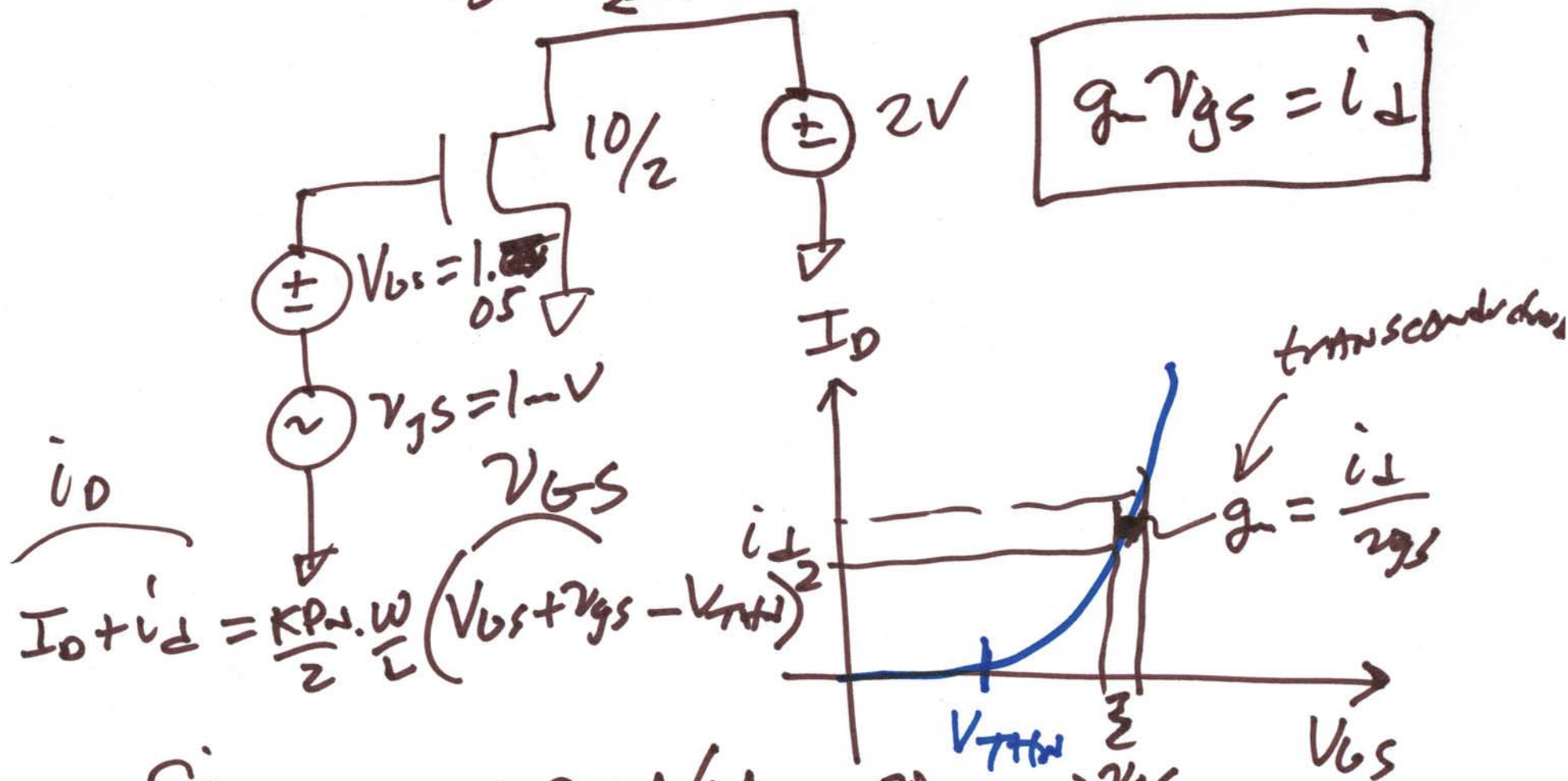$i_D = I_D + i_d$ $V_{GS} > V_{THN}$ YES $V_{DS} > V_{GS} - V_{THN}$ YES




$$g_m = \frac{\delta i_D}{\delta V_{GS}} \bigg|_{\substack{I_D = \text{const} \\ V_{DS} = \text{const}}} = \frac{K_P N \cdot W}{L} (V_{GS} + v_{gs} - V_{THN})$$

Small-signal Approx. $V_{GS} \gg v_{gs}$

$$g_m \approx \frac{K_P N \cdot W}{L} (V_{GS} - V_{THN})$$

CMOSedu.com
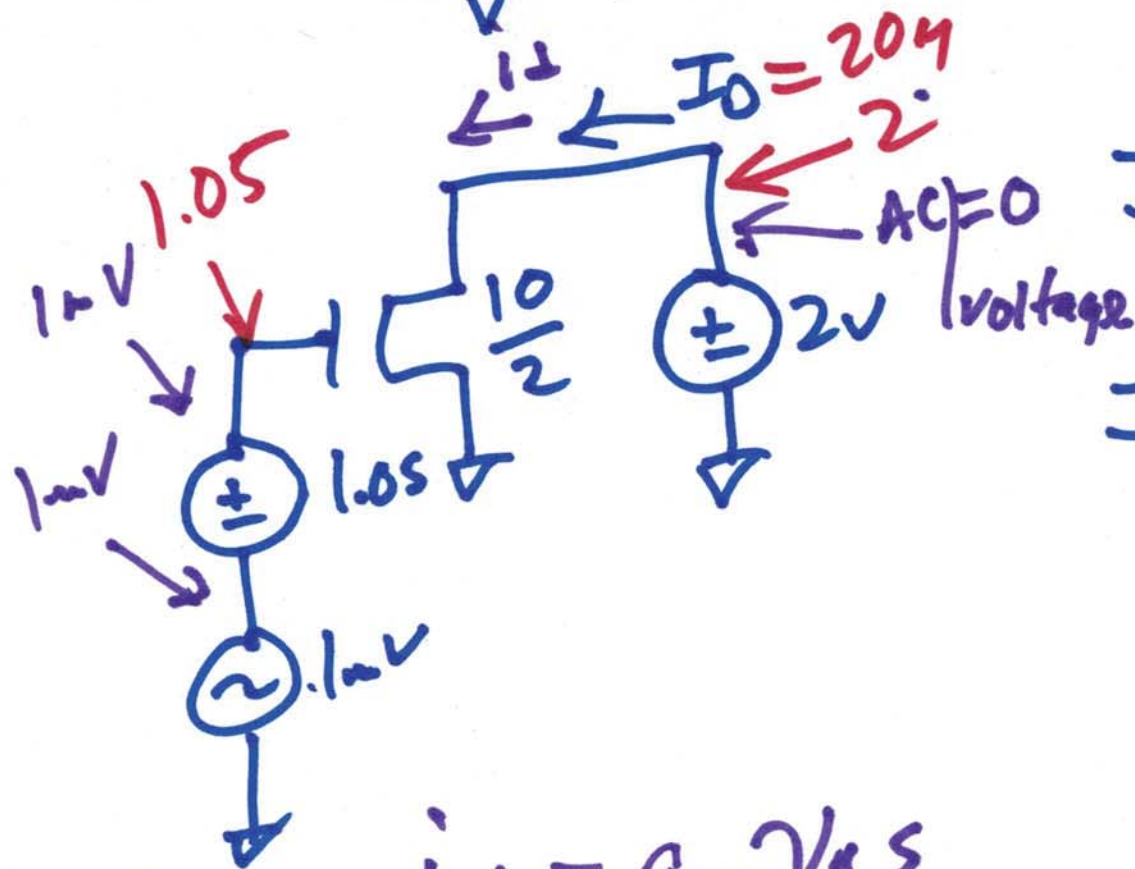
$$K_{PN} = 120 \frac{\mu A}{V}, V_{THN} = 0.8 V$$



$$I_D = \frac{120 \mu A}{2} \cdot \frac{10}{2} (1.05 - 0.8)^2$$

$$I_D = 204 A$$

$$g_m = K_{PN} \cdot \frac{W}{L} (V_{GS} - V_{THN})$$

$$= \frac{120 \mu A}{V} \cdot \frac{10}{2} (0.25)$$

$$= 150 \mu A/V$$

$$i_d = g_m v_{gs}$$

$$= 150 \frac{\mu A}{V} \cdot 1 mV$$

$$= 150 nA$$

$20 \log 10^{-3}$
 $-60 dB$

