


EE 420 / ECE 620

Lecture 7

Spring 2016


2/9/16

DC calcs

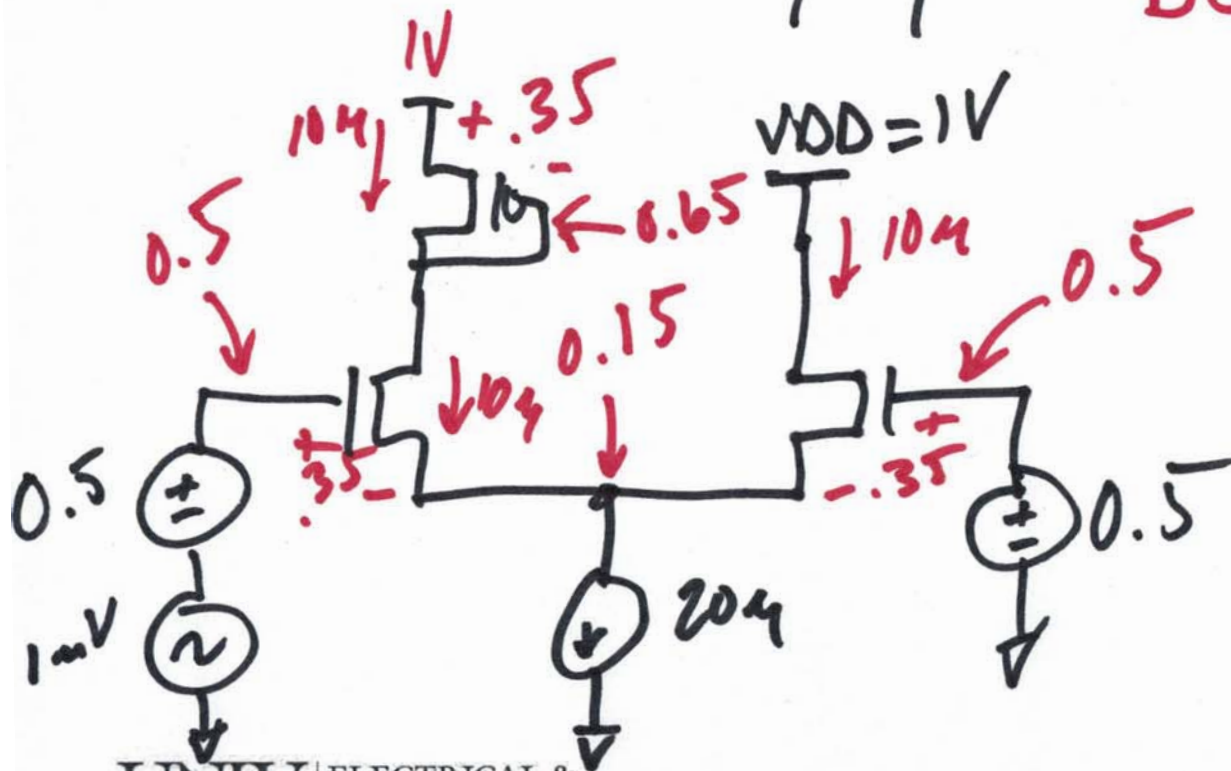


$$g_m = K_P \frac{W}{L} (V_{DS} - V_{TH}) \quad \text{AC CKT}$$
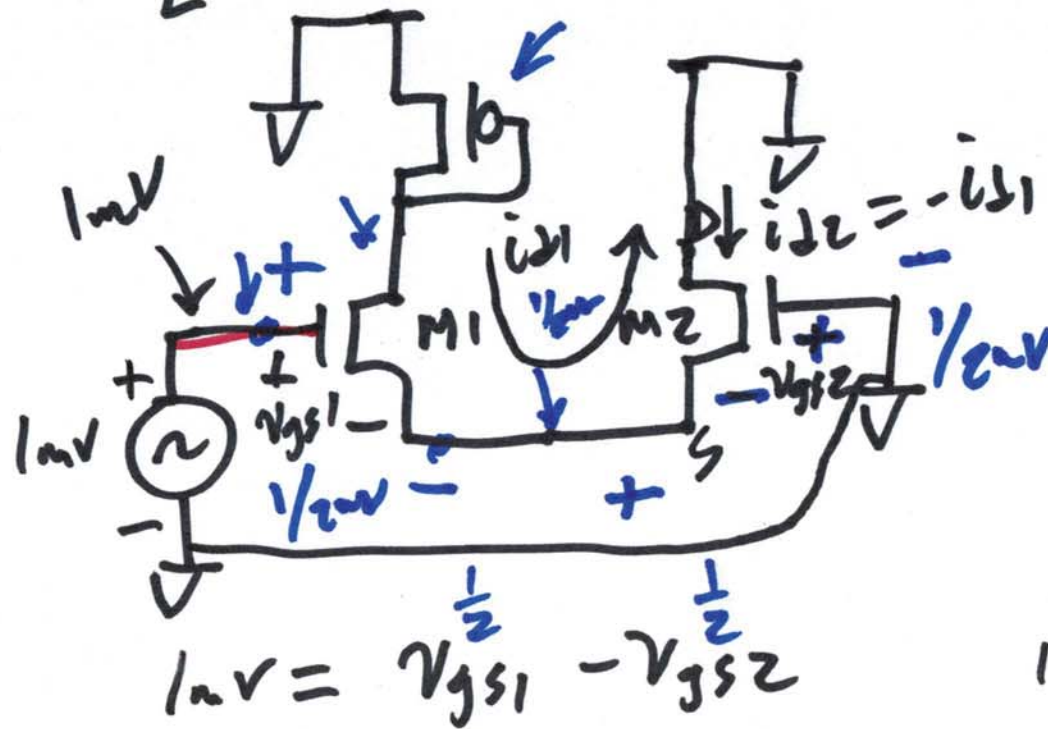
$$g_m = \sqrt{2 \cdot K_P \frac{W}{L} I_D}$$



$$1mV - v_{gs1} + v_{gs2} = 0$$

$$1mV = v_{gs1} - v_{gs2}$$

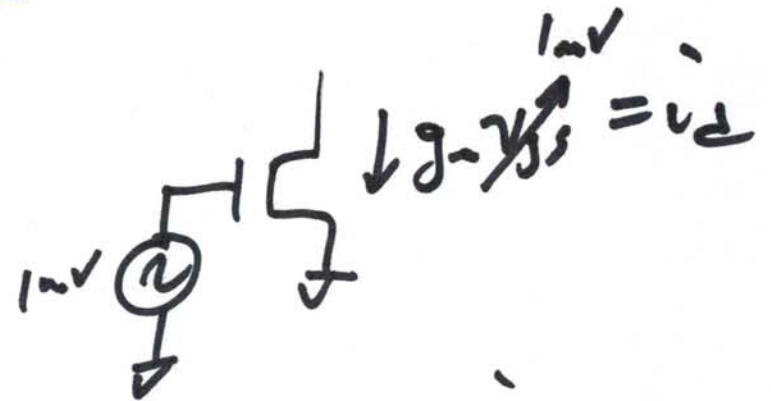

$$v_{gs1} = \frac{i_{d1}}{g_{m1}}$$

$$v_{gs2} = \frac{i_{d2}}{g_{m2}}$$


$$i_{d1} = -i_{d2}$$

CMOSedu.com

$$i_{d1} = \frac{1mV \cdot 150\mu}{\frac{1}{2}} = 75\mu A$$

$$= i_{d1} \left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right)$$

$$= i_{d1} \cdot \frac{2}{g_{m1}}$$

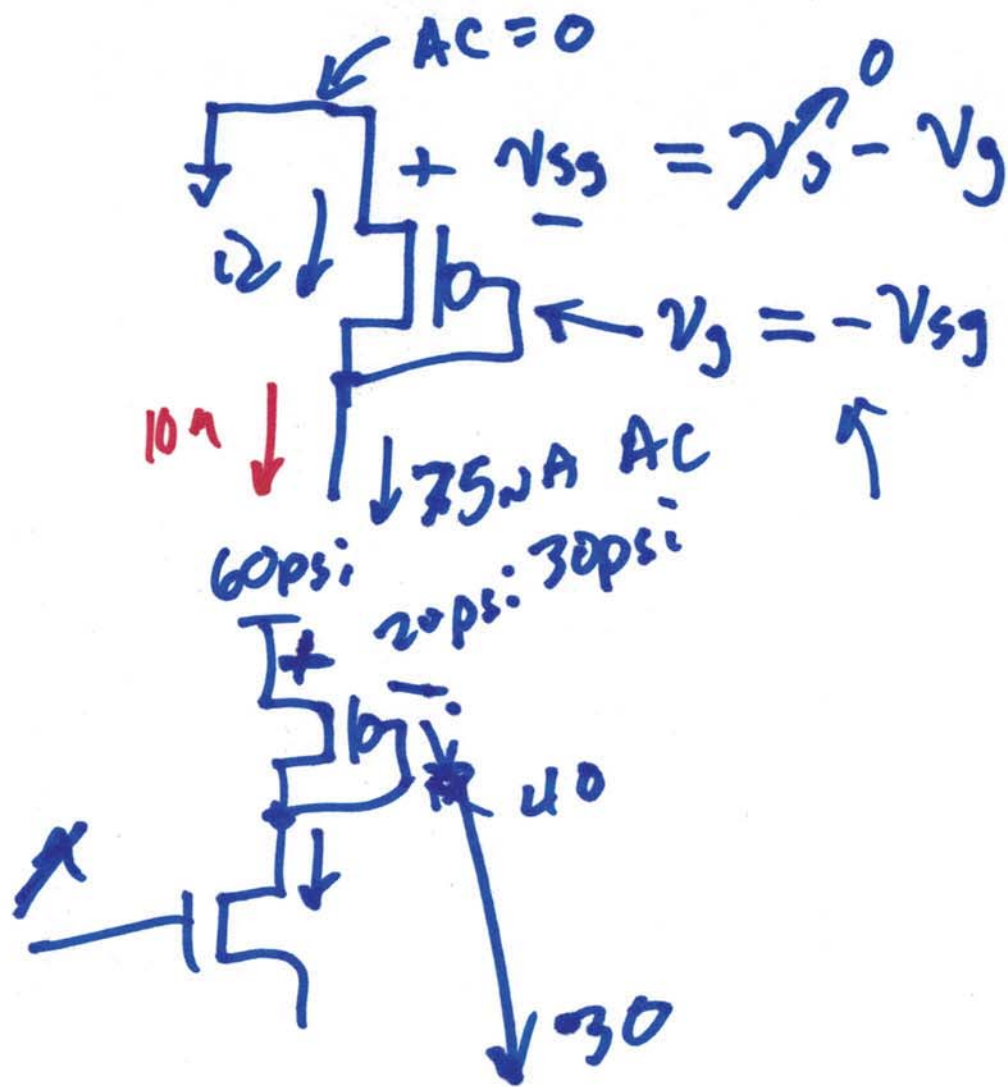

$$i_d = 75 \mu A$$


$$g_m V_{sg} = i_d$$

$$150 \mu S \cdot V_{sg} = 75 \mu A$$

$$V_{sg} = \frac{1}{2} mV$$

$$V_g = -\frac{1}{2} mV$$

Temp Behavior

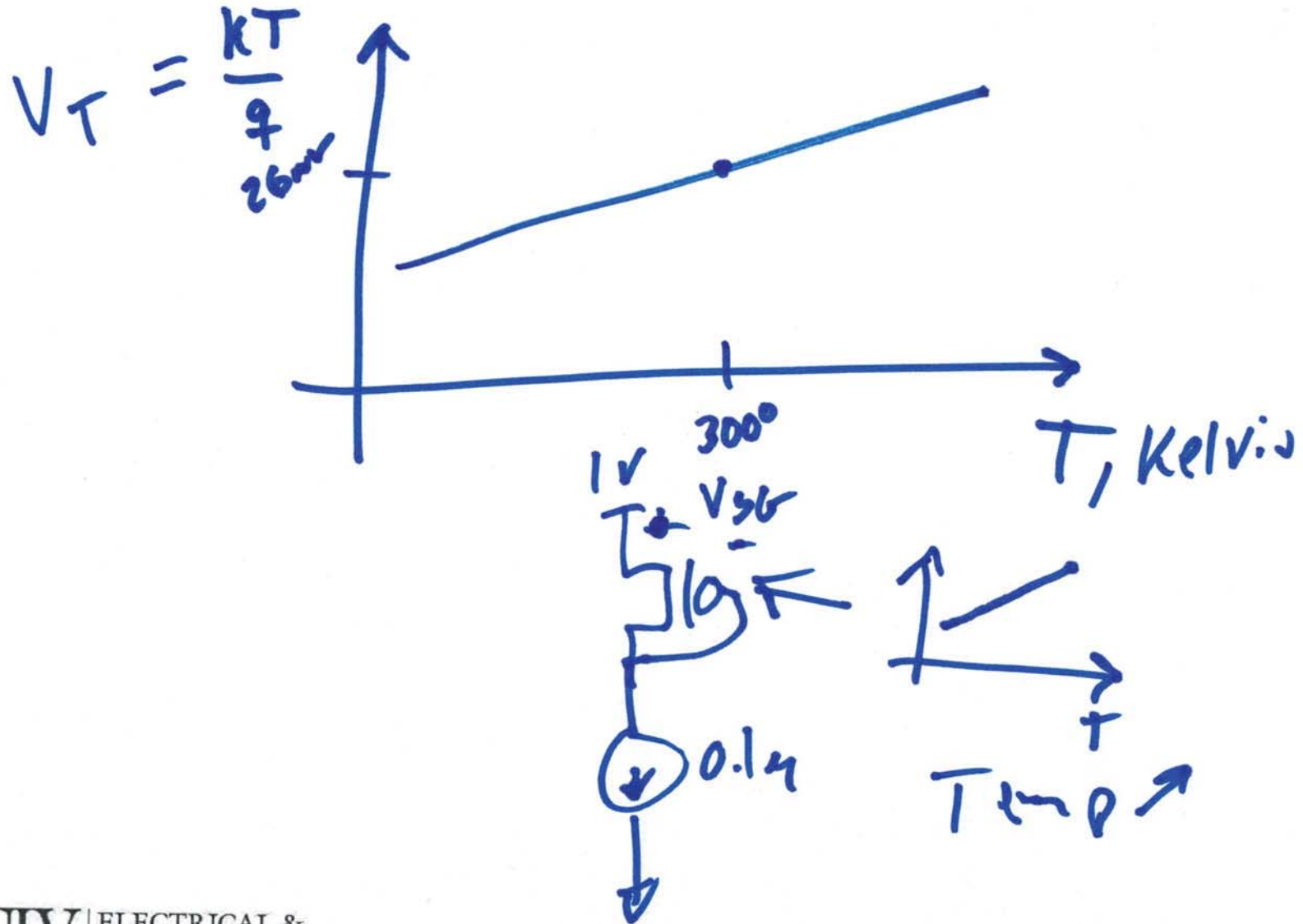

4)

$$I_D \uparrow \quad g_m r_o \downarrow$$

open gain $\nearrow$

$$g_m = \sqrt{2K_P \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

$$(V_{GS} - V_{TH}) = V_N$$

$$g_m r_o \propto \frac{1}{\sqrt{I_D}}$$

$$f_T \quad I_D \uparrow \quad f_T \uparrow$$

$$V_{GS} \uparrow \quad f_T \uparrow$$

$$I_D \uparrow \quad g_m r_o \downarrow$$

$$V_N \uparrow \quad f_T \uparrow$$