


# Lecture 10


EE 420 / ECE 620

Analog IC Design


Feb. 22, 2017
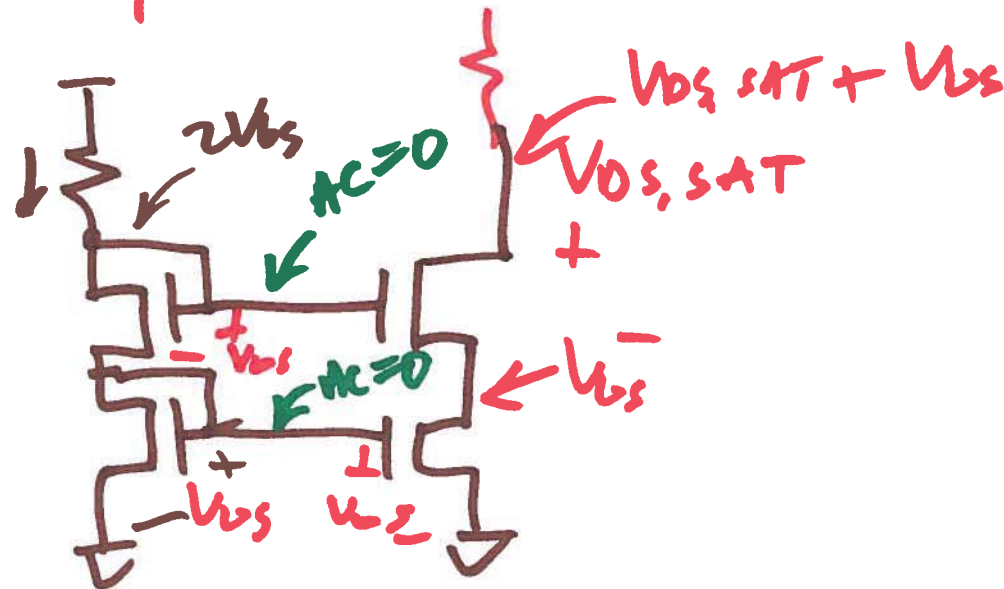
$$\frac{K_{pW}}{2} \cdot \frac{(V_{OS} - V_{TH})^2}{C} = \frac{W(D-2V_{TH})}{R}$$



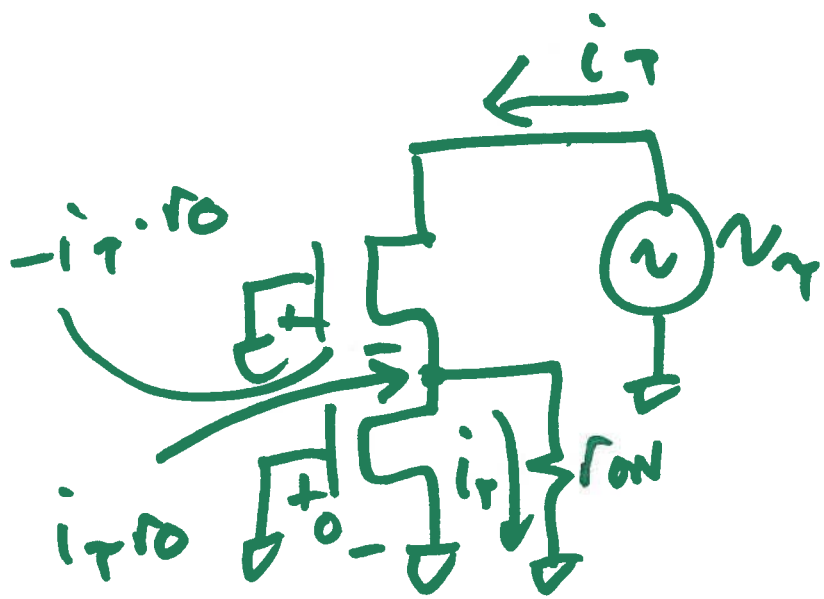

AC CKT

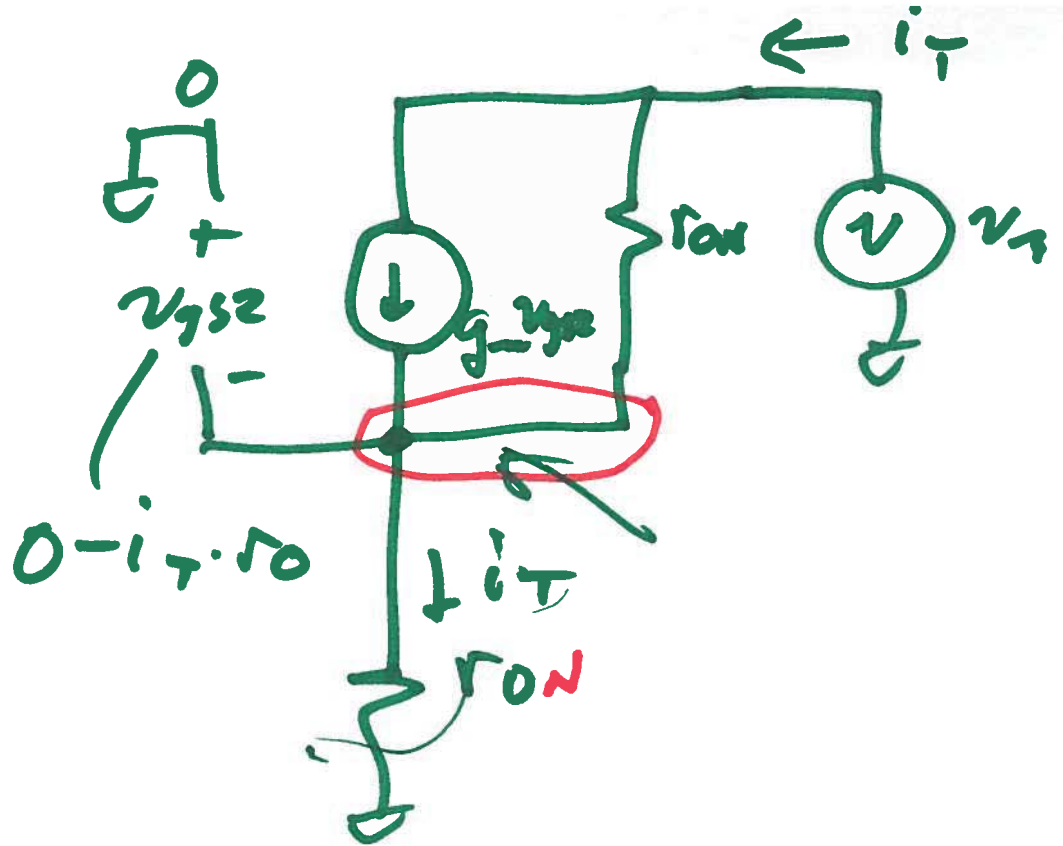


$$\frac{v_T - (i_T r_{ON})}{r_{ON}} + g_{mN} (-i_T r_{ON}) = i_T$$

$$v_T = (g_{mN} r_{ON}^2 + r_{ON} + r_{ON}) i_T$$

$$R_{ocnsn} = \frac{v_T}{i_T} = g_{mN} r_{ON}^2 + r_{ON} + r_{ON} \approx \underline{\underline{g_{mN}^* r_{ON}^2}}$$

2)



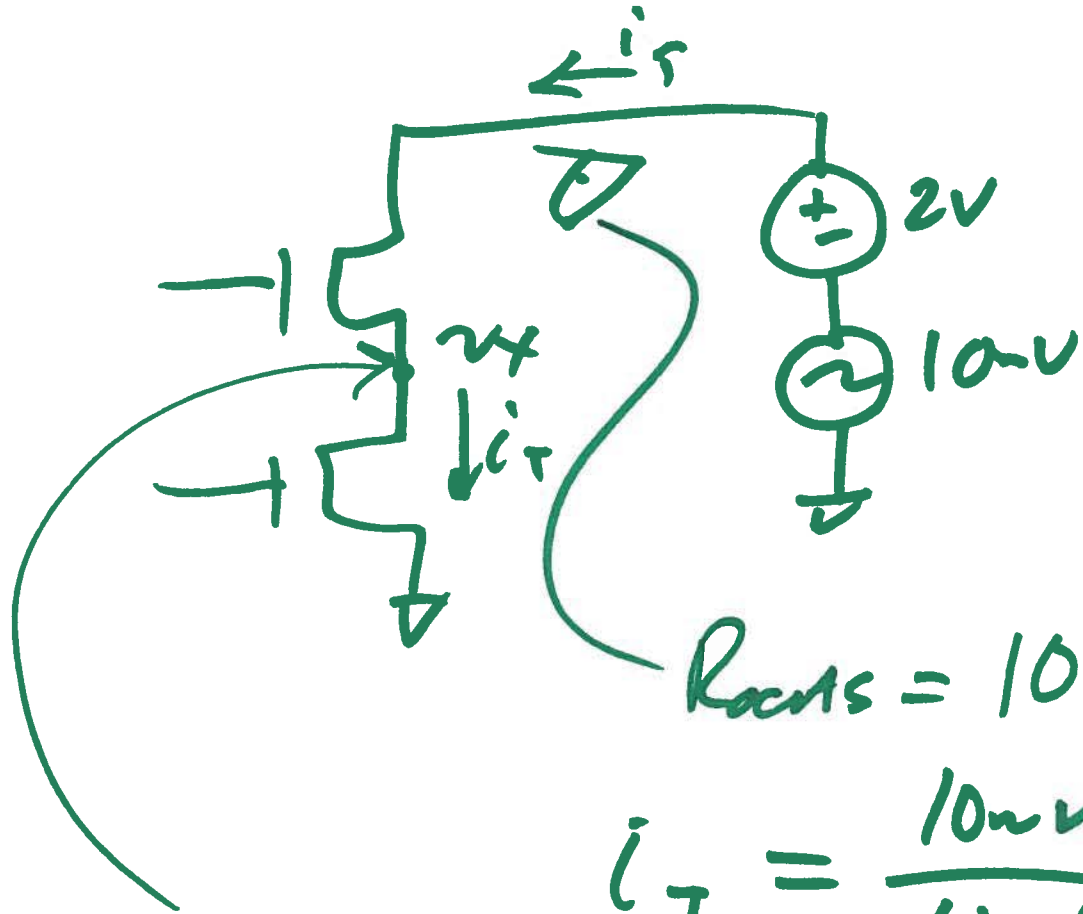

$$R_{out5} = 10 M\Omega$$


$$i_T = \frac{10\mu V}{10 M\Omega} = \underline{\underline{1.0 nA}}$$

$$v_x = i_T \cdot r_{on}$$



$$10^{-9} \cdot 100K$$

$$v_x = 10^{-9} \cdot 10^5 = 10^{-4} V = 0.1 mV$$


4)

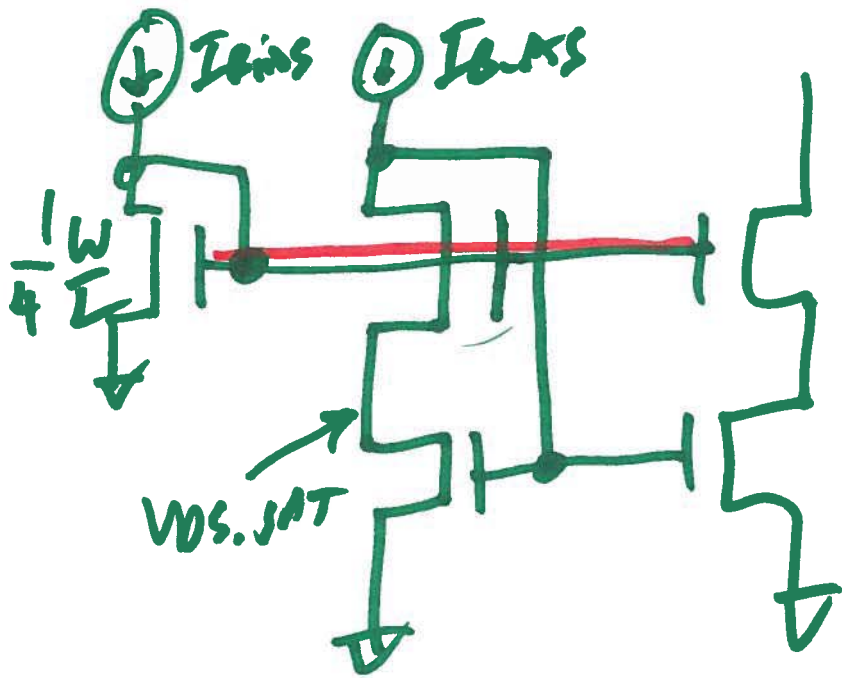

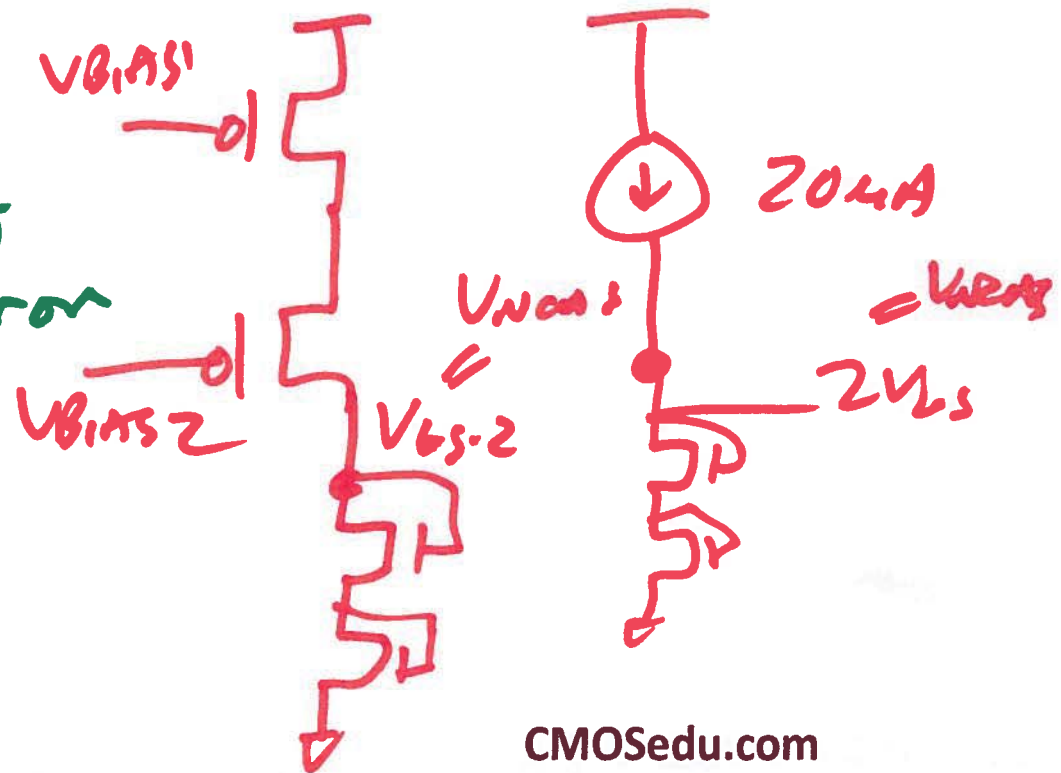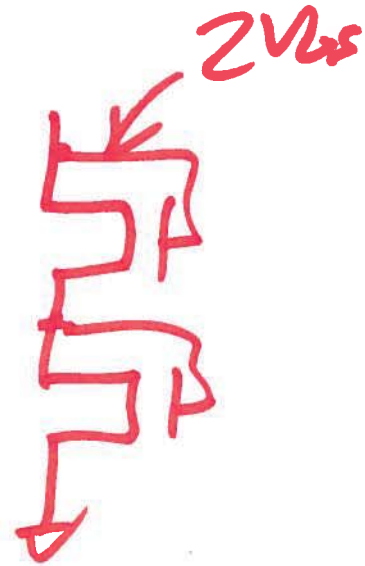Low-Voltage  
wide-swing  
Current  
Mirror




5)

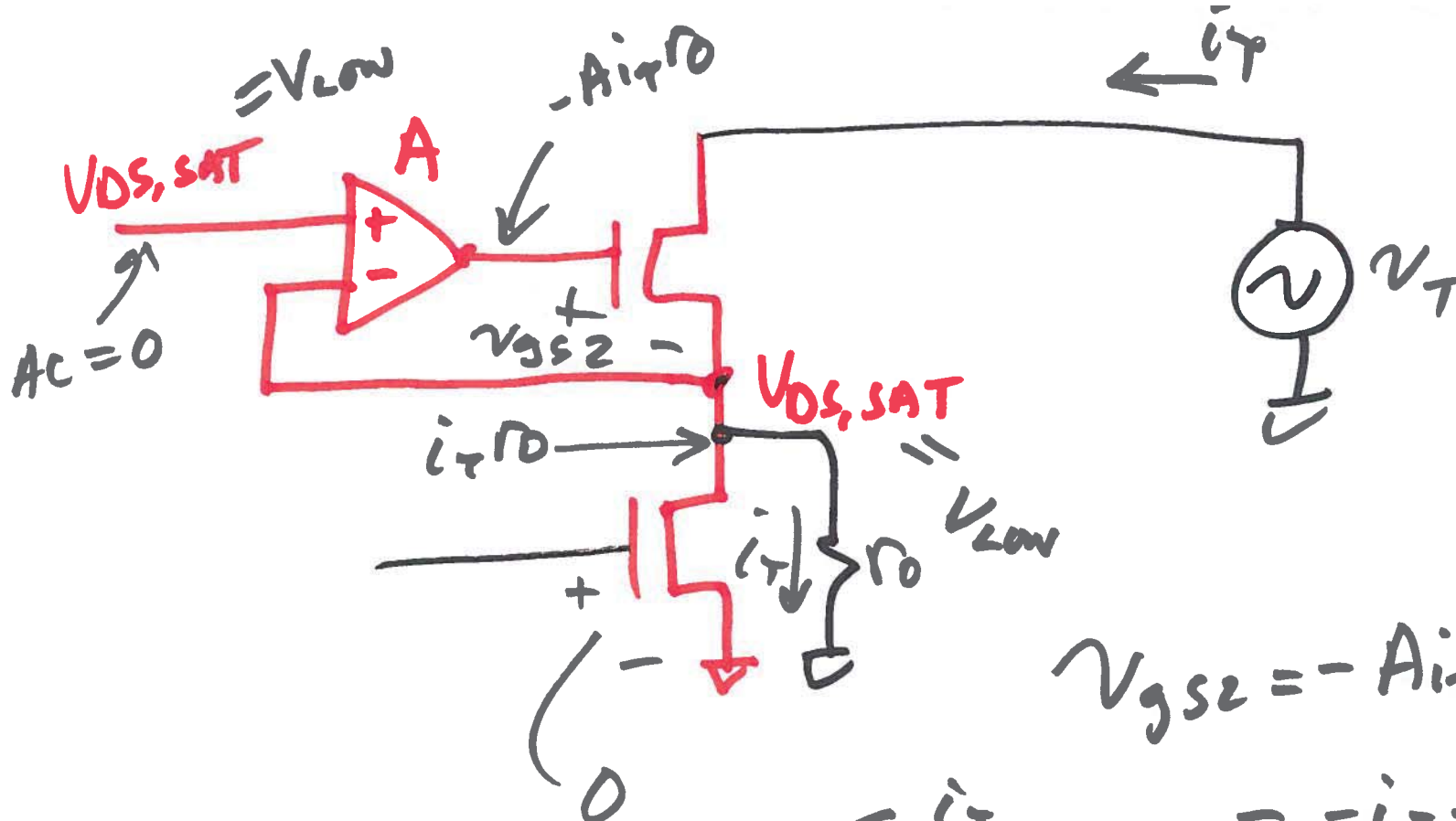

$$v_{gs2} = -A i_T r_o - i_T r_o$$

$$= -i_T r_o (1+A)$$

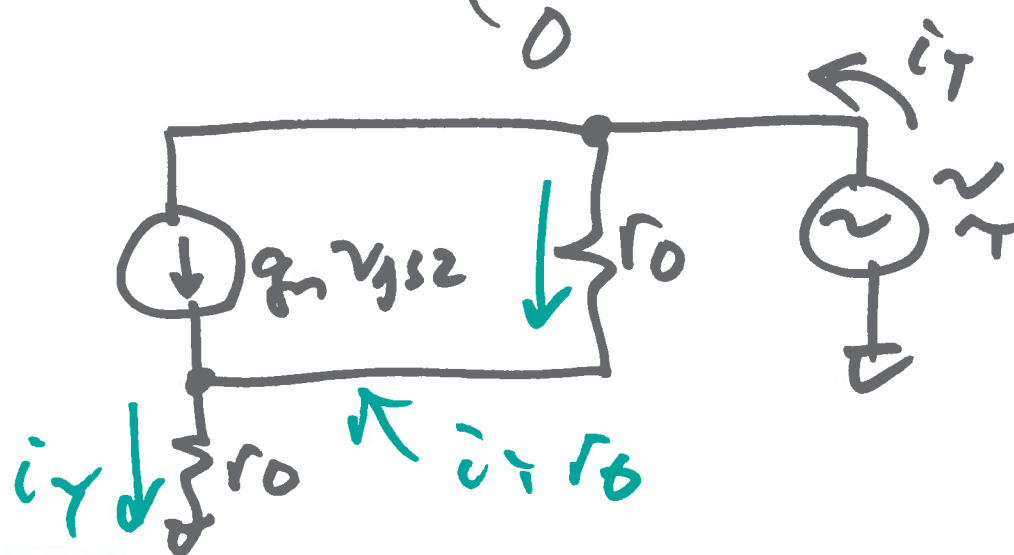

$$i_T = \frac{v_T - i_T r_o}{r_o}$$

$$+ g_m (-i_T r_o)(1+A)$$

6)

$$i_T(r_o + r_o + g_m r_o^2(1+A)) = v_T$$

$$R_{out} \Big|_{r.l.s.} = \frac{v_T}{i_T} = 2r_o + g_m r_o^2(1+A)$$

$$\approx \underline{\underline{g_m r_o^2(1+A)}}$$