

EE 420 / ECG 620

$$i_d = \frac{v_{sg}}{g_m} \cdot g_m$$

$$v_{nt} = -\frac{1}{g_m} \cdot i_d$$

Lecture 12

MARCH 1, 2017

$$v_{nt} = -6.5k \cdot 150\mu A$$

Analog IC DESIGN

$$= -975\mu V$$

$$\approx -1\mu V$$

$$20 \log 10^{-3} = -60 \log 10$$


$$= -60 \text{ dB}$$

$$AC = 150\mu A$$

$$10^{-3} = 0.001\text{V}$$


$$= 1\mu V$$
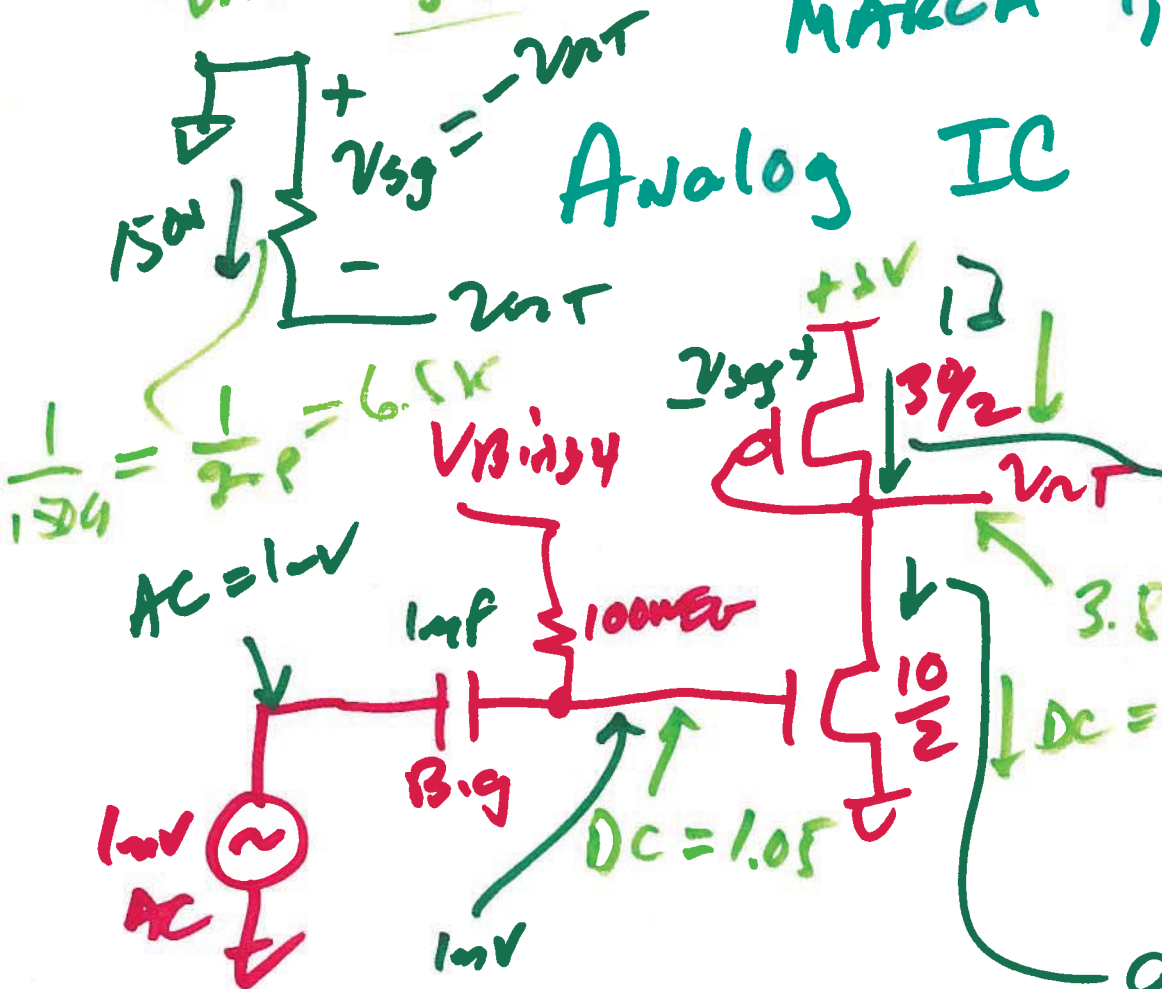
$$g_m v_{sg} = 150\mu \cdot 1\mu V = 150\mu A$$



1)

COMMON - SOURCE

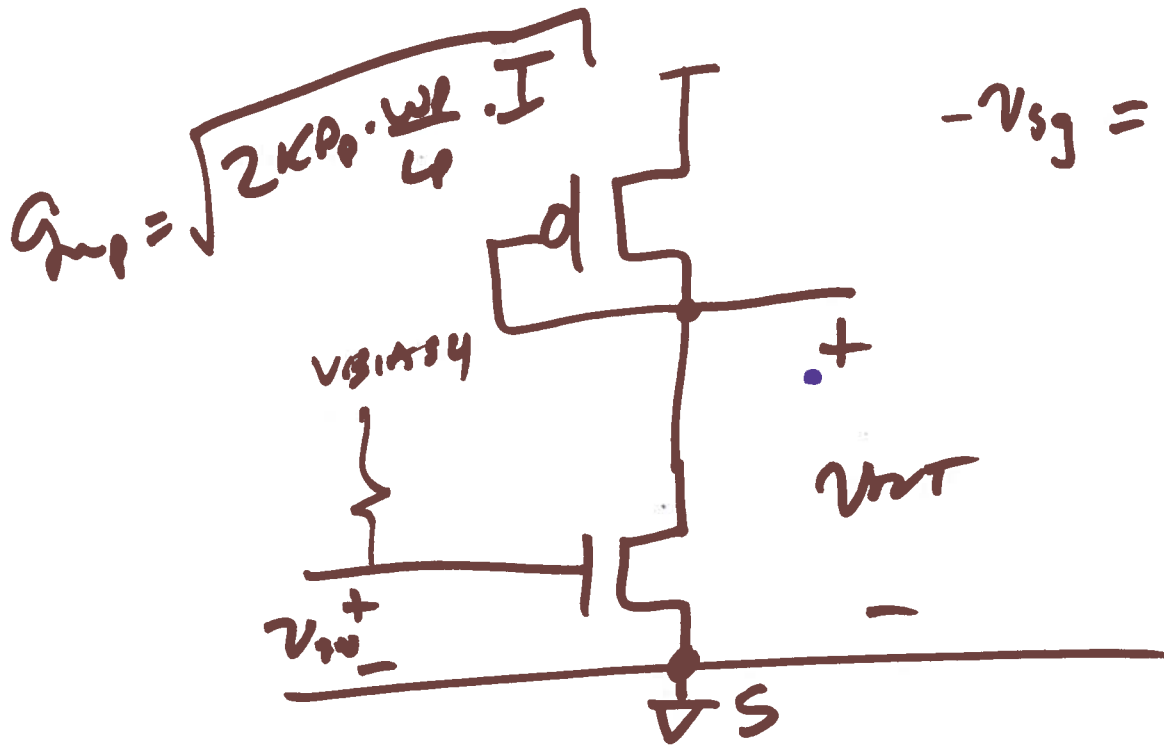

$$\frac{v_{OUT}}{v_{IN}} = -\frac{g_{mP}}{g_{mN}}$$




$$-v_{sg} = v_{IN} - v_{sg} + v_{OUT}$$

$$i_D = g_{mP}(-v_{IN})$$

$$v_{OUT} = v_{gs} - v_{IN}$$

$$\frac{v_{OUT}}{g_{mN}} = \frac{g_{mP}(-v_{IN})}{g_{mN}}$$
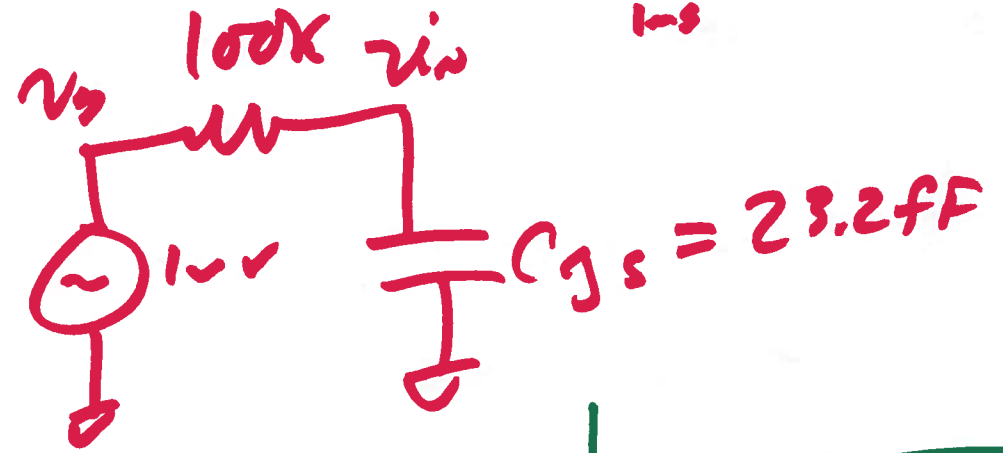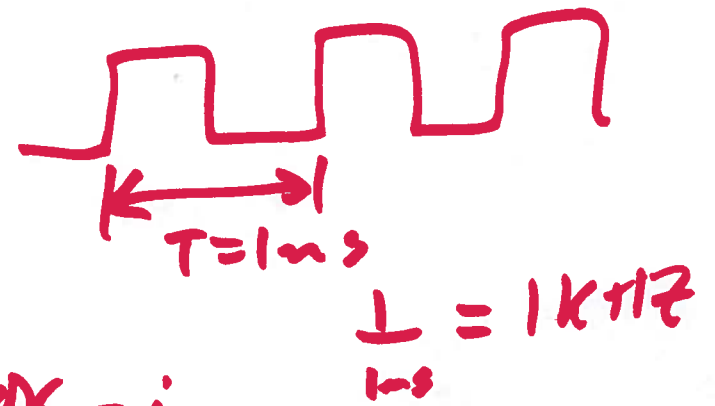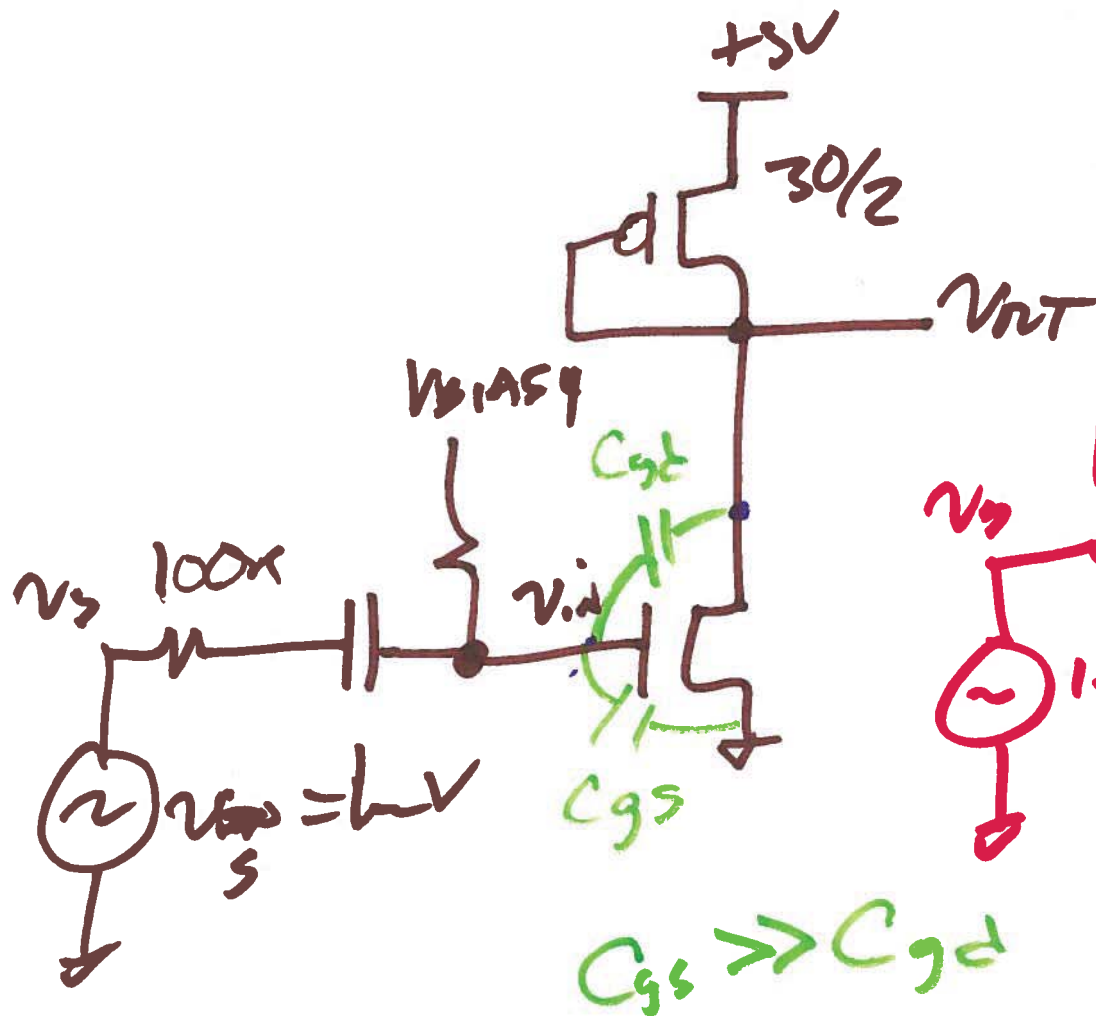
$$\frac{v_{OUT}}{v_{IN}} = -\frac{g_{mN}}{g_{mP}} \approx -1 \frac{V}{V}$$



$C_{gs} \gg C_{gd}$



$(C_{gs} + 2C_{gd})$


$$f_{3dB} = \frac{1}{2\pi \cdot 10^5 \cdot 23.3 \cdot 10^{-15}}$$

$$= \frac{0.159}{23.3 \cdot 10^{-10}}$$

$$63. \text{MHz} = \frac{1.59}{23.3} \cdot 10^{-9}$$

3)

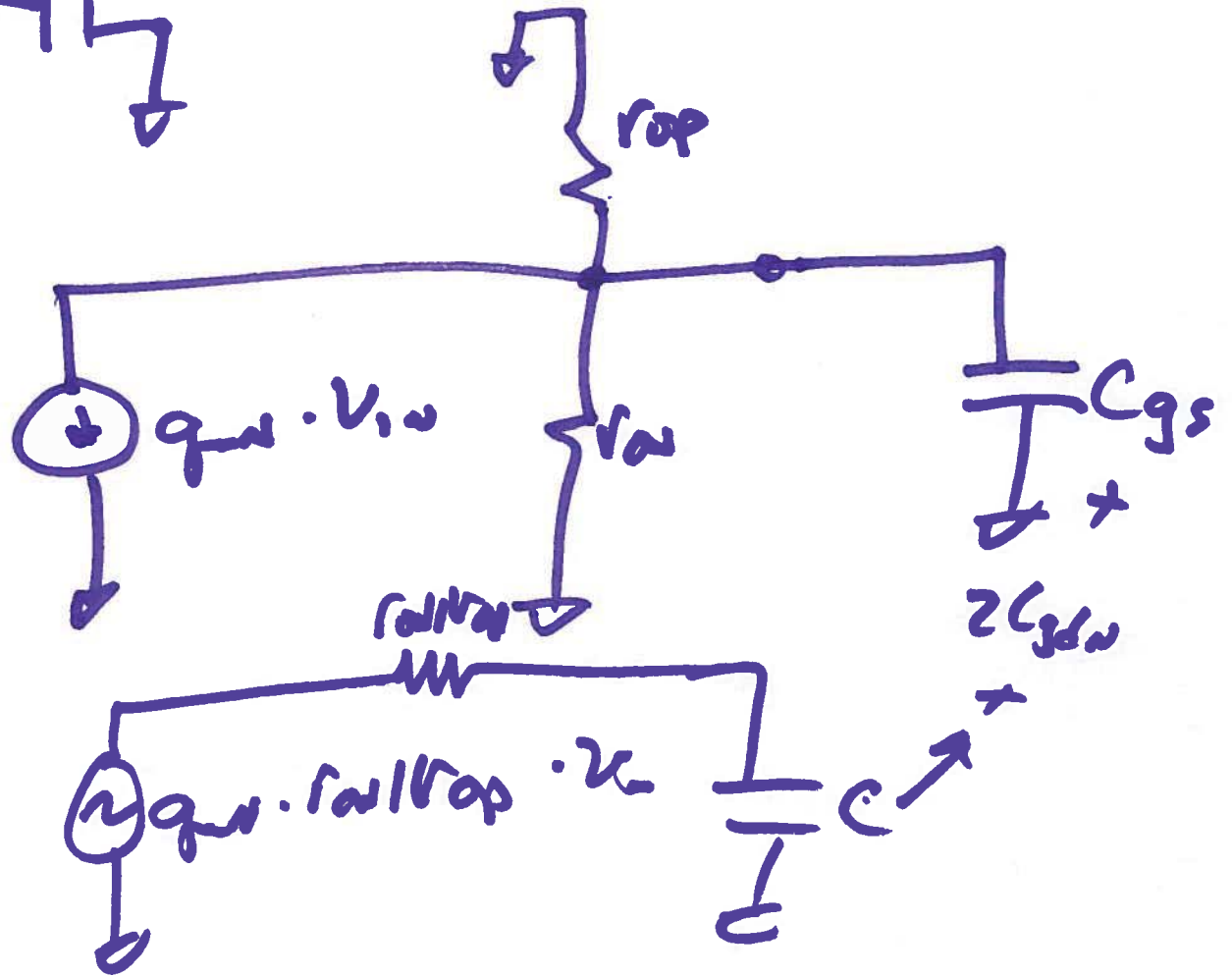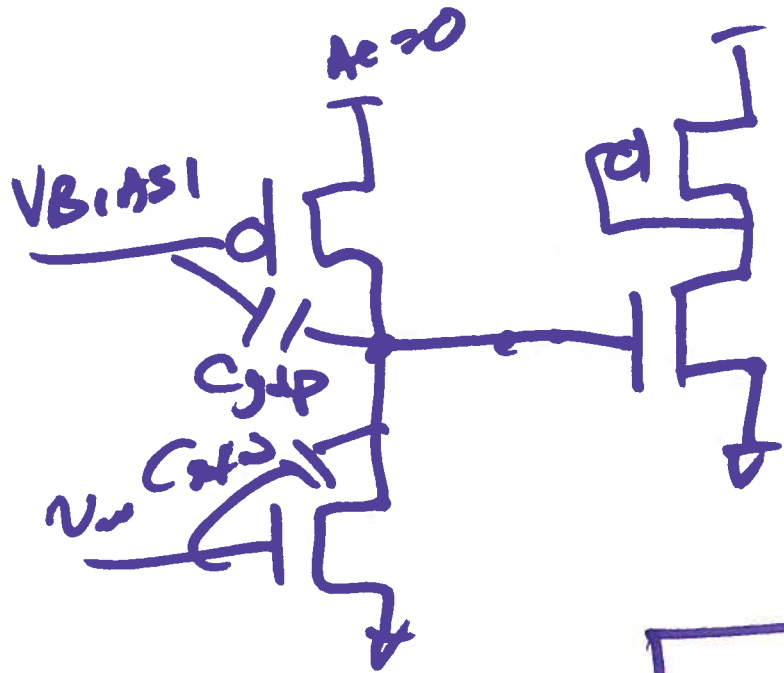

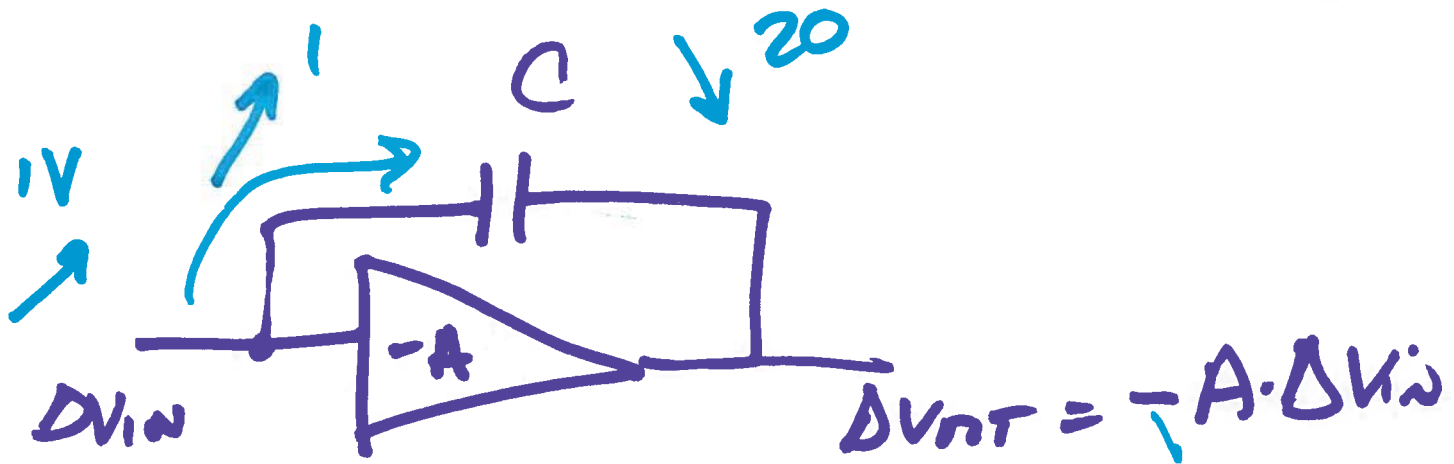

~~$-A \cdot 1$~~

ΔV_{in}

\downarrow

$\frac{1}{C(1+A)}$

\downarrow

ΔV_{out}

\downarrow

$\frac{1}{C(1+\frac{1}{A})}$

$-20V$

5)