


EE 420 / ECG 620

Analog IC Design

Lecture 13


UNLV

MARCH 6, 2017

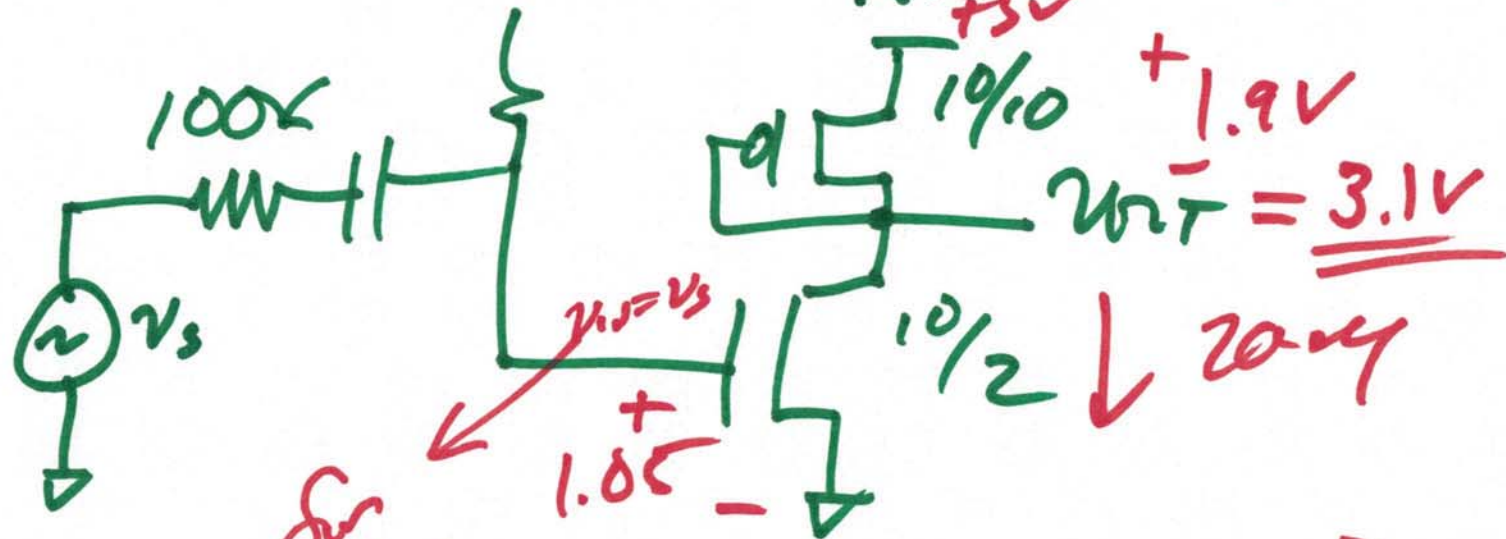

$$20\mu A = \frac{40\mu A}{2} (V_{SG} - 0.9)^2$$

$$V_{SG} = 1.9V$$

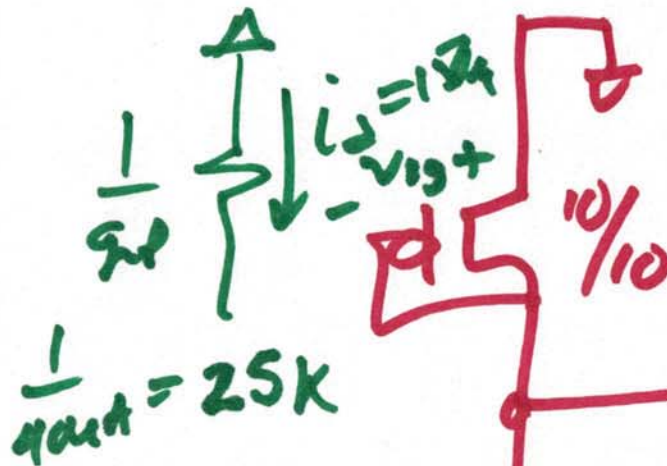

$$g_p = k_p \cdot \frac{W}{L} (V_{SG} - V_{TP})$$

$$g_p = 40 \frac{\mu A}{V}$$

$$g_m v_s = 150 \mu A \cdot 1V = 150 \mu A$$

$$v_{sg} = \frac{i_d}{g_p}$$

Small-signal but will assume P (+, -)

$$v_{mT} = -v_{sg} = -\frac{i_d}{g_p}$$


$$\frac{9K}{9K + 13.5K}$$

$$\frac{2}{2+3} = \frac{2}{5} = 0.4$$

$$\frac{4K \cdot 25K}{6.5K} = -\frac{g_m}{g_p}$$


$$v_s = \frac{i_d}{g_p} = \frac{-i_d \cdot \frac{1}{g_p}}{i_d \cdot \frac{1}{g_m}}$$

2)

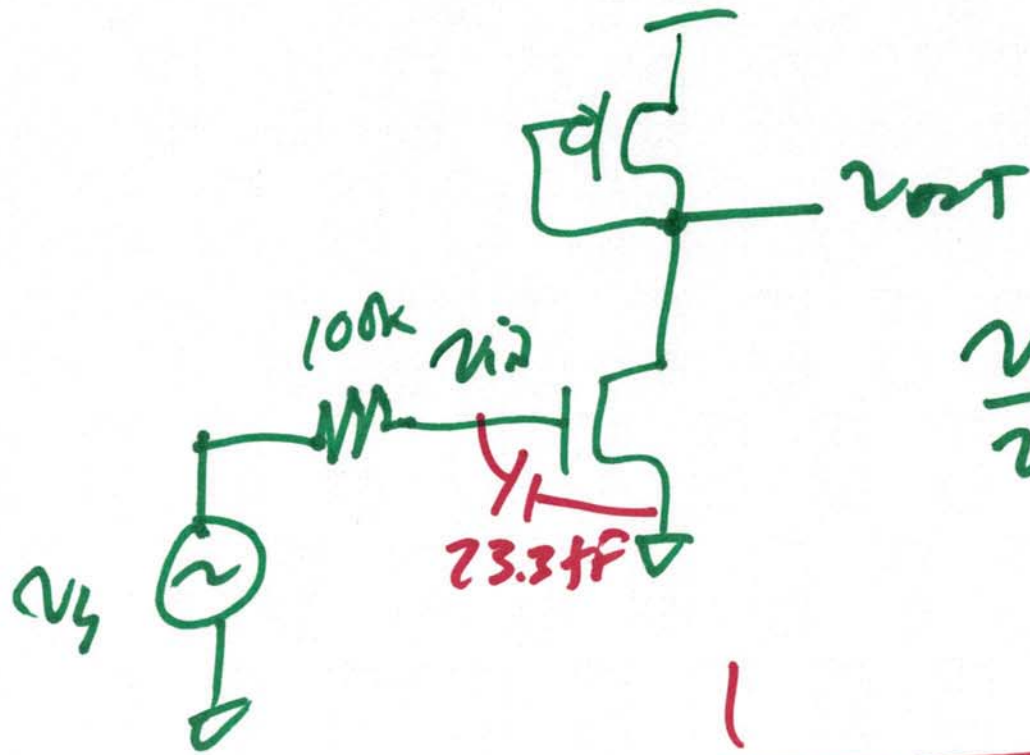

$$\frac{v_{out}}{v_{in}} = - \frac{g_{mN}}{Z_P} = - \frac{1}{Z_P} \cdot \frac{1}{g_{mN}}$$
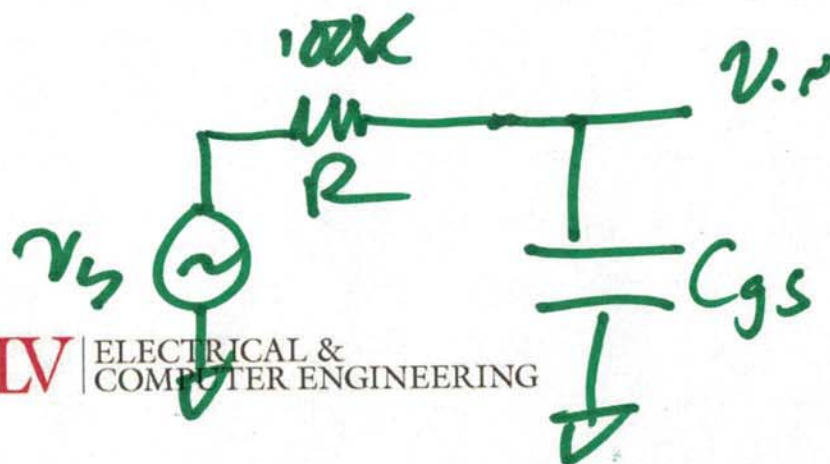
$$f_{3dB} = \frac{1}{2\pi \cdot 100k \cdot 23.3fF} = 68MHz$$



$$v_{in} = v_s \cdot \frac{1/j\omega C_{gs}}{1/j\omega C_{gs} + R}$$

$$\frac{v_{in}}{v_s} = \frac{1}{1 + j\omega C_{gs} \cdot R}$$

CMOSedu.com

3)


$$\frac{V_{out}}{V_{in}} \cdot \frac{V_{out}}{V_{in}} = -\frac{g_m R}{g_m} \cdot \frac{1}{1 + j\omega C_{gs} \cdot R}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\frac{g_m R}{g_m}}{1 + j\omega C_{gs} \cdot R}$$

$$f_{3dB} = \frac{1}{2\pi C_{gs} \cdot R} = 68 \text{ MHz}$$

$$\frac{-4}{1 + j \frac{f}{f_{3dB}}} = \frac{-4}{1 + j \cdot f \cdot 2\pi C_{gs} \cdot R}$$

4)

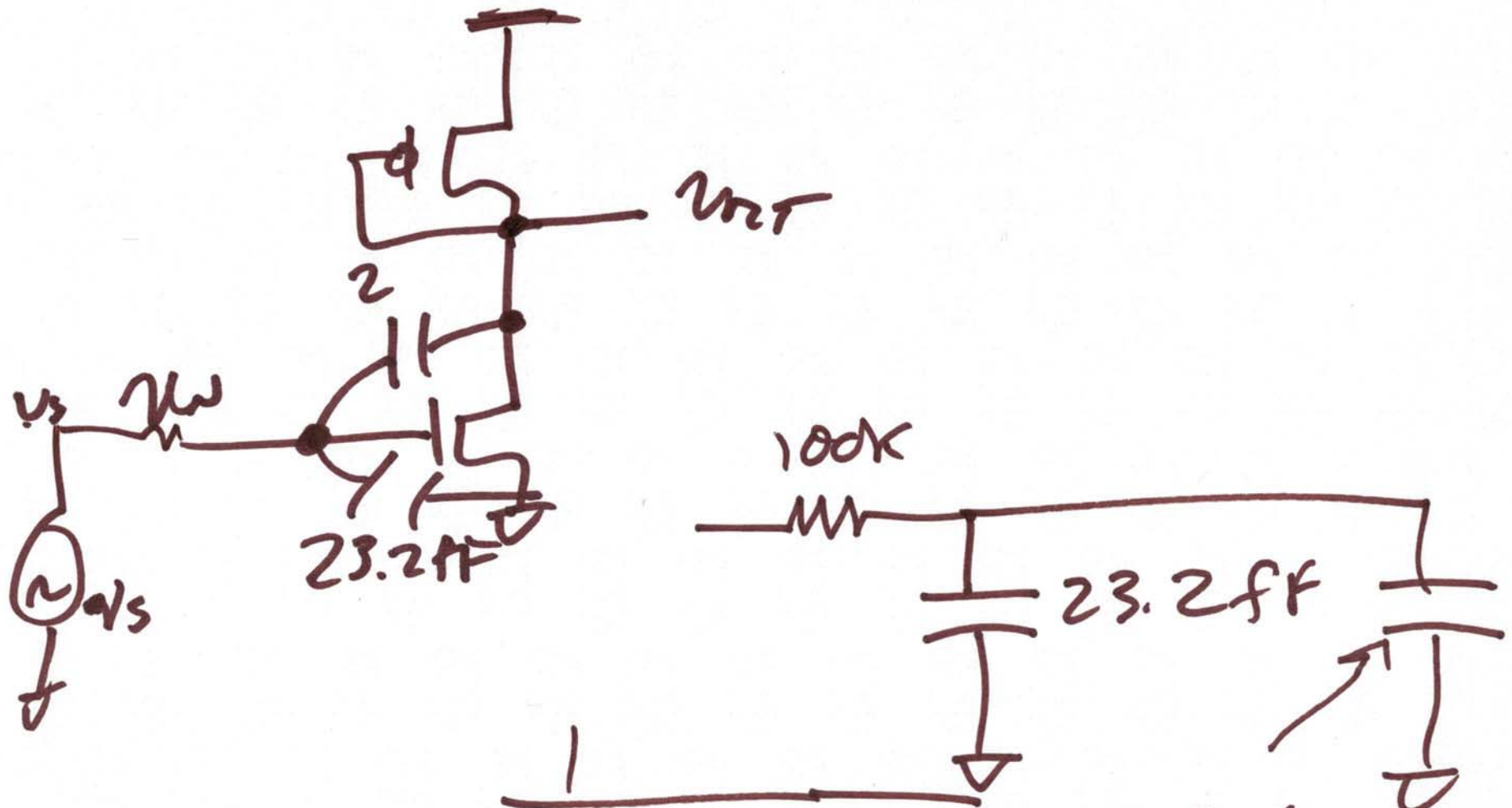


$$f_{3dB} = \frac{1}{2\pi \cdot 100k \cdot 33.2fF}$$

$$= \underline{\underline{48kHz}}$$

$$23.2fF (1 + |4|)$$

$$10fF$$

5)

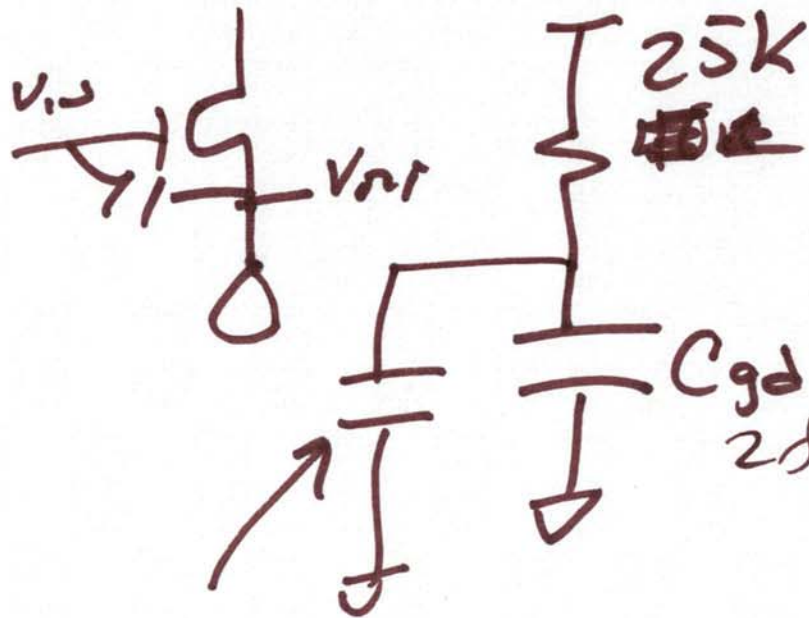

$$C_{gd} \left(1 + \frac{1}{A}\right) \approx C_{gd}$$

2 fF

$$C_{ox}' \cdot \frac{2}{3} \cdot W \cdot L = 30 \text{ fF}$$

$$\frac{f_{3dB}}{2\pi} = \frac{200 \text{ MHz}}{2\pi}$$

$$2 \cdot 10^9$$

$$200 \text{ MHz}$$

$$1.75 \text{ fF} \cdot \frac{2}{3} \cdot 10 \mu \cdot 10 \mu = 30 \text{ fF} \cdot X$$

$$f_{3dB} = \frac{1}{2\pi \cdot 25 \text{ k} \cdot 30 \text{ fF}} = 4 \times \frac{.159}{25 \text{ k} \cdot 30 \text{ fF}} = \frac{.159}{800 \cdot 10^{-12}}$$

$$200 \text{ MHz} \approx \frac{1.59}{800} \cdot 10^9$$


6)

Homework &
Quizzes

Last year's Midterm

Examples from the book

EOC from the book

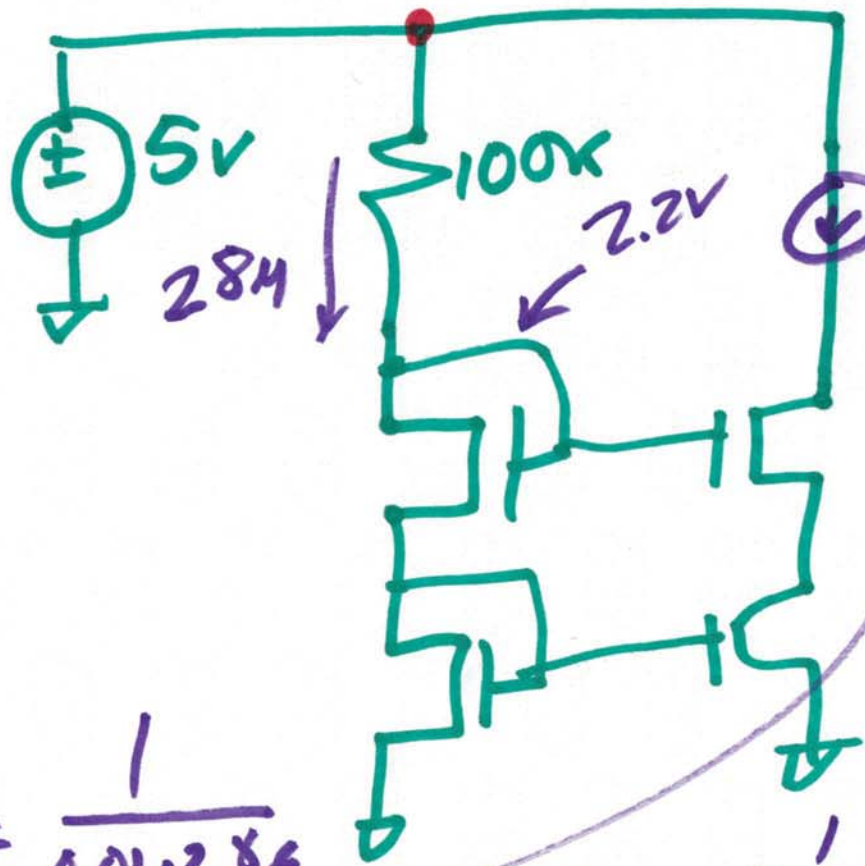

$$\frac{5 - 2V_{GS}}{100k} = \frac{1204.5}{2} \cdot 5 (V_{GS} - 0.8)^2$$

$$5 - 2V_{GS} = 30(V_{GS} - 0.8)^2$$

V_{GS}		
1V	3	1.2
1.1	2.88	2.7
1.15	2.7	3.675
1.05	2.9	1.875
1.08	2.84	2.35


$$r_o = \frac{1}{0.01 \cdot 284}$$

$$g_m = \sqrt{2 \cdot 284 \cdot \frac{10}{2}}$$

$$r_o = 0.9 \cdot I_D$$

$$i_T = \frac{1\mu V}{R_{out}} = \frac{1\mu V}{g_m r_o^2}$$

8)

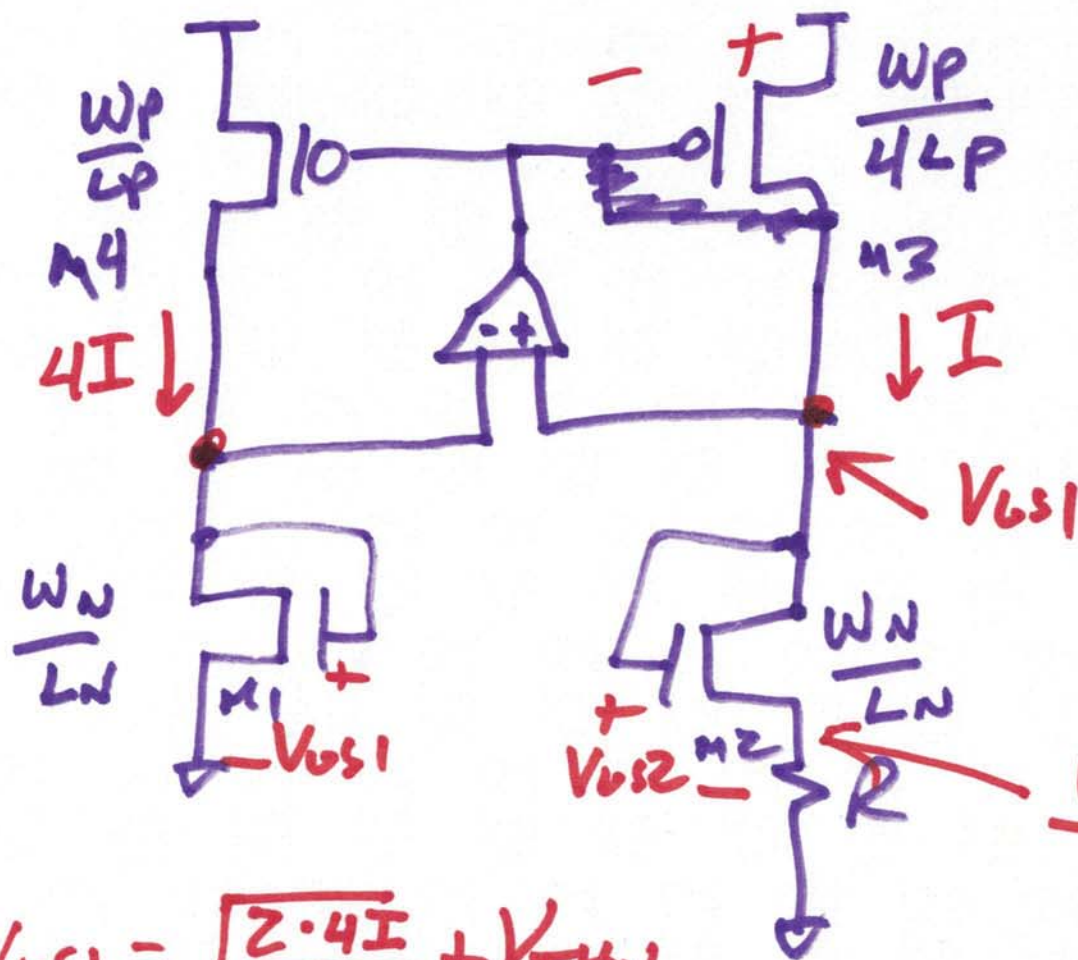

Calculate the current in the circuit

$$\frac{V_{bs1} - V_{bs2}}{R} =$$

$$V_{bs1} = \sqrt{\frac{2 \cdot 4I}{K_{PN} \cdot \frac{W_p}{L_p}}} + V_{THN}$$

$$V_{bs2} = \sqrt{\frac{2I}{K_{PN} \cdot \frac{W_p}{L_p}}} + V_{THN}$$

9)