

EE 420 / EELG 620

Electronics II / Analog IC

Lecture 16 Design

MARCH 20, 2017

$$i = \frac{V_{NT} \left(\frac{1}{|A|} + 1 \right)}{1/j\omega C}$$


$$\rightarrow V_{NT} = i \cdot \frac{1}{j\omega C \left(1 + \frac{1}{|A|} \right)}$$

Derive Miller's Theorem


$$i = \frac{V_{in} - V_{out}}{1/j\omega C}$$

$$= \frac{V_{in} (1 + |A|)}{1/j\omega C}$$


$$V_{in} = i \cdot \frac{1}{j\omega C (1 + |A|)}$$

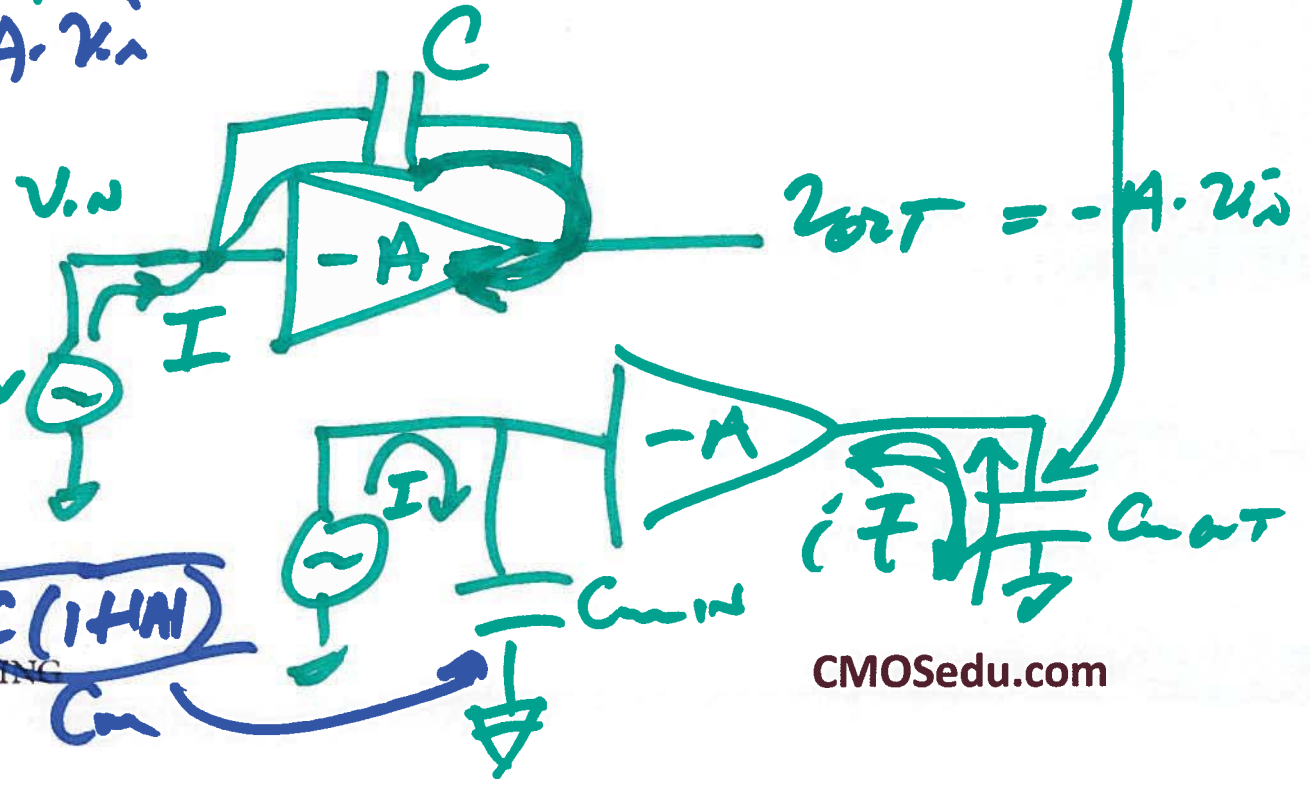

11)

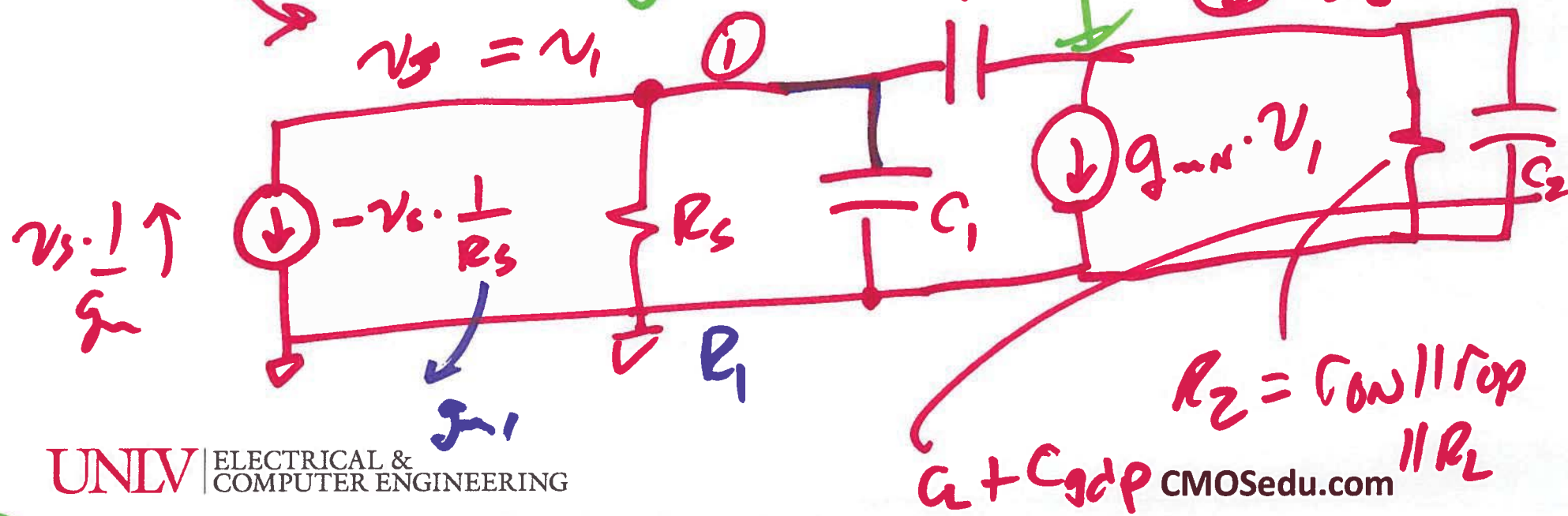

21

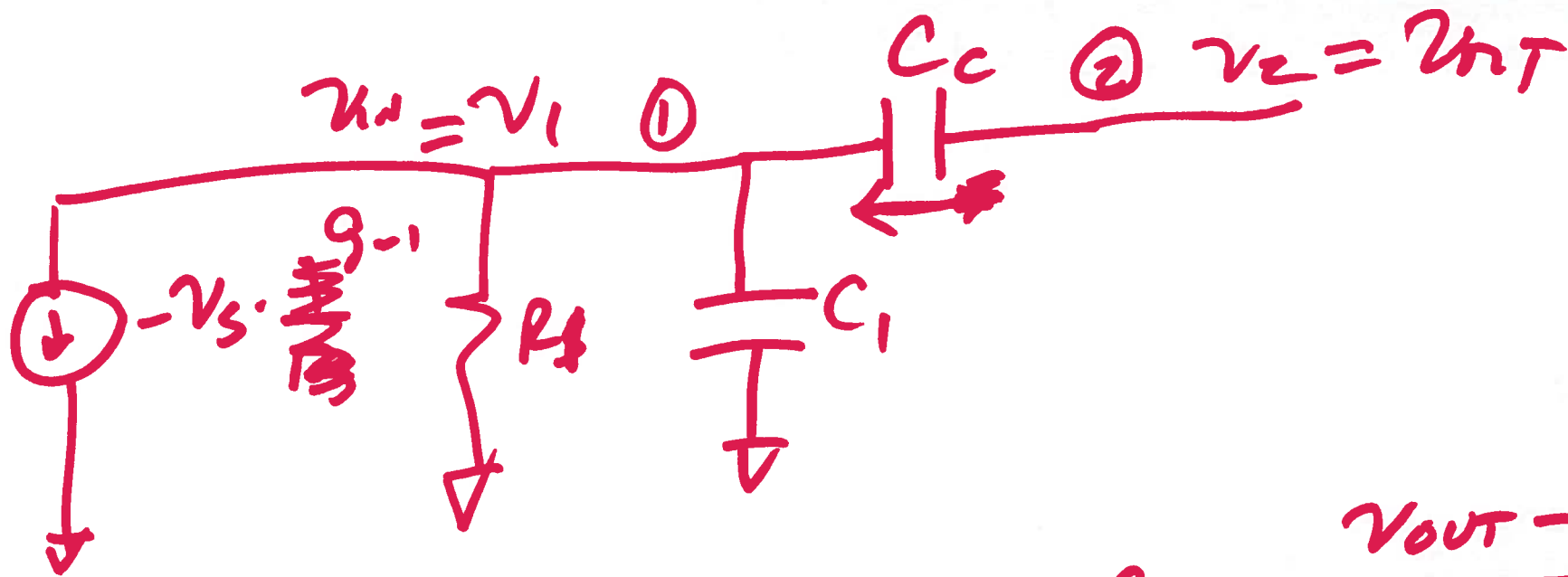


$$v_{in} \cdot R_1 \parallel \frac{1}{j\omega C_1} - v_s \cdot g_{m1} = \frac{v_{out} - v_{in}}{1/j\omega C_c}$$


$$v_{in} \cdot \frac{R_1 \cdot \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} - v_s g_{m1} = j\omega C_c (v_{out} - v_{in})$$

$$v_{in} \cdot \frac{R_1 / j\omega C_c}{1 + j\omega C_1 R_1} - v_{in} \frac{g_{m1}}{j\omega C_c} = v_{out} - v_{in}$$

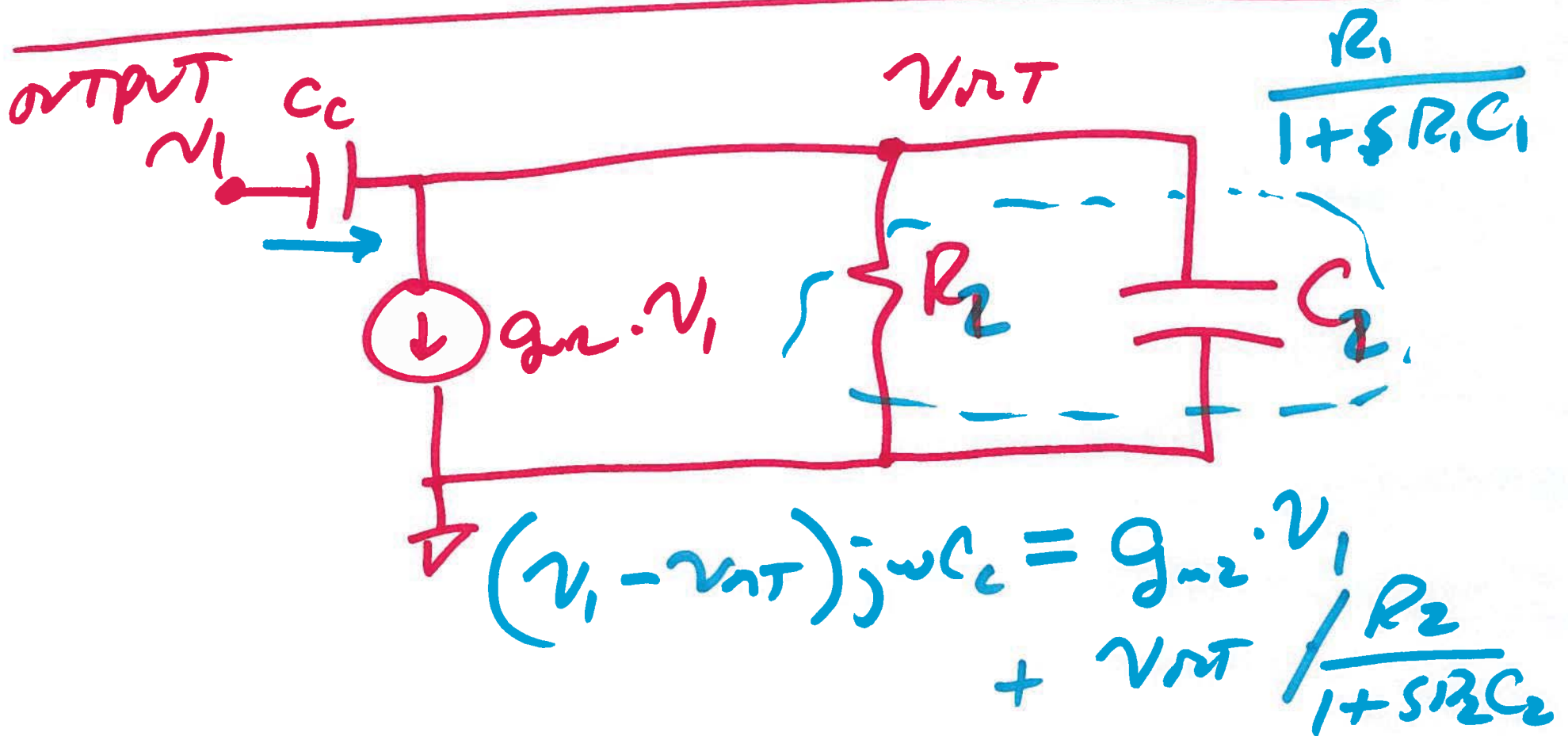3)

INPUT $V_{in} \left(1 + \frac{R_1}{sC_c R_1 + sC_c} - \frac{g_m}{sC_c} \right) = 2v_T$



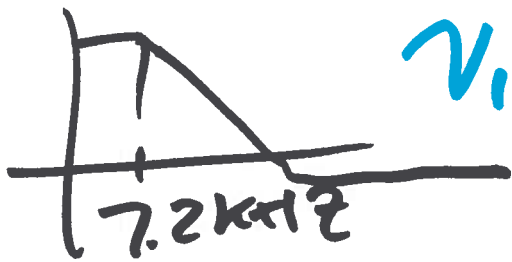

$$v_1(-g_{m2} + j\omega C_c) = v_{out} \left(j\omega C_c + \frac{1+sR_2}{R_2} \right)$$

$$\frac{v_{out}}{v_1} = \frac{-(g_{m2} - j\omega C_c)}{j\omega C_c + \frac{1+sR_2}{R_2}} \cdot \frac{R_2}{R_2}$$


$$\text{zero} = -g_{m2} \cdot R_2 \cdot \left(1 - \frac{j\omega C_c}{g_{m2}} \right)$$

$$\downarrow f_z = \frac{g_{m2}}{2\pi C_c}$$

$$f_z = \frac{1}{2\pi r_{o1||r_{o2}} \cdot 10pF} \approx \underline{\underline{7.2k}}$$

$$f_z = \frac{g_m}{2\pi C_c} = \frac{1}{2\pi \cdot \frac{1}{g_m} \cdot C_c} = \underline{\underline{2.4MHz}}$$

pole $\rightarrow f_z$

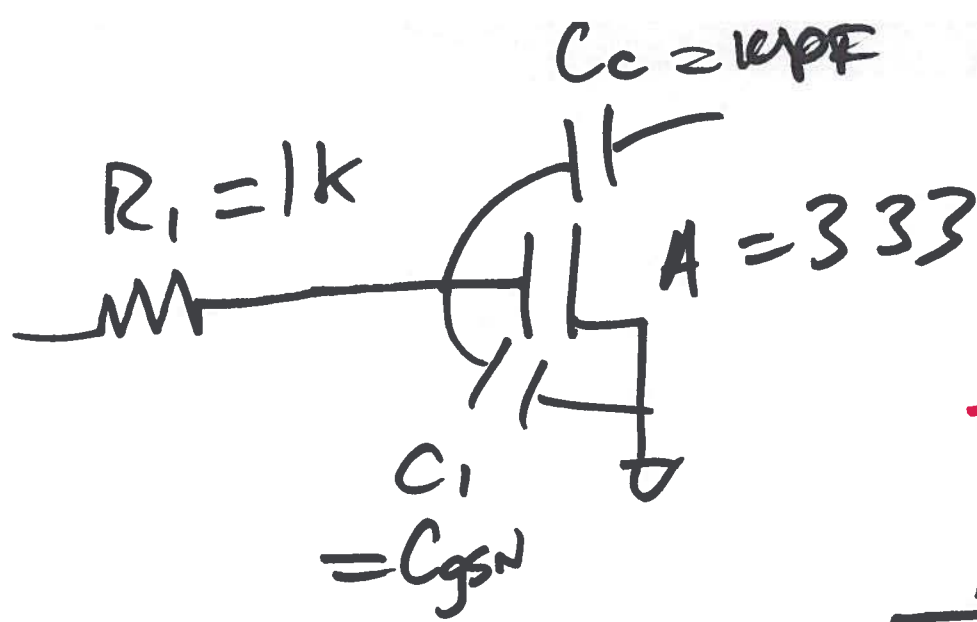

$$f_2 = \frac{1}{2\pi \cdot 6.5k \cdot 30pF}$$

$$= \frac{1}{16} \text{ MHz}$$

$$f_{3dB} = \frac{1}{2\pi \cdot 1k \cdot (23f + 333 \cdot 10pF)}$$

$$47kHz \approx \frac{15.9 \text{ MHz}}{333} \approx \frac{1}{2\pi \cdot 333 \cdot 10pF \cdot 10^3}$$

$$f_2 = \frac{1}{2\pi \cdot \frac{1}{g_m} \cdot (C_1 + \cancel{C_1 \cdot C_2} + C_2)}$$

$\frac{1}{g_m} = 21.66$
 $C_1 = 23f$
 $C_2 = 6pF$
 $\frac{1}{g_m} \cdot C_1 = 15f$

$$= \frac{100 \text{ MHz}}{2\pi \cdot 333}$$

$$= \frac{15.9 \text{ MHz}}{333}$$

6)