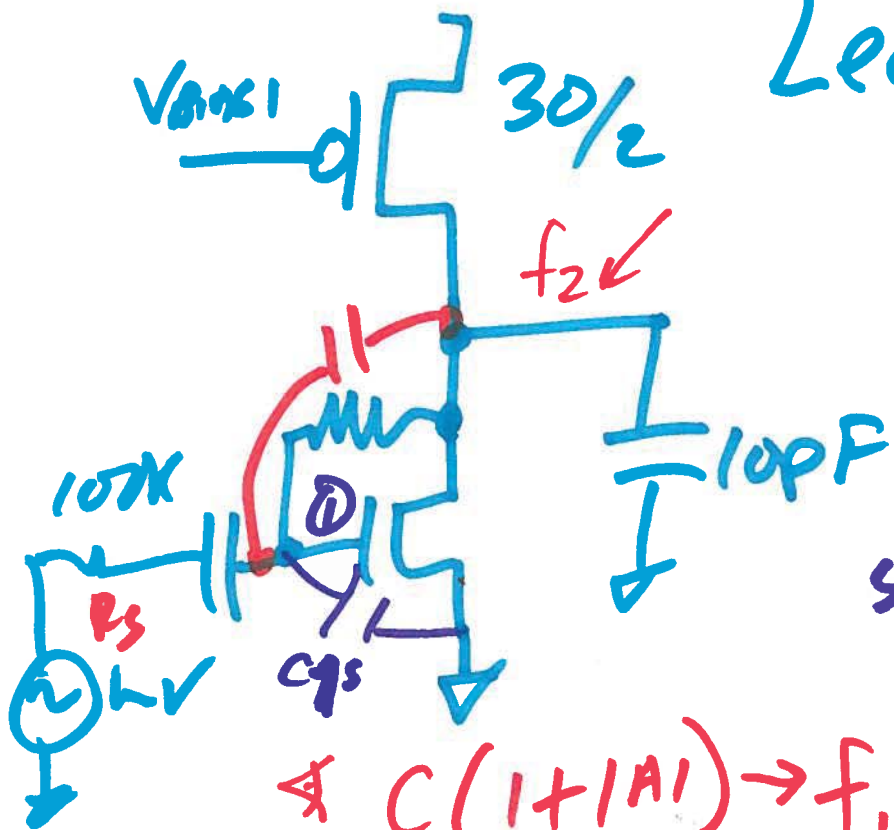


EE 420 / ELG 620

Analog IC Design

March 22, 2017

Lecture 17



~~$$f_i = \frac{1}{2\pi \cdot 100k (23.2fF + 1.8fF)}$$

$$= 25fF = C_{gd}$$

$$= 63MHz$$~~

input not pole splitting
 wrong! -5

$$C(1+|A|) \rightarrow f_i \approx \frac{1}{2\pi R_s C(1+|A|)}$$

2. parallel
 CMOSedu.com


11

$$f_{in} = \frac{1}{2\pi \cdot 100k (23.2ff + 2f(1 + \frac{33k}{33}))}$$

$$= \underline{\underline{2.4 MHz}} \quad 18 MHz$$

$$f_{out} = \frac{1}{2\pi \cdot \underbrace{1MEF \parallel 600k}_{300k} \cdot 10pF} = \underline{\underline{7.8 kHz}}$$

$$= \underline{\underline{375k}}$$

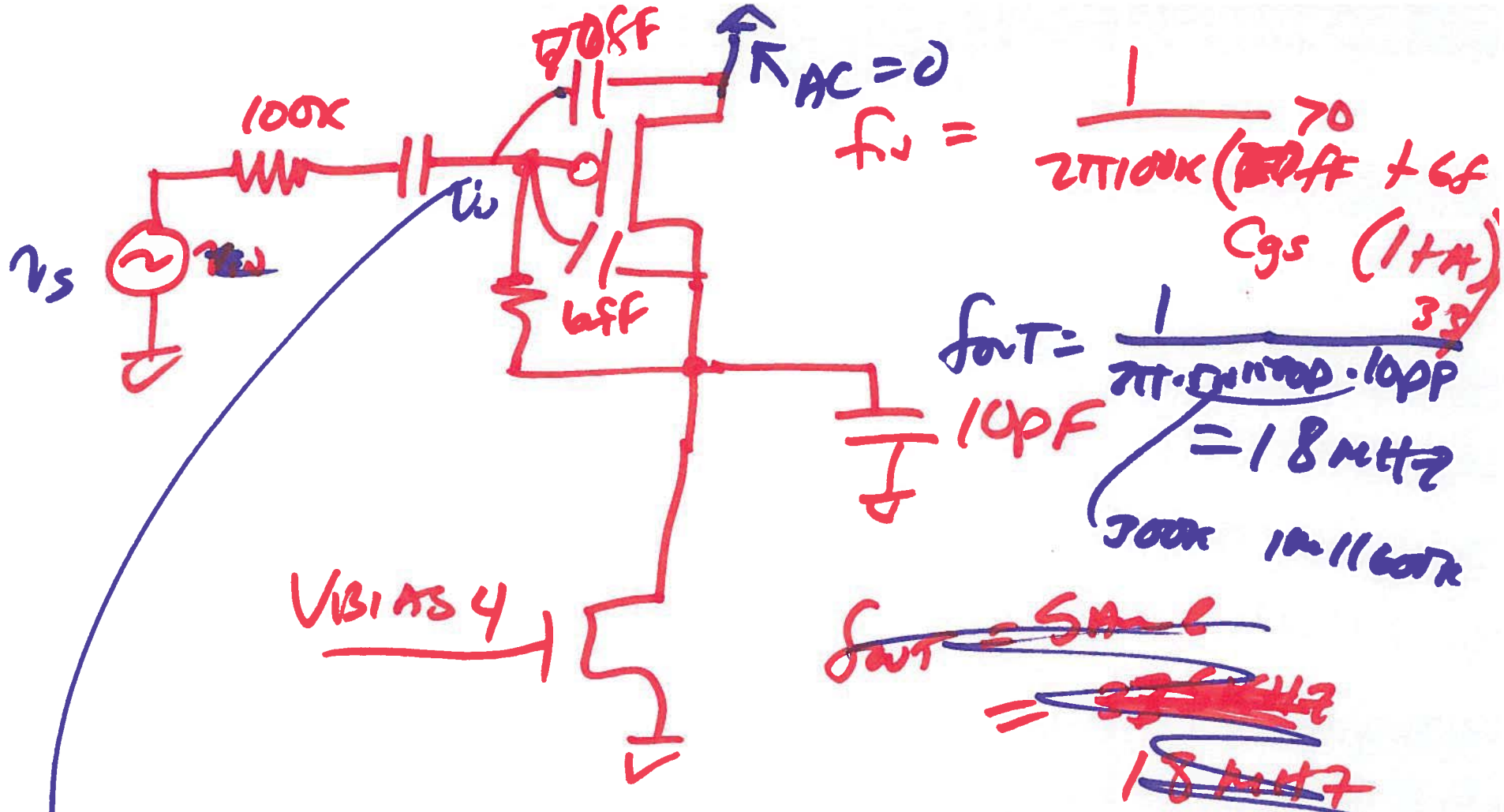

$$f_{in} = \frac{1}{2\pi \cdot 100k \cdot (70pF + 6pF(1+A))}$$

$$f_{out} = \frac{1}{\pi \cdot 300k \cdot 10pF} = 53kHz$$

$$f_{in} = \frac{1}{2\pi \cdot 100k \cdot (70pF + 6pF(1+A))} = 2.6MHz$$

$$f_{out} = \frac{1}{\pi \cdot 300k \cdot 10pF} = 53kHz$$

3)

$$f_{sw} = \frac{g_m}{2\pi \cdot 100f}$$

$$= \frac{1589}{2\pi \cdot 100} = 2.4 \text{ MHz}$$

AC=0



at high freq.

$$v_{out} = -g_m v_i \cdot \frac{1}{j\omega C_L}$$

$$\frac{v_{out}}{v_i} = \frac{-g_m}{j\omega C_L}$$

$$\left| \frac{v_{out}}{v_i} \right| = 1 = \frac{g_m}{2\pi f_{sw} C_L}$$

$$f_{sw} = \frac{g_m}{2\pi C_L}$$

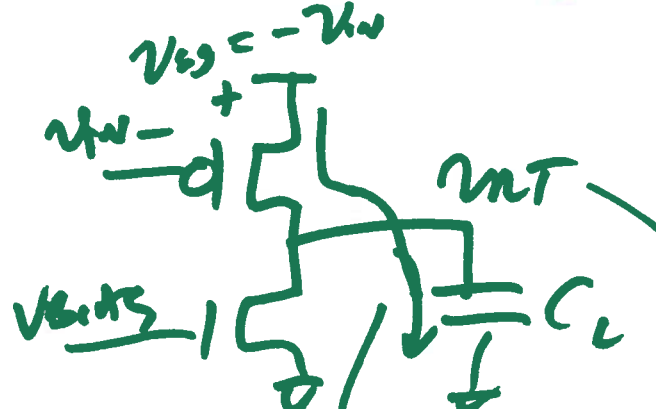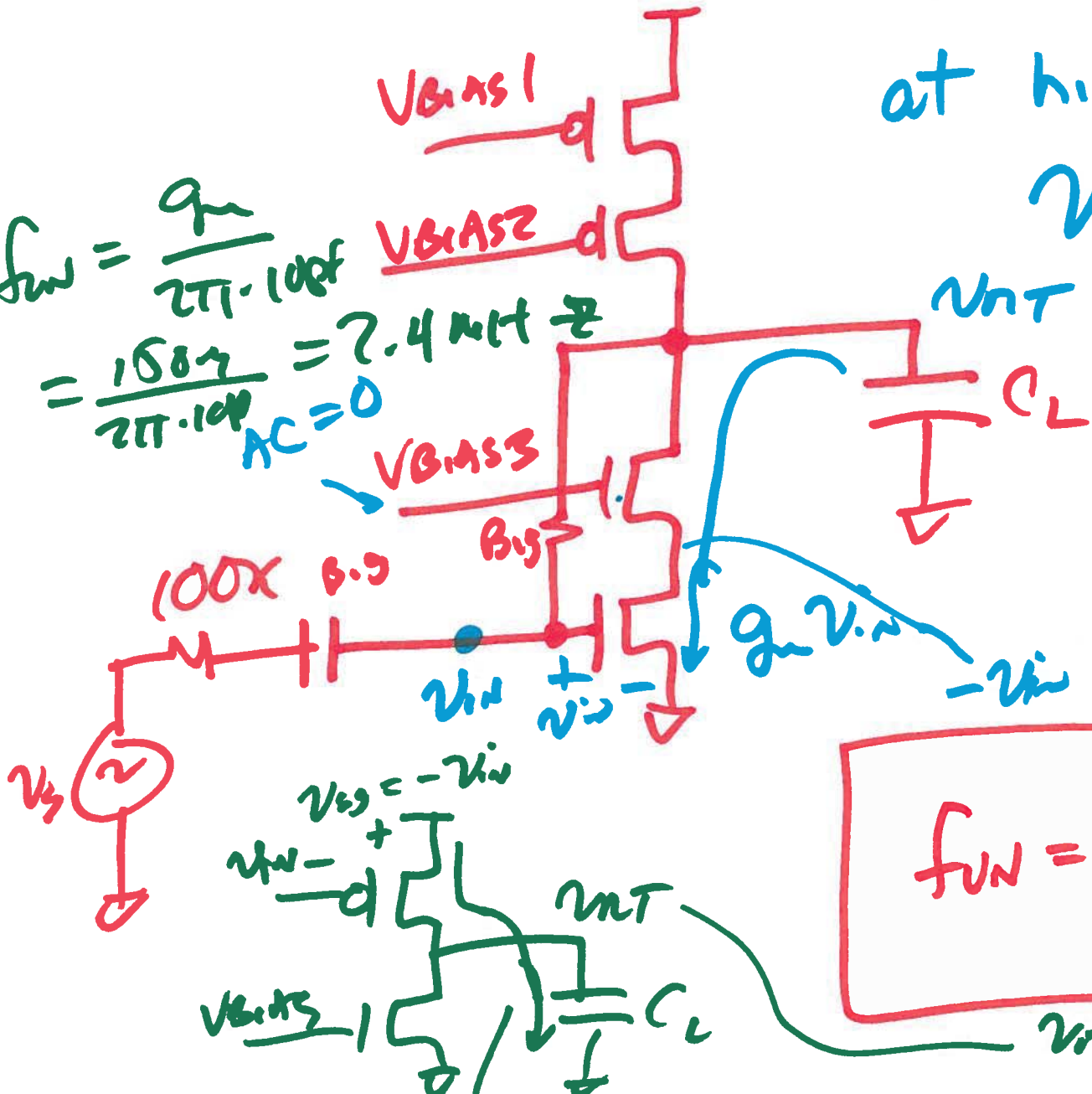

$$v_{out} = g_{mp}(-v_i) \cdot \frac{1}{j\omega C_L}$$

$$g_{mp} \cdot v_{sg} = g_{mp}(-v_i)$$

4)

$$f_{w1} = \frac{g_m}{2\pi C_L} = \frac{150 \mu}{2\pi \cdot 10p} = 2.4 \text{ MHz}$$

$$f_z = \frac{g_{m2}}{2\pi \cdot 10pF} = 2.7 \text{ MHz}$$



$$f_{NT} = \frac{1}{2\pi \cdot R_{out} \parallel R_{comp} \cdot 20pF}$$

$$f_{w2} = \frac{1}{2\pi \cdot 10^9 \cdot 20 \cdot 10^{-12}}$$

$$= \frac{1}{2\pi \cdot 20 \cdot 10^{-3}}$$

$$= \frac{0.159}{0.2} = 7 \text{ Hz}$$
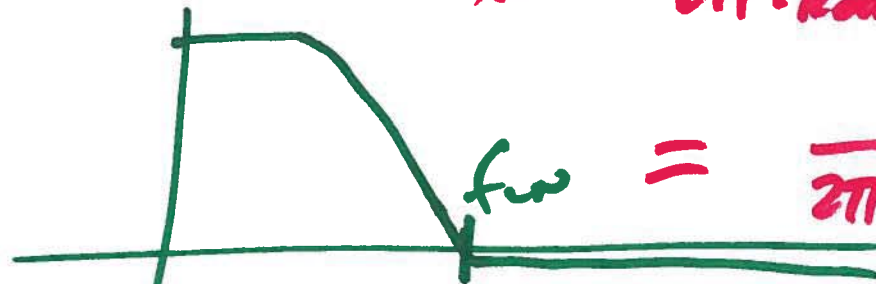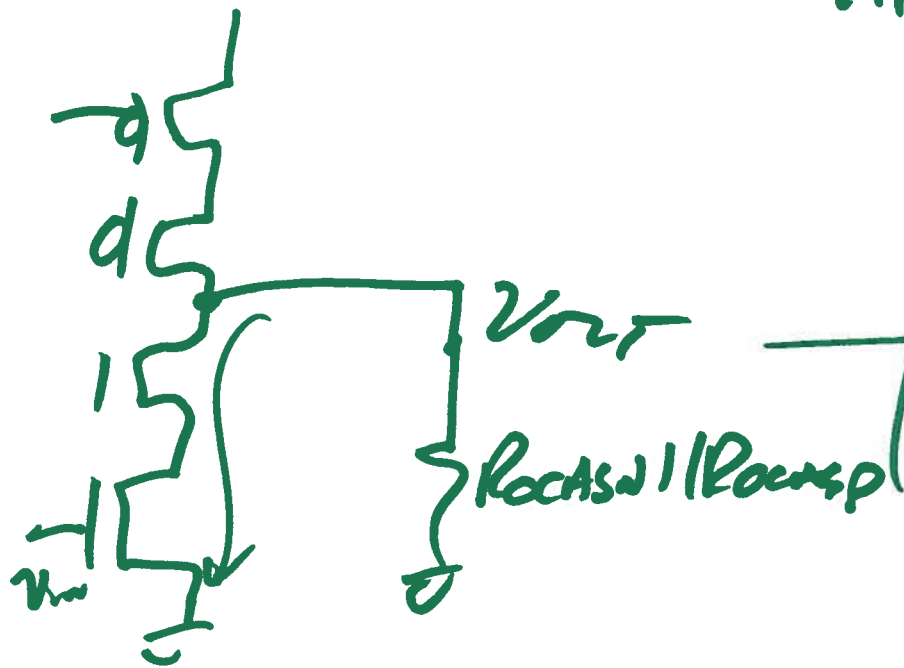
$$\frac{v_{NT}}{v_{in}} = -g_m \cdot R_{out} \parallel R_{comp}$$



$$21.65 \nearrow f_1 \approx \frac{1}{2\pi \cdot 1504 \cdot 16 \cdot 100k \cdot 10pF} = 1 \text{ Hz}$$

$$21.66 \searrow f_2 \approx \frac{1504}{2\pi (C_1 + C_1 + \frac{C_2}{10p})} = \frac{154}{2\pi 10p} = 2.4 \text{ kHz?}$$